

# EDN

Fast MOS static RAMs rival  
ECL devices' access times


Programming aids simplify  
code design and modification

Digitizing-tablet resolution  
extends beyond 1000 lpi

Electro preview

ELECTRONIC TECHNOLOGY FOR ENGINEERS AND ENGINEERING MANAGERS

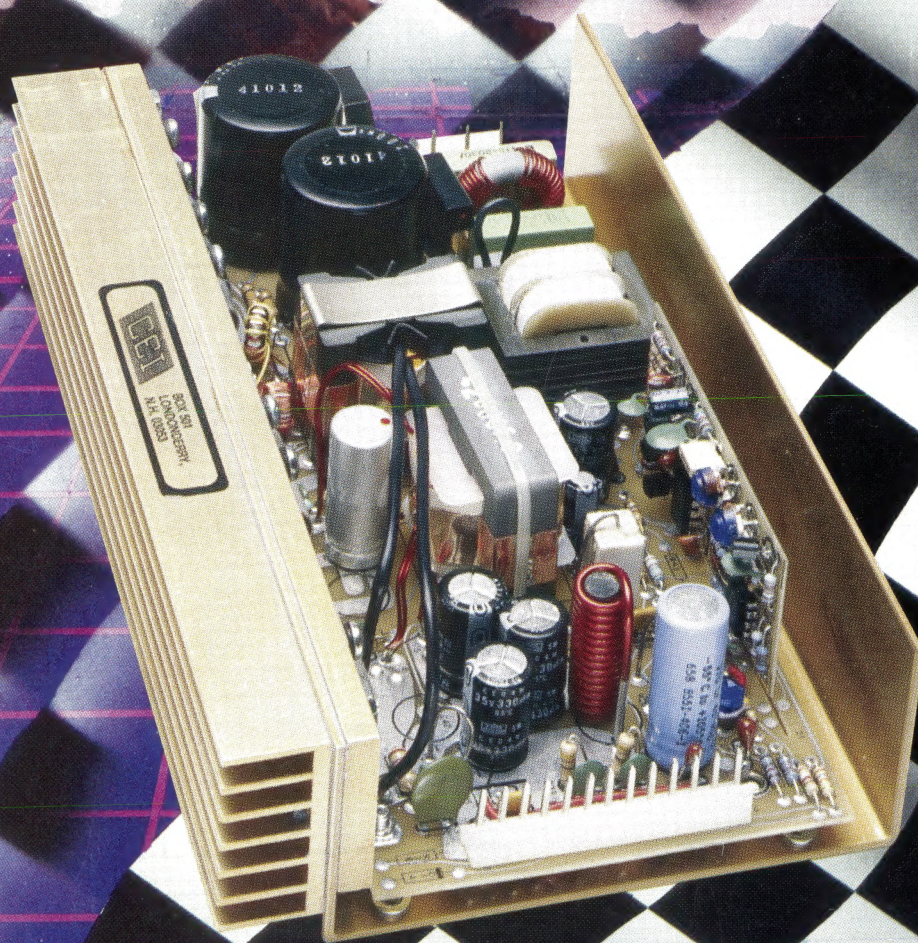High-frequency switching circuit  
winning power-supply





# stands alone.



error correction technique, the ICL7134 provides up to 14 bits of accuracy and ultra-high stability over the entire operating temperature range. Plus the same cool low-power CMOS performance.

Right now, we've got plenty of stock available. So once you see how easily the ICL7115 interfaces to your hardwired system and hooks up to 8- or 16-bit buses, you can spec the A/D chip that stands without peer.

Matter of fact, give us a call today and we'll put this super A/D converter in your hands. After all, we designed the ICL7115 for great engineers. Like you.

Call us for your free evaluation ICL7115, or write Intersil, Inc., Mail Stop R1-26, 10600 Ridgeview Court, Cupertino, CA 95014. In Europe, call (02) 673-93-79 or 660-20-14. Or write General Electric, International Operations, Chaussee de la Hulpe, 150-Bte. 5, 1170 Brussels, Belgium.

And discover—first hand—why GE stands for Great Engineering.



GE and  are registered trademarks of General Electric Company, U.S.A.

## Sample the future. Call 800-626-2001.

Ext. 428. Free evaluation ICL7115s are available to the first 3000 qualified callers.



# Our ICL7115

100011001010010100111010100100011001110011100011001011110010010  
0001100101001010011101010010001100111001110001100111000011100011  
100011001010010100111010100100011001110011100011001011110010010  
100011001010010100111010100100011001110011100011001110000111000  
100011001010010100111010100100011001110011100011001011110010010  
000110010100101001110101001000110011100111000110011100001110001  
100011001010010100111010100100011001110011100011001011110010010  
00011001010010100111010100100011001110011100011001011110010010  
100011001010010100111010100100011001110011100011001011110010010  
00011001010010100111010100100011001110011100011001011110010010  
100011001010010100111010100100011001110011100011001011110010010

INTERSIL  
ICL7115

The only 14-bit monolithic A/D converter on the market today—that's Intersil's ICL7115. It's the chip that will change the definition of signal processing.

Data acquisition and data logging applications are a whole new ball game with the ICL7115. It's monolithic, which means lower cost and higher reliability than systems built with hybrids or modules. And its successive approximation technique gives you 25,000 conversions per second, for more rapid sampling and greater digitizing capabilities.

The key to the ICL7115 is our proprietary

EPROM error correction technique. Unlike conventional techniques such as laser trimming, this unique EPROM correction method compensates for linearity and full-scale error with greater precision and stability, over the entire operating temperature range.

Though it's a hot new product, the ICL7115 is a very cool performer: thanks to our advanced CMOS technology, the whole package dissipates only 10mW.

And if your system requires equal precision in a D/A converter, our ICL7134 meets the challenge. Utilizing the same proprietary EPROM



**GE  
stands for  
Great  
Engineering  
in analog  
signal  
processing:**



# Measurement, Math, Memory and More.

What instrument is no bigger than a lunchbox, takes measurements like four high-performance multimeters, gathers data like a logger, and stores tens of thousands of readings?

Only one instrument is like that—Wavetek's new Model 52 Data Multimeter.

It measures DC voltage and current, AC voltage (to 1 MHz) and current, resistance, volt-amperes, dB, frequency, period, time interval and pulse width. And it accepts industry-standard thermocouples—J, K, E and T.

The data is shown in numeric and/or bar graph form on the large, high-resolution LCD. The display also helps with setup by providing complete menus for every function.

Four parallel, isolated A-D channels let the Model 52 do the work of four ordinary DMMs. Built-in computing functions calculate deltas, percentages, minimum/maximum readings and averages and detect alarm thresholds. You can even program your own math functions.

Model 52 is also a data logger. Add optional multiplexers and you can gather up to 252 channels of analog data and store the readings in nearly a megabyte of RAM. Digital I/O options add up to 32 bits of digital input and output as well as D/A capability for external control applications.






Internal batteries protect your data and provide total portability. Leave it on a mountaintop and gather data for months, or put it in a plane and take readings on the fly.

The Model 52 is easy to live with. You can transfer data to any computer's database at your convenience using the standard RS-232 or optional IEEE-488 interface. Unique Flex-Cal closed-box calibration saves your valuable time.

Surface-mounted devices and a custom gate array make it possible to offer all these features in such a compact package—and at prices beginning under \$3,000\*. Also available is the remote-only Model 51 for an even lower price.


For more information, call us at (619) 279-2200, or write Wavetek San Diego, Inc., 9045 Balboa Ave., P.O. Box 85265, San Diego, CA 92138. TWX 910-335-2007.

\*U.S. Prices only.

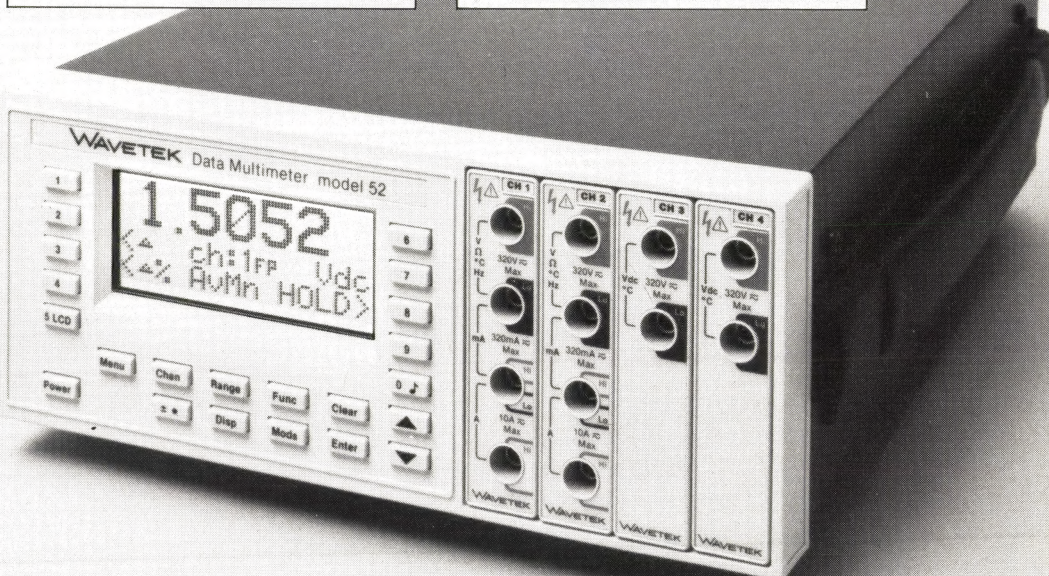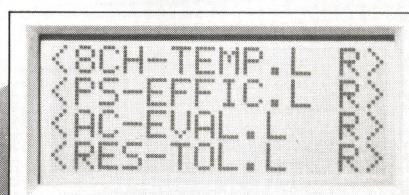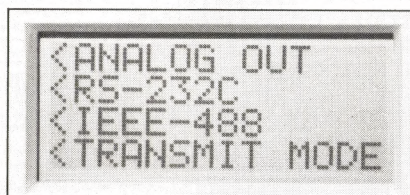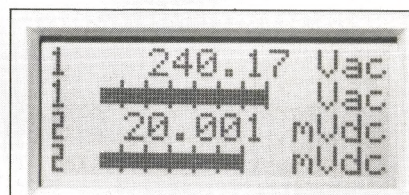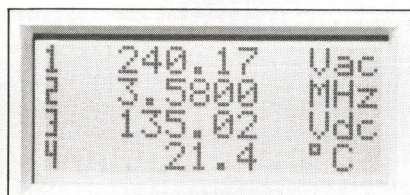



# PRO-LOG POWERS UP THE STD BUS.

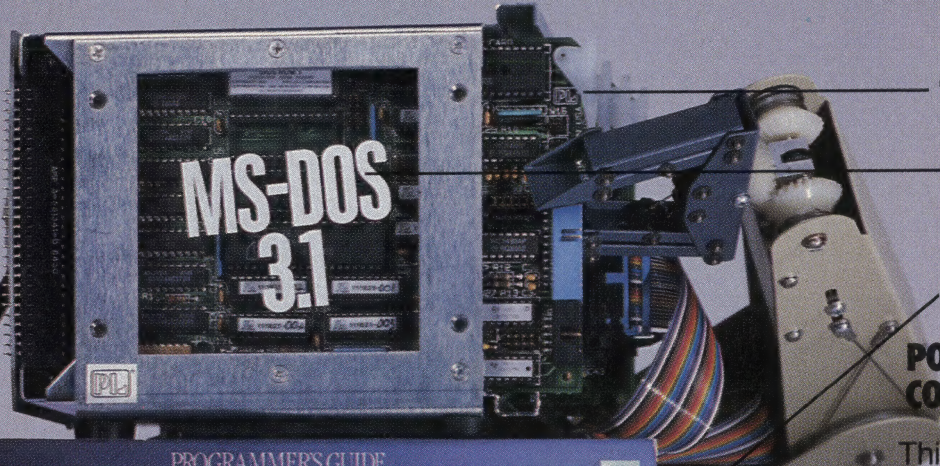

THESE STD BUS CARDS

+

THIS ROM-BASED  
OPERATING SYSTEM

+

ANY OF THESE TOOLS

=

**POWERFUL, CONVENIENT &  
COST-EFFECTIVE SOLUTIONS**

This formula can solve:  
robotics, data acquisition, test,  
measurement, process control  
applications, and more.

## WE PROVIDE THE CONSTANTS, STD DOS:

- 8088 CPU, 5 MHz
- MS-DOS® 3.1
- 384K Bytes RAM
- 128K-Byte ROM Disk
- 128K-Byte RAM Disk
- Two serial ports
- Full documentation
- PL-DOS utilities
- Prototype and OEM versions

## YOU CHOOSE THE VARIABLES:

- Additional STD Cards
- High-level languages
- Applications software

For more information, call  
(800) 538-9570 or (408) 372-  
4593 (inside CA) TODAY!

*MS-DOS® is a registered trademark of  
Microsoft Corporation.*

Pro-Log Corp., 2560 Garden Road, Monterey,  
CA 93940 (408) 372-4593, TLX: 171879  
Outside CA: (800) 538-9570; Australia (3) 836-  
3533; Germany (07131) 50030; Canada (416)  
625-7752; England (276) 26517; France (\*3)  
956-8142; Italy (2) 498-8031; Switzerland (01)  
62 44 44; China (852) 3-932706




**PRO-LOG®**  
CORPORATION

©1985 ADGroup International PL050

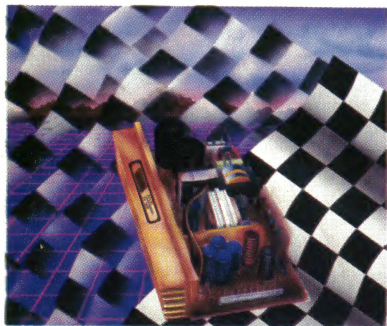Circle 50 for direct factory response    Circle 11 for literature only





*On the cover: You can stay out in front of the competition by designing high-frequency off-line switching power supplies into your products. Such supplies, which operate at frequencies greater than 50 kHz, are achieving high power densities while offering such features as inrush limiting, line filtering, and remote sensing. See pg 130. (Photo courtesy CEI Corp)*

## DESIGN FEATURES

### Special Report: High-frequency off-line switching power supplies 130

Today's faster switching circuitry allows manufacturers to build smaller off-line switching power supplies. The smaller the supply, however, the greater its potential for internal heating and safety problems. Manufacturers avoid these potential problems by employing innovative thermal designs and packaging methods.—*Chris Everett, Western Editor*

### Feed analog signals to IBM PC-compatible personal computers 153

A personal-computer-based data-acquisition system converts analog signals from low-level sensors—first, to a level an analog-I/O system can use, and second, to the digital ones and zeros the computer can use. Some guidelines can help you implement hardware and software solutions to the sometimes thorny interface problem.—*J Croteau, D Grant, and S Wurcer, Analog Devices Inc*

### PC-based programs aid analog-circuit design and analysis 175

You can use analog-circuit simulation software that runs on the IBM PC and compatible computers to analyze circuit designs. The programs, which augment (rather than replace) your circuit-design knowledge, let you analyze a circuit's ac and dc performance and conduct transient, Fourier, and Monte Carlo analyses.—*Richard E Kiefer, Consultant*

### EPLD macrocells and feedback signals ease circuit design 200

The AND arrays, programmable macrocells, and feedback paths of an erasable programmable-logic device augment your ability to design general-purpose logic circuits. Designs based on the device can perform their functions with fewer components than corresponding discrete-IC implementations.—*Don Faria, Altera Corp*

### Designer's Guide to: Linear control-system theory—Part 2 219


Advanced dynamic signal analyzers (DSAs) give designers a choice of techniques for measuring a system's open-loop frequency response. This article considers the effect of DSAs on the graphical measurement techniques of linear control-system theory.—*Steve Ashbjornsen and Owen Brown, Hewlett-Packard Co*

*Continued on page 7*

EDN (ISSN 0012-7515) is published 45 times a year, biweekly with one additional issue in January, February, March, August, and December, two additional issues in April, June, July, September, and November, and three additional issues in May and October by The Cahners Magazine Division of Reed Publishing USA, 275 Washington Street, Newton, MA 02158. William M Platt, President; Terrence M McDermott, Executive Vice President. Copyright 1986 by Reed Publishing USA, a division of Reed Holdings, Inc; Norman L Cahners, Honorary Chairman; Saul Goldweitz, Chairman; Ronald G Segel, President; Robert L Krakoff, Executive Vice President. Circulation records maintained at Cahners Publishing Co, 270 St Paul St, Denver, CO 80206. Second class postage paid at Denver, CO 80202 and additional mailing offices. Postmaster: Send address changes to EDN, 270 St Paul St, Denver, CO 80206.


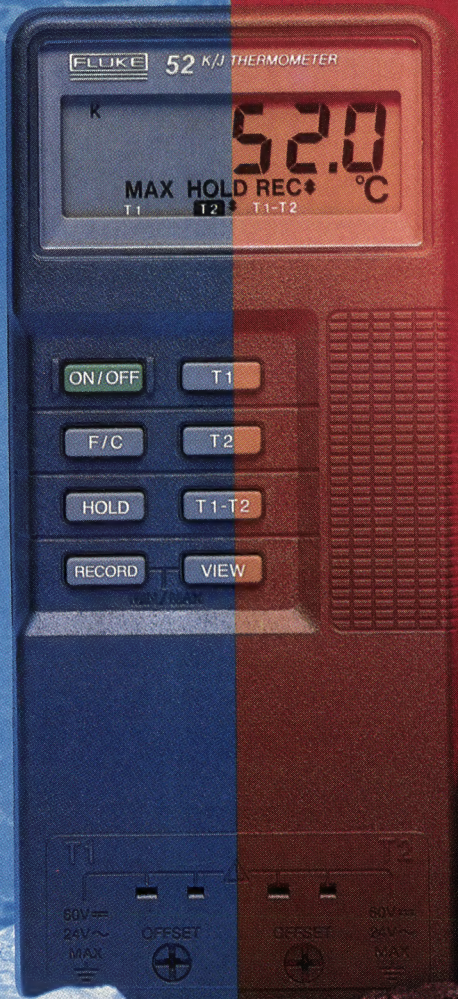
# Now scan and record temperatures from freezing to scorching.



## The new Fluke 52 goes to great extremes to outperform any other handheld thermometer.

With extra features, like our exclusive SCAN mode. Touch the button, and your Fluke 52 sequentially scans the readouts of two temperature inputs, and their difference.

Hit the RECORD button, walk away, and record the minimum and maximum from any one of these three channels for up to 1,200 hours. For troubleshooting intermittent problems, overnight monitoring, inlet/outlet servicing, and comparing trend information, it can't be beat.

If you don't need the scanning and recording features, you may prefer the single-point Fluke 51. Like the 52, it's easy to use, offers unsurpassed accuracy with resolution to 1/10th of a degree, and can use any K or J type thermocouple probe to fit your application.

Even the warranty goes to great extremes: three years on parts and service — the longest in the industry. And prices start as low as \$119.

But you don't have to go to extremes to get one.

Just contact your local supplier now for immediate delivery.

Or for more information, call toll-free **1-800-227-3800, Ext. 229**. From outside the U.S. call 1-402-496-1350, Ext. 229.

FROM THE WORLD LEADER IN  
HANDHELD TEST INSTRUMENTS.



**Fluke 51** Single Input

**Fluke 52** Dual Input

Measurement range: K-type: -200°C to +1370°C (-328°F to +2498°F)  
J-type: -200°C to +760°C (-328°F to +1400°F)

Accuracy: K-type is  $\pm(0.1\%$  of reading  $+0.7^\circ\text{C}$  or  $1.3^\circ\text{F}$ )  
J-type is  $\pm(0.1\%$  of reading  $+0.8^\circ\text{C}$  or  $1.4^\circ\text{F}$ )

°C or °F Selectable

Hold Mode

Scan, Differential, and Min/Max Recording Modes (52 only)

Standard mini-connector input

1200 hour 9V battery life


3-year warranty

General-purpose K-type bead probe included (two with 52).




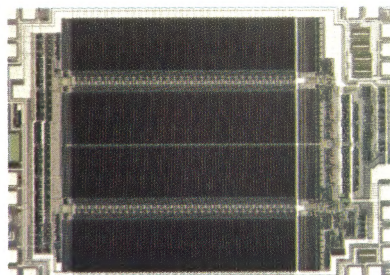IN THE U.S. AND NON-EUROPEAN COUNTRIES: John Fluke Mfg. Co., Inc., P.O. Box C9090, M/S 250C, Everett, WA 98206; Sales: (206) 356-5400; Other: (206) 347-6100.  
EUROPEAN HEADQUARTERS: Fluke (Holland) B.V., P.O. Box 2269, 5600 CG Eindhoven, The Netherlands, (040) 458045, TLX: 51846.  
© Copyright 1985 John Fluke Mfg. Co., Inc. All rights reserved. Ad No. 4701-50





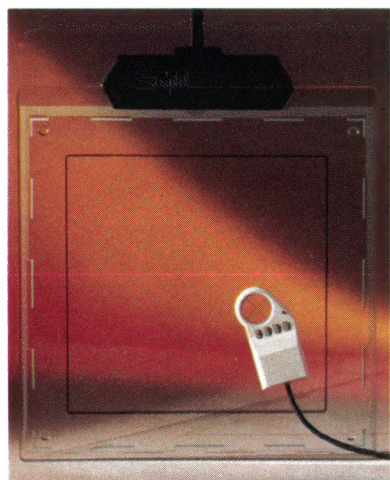You can now employ MOS static RAMs in applications once served only by 1k- or 4k-bit ECL memories. The 16k- and 64k-bit MOS devices are achieving access times as low as 25 to 35 nsec (pg 57).



Resolution, accuracy, and hardware and software compatibility are key specs to consider when choosing digitizing tablets (pg 69).

## TECHNOLOGY UPDATE

### Process improvements and special features reduce high-end static-RAM access times 57

Today's fast 16k- and 64k-bit MOS static RAMs have seen their access times fall to the 25- to 35-nsec range, approaching the speeds of ECL static RAMs.—*Maury Wright, Western Editor*

### Digitizing tablets offer choices of formats, operating modes, and pointers 69

Whether you're digitizing schematic diagrams or a 3-dimensional shape, you can choose from a variety of digitizing tablets, pointing devices, and output formats.—*Jon Titus, Senior Editor*

### Programming aids minimize errors during software design, coding, and modification 79

By employing one or more programming aids, you can make your computer handle much of the tedious work associated with program or software-system design.—*Chris Terry, Associate Editor*

### Varied Electro/86 program will emphasize IC- and system-design topics 97

The conference will include talks on the latest developments in semi-custom ICs, ASICs, logic arrays, VLSI circuits, and other subjects.—*Joanne Clay, Staff Editor*

## PRODUCT UPDATE

Networking products	107
Arbitrary-waveform synthesizer	109
Low-cost STE Bus-based development systems	110
Electrically erasable standard memory cells	112
Low-cost, PC-based LAN	114
Voltmeter with 8-bit digitizer	116
60W switching power supply	118

## DESIGN IDEAS


Dual one-shot forms frequency discriminator	241
Matched FETs provide balanced modulator	242
Lamps improve solenoid-driver efficiency	244
Switching supply is small and efficient	244
Square-root algorithm is fast and simple	246

Continued on page 9

Advertising and editorial offices: 275 Washington St, Newton, MA 02158. Phone (617) 964-3030. Subscription offices: 270 St Paul St, Denver, CO 80206. Phone (303) 388-4511. EDN is circulated without charge to those qualified. Subscription to others: Continental US \$90/year, \$5/copy; Canada and Mexico \$100/year, \$6/copy; Europe Air Mail \$125/year, \$7/copy; all others surface mail \$155/year; all other airmail \$175/year. Special issue prices may vary. Send requests for qualification forms and/or change of address to subscription office.  
© 1986 by Reed Publishing USA, Division of Reed Holdings, Inc. All rights reserved.



# Solartron Instruments

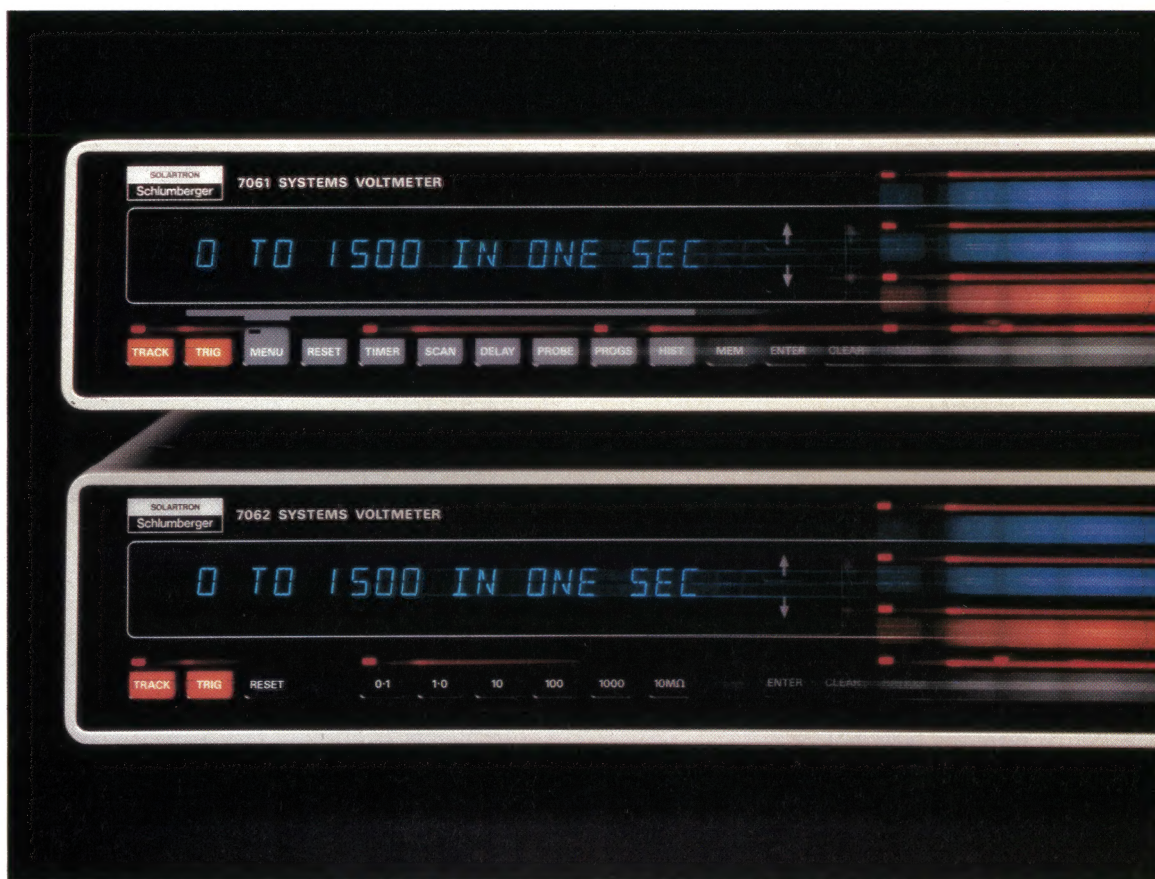

## DMMs on The ATE Fast Track

When speed is critical, Solartron's 7061 is the answer. Responding within 3 ms to an external trigger, the 7061 can output 300 readings per second on the IEEE-bus or signal an alarm condition within 1 ms. User-selected integration times provide 4-1/2 to 7-1/2 digit resolution.

An internal memory captures up to 8000 readings at a rate of 1500 readings per second, compares

them to a defined input level, and produces a before and after record of results. An extensive math and statistics package is available for data reduction. A scanner option provides 16 input channels in addition to the main and reference inputs. All 18 channels may be scanned in any sequence at a rate of 300 channels per second and independently set for any measurement function, scale length, and post-processing.

The 7062 provides identical superior performance and functions with a simplified front panel, for use under exclusive computer control.

- **Voltage:** dc and true rms ac
- **Current:** dc and ac
- **Resistance:** 2- and 4-wire
- **Temperature:** °C and °F
- **Ratio:** anything to anything

**See us at Electro, Booth 2111-2113**

Solartron Instruments, 2 Westchester Plaza, Elmsford, NY 10523  
Telephone (914) 592-9168,  
outside NY 1-800-CALL SOLARtron

SOLARTRON  
Schlumberger



**VP/Publisher**  
F Warren Dickson  
**VP/Editorial Director**  
Roy Forsberg

**Editor**  
Gary Legg

**Managing Editor**  
Rick Nelson

**Assistant Managing Editor**  
Joan Morrow

**Home Office Editorial Staff**  
275 Washington St, Newton, MA 02158  
(617) 964-3030

Tom Ormond, *Senior Editor*  
Jonathan Titus, *Senior Editor*  
Bill Travis, *Senior Editor*  
Deborah Asbrand, *Staff Editor*  
Joanne Clay, *Staff Editor*  
Tarlton Fleming, *Associate Editor*  
Eva Freeman, *Associate Editor*  
Clare Mansfield, *Staff Editor*  
Charles Small, *Associate Editor*  
David Smith, *Associate Editor*  
George Stubbs, *Staff Editor*  
Chris Terry, *Associate Editor*  
Valerie DeSalvo, *Assistant Editor*  
Helen McElwee, *Assistant Editor*  
Cynthia B Rettig, *Assistant Editor*  
Steven Paul, *Production Editor*

**Editorial Field Offices**  
Margery S Conner, *Western Editor*  
Newbury Park, CA: (805) 499-7901  
Denny Cormier, *Western Editor*  
San Jose, CA: (408) 296-0868  
Bob Cushman, *Special Features Editor*  
Port Washington, NY: (516) 944-6524  
Chris Everett, *Western Editor*  
San Jose, CA: (408) 296-0868  
Steven H Leibson, *Southwestern Editor*  
Boulder, CO: (303) 494-2233

J D Mosley, *Texas Editor*  
Arlington, TX: (817) 465-4961  
Maury Wright, *Western Editor*  
San Diego, CA: (619) 748-6785  
Peter Harold, *European Editor*  
0603-630782  
(St Francis House, Queens Rd,  
Norwich, Norfolk NR1 3PN, UK)

**Contributing Editors**  
Robert Pease, Bob Peterson, Don Powers

**Editorial Services**  
Kathy Leonard, *Office Manager*  
Laureen Ouellette, Darlene Thomas,  
Nancy Weiland

**Art Staff**  
Susan Barrow-Williams, *Director*  
Kathleen Ruhl, *Assistant Director*  
Roseanne D Coveney, *Illustrator*  
Chin-Soo Chung, *Illustrator*  
Debi Queally, *Illustrator*

**Production/Manufacturing Staff**  
William Tomaselli, *Production Supervisor*  
Donna Pono, *Production Manager*  
Patricia Hadidian, *Production Assistant*  
Elizabeth Wojciechowicz, *Production Assistant*  
Diane Malone, *Composition*

**Graphics Director**  
Norman Graf

**VP/Production/Manufacturing**  
Wayne Hultitzky

**Director of Production/Manufacturing**  
John R Sanders

**VP/Research**  
Ira Siegel

**Marketing Communications**  
Deborah Virtue, *Manager*  
Jennifer Ware, *Promotion Manager*  
Corie Rand, *Promotion Coordinator*  
Susan Odell, *Promotion Assistant*

## EDITORIAL

51

You're likely to be unsettled, as we are, to note the harmful methods a few ads still employ to get a reader's attention. The arguments frequently used to justify such ads all have serious flaws.

## NEW PRODUCTS

Computer-Aided Engineering .....	259
Computers & Peripherals .....	267
Components & Packaging .....	278
ICs & Semiconductors .....	289
Computer-System Subassemblies .....	301
International .....	313
Instrumentation & Power Sources .....	324
Software .....	335

## PROFESSIONAL ISSUES

Employees find their pension benefits often add up to unkept promises .....	367
---	-----

## LOOKING AHEAD

379

Monolithic units swell data-converter market . . . Portable data recorders: programmability the key.

## DEPARTMENTS

News Breaks .....	19
News Breaks International .....	22
Signals & Noise .....	31
Calendar .....	40
Leadtime Index .....	124
Literature .....	353
Market Forecast .....	360
New Books .....	362
Career Opportunities .....	371
Business/Corporate Staff .....	376
Advertisers Index .....	377



▽BPA ABP

**Cahners Publishing Company** □ Publishers of specialized business publications in Building & Construction □ Electronics & Computers □ Foodservice □ Manufacturing □ Medical/Health Care □



WE COULD HAVE  
CALLED IT A  
32-BIT  
MICROPROCESSOR.

WE COULD HAVE  
CALLED IT A  
10-MIP  
COMPUTING ELEMENT.

WE COULD HAVE  
CALLED IT THE FIRST  
CONCURRENT  
SOLUTION.

INSTEAD  
WE CALL IT THE  
TRANSPUTER.



INMOS introduces the transputer family. A range of evaluation boards for the first transputers is available now.

The transputer is a fast, easy to use VLSI component designed for applications ranging from single microprocessor systems to supercomputers.

The IMS T414 is the first transputer, integrating a 32 bit microprocessor, four inter-transputer communication links, 2 Kbytes of RAM, a 32 bit memory interface and a memory controller onto a CMOS chip.

The microprocessor runs at 10 MIPS and is designed specifically for the execution of high level languages. It combines direct support for multi-tasking, floating point, block transfer and record handling with sub-microsecond procedure call and task switching.

Each transputer link provides a full duplex, 10 Mbits/sec, point to point connection with an on chip DMA controller. Links are used for inter-transputer communication or, via an INMOS Link Adaptor, interfacing to industry standard byte wide peripherals.

The memory interface provides access to a linear 4 Gbyte address space at a data transfer rate of up to 25 Mbytes/sec.

Transputers are designed for ease of engineering. All transputer family devices operate from a single 5 MHz clock input, which is used to derive high speed internal clocks for all on chip systems.

When transputers are directly connected via links, additional components are not necessary. Independent or common clocking can be used, regardless of timing skew.

The configurable memory controller also requires no external components. It provides all

the necessary timing and refresh signals for memory systems, comprising any mix of ROM, SRAM, DRAM and memory mapped peripherals.

Transputers are designed for ease of programming. INMOS offers development systems which provide integrated editing, compiling and source level debugging for both single and multiple transputer applications, using C, Pascal, Fortran and occam.

In applications requiring only a single computing element, the transputer's speed, minimal support component requirements and programming efficiency provide significant cost/performance advantages over conventional microprocessors.

Systems of any size can be built from inter-connected transputers, using the links. The same program can be configured to run on one, tens or thousands of transputers allowing a simple trade off between performance and cost.

The transputer family already includes 32 bit and 16 bit transputers, peripheral controllers, evaluation boards and development tools. Start assessing its capability for yourself now with an IMS T414 evaluation board.

INMOS Corporation, P.O. Box 16000, Colorado Springs, Colorado 80935, USA. Tel: (303) 630-4000. Tx: (910) 920-4904

INMOS Limited, Whitefriars, Lewins Mead, Bristol, U.K. BS1 2NP. Tel: 0272 290861 Tx: 444723.

INMOS GmbH, Danziger Strasse 2, 8057 Eching, West Germany. Tel: 089 319 10 28. Tx: 522645.

INMOS Sarl, Immeuble Monaco, 7 Rue Le Corbusier, Silic 219, 94518 Rungis Cedex, France. Tel: (1) 687 22 01. Tx: 201 222.

#### TRANSPUTER PRODUCTS

<b>IMS T414</b>	<b>32 Bit, 2 Kbyte RAM, 4 Transputer links</b>
<b>IMS T212</b>	<b>16 Bit, 2 Kbyte RAM, 4 Transputer links</b>
IMS C001	Transputer Link Adaptor, Separate 8-Bit input and output
IMS C002	Transputer Link Adaptor, Multiplexed 8-Bit input/output

#### DEVELOPMENT TOOLS

IMS D100	INMOS Transputer Development System
IMS D600	Transputer Development Software, VAX-VMS
IMS D700	Transputer Development Software, IBM-PC

#### EVALUATION BOARDS

IMS B001	Double Eurocard, IMS T414, 64 Kbyte RAM, 2 x RS232C ports
IMS B002	Double Eurocard, IMS T414, 2 Mbyte RAM, 2 x RS232C ports
IMS B004	IBM-PC add on card, IMS T414, 1 Mbyte RAM

inmos ● IMS and occam are trademarks of the INMOS Group of Companies.

For a complete data pack on the Transputer and its support products, fill in the response coupon, and post to INMOS Corporation P.O. Box 16000 Colorado Springs, Colorado 80935, USA. For faster response, call (303) 630-4000

EDN041786

Name \_\_\_\_\_

Title \_\_\_\_\_

Company \_\_\_\_\_

Street/PO address \_\_\_\_\_

City/State/Zip \_\_\_\_\_

Country \_\_\_\_\_

Telephone \_\_\_\_\_

☐ Please send Transputer data pack

☐ Please have a salesman call

☐ I am interested in ordering an Evaluation Board



inmos®

**TRANSPUTER FAMILY**





# A new force in power semiconductors.



There's a new name in power semiconductors.  
POWEREX, Inc.

It's a joining of forces that overnight has created a new leader in the power semiconductor industry.

POWEREX is a joint venture corporation of Westinghouse, General Electric, and Mitsubishi Electric America. It combines their experience . . . their people . . . their facilities . . . their traditions of quality and reliability.

And, of course, their products . . . a broad, growing line of power semiconductors, including rectifiers, thyristors, bipolar power transistors, triacs, isolated power modules, and assemblies.

POWEREX brings a commitment to the industry to set new standards of excellence in products and service. Look for new energy in product development and application support. New





products with higher switching speeds and improved efficiency. Faster responses to your delivery requirements through better inventory utilization and manufacturing processes.

POWEREX is a powerful synergy of people, technologies, and resources . . . a new force in power semiconductors.

For full information, write POWEREX, Inc., Hillis Street, Youngwood, PA 15697. Or call POWEREX headquarters at (412) 925-7272.


**POWEREX**

Joint Venture Corporation of Westinghouse, General Electric, and Mitsubishi.


CIRCLE NO 103



# Introducing four positively

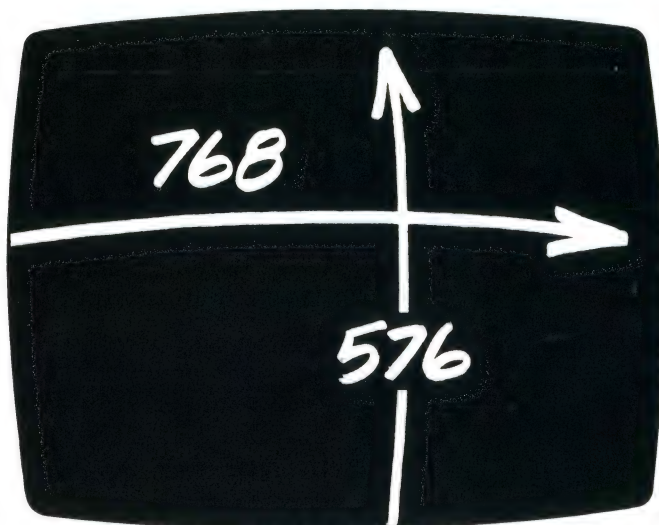

PERSONAL COMPUTER GRAPHICS

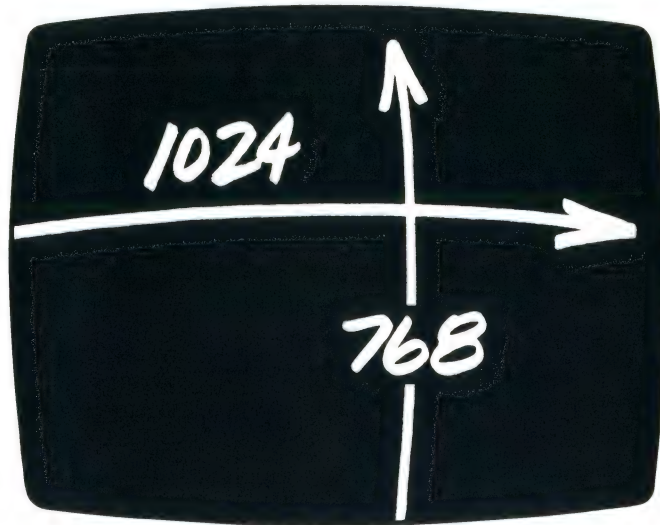



2-D ENGINEERING WORKSTATIONS

**Our new family of RAMDACs is bound to make a Brooktree convert out of you.**

Who gives a duck's tail about RAMDACs, anyway?

Apparently, none of our competitors. None has chosen to produce more than one RAMDAC. None, we believe, has taken the time or effort to design even *one* RAMDAC the right way. The Brooktree Way.

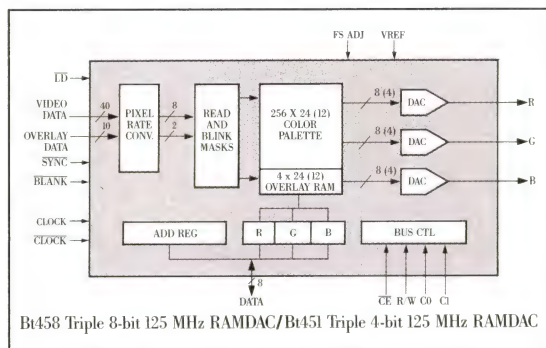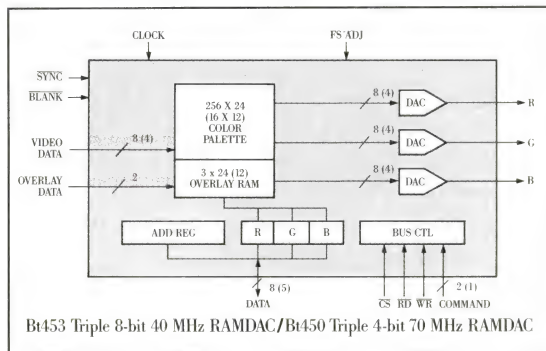We, on the other hand are now introducing four new RAMDACs—high performance D-to-A circuits with built-in color palettes. They make it easier than ever for you to achieve your new year's resolutions, no matter what type of graphics system you're designing. And they all take advantage of our revolutionary low-glitch architecture.



**Ask about our Sidecar RAM™**


Here's a vivid example of our commitment to elegant design: Each of our four new RAMDACs includes two overlay ports that address a separate color palette. This makes cursors, menus, alphanumeric overlays, etc. easier to handle.

Because this Sidecar RAM, as we call it, stores the colors for these overlay options, all the colors in the color palette RAM can be used to display rendered images.

**Ask about our**

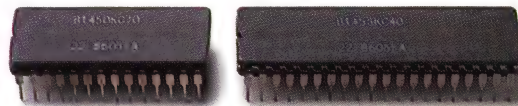
**Triple 4-bit RAMDAC.**

Our Bt450 is a 70 MHz, 16-color palette, Triple 4-bit






# revolutionary RAMDACs.

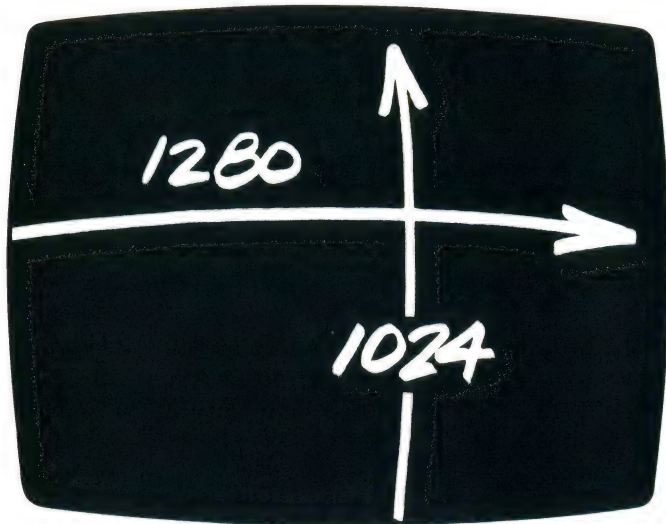

HIGH RESOLUTION ENGINEERING WORKSTATIONS

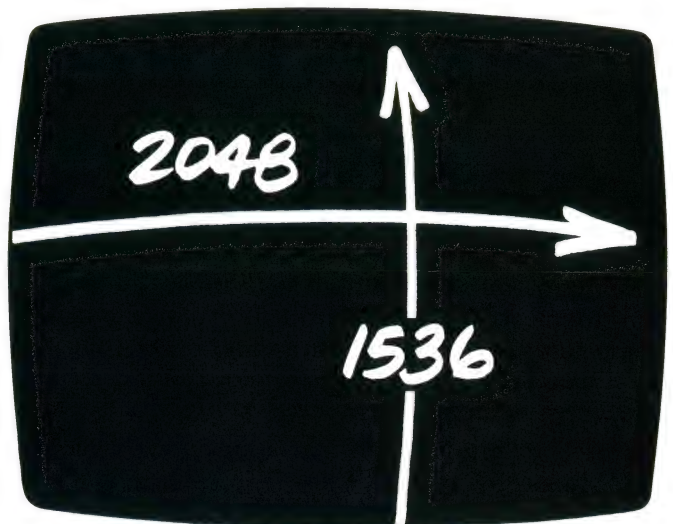

ULTRA-HIGH RESOLUTION WORKSTATIONS

RAMDAC—in a single monolithic CMOS chip.

Compare it to the TMS34070. It has a voltage output. Ours has an adjustable current output that drives doubly-terminated 75-ohm coax directly. Their part doesn't.

Our color palette is fully dual ported. Not theirs.

Ours is RS-343-A compatible, including SYNC tip and blanking pedestal. Theirs isn't.

Most important, the Bt450's overlay RAM and separate MPU port makes your design job a lot easier.

## Ask about our Triple 8-bit RAMDAC.

Our Bt453 is a 40 MHz, 256-color palette, Triple 8-bit RAMDAC—also in a single monolithic CMOS chip.

Frankly, it's not even fair to compare it to the MSG170. It's six bits. Ours is eight.

So only Brooktree can give you, simultaneously, 256 colors out of a 16.8 million-color palette. That means you can do solids modeling without color compromise.

## Who can you ask about our 125 MHz RAMDACs?

It's tough not having direct competition. Nobody to blow out of the water.

Our Bt451 is a 125 MHz 256-color palette,

Triple 4-bit RAMDAC. The Bt458 is a pin-compatible 8-bit version. Also 125 MHz. Both TTL-compatible. Not ECL.

And because they're pin compatible, you can design one system that can be switched from 4-bit to 8-bit DAC resolution by exchanging just one chip.

Just look at these features: On-chip 4:1 and 5:1 Pixel Rate Converter, direct interface to frame buffer RAM, separate MPU interface, blink/blank registers and fully dual-ported RAM cells.


Gee, do you think we should build a 250 MHz version, too?

## Now, ask for more information.

We've told you a lot about our new RAMDACs. But far from the whole story. For samples, call the Brooktree representative nearest you. His

responsiveness will absolutely amaze you.

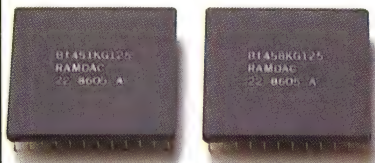
Brooktree Corporation,  
9950 Barnes Canyon Rd.,  
San Diego, CA 92121.  
1/800/VIDEO IC  
TLX 383 596



Brooktree™


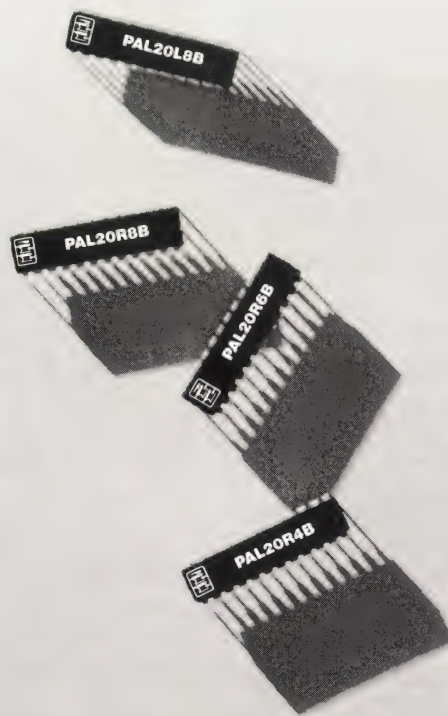
# The difference between our 15ns, 24-pin PAL<sup>®</sup> ICs and theirs.



**Ours.**



If you need production quantities of 15ns, 24-pin PAL® ICs, there's only one name worth knowing.

Monolithic Memories.

Our PAL 24B Series is available right now. It's pin-for-pin compatible with our PAL 24A Series, only 40% faster. And supported by PALASM® CAD software.

Here are the part numbers. PAL20L8B, PAL20R8B, PAL20R6B and PAL20R4B.

And here are the specs. Maximum propagation delay, 15ns. Maximum current drain, 210mA. All in a 300 mil SKINNYDIP® package.

The PAL 24B Series.

There's really nothing else to compare it to. Unless you count the 10ns series we'll be introducing soon.

For datasheets and samples, call us at (800) 247-6527, ext. 6005.

Or write Monolithic Memories, 2151 Mission College Blvd., Santa Clara, CA 95054.

PAL, PALASM and SKINNYDIP are registered trademarks of Monolithic Memories, Inc. © 1986, Monolithic Memories, Inc.

**Monolithic Memories** 

**Theirs.**



The ZZZ . . . ZL30 [ZL32]  
Logic Programmer  
A development tool  
A High—Speed Production system for PALs\* and IFLs



The ZL30 [ZL32] will give you the best of all worlds. A multi—functional, totally sophisticated tool designed with your needs firmly in mind **and already acknowledged as the “industry standard”.**

Now you can have flexibility and speed in one high—speed production/development system.

The ZL30 in conjunction with CUPL\* software, plus a PC makes the most powerful workstation for PALs\* and IFLs. In fact the **ZL30 is such a powerful combination that cloned lookalikes are inevitable. Don't be fobbed**

**off with pale imitations.**

Remember, there's only one Stag and there's certainly only one ZL30.

- Complete Stand—alone.
- Will program most 20, 24 and 28 pin PAL\*, EPLD and IFL.
- Includes Altera 40 pin EPLD. ■ RS232C, IEEE—488 Interfaces, plus parallel handler interface. ■ Durable, function, Edit keyboard.

- Green Alphanumeric Display
- Comprehensive Device Library
- Remote Control Option as standard. ■ Carries out customer vector tests, product performance checks as well as a continuity check on the sockets. ■ Ultra high speed — to a degree that would make other manufacturers envious.
- An extremely low cost.

***Start Buzzing — Call Stag today.***



\*CUPL — Assisted Technology.  
 \*PAL — Monolithic Memories Inc.



# NEWS BREAKS

EDITED BY JOAN MORROW

## **RAD-HARD 16k-BIT STATIC RAM MADE WITH CMOS PROCESS**

Boasting the greatest radiation hardness of any commercial CMOS memory, the HS-65262RH (16k-bit) static RAM from Harris Corp (Melbourne, FL, (305) 724-7800) resists latch-up from transient ambient radiation in excess of  $2 \times 10^{12}$  rads(Si)/sec. It withstands a total radiation dose of at least 200,000 rads(Si). Functionally compatible with Sandia's SA-3240 and Harris's HM-65262, the HS-65262RH delivers typical access times of 100 nsec over  $-55$  to  $+125^\circ\text{C}$  and operates asynchronously at supply currents of only 6 mA/MHz max from a 5V source. In its low-power standby mode, the part draws less than 200  $\mu\text{A}$ . Samples of the device are supplied in a 20-pin cerdip for \$1000 (100) for the Class-B version or \$1395 (100) for the Class-S version.—Denny Cormier

## **DUAL-PORT VIDEO-MEMORY TESTER TESTS AT 50 MHz**

The J937 Memory Test System from Teradyne (Canoga Park, CA) can test video RAMs at a system frequency of 50 MHz unrestricted and 100 MHz double-clocked. It has an accuracy of better than 1 nsec and capacitive loading of 30 pF. Because the system can test all parameters to spec, you can also use it for parts characterization and evaluation. Prices start at \$350,000.—Margery S Conner

## **MOTOROLA EXPECTS TO ENTER DSP MARKET IN THE THIRD QUARTER**

Motorola's Microprocessor Products Group (Austin, TX, (512) 440-2039) expects to join the growing ranks of DSP-chip suppliers in the third quarter. The company's first dedicated DSP product, the DSP56200, will provide either a dual- or single-channel finite-impulse-response (FIR) filter. When operating in its dual-channel mode, the chip will let you select as many as 128 taps per filter section. In the single-channel mode, as many as 256 taps will be available. Unused filter taps will provide general-purpose data storage in addition to the chip's 512 internal RAM locations for temporary data and filter coefficients. The manufacturer projects a price of less than \$25 per chip (1000).—Jon Titus

## **SEEQ UNVEILS INDUSTRY'S FIRST CMOS 256k-BIT EEPROM**

Last month, Seeq Technology (San Jose, CA, (408) 942-1990) introduced the 28C256, the first 256k-bit (32k-byte) EEPROM made in CMOS. By applying its low-power CMOS 1.25- $\mu\text{m}$  fabrication technology, Seeq has kept the part's active supply current to 60 mA from one 5V source; in standby mode, the 28C256 draws only 100  $\mu\text{A}$ . The company's high-endurance Q-cell design allows the 28C256 to support as many as 1,000,000 write/erase cycles with an average write time of 160  $\mu\text{sec}$  per byte during the part's 64-byte page-write mode; maximum read access time is 250 nsec. Other features include bulk chip erase, an on-chip timer, data polling, and power-up/-down protection. The 28C256 sells for \$195 (100).—Denny Cormier

## **CMOS CHIPS SHRINK PC/AT SINGLE-BOARD COMPUTER SIZE**

Two CPU/peripheral controller ICs used in Faraday Electronics' (Sunnyvale, CA) single-board computer line are offered for OEMs building PC and PC/AT bus-based systems. The FE3000 is compatible with Intel's 16-bit 80286 and is upward compatible with the 80386. The chip integrates 53 components and shrinks board size by 62%. It supports 6-, 8-, and 10-MHz clock speeds with zero wait states and can accommodate 256k- and 1M-bit dynamic RAMs. The chip incorporates nonmaskable-interrupt and DMA refresh-control logic, an 82288-compatible bus controller, and an 8284/82284-compatible clock generator.



# NEWS BREAKS

---

Faraday also offers the FE2010, capable of reducing an 8088-based PC mother board by 77%. Both devices work in conjunction with the company's PROM-based BIOS. The chips come in 84-pin J-leaded surface-mount plastic chip carriers. The FE2010 is priced at \$76, and the FE3000 sells for \$45 (100).—Margery S Conner

## **TWO COMPANIES INTRODUCE HIGH-SPEED CMOS GLUE LOGIC**

Despite the general slowdown in the TTL glue-logic market last year, two companies have introduced high-speed (greater than 50 MHz) CMOS versions of the widely used 54/74 Series logic devices. Parts from both companies satisfy MIL-STD-883.

Using its 1.2- $\mu$ m CEMOS process, Integrated Device Technology (Santa Clara, CA, (408) 727-6116) has started its 39C800 glue-logic line with three 9-bit noninverting devices: the IDT-39C823 bus interface register, the -39C843 bus interface latch, and the 39C863 bus transceiver. All three IDT parts cost \$5.90 (100).

VTC Inc (Bloomington, MN, (800) 882-2667), which released the first 20 of its 50 high-speed 1.6- $\mu$ m CMOS V54/74 ACT glue-logic devices late last year, including 8-, 9-, and 10-bit buffers, latches, flip-flops, and transceivers in 20- and 24-pin DIPs, is now offering all 50 parts in sample quantities for \$3.25 (100). In addition to improved noise margins over conventional TTL glue-logic devices, inputs to VTC's ACT parts can withstand 2000V of ESD.—Denny Cormier

## **CHIP MULTIPLIES TWO 16-BIT INTEGERS IN 5 nSEC**

Having a typical 5-nsec multiply time, the B3018 chip from Bipolar Integrated Technology Inc (Beaverton, OR, (503) 629-5490) operates on 16-bit words. An external connection lets you select a signed or an unsigned format for either integer or fractional values. The chip provides its 32-bit result in parallel; however, internal control circuits let you access the most-significant and least-significant words individually. You can force the chip to round or adjust the format of the multiplier's result. The chip's overflow, zero-status, and negative-sign flags are held in an internal status latch and are available separately on three output pins. The manufacturer expects to offer samples of the multiplier in a 108-pin PGA package in June for \$200 and \$300 per chip.—Jon Titus

## **FERROELECTRIC MEMORY CELLS PROMISE FAST, NONVOLATILE RAMs**

Ramtron (Colorado Springs, CO, (303) 594-4455) has developed a potassium-nitrate ( $K_2NO_3$ ) thin-film cell. The company is sampling a 1k-bit, undecoded, nonvolatile memory array with 15- $\mu$ m-square bit cells, which furnish access times of less than 20 nsec. The company has tested cells as small as 2- $\mu$ m square and claims access time is a function of feature size and that subnanosecond access times are feasible with conventional lithographic techniques. Each memory cell is composed solely of a capacitor, formed by metallizing plates on the top and bottom surfaces of a thin film of potassium nitrate. When the film is heated to approximately 125°C, the potassium-nitrate molecules become electrical dipoles and exhibit ferroelectric properties that remain after the film is cooled.

An electric field applied to the thin-film capacitor orients the dipole up or down depending on the applied field polarity, which varies the cell capacitance. At a 2000 Å film thickness, less than 4V generates a field strength adequate to flip the dipole orientation, making the device compatible with integrated circuitry. Once oriented, the dipole maintains polarity even in the absence of an electric field, resulting in nonvolatility. The company plans to offer fully operational, high-speed, nonvolatile RAMs by the end of this year. —Steven H Leibson



# Your design time's just been reduced!



Think about it—three raster scan DACs on a single chip. TRW LSI Products Division, the industry leader in high performance D/A converters has just produced a TRIPLE 4-bit DAC on a single bipolar monolithic chip—the TDC1334. It offers designers a significant reduction in CRT driver circuit design time.

We've reduced everything but the performance. The TDC1334 operates at 125MSPS with an on-chip reference. The power dissipation (1.5W max) is lower than three individual DACs combined and it can be operated in a TTL environment. Check out these other features:

- RGB complementary current outputs
- ECL compatible inputs
- Linearity error less than 1/8 LSB
- Registered data sync, blank and bright inputs
- Operates from a single -5.2V power supply
- Available in a 28 lead ceramic or CERDIP package

In addition, the low price of \$35.00 (U.S. dollars in 1000s CERDIP) will add to your overall design savings.

The TDC1334's monolithic construction enables designers to minimize and simplify board space and layout, reduce component requirements and reduce design time—a major cost factor in any system.

The TDC1334 is your one-chip solution to high volume production of CAD/CAE workstations, computer and business graphics, image processing and high resolution video. And TRW LSI always supports you with field and in-house application engineers, application notes and spec sheets. The DACs are available now from Arrow Electronics, Hall-Mark, and Hamilton/Avnet.

**Remember, you always get FULL SPEC PERFORMANCE from TRW LSI.**

Contact our Literature Service Department for a full data sheet and start reducing

your design time now. Call or write:

LSI Products Division,  
TRW Electronic Components Group,  
P.O. Box 2472, La Jolla, CA 92038,  
619.457.1000

In Europe, call or write:  
TRW LSI Products,  
Konrad-Celtis-Strasse 81,  
8000 Muenchen 70, W. Germany,  
089.7103.115

In the Orient, phone:  
Hong Kong, 3.856199;  
Tokyo, 03.461.5121; Taipei, 751.2062

©TRW Inc. - 1985 TRS-5108

**LSI Products Division**  
TRW Electronic Components Group



# NEWS BREAKS: INTERNATIONAL

BY PETER HAROLD

## **LOGIC ANALYZER SUITS INVESTIGATION OF 32-BIT SYSTEMS**

The PM3570 modular logic analyzer from Philips (Eindhoven, The Netherlands, TLX 51573) provides you with as many as 83 state-analysis channels and operates at clock speeds as high as 20 MHz. It has a 32-channel 100-MHz transitional timing analyzer, which you can reconfigure to provide several channel-number/frequency combinations, including 8-channel/400-MHz and 16-channel/200-MHz operation. Alternatively, you can use the timing section to implement an additional 32 state-analysis channels, to provide a total of as many as 115 state channels. The state and timing sections have cross-trigger/arm and time-correlated capabilities, with simultaneous display of state and timing information. Both the PM3570 and the entry-level PM3565, which can be fully upgraded to the PM3570 specification, feature software performance analysis and are priced from approximately Hfl 25,000.

## **PC-BOARD CAD SOFTWARE HANDLES 16-LAYER BOARDS**

Priced from £8000 and £12,000, the Ranger pc-board CAD software from Seetrax (Hayling Island, UK, TLX 86572) provides interactive or fully automatic component placement and routing of pc-board designs on IBM PC/AT, Olivetti M24-SP, or compatible computers. The system handles board sizes as high as 32.76 in. square with a working resolution of 0.001 in. You can design with as many as 16 track layers and 16 different track widths. Post-routing design-rule checks include automatic checking of track width, pad size, clearance, and connectivity. With a mouse, you can enter circuit data either as a schematic diagram or as a net list. In addition to generating the pc-board and solder-resist art, the CAD software produces circuit schematics, assembly drawings, parts lists, and NC-drill tapes.


## **FREQUENCY INVERSION IC SCRAMBLES VOICE-BAND COMMUNICATIONS**

The FX204 variable split-band frequency inversion IC from Consumer Microcircuits Ltd (Witham, UK, TLX 99382) allows you to scramble speech transmissions, making them unintelligible to unauthorized listeners. Operating over a 3400-Hz bandwidth, the IC uses switched-capacitor filters to split the voice band into high- and low-frequency bands; balanced modulators invert each frequency band around its own center frequency. You can externally program the split point to 32 different frequencies, suiting the device to fixed programmable or rolling-code speech scramblers. The IC can handle the input or output of synchronization tones if necessary. Fabricated in 5V CMOS, which suits it for use in battery-powered communications equipment, the IC comes in a 24-pin DIP or surface-mount package and sells for £8 to £9 (1000).
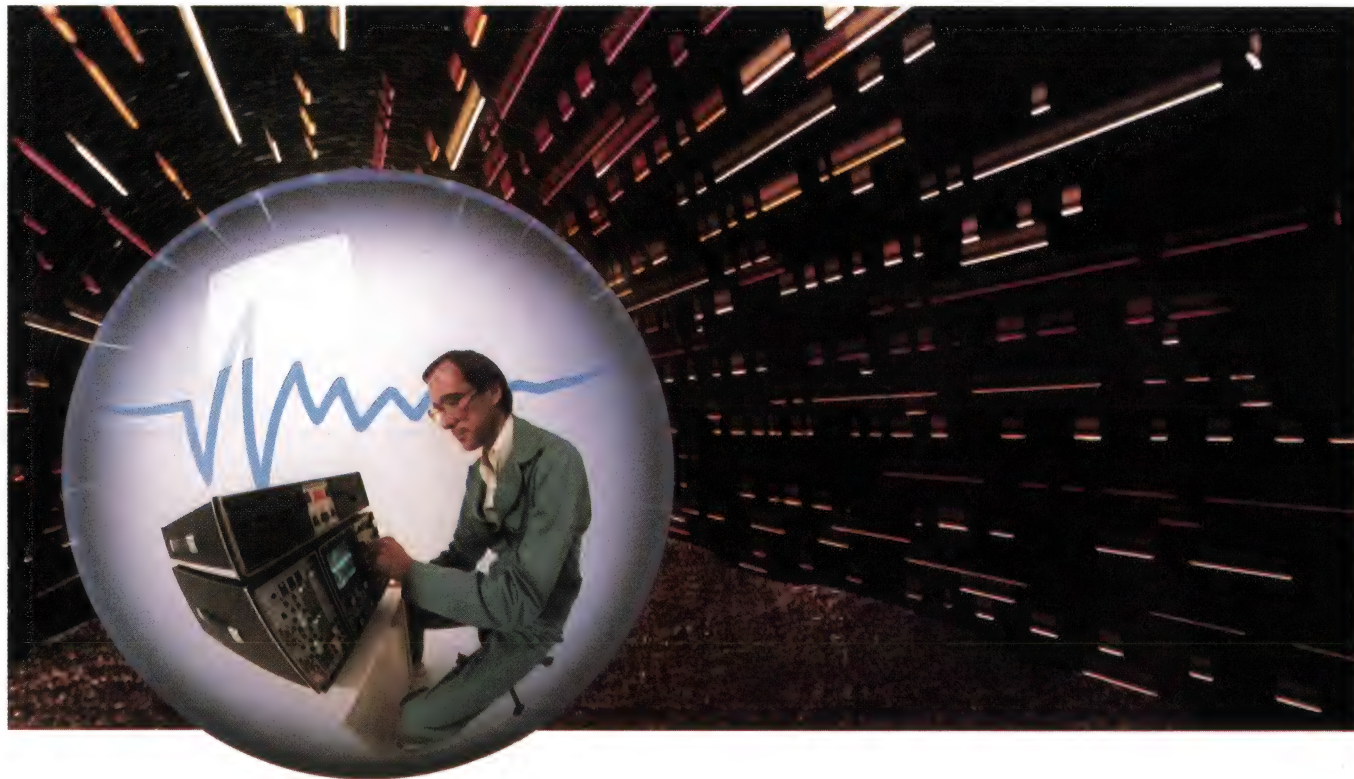
## **MAJOR VME BUS MANUFACTURERS ENDORSE VSB-BUS**

Philips (Eindhoven, The Netherlands), Plessey Microsystems (Towcester, UK), Thomson Semiconductors (Paris, France), and the originator of the VME Bus, Motorola (Phoenix, AZ), have jointly announced their commitment to support VSB (VME Subsystem Bus) as the preferred local extension bus for VME Bus systems. Developed by a working group of the IEC in conjunction with these companies and VITA (the VME Bus International Trade Association), the VSB is an amalgamation of the best features of the VMX Bus and Motorola's MVMX32 Bus, which it developed to support the 68020  $\mu$ P.





# TIME MACHINES.



**The Past.** Nicolet digital oscilloscopes can record the history of your signal before the trigger point. Examine what preceded an event as well as the event itself. Use expansion to analyze the signal in detail at up to 100 times the resolution of an analog scope. Store the signals on floppy disk or bubble memory for future recall and reference. Or plot them out in report ready format.

**The Present.** Compare live signals with each other or with previously stored signals. Store any signal with the touch of a button and use voltage and time numeric display for exact comparisons. You can even display related signals as functions of each other instead of time. Manipulate waveforms using the scope's built-in programs or transmit them to a computer and back for display.


**The Future.** Expecting a transient? Set-up your Nicolet scope to capture it while you're away! Some models can even capture a sequence of events and store them on disk or bubble memory automatically ready for instant recall and display.

**Get Results First Time, Everytime.** Don't miss important data because of set-up error. Nicolet scopes are easy to use. Find out how they can be the quickest solution to your signal problems. For more information, write Nicolet Oscilloscope Division, 5225 Verona Road, Madison, WI 53711. Or call 608/273-5008.

 **Nicolet**



# RF transformers

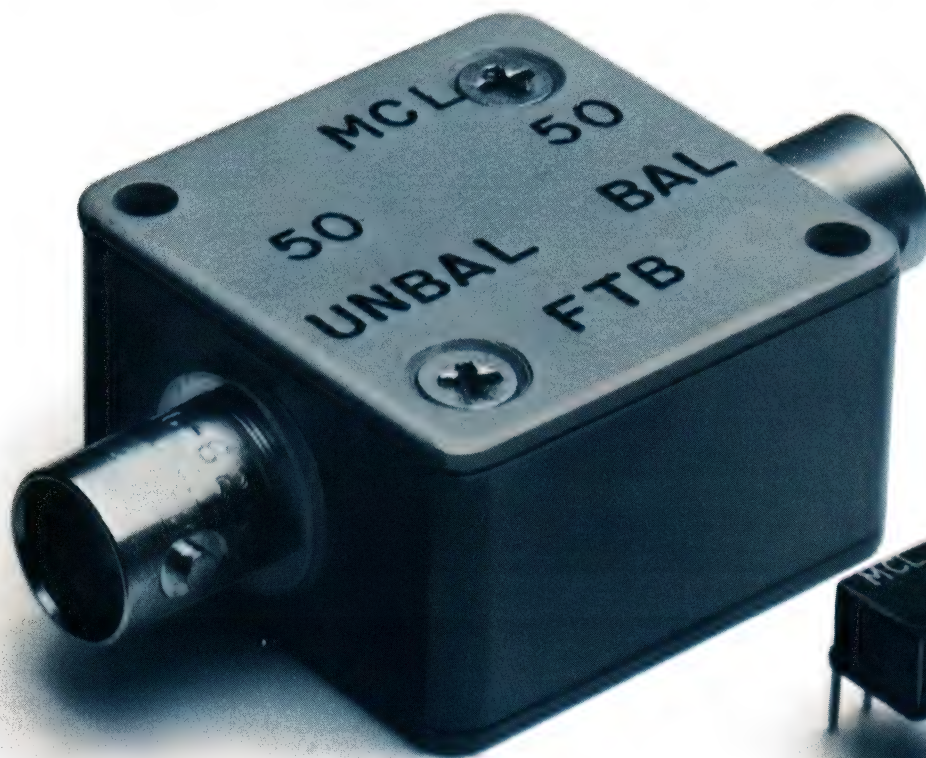

3 KHz-800 MHz  
over 50 off-the-shelf models  
from \$295

Choose impedance ratios from 1:1 up to 36:1, connector or pin versions (plastic or metal case built to meet MIL-T-21038 and MIL-T-55831 requirements\*). Fast risetime and low droop for pulse applications; up to 1000 M ohms (insulation resistance) and up to 1000V (dielectric withstanding voltage). Available for immediate delivery with one-year guarantee.

Call or write for 64-page catalog or see our catalog in EBG, EEM, Gold Book or Microwaves Directory.

\*units are not QPL listed



finding new ways...  
setting higher standards

**Mini-Circuits**

A Division of Scientific Components Corporation  
World's largest manufacturer of Double Balanced Mixers  
P.O. Box 166, Brooklyn, New York 11235 (718) 934-4500  
Domestic and International Telex 125460 International Telex 620156

CIRCLE NO 107

C71 Rev. Orig.



# RF switches



10 to 2500 MHz  
from \$19<sup>95</sup>

PSW 1211 (500 qty.)

Now, for your wideband systems design, under —\$20.00 SPST and SPDT pin diode switches that operate over the 10 to 2500 MHz range with less than 1 dB (typ.) insertion loss at 1000 MHz, 1.5 dB at 2500 MHz.

No waiting, immediate delivery . . . with one year guarantee. Call or write for our catalog or see our catalog in the Gold Book, EBG, EEM or Microwaves Product Data Directory.

**SPECIFICATIONS for**  
PSW 1111 (SPST) and PSW 1211 (SPDT)  
ZMSW 1111 and ZMSW 1211

FREQUENCY RANGE	10-2500 MHz
INSERTION LOSS	
10-2000 MHz	1.7 dB max.
2000-2500 MHz	2.7 dB max.
ISOLATION	
10-500 MHz	40 dB min.
500-1000 MHz	30 dB min.
1000-2000 MHz	25 dB min.
2000-2500 MHz	20 dB min.
SWR	1.5 max. ("on" state)
SWITCHING SPEED	1 $\mu$ sec. (max.)
MAXIMUM RF INPUT	+20 dBm
CONTROL	+5 V (5 mA max.)
OPERATING TEMPERATURE	-54°C to +100°C
STORAGE TEMPERATURE	-54°C to +100°C

<b>PRICE (6-24)</b>		(1-4)	
PSW 1111	\$29.95	ZMSW 1111	\$59.95
PSW 1211	\$29.95	ZMSW 1211	\$59.95



finding new ways . . .  
setting higher standards

**Mini-Circuits**


A Division of Scientific Components Corporation  
World's largest manufacturer of Double Balanced Mixers  
P.O. Box 166, Brooklyn, New York 11235 (718) 934-4500  
Domestic and International Telex 125460 International Telex 620156

CIRCLE NO 146

C80 REV. B




# When you positively custom

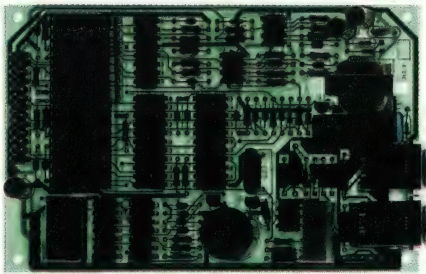

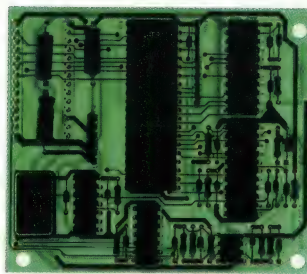
## Reliability

is your obvious first requirement in this vital link between your product and the outside world. At Ven-Tel — with 12 years experience and millions of modems designed and shipped—we don't take reliability for granted...so you can.


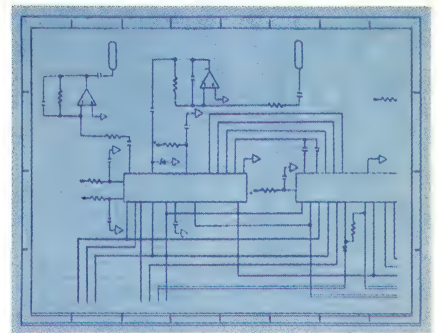
## Compatibility

with industry standards. All Ven-Tel modems utilize the industry standard "AT" command set, guaranteeing compatibility with virtually all types of software. And every Ven-Tel custom modem is fully compatible with our complete line of standard desktop and PC internal modems. We also meet Bell 212A and CCITT V.22bis standards in speeds up to 2400 baud.




## Quick Turnaround

is more than a phrase to us. We've built a reputation for meeting product deadlines among some of the nation's largest and most demanding manufacturers. From start to finish in as little as 90 days, Ven-Tel can help you get your product to market quickly. You can even begin development using our standard modules while your design is being finalized.

# take a good




# absolutely, need reliable modems...

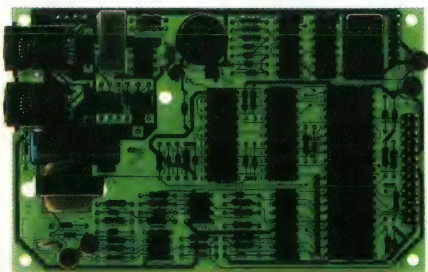

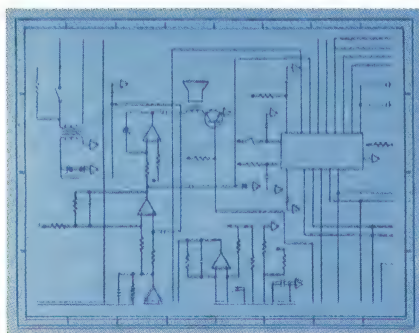
## Customizing

your modem is your choice. From our standard off-the-shelf boards, to complete custom design, to licensing our proprietary CMOS chip design (for quantities in excess of 100,000 annually), we guarantee the right modem solution based on your deadline, design and volume requirements. Custom hardware configurations and firmware give you maximum freedom for integrating the modem into your overall product design.


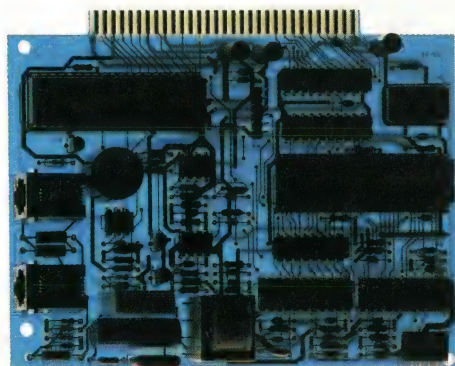
## Compact Size

is an important requirement in applications like credit check terminals, portable computers and trouble monitors. Ven-Tel modem density is state-of-the-art to provide excellent "real estate" value, with complete auto-dial/auto-answer, AT compatible, 212A modems—in as little as 12 square inches. With power requirements as low as 500mW.




## Competitive Pricing

makes the Ven-Tel custom modem package one definitely worth looking into. For quotations based on your modem specs or a discussion with our experienced OEM sales engineers, call **800/538-5121 (outside California)**. In California, call **408/727-5721**. Or contact us for our custom modem brochure: Ven-Tel, OEM Products Division, 2342 Walsh Avenue, Santa Clara, CA 95051.

# look at *Ven-Tel*



# NO ONE LIKES

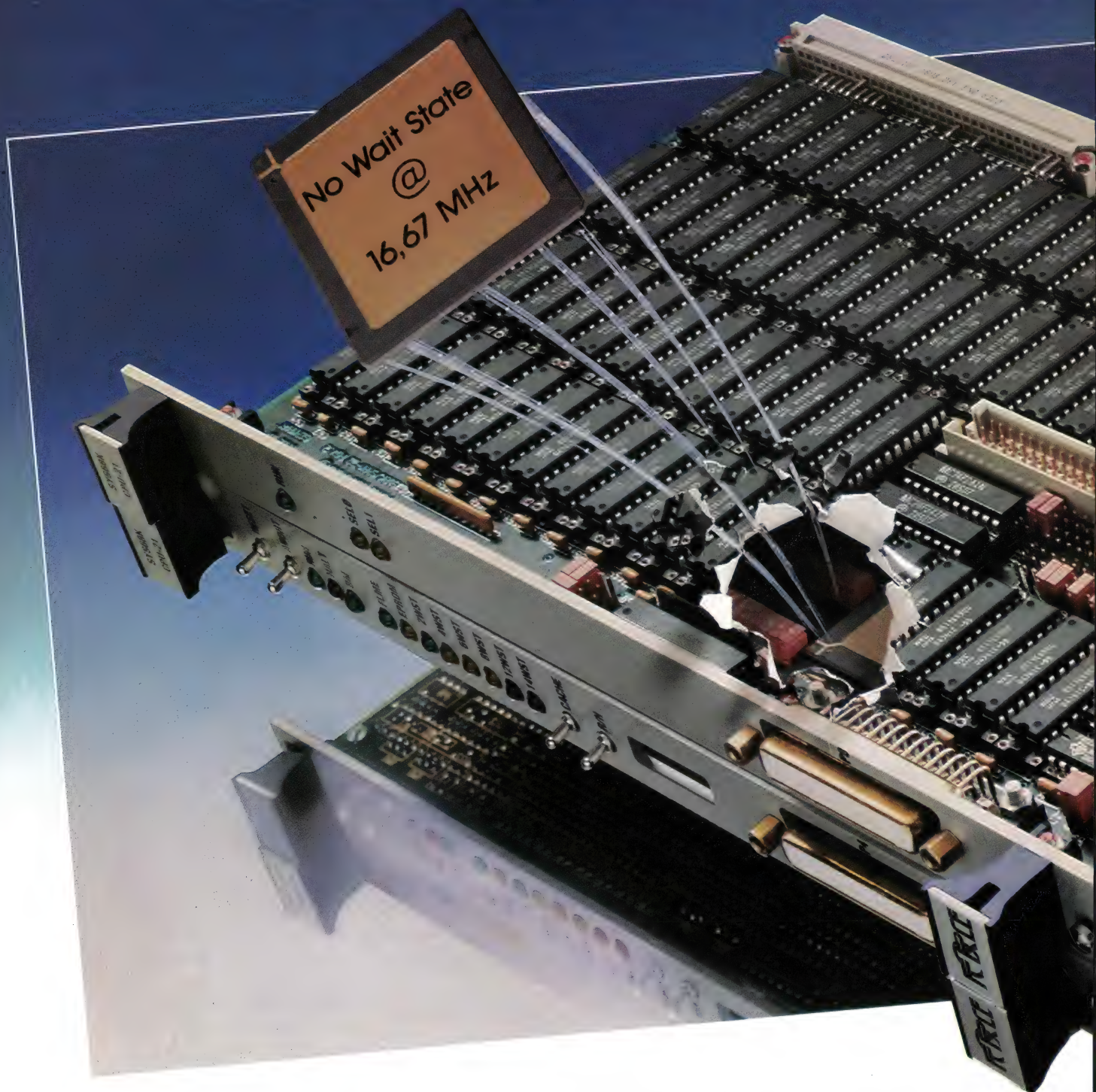

Your wait for 16 and 32 bit  
"WAIT STATE FREE"  
VMEbus CPU's is over.

Force Computers latest addition to its series of VMEbus CPU's features the popular 68020 at 16.67 MHz with zero wait states into 512 or 1024 KBytes of local RAM. Our design is so advanced that you will be able to accommodate speed improvements on the 68020 to 20 MHz without running into any "Wait States". NONE.

If your design calls for massive number crunching, we have good news for you. Our FPU runs at the same speed as the MPU.

If you don't like to wait, use our free advanced FORCEbus monitor. A one line assembler/disassembler for 68020 and 68881 with upload and download capabilities, self test, and memory test is included. Free. Built-in macro commands and benchmarks will give you the first glance at true 32 bit "NO WAIT STATE" performance.



# TO WAIT !



If you need more software, take a look at our PDOS\* Real-Time Operating System supporting C, FORTRAN 77, and PASCAL.

Or, if you think that 16 bit will do it for you, get your hands on our brand-new CPU-5 family with "NO WAIT STATE" performance at 12.5 and 16.67 MHz into 128 KByte of local RAM and Floating Point support. Yes, 68000 at 16 MHz.

Force supports you with VMX on both CPU-20 and CPU-5 families. Both with 700 page manuals.

In-circuit and dynamic test including a 48 hour burn-in at 60 degrees C will give you the quality you are looking for.

Need more support?

Don't wait. Call our application support team toll free, 1-800 BEST VME. In California, 1-800-237-8862.

\*PDOS is a trademark of Eyring Research Institute.



the intelligent choice

**Non-USA Readers Circle No. 148**

FORCE COMPUTERS GMBH  
DAIMLERSTRASSE 9  
D-8012 OTTOBRUNN  
TEL. (0 89) 6 09 20 33 [6 09 91-0]  
TELEX 524 190 forc-d  
TELEFAX (0 89) 6 09 77 93

FORCE COMPUTERS FRANCE  
11, RUE CASTEJA  
F-92100 BOULOGNE  
TEL. (1) 46 20 37 37  
TELEX 206 304 forc-f  
TELEFAX (1) 46 21 35 19





Incorporating a touch activated display into your system shouldn't be an after-thought. Adding touch is the best way to make your product truly interactive, easier to use, and better suited for the real world.

It's no wonder that touch is growing in popularity. And used in a wide range of applications—from interactive video displays in stores, banks, airports, and hotels to specialized systems in hospitals, training facilities, and factories.

But it's important to add the right touch. That's why Carroll Touch developed the Smart-Frame™ line of low-cost scanning infrared touch systems. Featuring a powerful, built-in microcomputer, these add-in units provide exceptional functionality and reliability at the right price. Just the right touch for a great design.

Discover more about Smart-Frame products. Contact Carroll Touch today.

**Start with the right touch.  
Finish with a great design.**



## **Carroll Touch**

a subsidiary of AMP Incorporated

**In Touch with Technology**

P.O. Box 1309  
Round Rock, TX 78680  
512/244-3500, Telex 881906

*Carroll Touch and Smart-Frame are  
trademarks of Carroll Touch, Inc.*

**CIRCLE NO 110**



# SIGNALS & NOISE

## US IC manufacturers ignore the ZIP at their peril

Dear Editor:

As a component engineer, I've seen US manufacturers of ICs make some costly mistakes in packaging. Over the last several years, the most common mistake they've made is to put memories in unnecessarily long DIPs—DIPs too long to allow engineers to fit everything they needed to on a pc board. Instead of a 0.045-in. maximum overhang from the centerline of the end pins to the edge of the package (half-lead style), which would allow for maximum packing of memory arrays, manufacturers used a package with an overhang of 0.050 in. or more. We found the memories we needed in short packages, though—in Japan.

It looks as if we're ready to hand Japan another victory. Many US manufacturers (especially the largest) are refusing our requests for a new package, while the Japanese are responding positively.

High-performance applications, such as ours at Intergraph, are often the proving ground for the latest ICs and, periodically, the latest packages. PGAs and SMDs have been discussed a lot lately, but a new package is poised to steal many of the SMD's applications. The ZIP (zigzag in-line package) offers greater density and is less expensive and easier to implement than are SMDs.

PC-board area is usually at a premium in high-performance applications. Although SMDs use considerably less space than do DIPs, ZIPs use even less space. An added bonus for pc-board designers is the easy straight-line routing of ZIP memory arrays.


Further, ZIPs use traditional soldering equipment and existing or modified SIP-insertion equipment. In contrast, SMDs require new equipment for both operations.

The only drawback ZIPs appear to have is that their pin count will probably peak at 24 or 28 pins,

which isn't really much of a limitation. High-performance dynamic RAMs, static RAMs, PROMs, PLDs, and glue parts, consisting mostly of 8-, 9-, or 10-bit-wide parts for bus applications, will fit easily in a 16- to 28-pin ZIP. (See the accompanying illustration, which depicts a ZIP for a 256k-bit dynamic RAM.)

The ZIP package is a definite winner in high-performance applications. US IC manufacturers had better wake up to that fact before they lose another proving ground and the revenue that goes with it.

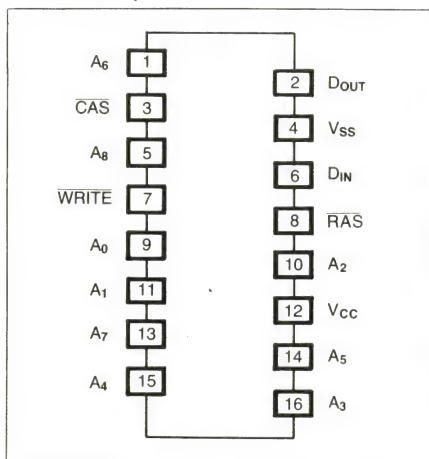*Sincerely yours,*  
M Tony Young  
Huntsville, AL



## Engineers need clerical help

Dear Editor:

I enjoyed your editorial "Cut out the paperwork" (EDN, October 31, 1985, pg 45). The problem is all too true. I have been an engineer in industry for 36 years, and during that time I have repeatedly been amazed and disheartened by the amount of clerical work and unnecessary paperwork required of us engineers.

Today, for example, I spent 15 minutes at the copy machine, 20 minutes running my own prints, 30 minutes filing new changes in specification books, 20 minutes trying to find a catalog in the library file, 10 minutes filling out company forms, etc.

*Continued on pg 34*

# POWER OP AMPS

INDUSTRY'S LARGEST SELECTION

## SHELF STOCK ON MIL-STD-883B PRODUCTS

COMPLIANCE  
WITH  
REV. C

10 MODELS  
UP TO  $\pm 150V$   
UP TO 10A

UNSURPASSED  
RELIABILITY



### DRIVES:


• MOTORS

• COILS

• TRANSDUCERS

• ACTUATORS

• PINS

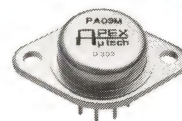

400V/ $\mu s$



$\pm 40V$  @ 10A



$\pm 145V$  @ 70mA



CALL

(800)421-1865

FOR OUR POWER  
OP AMP HANDBOOK  
OR CONSULT EEM/  
GOLD BOOK/IC MASTER

**APEX**  
 $\mu$ tech

DEDICATED TO EXCELLENCE

**APEX MICROTECHNOLOGY CORP.**

5980 N. Shannon, Tucson, AZ 85741 USA

France (6) 907.08.24 BRD (06152) 6003

Nippon (03) 244-3511 UK (01) 979 0123

CIRCLE NO 13



# TEK'S COST-EFFECTIVE, 32-BIT ANSWER FOR INDEPENDENT THINKERS.





**For less than \$10,000, you can add the Tek 6130 and turn your 4100 color graphics terminal into a 32-bit workstation.** It's a

combination that lets you configure a higher-performance, stand-alone system in RS-232 environments. Standard features of the 6130 include the UTek operating system—an extremely powerful yet friendly version of Unix—as well as 20 MB hard disk; 360 KB integrated flexible disk; 1 MB of parity RAM; Local Area Network (LAN) port; and GPIB port.

**To increase your productivity, UTek features an efficient Distributive File System (DFS).** It minimizes the number of operating system calls needed to perform standard Unix communications. In addition, UTek offers you productive features like electronic mail, network support, line and screen editors,

Connect a 4120 Series terminal to a 6130 for additional power and flexibility.




The 32-bit Tektronix 6130 supports Tek's 4100 family of desktop terminals and the 4692 high-performance color copier.

**Both the 6130 and 6130S Application Systems provide excellent communication capability with other computers via Ethernet and RS-232-C links.** You can communicate with other workstations at speeds of up to 1 megabit per second. Or download software from other hosts by

and remote login to access other workstations.

The optional Casual User Interface (CUI), a highly interactive menu-based program, enables you to perform basic system activities without detailed knowledge of the Unix command syntax.

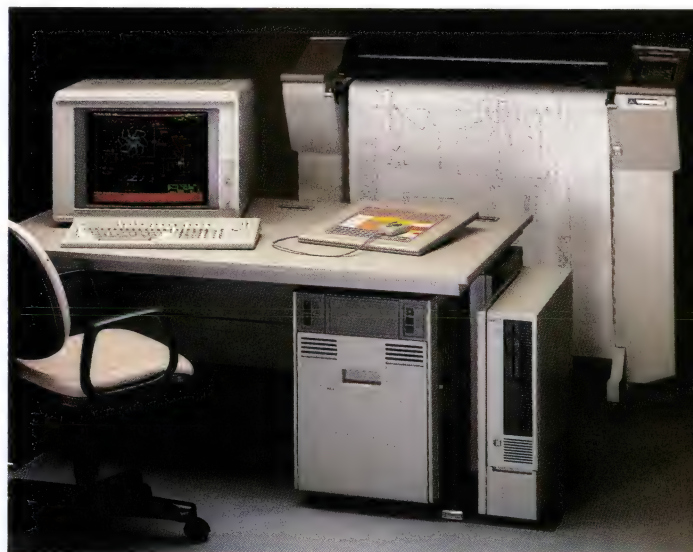**Five fully integrated application systems are now available for the 6130.** These preconfigured systems offer the hardware and



Choose from five fully integrated applications systems for the 6130 including the TekniCAD drafting system shown here.

software you need for applications such as computer-aided-drafting, technical data analysis and presentation, and Unix software development.

Because all the applications systems are built around Tek products, you're assured that they conform to industry standards for future growth.

using standard utilities, and execute it locally for fast, interactive response times.

And, like all Tek products, the 6130 and 6130S Application Systems are supported worldwide by a network of Tektronix sales and service professionals. The result: hardware and software you can count on.

To find out how you can add more power to your design environment, contact your local representative about the 32-bit Tek 6130 and 6130S Application Systems. Call 1-800-547-1512. In Oregon, 1-800-452-1877.




**Tektronix®**  
COMMITTED TO EXCELLENCE


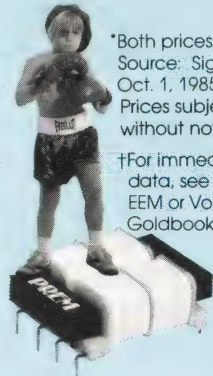
# Don't buy another Signal Transformer until you read this:

Compare Prem's price of \$8.35 on its SPW-306 to Signal's price of \$8.97 on its LP 40-300\*. Why pay more? Get a Prem quote today on your part number to see how much you can save. Your competitors are.



\*Both prices 10-24 quantities. Source: Signal Transformer Oct. 1, 1985 price list. Prices subject to change without notice.

†For immediate technical data, see Vol. 1 1985/86 EEM or Vol. 2 1985/86 Goldbook

**The Price Fighter**

†FREE Catalog with cross references

**PREM<sup>®</sup>**  
**MAGNETICS,**  
**INCORPORATED**

3521 North Chapel  
Hill Road  
McHenry, IL 60050  
815-385-2700  
TWX 910-642-3763

CIRCLE NO 14

## SIGNALS & NOISE

I think the problem has to do with corporate cultural taboos and status symbols. It is taboo for any engineer or engineering group to be provided with administrative or clerical assistants on a full-time basis. In fact, even to ask for such a thing is likely to get you classified as someone who "doesn't work well with facilities at hand" or "isn't productive without assistance." The corporate culture—and this problem is widespread throughout engineering companies—considers the engineer a body that generates certain outputs when given certain inputs, as a computer does. Computers don't need assistants. Neither do engineers.

Status is important, and balancing status so that no one feels discriminated against is even more important. An assistant, who would be a status symbol, cannot be tolerated.

The fact remains that the productivity of most engineers could be increased by 50% by eliminating dog work and most of the paperwork. It's surprising that for so many years the US corporate culture has put a higher value on status than on productivity and profit.


You can be sure that engineers who own and run their own companies have their own secretaries and other assistants. But companies don't perceive the need for this type of help at the lower engineering levels, and that's a mistake.

Your editorial should shake up some of the people who make this mistake. Keep punching away at the subject. It's important to the nation and to us engineers who are relegated to being our own clerks and gofers.

*Name withheld upon request*
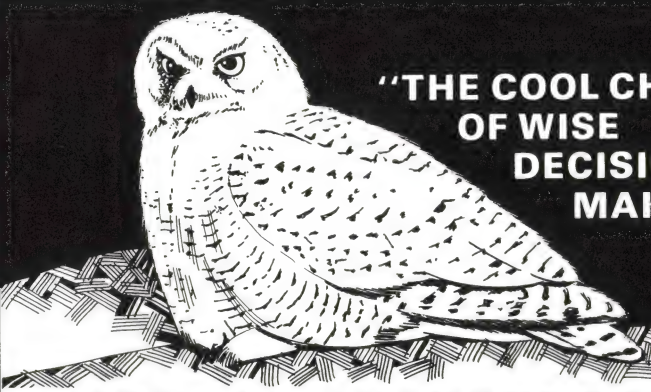
### WRITE IN

Send your letters to the Signals and Noise Editor, 275 Washington St., Newton, MA 02158. We welcome all comments, pro or con. All letters must be signed, but we will withhold your name upon request. We reserve the right to edit letters for space and clarity.



**"THE COOL CHOICE OF WISE DECISION MAKERS."**

## CMOS 8085 MICROPROCESSOR

AND PERIPHERAL CHIPS

CA80C85	8-bit 8085 Compatible Microprocessor
CA82C12	8-bit I/O Port
CA82C54	Programmable Interval Timer
CA82C59	Programmable Interrupt Controller
CA01C50	Clock/Calendar

For complete information on — package options  
— speed options  
— extended temperature and MIL spec product

Call Nick Keeble at (613) 836-1014 or in the USA 1-800-267-7231

**CALMOS<sup>®</sup>**  
**Calmos Semiconductor**

20 Edgewater St., Kanata, Ont., K2L 1V8 Tlx: 053-4501

CIRCLE NO 15



# THRIFTY & VERSATILE.



4SC510R2

## SPRAGUE MODULAR POWER SUPPLIES FOR DISPLAYS.

Sprague Series 200Z Modular Power Supplies meet a wide variety of needs at low cost. They're compact—measure but 2" x 2.5" x 0.9". They offer economical dc-to-dc conversion for high voltage

displays (planar gas-discharge, electroluminescent, and vacuum-fluorescent), liquid crystal displays, CMOS-based systems, and many other applications requiring nonstandard voltage levels. The versatility provided by both open-frame and encapsulated modular construction is further enhanced by options that include over-voltage protection, output-shutdown and output-voltage adjustment. Input voltages: 5 to 48 VDC. Single or dual output voltages: 12 VDC to 400 VDC. Delivery from stock or up to 4 weeks ARO. *Sprague Electric Company, a Penn Central unit, Worldwide Hdqtrs., Lexington, MA.* For applications assistance and prices, contact our Customer Service Center at 209/732-4585. For technical information, write for Brochure VS-111A to Technical Literature Service, Sprague Electric Company, 41 Hampden Road, Mansfield, MA 02048-1807.



CIRCLE NO 112





**Argentina:** Buenos Aires, Tel. 541-7141/7242/7343/7444/7545. **Australia:** Artarmon, Tel. (02) 439 3322. **Austria:** Wien, Tel. 62 91 11. **Belgium:** Bruxelles, Tel. (02) 242 7400. **Brazil:** Sao Paulo, Tel. (011) 211-2600. **Canada:** Scarborough, Tel. 292-5161. **Chile:** Santiago, Tel. 39-4001. **Colombia:** Bogota, Tel. 249 76 24. **Denmark:** Copenhagen, Tel. (01) 54 11 33. **Finland:** Helsinki, Tel. 17271. **France:** Paris, Tel. 43 38 80 00. **Germany (Fed. Republic):** Hamburg, Tel. (040) 3296-0. **Greece:** Athens, Tel. 9215311/319. **Hong Kong:** Kwai Chung, Tel. (0)-24 51 21. **India:** Bombay, Tel. 4930311/4930590. **Indonesia:** Jakarta, Tel. 512 572. **Ireland:** Dublin, Tel. 69 33 55. **Italy:** Milano, Tel. 2-67521. **Japan:** Tokyo, Tel. (03) 230-1521. **Korea (Republic of):** Seoul, Tel. 794-5011. **Malaysia:** Kuala Lumpur, Tel. 77 44 11. **Mexico:** Toluca, Tel. 91 (721) 613-00.



Electronic  
components  
and materials



# One standard. Zero defects.

## From IC people committed to quality.

Some IC companies talk about defect standards of 500 ppm as if they were proud of them. At Philips, we have a different philosophy: one defect is one too many. So zero defects is the standard we've set for our ICs. And the warranty for that standard goes like this: when you receive IC components from Philips, if you find a single defect in that batch, we'll take them all back for re-screening or replacement. The reason we can offer this warranty is that after 100% testing, we sample every batch. If we find a single defect, that batch isn't delivered.

The Philips IC activity is absolutely committed to a standard of zero defects. We have been for some time, in fact. In 1980, we instituted a rigorous 14-point program aimed at preventing mistakes – rather than correcting them. Since then, the program has evolved until it's now more than a program: it's a state of mind shared by everyone, from the design offices to the despatch department.

It's a state of mind marked by a determination to prevent all defects. By working with you and examining rejects, we'll carry zero defects beyond a standard to a reality. You'll find that same commitment to quality throughout Philips. That applies whether we're designing a VLSI chip containing more than 100 000 transistors, meeting delivery schedules, double-checking the accuracy of our paperwork, or simply getting your name right when you telephone us.

So while many IC companies are bragging about a standard of 500 defects per million, the people at Philips are working their way towards zero. And when you put your trust in that kind of individual commitment, you can't lose.

To find out more about the ways in which the Philips IC Zero Defects Standard can help you, contact your nearest Philips National Organisation and ask for more information.

**When you're offered zero, why settle for less?**

# One standard. defects.

**Netherlands:** Eindhoven, Tel. (040) 793333. **New Zealand:** Auckland, Tel. 605-914. **Norway:** Oslo, Tel. 680200. **Peru:** Lima, Tel. 326070. **Philippines:** Makati-Rizal, Tel. 86-89-51 to 59. **Portugal:** Lisboa, Tel. 683121. **Singapore:** Singapore 1231, Tel. 3502000. **South Africa:** Johannesburg 2001, Tel. 614-2362/9. **Spain:** Barcelona, Tel. 301 63 12. **Sweden:** Stockholm, Tel. 08/7821000. **Switzerland:** Zürich, Tel. 01-488 22 11. **Taiwan:** Taipei, Tel. 7120500. **Thailand:** Bangkok, Tel. 233-6330-9. **Turkey:** Istanbul, Tel. 43 59 10. **United Kingdom:** London, Tel. 01-580 6633. **United States:** Sunnyvale, California, Tel. (480) 991-2000. **Uruguay:** Montevideo, Tel. 91 43 21. **Venezuela:** Caracas, Tel. (02) 239 39 31.

---

---

---

---

---

---

---

---

---

---

# PHILIPS





## SHOGYO TRANSFORMERS AND ADAPTERS

### THE ANSWER TO YOUR CURRENT PROBLEMS.

Need transformers or wall-mount plug-in adapters? Call Shogyo.

Need line matching, lamp ballast, power and telephone coupling transformers? With lead wires, solder or PC terminals? Channel mount and in-line? Regulated or unregulated? UL/CSA approved? Call Shogyo.

You want quality, but your budget is tight? Your specifications are tough to fill, but you can't afford to wait for months? Call Shogyo. Here's why:

**Quality Control:** As a manufacturer, we can ensure product quality and reliability.

**Pricing:** You'll like our low manufacturer prices.

**Complete Custom Design Capabilities:** We produce for unique specifications.

**Fast Deliveries:** We deliver transformers, not excuses.

**Write or call for a FREE CATALOG.**

**Shogyo International Corporation,**  
287 Northern Boulevard, Great Neck,  
N.Y. 11021 (516) 466-0911

Telex: 12218 & 4758024

Cable: "SHOGYONEWYORK", Fax: (516) 466-0922.



# SHOGYO

*Specify Shogyo. Electronic components as good as your design.*

CIRCLE NO 29



## MEET THE SAILOR GENERATION

A new generation of design concepts...  
A new generation of programmers  
for EPROMs and PALs... Announcing  
the birth of the Sailor  
Series Programmers!

A state of the art  
dumb programmer,  
Sailor-8 operates as a  
slave to an IBM PC or  
compatible. The highly  
visual, Lotus 1-2-3 style  
user interface provides  
unprecedented ease  
of use as never before available on an  
EPROM programmer.

It's smooth sailing ahead with the  
advanced features of Sailor-8:

- macro file capability for

fully automated batch mode operation  
• checksum, date, and time stamping  
of EPROMs




- generation of serial  
and revision numbers
- full screen editing of  
buffer data
- library storage of  
EPROM masters on  
disk
- set mode program-  
ming of eight EPROMs  
in a single cycle (distinct

or identical data)

Let Sailor-8 turn all your EPROM pro-  
gramming chores into smooth sailing. It  
will lighten your load and give you more  
free time for life's real adventures!

**Join The Sailor Generation Today!**

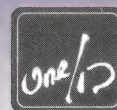

ONE/D  
505 W. Olive Ave.  
Sunnyvale, Ca 94086  
Phone 415-969-9900  
Telex 5101012668

**10-Day Money-Back Acceptance Period.**

Lotus 1-2-3 is a trademark of Lotus Development Corp. IBM is a trademark of IBM Corp.



# The new frontier in switcher technology

**Advanced surface mount technology achieves a breakthrough in switcher size and reliability.**

Todd engineers utilize clean, simple design with chip-on-board construction to reduce part count and increase MTBF. The new multi-output MDT series provides up to 60 amps of logic and memory, up to 16 amps of disk and tape, and up to 6 amps of RS232. Co-regulated control on the Disk/Tape output maintains  $\pm 5\%$  total band for extremely reliable disk drive operation. And there are many more benefits like Todd's


unique Veri-Drive Plus which increases switching efficiency and improves reliability.

Todd's MDT series meets all international safety standards. These switching power supplies are approximately 30% smaller in size than the industry average. The 160 and 220 watt series offer a choice of 18 models only 9" x 5" x 2.5". Or choose from 16 models in the MDT 300 and 400 watt series only 11.5" x 5" x 2.5".

Is it any wonder that Todd's new MDT series is called the New World Standard in switchers!

For all the facts about Todd's broad line of multi and single output switchers in standard,

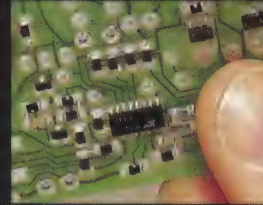
modified standard or custom designs ask for our new full color catalog, circle the reader service number or call 516-231-3366 to discuss your application.




Surface mount technology reduces size and increases reliability.
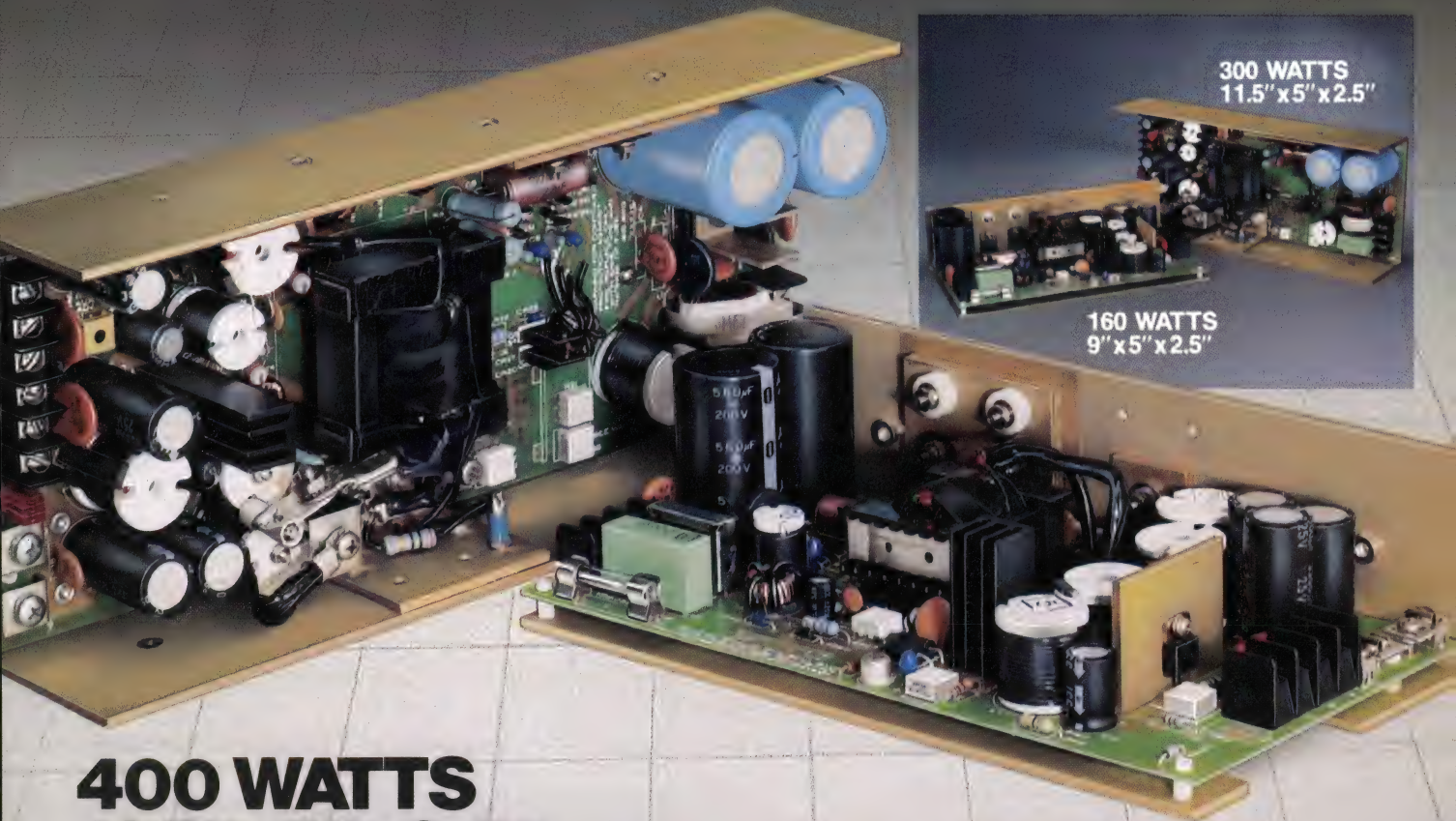
## TODD

Products Corp.  
50 Emjay Boulevard, Brentwood, NY 11717  
(516) 231-3366/TWX 510-227-4905



**400 WATTS  
11.5" x 5" x 2.5"**

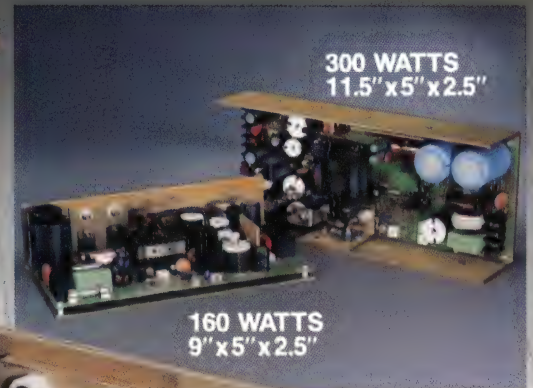

**220 WATTS  
9" x 5" x 2.5"**





# THE FIRST NAME IN MAGNETIC MATERIALS THE LAST WORD IN SERVICE

Basically, PERMAG'S got the largest, most comprehensive inventory of magnetic materials anywhere in the world. And a support staff of salesmen and customer service representatives going into the field and taking orders all across the U.S.A. But if we stopped at the basics we never would've become the best known name in magnetic materials. Our salesmen aren't just



friendly faces: they're resources, fully trained in a rigorous program at our on-going training facility in Chicago. And our customer service representatives aren't just telephone voices: they're experienced consultants who've helped many customers resolve tough fabrication and application problems. At PERMAG, we make sure you're not just supplied, but satisfied.



For one of our new catalogs or to see a salesman, mail the coupon.

**For faster assistance call toll free**

## 1-800-346-6600 EXT. B-185

### PERMAG CORP.

400 Karin Lane, Hicksville, NY 11801

EDN041786

☐ Have salesman call

☐ Please send me your latest Catalog

NAME \_\_\_\_\_

COMPANY \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_

STATE \_\_\_\_\_

ZIP \_\_\_\_\_

PHONE \_\_\_\_\_

## CALENDAR

**6th International Workshop on Expert Systems and their Applications**, Avignon, France. Agence de l'Informatique, Tour Fiat, Cedex 16, 92084 Paris-La Defense, France. (331) 47-96-43-14. April 28 to 30.

**Speech Tech '86**, New York, NY. Media Dimensions, 42 E 23rd St, New York, NY 10010. (212) 533-7481. April 28 to 30.

**Comdex/Spring**, Atlanta, GA. Interface Group, 300 First Ave, Needham, MA 02194. (617) 449-6600. April 28 to May 1.

**Dexpo South** (DEC-Compatible Exposition and Conference), Dallas, TX. Expoconsul International, 3 Independence Way, Princeton, NJ 08540. (609) 987-9400. April 28 to May 1.

**Technical Project Management Techniques** (short course), Milwaukee, WI. Peter Tocups, Center for Continuing Engineering Education, University of Wisconsin-Milwaukee, 929 N 6th St, Milwaukee, WI 53203. (414) 224-3952. April 28 to May 1.


**IEEE Applied Power Electronics Conference and Exhibit**, New Orleans, LA. Melissa Widerkehr, APEC, 655 15th St NW, Suite 300, Washington, DC 20005. (202) 347-5900. April 28 to May 2.

**Programming in Lisp and Prolog**, Boston, MA. Integrated Computer Systems, Box 45405, Los Angeles, CA 90045. (800) 421-8166; in CA, (800) 352-8251. April 29 to May 2.

**Design to Test** (short course), Milwaukee, WI. Peter Tocups, Center for Continuing Engineering Education, University of Wisconsin-Milwaukee, 929 N 6th St, Milwaukee, WI 53203. (414) 224-3952. May 1 to 2.


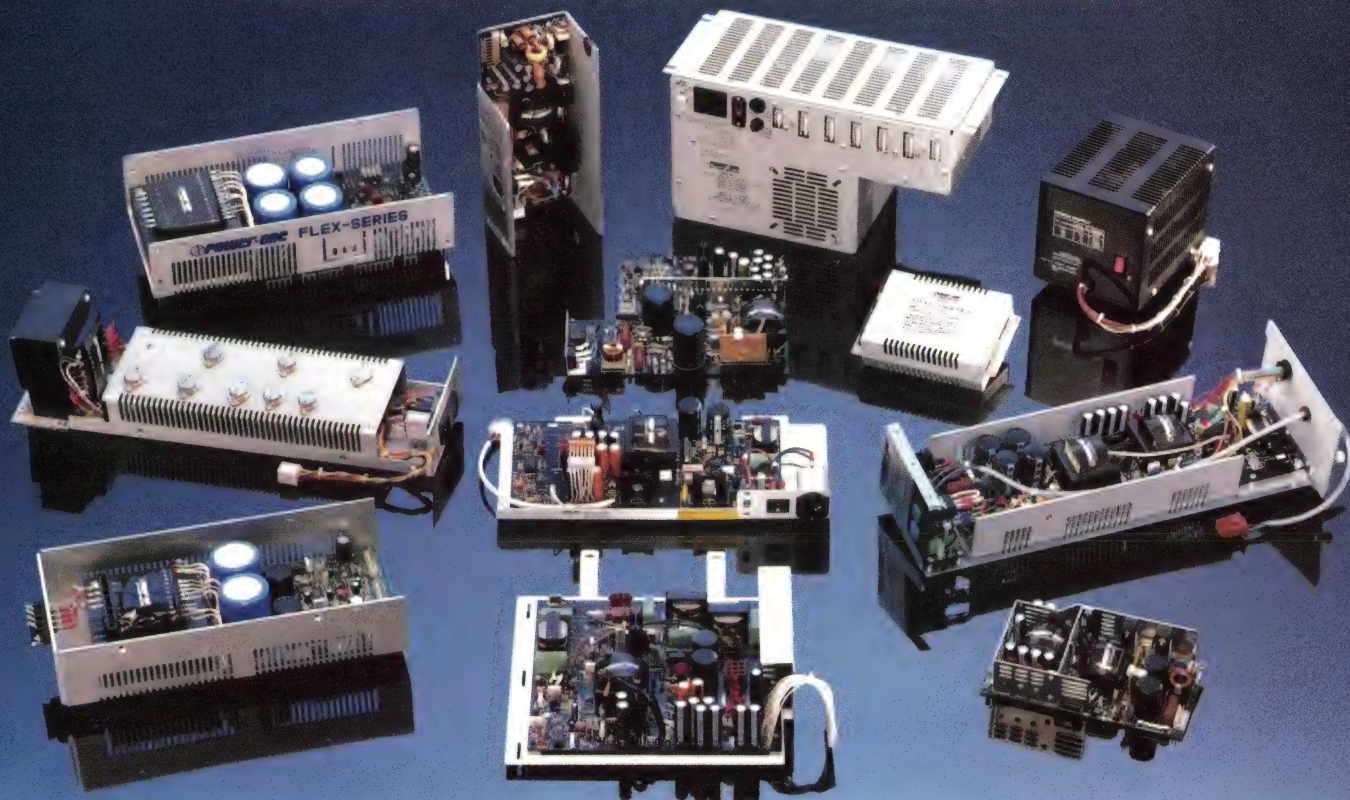
# We're Known for Our Standards. But We're Also Accustomed to Customs.



## Custom D.C. Power Supplies Built to Your Exact Specifications.

### Specialists in Customs

Custom D.C. power supplies have virtually become "standards" at POWER-ONE. Over the years we have provided the most cost-effective solutions to thousands of special requirements, with on-time delivery and dependable POWER-ONE service.

### Over 1-1/2 Million Custom Units Produced

Our basic philosophy in responding to special needs is simple... offer the lowest possible cost and lead time while guaranteeing POWER-ONE quality in every unit we build. That's why customers worldwide have turned to POWER-ONE for answers to unique design problems. And why they keep coming back.

### The Right Choice for Your Product

There is never a danger of "second-best" at POWER-ONE. Since our world-approved line of standards includes both linears and switchers, we not only know the technology that best suits your special needs, but *we have the capabilities to provide it!*

### Call Our Toll-Free **LITERATURE HOT-LINE** Today!

If you know the type of power supply you need, call the appropriate number below for our new Catalogs. If you need technical assistance, just ask. You'll get it.

#### LINEAR PRODUCTS

(800) 235-5943, Ext. 113

From CALIFORNIA: (800) 421-3439, Ext. 113

#### SWITCHING PRODUCTS

(800) 641-5986, Ext. 233

From CALIFORNIA: (800) 523-2534, Ext. 233




*"Innovators in Power Supply Technology"*  
**POWER-ONE**  
**D.C. POWER SUPPLIES**

#### POWER-ONE LINEAR PRODUCTS

740 Calle Plano • Camarillo, CA 93010-8583 • (805) 987-8741
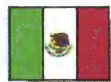
#### POWER-ONE SWITCHING PRODUCTS

833 Flynn Road • Camarillo, CA 93010-8702 • (805) 482-0757



See Us at Electro 2351-2353

CIRCLE NO 114



## Where's the control if the relays stick?

Maximum integrity in relays, micro-circuits, and shielding requires the cleanest unalloyed soft magnetic iron available. That's Remko.

The purity of Remko and the special metallurgical processes to which it is subjected make it very resistant to aging. In fact, we **guarantee** the aging values of Remko when it is heat-treated in accordance with our recommendations.

Furthermore, samples from every lot are continually tested for magnetic properties, and this certified information is available to you. Call Al Thomma at 1-800-321-3014 for more details.



CIRCLE NO 16


## INTERFACE PRODUCTS PUTS IT ALL TOGETHER!



Illuminated keyboards, annunciators and edgelighted panels. Integrated displays, digital readouts and special components. Custom or standard. Whatever your man/machine interface requirement, Interface Products can design and build it—from the entire black box to individual components.

Interface Products provides products for use in military, aerospace and commercial applications. From avionics displays to process controls, our products provide a reliable and functional interface between the operator and the system.

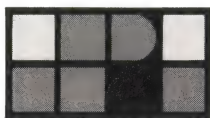Need bright solutions for your interface requirements? Let Interface Products put it all together for you. Call or write today for complete information.



**INTERFACE  
PRODUCTS,  
INC.**

2185 S. Grand Avenue, Santa Ana, CA 92705  
(714) 549-4977 • TWX 910-595-2569

CIRCLE NO 17

## CALENDAR

**Interfacing the IBM PC with the STD Bus for Instrumentation, Data Acquisition and Control** (short course), Indianapolis, IN. Pat Fox, Purdue University, School of Engineering and Technology, 799 W Michigan St, Indianapolis, IN 46202. (317) 264-2534. May 1 to 3.

**36th Electronic Components Conference**, Seattle, WA. Tom Pilcher, Publicity Chairman, Mallory Capacity Co, Box 372, Indianapolis, IN 46206. (317) 261-1306. May 5 to 7.

**Canadian High Technology Show**, Ottawa, Canada. International Marketing Services, 1030 S LaGrange Rd, LaGrange, IL 60525. (312) 354-3900. May 6 to 7.

**Grounding and Shielding** (short course), San Jose, CA. Interference Control Technologies, Box D, Gainesville, VA 22065. (703) 347-0030. May 6 to 9.

**Programming in Lisp and Prolog**, Palo Alto, CA. Integrated Computer Systems, Box 45405, Los Angeles, CA 90045. (800) 421-8166; in CA, (800) 352-8251. May 6 to 9.

**Programming in Lisp and Prolog**, Toronto, Canada. Integrated Computer Systems, Box 45405, Los Angeles, CA 90045. (800) 421-8166; in CA, (800) 352-8251. May 6 to 9.

**Association for Systems Management Annual Conference**, New Orleans, LA. Association for Systems Management, 24587 Bagley Rd, Cleveland, OH 44138. (216) 243-6900. May 11 to 14.

**American Consulting Engineers Council (ACEC) Annual Convention**, Orlando, FL. ACEC, 1015 15th St NW, Washington, DC 20005. (202) 347-7474. May 11 to 15.

**Optical Storage Forum**, Denver, CO. Cartlidge & Associates, 1101 S Winchester Blvd, Suite M-259, San Jose, CA 95128. (408) 554-6644. May 12 to 14.



# In the world of CMOS design, your competition is fierce.



With everyone jumping into CMOS, you need the best CMOS resources to help you stay ahead of the pack.

For more than 20 years RCA has been a world leader in CMOS. RCA invented CMOS,

and silicon-on-sapphire (SOS), the technology that's making headlines for speed and isolation even today.

As your CMOS supplier, we'll help you to survive and thrive in a fiercely competitive world.

**RCA**



# Unsurpassed CMOS experience gets you off to a good start.



RCA offers the world's broadest range of speeds in CMOS logic, including high-speed CMOS and new Advanced CMOS Logic (ACL) that's as fast as FAST.\* Our ASICs offer designer-friendly CMOS gate arrays and

standard cells, with a growing library of state-of-the-art macrocells. We offer CMOS microprocessors, with a complete line of peripherals and memories. And we're getting you off to a good start in CMOS flash converters.

\*FAST is a trademark of Fairchild Semiconductor Corp.



# New partnerships are rolling out the products for your future.



It takes innovation and cooperation to stay ahead today. That's why we've teamed up in the RCA/Sharp Microelectronics joint venture.

Our factory-of-the-future will be capable of producing submicron geometries in space-age clean conditions.

But the benefits of our shared expertise are available now.

We've just rolled out a new line of EPROMs and macrocells (including a 32-bit slice  $\mu$ P) resulting from an alliance with Wafer Scale Integration. And our new modem-on-a-chip comes from cooperation with Silicon Systems. Shouldn't you have a CMOS partner who knows how to make partnerships work?

**RCA**



# 50 ppm quality gives you the jump on the competition.



We're breaking through to new levels of quality and reliability. In "quality partnerships," we're helping customers eliminate incoming inspections. And helping them

squeeze more performance from their designs by tightening specs to the RCA quality zone.

If you're interested in just-in-time delivery, you need RCA quality standards.



# Your winning designs deserve world-class CMOS support.



Today's designs must compete with the best in the world. Be sure yours are backed by a CMOS supplier whose products, research, manufacturing and quality live up to the world-class challenge.

Call your RCA sales office or distributor to get a CMOS partnership started today. Or write: RCA Solid State, Box 2900, Somerville, NJ 08876.

Together, we can take on the world.

**RCA**





**“One, nobody has more  
military and JAN-qualified  
MOSPOWER than Siliconix.  
And two, they can deliver now.”**

**Our commitment to the hi-rel and military market is well-known. And we've just reaffirmed our market leadership with 16 new JAN-qualified MOSPOWER devices for power conversion and motion control applications. They're available now. Off the shelf. Like all Siliconix parts.**



Surrounding the Microprocessor.

**Siliconix**  
incorporated

2201 Laurelwood Road  
Santa Clara, CA 95054  
1-800-554-5565, Ext. 302

CIRCLE NO 118

We also have other MOSPOWER device families pending approval; and early next year we'll introduce the world's most advanced family of optimized MOSFETs hardened for both prompt-pulse and integrated radiation dosage.

As a company, we're totally dedicated to advancing the state-of-the-art in devices that surround the microprocessor. We build more of them, better, than anyone in the world. Which is why, whenever people talk about the latest in MOSPOWER, they're talking Siliconix. For more information or product literature call: 1-800-554-5565, Ext.302.

**SILICONIX MIL-QUALIFIED MOSPOWER PRODUCTS**

Part No.	Rating	Availability
JAN/JANTX/JANTXV 2N6661	90V/1.5A	NOW
JAN/JANTX/JANTXV 2N6756	100V/14.0A	NOW
TXV 2N6758	200V/9.0A	NOW
TXV 2N6760	400V/5.5A	NOW
JANTXV 2N6762	500V/4.5A	NOW
JANTXV 2N6764	100V/38.0A	NOW
JANTX/JANTXV 2N6766	200V/30.0A	NOW
JANTX/JANTXV 2N6768	400V/14.0A	NOW
JAN/JANTX/JANTXV 2N6770	500V/12.0A	NOW
JAN/JANTX/JANTXV 2N6788	100V/6.0A	NOW
JAN/JANTX/JANTXV 2N6790	200V/3.5A	NOW
JAN/JANTX/JANTXV 2N6792	400V/2.0A	NOW
JAN/JANTX/JANTXV 2N6794	500V/1.5A	NOW
JAN/JANTX/JANTXV 2N6796	100V/8.0A	NOW
JAN/JANTX/JANTXV 2N6798	200V/5.5A	NOW
JAN/JANTX/JANTXV 2N6800	400V/3.0A	NOW
JAN/JANTX/JANTXV 2N6802	500V/2.5A	NOW



## OKI 8-Bit Microcontroller Portable Development System

# The only **TRUE** CMOS ICE

Only from OKI: **TRUE** application ease,  
speed and economy—backed by exclusive  
OKI technology and warranty.

**Only** CMOS ICE with its own bond-out  
chip for **true** realtime In-Circuit  
Emulation—at high speeds to 16  
MHz, with unlimited breakpoints.

**Only** CMOS ICE with a **flash trace**  
included in its 2K x 64 realtime trace  
buffer memory.

**Only** CMOS ICE with EPROM program-  
mer built-in, ready and able to debug  
the complete 8-bit 51/52/59 family—  
in either CMOS or NMOS.

**Only** CMOS ICE with extended software  
options: macro-assembler, linker and  
symbolic debugger.

**Only** CMOS ICE with extended host-  
computer options: OKI's portable  
EASE 80C51/59 is totally compatible  
with any PC DOS, ISIS or CP/M-based  
system.\*

And you can ease your application  
along even faster and more cost-  
effectively, by starting out with the  
EPROM-piggyback development  
chips now available from  
OKI for every MCU  
in our optimized  
80C51-59 family.

### 80C51/59 Development Ease Available Now! Order complete data from OKI for:

- ☐ OKI EASE 80C51/59 ICE System
- ☐ OKI 8-bit MCU Piggyback Development Chips
- ☐ OKI 80C51-59 Single-Chip MCU Family

Name/Title \_\_\_\_\_  
Company \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_  
Tel: (\_\_\_\_) \_\_\_\_\_

Return coupon to Customer Service: **OKI Semiconductor**,  
650 N. Mary Avenue, Sunnyvale, CA 94086. Tel: **(408) 720-1900**

\*PCDOS is a trademark of Microsoft Corporation  
ISIS is a trademark of Intel Corporation  
CP/M is a trademark of Digital Research Corporation



# EDITORIAL

## Getting the (male) engineer's attention



You're likely to be unsettled, as we are, to note the methods a few ads (in this magazine and others in the industry) still employ to get a reader's attention. It's tempting, after an initial discomfort, to dismiss these familiar ads as harmless: "They don't show that much skin," "there are as many beefcake ads as cheesecake ones," and "sex is used to sell everything" are three arguments frequently used to justify them. But these arguments have serious flaws.

All the arguments fail completely to acknowledge the harmful effect of ads that treat women as objects, regardless of what's explicitly shown. The first implies that there is such a thing as too much skin—a point that the argument's proponent undoubtedly feels uniquely qualified to determine. This argument prudishly suggests that an ad could be objectionable only because of what it explicitly might show. As such, the argument is naive: Everyone knows the subtlety of suggestion is often more powerful than the direct assault. There's something equally unsettling about an ad that, for example, depicts fully clothed women while implying that they're confined to pink-collar ghettos—classes of low-paying jobs predominantly held by women.

The second argument concedes that the ads might be degrading but contends that both sexes are treated equally. Philosophy professor Ann Garry refuted this view in her essay "Pornography and Respect for Women." She noted that "losing respect for men as a class (men with power, typically Anglo men) is more difficult than losing respect for women or ethnic minorities as a class." Moreover, ads depicting men often involve sports themes, and an athletic image commands respect in our society. In contrast, the ads featuring women concentrate on the model, or a part of the model, purely as a prop to a (male) reader's successful lifestyle.

Relative to the "sex is used to sell everything" argument, we acknowledge that people buy a plethora of products, from perfume to automobiles, that they hope will at least slightly enhance their attractiveness. We sidestep the question of whether sex should be used to sell sex appeal; we simply note that sex is inappropriate for selling single-board computers.

**Rick Nelson**  
Managing Editor



# WEEK 25

Design with our new Am29525 Dual 8-Deep Pipeline Register and your pipelined system will never work better. That's because the Am29525 is the only pipeline register that also lets you dip into the data in any order, at any time.

To start with, the Am29525 is a pipeline register that is dual 8-byte deep. Or single 16-byte deep. It's programmed to hold, shift or load data via microcode instructions. And, while the I/O is three-state TTL-compatible, the innards are straight ECL. So its access time is a swift 21ns.

---

## Am29525

---

### Out of order.

---

On the other hand, the Am29525 is also a random access register file, with all 16 internal registers instantly available. Instead of the confines of first-in, first-out rules, you can grab an arbitrary 8-bit word whenever you want. So system performance is significantly improved.

What's more it's available in space saving, .4" wide 28-pin DIP packages.

The Am29525.

It's unlike any pipeline register you've ever used. Because it's more flexible than any pipeline register you've ever used.

Sometimes you improve things by not following orders.

**CIRCLE NO 156**

# WEEK 26

Ask us if we second source the popular X305 microprocessor architecture and we'll answer instantly: You bet.

---

## Am29X305A

---

### Got a second?

---

Our new Am29X305A 8-Bit Microcontroller is a plug-in replacement for the 8X305 chip you're using now. The same 200ns speed. The same highly integrated design that lets you read, mask, shift, operate on, rotate, merge and store data in a single instruction. Now available from two sources, assuring you of a steady supply for all your manufacturing needs.

One more thing. The Am29X305A is fabricated using our IMOX™ process, known throughout the industry for its outstanding performance.

And that makes the Am29X305A second to none.

**CIRCLE NO 195**

# WEEK 27

Floating point arithmetic is no longer the chore it used to be, thanks to our new Am29325 32-Bit Floating Point Processor.

Sure it's fast. A worst-case multiply takes but 150ns. But the real story is how easy it is to use. The Am29325 is a single-chip, non-pipelined, drop-in part—a true, easy-to-interface, black box solution.

---

## Am29325

---

### It's simple arithmetic.

---

Forget about internal pipeline registers, latency delay times, exotic software routines. Instead, start developing more powerful and more accurate array processors, desk top computers, digital signal processors and sophisticated robots that take less time to design and even less time to debug.

The Am29325. One easy-to-use chip that adds up to higher performance.

Could arithmetic be any simpler?

**CIRCLE NO 119**



# WEEK 28

Every new IC claims reduced boardspace. But this baby delivers. The Am29C101 is a CMOS 16-Bit Slice, and the newest member of our 2900 family gone CMOS. It is equivalent to four 2901s. Plus one 2902.

The pin count went from 172 to 64. And package count from 5 to 1.

Power's part of the reducing program. You'll need only 0.7W. (Equivalent bipolar parts typically require 5.8W.)

## Am29C101

### Lose ugly fat. Fast.

How much performance did we have to sacrifice? None. The speed of the Am29C101 is equivalent to 2901C-based systems.

The Am29C101 is software compatible, so the only thing you'll need to modify is your PC board layout.

It's expandable for longer word lengths (16-, 32-, 48-bit systems, etc.). And it's available in 64-pin plastic or ceramic DIP, 68-pin PLCC, or ceramic LCC.

Ask for the Am29C101 and cut the fat out of your next system.

CIRCLE NO 234

On October 1, 1985, Advanced Micro Devices told the world it would deliver fifty-two new products in one year. A new product every week. Tall order.

So where's seeking the impossible gotten us? Right where we expected. After twenty-six weeks, we're 26 for 26. Batting a cool 1,000. And here's what the world is telling us:

"Reduced networking costs." "State machines that have simplified the state-of-the-art." "More powerful, smaller air traffic control systems." "Extraordinary graphics for ordinary workstations." "PC's with fax capabilities."

And more. But that's only half the story. Watch this space for more chances to make your best idea better than you hoped it could be.

More new products. One a week. Every week. On the shelf. In volume.

Watch us open up the lead.

The International Standard of Quality guarantees a 0.05% AQL on all electrical parameters, AC and DC, over the entire operating range.

INT STD 840



## Advanced Micro Devices

For more information, contact the sales agent nearest you or write the word "Twenty-eight" on your letterhead and mail to Advanced Micro Devices, Mail Operations, P.O. Box 4, Westbury-on-Trym, Bristol BS9 3DS, United Kingdom.



# Copies of articles from this publication are now available from the UMI Article Clearinghouse.

For more information about the Clearinghouse,  
please fill out and mail back the coupon below.

Yes! I would like to know more about UMI Article Clearinghouse.  
I am interested in electronic ordering through the following  
system(s):

- ☐ DIALOG/Dialorder                      ☐ ITT Dialcom  
☐ OnTyme                                      ☐ OCLC ILL Subsystem  
☐ Other (please specify) \_\_\_\_\_  
☐ I am interested in sending my order by mail.  
☐ Please send me your current catalog and user instructions for  
the system(s) I checked above.

Name \_\_\_\_\_  
Title \_\_\_\_\_  
Institution/Company \_\_\_\_\_  
Department \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_  
Phone (        ) \_\_\_\_\_

**UMI**Article  
Clearinghouse

Mail to:

University Microfilms International  
300 North Zeeb Road, Box 91  
Ann Arbor, MI 48106



# Power from...

## Powertrade


### NEW DC-DC Modules

DC-DC Industry Standard  $2\frac{1}{2}" \times 3\frac{1}{2}"$   
PCB mounting  
Ventilated case  
Wide input range  
Singles, Duals,  
Triples  
10, 15, 20, 25 watts



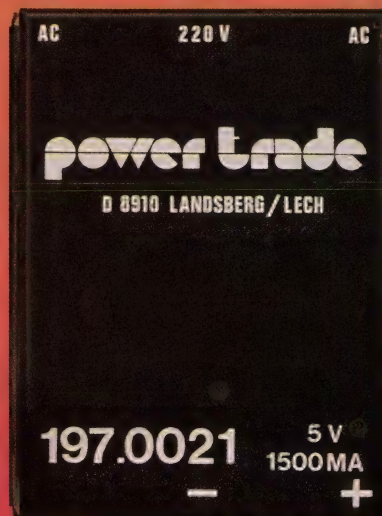
### AC-DC

Industry Standard  $2\frac{1}{2}" \times 3\frac{1}{2}"$   
PCB or Chassis mounting  
Ventilated case  
Runs 20°C cooler than encapsulated  
115, 220, 240V input versions  
Single and Dual output  
 $2\frac{1}{2}$  – 15 watts  
Low noise


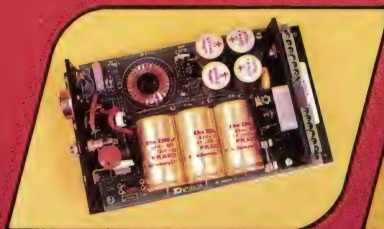
### NEW

Industry Standard  $8" \times 5" \times 11"$   
Power Supplies to 1500 watts.




Eurocard switching regulators  
up to 75 volts, 12 amps,  
200 watts.



Quality bench P.S.U.'s multi  
output to 400 volts.
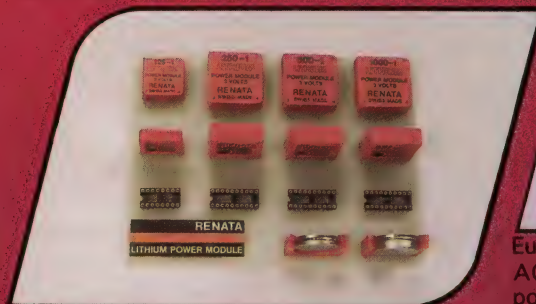
### NEW

Renata Lithium Power  
Modules and button cells  
now available.



Europe's widest range of  
AC/DC, DC/DC encapsulated  
power supplies.

**Gresham Powerdyne LIMITED** **power trade**

Osborn Way, Hook, Hampshire, England RG27 9HX  
Tel. (0256 72) 4246/3939 Telex 858415 (GRESH P)


Lechwiesenstrasse 9 D-8910 Landsberg, Germany.  
Tel. (0 8191) 4 60 68 Telex 5 27 115 POW D.



# HEXFET®



**Number 1  
in power MOSFETs!**

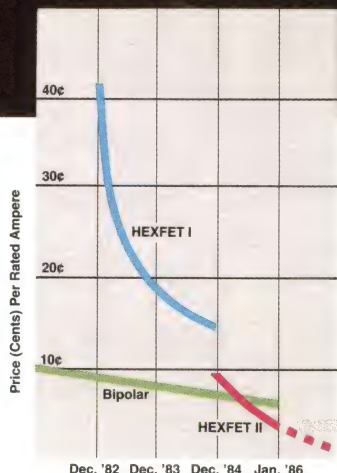

Typical HEXFET price declines since 1982

Now you can design-in 50V power MOSFETs with HEXFETs that cost less than you would pay for conventional, harder-to-drive, less reliable competitive or bipolar equivalents.

At the 100-piece price, for example, the HEXFET IRFZ22 costs 16% less than the popular D44H5 bipolar. And our IRFZ10 is almost 9% less than the MJE3055T in the 500-piece range.

Most important of all, you are guaranteed a more rugged device that switches faster, handles full rated current/voltage without second breakdown, and is easier to parallel.

In short, HEXFETs make the best cost-effective alternative to your bipolar design. It's one more reason why they are today's quality choice in power MOSFETs. Call or write for data.

***breaks the bipolar  
price barrier!***

**International  
IOR Rectifier**

WORLD HEADQUARTERS: 233 KANSAS ST., EL SEGUNDO, CA 90245, U.S.A. (213) 772-2000. TWX 910-348-6291, TELEX 472-0403  
EUROPEAN HEADQUARTERS: HURST GREEN, OXTED, SURREY RH8 9BB, ENGLAND TELEPHONE (088 33) 3215/4231, TELEX 95219

CIRCLE NO 120

Power MOSFETs • CMOS Power ICs • Commercial/Custom Power Packages • Schottkys  
Rectifiers • Thyristors (SCRs) • Diode Bridges • Molded Circuits • Assemblies



# TECHNOLOGY UPDATE

## Process improvements and special features reduce high-end static-RAM access times


Maury Wright, *Western Editor*

Today's fast 16k- and 64k-bit MOS static RAMs have seen their access times fall to the 25- to 35-nsec range, approaching the speeds of ECL static RAMs. Furthermore, these devices offer such features as output-enable pins, separate I/O, reduced chip-select access times, and reset functions, allowing board- and system-level designers to achieve further reductions in effective access time. You will find a larger variety of these specialized features in 16k-bit offerings; manufacturers have only just begun to enhance the fast 64k-bit static RAMs.

These improvements in fast static RAMs allow designers the luxury of employing low-cost, high-density MOS static RAMs in applications traditionally served only by ECL memories. Such applications include caches, communications, imaging systems, control stores, and data-acquisition systems. Some applications require absolute chip-access times substantially less than 25 nsec and therefore must employ ECL memories. ECL offerings, however, typically provide only 1k- or 4k-bit densities, so you might find you need more chips to fulfill your memory requirements. Many designers are restructuring system architectures to use the 25-nsec MOS memories, even in minicomputer and mainframe caches.
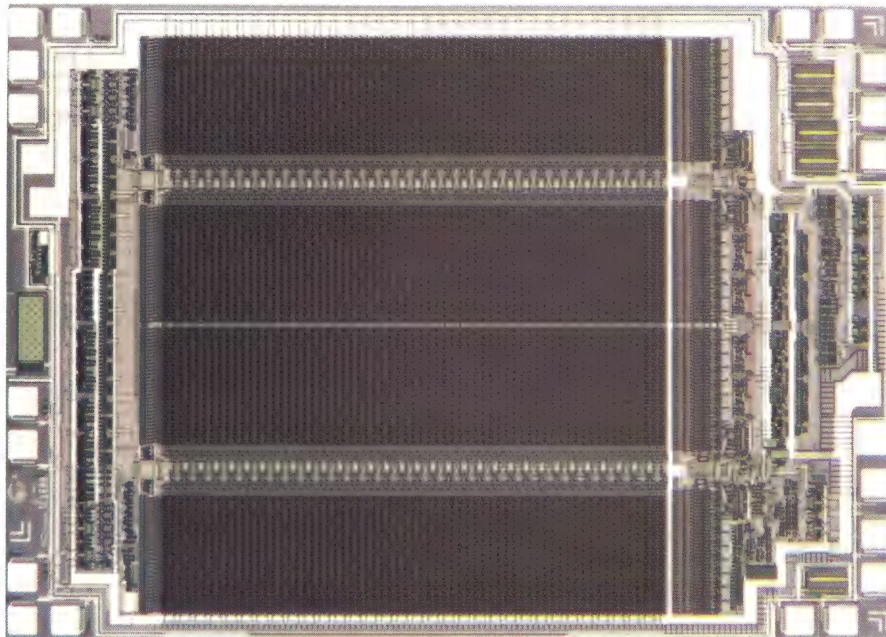
### MOS RAMs for non-MOS $\mu$ Ps

Some applications that have traditionally called for ECL memories don't use a processor based on ECL ICs; chances are fast MOS static RAMs will fit your needs here as well. The propagation delay in a



*Sub-35-nsec 16k-bit static RAMs from Cypress include ICs with  $\times 1$  and  $\times 4$  organizations. The CY7C168 is a 4k $\times$ 4-bit device that specs a 25-nsec access time.*

buffer between an ECL memory and a MOS processor diminishes the access-time improvement over MOS devices that ECL memories normally would confer. Meanwhile, the special features that effectively reduce access time ease integration of MOS static RAMs into these applications.

Until recently, a static RAM was regarded as "fast" by virtue of its application; ie, it was fast if you used it with a non-MOS  $\mu$ P, according to Lane Mason, senior industry analyst for Dataquest Inc (San Jose, CA). The MOS  $\mu$ Ps were too slow to utilize effectively the speeds of the fast static RAMs. Now, Mason admits, that characterization must change. Fast MOS static RAMs turn up in increasing numbers of designs based on MOS  $\mu$ Ps or MOS bit-slice processors. New  $\mu$ Ps with 8-, 16-, and 32-bit data paths feature clock rates approaching 20 MHz. General-

purpose computer designs with such high-performance  $\mu$ Ps can use the fast static RAMs for a cache.

Designs with an embedded  $\mu$ P often require faster access than the system CPU itself actually demands. For example, an imaging system may require that a special-purpose controller read memory faster than the CPU can access the same shared memory. Today's MOS static RAM prove useful in these applications as well.

Static RAMs primarily feature either  $\times 1$  ("by 1"),  $\times 4$ , or  $\times 8$  organizations. Typically, the popularity of a particular package and organization leads to a de facto standard, often followed by JEDEC imprimatur. JEDEC publishes official standards for the static-RAM packages and pinouts.

The commodity market for static RAMs (ie, for slower, low-cost devices produced in large quantities)



# The Technology Of Diversity

"...valuable resources, many of which simply aren't available from other suppliers."

*Anthony Capponi*


Anthony Capponi  
District Manager  
Structured Products Department  
Southwestern District

"GE Plastics has attained global leadership first by inventing advanced polymers and then maximizing their effectiveness in diverse markets. Our versatile line of extruded LEXAN® sheet products is an excellent example of high-performance polycarbonate technology ready-made to deliver impact toughness, clarity, energy efficiency and high light transmission in architectural, security and greenhouse glazing—weather and vandal resistance in outdoor signage.

We also supply our polycarbonate in a wide range of high performance films that set new performance standards in applications ranging from graphics and membrane switches to high-tech packaging.


GE Plastics' diversity of expertise gives customers valuable resources, many of which simply aren't available from other suppliers."

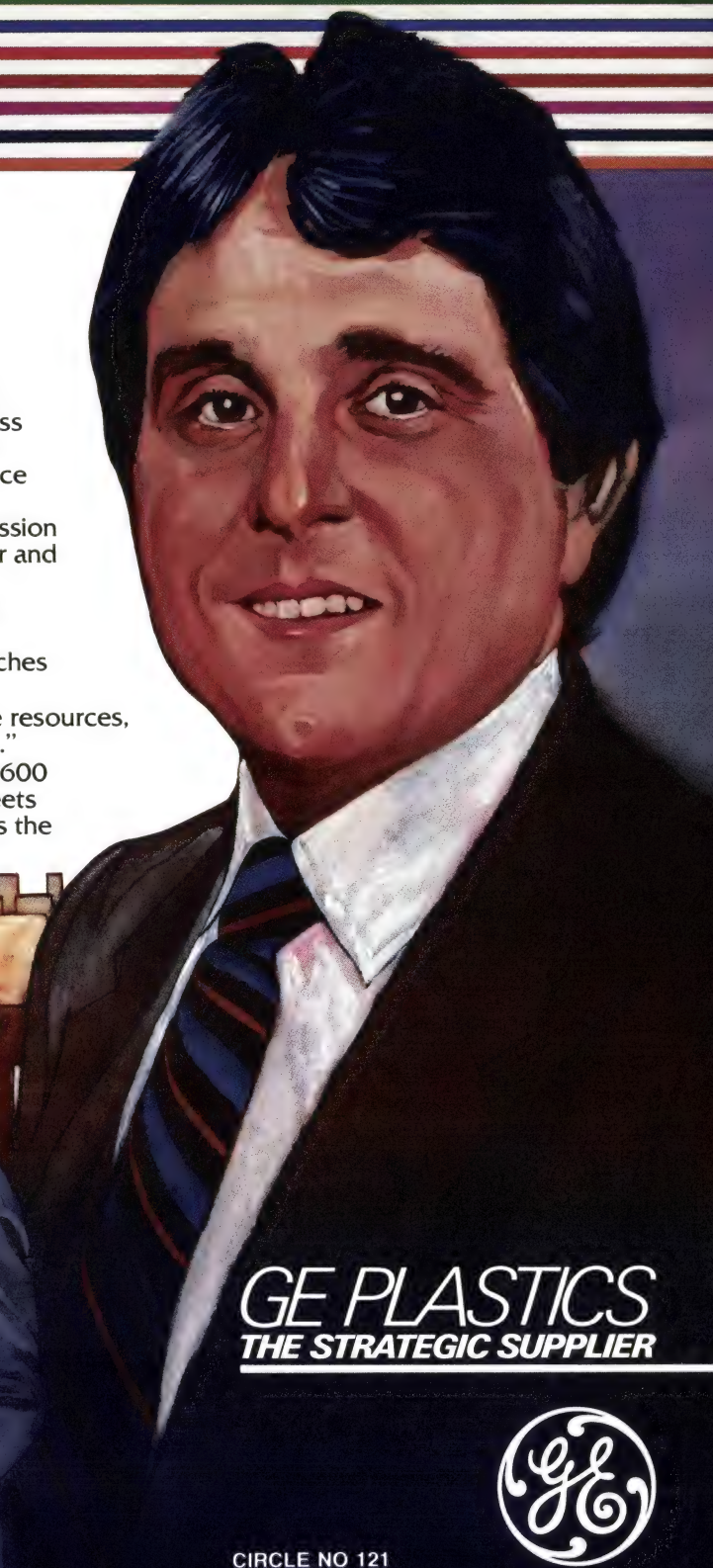Start a dialogue with GE Plastics. Call toll free (800) 845-0600 from anywhere in the U.S. or Canada and request our Sweets catalogue brochure and our 64-page Properties Guide. It's the first step in putting GE Plastics' diversity to work for you.



**GE PLASTICS**  
**THE STRATEGIC SUPPLIER**



 and ® Registered Trademarks of General Electric Company.  
\* Registered U.S. Patent and Trademark Office.

CIRCLE NO 121



# TECHNOLOGY UPDATE

centers on  $\times 8$  organizations, for which there are established industry standards. Industry standards also exist for  $\times 1$  and  $\times 4$  parts. Manufacturers of fast static RAMs use standard organizations and packages whenever possible, but many of the special features found in fast static RAMs require some diversion from a standard. For example, a reset function requires an additional input not found on a standard static RAM.


Applications that simply require the improved densities and speeds benefit from the availability of standard sub-35-nsec static RAMs from many sources. Choosing a memory with a special feature may limit you to a single source. Because the special features simplify the static RAMs' integration into specific applications, designers must balance tradeoffs between simplicity of design and multiple sources.

## Sub-35-nsec parts fall to \$10

At the level of 16k-bit densities, industry-standard fast MOS static RAMs have dropped to \$10 to \$35 in OEM quantities. For example, Cypress offers the 16k $\times$ 1-bit CY7C167 and the 4k $\times$ 4-bit CY7C168 static RAMs, each featuring a 25-nsec access time. The former costs \$18, the latter \$19.50 (100). In quantities of 5000, the industry-standard 4k $\times$ 4-bit IMS1423 from Inmos drops to \$12. Lattice Semiconductor also provides standard, 25-nsec, CMOS static RAMs in 16k-bit densities. The 4k $\times$ 4-bit SR16K4 costs \$22 and the 2k $\times$ 8-bit SR16K8 sells for \$25 (1000).

For 16k- or 64k-bit, NMOS or CMOS static RAMs, the access time determines the price. Access times for the static RAMs described here are minimum figures; most vendors that offer 25-nsec parts also offer slower parts, and you may specify a memory that's 10- to 20-nsec slower for cost savings approaching 50%.

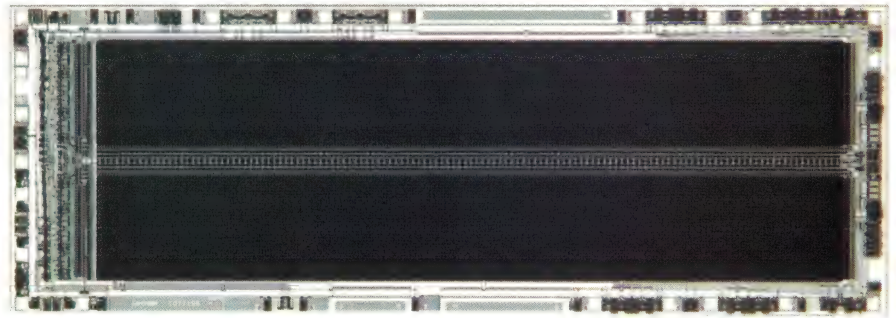As an example of such cost savings, consider some 16k-bit offerings that spec 35-nsec min access



*This industry-standard, 35-nsec, 16k $\times$ 4-bit static RAM, the IDT7188 from Integrated Device Technology, comes in nonstandard versions that provide special features for reduced effective access time.*

times. Vitelic's 16k $\times$ 1-bit V61C67, 4k $\times$ 4-bit V61C68, and 2k $\times$ 8-bit V61C16 static RAMs cost \$11, \$12.76, and \$14.51 (100), respectively. These CMOS ICs suit low-power and battery-backup applications. In active mode, the  $\times 8$  static RAM consumes 200 mW, and the  $\times 1$  and  $\times 4$  offerings consume 150 mW. All devices consume 0.5  $\mu$ W in standby mode and 0.1  $\mu$ W in a low-voltage data-retention mode. In the low-voltage mode, the ICs retain data when powered from a 2V supply.

For applications that are less power sensitive, NMOS 16k-bit fast static RAMs do the job and cost less than the CMOS parts. Toshiba currently offers the 2k $\times$ 8-bit TMM2018 and the 4k $\times$ 4-bit TMM2068 NMOS static RAMs, which spec 35-nsec access times. Both parts consume 825 mW when active and 110 mW in standby mode. The parts cost \$10 and \$8.30 (100), respectively, and they come in industry-standard configurations.

A number of 16k-bit static RAMs implement special features that trim the memories' effective access times. Toshiba's 4k $\times$ 4-bit static RAM, for example, furnishes an output-enable pin. The 35-nsec TMM2078 comes in a 22-pin package and costs \$9.90 (100). All of the 16k-bit Toshiba parts will achieve 25-nsec access times in the second or third quarter and will cost 10 to 20% more.

According to Jim Townsend, strategic marketing manager at Toshiba, the output-enable feature

improves system speed by 5 to 10 nsec. The output enable allows you to design a board architecture that frees the bus faster than standard 4k $\times$ 4-bit static RAMs can (the standard parts use common-I/O pins, ie, input and output data are on the same pin). A typical board architecture employs parallel data lines from multiple static RAMs. During a read operation, a single RAM ties up the bus until the processor removes the input address to the static RAM. If implemented in the board design, a static RAM with output enable will release the bus upon completion of the read operation and before the static RAM is deselected.

An industry-standard  $\times 4$  package requires 20 pins without the output enable; no standard currently exists for  $\times 4$  parts with the output-enable feature. Industry-standard static RAMs typically implement output enable on all  $\times 8$  designs. Because such devices have eight data lines on a single IC, the output-enable feature simplifies device timing.

Another useful feature is separate data I/O. In the case of  $\times 1$  devices, the provision of separate I/O lines only requires one extra pin. Separate I/O provides an optimum configuration, and the industry accepts the 1-pin penalty. Industry standards to date do not include separate I/O for  $\times 4$  static RAMs, but the need for improved speeds and densities is leading designers to demand such features, despite the additional cost.



(a) Block diagram of a 74F138 decoder. The decoder has three outputs:  $\overline{CE}_7$  connected to MEMORY ROW 7,  $\overline{CE}_1$  connected to MEMORY ROW 1, and  $\overline{CE}_0$  connected to MEMORY ROW 0. A green arrow labeled '3' indicates the SYSTEM ADDRESSES bus, which is connected to the decoder and the memory rows.

(b) Timing diagram showing the relationship between SYSTEM ADDRESSES,  $\overline{CE}$ , and DATA OUT. The diagram compares two types of RAMs:  $t_{ACS}$ -LIMITED RAMs and 51C69 RAMs. For  $t_{ACS}$ -LIMITED RAMs, the data becomes valid after  $t_{ACS}$  from the falling edge of  $\overline{CE}$ . For 51C69 RAMs, the data becomes valid after  $t_{AA}$  from the falling edge of  $\overline{CE}$ . The diagram also shows  $t_{DECODE}$  and  $t_{ACS}$  for the decoder output, and an 'ACCESS-TIME IMPROVEMENT' region for the 51C69 RAMs.


Semiconductor manufacturers typically distinguish between two types of read cycles when measuring access times. In one case, the address lines stabilize before the chip-select input goes active—for example, when high-order bits needed to address several banks of RAM must go to a decoder before activating the chip-select pin. In the second case, the address lines stabilize after chip select is activated. (Fig 1).

EDN April 17, 1986



# When Performance Counts
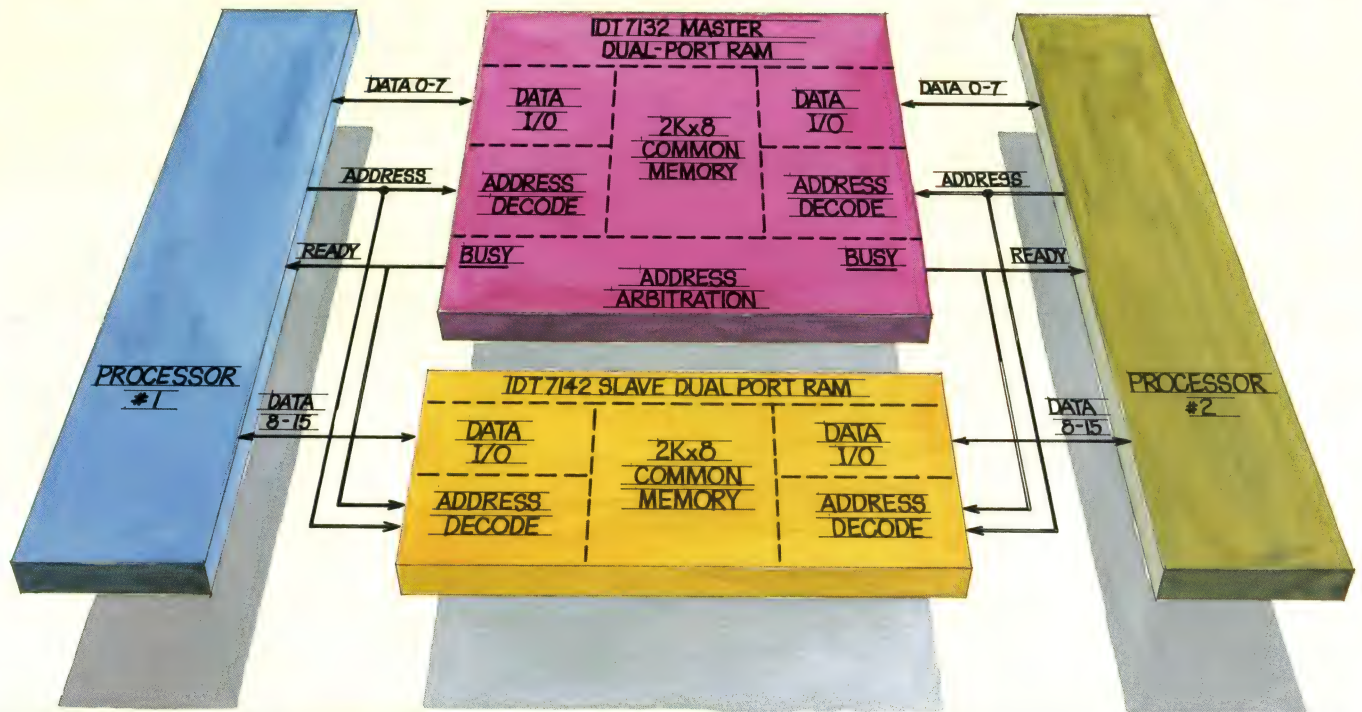
## Expandable 55ns Dual Port CMOS Static RAMs




**New "MASTER/SLAVE" combo is the only way to expand width and eliminate "system deadlock" without incurring a speed penalty due to extra logic.**

We've led the market with the industry standard IDT7130 (1Kx8) and the IDT7132 (2Kx8) "MASTER" dual port RAMs. Used in multiprocessor systems, they provide fast, asynchronous, simultaneous access of a common memory from two totally independent data/address ports. On chip arbitration logic resolves conflicts when the addresses match.

Now we are introducing the IDT7140 (1Kx8) "SLAVE" and the IDT7142 (2Kx8) "SLAVE" dual port RAMs which permit width expansion to x16, x32 or greater while maintaining a 55ns access time. All you do is add as many SLAVES as you need to one MASTER.

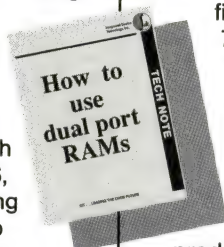A SLAVE eliminates catastrophic "system deadlock" in width expansion encountered when using dual port memories. Without a SLAVE you must use external logic for address arbitration to avoid deadlock—and that causes performance degradation.



**Industry's fastest.** All four of these dual port static RAMs have access times of 55ns.

**Cascadable in depth.** To 4K, 8K, 16K or more.

**Low-power and battery backup.** Typically 325mW active and 1mW standby, the low-power version permits battery backup at 200µW from a 2 volt battery.

**Availability.** Commercial/military product from stock in 48-pin DIPs or LCCs.

**May we be of assistance:** Call or fill in the bingo for a copy of our *Technical Note* explaining (1) how and when to use dual port static RAMs (2) how to avoid "deadlock."

Also ask for our *Product Selector Guide* on high-speed CEMOS™ MICROSLICE™ (bit-slice microprocessor

products), **Subsystems, Memory**

**Interface Logic, Digital Signal Processing Circuits** (multipliers, MACs, and FIFOs), and one of the fastest, broadest lines of **Static RAMs** in the world.

CEMOS and MICROSLICE are trademarks of Integrated Device Technology, Inc.

### Our Static RAM Family (available now)

Size	P/N	Worst Case Comm'l Speed
16Ks		
16Kx1	IDT6167A	25ns
4Kx4	IDT6168A	25ns
4Kx4	IDT71681A*	25ns
4Kx4	IDT71682A**	25ns
2Kx8	IDT6116A	35ns

64Ks		
64Kx1	IDT7187	35ns
16Kx4	IDT7188	35ns
16Kx4	IDT7198***	35ns
16Kx4	IDT71981*	35ns
16Kx4	IDT71982**	35ns

#### Dual Port Static RAMs

1Kx8	IDT7130 MASTER	55ns
2Kx8	IDT7132 MASTER	55ns
1Kx8	IDT7140 SLAVE	55ns
2Kx8	IDT7142 SLAVE	55ns

\* Separate I/O—outputs ON at write

\*\* Separate I/O—outputs 3-state at write

\*\*\* Extra OE and CS

Leading the CMOS Future




## Integrated Device Technology

Static RAM Division

3236 Scott Boulevard  
Santa Clara, CA 95054-3090  
(408) 727-6116  
TWX 910-338-2070



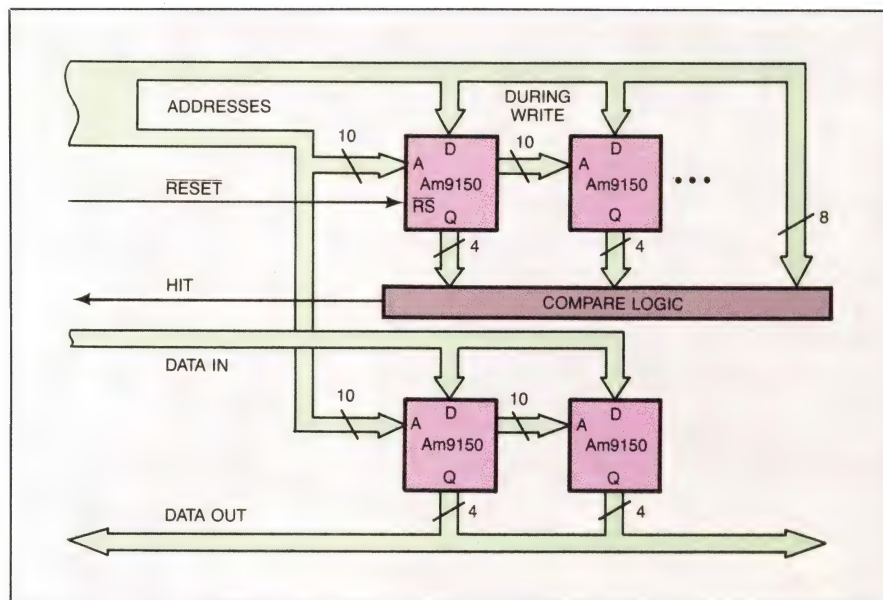

**Fig 2—A static RAM with a reset function—AMD's Am9150, for example—can serve as a tag buffer in a cache-memory system that requires initialization on context switches.**

The tag buffer requires initialization on context switches or other operations requiring major cache content changes. Without initialization, the cache controller may mistakenly determine that the cache contains a given address. The reset function allows the processor to clear the tag buffer without wasting the time required to zero each buffer location.

## Static RAM clears in 40 nsec

Advanced Micro Devices implements the clear function on the 1k×4-bit Am9150 static RAM. Fig 2 illustrates the use of AMD Am9150s in a cache application. An active signal applied to the reset pin will clear the RAM in 40 nsec. The device features separate I/O and a 20-nsec access time. It costs \$24.95 (100). Later in the year, AMD plans to implement the reset feature in higher-density memories.

When designing static RAMs with densities greater than 16k bits, manufacturers tend to concentrate more on speed and cost than on special features. Actually, manufacturers have only recently begun to ship fast 64k-bit static RAMs. Even so, the designs are maturing rapidly, and a few 64k-bit memories provide added features that reduce effective access times.

Manufacturers initially designed sub-35-nsec 64k-bit static RAMs with ×1 organizations, but parts with ×4 and ×8 organizations are starting to appear. Hitachi, for instance, initially offered only a part with a ×1 organization. The 64k×1-bit HM6787 was followed shortly by the 16k×4-bit HM6788.

## Mixed process smooths access

The two static RAMs cost approximately \$40 each (10,000) and employ Hitachi's Hi-BiCMOS process. This process mixes bipolar and CMOS technologies in a single IC. The RAM designs employ CMOS circuitry in the RAM array, and bipolar technology at the outputs contributes to the devices' 25-nsec

Most manufacturers spec the same access time for both types of read cycle, because they measure it from the last event that occurs, whether it's chip-select activation or address-line stabilization. In the first case, however, the access time will actually be longer, because the chip-select decoding time has been ignored.

Intel's 51C66 and the 51C69 furnish the same real access time regardless of the type of read cycle employed. When address stabilization is the last event, the static RAMs furnish a 25-nsec min access time. When the addresses stabilize before chip-select, however, the memories effectively hide the typical 10-nsec propagation delay associated with chip-select decoding, and they reduce the access time from chip-select to data-valid to 15 nsec.


Other fast static RAMs from Intel are the 16k×1-bit 51C67 and the 4k×4-bit 51C68. The parts spec 30-nsec access times and provide a low-voltage mode but not reduced chip-select access time. They cost \$16.25 and \$17.88 (100), respectively. All the Intel parts feature industry-standard pinouts.

Another special static-RAM fea-

ture that improves system or software performance is a reset pin for a clear function. The task of clearing a standard static RAM requires very little software, but a loop must execute once for every location in the RAM array. Even a memory as small as 4k bytes, with write cycle times of approximately 50 nsec, wastes 200 μsec when doing no more than writing zeros to memory. Communication and data-acquisition applications often require the clearing of much larger memory banks. Static RAMs with the reset capability clear the memory in one cycle.

Another application of the reset function, a tag buffer for cache memory, requires memory initialization on power-up, context switches, and other operations. The tag buffer stores information that refers to main-memory addresses that are mapped into the cache. When executing a given instruction, the processor produces a physical address, and the cache controller must determine if the address currently resides in the cache. The cache controller checks the tag buffer and fetches the required address from main memory if it does not already reside in the cache.





# BEFORE YOU BUY INTEL'S iSBC 86/35, CONSIDER THE STAKES.

You've made the right design decision.

But now you're ready to manufacture. And there's a lot at stake. Budgets. Delivery times. Ease of assembly. Profits.

So consider the 100% Intel-compatible ZBC 86/36, from Zitel.

First, the ZBC 86/36 costs 15%-30% less. Giving you an immediate advantage.

Then, there's our easy-to-manufacture PAL architecture. With only 30 configuration stakes. Not 300. So you'll reduce configuration errors, reduce labor costs, and save time.


And consider this: The ZBC 86/36 includes 1 Megabyte of on-board memory, an on-board socket for your 8087 math co-processor, and optional on-board parity checking. All in a single card slot. Plus a full 5-year warranty.

So call for a free evaluation unit. Or for more information on all our open bus products. (408) 946-9600.

Because there's more at stake than meets the eye.


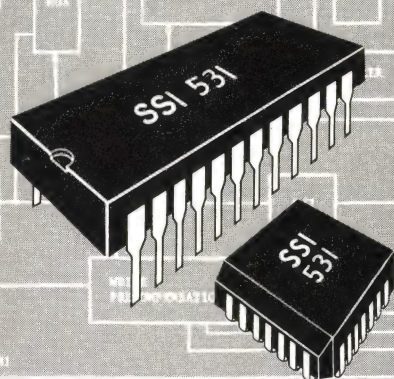
## NEW DATA SEPARATOR FOR MFM ENCODED SYSTEMS



### FEATURES:

- MFM and RLL data synchronization
- Ideal for operation with the WD1010/WD2010 controller family
- Fast acquisition PLL
- High performance 20MHz VCO
- Bipolar technology for precise bit cell control
- Crystal controlled reference oscillator
- Write Data precompensation
- No external delay lines or active devices required
- +5V operation
- 24 pin PDIP and 28 pin PLCC

The new SSI 531 Data Separator performs Read Data synchronization and Write Data precompensation for MFM encoded systems. The interface of the 531 has been optimized for use with the WD1010/WD2010 family of hard disk drive controller devices. Integrated into the unit is a high performance Phase Locked Loop (PLL) for data synchronization, a crystal-controlled reference oscillator for Write Data synchronization, and a write precompensator circuit that eliminates the requirement for an external delay line.

The 531 has been developed in an advanced bipolar process for precise bit cell control, resulting in reduced system sensitivity to bit jitter and superior error rate performance. It operates from the +5V power supply, and it is priced under \$10 in OEM production quantities.

For more information, contact: **Silicon Systems**, 14351 Myford Road, Tustin, CA 92680. (714) 731-7110, Ext. 575.



CIRCLE NO 18

## TECHNOLOGY UPDATE

access times. The static RAMs consume 300 mW when active and 20 mW in standby mode.

IDT currently offers the industry-standard 16k×4-bit IDT7188 and 64k×1-bit IDT7187 static RAMs, which spec 35-nsec access times and cost \$100 (100). The company also provides three variations to the standard 16k×4-bit design. The \$100 (100) IDT7198 includes an output-enable pin and an extra chip-select pin. The additional chip-select pin simplifies decoder circuitry. The IDT71981 and IDT71982 each cost \$100 (100); both provide separate I/O, and the former employs an output that tracks the input. Like IDT's 16k-bit static RAMs, the 64k-bit parts include a low-voltage mode.

### Cache tag adds compare logic

Around midyear, IDT plans to introduce some 8k×8-bit parts. One will be an industry-standard part, another (the IDT7165) will have a reset function, and a third (the IDT7174) will be a cache-tag device. The cache-tag part will include a reset function and a compare output for tag-buffer applications. The

initial offerings will feature 45-nsec min access times, but process tuning should quickly bring the access times down to 35 nsec.

Lattice's 64k-bit static-RAM family already includes 35-nsec ×8 ICs in addition to ×4 and ×1 parts. The \$37.50 SR64K1 is an industry-standard 64k×1-bit memory. The \$55 16k×4-bit choices include a standard SR64K4 part in a 22-pin package and the SR64E4 with output enable in a 24-pin package. The 8k×8-bit SR64K8 costs \$60 (1000).

Cypress plans to introduce two families of fast 64k-bit static RAMs in the second quarter. Each family will contain parts with the same organizations and features but slightly different process technologies. The CY7CXXX family will be a continuation to 64k bits of the company's 16k-bit CMOS static RAMs. The CY8CXXX family will implement Cypress's new BridgeMOS process, which employs CMOS cells with output drivers optimized for TTL or CMOS interfaces. All products in both families will feature 25-nsec access times.

The 64k-bit families will include members with ×1, ×4, and ×8 or-

## For more information . . .

For more information on the static RAMs discussed in this article, contact the following manufacturers directly or circle the appropriate numbers on the Information Retrieval Service card.

**Advanced Micro Devices Inc**  
Box 3453  
Sunnyvale, CA 94088  
(408) 732-2400  
Circle No 716

**Integrated Device Technology Inc**  
3236 Scott Blvd  
Santa Clara, CA 95052  
(408) 727-6116  
Circle No 720

**Visic Inc**  
1120 Ringwood Ct  
San Jose, CA 95131  
(408) 945-9991  
Circle No 724

**Cypress Semiconductor Corp**  
3901 N 1st St  
San Jose, CA 95134  
(408) 943-2600  
Circle No 717

**Intel Corp**  
151 Blue Ravine Rd  
Folsom, CA 95630  
(916) 351-2740  
Circle No 721

**Vitelco Corp**  
4701 Patrick Henry Dr,  
Suite 1301  
Santa Clara, CA 95054  
(408) 727-7256  
Circle No 725

**Hitachi America Ltd**  
2210 O'Toole Ave  
San Jose, CA 95131  
(408) 942-1500  
Circle No 718


**Lattice Semiconductor Corp**  
15400 NW Greenbrier Pkwy  
Beaverton, OR 97006  
(503) 629-2131  
Circle No 722

**Inmos Corp**  
Box 16000  
Colorado Springs, CO 80935  
(303) 630-4000  
Circle No 719

**Toshiba America Inc**  
2692 Dow Ave  
Tustin, CA 92680  
(714) 832-6300  
Circle No 723


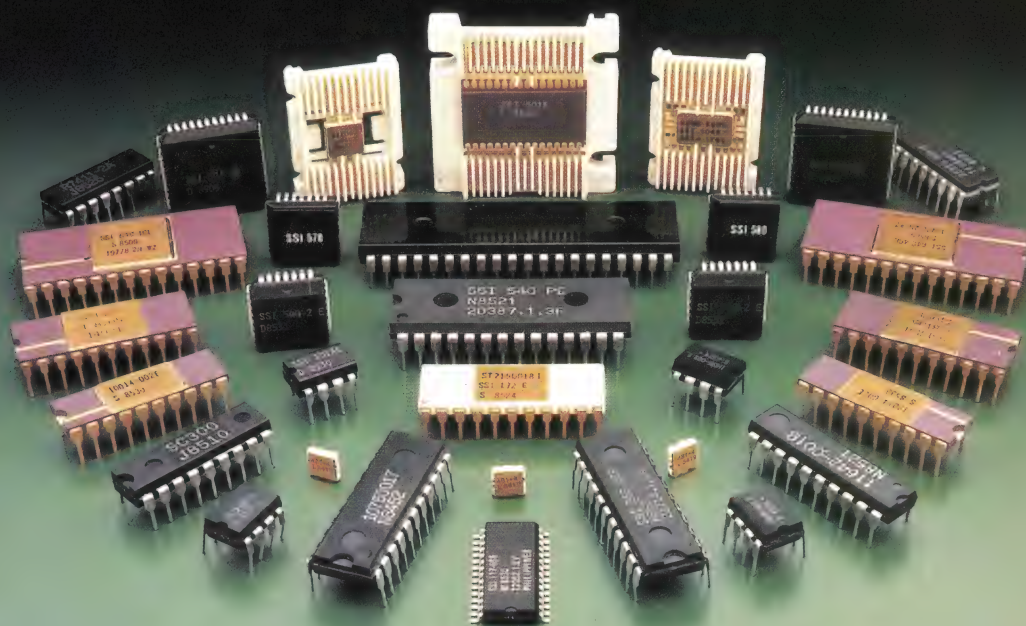
# IN TELECOM AND MICROPERIPHERAL ASIC's ONE COMPANY SHINES BRIGHTER— **SILICON SYSTEMS**



**N**o other company can offer you comparable lines of innovative VLSI standard IC's designed for telecom and microperipheral applications.

## **One-chip Telecom IC Solutions**

As the first company to fully integrate Touch-Tone™ receiver electronics onto a chip, Silicon Systems has gone on to develop a full-line of standard CMOS and Bipolar Telecom IC's incorporating analog, digital, and analog/digital designs on single chips. Today, SSI's broad line of telecom application-specific circuits covers Modems, T-1, Switching and Tone Signalling Products.

This fast-growing line of standard ASIC's also includes the industry's most complete selection of high performance Modem

IC's, DTMF Receivers, Transceivers, Call Progress Detectors, Crosspoint Switches, T1 Transmitter, Receiver and Transceivers. All are in CMOS with its inherent benefits of low power and optimized performance.

## **Microperipheral IC Solutions**

Silicon Systems also offers the industry's most complete selection of Hard Disk Drive Electronics. Beginning with our industry standard product line of Read/Write Amplifiers, the company continues to maximize the electronic integration of rotating memory systems. Additional product families now include IC's for Data Separation, Head Positioning, Read Data Processing, Motor Control and Support Logic.

Microperipheral IC solutions continue to

be extended into new applications including data conversion, graphics, and other interface product areas.

## **The Smart Solution**

Contact Silicon Systems today for your copy of the new Short Form Catalog that lists all of the company's Telecom and Microperipheral standard products. One of these standard CMOS or Bipolar products could be the smart solution to your specific design problem. If not, our design engineers, using leadership design automation tools, can tailor the optimum circuit for your custom requirements.

**Silicon Systems**, 14351 Myford Road, Tustin, CA 92680. (714) 731-7110.



Circle 9 for Career Information


Circle 48 for Product Information




# ULTRA STABLE VOLTAGE REFERENCES

HIGHEST ACCURACY  
IN INDUSTRY

Example: VRE102MA

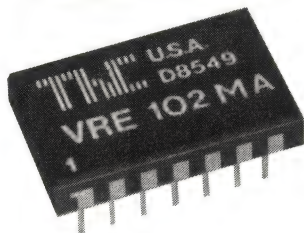

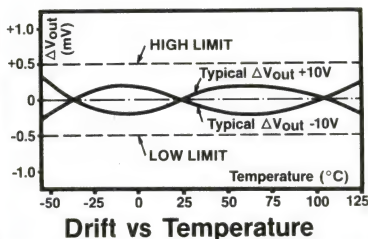- Output:  $\pm 10\text{VDC}$
- Initial Tolerance:  $\pm 0.8\text{mV}$
- TC:  $\pm 0.5\text{ppm}/^\circ\text{C max}$   
( $-55$  to  $+125^\circ\text{C}$ )
- Time Stability:  $6\text{ppm}/1000\text{ hrs.}$
- Warm-up Drift:  $3\text{ppm typ.}$
- Hermetic 14 Pin Ceramic DIP
- Industry Standard Pinout
- MIL-STD-883C Screening
- Line Regulation:  $3\text{ppm/V typ.}$



FOR INFORMATION CALL:  
**(602) 742-5572**

Choose from 12 models  
each available in 2  
military and  
commercial grades.  
Military grades screened  
to MIL-STD-883C.

**THALER  
CORPORATION**  
10940 N. Stallard Place  
Tucson, Arizona 85704  
(602) 742-5572  
Telex: 825193  
CIRCLE NO 19

## TECHNOLOGY UPDATE

ganizations. The  $16\text{k}\times 4\text{-bit}$  variations will include versions with an output-enable function, with separate I/O, and with separate I/O and a transparent-write function. The  $8\text{k}\times 8\text{-bit}$  memory will come in a 28-pin, 300- or 600-mil-wide package. Prices for the industry-standard CY7CXXX parts will range from \$40 to \$85 for the  $64\text{k}\times 1\text{-bit}$  CY7C187 and from \$60 to \$125 (1000) for the  $8\text{k}\times 8\text{-bit}$  CY7C186.

Prices for the CY8CXXX BridgeMOS family will typically be 15 to 25% greater than prices for the CMOS parts. The BridgeMOS process renders the RAMs compatible with different logic families. Some standard CMOS static RAMs sacrifice optimum CMOS drive capabilities to remain TTL compatible. The BridgeMOS static RAMs maintain TTL compatibility and drive CMOS circuits from rail to rail.

### Parity added in $\times 9$ static RAM

Toshiba will introduce a byte-wide  $64\text{k-bit}$  part before it introduces  $64\text{k-bit}$  static RAMs with other organizations. The company's first 35-nsec offering will actually be a  $72\text{k-bit}$  static RAM with an  $8\text{k}\times 9\text{-bit}$  organization. The TMM2089 reflects Toshiba's plans to migrate from  $\times 8$  to  $\times 9$  organizations for all byte-wide static RAMs.

Consumers of commodity static RAMs have been begging for a parity bit in high-density parts. Because JEDEC standards for byte-wide static RAMs leave an open pin, Toshiba's  $\times 9$  parts can supply the parity bit and still maintain compatibility with industry standards. Users requiring only eight bits can leave one data bit unconnected. The ninth bit increases cost because of an increase in the size of the silicon array. Toshiba believes, however, that by not building distinct  $\times 8$  and  $\times 9$  parts, higher manufacturing volumes will offset the cost difference.

The TMM2089 will cost \$35 (100), and the company plans to have samples available in this quarter. The

company also plans to have samples of two 25-nsec  $16\text{k}\times 4\text{-bit}$  CMOS static RAMs in the third quarter. The TC55416 with common I/O and the TC55417 with an output-enable pin will both cost approximately \$28 (100).

As fast static RAMs move into the applications once reserved for ECL devices, so will improved dynamic RAMs take over some traditional static-RAM applications. Designers have preferred static RAMs because of speed advantages, but dynamic-RAM manufacturers have implemented such special modes as the nibble mode and static-column addressing to lower access times to the 50-nsec range.

Dynamic RAMs also cost less than static RAMs, though the former require refresh circuitry. When memory requirements are small, the attendant refresh circuitry can be as costly as the memories themselves. For large amounts of memory, however, the cost of refresh circuitry is distributed over many parts, and the advantage of dynamic RAMs emerges.

Another threat to the traditional static-RAM realm is Visic's hierarchical RAM (HRAM) family, the members of which spec 35-nsec access times. Visic expects that, by midyear, the  $64\text{k}\times 1\text{-bit}$  V64H1 and the  $16\text{k}\times 4\text{-bit}$  V1HH4 will cost less than \$20 (1000). All HRAMs feature 25-nsec static-column access times, and the  $\times 1$  part includes a 4-bit snap mode with 10-nsec read cycles (the snap mode is similar to the nibble mode in a dynamic RAM). The company also recently introduced the \$30  $8\text{k}\times 9\text{-bit}$  V8K9 HRAM, which has a built-in parity checker. Like the dynamic RAM, the HRAM requires refresh circuitry, but it still can compete in static-RAM markets.

**EDN**

Article Interest Quotient  
(Circle One)  
High 500 Medium 501 Low 502



# Picture this on a \$2,500 CAD program.

When Ultracam Incorporated set out to design the Ultracam™ K35, they knew that their design tool needed to be as professional as the camera they were designing. That's why they chose AutoCAD™ the most widely used computer-aided design and drafting tool in the world today.

## Mainframe CAD Capability at 5% of the Price

If you have an IBM PC, PC/XT, PC/AT, NEC, DEC, TI, Tandy, Wang, or one of over 30 desktop computers AutoCAD supports, you already own the most expensive part of a CAD system. Add AutoCAD for only \$2500 more, and you can have the power of CAD on your desktop at a price you can afford. With a pointing device and a plotter (the choice is yours, we support over 50 popular peripherals,) you can assemble a complete CAD workstation for less than \$10,000.

Once you've installed AutoCAD on your computer, you'll have a tool at your fingertips which removes the drudgery from designing.

## Quick to Learn, Easy to Use

The beauty of AutoCAD is that you need no prior knowledge of computers. Even if you've never seen a CAD system, you'll pick it up in a matter of days, and feel comfortable within a week.

Simple pop-up menus point you in the right direction. You can also easily create your



own menus. On-line HELP keeps you on track.

## Sailboats, Landscapes, and Custom Homes

Since AutoCAD is general-purpose and user-customizable, it doesn't matter what type of drafting your work requires.

Ultracam K35 is a trademark of Ultracam Incorporated. AutoCAD, CAD/camera and AE/CADD are trademarks of Autodesk Inc.



Camera designs provided courtesy of Ultracam Incorporated.

Tens of thousands of AutoCAD users are creating drawings and developing designs in every discipline with ease and accuracy never experienced before.

## The Heart of Your CAE System

Drawings are only part of the story. Pre-defined standard symbols, translators to allow AutoCAD to exchange drawings with mainframe CAD systems, data base analysis programs for bill of material lists, job costing and drawing distribution by telephone are only some of the capabilities available with AutoCAD. These capabilities make AutoCAD the central component in your desktop computer-aided engineering (CAE) system.

Whether you're in a two-person shop or a two-billion dollar company, you'll find that AutoCAD pays for itself in just a few months.

In the future, AutoCAD will run on newer, more powerful computers as they become available—so that you can be sure your investment in creating drawings and training staff won't be wasted.

## Powerful New Capabilities

Call or write us today for the name of the dealer nearest you and a demonstration of the latest in AutoCAD capabilities, including polylines, curves, and 3D visualization with hidden line removal. Also ask about other cost-effective Autodesk products: AE/CADD™ and CAD/camera™.

AutoCAD, world leader in design and drafting software, will save you time and money.



# AUTOCAD™

AUTODESK, INC.

2320 MARINSHIP WAY  
SAUSALITO, CA 94965

(415) 331-0356


or (800) 443-0100 EXT. 406

TELEX 275946 ACAD UD

CIRCLE NO 124


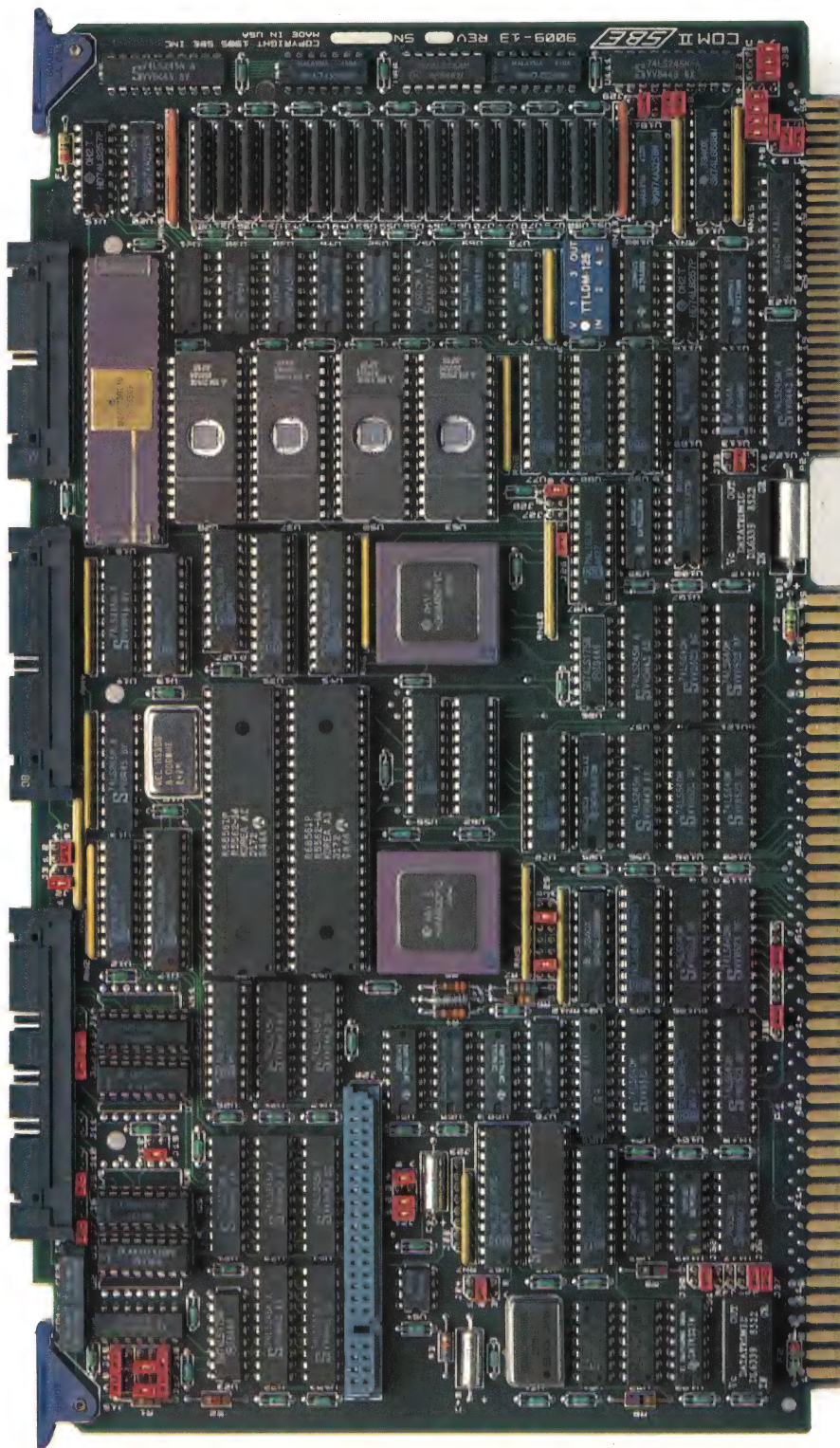
# Faster data communications. 4 million bps. \$1240.



A sizzling 4 million bps. Full duplex communications on two serial ports.


That's faster than the T1 rate. Fast enough to transfer massive blocks of data in a few seconds.

Our COM-2 board gets that speed from a 68000 CPU plus a 4-channel DMA controller running at 10 MHz. It's a Multibus\* card, and it costs only \$1240 in lots of 100.

Choose any interface. Either RS-232 or RS-422 on board. Or a miniature off-board module with a choice of RS-423, RS-449, fiber optics or direct-connect modem. Or your own custom interface.

You get 128K of dual-ported, parity-protected dynamic RAM on board, expandable to 512K. And the 68000 accesses all that memory at 10 MHz with no wait states.

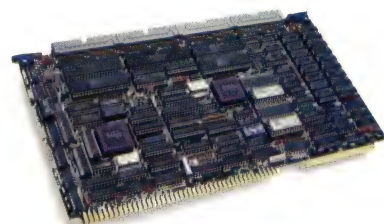To satisfy a wide variety of needs, we've included a 16-bit iSBX connector, a 24-bit parallel port, and sockets for 256K of EPROM.



**Our communications family includes the COM-8. Eight channels. 800,000 bps.**

We back up our boards with in-depth technical support. Because only when you succeed do we succeed.

We're SBE, Inc., 2400 Bisso Lane, Concord, CA 94520. TWX 910-366-2116. (Answerback: SBE CNCD)

Phone free 1-800-221-6458 for literature mailed today. In California call 1-800-328-9900 or (415) 680-7722.

CIRCLE NO 125

**SBE, INC.**

Microcomputer boards and systems.

\*Multibus is a trademark of Intel.

See us at the Electro-Mini Micro Show  
Booth #2521



## Digitizing tablets offer choices of formats, operating modes, and pointers

Jon Titus, *Senior Editor*

Whether you're digitizing schematic diagrams, data plots, mechanical drawings, or a 3-dimensional shape, you can choose from a variety of digitizing tablets, pointing devices, and output formats to fit your needs. Nevertheless, you must consider the resolution and accuracy necessary for your application as well as hardware and software compatibility—for after all, tablets transfer their data to computers.

Digitizing tablets—most of which are 2-dimensional—use electrical fields, sounds, or resistances to locate a point on a flat surface and convert it to a set of X and Y coordinates that a computer program can process. To digitize graphic information, you mount a drawing, schematic diagram, or other graphic information on the tablet's work surface and move a stylus from point to point. After moving the stylus to a new point, pressing a button causes the digitizer to output the point's X and Y coordinates.

To decide what type of digitizer your application will require, consider the information you're digitizing, and thus the resolution you'll need. For instance, digitizing fine lines on a scaled mechanical drawing requires more resolution than digitizing general building locations on a map. Typical resolutions range from 100 to greater than 1000 lpi, or from 0.010 in. to less than 0.001 in. Tablets in Summagraphics' MM Series, for example, let you preset a resolution that ranges from 100 to as many as 1000 lpi. Thus, programs can select the resolution that best suits specific digitizing needs.

A tablet's accuracy specification lets you know how well it locates the actual coordinates of a point on its surface. The amount of accuracy you get depends on how much money you're willing to spend. Tablets under \$1000 provide an accuracy of about  $\pm 0.025$  in., whereas more expensive tablets offer accuracies as great as  $\pm 0.003$  in. (Table 1).

Of course the price you'll pay

doesn't just hinge on the accuracy you specify: You'll also confront many tablet sizes, mounting styles, and options. Tablets range from 6×6 in. to greater than 60×72 in. You can buy tablets that sit on desk tops, have their own floor stands, mount on walls, or fit in desk-top cutouts.

Most digitizers provide either opaque or translucent work sur-



*If you have a clear tablet, you can place it over artwork or other data for digitizing. For example, you can use this Scriptel tablet over a CRT screen to digitize graphic data accurately or to make menu selections.*



# TECHNOLOGY UPDATE

**TABLE 1—REPRESENTATIVE DIGITIZING TABLETS**

MANUFACTURER	MODEL	SIZE RANGE (IN.)	RESOLUTION	ACCURACY	INTERFACE	DIAGNOSTICS	POINTERS
ALTEK	DATATAB	12x12 TO 42x130	0.001 IN.	± 0.01 TO ± 0.003 IN.	RS-232C	YES	STYLUS CURSOR
ARISTO GRAPHICS	SERIES-200	20x20 TO 40x60	0.001 IN.	± 0.001 IN.	RS-232C	YES	STYLUS CURSOR
CALCOMP	2200 SERIES	12x12 AND 12x18	200 LPI	± 0.025 IN.	RS-232C	NO	STYLUS CURSOR
	9100 SERIES	17x24 TO 44x60	1279 LPI OR 50 LINES/mm	± 0.01 IN.	RS-232C IEEE-488	NO	STYLUS CURSOR
COMPUTER TALK	MODEL 600	TO 8x10 FT	0.01 TO 0.001 IN.	± 0.01 TO ± 0.005 IN.	RS-232C	YES	CURSOR
GTCO	TYPE 5A	11x11 TO 42x60	0.001 IN. OR 0.025 mm	± 0.01 TO ± 0.003 IN.	RS-232C	YES	STYLUS CURSOR
HEWLETT-PACKARD	9111A	8.6x11.8	0.10 mm	± 0.6 mm	IEEE-488	NO	STYLUS
HITACHI	HDG SERIES	11x11 TO 44x60	0.001 IN.	± 0.01 TO ± 0.005 IN.	RS-232C IEEE-488 PARALLEL TTL	YES	STYLUS CURSOR
HOUSTON INSTRUMENT	SERIES-1000	5x5 TO 11x17	0.005 IN.	± 0.015 IN.	RS-232C	YES	CURSOR
	SERIES-8000	11x11 TO 24x36	0.001 IN.	± 0.01 IN.	RS-232C	YES	CURSOR
MICRO CONTROL SYSTEMS	PERCEPTOR	40x31x38	0.007 TO 0.010 IN.	0.007 TO 0.02 IN.	RS-232C	NO	STYLUS
NUMONICS	2200 SERIES	6x6 TO 36x48	0.001 IN. OR 0.025 mm	± 0.01 TO ± 0.005 IN.	RS-232C IEEE-488 PARALLEL TTL	YES	STYLUS CURSOR
SCIENCE ACCESSORIES	GP-7	18x24 20x26	0.01 IN. OR 0.01 cm	± 0.01 IN. OR ± 0.01 cm	RS-232C PARALLEL TTL	NO	STYLUS CURSOR
	GP-8	24x24 TO 60x72	0.01 IN. OR 0.01 cm	± 0.01 IN. OR ± 0.01 cm	RS-232C PARALLEL TTL	NO	STYLUS CURSOR
	GP-8-3D	10x10x10 FT	0.01 IN. OR 0.01 cm		RS-232C PARALLEL TTL	NO	STYLUS
SCRIPTEL	SPD SERIES	12x12 TO 24x36	0.001 IN.	± 0.025 IN.	RS-232C PARALLEL TTL	YES	STYLUS CURSOR
SUMMAGRAPHS	MM SERIES	6x9 TO 11.7x11.7	0.001 IN.	± 0.025 IN.	RS-232C	YES	STYLUS CURSOR
	MICROGRID	20x20 TO 42x60	0.001 IN.	± 0.010 IN.	RS-232C IEEE-488 PARALLEL TTL	YES	STYLUS CURSOR
TEKTRONIX	TEK-4957	11x11	0.001 IN.	± 0.025 IN.	RS-232C	YES	STYLUS CURSOR
	TEK-4958	17x24 TO 36x48	0.001 IN.	± 0.01 IN.	RS-232C	YES	STYLUS CURSOR

faces. You can also buy backlit tables that light negatives, x-rays, film drawings, and other transparent or translucent media. Scriptel Corp's SPD Series tablets feature a clear position-sensing layer in a transparent glass carrier. Unlike opaque tablets, you can position the SPD Series tablets over original material you want to digitize. You can also put the tablet on a light table or over a display screen to digitize data.

All digitizing tablets provide an origin for the X and Y coordinates. Tablets like the Numonics Model 2200 let you move the origin to any point on the tablet's work area. A programmable origin lets you set a consistent starting point for each digitizing task. The Summagraphics MM Series and the Hitachi HDG Series tablets let you fix the origin at one of two adjacent tablet corners. Thus, you can maintain the same coordinate orientation when

you rotate the tablet 90°.

Once you've set a tablet's origin, you trace lines or locate points with a stylus. Pressing a button on the stylus sends your computer the point's X and Y coordinates. You can select a plain stylus point or one with a pen in it. The pen marks the points and lines you've digitized. Pen points are replaceable and interchangeable with nonmarking points. Because stylus tips aren't very fine, the points you locate with



# TECHNOLOGY UPDATE

	ORIGIN RELOCATION	OUTPUT MODES					BASE	NOTES	PRICE
		POINT	STREAM	INCREMENT	SWITCHED STREAM	POLLED			
	YES	•	•	•	•	•	OPAQUE BACKLIT	CHOICE OF TWO CONTROLLERS	\$4000 FOR 36x48 IN.
	NO	•	•	•		•	OPAQUE	RS-423 OPTIONAL INTERFACE	FROM \$11,000
	NO	•	•		•		OPAQUE		FROM \$695
	NO	•	•	•	•	•	OPAQUE BACKLIT	REAR PROJECTION RS-449	FROM \$3800
	YES	•					OPAQUE BACKLIT	TABLETS CUSTOM BUILT TO CUSTOMER SPECIFICATIONS	FROM \$2500
	NO	•	•	•			OPAQUE		FROM \$995
	NO	•	•				OPAQUE BACKLIT	MENU MODE	FROM \$2275
	YES	•	•	•	•	•	OPAQUE BACKLIT	TWO ORIGIN POSITIONS	FROM \$973
	YES	•	•	•	•	•	OPAQUE	TWO ORIGIN POSITIONS	FROM \$495
	YES	•	•	•	•	•	OPAQUE		FROM \$1150
	NO	•	•	•		•	N/A	5 POINTS PER SECOND 3 DIMENSIONAL	\$9500
	YES	•	•	•	•	•	OPAQUE	MENU MODE	FROM \$859
	YES	•	•		•	•	N/A	ANY FLAT SURFACE	FROM \$1000
	YES	•	•		•	•	N/A	ANY FLAT SURFACE	FROM \$1000
	NO	•	•			•	N/A	3 DIMENSIONAL	FROM \$7500
	YES	•	•	•	•	•	CLEAR	CLEAR BASE	FROM \$1095
	YES	•	•	•	•	•	OPAQUE	TWO ORIGIN POSITIONS	FROM \$999
	YES	•	•	•	•	•	OPAQUE		FROM \$2524
	YES	•	•	•	•	•	OPAQUE	MENU MODE	\$995
	NO	•	•				OPAQUE	MENU MODE	FROM \$4500

them may not give you the accuracy you need or expect from your tablet.

To increase your measuring accuracy, you can use a handheld cursor or puck, which you move across the digitizer's surface. The cursor contains a reticle and at least one push-button. The reticle's fine cross hairs help you accurately locate each point for digitizing. Pressing the cursor's button sends the coordinates at the cross hairs to the computer. Depending on your soft-

ware's capabilities, and the number of available buttons on the cursor, you can assign each button a specific command or operation. For example, you can use the buttons to let the computer know whether you're digitizing points or selecting alphanumeric font sizes or electronic symbols.

## Serial formats aren't standard

Almost all digitizing tablets communicate with host computers

through standard RS-232C I/O ports. Keep in mind, however, that the RS-232C specification defines the signal lines, not the data's format. Most manufacturers let you select either an ASCII or a packed-binary data format for the X-Y-coordinates and the pushbutton information the tablet sends to the computer. Nonetheless, ASCII and packed-binary data formats vary from manufacturer to manufacturer, so before you select a tablet that



(a) $X_1 X_2 X_3 X_4 X_5 Y_1 Y_2 Y_3 Y_4 Y_5$ PB CR LF
(b) PB SG $X_1 X_2 X_3 X_4 X_5$ SP SG $Y_1 Y_2 Y_3$ $Y_4 Y_5$ CR LF
(c) $X_1 X_2 X_3 X_4 Y_1 Y_2 Y_3 Y_4$ SB CR LF*

PB = PUSHBUTTON-STATUS BYTE  
 SG = SIGN BYTE  
 SB = STATUS BYTE  
 SP = SPACE  
 CR = CARRIAGE RETURN  
 LF = LINE FEED  
 \* LINE-FEED BYTE OPTIONAL

**Fig 1—Digitizing tablets output ASCII transmissions that vary from manufacturer to manufacturer. The Scriptel SPD format (a) supplies 13 data bytes, whereas the Numonics format (b) supplies 16 bytes. Calcomp's 2200 Series tablets (c) let you select a 10- or an 11-byte format.**

otherwise meets your needs, be sure your software accepts the tablet's data format.

For example, if your software operates with coordinates sent in Scriptel's SPD ASCII format, the computer expects to receive 10 X-Y-coordinate bytes and subsequent pushbutton-status, carriage-return, and line-feed bytes (Fig 1). The software won't operate properly if you send the computer data from a Calcomp 2200 Series digitizer. The Calcomp unit transmits only eight X-Y-coordinate bytes, followed by status, carriage-return, and line-feed bytes.

A packed-binary format requires fewer bytes for RS-232C transmissions, but again packed-binary data formats vary (Fig 2). A few manufacturers offer parallel TTL or IEEE-488 interfaces instead of an RS-232C port. If you can't easily reconfigure your software for a particular data format or I/O interface specification, check the software's documentation for a list of compatible tablets.

To help you circumvent the data-compatibility problem, Scriptel's SPD Series tablets let you select, under software control, any one of 13 common data formats. Likewise, Hewlett-Packard furnishes an extensive set of support hardware and

CALCOMP BINARY FORMAT									
BIT									
	7	6	5	4	3	2	1	0	
1	P	1	D	C	B	A	0	0	
2	P	0	$X_5$	$X_4$	$X_3$	$X_2$	$X_1$	$X_0$	
3	P	0	$X_{11}$	$X_{10}$	$X_9$	$X_8$	$X_7$	$X_6$	
4	P	0	$Y_5$	$Y_4$	$Y_3$	$Y_2$	$Y_1$	$Y_0$	
5	P	0	$Y_{11}$	$Y_{10}$	$Y_9$	$Y_8$	$Y_7$	$Y_6$	

P = PARITY  
 A,B,C,D = PUSHBUTTONS

NUMONICS BINARY FORMAT									
BIT									
	7	6	5	4	3	2	1	0	
1	1	PS	$B_8$	$B_4$	$B_2$	$B_1$	$X_{15}$	$X_{14}$	
2	0	$X_{13}$	$X_{12}$	$X_{11}$	$X_{10}$	$X_9$	$X_8$	$X_7$	
3	0	$X_6$	$X_5$	$X_4$	$X_3$	$X_2$	$X_1$	$X_0$	
4	0	0	0	0	0	0	$Y_{15}$	$Y_{14}$	
5	0	$Y_{13}$	$Y_{12}$	$Y_{11}$	$Y_{10}$	$Y_9$	$Y_8$	$Y_7$	
6	0	$Y_6$	$Y_5$	$Y_4$	$Y_3$	$Y_2$	$Y_1$	$Y_0$	

PS = PEN DEPRESSED OR SWITCH  
 0 ACTIVE  
 $B_N$  = PUSHBUTTON BINARY CODE

SCRIPTEL BINARY FORMAT									
BIT									
	7	6	5	4	3	2	1	0	
1	1	0	0	0	$B_4$	$B_3$	$B_2$	$B_1$	
2	0	0	0	0	0	SG	$X_{15}$	$X_{14}$	
3	0	$X_{13}$	$X_{12}$	$X_{11}$	$X_{10}$	$X_9$	$X_8$	$X_7$	
4	0	$X_6$	$X_5$	$X_4$	$X_3$	$X_2$	$X_1$	$X_0$	
5	0	0	0	0	0	SG	$Y_{15}$	$Y_{14}$	
6	0	$Y_{13}$	$Y_{12}$	$Y_{11}$	$Y_{10}$	$Y_9$	$Y_8$	$Y_7$	
7	0	$Y_6$	$Y_5$	$Y_4$	$Y_3$	$Y_2$	$Y_1$	$Y_0$	

$B_N$  = PUSHBUTTON DATA BITS  
 SG = SIGN BIT

**Fig 2—Packed-binary data formats for tablets offer faster transmission speeds than ASCII formats. However, manufacturers' formats differ.**

software that links its Model 9111 digitizer and HP computers over an IEEE-488 bus. However, before you can use the 9111A tablet with non-HP computers that support an IEEE-488 interface, you must develop your own driver routines.

## Tablets offer menu selections

Although users most frequently employ tablets to digitize graphic information, you can also use a tab-


let to select menu items. For this task, you won't need high accuracy or resolution: The computer simply needs to know you're pointing to a selection within a defined area.

You have two ways of selecting menu items. You can use the cursor like a mouse, moving a pointer on the computer's display screen, or you can use the cursor to select items from a printed menu on the tablet's work surface. One advantage of using printed tablet menu items is that you can see all the selections at once, without switching between screen menus.

Thus, although tablets add to the cost of a computer system, they provide convenience and they don't obscure information on a monitor screen. The Numonics Model 2200 digitizer lets its host computer configure a set of menu-cell spaces in the work area. Likewise, you can specifically configure Tektronix's TEK-4957 tablet to operate in a menu-selection mode.

Besides letting you select menu-type operations, many tablets also let you select different types of data-output operations. Depending on your tablet, you can select point, stream, switched-stream, polled, and incremental operations.

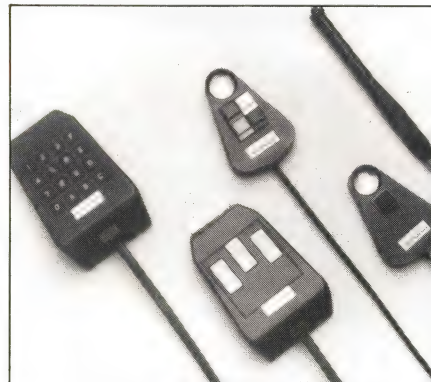In the point mode, you locate each point with the stylus or cursor and press a button to send the coordinates to the computer. When it's in



**Different types of digitizer pointing devices let you select one that best meets your needs. Houston Instrument's multibutton cursors let you control computer operations from your tablet's surface without forcing you to use the computer's keyboard.**



# VERSATEC SPECTRUM. THE WORLD'S MOST VERSATILE COLOR HARD COPY DEVICE.

The Versatec Spectrum electrostatic plotter/printer does it all. Plots A (11" x 8½") and B (11" x 17") page drawings. Plots in full color or black and white. Prints software listings, parts lists, reports, or other alphanumeric printing with a built-in character generator at 1000 lines per minute. Produces hard copies direct from monochrome or color displays with an optional video interface that includes a frame-buffer. And all at a lower cost per copy than other technologies.

Here is the trouble-free throughput you need. Plot. Print. Make copies from your local workstation. Use as a network plot server and for unattended remote applications. Only Versatec Spectrum automatically

handles any mix of A- and B-size, color and monochrome, graphics and text. No need for an operator to change donor rolls, pens, or input paper sizes. And you can run over 300 pages without changing paper. Interfaces and software are available for popular computers, workstations, and terminals.

Get support from the leader. Versatec, the leader in electrostatic plotting, assures customer satisfaction with worldwide service and supplies.

Discover Versatec Spectrum, the world's most versatile color hard copy device. For more information, circle the readers' service number, call toll-free 800/538-6477\*, or visit your nearby Versatec sales office.



2710 Walsh Avenue  
Santa Clara, California 95051  
Telephone: (408) 988-2800  
TWX: 910-338-0243  
Telex: 334421

Versatec and Spectrum are trademarks of Versatec, Inc. Xerox is a trademark of Xerox Corporation.

\*In California, call toll-free 800/341-6060.

**It's a Versatec.**  
CIRCLE NO 126





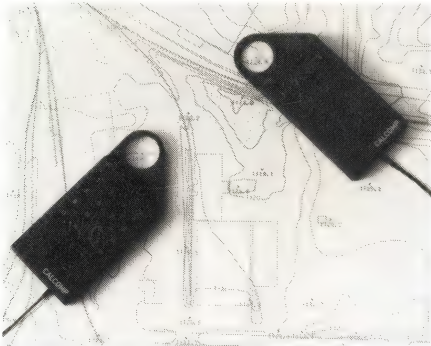
# TECHNOLOGY UPDATE

the stream mode, a tablet continuously transmits the cursor's coordinates to the computer. However, when you select the switched-stream mode, the tablet transmits the coordinate stream only for as long as you continue pressing the cursor's pushbutton.

In the polled mode, the tablet lets the computer's software request specific information about the cursor's location and the pushbut-



*A cursor's cross hairs let you accurately locate points on your artwork. A cursor offers better resolution than a stylus with a blunt pointer. Calcomp's cursors provide four or 16 pushbuttons and four indicators.*

tons' status. The incremental mode sets a dead zone around the cursor. The tablet sends the computer new position information only after the



*You can digitize 3-dimensional objects by using Micro Control Systems' Perceptor. A captive stylus controls potentiometers that provide 3-D coordinates to a computer. The digitizing volume is 20,000 in.<sup>3</sup>*

cursor moves outside the dead zone.

Because almost all digitizers are tied to a fixed electrically active base, their use is limited in some applications. In contrast, however, Science Accessories Corp's GP-7 and GP-8 sonic digitizers require only a flat surface and thus can serve special needs. For example, at Boeing Aircraft Corp, a GP-8 digitizer sits on a wiring-harness layout table and transmits connector and termination locations to a computer.

Instead of the tablet's base being electrically coupled to its cursor or stylus, a sonic digitizer uses a set of microphones to generate coordinates for the sound source in the stylus. The GP-7 digitizer module sits behind your graphic material and provides an 18×24-in. or 20×26-in. active work area. A narrow L-shaped case houses the GP-8 digitizer, which positions sensors along your work area's length and width. Standard work areas for the GP-8 range from 20×20 in. to as large as 60×70 in.

Also, because sonic digitizers don't depend on proximity to a special work surface, they can digitize 3-dimensional objects. However, such digitizers require extra microphones and control circuits. Science Accessories Corp's 3-dimensional digitizer operates within a 20×20×20-ft volume, providing a resolution of 0.01 in.

Micro Control Systems Inc also sells a 3-dimensional digitizer, Perceptor, but it has a different digitizing approach. Instead of using a freely moving sonic stylus, you locate points on an object's surface with a captive stylus. Potentiometers within the Perceptor's five mechanical joints let an internal microprocessor compute 3-dimensional Cartesian coordinates. **EDN**

## For more information . . .

For more information on the digitizing tablets described in this article, circle the appropriate numbers on the Information Retrieval Service card or contact the following manufacturers directly.

**Altek Corp**  
2150 Industrial Parkway  
Silver Spring, MD 20904  
(301) 622-3906  
Circle No 701

**Aristo Graphics Corp**  
5 Emery Ave  
Randolph, NJ 07869  
(201) 366-7000  
Circle No 702

**Calcomp**  
2411 W La Palma Ave  
Anaheim, CA 92801  
(714) 821-2000  
Circle No 703

**Computer Talk Inc**  
Box 148  
Morrison, CO 80465  
(303) 697-5485  
Circle No 704

**GTCO Corp**  
1055 First St  
Rockville, MD 20850  
(301) 279-9550  
Circle No 705

**Hewlett-Packard**  
Box 10301  
Palo Alto, CA 94303  
Phone local office  
Circle No 706

**Hitachi America Ltd**  
950 Benicia Ave  
Sunnyvale, CA 94086  
(408) 773-8833  
Circle No 707

**Houston Instrument**  
Box 15720  
Austin, TX 78761  
(512) 835-0900  
Circle No 708

**Micro Control Systems Inc**  
27 Hartford Tpk  
Vernon, CT 06066  
(203) 647-0220  
Circle No 709

**Numonics Corp**  
418 Pierce St  
Lansdale, PA 19446  
(215) 362-2766  
Circle No 710

**Science Accessories Corp**  
970 Kings Hwy W  
Southport, CT 06490  
(203) 255-1526  
Circle No 711

**Scriptel Corp**  
4145 Arlingate Plaza  
Columbus, OH 43228  
(614) 276-8402  
Circle No 712

**Summagraphics Corp**  
Box 781  
Fairfield, CT 06430  
(203) 384-1344  
Circle No 713

**Tektronix Inc**  
Box 500  
Beaverton, OR 97077  
(503) 627-7111  
Circle No 714

Article Interest Quotient  
(Circle One)

High 503 Medium 504 Low 505



# Logic Analysis System LAS



## Full house

With the Logic Analysis System LAS you always have a strong card in your hand. The modular design of the LAS affords optimal configuration for your measurement. The LAS with seven options and  $\mu$ P probes to match all standard microprocessors is counted amongst the best of logic analysis systems.

### 8-bit $\mu$ P probes:

8080; 8085/NSC 800; Z80; 6502;  
6800/02/08; 6809/09E; 8031/51

### 16-bit $\mu$ P probes:

8086/88; 80186/88; 68000

### Ethernet test probe

Ask for the detailed brochure **Info LAS**

CP/M-86 operating sy  
Floppy drive  
Basic postprocessing  
256 Kbyte RAM  
Real-time clock  
RS 232 C, IEEE 488

Event-timing analysis

Rohde & Schwarz GmbH & Co. KG  
Postfach 80 14 69  
D-8000 Muenchen 80  
Federal Republic of Germany  
Telex 523 703 (rus d)  
Tel. internat. + (49 89) 41 29-0

CIRCLE NO 43



**ROHDE & SCHWARZ**



# NEWS FROM PHILIPS

INTEGRATED CIRCUITS □ SEMICONDUCTORS □ ELECTRON TUBES □ COMPONENTS □ ASSEMBLIES □ MATERIALS

## COMPUTER-CONTROLLED CONNECTOR CIRCUIT CUTS CABLE CHANGE-OVERS



As part of our total computer-controlled television concept, we are supplying a versatile switching circuit for use with a peritelevision connector as specified by CENELEC. The TDA8440 offers flexibility and low-distortion performance unobtainable in discrete solutions. By performing peritelevision connector switching functions to select signal source under control of a microcontroller, the bipolar IC eliminates manual interchanging of cordsets at the rear of a display unit or tv set. Although communication is normally via the two-line serial I<sup>2</sup>C bus, non-I<sup>2</sup>C bus control is also possible. The circuit can also be controlled by the d.c. level on the function switching pin of the peritelevision connector.

The TDA8440 can select one of two video signals together with their stereo/dual sound channels. An off position can also be selected so that the input signal can be derived from another TDA8440. The circuit has two three-state switches for audio channels and one three-state switch for the video channel. There is a video amplifier with a selectable gain of one or two. Expansion up to seven devices is possible. Minimum crosstalk attenuation for video switching is 60 dB and total harmonic distortion for the audio channel is maximum 0,1 %. The 18-pin IC operates from a supply voltage of 10 to 13,2 V and requires a maximum unloaded supply current of 50 mA. The operating ambient temperature range is 0 to 75 °C.

CIRCLE 1


## PHONE PERIPHERAL POWER SUPPLY PROVIDES FRESH APPLICATION POSSIBILITIES

We are introducing a completely new concept to line-powered electronic telephone sets in the form of an integrated circuit which provides a power supply for peripherals such as extended dialling and/or loudspeaking facilities. The TEA1080 improves the performance of electronic telephone sets by eliminating disturbances/distortion caused when peripherals are powered directly from the line. In addition the bipolar circuit allows the use of peripherals not suitable to be powered directly from the line, for example


memories, displays and microcontrollers. Operating over a line voltage range of 2,5 to 10 V, the new IC has a d.c. output voltage range of 2 to 9,5 V and a maximum d.c. output current of 30 mA. Since it has a high input impedance to audio frequencies of over 8 k $\Omega$  the TEA1080 can be connected directly to the telephone line (via a polarity guard). It offers two modes of operation: either a regulated output voltage or a constant d.c. voltage drop in series with a resistor between the line and its output terminal.

The circuit can handle large speech signals. For example, at a typical a.c. line level of 1,5 V imposed on a d.c. level of 4,5 V, the distortion of the line signal is less than 2 % for an output current of 15 mA.

The TEA1080 is powered by a part of the surplus of the line current which is normally sunk to the voltage regulator of the speech/transmission circuit. The circuit requires only five or six external capacitors and resistors. Maximum internal supply current is 1 mA and operating ambient temperature range is -25 to 70 °C. The TEA1080 comes in an 8-pin plastic DIL.

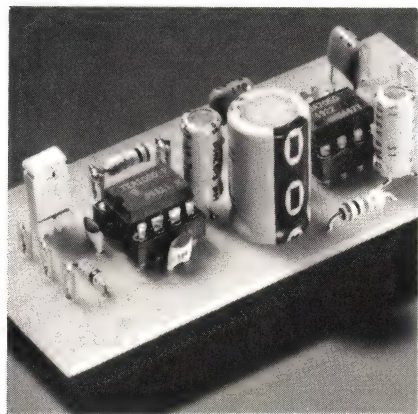

CIRCLE 2

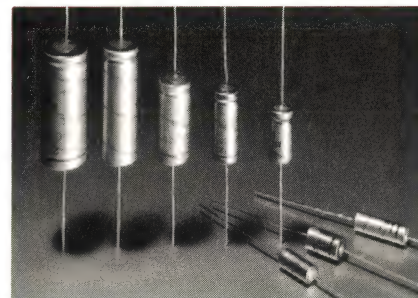

## SOLID ALUMINIUM ELECTROLYTICS COMPLEMENT EXISTING SERIES

Philips is complementing its existing 123-series of axial solid aluminium electrolytics with a new series offering enhanced CV-products in smaller can sizes. The new 125-series brings all the advantages of solid aluminium electrolytics to applications previously only covered by solid tantalum electrolytics. Advantages such as: no failure mechanism; wide operating temperature range from -55 to +125 °C; reverse voltage capabilities; high ripple current; and no requirement for a charge/discharge series limiting resistor.

The new series covers three can sizes: can size B (5 x 15 mm); can size A3 (6 x 10 mm); and can size A2 (5 x 10 mm). Can size B is identical in dimensions, CV-product and specifications to the CSR-13 (tantalum standard) can size B. Can size A3 is identical to can size B in CV-product and specifications; the feature of this type is its short length making it very suitable for automatic insertion. Can size A2 covers a lower CV-product range and is also ideal for automatic insertion.

The 123- and 125-series together now offer equivalents for all tantalum can sizes, as well as two larger sizes (can sizes 5 and 6).

Specified to the IEC384-4 long life grade, the new 125 capacitors offer long life and high reliability, for example endurance test lifetime at 125 °C is 2000 hours. Nominal capacitance range (E6 series) is 0,22 to 68  $\mu$ F with a tolerance of 20 %. Rated voltage range is 4 to 35 V. Climatic category is 55/125/56.

CIRCLE 3



Electronic  
components  
and materials





# THE COMPLETE COMPONENT COMPANY

Philips Electronic Components and Materials Division, 5600 MD Eindhoven, The Netherlands

## FASTEST PROMs ON THE MARKET STORE 16 TO 64 KBITS

We are supplying a new family of high-speed bipolar PROMs consisting of the 16 Kbit 82HS195/195A/195B, the 32 Kbit 82HS321/321A/321B and the 64 Kbit 82HS641/641A/641B. The 82HS195B, 82HS321B and 82HS641B are the fastest 16, 32 and 64 Kbit PROMs in the industry with maximum access times of just 25, 30 and 35 ns respectively.

The speed capability of the PROMs is a direct result of a new proprietary process technology known as HS2Z. This combines the best features of oxide isolation and vertical fuse integration. In addition to high speed, PROMs made with HS2Z demonstrate low power dissipation and very high field fusing yields. Applications for the TTL-compatible devices include high-speed electronic data processing, telecommunications, sequential control, microprogramming, control store, random logic and code conversion. The devices are field programmable using commercially available PROM programmers and have been tested to programming yields of better than 98 %.

The 20-pin N82HS195 (the N prefix

indicates the commercial operating temperature range of 0 to 70 °C) has a maximum access time of 45 ns; the N82HS195A is rated at 35 ns maximum and the N82HS195B at 25 ns. The extended temperature version (prefix S; -55 to +125 °C) offers a maximum access time of 35 ns. Power dissipation is typically 35  $\mu$ W per bit. These 16 Kbit PROMs are organized 4 K x 4 bits.

The 24-pin N82HS321, N82HS321A and N82HS321B have maximum access times of 45, 35 and 30 ns. Typical power dissipation is 20  $\mu$ W per bit. Organization of these 32 Kbit devices is 4 K x 8 bits. Organized 8 K x 8 bits, the 24-pin N82HS641, N82HS641A and N82HS641B have maximum access times of 55, 45 and 35 ns and a typical power dissipation of 20  $\mu$ W per bit.

All the PROMs have on-chip decoding and a chip-enable input for memory expansion. They need no separate fusing pins and feature three-state outputs for optimization of word expansion in bussed organizations. The PROMs are supplied with all outputs at a logic HIGH. They are available in ceramic or plastic DILs, and in plastic leaded-chip-carriers.

CIRCLE 4

## WIDEBAND TRANSISTOR HAS HIGH POWER HANDLING CAPABILITY

Philips is expanding its line of wideband transistors with a new type possessing a transition frequency of typically 7.5 GHz and exhibiting the highest presently available power handling capability for this category of transistor. The BFG195 can handle a power dissipation of 0.5 W and features a unilateral power gain of 12 dB at an operating frequency of 2 GHz.

The BFG195 is for applications in high-gain wideband systems up to 2 GHz, for example in the first intermediate frequency section of satellite tv receivers.

The BFG195 incorporates Philips second wideband transistor crystal with a transition frequency of 7.5 GHz. The first in the range, the BFG65, is a lower power-rated type. The higher power handling capability of the BFG195 is due to a larger active area of the crystal almost three times the size of the BFG65 crystal. The improvement in power handling performance has been achieved without any increase in distortion.

The npn transistor is encapsulated in the plastic crosspack SOT-103. Maximum collector-emitter voltage is 10 V.

CIRCLE 5


## STATE-OF-THE-ART 8-BIT MICROCONTROLLERS AVAILABLE NOW

As a true alternate source for Intel's 8051 family of 8-bit microcontrollers, we provide a reliable European source for the latest state-of-the-art versions of these industry-standard devices. New types include the MAB8052AH, MAB8032AH and a very fast 15 MHz version of the MAB8031AH. All these microcontrollers are manufactured in an advanced 2 micron NMOS process.

The MAB8052AH contains a non-volatile 8 Kbytes of ROM and 256 bytes of RAM, 32 I/O lines, and three 16-bit timer/event counters. External memory is expandable up to 128 Kbytes. The architecture features non-page orientated instructions, direct addressing, four 8-bit register banks, stack depth up to 256 Kbytes, and binary and BCD arithmetic plus bit handling capabilities.

The MAB8032AH is a ROMless version of

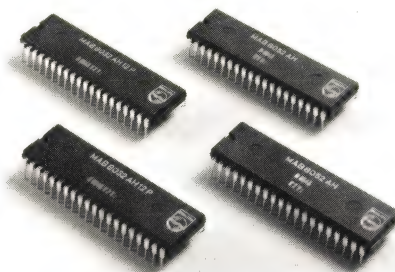the MAB8052AH. Both devices have a 12 MHz on-chip oscillator resulting in an execution speed of 1  $\mu$ s for 58 % of the instructions. The instruction set consists of 255 instructions 44 % of which are one byte, 41 % two byte and 15 % three byte. With an external clock, frequency is variable from 3.5 to 12 MHz. Both the MAB8052AH



and MAB8032AH are packaged in a 40-lead plastic DIL. The devices will soon also be available in the 44-lead PLCC44 plastic leaded-chip-carrier.

The MAB8031AH is a ROMless version of the MAB8051AH. The new 15 MHz type is an addition to the existing 8, 10 and 12 MHz versions. The MAB8031AH features 128 bytes RAM, 32 I/O lines, and two 16-bit timer/event counters. The device is available in either a 40-lead plastic DIL or a 44-lead plastic leaded-chip-carrier.

For the MAB8031AH different versions are available covering the temperature ranges 0 to 70 °C, -40 to 85 °C, and -40 to 100 °C. This makes the device suitable for a wide variety of control applications under different environmental conditions.

CIRCLE 6

# PHILIPS



On November 13, 1985,  
Thomson acquired most of Mostek's assets.  
It's good news for Thomson.  
It's good news for Mostek.

And it's good news for you.

Now with the newly formed THOMSON COMPONENTS-MOSTEK CORPORATION, we are reinforcing both our product-based technologies and our worldwide marketing network.

But when you get right down to it, products and technologies are not enough. A company's most valuable assets are the trust and respect of its customers.

And we are going on record as saying that THOMSON SEMICONDUCTEURS is committed to earning your trust and respect. Not to mention your business.

We have an outstanding track record for growth — 11% in 1985. For a company our size, we now have a larger base of diversified products than anyone in the industry.

What's more, we're working hard at matching our products to your application requirements and improving the service and support that goes with them.

In coming weeks, you'll be learning more about both our products and company. But in the meantime, we just wanted to let you know how much we appreciate your support. And how much we value your business.



Jacques Noels  
Chairman





## Programming aids minimize errors during software design, coding, and modification

Chris Terry, *Associate Editor*

You can't yet find a computer that programs itself—such things exist only in the realm of science fiction—but by employing one or more programming aids, you can make your computer handle much of the tedious work associated with program or software-system design. These programming aids—which include structured-analysis tools, syntax editors, language-sensitive editors, interpreters, formatters, profilers, and source-code managers—check large quantities of data rapidly for internal consistency, adherence to syntactical rules, and correlations between data sets. Such checks minimize the errors that can occur during program or software-system design, during coding, and during program modification.

### Computerized system analysis

When you're designing a program or software system, you'll find structured-analysis tools invaluable. The structured-analysis technique, which was originally developed by Yourdon Associates (now Yourdon Inc) of New York, uses data-flow diagrams (DFDs) to describe a proposed software system. DFDs define each item of data used as input to a transformation process, the data transformations that take place, and the data items that emerge from the process.

DFDs are simple and clear enough to allow your customer to understand precisely what a program will do, so that you and the customer can readily agree on the software system's specifications. The DFD's process symbols represent complex tasks or even whole programs. When the analyst and

programming team begin to build the system from the top down, they expand the DFD's process symbols at each level, splitting complex tasks into simpler tasks or even new DFDs.

For your entire software system to be internally consistent, you must build a data dictionary as your design proceeds from level to level. The entries in the data dictionary completely define all input data items, all intermediate products, and all output data items. Programmers working on different parts of the system refer to the data dictionary to ensure that they don't

give different names to the same data item.

Although structured analysis is invaluable in creating new systems, it entailed a lot of clerical overhead until recently. Although you could easily build and update the data dictionary with a word processor—or even create DFDs with a graphics package—you couldn't integrate the data dictionary with the DFDs in the computer. Your project depended, therefore, on the frequent manual updating of the dictionary and the DFDs, and the circulation of this information, on paper, to the programming team.



*You can develop data-flow diagrams (DFDs) for a complex software system with the aid of Tektronix's structured-analysis tools for VAX/VMS and Unix systems. You specify data items with the graphics editor, and the software automatically places the items in the project's data dictionary.*





# THE INTEGRATED SOLUTION FOR MICROPROCESSOR DEVELOPMENT/DEBUG

**Single vendor convenience and accountability... Multi-vendor flexibility and savings.**

Introducing New Micro, the company dedicated exclusively to the integration of popular multi-vendor microprocessor development tools.

A joint venture of both companies, New Micro combines the applications and systems integration experience of ARS Microsystems, Europe's leading development systems house, with the extensive in-circuit emulator design and manufacturing capability of Microtek International, developer of the widely used MICE emulators.\*

New Micro does the work for you. We identify and integrate software from our own line, your host computer supplier and third party vendors. The result is a cost-effective system that's tailored to your needs. A system that offers outstanding quality assurance because its debugging software enhances the diagnostic capabilities of its MICE emulators.

The New Micro Solution...

- Minimizes your time spent in locating and integrating programming tools.
- Assures you the most effective combination of software and hardware tools.

- Helps keep your development time and costs under tight control.
- Maximizes your software development productivity.

If your operating system is PC-DOS, MS-DOS, VAX/VMS or UNIX, New Micro can configure a system for your single user, networked or multi-user environments. A system that does the total job with Microtek's emulation and debugging software for all popular microprocessors from Intel, Motorola, Zilog, National Semiconductor and other leading manufacturers.

For an analysis of your system needs, or a demonstration of popular integrated debugging tools with your host system, call us.


## New Micro, Inc.

16901 South Western Avenue,  
Gardena, California 90247  
(213) 538-5369

\*New Micro, Inc. is the exclusive U.S. distributor for Microtek International in-circuit emulators.

NOTE: PC-DOS, MS-DOS, VAX/VMS, UNIX, CP/M-86 are trademarks of IBM Corporation, Microsoft Corp., Digital Equipment Corp., AT&T, Digital Research Inc., respectively.

CIRCLE NO 176

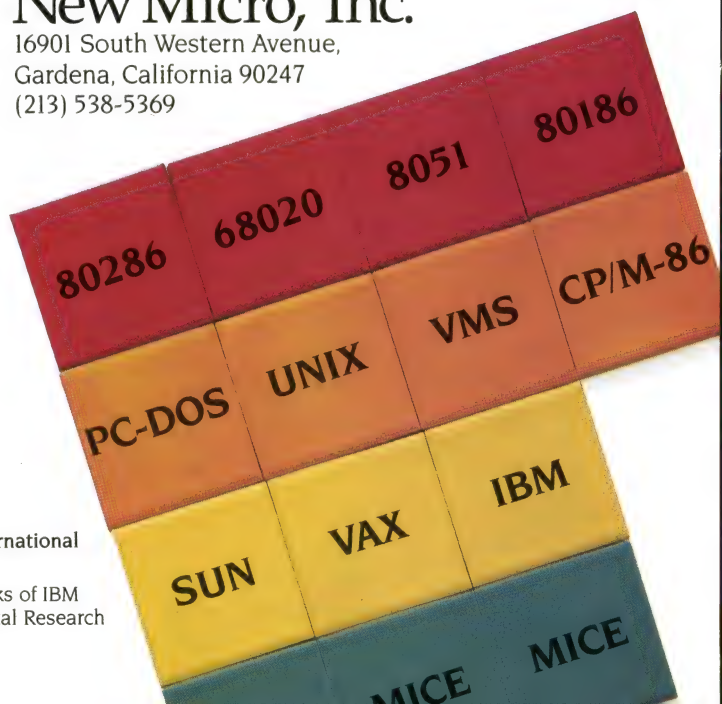




# TECHNOLOGY UPDATE

A number of new programming tools, however, let you integrate the DFD with the data dictionary and perform all updating on the computer. One such tool, Analyst Toolkit from Yourdon Software Engineering (a joint venture of Yourdon Inc and the Cadware Group Ltd of New Haven, CT), runs on the IBM PC, PC/XT, PC/AT, and compatibles. The software package's graphics allow you to create symbolic graphic models of real-time, on-line, and batch-processing systems, as well as other types of systems.

You use a mouse to draw DFDs, entity-relation diagrams, state-transition diagrams, and free-form graphics. You build the data dictionary from your diagrams by means of the diagram-extraction feature. Error-checking facilities test the graphics models at all stages of the design for consistency and accuracy. The Analyst Toolkit requires 640k bytes of RAM and 10M bytes of hard-disk storage; it costs \$3500.

Tektronix offers structured-analysis editors that run on DEC VAX computers under Unix or VMS. These graphics editors let you build and display DFDs by extracting existing data items from the data dictionary. When you introduce new data items into a DFD, the editor prompts you for their definitions, checks them for consistency, and then automatically incorporates them into the data dictionary. Prices for the software start at \$16,500.

Another set of structured-analysis tools, Teamwork/SA from Cadre Technologies, runs on Domain workstations from Apollo (Chelmsford, MA). Both single- and multiple-user packages are available. The multiuser version lets all members of a design team access a central project library that includes data dictionaries, DFDs, process specifications, and project-management data. In addition, team members can enter annotations consisting of information necessary to the system model that doesn't fit into

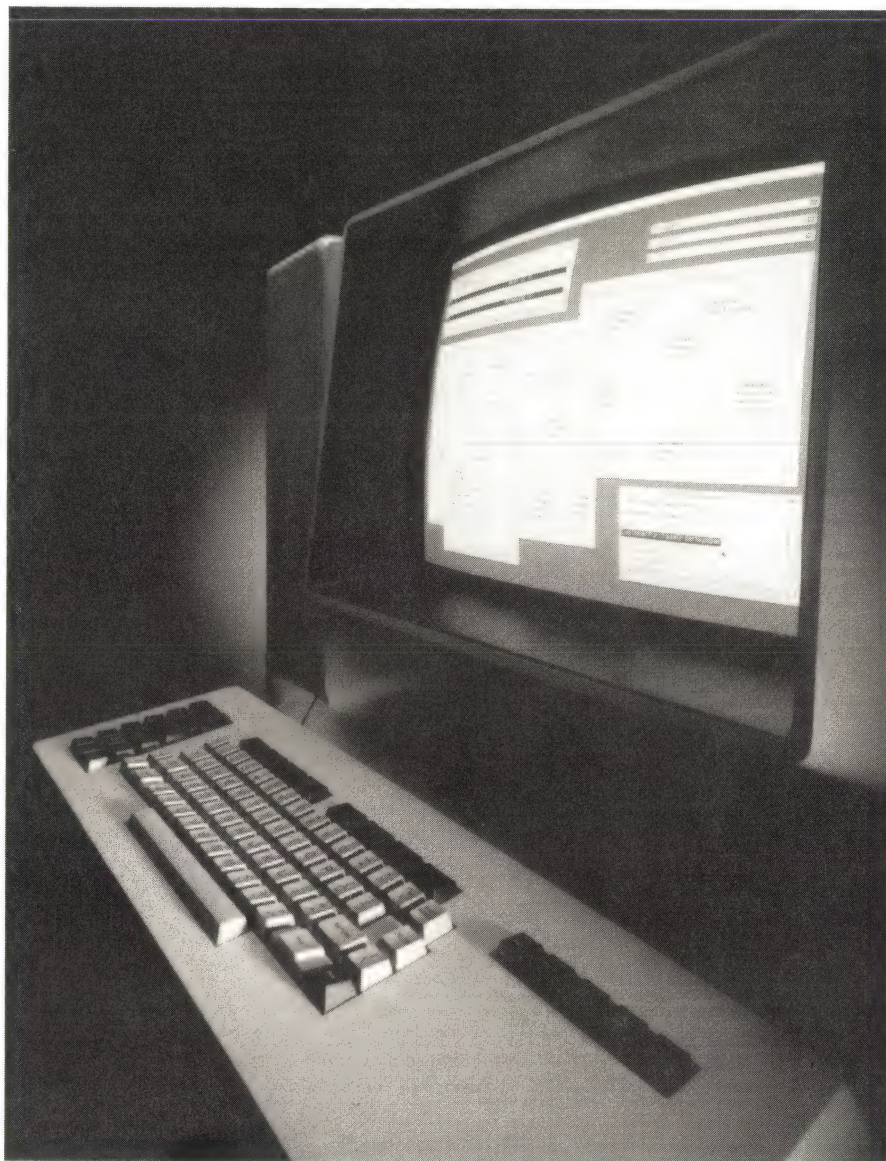

*You can integrate all phases of software design, from system analysis to coding and maintenance, by using Teamwork/SA from Cadre Technologies Inc. The package's language-sensitive editors provide templates and on-line help for C, Pascal, and Ada programmers.*

the standard structured model. Such annotations can consist of free-form text, and you can cross-reference them to many portions of the structured specification.

Teamwork/SA provides a graphics editor, a process-specification editor, analysis utilities, and a consistency checker. The graphics editor is syntax oriented and operates strictly according to Yourdon Associates' rules for building DFDs and for establishing their relationships to other objects in the system specifications. The process-specification editor also adheres to these rules.

The package's analysis utilities can manipulate objects in the system only according to these rules, and its consistency checker detects both specification errors within a given DFD and inconsistencies between DFDs. Teamwork/SA costs \$8900 per workstation.

An even more extensive system, Promod from Promod Inc, supports all stages of your software-system design, from structured analysis through coding and maintenance. The software operates on DEC VAX systems and on all IBM PC configurations. The project library inte-



```
-- The buffering task contains an internal pool of characters
-- processed in a round-robin fashion. The pool has two indices,
-- an IN_INDEX denoting the space for the next character and an
-- OUT_INDEX denoting the space for the next output character.

POOL_SIZE : constant INTEGER := 100;
POOL : array (1 .. POOL_SIZE) of CHARACTER;
COUNT : INTEGER range 0 .. POOL_SIZE := 0;
IN_INDEX, OUT_INDEX : INTEGER range 1 .. POOL_SIZE := 1;

begin
  if {condition} then
    {statement}...
  elsif {part}...
  {else_part}
  end if;
  {statement}...
  {exception_part}
end BUFFER;
Buffer LSEDEMO.ADA
```

Write Insert Forward

*Language-sensitive editors keep you from making syntax errors. This editor, DEC's LSE, also shows you the names and data types of variables you've declared in the module you're working on.*

grates the data dictionary, DFDs, and minispecs during the structured-analysis phase of development. Promod also provides code-frame generators for C, Pascal, and Ada for use during the coding phase. These frames let you view the variables and data types that you've declared and entered in the data dictionary, ensuring that the code is syntactically correct and the variables are consistent.

The package also provides a comprehensive documentation facility, which takes the relationships between modules into account, and a version-maintenance facility, which ensures that when you rebuild your system after modifying it you use only the latest version of each module. Prices start at \$9950 for the IBM PC version and \$37,500 for the VAX-11/780 version.

## Find errors while coding

Once your system analysis and design are complete, you can use another set of programming aids—syntax checkers, language-sensitive editors, interactive interpreters, formatters, and profilers—to ease your coding task. You don't need as much computing power to reduce coding errors as you do to automate system analysis, so you can usually use these tools on a personal computer.

If you use a syntax checker, you must first write the code with a standard editor. One example of a syntax checker is the Unix Lint utility, which comes in several versions for the MS-DOS environment. For example, Gimpel Software offers PC-Lint for \$98. Entelekon offers a Lint package for \$129.95.

## Language-sensitive editors

Unlike syntax checkers, which check code after you've entered it, language-sensitive (or syntax-directed) editors operate according to the rules of one or more high-level languages (eg, Fortran, C, Pascal), detecting or correcting illegal statements as you enter them. Hyper-Micro Inc offers ESP, a syntax-directed editor that comes in versions for C and Pascal. The editor, which costs \$200, recognizes the rules of the language and detects errors in the statements you enter. For example, the moment you enter the word "if" on a line, the editor displays a template showing the correct format of the If... Then... Else construction, with place holders that you can overwrite with your statements.

The software handles the tedious syntactic details automatically, without your intervention. For example, it inserts a semicolon at the end of each statement, pairs Begin

and End statements (in Pascal) or braces (in C), and checks syntax, ensuring, for example, that you've declared variables properly and haven't mismatched data types. To use this program as a standard multiwindow text editor, you simply turn off the language-sensitive features and use just the general features, such as the global-search-and-replace and cut-and-paste functions.

Spruce Technology offers a similar syntax-directed editor for C programmers. The package, FirstTime, has macro capabilities, so you can generate whole program and statement structures on the screen with a single keystroke. It costs \$295.


Some expert C programmers have found that, at least in the early versions, these packages reject some constructs that a Unix compiler would accept and handle correctly. Nevertheless, both packages are valuable aids to programmers who are not yet expert in C and Pascal or who want to avoid some of the syntactic detail so they can concentrate on the program logic.

C Ware Corp offers See, a general-purpose, full-screen editor that can edit two files simultaneously. The editor, which costs \$50, has macro capabilities. It provides automatic indentation and matching of parentheses, brackets, and braces. The matching feature ensures that your program's structure is correct while giving you more freedom than do the mandatory templates and syntax checking of ESP and FirstTime.

Alice, a Pascal package distributed in the US by Software Channels Inc, combines a fill-in-the-blanks editor and syntax checker with an interpreter and extensive on-line help files. When you write a program or module with the editor, you can execute it immediately with the interpreter, either at full speed or one statement or one procedure at a time. A backward-tracing feature lets you find out just how the program reached a particular state-



# FORCEFUL.

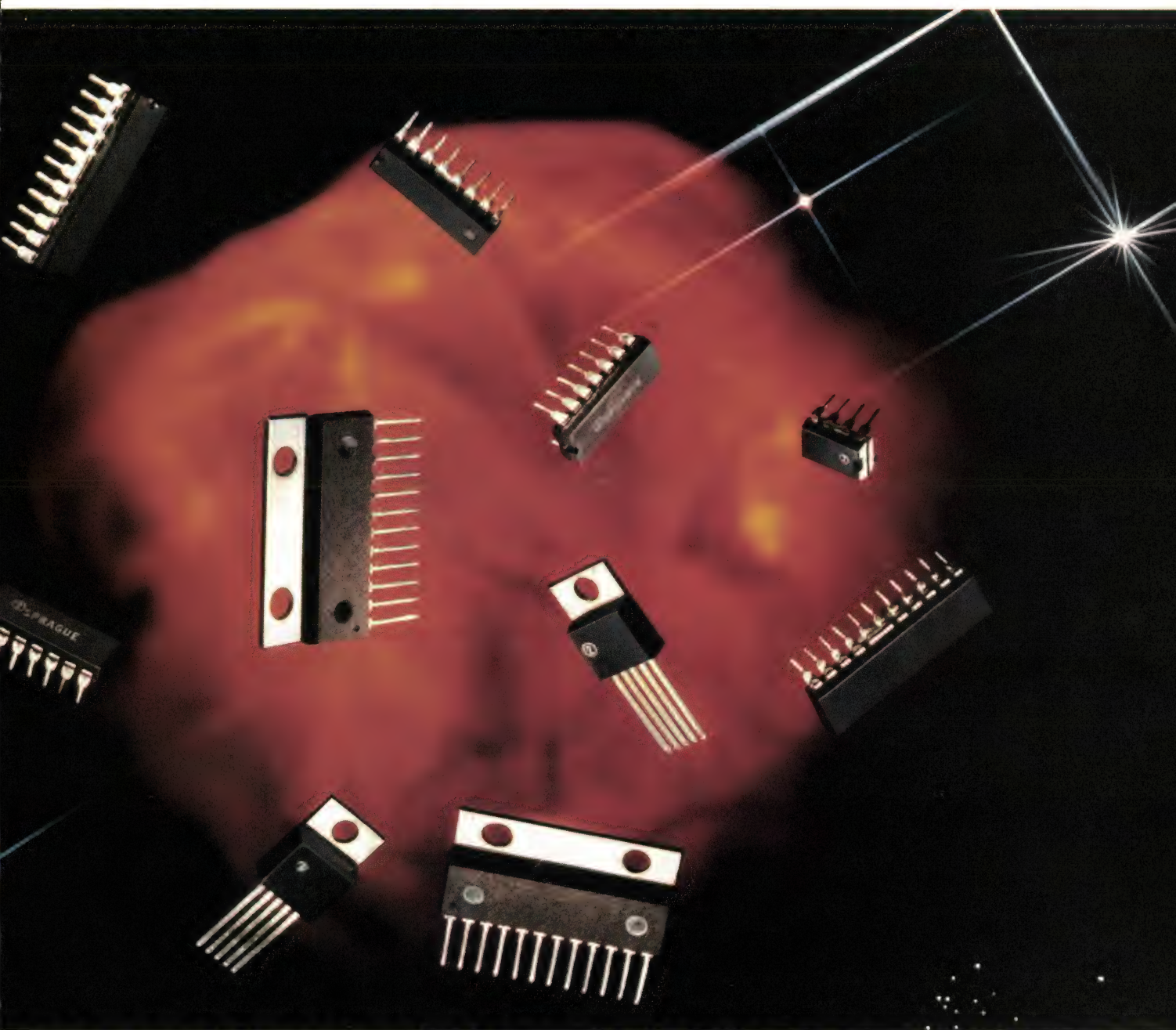

4SS-5116

**SPRAGUE** Sprague has led the way in power interface since 1970. After originating its line of  
**PICs EXCEL AS** Power ICs (PICs), Sprague has increased emphasis on circuits for stepper, servo, and  
**MOTOR MUSCLE.** brushless d-c motors. Output drive capabilities have been extended to  
 $\pm 4$  A per channel and to sustaining voltages exceeding 60 V. Motor  
driver types include half-bridge, full-bridge, dual full-  
bridge, three-phase, translator/driver, and power driver  
sink or source arrays. All devices include diode transient  
protection. Many feature current limiting (PWM), thermal shutdown, over-voltage and/or short-circuit protection. *Sprague*  
*Electric Company, a Penn Central unit, World Hdqtrs., Lexington, MA. For Brochure WR-202,*  
*write to Technical Literature Service, Sprague Electric Company, P.O. Box 9102, Mansfield,*  
*MA 02048-9102. For applications assistance, call Mark Heisig or Tom Truax at (617) 853-5000.*



CIRCLE NO 177



# TECHNOLOGY UPDATE

ment. The package, which provides a number of other debugging features, costs \$95.

One drawback of Alice is that it stores source code as a binary, tokenized file, so it doesn't let you use existing source-code files without rekeying them via Alice's editor. Turbo-Pascal source-code is an exception, however: A utility that comes with Alice can convert Turbo-Pascal source-code files to Alice's format. The utility performs syntax-checking on your code during conversion. Another drawback is that Alice is based on Waterloo Pascal, so its extensions may not correspond to those your compiler supports.

Language-sensitive editors that run on IBM PCs and compatibles are limited to some degree, both by the PCs' computing power and by the fact that the editors are chiefly for novices and programmers who work in the PC-DOS environment. However, for the professional programmer who works in a VAX environment under VMS or Unix, vendors offer a number of very sophisticated language-sensitive editors.

Language-sensitive editors for the VAX include Digital Equipment Corp's LSE, which provides both templates and on-line help for the Ada, Basic, Bliss, C, Cobol, Fortran, Pascal, and PL/I languages. The LSE is part of the company's VAXset package, which includes maintenance software and test facilities and starts at \$13,800 for the MicroVAX. You can choose the fill-in-the-blanks mode, in which you complete statements such as "If . . . Then" statements. Optional statements, such as "Else" and "Else if," will disappear if you don't use them. Alternatively, you can enter your code in free form but call up help screens for any constructs about which you are in doubt. If you're writing an Ada program, for example, you can call up and view the data types and variables that you've declared, to make sure

they're consistent.

The LSE can compile your program for error checking only (not for code generation) from within the editor. Compilation errors appear in one window, and the source code that caused the errors appears in a second window. You can immediately correct the error and continue the compilation. When you reach the end of the program, you can compile for code generation and link the modules.

A syntax-directed editor for Pascal programs in VAX or PDP-11 environments is the \$1250 Pasced package from Real Time Products. Like Alice, Pasced stores programs in binary, tokenized form that represents their internal tree structure. However, Pasced lets you view external source-code files on a read-only basis, and you can import all or part of an external file by using a conversion utility, which checks the syntax of imported code during the conversion process.

## Interpreters debug quickly

Another programming tool that can save you a lot of work on compiled programs is an interactive interpreter, which executes a module or a program and finds both syntax and logic errors before you compile and link the program.

Although compiled programs run very quickly, corrections to them require a lot of work. You write your program with a standard editor, then leave the editor and invoke the compiler, which tries to process the whole program, generating executable code unless it encounters a drastic error. When the compilation is complete, you must inspect and record the list of errors, return to the editor to make the corrections, and reinvoke the compiler. When the compiler finds no more errors, you have to invoke the linker before you can run the program. Any change to the program, no matter how small, requires you to repeat the entire edit-compile-link-run cycle.

Interactive interpreters, however, let you correct errors before you compile code. Vendors are offering an increasing number of interpreters for C and Pascal. In the personal-computer environment, where C and Pascal compilers differ considerably from each other as well as from the corresponding Unix or VMS compilers, each interpreter operates in conjunction with a specific MS-DOS compiler. For example, Gimpel Software supplies C-terp in five different versions that work in conjunction with the Lattice (Glen Ellyn, IL), Computer Innovations (Tinton Falls, NJ), Aztec (from Manx Software Systems), Mark Williams (Chicago, IL), and Microsoft (Redmond, WA) 3.0+ C compilers. C-terp costs \$300.

MS-DOS users can choose from at least six other C interpreters ranging in price from \$49 for Apprentice C (from Manx Software Systems) to \$500 for Smart C (from AGS Computers). The Smart C package includes a migrator program that translates any C source file in ASCII format into a form that Smart C can use both to edit and to interpret. Further, once the editor has checked the program for syntax errors and the interpreter has successfully run the program, you can create a clean source-code file in ASCII format. The company claims that such an output file will be compatible with most commercially available compilers and will compile cleanly without modification.

C interpreters are also available for minicomputer or workstation environments. Smart C, for example, comes in versions for the AT&T 3B series and for VAX systems running Unix System V, Berkeley BSD 4.2, or Xenix. The VAX 11/780 version costs \$10,000.

Catalytix's Safe C, a package that contains a stand-alone interpreter as well as a number of analytical utilities, runs on a number of computers under a variety of operating systems, including MS-DOS, VAX/VMS, and Unix. It costs from \$1000



# WE'VE PACKED THE NULLING CAPACITORS INTO YOUR LOW OFFSET OP AMP...

...to save you space and cost.

Finally, the world's first completely monolithic CMOS chopper stabilized operational amplifier family has been developed by Teledyne Semiconductor. Available in single, dual and quad versions, this new innovation in op amp technology eliminates the need for external chopper capacitors giving you the advantage of reduced part count, reduced assembly time and cost, simplicity in PC board layout, and increased system reliability and performance.

Low Vos errors eliminate trim procedures during manufacturing, periodic re-calibrations, and reliability problems caused by damaged or mis-adjusted trim potentiometers.

The TSC911 single, TSC913 dual and TSC914 quad, feature  $15\mu\text{V}/^\circ\text{C}$  maximum offset voltage and  $0.15\mu\text{V}/^\circ\text{C}$  maximum offset voltage temperature drift and operate from a  $\pm 5\text{V}$  or single  $+5\text{V}$  to  $+15\text{V}$  power supply. Other key features include:

- Low power supply current (single) .....  $350\mu\text{A}$
- Low noise (0.1 to 1 Hz) .....  $0.65\mu\text{Vp-p}$
- High open-loop DC gain ..... 115dB
- High common mode rejection ratio ..... 110dB

On chip capacitors make these "user friendly" devices pin compatible with popular lower precision, higher power op amp such as the 7650, 741/OP07, 1458, and LM348/OP11.

For more information on this unique family of devices call (415) 968-9241 or use the convenient coupon below.

CIRCLE NO 178

## TELEDYNE SEMICONDUCTOR

1300 Terra Bella Avenue • P.O. Box 7267 • Mountain View, CA 94039-7267 • (415) 968-9241

Please send me more information on the TSC911, single: ☐ TSC913, dual: ☐ TSC914, quad: ☐

486EDN911

PLEASE HAVE A SALESPERSON CALL ME ☐

Name \_\_\_\_\_ Title \_\_\_\_\_

Company \_\_\_\_\_ Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_ Tel: (     ) \_\_\_\_\_ - \_\_\_\_\_



# WORLD'S SMALLEST DIP SWITCH



## BETTER HEAT CONVECTION.

### OLD DIP SWITCH



HIGH DIPS SHADOW LOW IC'S

### NEW DIP SWITCH



THE LOW PROFILE K40 DIP IS  
THE SAME SIZE AS AN IC

### NO MORE HAND LABOR.



## YOU CAN USE AUTOMATIC INSERTION EQUIPMENT!

If you don't have automatic insertion equipment, we're banking that some day you will. To prove that, we'll charge you the same low price for all your purchases—no more need for the low-volume premium prices you're paying now.

## AVAILABLE IN 2, 3, 4, 5, 6, 7 & 8 POSITIONS

### FREE SAMPLE!

WITH STAPLED BUSINESS  
CARD TO YOUR LETTERHEAD

**AMERICAN RESEARCH  
& ENGINEERING**

1500 EXECUTIVE DRIVE  
ELGIN, IL 60120  
312-888-7245

*America can do it better!*

# TECHNOLOGY UPDATE

to \$8000, depending on the operating system you buy it for. This interpreter implements an abstract machine for C, so the debugged source code will compile cleanly on any other machine. The interpreter has a number of debugging features: It can perform single-stepping, in which the interpreter stops at each semicolon; it can set breakpoints at any point in the source code, so they can depend upon any group of conditions; and it can trace at every expression, statement, and function call.

If you don't use a language-sensitive editor or an interpreter while coding, but simply use a standard editor to write source code for your compiler, you can easily miss a closing parenthesis or brace, or change the indentation level by mistake. Formatters and profilers help you

avoid such errors. Formatters let you arrange lines of code so they're easy to read. Profilers provide statistics on how many times each procedure or function is called.

Source Print from Aldebaran Laboratories Inc, a formatter for the MS-DOS environment, formats your C, Pascal, or Modula-2 source code by emphasizing reserved words, indenting nested structures, and placing vertical lines between paired braces or Begin... End pairs to show the level of nesting. The program also prints statistics on the number of characters and lines in the file. You can choose to have the program number each line of the program. Source Print sells for \$97.

Catalytix offers a dynamic profiler for use with the company's Safe C interpreter. The profiler, which

## For more information . . .

For more information on the programming aids described in this article, circle the appropriate numbers on the Information Retrieval Service card or contact the following vendors directly.

**AGS Computers Inc**  
1139 Spruce Dr  
Mountainside, NJ 07092  
(201) 654-4321  
Circle No 659

**Aldebaran Laboratories Inc**  
3738 Mt Diablo Blvd #312  
Lafayette, CA 94549  
(415) 283-7084  
Circle No 660

**Cadre Technologies Inc**  
222 Richmond St  
Providence, RI 02903  
(401) 351-5950  
Circle No 661

**Catalytix Corp**  
55 Wheeler St  
Cambridge, MA 02138  
(617) 497-2160  
Circle No 662

**C Ware Corp**  
Box C  
Sunnyvale, CA 94087  
(408) 720-9696  
Circle No 663

**Digital Equipment Corp**  
Phone local office

**Entelekon**  
12118 Kimberley  
Houston, TX 77024  
(713) 468-4412  
Circle No 664

**Gimpel Software**  
3207 Hogarth Lane  
Collegeville, PA 19426  
(215) 584-4261  
Circle No 665

**Hyper-Micro Inc**  
2308 4th Ave  
Seattle, WA 98121  
(206) 441-9814  
Circle No 666

**Manx Software Systems**  
Box 55  
Shrewsbury, NJ 07701  
(201) 530-7997  
Circle No 667

**Promod Inc**  
22981 Alcalde Dr  
Laguna Hills, CA 92653  
(714) 855-3046  
Circle No 668

**Real Time Products**  
1 Paul St  
London EC2A 2JJ UK  
01-588-0667  
Circle No 669

**Seidl Engineering**  
1163 E Ogden Ave, Suite 705-171  
Naperville, IL 60540  
(312) 983-5477  
Circle No 670

**Softfocus**  
1343 Stanbury Dr  
Oakville, Ontario,  
Canada L6L 2J5  
(416) 825-0903  
Circle No 671

**Software Channels Inc**  
Four Kingwood Pl  
Kingwood, TX 77339  
(713) 359-1024  
Circle No 672

**Spruce Technology Inc**  
189 E Bergen Pl  
Red Bank, NJ 07701  
(201) 741-8188  
Circle No 673

**Tektronix Inc**  
Box 14752  
Portland, OR 97214  
(800) 245-2036  
Circle No 674

**Yourdon Software Engineering**  
1501 Broadway  
New York, NY 10036  
(212) 391-2828  
Circle No 675





# Parlex Hybrids

Custom thick-film hybrids. Engineered to produce imaginative, creative, space-saving assemblies. Chip-and-wire bonding, precision resistors and capacitors—combined to create amplifiers, oscillators, filters, bar-code

readers, and many other custom circuits. SIP, DIP, and custom packages, frequently combined with flex circuits and flat cable.

When you need innovative design and packaging send your schematic to us at Parlex. We're your best source for custom hybrids.

Parlex also manufactures Flexlayers®, a multilayer structure made of flex circuits or a combination of flex and rigid circuits. Other Parlex custom products include: Flexible Circuitry, Multilayers, Flat Laminated Cable, Printed Circuit Boards.

\* Flexlayers is a registered trademark of Parlex Corporation.

**Parlex**  
CORPORATION

Parlex Corporation 145 Milk Street  
Methuen, MA 01844 Tel: 617-685-4341

CIRCLE NO 179



# epo-tek®

## THE NEED

**A high quality epoxy with very specific performance requirements.**


## THE SOURCE

**EPO-TEK epoxies from Epoxy Technology.**


In electronics, microelectronics, optics, optoelectronics or any application which requires an epoxy with specific performance parameters, trust EPO-TEK epoxies from Epoxy Technology Inc. (EPO-TEK epoxies are also used in the professional restoration of valuable glass, ceramic and wood artifacts.)

**Call or send for our free product brochures.**

**Optics, optoelectronics brochure**

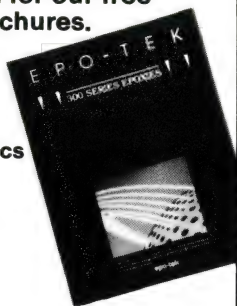

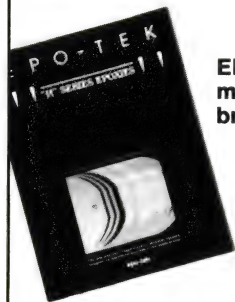**Electronics, microelectronics brochure**



**No one knows more about epoxies than Epoxy Technology.**

**(800) 227-2201**

14 Fortune Drive  
Billerica, MA 01821  
(617) 667-3805  
in Massachusetts

**epoxy technology inc.**



# epoxies

## TECHNOLOGY UPDATE

costs from \$1000 to \$8000, depending on the operating system, produces both statement- and function-level statistics. It indicates how many times each statement or function was executed. The software prints the statement-level statistics alongside the statements to which they refer, and it presents the function-level profile in the form of a histogram. The statistics this program provides are useful both for finding sections of code that don't get executed and for identifying potential bottlenecks.

When you modify your completed system, you must make sure that your next release contains the latest versions of every module. If you're working under Unix, you can use the Make utility, which analyzes the intermodule dependencies of a software system. When you change one module and recompile it, the Make utility constructs a command file containing all the commands you need to change, recompile, and relink all the modules affected by the change. Of course, you have to set up the dependencies in the first place, but a command language associated with the Make utility allows you to do so relatively easily.

The Make utility is part of the Unix environment and comes with that operating system, but if you're working in an MS-DOS environment, you can use one of several add-on versions of the utility. Softfocus offers a Make utility for \$59 that works with programs written in any high-level language. Seidl Computer Engineering offers SMK, another version of the utility, for \$100. SMK works in conjunction with Seidl's SVM (\$300), a version manager that maintains a complete revision history of any text or source-code file. The manager ensures that when you rebuild your software system, either to upgrade it or reconfigure it for different hardware, you link in the correct versions of the required modules. You can purchase both SVM and SMK for \$380.

An even more extensive version-maintenance system from DEC consists of two programs: the code-management system (CMS), and the module-management system (MMS), which are part of the VAXset package. The CMS automatically records every change to all of a project's source-code files, the dates of the changes, and the names of the programmers who made the changes. CMS merges modifications and stores current and historic versions of all source-code files in a library. The program, which is similar in function to the Unix SCCS (source-code control system), allows you to reconstruct any phase of a project.

The MMS follows instructions and rules in a system-description file in which you've described the interrelationships of the various components of your software system and defined the module dependencies. When you rebuild your system, MMS determines which modules of the system have changed since the last release and need to be recompiled. The software then makes sure that the rebuilt system incorporates all the latest changes.


The design, coding, and system-maintenance tools that are rapidly becoming available for personal computers, workstations, and minicomputers, are beginning to do for software engineers what CAE systems do for electronic-hardware designers. By lifting much of the clerical burden, these tools leave the engineer free to concentrate on the aspects of design that require imagination and intelligence. Although software-design and coding tools are not yet complete expert systems, you can expect to see software vendors applying some of the emerging artificial-intelligence techniques to design, coding, and maintenance tools in the near future.

**EDN**

**Article Interest Quotient  
(Circle One)**

**High 506 Medium 507 Low 508**



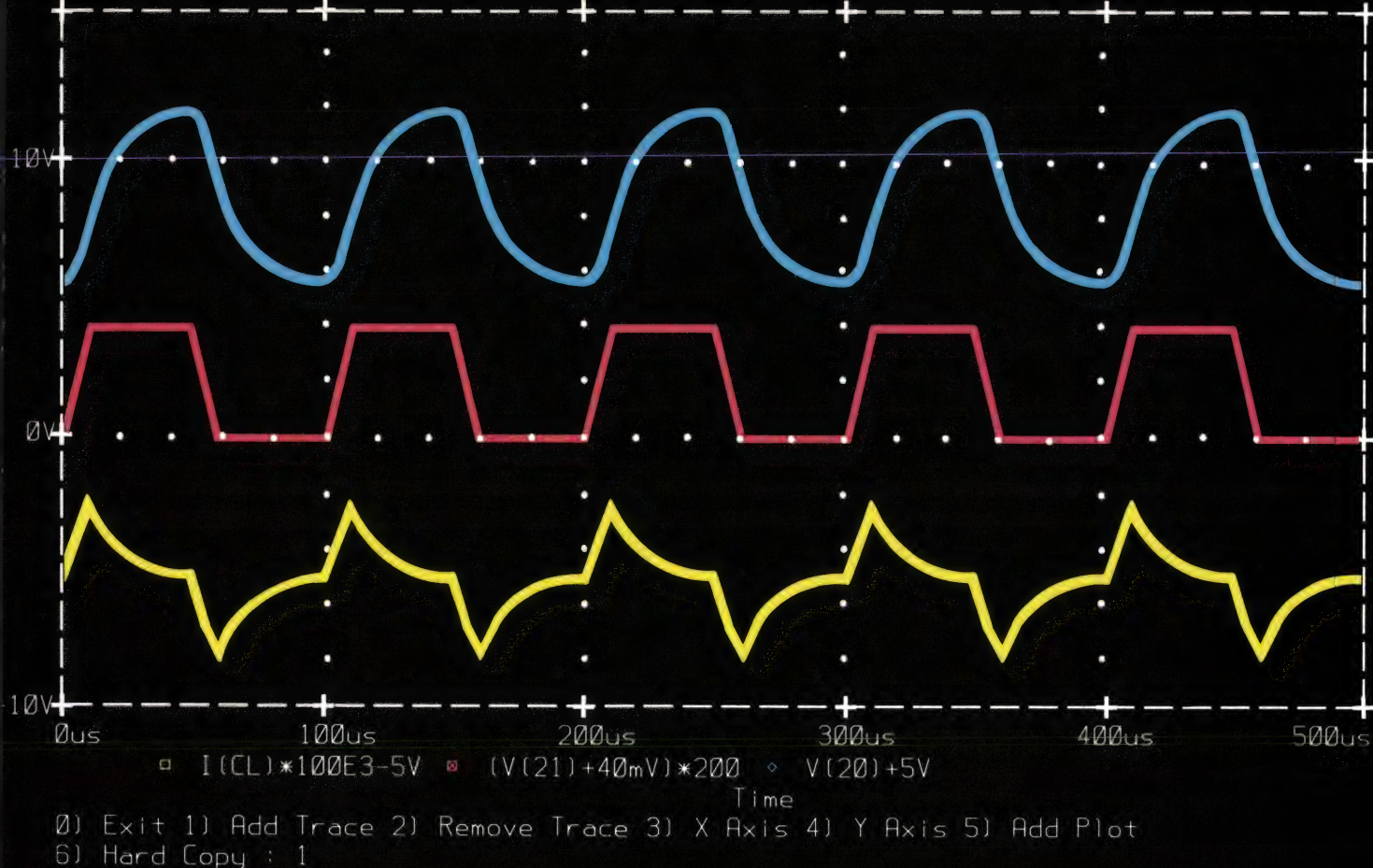

# Accuracy. Speed. Reliability. Support. PSpice.

Since its introduction over two years ago, MicroSim's PSpice has become the most popular commercial SPICE program in the world.

With over 20 years of combined real world experience in CAD, MicroSim offers an analog circuit simulator based on Berkeley version 2G.6 that has set the standard for IBM PC based machines.

PSpice allows you to simulate up to 140 transistor circuits (and over 10,000 nodes). With PSpice you will be able to design in minutes complicated circuits that used to take hours, without doing costly breadboarding, all with the convenience of using your own PC.


Besides offering improved convergence properties over other

SPICE-based programs, we also offer:

- a GaAs MESFET model
- a device library which includes bipolar transistors, power MOSFETs, opamps, diodes and comparators
- full telephone and mail-in support.

In addition we also offer an innovative graphics post processor called Probe that transforms your CRT into a "software oscilloscope". (The picture above was generated using Probe.)

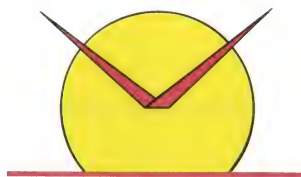If you are interested in doing your circuit simulations in a timely manner and at a fraction of a mainframe's cost, please give us a call today!



**MicroSim Corporation**

23175 La Cadena Drive • Laguna Hills, CA 92653  
(714) 770-3022 • (800) 826-8603 • Telex: 265154 SPICE UR  
CIRCLE NO 180







# Seventy-two hours ago you didn't know you needed an emulator.

## **Applied Microsystems emulators solve problems you don't expect.**

Before you spend another long night trying to debug your system, call Applied Microsystems. Whether you're working with an 8-bit, 16-bit or even a 32-bit micro-processor. Intel, Motorola or Zilog. One processor or several. No bug is buried too deep for Applied Microsystems emulators.

## **Making a reliable 8-bit favorite even better.**

Our 8-bit EM has been cited by a leading engineering magazine as the best 8-bit in-circuit emulator on the market. It's a big favorite among engineers because they can rely on it 99.8% of the time.

But instead of relaxing, we started improving.

Now, drive your EM with a VAX, Sun, Apollo or PC using our host-resident remote control software. The optional logic state probe lets you qualify breakpoints with logic conditions anywhere in the system and cross-trigger to your 16-bit ES emulator. So you can find bugs caused by the interaction of the two. We've also

included new high performance cross-assemblers.

Best of all, in addition to more capabilities, we've even held our low price.

## **Our 16-bit emulator keeps state-of-the-art system debug from turning into a state of siege.**

It takes a powerful emulator, not promises, to get a bug-free product to market quickly. Applied Microsystems' 16-bit ES emulator runs identically to the processor in your target system. At the full-rated clock speed.

Our unique Event Monitor System lets you precisely control and monitor emulation flow with a combination of address, data, status, pass counter, and logic state events. You can quickly sort through thousands of bytes of code to find the small sections where bugs are embedded. Once discovered, use our resident symbolic debug to quickly patch in new code and test it in real time.

## **Dig out bugs from the source to the bit.**

Validate™ our new family of enhanced development environments, offers you the combined power of integrated hardware and software tools. Centered around a true source-level debugger, Validate works with "C" and Pascal on UNIX and VMS systems.

## **New! Real-time emulation for the 32-bit 68020.**

Working with the 68020? Applied Microsystems has a new 32-bit emulator for our ES series. All the powerful debug features you expect from the ES. And it's available now.

---

### **PROCESSORS SUPPORTED BY APPLIED MICROSYSTEMS**

---

**8-BIT:** 8080, 8048 family, 8085, 8088, 80188, Z80, NSC-800, 6800 family, 6809, 6809E, 68008, V20

---

**16-BIT:** 68000, 68010, 8086, 80186, Z800X, V30

---

**32-BIT:** 68020

---

## **Ask us for the facts. You'll like what you hear.**

Call toll-free for the technical and applications information that supports our promises: 1-800-426-3925. In Washington, call (206) 882-2000. Or write Applied Microsystems, P.O. Box 97002, Redmond, WA 98073-9702.

In Europe: Brooke House, Market Square, Aylesbury, Buckinghamshire, HP20 1SN, England. Tel: 44 (0296) 34822.



**Applied  
Microsystems  
Corporation**



# THE 68000 SERIES: SIGNETICS TAKES FIRST PLACE IN PERIPHERAL DESIGN.

Nobody has designed as many peripherals for the 68000 microprocessor as Signetics. Nobody.

We've made 15 so far. More than Hitachi, Mostek and Rockwell combined.

More, even, than Motorola.

It just goes to show that a solid reputation as a maker of standard products doesn't necessarily mean you can't dazzle 'em with innovation from time to time.

So give us a chance to dazzle you. Call us toll-free or send us the coupon.

Signetics. Surprisingly, the leader.





## 68000 Peripherals Conceived and Designed by Signetics

PART #		DESCRIPTIONS	Samples Available
68154	IGOR	Interrupt Requestor	NOW
68155	IVHAN	Interrupt Vectorizer and Handler	NOW
68172	BUSCON	VMEbus Master/Slave Controller	NOW
68175	BUSMAS	VMEbus Master	NOW
68430	DMAI	Direct Memory Access Interface	NOW
68454	IMDC	Intelligent Multiple Disk Controller	NOW
68459	DPLL	Disk Phase Locked Loop	NOW
68562	DUSCC	Dual Universal Serial Communications Controller	NOW
68652	MPCC	Multi-Protocol Communications Controller	NOW
68653	PGC	Polynomial Generator Checker	NOW
68661	EPCI	Enhanced Programmable Communications Interface	NOW
68681	DUART	Dual Universal Asynchronous Receiver/Transmitter	NOW
68905	BMAC	Basic Memory Access Controller/16 bits	NOW
68906	BMAC	Basic Memory Access Controller/32 bits	NOW
68920	MAC	32 bit Memory Access Controller.	Late 1985

Yes, please rush me more information on the Signetics 68000 family of peripherals.

Name \_\_\_\_\_

Position \_\_\_\_\_

Company \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Phone \_\_\_\_\_

Send coupon to: Signetics Corporation, 811 E. Arques Avenue, MS/27  
P.O. Box 3409, Sunnyvale, CA 94088-3409

EDN041786 SS

# VLSI from Signetics

a subsidiary of U.S. Philips Corporation

800-227-1817 Ext. 914D

Ask about a Signetics design seminar in a city near you.


CIRCLE NO 182

# LEADING the WAY!





# Unbeatable logic

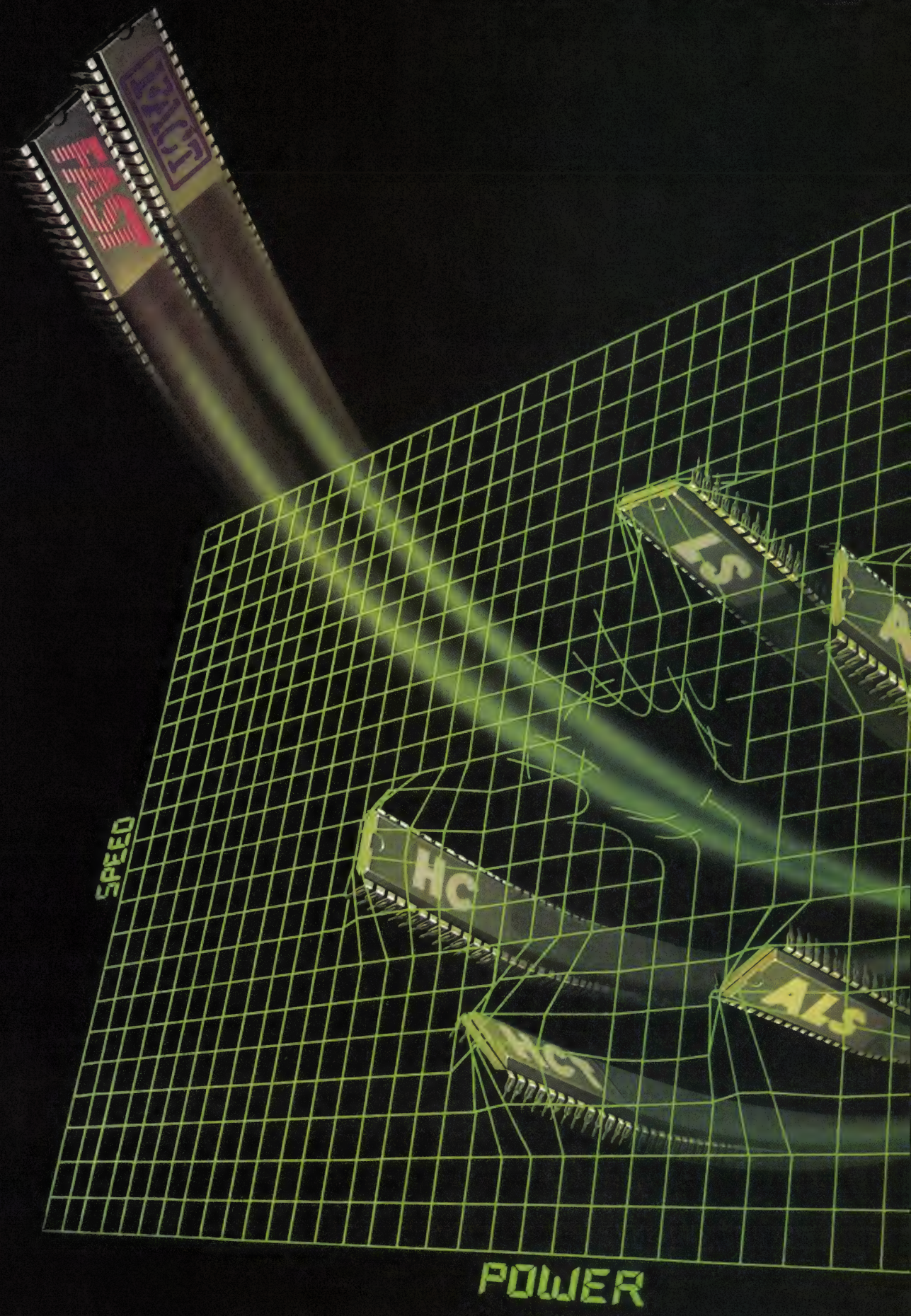



In today's logic arena, one team is the hands down winner in the competition against LS, AS, ALS, HC, HCT and S technologies:

FAST™ and FACT from Fairchild. Individually, they're the industry giants in bipolar and CMOS logic. Together, they're the reigning choice for speed/power superiority in virtually any logic application.

### **FAST. The logic is undeniable.**

Consistency makes FAST the first choice of designers for speed-critical paths. It offers excellent speed/power performance—3ns gate delays and up to 64mA output drive. And you can choose from a broad line of the most popular, useful functions: over 100 SSI, MSI, and LSI devices.

As the leading Advanced Schottky TTL family, FAST provides all the processing and packaging options you need. Including our new SOICs, and one of the broadest selections of JAN-qualified parts in the industry.

### **The FACTs speak for themselves.**

Fairchild Advanced CMOS Technology (FACT) features the lowest power consumption in the industry,

along with the highest noise immunity available.

FACT also has more complete specs than any other CMOS logic technology. Including guaranteed latch-up and ESD specifications. Plus dynamic output current specs that allow you to drive low-impedance

transmission lines, and guarantee incident wave switching.

And speed? FACT devices are manufactured with the Fairchild 1.2-micron process, resulting in CMOS logic with typical operating frequencies of 150 MHz—the industry's fastest.

### **Together, they're unbeatable.**

With TTL-compatible inputs, FACT's ACT devices interface directly with FAST to optimize speed and power in a way no other technology can equal. Which eliminates the need to make speed or power trade-off decisions required with any single technology. Best of all, FAST and FACT are both available from the high-performance, high-technology logic leader:

For more information, call The Fairchild Customer Information Center at 1-800-554-4443. And ask for your free FACT and FAST Data Books and current availability guides.

FAST and FACT. A breakthrough in teamwork the competition can't keep up with.

© 1986 Fairchild Semiconductor Corporation  
FAST (Fairchild Advanced Schottky TTL) and  
the FACT (Fairchild Advanced CMOS Technology)  
logo are trademarks, and the FAST logo is a  
registered trademark of Fairchild Semiconductor  
Corporation. Ad Packet Code C07

## **We're taking the high ground.**

## **FAIRCHILD**

A Schlumberger Company

CIRCLE NO 183



# Experience Counts.

American Automation has designed more emulators than C Language for selected

For each EZ-PRO emulator, American Automation provides complete software support: macro cross-assembler, linker, symbolic debugger.

Count on EZ-PRO from American Automation for the features you need for your projects, including Deep Trace,<sup>TM</sup> 4,096 real-time events, 256 break-points with zoning, complex triggering, on-line assembly/disassembly.

CENTRAL PROCESSORS:						
<b>Intel:</b>	8031	<b>Motorola:</b>	<b>Hitachi:</b>	<b>Rockwell:</b>		
	8032				6301	6502
	8035				6303	6503
	8039				6309E	6504
	8044				64180	6505
	8048					6506
	8049					6507
	8050					6512
	8051					6513
	8052					6514
	8085A/A-2			6515		
	8086					
	8088					
	80186					
80188						
80286						
<b>Harris:</b>	80C86	<b>NEC:</b>	<b>Zilog:</b>	<b>Signetics:</b>		
	80C88					
	V20	Z80A				
	V30	Z80B				
		Z80H				
		Z8001				
		Z8002				
			<b>National:</b>			
			NSC800			

\*Connected to PC  
with MSDOS 3.1

IBM is a trademark of  
International Business Machines, Inc.



## Varied Electro/86 program will emphasize IC- and system-design topics

Joanne Clay, *Staff Editor*

Sessions on IC and system design will highlight the Electro/86 conference, which will cover a wide variety of technical subjects. The conference, which will be held from May 13 through 15, 1986, at the Bayside Exposition Center and World Trade Center in Boston, MA, will include talks on the latest developments in semicustom ICs, ASICs, logic arrays, VLSI circuits, memory technology, fault simulation, packaging methods, interconnect technology, and other subjects.

Engineers interested in IC design will want to attend the discussions

on application-specific ICs. As participants in **session 4** will report, IC manufacturers are making many of the standard VLSI functions available as macrocells for their standard-cell libraries. By incorporating these macrocells in semicustom ICs along with random logic, manufacturers can now actually build a system on a chip.

ASICs are becoming increasingly important for OEMs who wish to create competitive systems, as speakers in **session 7** will point out. They'll discuss how OEMs can maximize the benefits of ASICs by understanding the choices they must make in system design, ASIC prod-

uct selection, CAE design tools, and vendor interfaces.

Individuals interested in semicustom-IC design will also want to attend **session 1**, which will focus on choosing design centers for custom- and semicustom-IC design. Lecturers at this session will explore the differences between manufacturer, distributor, and independent design centers. They'll also consider the tradeoffs—including multiple sourcing, technology sources, speed, power, turnaround time, and cost—involved in choosing a design center or doing designs in house.

The ever increasing complexity of LSI/VLSI designs is making fault

### ELECTRO/86 PROFESSIONAL PROGRAM BAYSIDE EXPOSITION CENTER BOSTON, MA

		ROOM A	ROOM B	ROOM C
TUESDAY MAY 13	9:00 AM TO 11:00 AM	1 CHOOSING A DESIGN CENTER FOR YOUR CUSTOM/SEMICUSTOM SYSTEM DESIGN	2 THE STRATEGIC DEFENSE INITIATIVE IN PERSPECTIVE	3 PERSPECTIVES ON SURFACE MOUNTING IN THE UNITED STATES
	12:30 PM TO 2:30 PM	4 ADDING VLSI FUNCTIONS TO STANDARD CELL LIBRARIES FOR APPLICATION-SPECIFIC IC DESIGN	5 ENGINEERING EDUCATION—WHAT'S WRONG, AND WHAT NEEDS TO BE DONE TO CORRECT IT?	6 HIGH-PERFORMANCE INTERCONNECT TECHNOLOGY: TAPE AUTOMATED BONDING (TAB)
	3:30 PM TO 5:30 PM	7 ASIC: CHOICES FOR A NEW GENERATION	8 SIGNAL-FLOW ANALYSIS*	9 SURFACE MOUNTING WITH INTEGRATED CIRCUITS
	9:00 AM TO 11:00 AM	10 RECENT ADVANCES IN DISCRETE MOS-GATED POWER STRUCTURES	11 VLSI DESIGN WITH SILICON COMPILERS	12 BEYOND MEMORY—DIVERSE APPLICATIONS OF ELECTRICALLY ERASABLE MEMORY TECHNOLOGY
WEDNESDAY MAY 14	12:30 PM TO 2:30 PM	13 POWER-IC AND SMART-POWER-IC TECHNOLOGY	14 AN OVERVIEW OF OFFSHORE OPPORTUNITIES FROM FOUR WORLD AREAS	15 THE FASTEST SILICON TODAY—BIPOLEAR ECL
	3:30 PM TO 5:30 PM	16 HOW BRUSHLESS DC MOTORS ARE COMING OF AGE IN THE WORLD TODAY	17 GOING PUBLIC	18 RECENT DEVELOPMENTS IN LOGIC-ARRAY TECHNOLOGY
	9:00 AM TO 11:00 AM	19 GROUNDING AND SHIELDING ELECTRONIC INSTRUMENTATION*	20 COMMUNICATION FUNDAMENTALS IN FLEXIBLE AUTOMATION*	21 SYSTEM IMPLICATIONS AND APPLICATIONS RESULTING FROM RECENT DISK-CONTROLLER-IC TECHNOLOGY ADVANCES
THURSDAY MAY 15	12:30 PM TO 2:30 PM	22 THE WHYS AND WHEREFORES OF THE TRANSFER OF TECHNOLOGY	23 THE NEXT GENERATION OF PROGRAMMABLE LOGIC DEVICES WILL LAUNCH A NEW ERA IN SYSTEM DESIGN—I	24 FAULT-SIMULATION TECHNIQUES AND TESTABILITY ANALYSIS
	3:30 PM TO 5:30 PM	25 RADAR—LATEST DEVELOPMENTS AND FUTURE TRENDS*	26 THE NEXT GENERATION OF PROGRAMMABLE LOGIC DEVICES WILL LAUNCH A NEW ERA IN SYSTEM DESIGN—II	27 NONSTANDARD ATMOSPHERIC EFFECTS ON RADAR- AND COMMUNICATION-SYSTEMS PERFORMANCE

\*MINITUTORIALS



# TECHNOLOGY UPDATE

simulation and testability analysis more and more important. Participants in **session 24** will investigate and redefine the problem of testability analysis by presenting appropriate fault models for these VLSI circuits. The speakers will discuss the various solutions presented by leading researchers in the field and will evaluate the solutions from a user's perspective.

The next generation of programmable-logic devices (PLDs) will be the topic of **sessions 23 and 26**, which will run in series. Speakers at these sessions will discuss the architecture of the new devices and investigate advanced software tools and new design techniques for PLDs.

The use of monolithic ICs to re-

place discrete circuits and logic in driving high-voltage or high-current resistors, capacitors, and inductive loads will be covered in **session 13**. Participants will discuss these monolithic-IC technologies and delineate the strengths of each in terms of their benefits for the user and their parametric performance.

Also related to IC design is **session 9**, which will investigate surface mounting with ICs. Session participants will cover relevant issues in surface-mount technology, such as packaging trends, standardization, electrical characteristics, the reliability of components and assemblies, computer-aided design, and automatic placement. **Session 3** will also look into surface mounting. It will present perspec-

tives and trends in the US from the viewpoints of a professional forecaster, a successful user of the technology, a passive-component supplier, and a supplier of active components.

The presentations related to system design include **session 12**, which will investigate applications of electrically erasable memory technology in nonmemory products. **Session 15** will review the bipolar ECL devices currently available to the system designer, and **session 21** will consider the system implications and applications of recent advancements in disk-controller ICs. Speakers at this session include disk-controller-IC users, who will indicate how system designers can use the technological changes in

## Mini/Micro Northeast-86

Sessions on data communications and microprocessors will predominate at Mini/Micro Northeast-86, a conference that targets system designers. The conference, which offered only nine sessions last year, will include 27 sessions this year and will take place concurrently with Electro at the World Trade Center in Boston, MA. Like Electro, Mini/Micro Northeast will feature four minitutorials, which will provide basic information in subjects that may be outside the area of specialization of many engineers.

Among the data-communication topics the program will cover is satellite data communication, the subject of **session 4**, a minitutorial that will present the current technology for data communications utilizing micro Earth stations. **Session 13** will focus on the current status of and new uses for fiber-optic systems in applications other than telecommunications. Participants in this session will report on fiber/cable status and describe applications of fiber-optic systems in data links and local-area networks (LANs).

For registrants who wish a general understanding of the theory, problems, and opportunities of the proposed Integrated Services Digital Network (ISDN), **session 1** will give an overview of ISDN architecture, standards, implementation, and services. The session, which will be presented from the point of view of a provider of ISDN services, will predict the future direction of the ISDN.

**Session 10** will also touch on the ISDN. Speak-

ers in this session will explore the industry's progress toward implementing communications standards that will allow today's office automation systems to integrate LAN, PBX, and ISDN services in a user-friendly and cost-effective manner.

Sessions on microprocessors will include talks on 32-bit high-end microprocessors, the topic of **session 15**. Lecturers at this session will examine the options available to system designers who are considering different types of core processors for their systems. Speakers will discuss 32-bit, reconfigurable, and RISC devices. **Session 12** will concentrate on the bus options available to the user of these high-level computer architectures.

Other microprocessor topics to be covered at Mini/Micro Northeast will include a discussion, in **session 18**, of programmable, single-chip digital signal processors (DSPs). Participants will give information on specific DSP products. In addition, **session 27** will probe new applications for low-cost microcontrollers, and **session 19** will investigate various methods of generating software for  $\mu$ Ps. Speakers will consider evaluation boards, emulators, computer generation, and high-level-language compilers.

Bit-slice microprocessors will be the subject of **session 3**, which will focus on new concepts in CMOS bit-slice  $\mu$ Ps and provide design information and examples of applications for these innovative  $\mu$ Ps. Concentrating on high-end systems that use bit-slice processors, **session 6** will present informa-



# TECHNOLOGY UPDATE

these ICs to their best advantage.

Finally, **session 18** will survey recent developments in logic-array technology, presenting the design choices available to engineers who are creating new systems. Other technical sessions in Electro's varied program will include discussions of interconnect technology, fault simulation, signal-flow analysis, and discrete MOS-gated transistors.

To explore technical areas outside your particular field, you may want to attend one or more of the minitutorial sessions at Electro/86. Engineers will have the opportunity to acquaint themselves with four technical fields in minitutorial **sessions 8, 19, 20 and 25**, which will be free of charge to conference registrants.

**Session 8**, on signal-flow analysis,

will review the classical theory of signal-flow graphs. At this session, Ronald E. Scott of Northeastern University will introduce the basic concepts of signal-flow analysis, describe the algebra for reducing them, and examine the derivation of Mason's general reduction formula. Scott will concentrate on presenting practical applications to solving problems in transistor circuits, op-amp circuits, servomechanisms, and electromechanical circuits.

**Session 19** will cover the principles involved in typical grounding and shielding problems. Bruce Wedlock of Lowell Institute School (Cambridge, MA) will explain grounding and shielding techniques that replace the trial-and-error method with sound, systematic

methods of shielding. This introductory-level tutorial will target electronic-circuit designers. Scheduled for the same time slot is **session 20**, which will focus on the fundamentals of machine-to-machine communication. Session chairman Robert E. Parkin and four other speakers will analyze such subjects as robotic movement and path planning, sensors, vision, and the implementation of flexible automation.

The final Electro minitutorial, **session 25**, will review the latest advancements—and predict future trends—in radar-system technology. Eli Brookner of Raytheon Co (Wayland, MA) will discuss monolithic microwave integrated circuitry (MMIC), ultralow-sidelobe antennas, synthetic aperture radar,

tion on a variety of applications from the systems-level approach to the design process.

In addition to sessions on data communication and  $\mu$ Ps, Mini/Micro will offer sessions on a number of other subjects, including computer-aided de-

sign, personal computers, telecommunications, process control, LSI devices, product standards, engineering management, automated testing, real-time systems, static RAMs, smart cards, Unix, and software design.

## MINI/MICRO NORTHEAST-86 PROFESSIONAL PROGRAM WORLD TRADE CENTER, BOSTON, MA

		ROOM A1	ROOM A2	ROOM A3
TUESDAY MAY 13	9:00 AM TO 11:00 AM	1 INTEGRATED SERVICES DIGITAL NETWORKS*	2 MICRO-TO-MAINFRAME COMPUTER-AIDED DESIGN	3 THE CMOS REVOLUTION HITS BIT-SLICE MICROPROCESSORS
	12:30 PM TO 2:30 PM	4 SATELLITE DATA COMMUNICATION*	5 USING THE PC FOR LOGIC DESIGN	6 ADVANCED APPLICATIONS USING NEW-GENERATION BIT-SLICE PROCESSORS
	3:30 PM TO 5:30 PM	7 TELECOMMUNICATIONS: INTERFACING TO THE NETWORK	8 ENHANCING YOUR PC ENGINEERING WORKSTATIONS	9 DESKTOP COMPUTERS IN PROCESS CONTROL*
WEDNESDAY MAY 14	9:00 AM TO 11:00 AM	10 INTEGRATING ISDN AND LAN SERVICES IN THE OFFICE ENVIRONMENT	11 PRODUCT STANDARDS: A GROWING CONCERN*	12 BUS WARS—THE 32-BIT FRONTIER
	12:30 PM TO 2:30 PM	13 OPTICAL COMMUNICATION	14 SMARTER CHIPS FOR BETTER DESIGN	15 32-BIT HIGH-END MICROPROCESSORS
	3:30 PM TO 5:30 PM	16 ENGINEERING MANAGEMENT TECHNIQUES FOR THE FUTURE	17 NONIMPACT PRINTING FOR INSTRUMENTATION, SCIENTIFIC, AND ENGINEERING APPLICATIONS	18 PROGRAMMABLE SINGLE-CHIP DIGITAL SIGNAL PROCESSORS
THURSDAY MAY 15	9:00 AM TO 11:00 AM	19 ALTERNATIVE METHODS FOR MICROPROCESSOR SOFTWARE GENERATION	20 PC-BASED CAE—IS IT THE TOTAL SOLUTION?	21 TOOLS FOR MIL-STD-1758A SOFTWARE DEVELOPMENT
	12:30 PM TO 2:30 PM	22 SOFTWARE DESIGN TOOLS FOR REAL-TIME SYSTEMS	23 COMPUTER-INTEGRATED TEST—CLOSING THE QUALITY FEEDBACK LOOP	24 FUTURE TECHNOLOGY OF SMART CARDS IS AVAILABLE TODAY
	3:30 PM TO 5:30 PM	25 USING UNIX IN A REAL-TIME ENVIRONMENT	26 SYSTEM AND APPLICATION IMPLICATIONS FROM FAST STATIC-RAM ADVANCES	27 NEW APPLICATIONS FOR LOW-COST MICROCONTROLLERS

\*MINITUTORIALS



# TECHNOLOGY UPDATE

adaptive array processing, the impact of VLSI circuits and VHSICs (very-high-speed ICs) on digital radar signals and data processors, systolic-array signal processors, silicon compilers, and residue arithmetic. Instead of giving detailed mathematics and derivations, the session will summarize key points of the technology.

Electro/86 registrants will also have the opportunity to explore some nontechnical subjects of interest to engineers. These five sessions will include discussions of various business, educational, and legal topics. For example, participants in **session 2** will undertake a comprehensive critical analysis of the President's Strategic Defense Initiative (SDI) proposal from technical, legal, computational, and political points of view.

Speakers in **session 5** will consider the growing mismatch between engineering education and proper preparation for engineering practice. The discussion will focus on identifying current inadequacies and misconceptions in engineering

education and recommending measures the engineering community can take to correct the problems.

Discussions in **session 14** will investigate opportunities for electronics firms to cut costs by manufacturing their products offshore. The session's four papers will inform the audience about specific opportunities in four offshore areas—the Eastern Caribbean, Mexico, Hong Kong, and Scotland.

**Session 22** will deal with the purchase and sale of privately developed technology and with obtaining US government-developed technology. Participants in this session will also address the issues of intellectual-property rights, commercial contracts, the law of sales, and making transactions that are beneficial to both parties. Finally, **session 17** will present a discussion of the advantages and disadvantages a company faces in undertaking an initial public offering of its stock.

The professional sessions represent only some of the events scheduled for Electro/86. The conference will also offer special tutorials, a

keynote breakfast, a marketing conference, and a film program.

Registrants can choose from four tutorials, which they can attend for a fee. The tutorial entitled "Topics on the strategic defense initiative" will explore the engineering problems associated with the SDI. "Personal-computer-based artificial intelligence/expert systems" will focus on tools for the effective, easy application of AI techniques by end users for solving nontraditional problems on 16-bit personal computers, especially the IBM PC. In the two remaining tutorials, industry experts will consider whether silicon compilers will render gate arrays obsolete and will explore new applications for LANs in business, industry, and science.

This year's keynote speech will focus on communications, which is the conference's theme. At the keynote breakfast, Robert Allen, chairman and CEO of AT&T Information Systems, will speak on "Integration and cooperation: The key to success in the information age." Allen will describe strategy and direction for his company as well as for the office-automation industry as a whole.

Another special event scheduled for Electro is a marketing conference entitled "Will electronics be the next shoe/textile industry?" At the conference, a 5-member panel will examine the trends in the electronics industry that are causing local companies to buy components and subsystems directly from offshore companies. The panel will also consider the effect of this trend on distributors and representatives, many of whom are being left out of the sales chain in such transactions. The panelists, who represent different viewpoints, will read brief statements and then answer questions from the audience. **EDN**

## Electro schedule and registration information

Electro/86 will take place Tuesday May 13 to Thursday May 15, 1986, in the Bayside Exposition Center, Boston, MA. Mini/Micro Northeast will take place at the same time in Boston's World Trade Center.

More than 1200 exhibits will be on display from 10 AM to 6 PM on Tuesday and Wednesday and from 10 AM to 5 PM on Thursday. Electro exhibits will be in both buildings; all Mini/Micro exhibits will be at the World Trade Center.

Complimentary-registration forms for Electro and Mini/Micro Northeast are available through any of the exhibiting companies and from many local engineers and manufacturers' representatives. Complimentary-registration forms must be received by April 25, 1986. Registration at the door for the conferences is \$10 for IEEE members, \$20 for nonmembers.

Fees for Electro tutorials range from \$160 to \$190 for IEEE or ERA (Electronic Representatives Association) members and from \$200 to \$230 for nonmembers. Tickets to Tuesday's marketing conference are \$30. Tickets to the keynote breakfast, which will be held on May 13 at 7 AM at Anthony's Pier 4 restaurant, are \$20.

For more information, contact Electro-Mini/Micro Northeast, 8110 Airport Blvd, Los Angeles, CA 90045. Phone (213) 772-2965.

Article Interest Quotient  
(Circle One)

High 509 Medium 510 Low 511



# There's only one signal generator that's a better value than the 6060A. The new 6060B.



## Price, features and performance. Judge the new 6060B by its specifications.

When we introduced the 6060A, it was without a doubt the best signal generator value on the market. With its unique architecture, this fully programmable synthesized RF signal generator offered the RF industry the performance it needed for design, testing and maintenance applications. Yet it was priced well below other generators in its class.

The new 6060B takes this remarkable signal generator another major step ahead.

### New wider frequency range.

The 6060B has an even wider output frequency range. Low end coverage is extended to 10KHz for VLF and LF applications and still maintains the capability to output frequencies up to 1050MHz.

## Better residual FM and amplitude accuracy.

Guaranteed amplitude accuracy is now  $\pm 1.0\text{dB}$  from  $+13\text{dBm}$  to  $-127\text{dBm}$ , improved from  $\pm 1.5\text{dB}$ . You can rely on precise amplitude control across the frequency range.

Residual FM performance specification has been improved by better than 30% in all bands. It is now guaranteed less than 10Hz rms (.3 to 3KHz) at 500MHz.

### Three options now included standard.

We've added three popular options to the standard 6060B model for much less than you'd pay for each separately. Now standard are: Non-Volatile Memory that can store 50 instrument settings up to two years without power, Reverse Power Protection, and Sub-Harmonic External Reference input.

## Good news on the bottom line.

Although we've boosted performance and standard features, the 6060B is still priced at a modest **\$4995\***. We think that makes it an unbeatable value in general purpose signal generators. Second to none.

For more information about the 6060B, call **1-800-426-0361** or contact your local Fluke Sales Engineer or Representative.

### Fluke 6060B

Frequency range	10KHz - 1050MHz
Amplitude range	+13dBm to -127dBm
Accuracy	$\pm 1.0\text{dB}$
Harmonics	$< -30\text{dBc}$
Spurious	$< -60\text{dBc}$
Modulation	AM/FM
IEEE-488 Interface, opt. 488 switch speed	$< 100\text{ ms, typ.}$


**FLUKE**®

\*Suggested U.S. price only


IN THE U.S. AND NON-EUROPEAN COUNTRIES: John Fluke Mfg. Co., Inc., P.O. Box C9090, M/S 250C, Everett, WA 98206, Sales: (206) 356-5400, Other: (206) 347-6100.  
EUROPEAN HEADQUARTERS: Fluke (Holland) B.V., P.O. Box 2269, 5600 CG Eindhoven, The Netherlands, (040) 458045, TLX: 51846.  
© Copyright 1985 John Fluke Mfg. Co., Inc. All rights reserved. Ad No. 4405-6060




# SIXTEEN TOUGH ASSIGNMENTS.

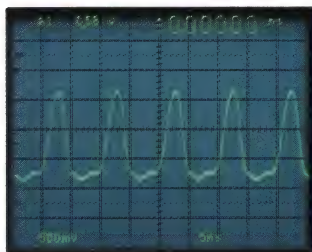

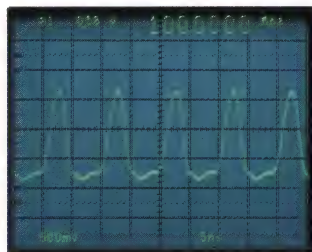
**A period measurement** is made on a 100 MHz clock using the extended accuracy and resolution of the Counter/Timer/Trigger in the 2465 DVS.



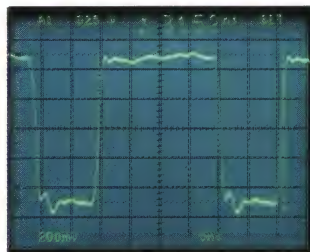
**A frequency measurement** is made with the same high precision. Simply press two buttons, and the period measurement on the left is converted to frequency.



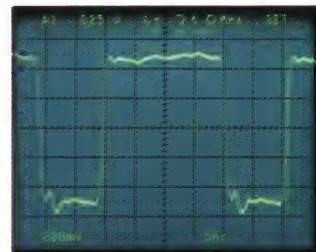
**Short time intervals** can be measured most accurately with the easy-to-use time cursors. They also make quick work of longer intervals, with 1% accuracy.



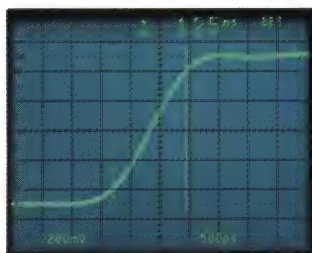
**Calculated frequency** takes only seconds. The time cursor measurement on the left can be converted to frequency with push-button ease and 1% accuracy.



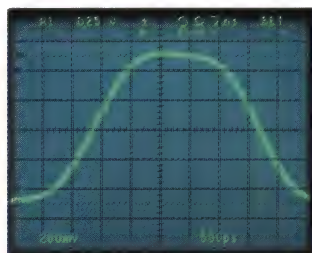
**This fast-pulse rise time** is nearly that of the scope. The 2465 achieves maximum bandwidth with minimum waveform aberrations. This level of pulse



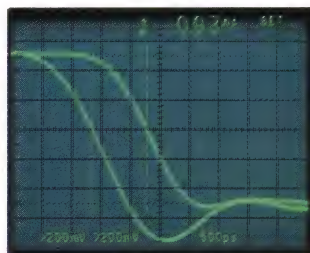
response ensures that **pulse width** and amplitude measurements on fast waveforms (above) truly reflect conditions in a circuit under test.



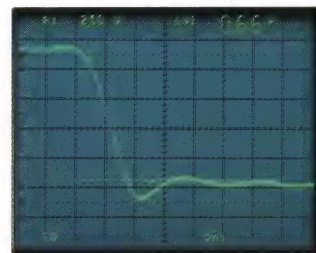
**Propagation delay** measurement accuracy is assured by built-in propagation delay matching. Delay between Channels 1 and 2 can be corrected to the probe tip.



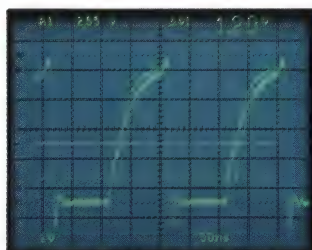
**Overshoot and ringing** measurement accuracy requires flat response in a probe/oscilloscope system. Tek probes and scopes are designed to work together.



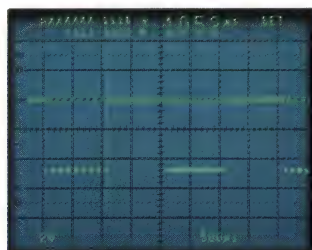
**Logic-level violations** can be spotted quickly on a TTL waveform (above) with measurement cursors set to define logic-level boundaries.



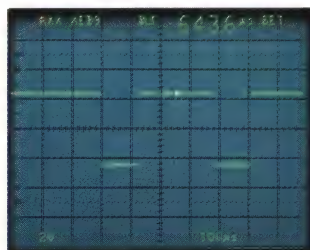
**The Word Recognizer** (with a binary word) is used to pick out a pulse train in a data stream. The time cursors measure pulse train duration.



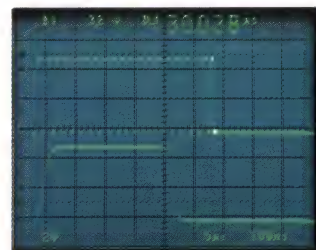
**Identify a word position.** The Word Recognizer (in HEX) is intensifying a word position and measuring delay relative to a waveform on another line.



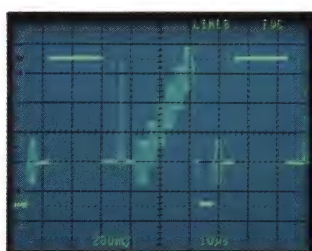
**Delayed sweep** is used to expand the last pulse in a pulse train. The intensified zone identifies the expanded pulse position.



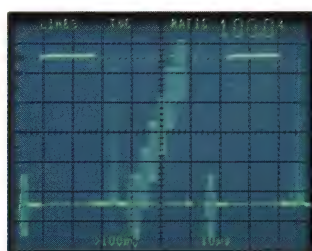
**TV line trigger** in the 2465 DVS displays a full-field composite test signal. The built-in TV clamp circuit removes hum and tilt on the ac-coupled video.



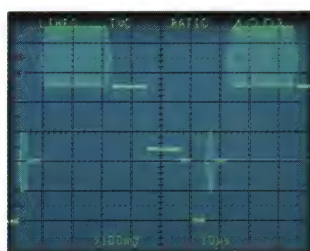**Calibrate cursors** in IRE units with variable attenuation. Blanking level to reference white level is defined as 100 IRE units in NTSC video.



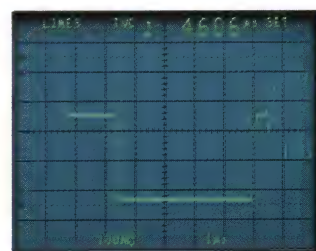**Burst amplitude** should be 40 IRE units in NTSC video. The cursors quickly measure other waveform amplitudes. Field triggering checks any line.



**Sync width** and blanking are common, easy-to-make timing measurements. Accurate time measurements can be made anywhere in a video system.



# FIVE EASY ANSWERS. THE TEK 2400 SERIES.



**You can simplify even the most complex measurements with the performance and convenience of Tek's 2400 Series family.**

No other portable scopes meet such diverse requirements in research and design, manufacturing and service.

**The 300 MHz 2465 and 150 MHz 2445 are at the foundation of the family.**

They include all the features that set a new high performance precedent. For example, standard delayed sweep  $\Delta$ -Time to 0.5% accuracy. Coupled sweep speeds to 1 ns/div in the 2445 and 500 ps/div in the 2465 for tough timing measurements. And four-channel capability for observing and troubleshooting logic circuits.

Best of all, these stand-alone scopes are proof that powerful capability doesn't have to be complicated. Time and voltage cursors for fast and easy measurements, CRT readouts showing waveform parameters and front

Features	2445	2465	2465 CTS	2465 DMS	2465 DVS
Bandwidth	150 MHz	300 MHz	300 MHz	300 MHz	300 MHz
Max. Sweep Speed	1 ns/div	500ps/div	500ps/div	500ps/div	500ps/div
Accuracy; Vert/Hor	2%/1%	2%/1%	2%/1%	2%/1%	2%/1%
Vertical Sensitivity	2 mV/div	2 mV/div	2 mV/div	2 mV/div	2 mV/div
Trigger Freq. Range	250 MHz	500 MHz	500 MHz	500 MHz	500 MHz
Trigger Modes	Auto Level, Auto, Norm, Single Sequence				
Counter/Timer/Trigger/Word Recognizer	*	*	STD	STD	STD
DMM	*	*	N/A	STD	STD
Video/TV	*	*	N/A	N/A	STD
Four P6131 Probes	*	*	STD	STD	STD
GPIO	*	*	STD	STD	STD
Rackmount	*	*	*	*	*
Warranty	3-year on parts and labor, including CRT				
Price†	\$3590	\$5350	\$7150	\$8400	\$9200

#### Software

TEK GURU for IBM PC/XT/AT and 2445/65/GPIO	\$595
EZ-TEK 2400 for TEK 4041 and 2445/65/GPIO	\$400

\*Configurable only at time of order. Additional cost required.

†Prices subject to change without notice.

IBM PC is a registered trademark and AT and XT trademarks of International Business Machines Corporation.

panel settings, and simplified trigger operation make these scopes a pleasure to use.

**Three specially configured, specially priced Special Editions offer enhanced measurement capabilities for both systems and stand-alone use.** At the top is the 2465 DVS with integral GPIO interface, DMM, Counter/Timer/Trigger/Word Recognizer, and Video measurement capabilities. Easily the most powerful portable ever developed.

**The 2465 DMS and 2465 CTS are special editions with different feature sets.** The 2465 DMS provides all the capabilities of the DVS except Video. The 2465 CTS provides all the features of the DVS except Video and DMM.

**Call your Tek Sales Engineer for a demo today!** Or call the Tek National Marketing Center toll-free, 1-800-426-2200. In Oregon, call collect, (503) 627-9000.

**Tektronix®**  
COMMITTED TO EXCELLENCE



# "I Got Mad As Hell And Decided Not To Take It Anymore. . ."

"My name is Roy Albano. I am a design services manager, whose responsibilities have ranged from selecting CAD systems to supervising engineers and PCB designers. My current employer, Diceon Electronics, Inc. of Irvine, California has been a leader in supplying state-of-the-art finished printed circuit boards to the majority of U.S. manufacturers—for applications in the commercial electronics industries. Throughout my many years of gaining knowledge and experience in PCB design, while working for other companies, **I went from observing laboriously tedious manual PCB layout methods to eventually ending-up a true believer in CAD as the only answer to improving efficiency and reducing product cost.** Countless times during this transitional period I was frustrated, had my designers spend long hours at the drafting boards and still, quite often, could not meet various design deadlines."

"So I recommended to one of my previous employers to get a CAD system, which was promising miracles and answers to all my PC design problems. We got this system and, after some time passed, I got mad. This CAD system fell far short of its seller's claims and left us basically operating nothing more than a glorified electronic pen and a screen to play with. So I looked long and hard and, in conjunction with other engineers, I decided to get a larger, seemingly far more sophisticated CAD system for PCB design. This was not at Diceon, but at another large electronics company in Southern California. The selected CAD machine utilized an automatic router, with solutions of at least (I was promised and verified it myself on small sample boards) 80-90 percent hook-up success. We were all impressed and bought it. We did not realize then that it would take us eight months to get familiar with this thing—although we were already fairly well experienced CAD users. Even after we had finally managed to understand the



Mr. Roy Albano  
Manager of Design Services  
Diceon Electronics, Inc.

"beast," we still ended up working manually nights and weekends to accomplish the job. And the last minute engineering changes—requested invariably just as we were about to complete the design—drove us bananas. That CAD system could not assist us in solving changes within a reasonable time frame. I think we spent so much time at work trying to accomplish the design tasks, satisfy the engineers, and fight our CAD system, that even my dog stopped recognizing me and would not let me into my own house without me first showing him proper I.D. . . ."

You see, a 90 percent routing solution sounds great, provided the PCB has about 300-400 traces to be connected. But today's typical PC boards have an average of 2000-6000 traces to be connected, and the missing 10 percent represents 400-600 lines that have to be "stitched in" manually. And these last lines are the most difficult ones, taking up the most time and yes, even a designer's zest for life.

"Yet, I continued hearing of great new things in CAD (which did not materialize) and I looked at some ten more CAD systems over the past 5 years. They were all long on promises, but short on true performance. **By this time, I knew well how to put CAD**

systems to the test through my own benchmark—still nobody seemed to fill the design needs we had. I spent a lot of time visiting other electronics companies, discussing this dilemma with other PC designers, service bureaus, CAD users, and their managers and also visiting individual CAD vendors. In short, I gained a lot of additional experience in CAD and what it should do regarding the latest design criteria."

To the majority of decision makers in the fast-changing electronics industry, it is crystal clear that any company which can design a PCB faster than their competitors will be able to bring out a newly finished product to market even faster—thus gaining invaluable marketing, sales, and time advantages.

"My present employer, Diceon Electronics, Inc., can easily qualify as one to consistently offer new, reputable, and reliable products to the marketplace. In order to get these new products to market as quickly and efficiently as possible, we needed a superior CAD system. So I got mad as hell and decided not to take it anymore and began demanding (quite vocally) from the existing CAD vendors to provide us with a meaningful tool for PC design—but I got nowhere. . . .**until I discovered Calay!**"

"By pure coincidence, about 2 years ago, I heard from someone about a new CAD system recently introduced in the U.S. called Calay. This was in 1983 and we saw no flashy ads, no evidence of aggressive marketing—not even a salesman from Calay to call us. After a few inquiries, we found out that some of the best service bureaus and the toughest large manufacturers of electronic equipment were in fact already using a Calay VO3 System for their PC designs. We made numerous phone calls and what we heard from these existing



# • • • Until I Discovered Calay™

users of Calay sounded almost too good to be true. We called Calay and spoke to Dick Finn, their General Manager, and the ensuing conversation prompted me to make sure that, this time (in addition to our other engineers), I was personally going to verify the facts. I did not want to spend big money on promises alone."


Diceon people contacted Wolfgang Schenke, the Calay Vice President of R&D, and arranged a benchmark with him. Calay's benchmark criteria were not like anything they'd ever done or heard of before. To maintain true results and credibility, the Calay people insisted that no information be given about the test by Diceon to Calay ahead of Roy's arrival at Calay. No net list, no placement, no component description, not even any portions of schematics or board outline. The job was to be done "from scratch"—thus simulating the Diceon production environment, in order to get a meaningful assessment of Calay capabilities.

"Since that time, we have utilized exclusively Calay systems for our facility—and Diceon Electronics has grown and continued to be viewed as one of the best recognized and profitable technological leaders in its field. Calay's technical staff has been supporting us fully and we learned to appreciate their candor, straightforwardness, knowledge, and credibility. The Calay System is the only one so far I have had full confidence in. No more long hours and weekends spent on designs—and I became friends with my dog again. . . I also experienced the awakening that Calay is really what CAD is all about, and we got our toughest PC boards designed faster on Calay and, as a result, we get our product out on the market ahead of our competition."



Mr. Chris Christofferson  
Manager of Engineering Services, Sun Microsystems, Inc.  
Mr. Richard A. Finn  
President & CEO, Calay Systems, Inc.

Typically, PC boards are Calay-routed day, night, or during weekends without operator presence or assistance. Even complex digital or analog boards, multilayer boards, chip carrier (SMD) boards, odd-shaped boards, and those very dense boards. No more long hours to find the solution—the Calay VO3 CAD System does it 100 percent in most cases. The system is magnificently user friendly, simple and user definable. It is even more efficient when interfaced to any CAE workstation for schematics generation, including back-annotation. And the Calay router is truly AWESOME. Coupled with on-line design rule check and easy creation of new library components, high resolution graphics, and powerful interactive features the Calay System offers not only the premier solution, but also the complete solution for PCB design. Starting at the net list and the component

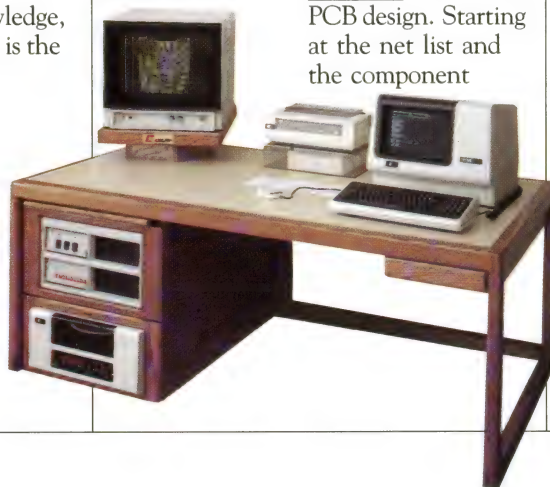

creation and placement, to the routing and post processing documentation, Calay reliably takes the user from the beginning to the successful end of the total design cycle. Users don't have to worry about engineering change orders anymore because Calay's flexibility allows them to make all the changes they want without requiring them to start the design or routing process all over again.

"As a result, Diceon products deliver more state-of-the-art capabilities than our competition. In fact, our cost to design and manufacture PC boards is extremely reasonable. You see, with the Calay System, we get both fast turnaround and boards that can be economically manufactured."

"At Diceon Electronics, we can't afford to be second best. That's why we have Calay CAD Systems in our design engineering department supporting us day-in and day-out. Maybe you can't afford to be second best either. . ."

So if you're mad as hell, you don't have to take it anymore. Do what Roy did—give Calay a call.

Corporate Headquarters:  
CALAY SYSTEMS, INC.  
2698 White Road  
Irvine, CA 92714  
(714) 863-1700, Telex 6711321

Regional Offices:  
4633 Old Ironsides, Suite 403  
Santa Clara, CA 95054  
(408) 748-1901  
70 Walnut Street  
Wellesley, MA 02181  
(617) 239-8111


European Contact:  
CALAY EUROPE  
6050 Offenbach/Main  
Heinrich-Krumm Str. 5  
Tel. (0611) 892-065, Telex 041 52775  
West Germany



Advanced CAD for Printed Circuit Board Design

©Copyright, 1985 Calay Systems, Inc.



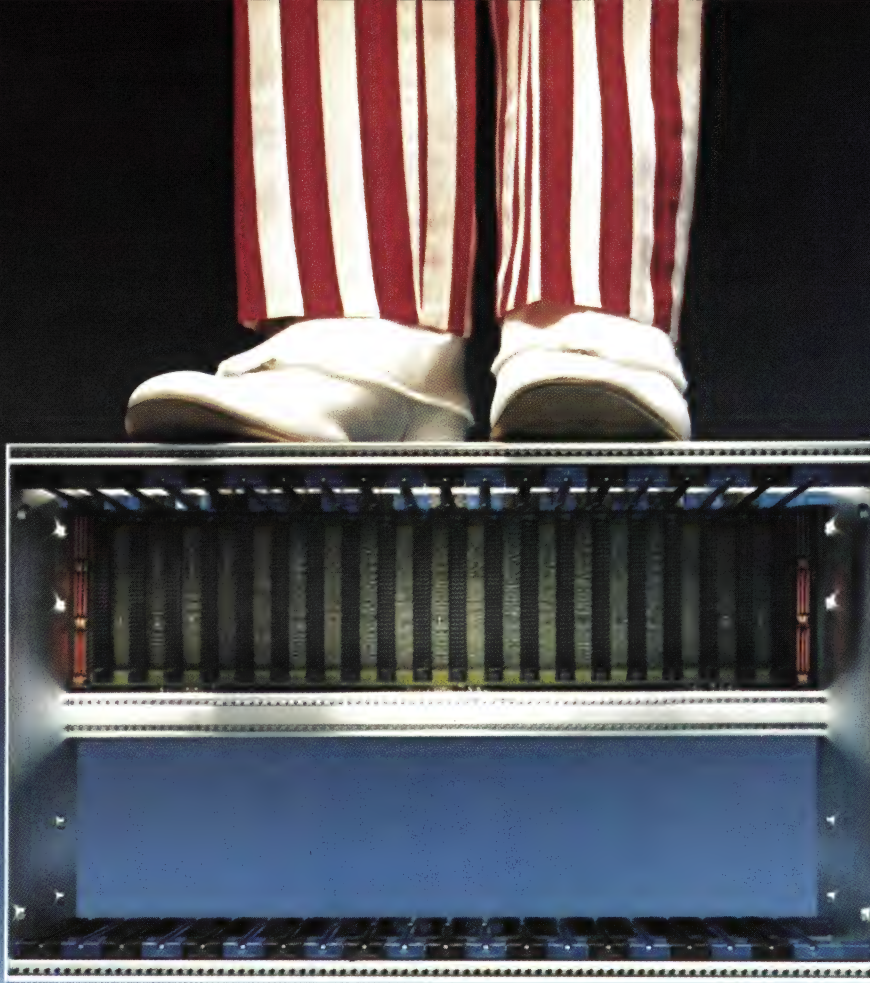

# The Americanized VME Card Cage. We Stand On Our Reputation.

One reason Electronic Solutions became the world's leading supplier of Multibus card cages is that five generations of improvement gave our cages a reputation for indestructibility second only to a rock.

So when we decided to build an Americanized version of the VME card cage it was only natural that we would want to build it the same way. Because European kit-style cages don't measure up when it comes to strength.

Introducing Electronic Solutions V-800 Series VME Card Cages. We took a stand for ruggedness and rigidity. Right on top of them — to prove that a V-800 card cage could maintain its precise card alignment through thick and thin.



Rigidity gives your VME cards less room to flex and that means less room for things to go wrong. Connectors stay connected. And so do printed circuits. So when your system is shipped, moved, or dropped from a forklift the odds are a lot better that it will remain functionally intact.

But that's not the only part of our reputation we built into our VME card cages.

Our V-800 Series cages feature advanced, low-noise, high-performance backplanes designed for the fastest VMEbus signals. You can mount our new cages on any axis. And you can use our exclusive center adapter to convert any double slot to two singles or any triple size slot to a double and a single.

Electronic Solutions V-800 Series VME card cages. Step up to the best there is.

Call toll free or write for complete information today.



**Electronic  
Solutions**

9255 Chesapeake Drive, San Diego, CA 92123 (619) 292-0242 • Telex II (TWX): 910-335-1169

**Call toll free: (800) 854-7086 In Calif. (800) 772-7086**

CIRCLE NO 187



## Networking products link VAXs, IBM PCs, and Intel $\mu$ P development systems

Intel  $\mu$ P development systems and software now work with host computers other than Intel products. The Open Development Networking products link DEC VAXs, IBM PCs, and the company's development systems and System 310 computers.

The Open Development Networking products presently include two pieces of hardware and two communications programs. The hardware products are the Network Resource Manager (NRM) and the Compilengine. The two software packages, VAX Link R2.1 and PC Link, connect the NRM with VAXs


and PCs, respectively, via Ethernet.

The NRM is a 560M-byte file server with its own local processors and two Ethernet ports. Any workstation on the network can gain access to files stored in the NRM's protected hierarchical file system; this operation is transparent to the user. The NRM also handles shared resources such as tape archiving and spooled printing. In addition, the NRM can distribute job control to idle development systems in the network, to the VAX, or to the Compilengine.

The Compilengine is a specialized

computer that handles time-consuming compilations and module linking. According to Intel, the Compilengine runs typical  $\mu$ P compilation jobs 35% faster than an IBM PC/AT, twice as fast as a VAX 11/780 (with a single user), and five times faster than an Intel Series IV development system.

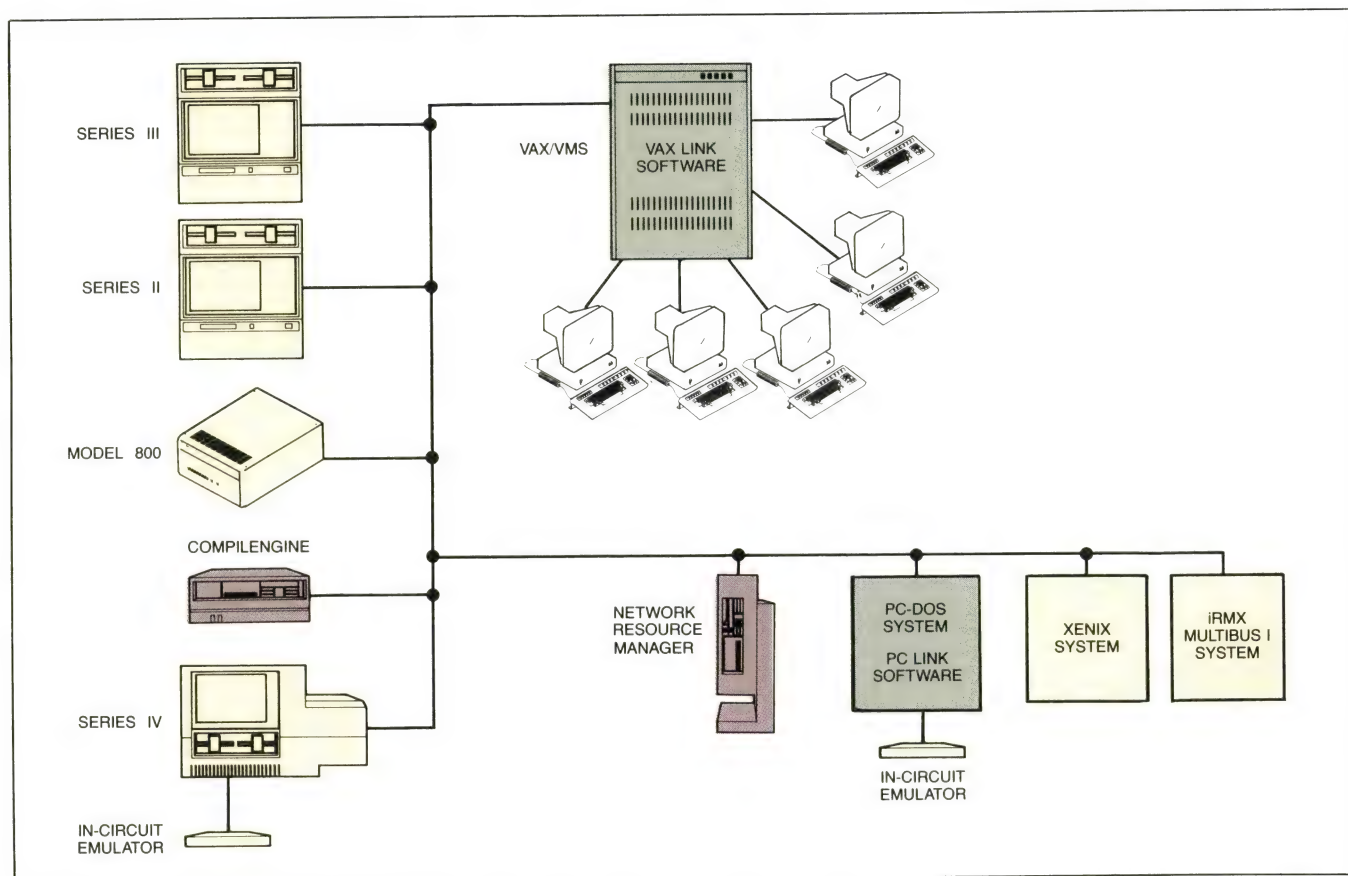The VAX Link R2.1 software package enables file copying and distributes job control between VAXs running VMS R4.2 and the Intel NRM. The VAX Link software uses a VAX computer's Ethernet board for I/O and is compatible with—but not a part of—Decnet.



*Now you can share software-development tasks among VAXs, IBM PCs, and Intel  $\mu$ P development systems that are all connected in an Ethernet network. The Network Resource Manager, the Compilengine, and the VAX Link and PC Link software packages combine to let you share files and distribute job control among the available resources.*



# Presenting a breakthrough in relay miniaturization: The moving loop.


The size of our moving loop relays will surprise you. Our DPDT G5A, for instance, uses only two-thirds the board area of similarly rated relays, yet it switches up to 1 A at 30 VAC, VDC. Developed to simplify PC board layout, it measures just .31"H x .63"W x .39"D.

The G5A's space-saving secret is an advanced armature design that eliminates the need for a pivoting core. This design offers:

- Higher coil sensitivity • Low power consumption (200 mW)
- Fast response, less contact bounce • Higher coil overvoltage limits, reduced electromagnetic interference.
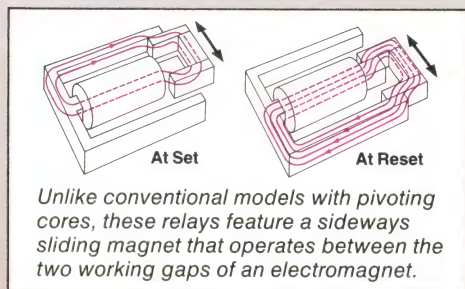
## Call 1-800-62-OMRON

Or write: One East Commerce Dr., Schaumburg, IL 60195



# OMRON

We're in control

## UPDATE

The PC Link software works with an add-in Ethernet controller plugged into an IBM PC/XT or PC/AT. The board has its own local processor and memory. The PC user gains access to files on the NRM as though they were stored on PC-DOS drives. The software also supports remote printing. The software's file servers communicate with Intel Xenix or RMX-86 systems. The company also offers a standard Multibus I Ethernet communications board that allows you to connect board-level systems to the network.

The products are based on the International Standards Organization's 7-layer Open Systems Interconnect model for networking. The NRM with a 40M-byte hard disk costs \$14,995—\$23,995 with a 140M-byte disk and a 60M-byte streaming tape drive. The Compilengine costs \$13,995. The PC Link software and add-in board together cost \$1250, and the VAX Link software sells for \$7500.—**Charles H Small**

Intel Corp, Literature Dept  
W274, 3065 Bowers Ave, Santa Clara, CA 95051. Phone (408) 987-8080.

Circle No 732



# Arbitrary-waveform synthesizer creates 50-MHz waveforms

The \$24,000 Hewlett-Packard HP 8770A arbitrary-waveform generator creates waveforms that have significantly higher bandwidths than any other available generator can manage. The 8770A generates 50-MHz (max) waveforms at 125M samples/sec with 12-bit resolution; all other available 12-bit arbitrary-waveform generators run at less than 40M samples/sec.

The generator's 50-MHz analog output ranges from 2V p-p (+10 dBm) down to -100 dBm. Harmonic distortion is less than -50 dBc, and nonharmonic distortion is below -60 dBc. Two-tone linearity is under -57 dBc for a 124-kHz separation, and single-sideband phase noise for a 10-MHz signal is typically -125 dBc/Hz at a 10-kHz offset.

At 125M samples/sec, the instrument could run through its sample memory very quickly. But the 8770A combines a 128k-sample pattern memory with a sequencing

function that can repetitively reuse specified portions of memory to provide extended output waveforms of long duration.


The 8770A and the \$5000 HP 11775A waveform-generation software compose the waveform-synthesis system. The software package runs on HP 9000 Series 200 computers. With the aid of the software, you can create and modify complex waveforms. The package's FFT routine allows you to specify your waveform in either the time or frequency domain.

In operation, you define your waveform mathematically, describing its segments or constructing them by using menu selections. Delivery, 16 weeks ARO.

—Charles H Small

Hewlett-Packard Co, 1820 Embarcadero Rd, Palo Alto, CA 94303.  
Phone local office.

Circle No 730

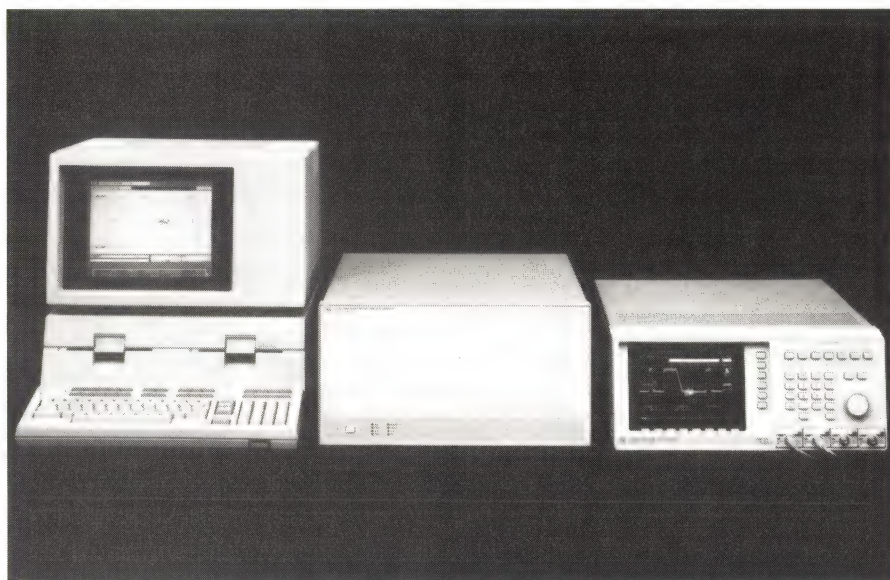

**This HP 8770S arbitrary-waveform synthesizer system** comprises an HP 9836A computer (left) running the HP 11775A waveform-generation software, and the HP 8770A arbitrary-waveform synthesizer (center). The digitizing oscilloscope on the right displays the synthesizer's output.



## Low-cost STE Bus-based development systems target 8/16-bit I/O and control designs

The STE Bus-based PII-DS-S1 and PII-DS-S2 development systems allow you to build 8/16-bit  $\mu$ C designs for low-cost, STE Bus I/O and industrial-control applications. The system enclosure has room for the development-system boards and for a number of target-system boards as well. The basic development-system components include a CPU board, associated development software, an SCSI board, a disk-controller board, and a system enclosure with two floppy drives and a Winchester drive—all for less than \$5000.

STE Bus systems use single-height Eurocards and a substantially simpler interface than the VME Bus. Because of the Eurocard form factor, an STE Bus system is physically compatible with VME and Multibus II systems and can even serve as an I/O subsystem for the high-end buses. Designers of STE Bus-based I/O and control systems now have a variety of general-purpose CPU, peripheral-controller,

memory, and other boards to choose from. The PII-DS-S1 and -S2 development systems provide the engineer with a means for designing the custom boards typically required in the I/O and control environments.

The two development systems offer identical hardware with the exception of the CPU boards. The -S2 CPU board includes an 8-MHz Motorola 68008  $\mu$ P, 512k bytes of dynamic RAM, and two serial channels. The -S1 CPU board has two DMA channels, two serial channels, an MMU, 256k bytes of dynamic RAM, and a 6.144-MHz 64180. Both boards act as the bus arbiter and system controller in an STE development system.

Development-system peripherals include dual 3.5-in., 1M-byte floppy disks and a 3.5-in., 25.5M-byte (unformatted) Winchester. An STE Bus SCSI host adapter interfaces to the Winchester; a dedicated controller handles the floppy-disk drives.


A 19-in. rack-mountable chassis provides the mechanical backplane

for all the development-system components. The standard development system only uses three of the backplane's 10 STE Bus slots, so you can use the backplane to hold part or all of your target system. The standard system comes in a 21-in. ruggedized enclosure. It operates from a 250W switching power supply.

Software options vary between the two development systems. The 68008-based CPU board includes the multiuser, multitasking PDOS operating system. For 64180-based systems, the user may choose the CP/M+ or the ZRDOS operating system. All operating systems include some development tools, such as an editor, linker, and assembler. Software offerings from a variety of vendors support the three operating systems.—**Maury Wright**

*Performance Interconnect Inc., 8950 Villa La Jolla Dr, Suite 2144, La Jolla, CA 92037. Phone (619) 457-0665.*

**Circle No 729**

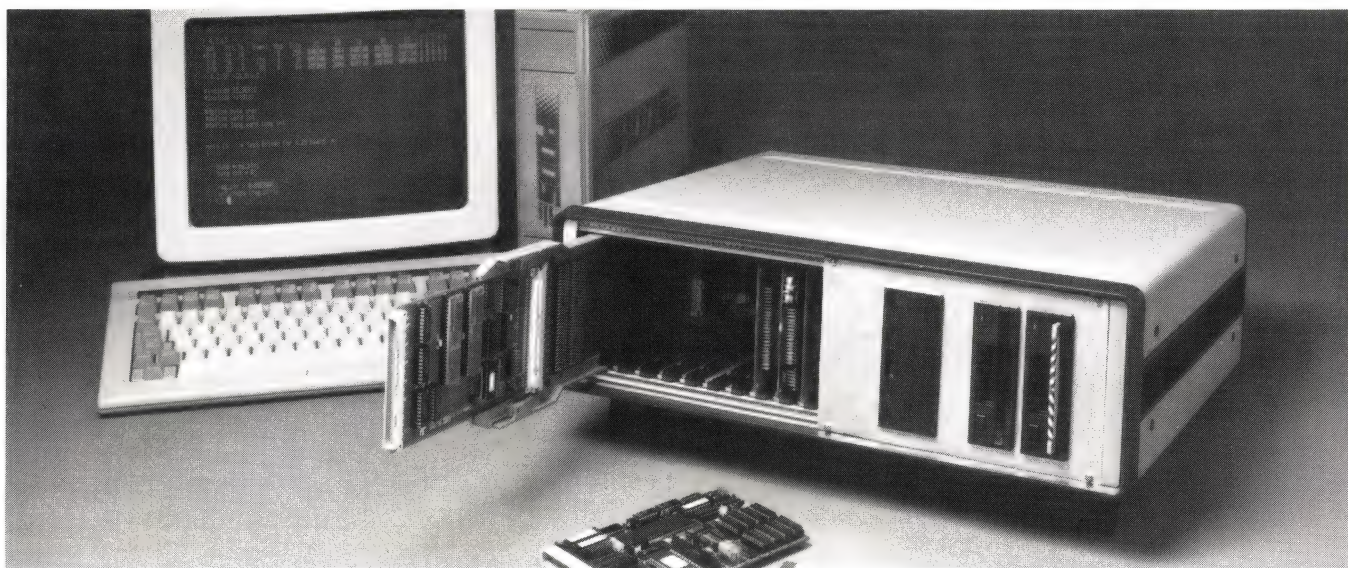

*Because the basic system boards occupy only three of 10 available slots in the system backplane, the PII-DS-S1 and -S2 development systems accept part or all of your STE Bus I/O or control target system.*





# Hughes' Connector Line: When You Care Enough to Spec the Very Best.

These hi-rel, hi-density connectors serve the military everywhere—eloquent testimony to their versatility, reliability and exclusive features.

- Highest contact density, with 110 contacts to the square inch.
- Super-sealing, with seals on the contacts in some environmental types.
- Positive polarization with our exclusive Polar-Hex center jackscrew coupling.
- MIL-C-28840 and MIL-C-55302 versions that incorporate superior design features and qualify to spec limits.

- And our MIL-C-28876 fiber optic connector, the only multi-channel type to meet mil spec.

For more information about our standard line, phone Bob Torres at 714-660-5829. In England, Hugh McNally at 932-47262.

**HUGHES**  
AIRCRAFT COMPANY

CONNECTING DEVICES DIVISION  
Industrial Electronics Group



## Electrically erasable standard memory cells yield custom ICs with nonvolatile memory

You now can create a custom IC that includes nonvolatile memory by using the first available electrically erasable standard memory cells. These cells are compatible with the manufacturer's digital and analog standard cells, so you can integrate linear and memory functions with digital logic. The nonvolatile memory cells allow you to add configuration and adjustment features to your circuit.

The electrically erasable cells are fabricated using a 2- $\mu$ m CMOS technology. The vendor has integrated as many as 8k bits of electrically

erasable memory on one IC, although it stresses that the cells are most useful for small amounts of storage. Large memory blocks use silicon inefficiently because of the relatively large size of the electrically erasable cell. The memory cells have parallel data-storage bits for redundancy (ie, each memory cell stores its data on two separate transistors), thereby increasing the effective yield of the IC. Differential sensing allows the overall chip supply voltage to vary between 3 and 6V. The cells have the typical endurance specifications for electrical-

ly erasable devices—10,000 cycles and 10-year data retention.


In addition to the memory cell, the company offers high-voltage generator and interface cells. These cells provide the voltages and programming signals required to write data to the electrically erasable cells. Each memory cell is embedded in a digital flip-flop and latch so it can operate directly with other on-chip logic; you don't need to worry about the details of writing to and erasing from the electrically erasable cells.

The nonvolatile memory cells are useful as replacements for conventional adjustment components like potentiometers and DIP switches. For example, a nonvolatile register can store calibration settings, I/O format selections, or system access codes. In potentiometer applications, the memory cells can work with on-chip analog cells to form a linear adjustment circuit that's digitally controlled. In addition, by building a chip with nonvolatile memory, you can automate system-test, calibration, and maintenance operations.

To create your chip using the electrically erasable cells, you submit your system design and specifications to the manufacturer. It charges between \$5000 and \$25,000 for the design, depending on the complexity, and approximately \$30,000 for the tooling and fabrication of prototypes. The unit cost of production devices is \$0.0015/gate typ.—**David Smith**

Sierra Semiconductor Corp, 2075 N Capitol Ave, San Jose, CA 95132. Phone (408) 263-9300.

Circle No 727

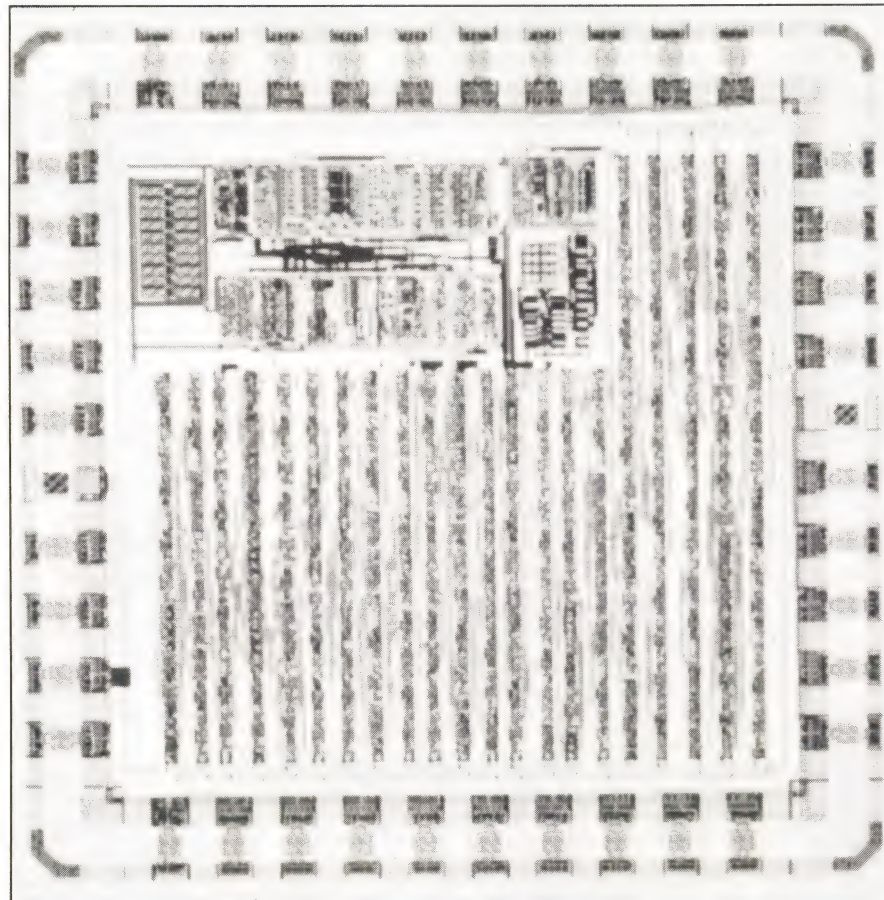


*The first electrically erasable standard memory cells implement nonvolatile storage in this IC design. The electrically erasable cells are compatible with the vendor's digital and analog standard cells.*


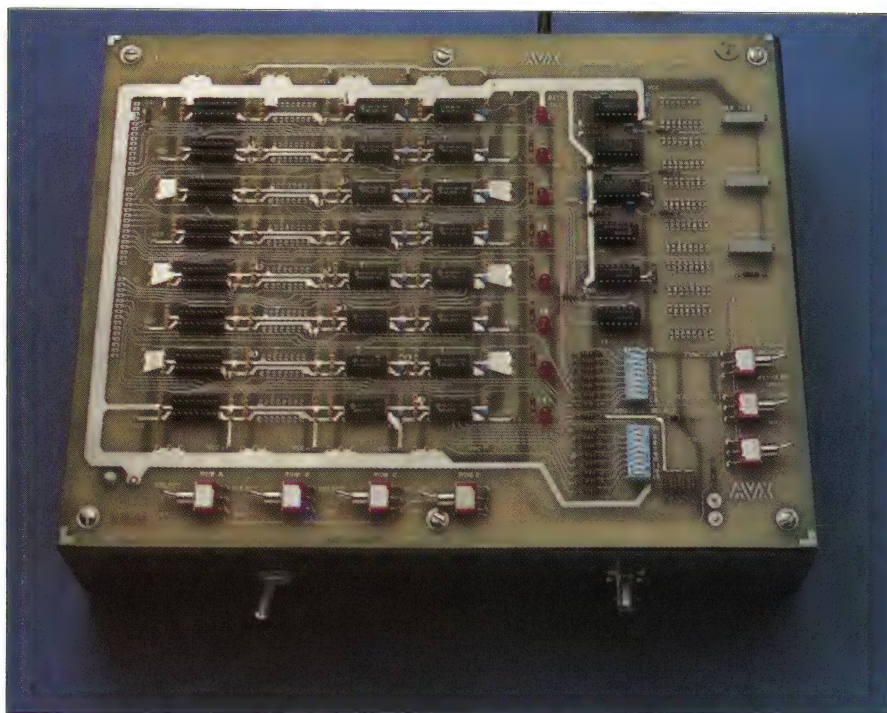
# Decoupling IV

**AVX**  
Techfile Series

TECHNICAL INFORMATION FROM THE LEADER IN MLCs



## MLC Decoupling of 256-K Dynamic RAMs

A dynamic RAM's sensitivity to decoupling-induced "soft-errors" (random loss of one or more bits of memory) increases dramatically with higher speeds, higher density, and an increased number of sense amplifiers. The new 256-K DRAM designs have large, instantaneous current demands which must be satisfied by a local current source.

That source is the decoupling capacitor directly adjacent to the RAM package. And the capacitor most often used for this application is a multilayer ceramic capacitor (MLC) because of its low series inductance, low series resistance, and high capacitance in a small size.

### Test Results

Tests were conducted by AVX on a 256-K DRAM memory board to determine the noise level obtained with various values of MLC capacitors. Figure 1 compares the results obtained using 256-K DRAMs with those from similar board tests on 64-K DRAMs. As indicated, 0.33- $\mu$ fd capacitors are required on the 256-K DRAM board to obtain a noise level equivalent to that obtained using 0.1- $\mu$ fd capacitors on the 64-K DRAM board. Performance improvements on the 256-K DRAM

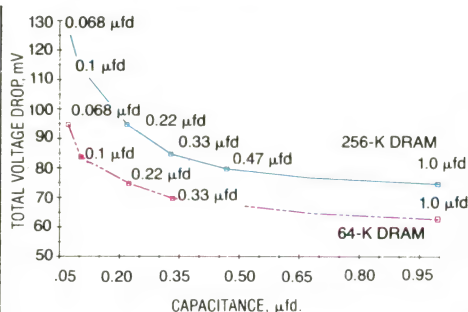


Fig. 1. Decoupling characteristics for 64-K and 256-K DRAMs with AVX MLC capacitors (including V-bump and V-droop).

test board leveled off between 0.33- $\mu$ fd and 1.0- $\mu$ fd, indicating that the preferred value for decoupling is about 0.33- $\mu$ fd.

Figure 2 shows the scope traces obtained during refresh cycle on the 256-K DRAM test board with a 0.33- $\mu$ fd AVX MLC. In all tests, the general decoupling scheme used was one MLC capacitor for each DRAM, with no board-level bulk capacitors.

### Discussion

General-application ceramic formulations, such as Z5U, show considerable change in capacitance with temperature. However, this change has

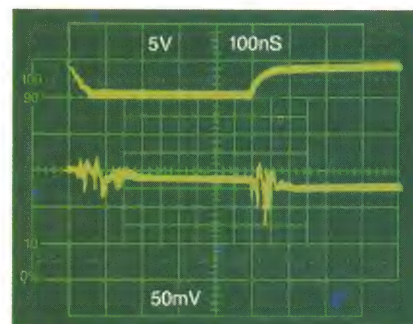


Fig. 2. Scope traces for refresh cycle on 256-K DRAM test board with 0.33- $\mu$ fd AVX MLCs.

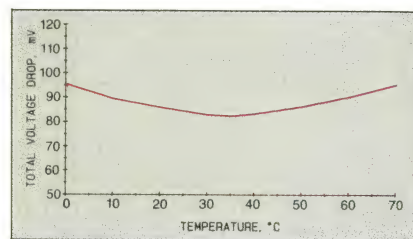


Fig. 3. Effect of temperature on 256-K DRAM decoupling with 0.33- $\mu$ fd AVX MLCs (Z5U).

little effect on the total noise level for 256-K DRAM when the correct value is chosen. Thus, the 0.33- $\mu$ fd value is high enough to meet the 256-K DRAM's current requirements over its full operating temperature range, as shown in Fig. 3.

For a complete technical paper describing these tests in detail, complete and return the coupon below.

- ☐ Please send me the AVX Technical Paper, "Decoupling 256-K DRAMs."
- ☐ Please send me literature describing AVX MLCs
- ☐ Please send me samples

EDN 41786

Name \_\_\_\_\_

Title \_\_\_\_\_

Company \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

Phone \_\_\_\_\_

Send to: AVX Corporation, Dept. 25,  
PO Box 867, Myrtle Beach, S.C. 29577

**AVX** Technology  
For The Times

AVX and AVX TechFile are trademarks of AVX Corporation.  
© 1984 AVX Corporation.



## Low-cost, PC-based LAN rivals Ethernet with 300k- to 450k-bps effective data rates

The Microlan 1553-Net local-area network provides twice the effective data bandwidth as a similar Ethernet configuration at approximately one-half the cost, according to the manufacturer. Microlan controller boards fit into the short slot in IBM PCs, PC/XTs, PC/ATs, and compatible systems and come with software that features pop-up windows and 100 levels of security. Microlan boards are also available for Apple II computers and systems employing the S-100 Bus.

Although the Microlan network has a lower specified bandwidth than an Ethernet network (3M bps vs 10M bps), the company states that the network's encoding techniques result in an effective data-transfer rate of 300k to 450k bps, a higher rate than Ethernet's estimated 100k-bps effective rate. One Microlan network can comprise as many as 253 nodes. The nodes connect to a 50 $\Omega$  coaxial cable by means of BNC connectors. The cable can

be as long as 1500 ft. A Microlan board requires at least 128k bytes of memory and draws 0.5W from the PC's power supply.

The board implements a LAN protocol that's a derivative of the MIL-STD-1553 military-aircraft communications protocol. A CRC algorithm checks data blocks; the board also performs parity checking and Manchester encoding. For arbitration of bus usage, the network uses carrier-sensed multiple access/collision detection/collision avoidance (CSMA/CD/CA) techniques. These techniques prevent two or more nodes from transmitting data at the same time.

The vendor's network software, PC-NOS, runs in the background to execute network programs, gain access to remote data, and prevent data destruction, which can be caused by simultaneous access of files. The software works under PC-DOS 2.0 or MS-DOS 2.0 to allow PCs on the network to share files

and such hardware resources as disks, printers, keyboards, displays, modems, clocks, and gateways to other networks. Once a connection to a remote resource is established, the resource sharing is transparent to the user. The software includes commands to attach and disconnect your PC to remote devices, and to lock files that are on your PC so that other PCs can read them but not write to them. All PC-NOS routines are available in Basic, Fortran, assembly, and Forth languages.


The main program in the software, Server, executes as a command (.COM) file. It initializes itself and then returns control to the operating system after it sets its break address, so that the operating system will not write over it. Server uses interrupt vector INT 13H to intercept and service calls for remote files.

When you log on to a Microlan network, the system asks for a password and then establishes access and security privileges. Access control is hierarchical, extending from nodes down to peripherals, directories, and files.

A Microlan card costs \$350. An XL version contains ROM to allow a diskless node to boot up from another node; this card costs \$450. A Lanstarter kit includes two Microlan cards, the PC-NOS software, manuals, and a 25-ft cable for \$1150. A network-expansion kit is identical to the Lanstarter kit except that it has one card and costs \$575.—**David Smith**

*Fast Feedback Technologies, 1505 Aviation Blvd, Redondo Beach, CA 90278. Phone (213) 379-6100.*

**Circle No 726**

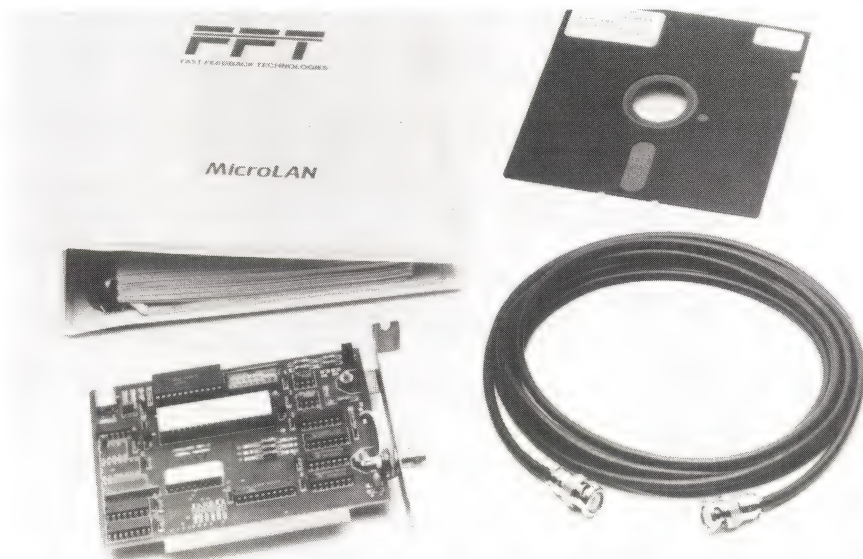


*Furnishing effective data rates of 300k to 450k bps, the Microlan local-area network costs less per node than other networks with similar configurations, according to the manufacturer. Plug-in boards are available for IBM PCs and compatibles and for Apple II and S-100-based computers.*


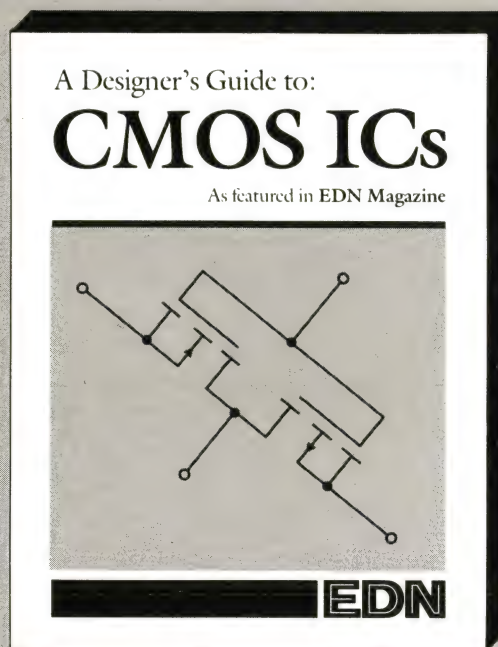
# SEE WHAT A *DIFFERENCE* CMOS MAKES!

CMOS is fast becoming the chosen technology for developing integrated circuits. That's because CMOS ICs are able to implement ultra-complex system-level functions on a chip!

Now you can meet the special challenges posed by this new breed of ICs with *A Designer's Guide to CMOS ICs*. You'll learn the advanced design and fabrication techniques required. Plus the latest linear and digital CMOS ICs available.



## Mail coupon to:

CMOS IC Reprints  
**EDN Magazine**  
Cahners Building  
275 Washington Street  
Newton, MA 02158-1630

Please send \_\_\_\_ copies of  
*A Designer's Guide to CMOS ICs*  
(92 pages)

- ☐ \$6.95 UPS  
☐ \$8.95 non USA

Check or money order made out to  
**EDN REPRINTS** must accompany  
each order. No COD. Mass.  
residents add 5% sales tax.

**Please print clearly.**

**This is your mailing label.**

NAME \_\_\_\_\_

TITLE \_\_\_\_\_

COMPANY \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_



**NEW!**

## Qualidyne announces



### The Case 23

A new switching power supply delivers 400 to 600W, up to 7 outputs with a power density of 2.81W/in<sup>3</sup>.

- 3" x 5" x 14.25" package
- 1 - 7 outputs
- 400 - 600W fan cooled
- UL and International Safety Standards
- Ball bearing, brushless DC fan
- EMI filtering to FCC 20780 Class A
- Variety of standard options
- Main channel pre-load standard
- Modular design
- 48V DC input up to 400W

For additional information on this or other Qualidyne products, please call or write:

#### QUALIDYNE SYSTEMS, INC.

3055 Del Sol Boulevard  
San Diego, California 92154  
619/575-1100  
TELEX: ESL227140



See pages D. 1803-1809 in EEM.

CIRCLE NO 23

## PRODUCT UPDATE

### Single unit combines voltmeter and high-speed, 8-bit digitizer

At first glance, the Model 194 looks like just another system voltmeter. But behind the instrument's front panel is a 1M-sample/sec, 8-bit digitizer and waveform-analysis software along with the expected 4½-digit voltmeter.

The instrument comes with built-in waveform-analysis routines for averaging, true-rms calculation, integration, and determining standard deviations and peak-to-peak readings. The 194 also identifies the positive peak, the negative peak, and the value of the sample at the trigger point. When an optional second channel is installed, the instrument becomes the Model 1944 system voltmeter, which computes the ratio and difference of parameters from each channel.

The instrument can store 64k 8-bit samples; because the 4½-digit voltmeter mode is equivalent to 16-bit digitization, you can store only 32k 16-bit samples in that mode. The maximum reading rate in the 4½-digit mode is 100k samples/sec.

In the 4½-digit mode, the instrument's dynamic range is 10 µV to 200V; in the high-speed, 8-bit mode,


the resolution is 2.56 mV. The meter can store either pretrigger or post-trigger data. The programmable sample period, ranging from 1.0 µsec to 1.0 sec, has a minimum increment of 0.1 µsec over the entire range.

The unit operates from any of five trigger sources. It provides an IEEE-488 interface for external control. In DMA mode, the unit transfers data at 90k bytes/sec over the IEEE-488 bus. Furthermore, internal software can expand a short mnemonic into an elaborate command string, thus lowering IEEE-488 bus overhead. The software can also translate command strings for other brands of voltmeters into strings comprehensible by the 194.

You can set the unit's input filter for a full bandwidth of 750 kHz, or you can use one of two lowpass filters—50 kHz or 500 kHz. \$3995; the 2-channel Model 1944 adds \$1895.—**Charles H Small**

Keithley Instruments Inc, 28775  
Aurora Rd, Cleveland, OH 44139.  
Phone (216) 248-0400. TLX 985469.

Circle No 731

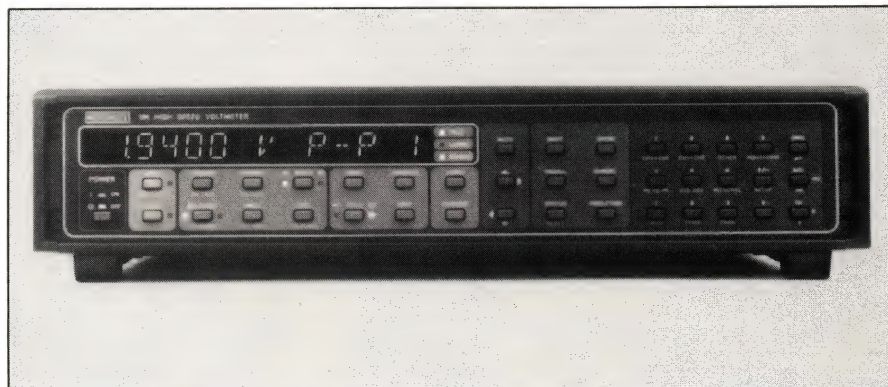

Combining a high-speed digitizer with a system voltmeter, the Model 194 spans the sampling-speed gap between voltmeters and digitizers. The 194 covers the 100k- to 1M-sample/sec range.



# Hyspeed from Hybrid



*Hybrid Systems' new CMOS Flash Converters and High Speed Hybrids provide an unbeatable combination of speed and uncompromising quality.*

**N**ow, Hybrid Systems brings its 20-year reputation for high quality, high reliability, and high performance to a new line of high speed products. Our monolithic flash converters and high speed hybrids are designed to meet the needs for fast digitizing and low power consumption in the most demanding real time data acquisition and analysis applications.

#### **ANALOG TO DIGITAL**

	RESOLUTION	CONVERSION TIME	POWER
HS9582*	6-bits	40 nsec	150mW
HS9583*	8-bits	200 nsec	75mW
HS9584*	8-bits	50 nsec	300mW
HS9520	12-bits	2.0 $\mu$ sec	1.2W

#### **DIGITAL TO ANALOG**


	RESOLUTION	SETTLING TIME	POWER
HS9393	12-bits	50 nsec	495mW

#### **SAMPLE AND HOLD**

	RESOLUTION	ACQUISITION TIME	POWER
HS9720	12-bits	200 nsec	765mW

\*Flash Converters

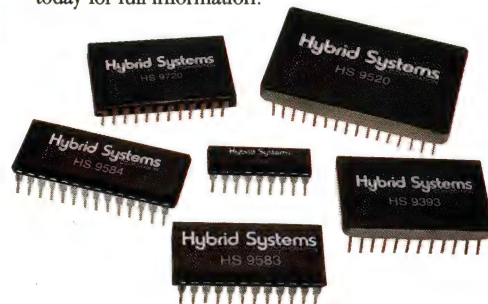All high speed components meet commercial and military temperature ranges. All products for military applications are processed to MIL-STD-883. Better still, all carry a name that is synonymous with expertise, reliability, and unsurpassed customer service: Hybrid Systems Corporation. Contact us today for full information.




# Hybrid Systems

CORPORATION

22 Linnell Circle, Billerica, MA 01821 617-667-8700


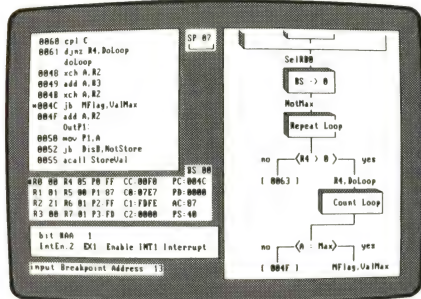
# IBM-PC based microcomputer development tools!



(8051 debug/simulator shown)

Your IBM PC can Assemble, debug and program (EPROM) code for these popular microcomputers:

**8096**

**8051**

**8049**

**7000**

**8088**

**8085**

**320**

**28**

Step your code, watch registers & memory change, interrupts occur, stack push & pop. Flowgraph auto-documents code! You set breakpoints & register traps, count machine cycles, and scan source code and symbols. Single-key commands prompt for arguments if needed. Have more fun and get more done!

DBG	XASM	PROG
✓	✓	✓
✓	✓	✓
✓	✓	✓
✓	✓	✓
✓		✓
	✓	✓
	✓	✓
\$595 except 8096 and 8088	\$295	\$245 Kit form

debug demo diskette and manual only \$39.50




**Cybernetic Micro Systems**  
P.O. Box 3000  
San Gregorio, CA 94074 U.S.A.

(415) 726-3000 • Telex 171135 Attn: Cyber

**CIRCLE NO 190**

## PRODUCT UPDATE
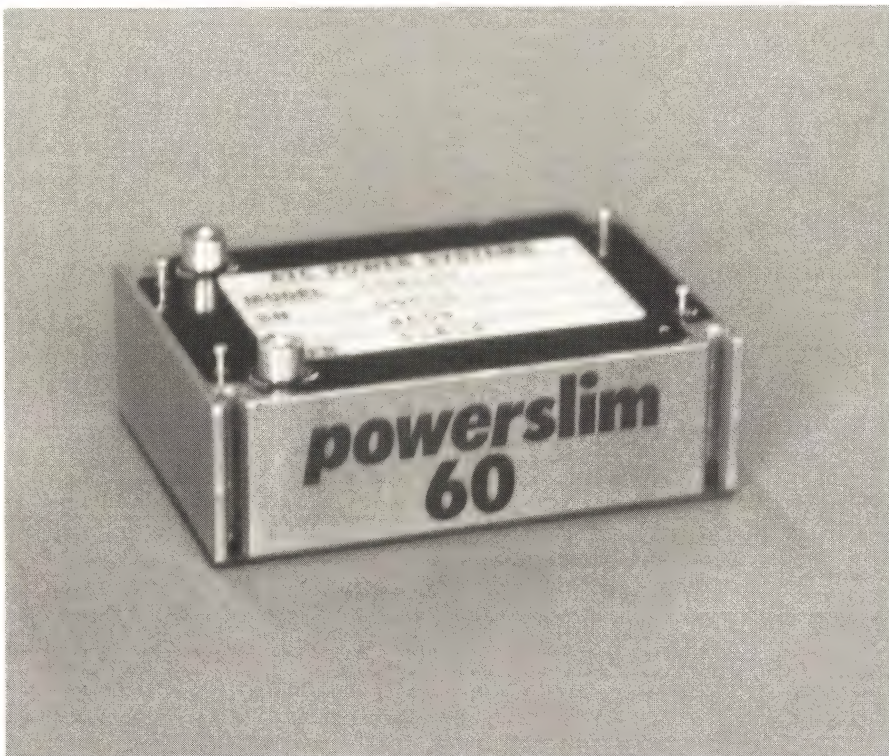
### 60W switching power supply offers 5 or 15V at 10W/in.<sup>3</sup>



*Because it uses a 250-kHz switching frequency, the Powerslim 60 delivers 5V±1% at 12A or 15V±1% at 4A from a 2×3×1-in. package.*

The Powerslim 60 operates at a 250-kHz switching frequency, which allows the 2×3×1-in. module to deliver 60W—yielding a 10W/in.<sup>3</sup> power density. The single-channel supply accepts a 28V dc nominal input (18 to 40V dc). You can select from two output ratings: 5V±1% at 12A or 15V±1% at 4A.

Line and load regulation spec 0.1 and 0.5%, respectively. The temperature coefficient is 0.03%/°C. Ripple measures 1% p-p from dc to 100 MHz.

The Powerslim 60 settles within 0.5 msec in response to a 50 to 100% load change. Overshoot and undershoot are limited to 100 mV. The supply, which features output short-circuit protection, meets MIL-461 emissions standards and

withstands input transients in accordance with MIL 704. \$850.

(For more on high-frequency switching power supplies, see pg 130.)

ATC Power Systems Inc, 472 Amherst St, Nashua, NH 03063. Phone (603) 882-1366.

**Circle No 728**



**FEW REMEMBER WHO WAS SECOND TO SOLO THE ATLANTIC...**



**OR SECOND  
IN THE MARKET...**



# AT&T DOESN'T IMMORTALITY... WAY TO MAKE

Today, the product that's first in the market is likely to win the biggest share of market.


So when you're racing to get a great idea off the ground—ahead of your competitors—you need more than just a "supplier."

You need a company with a broad line of high-performance components and electronic systems. A company with a networking point-of-view, an end-to-end capability, and the people and resources to assure all-out technical support.

AT&T.

Ready now to offer you the total commitment to quality and reliability that we've always insisted on in the systems and products we develop for ourselves.

Ready now to deliver solutions.

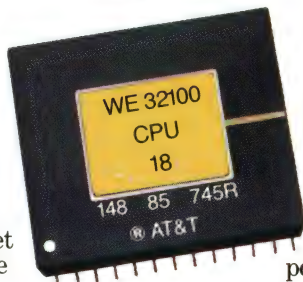

**WE32100,  
heart of the first  
full 32-bit chip set.**

## **We'll keep you on the leading edge.**


Because that's where AT&T Bell Laboratories keeps us.

Our new 32-Bit UNIX™ Microsystem, for example, delivers performance others only promise. It's a chip set that's 100% complete, 100% CMOS, and 100% TTL-compatible—fully able to reduce your design time by as much as 50 percent.

In data communications devices, we're state-of-the-art every step of the way. (As you might expect from the company that developed the world's biggest, most reliable communications network.)

Right now, for example, AT&T is the only company in volume production of a microprocessor-controllable, single-package modem that can handle up to 2400 bits per second.

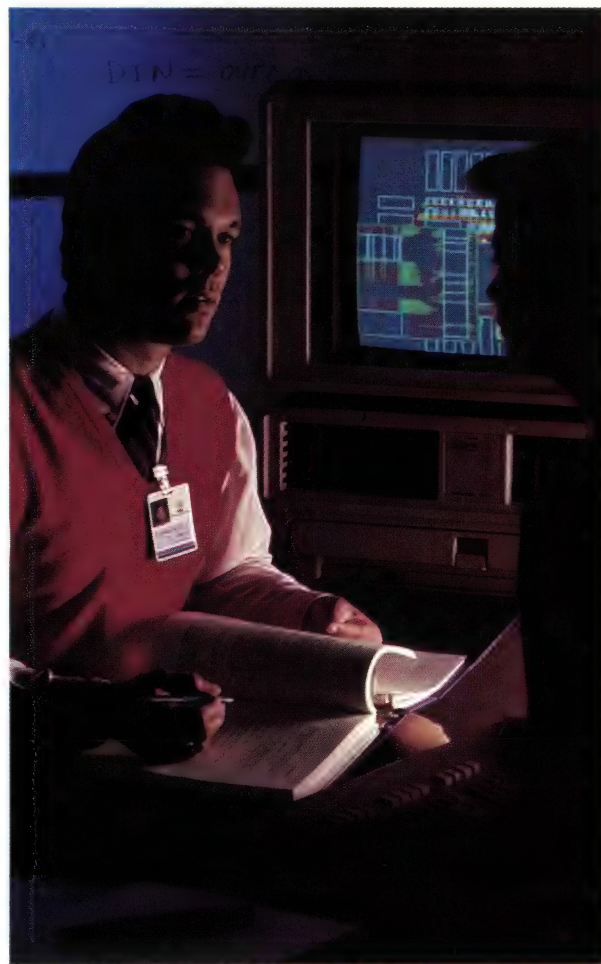Our Digital Encryption Processor is the only software-programmable,



**When off-the-shelf won't do, our advanced custom design gives you the edge.**

encryption processor available.

And our X.25 Protocol Controllers offer the widest range of applications, from PCs to satellites.

In memory, not only are we currently delivering an American-made 256K DRAM, but we offer a range of



*Few remember James Mollison, the second man to fly solo across the Atlantic, because 'Lindy' did it first.*



# PROMISE YOU JUST THE FASTEST AN IDEA FLY.

leading-edge specialty memories.

And our third-generation, single-chip Digital Signal Processor gives you the edge you need to design-in superior system performance at a competitive price.

and engineering personnel. And with powerful CAD software that helps make sure your devices work the first time. The commitment and resources to deliver solutions—that's what makes AT&T, AT&T.

## It all takes power.

AT&T's board-mounted power products cut design time with unmatched flexibility. Our low profile power converters are modular in design and about one quarter the size of conventional DC/DC circuit board converters. So they can be mounted in more places. And in the tightest situations.

Whatever your power needs, from

board-mounted to off-line switchers, we can work with you to develop a system to meet your needs.


## Networking products that lock-in the future.

For local or long-haul transmission, AT&T offers a complete family of fiber optic products and apparatus.

In local area networks, our new ST™ Connector can actually double your network connections—or double the distance between connections—without affecting the fiber optic cable or electronics.

And for high performance data transfer, AT&T's ODL® 50 and ODL® 200 Lightwave Data Links, with bit rates up to 200 Mb/s, incorporate the latest optical and integrated circuit technology. These products, as well as our ODL RS232-I Fiber Optic Modem, a high performance data interface, readily mate with the ST Connector.

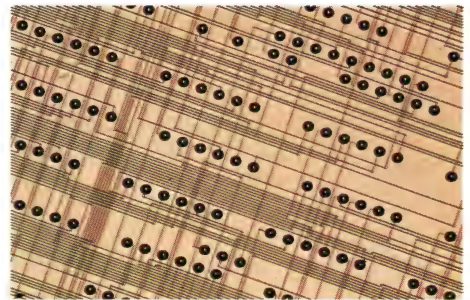Our newest addition to the AT&T lightwave family—the ASTROTEC™ ceramic laser module—is a reduced-size, long-wavelength laser that offers highly reliable, low cost performance.



Advanced processing technology provides superior buried microvias in multilayer printed wiring boards.

## News in ac plasma.

AT&T has just introduced a new light-weight, compact ac plasma display for alphanumeric and graphic images. It offers excellent visual characteristics in virtually unlimited applications.


## We'll work with you, all the way.

Call us right from Day One, and we'll put our expertise at your disposal. Call us when you hit a snag, and we'll work out a solution together. After all, we've got the world's greatest problem-solvers on call—the men and women of AT&T Bell Laboratories.

For more information, phone AT&T at 1 800 372-2447. We'll help you put wings on your concept, and "first" on your product.

(In Europe, phone AT&T Microelectronics in Munich, Germany, at 089/95970. Telex 5216884 attm d.)


© 1986 AT&T Technologies, Inc.

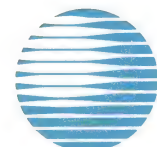

**AT&T**

The right choice.

CIRCLE NO 191

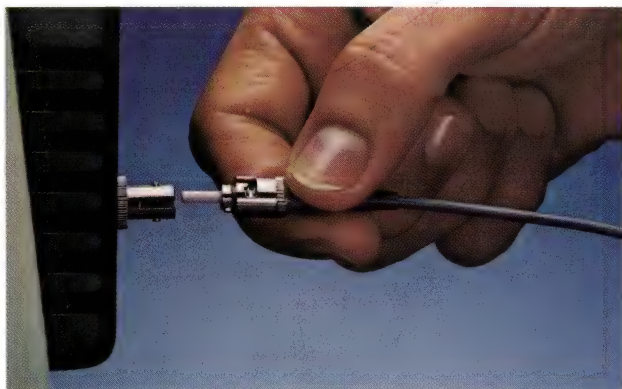

New ST™ Connector doubles your connections.

Count on AT&T's advanced technology to help you move your product out the door on schedule.

## Advanced custom design capability.

Nobody knows better than you—moving to market first, and staying there, can require custom designed components.

At AT&T, we'll get involved at any stage of your product design—from layout to prototype to production. We'll support you with the industry's most advanced CAD/CAM software, rapid prototype turnaround, and unsurpassed volume manufacturing capability. Everything you need to ensure the success of your product—on your manufacturing line and in the market.

Your specialized interconnection needs will be taken care of—from flexible printed wiring to multilayer boards to hybrid ICs—all produced with our high standards of quality and reliability.

We'll meet your application-specific IC needs with expert design



# Fluorinert<sup>®</sup> Liquids prevent rejects from boxing in profits.





Product failure can come from a lot of different sources. Unreliable solder joints. Ineffective defect testing. Inefficient component cooling. All together, that can add up to a lot of rejects. And a lot of lost profits. Fluorinert® Liquids reduce the risk of product failure. And increase your chances for profits and productivity.

**Vapor phase soldering** with Fluorinert® Liquids provides a faster, more reliable soldering method for electronic components and assemblies. This results in a higher yield and reduced costs.

**Direct contact cooling** with Fluorinert® Liquids removes heat rapidly so component temperatures are kept lower, reducing failure rates and increasing reliability. At the same time, components can be packaged closer together, maximizing power density and miniaturizing the package.

**Gross leak, thermal shock, and liquid burn-in testing** with Fluorinert® Liquids detect more defects before they have a chance to become rejects.

Fluorinert® Liquids don't make problems while they're solving problems, either. They leave essentially no residue, so no clean-up is necessary. They're colorless, odorless, non-flammable, non-explosive, non-corrosive, and will not remove markings.

**FC** numbers (FC-72, FC-77, FC-70, FC-40, etc.) identify individual Fluorinert® Liquids. They offer a wide range of boiling points, making it easy to select the liquid that's right for your application. FC numbers are solely 3M designations for our fluorochemical products.

And in addition to making Fluorinert® Liquids easy to choose, we make them easy to use. We

offer comprehensive technical assistance, including recommendations for fluids and application equipment; testing and production methods; evaluation of results; an extensive service bulletin program covering technological advances; and on-site applications seminars.

3M developed perfluorinated liquids 35 years ago, and we've been supplying them to the electronics industry for the past 25 years. So you can trust us, the industry leader, to help you select and use the right Fluorinert® Liquid for peak performance. And peak profitability.

For more information, write: Commercial Chemicals Division/ 3M, Building 223-6SE, St. Paul, MN 55144. Or call our hotlines: 612/733-6282 (testing/cooling) 612/733-7424 (soldering).

CIRCLE NO 192





# LEADTIME INDEX

Percentage of respondents

ITEM	Off the shelf	1-5 weeks	6-10 weeks	11-20 weeks	21-30 weeks	Over 30 weeks	Last month's average (weeks)	Average (weeks)
<b>TRANSFORMERS</b>								
Toroidal	0	18	27	55	0	0	11.3	7.8
Pot-Core	0	22	45	33	0	0	9.3	9.1
Laminate (power)	0	21	57	22	0	0	8.4	7.3
<b>CONNECTORS</b>								
Military panel	14	0	72	14	0	0	8.0	10.9
Flat/Cable	15	54	31	0	0	0	3.5	5.0
Multipin circular	11	22	45	22	0	0	7.6	10.6
PC	13	40	47	0	0	0	4.5	7.3
RF/Coaxial	0	40	60	0	0	0	5.6	8.0
Socket	25	44	31	0	0	0	3.4	4.5
Terminal blocks	14	52	33	0	0	0	3.7	4.7
Edge card	11	44	45	0	0	0	4.4	4.4
Subminiature	8	75	17	0	0	0	2.8	3.7
Rack & panel	0	40	60	0	0	0	5.6	6.7
Power	0	33	56	11	0	0	6.9	5.6
<b>PRINTED CIRCUIT BOARDS</b>								
Single-sided	0	65	35	0	0	0	4.1	4.0
Double-sided	0	50	50	0	0	0	5.0	4.3
Multilayer	0	10	60	30	0	0	9.8	6.2
Prototype	0	100	0	0	0	0	2.0	2.8
<b>RESISTORS</b>								
Carbon film	44	24	32	0	0	0	3.0	2.6
Carbon composition	26	26	37	11	0	0	5.2	3.5
Metal film	39	30	31	0	0	0	3.0	2.6
Metal oxide	33	27	40	0	0	0	3.7	3.6
Wirewound	14	36	50	0	0	0	4.7	4.9
Potentiometers	8	42	46	4	0	0	5.2	5.4
Networks	40	20	20	20	0	0	5.2	3.5
<b>FUSES</b>								
	35	45	20	0	0	0	2.5	1.6
<b>SWITCHES</b>								
Pushbutton	29	24	41	6	0	0	4.7	3.5
Rotary	7	22	57	14	0	0	7.3	5.2
Rocker	15	39	23	23	0	0	6.3	4.0
Thumbwheel	0	18	46	36	0	0	9.8	5.4
Snap action	22	45	11	22	0	0	5.3	4.5
Momentary	27	37	9	27	0	0	5.8	3.3
Dual in-line	20	40	20	20	0	0	5.6	5.1
<b>WIRE AND CABLE</b>								
Coaxial	44	28	22	6	0	0	3.2	1.7
Flat ribbon	53	37	10	0	0	0	1.6	1.4
Multiconductor	26	58	16	0	0	0	2.4	2.6
Hookup	42	50	8	0	0	0	1.7	1.1
Wire wrap	42	33	25	0	0	0	2.7	1.7
Power cords	27	53	13	7	0	0	3.2	2.5
Other	40	40	20	0	0	0	2.4	6.0
<b>POWER SUPPLIES</b>								
Switching	0	40	33	20	7	0	8.4	7.0
Linear	0	27	55	9	9	0	8.7	6.9
<b>CIRCUIT BREAKERS</b>								
	0	27	55	18	0	0	7.8	7.7
<b>HEAT SINKS</b>								
	19	25	44	12	0	0	6.0	4.2

ITEM	Off the shelf	1-5 weeks	6-10 weeks	11-20 weeks	21-30 weeks	Over 30 weeks	Last month's average (weeks)	Average (weeks)
<b>RELAYS</b>								
General purpose	25	30	35	10	0	0	5.0	3.4
PC board	7	33	33	27	0	0	7.6	4.4
Dry reed	0	33	67	0	0	0	6.0	6.3
Mercury	0	33	50	0	17	0	9.0	7.0
Solid state	8	34	25	25	8	0	8.8	6.8
<b>DISCRETE SEMICONDUCTORS</b>								
Diode	17	26	52	5	0	0	5.5	4.6
Zener	24	32	36	8	0	0	4.8	4.6
Thyristor	11	39	33	17	0	0	6.1	5.0
Small signal transistor	18	32	36	14	0	0	5.7	5.6
FET, MOS	0	0	55	36	9	0	12.6	8.4
Power, bipolar	14	29	29	21	7	0	8.1	7.2
<b>INTEGRATED CIRCUITS, DIGITAL</b>								
CMOS	19	24	33	19	5	0	7.4	6.7
TTL	18	24	23	29	6	0	9.0	7.2
LS	13	33	20	27	7	0	8.3	7.8
<b>INTEGRATED CIRCUITS, LINEAR</b>								
Communication/Circuit	9	9	55	18	9	0	9.8	6.2
OP amplifier	13	25	37	19	6	0	8.1	7.9
Voltage regulator	24	23	29	18	6	0	7.2	6.9
<b>MEMORY CIRCUITS</b>								
RAM 16k	17	33	8	42	0	0	8.0	4.0
RAM 64k	17	42	16	25	0	0	6.2	3.0
RAM 256k	13	38	12	37	0	0	7.8	3.3
ROM/PROM	23	33	11	22	11	0	8.0	4.0
EPROM	17	50	8	17	8	0	6.5	5.2
EEPROM	14	43	0	29	14	0	9.1	6.2
<b>DISPLAYS</b>								
Panel meters	10	40	40	10	0	0	5.6	6.0
Fluorescent	0	25	75	0	0	0	6.5	8.0
Incandescent	0	40	60	0	0	0	5.6	5.7
LED	15	30	40	15	0	0	6.2	5.2
Liquid crystal	0	17	67	16	0	0	8.3	9.3
<b>MICROPROCESSOR ICs</b>								
8-bit	6	44	31	19	0	0	6.4	5.5
16-bit	0	12	38	50	0	0	11.3	7.2
<b>FUNCTION PACKAGES</b>								
Amplifier	18	18	55	9	0	0	6.2	6.3
Converter, analog to digital	0	40	40	20	0	0	7.2	9.1
Converter, digital to analog	0	30	40	30	0	0	8.6	8.5
<b>LINE FILTERS</b>								
	10	10	70	10	0	0	7.4	7.5
<b>CAPACITORS</b>								
Ceramic	28	36	32	4	0	0	3.9	4.2
Ceramic monolithic	17	44	33	6	0	0	4.4	3.7
Ceramic disc	18	47	29	6	0	0	4.2	5.1
Film	17	28	39	16	0	0	6.3	4.9
Electrolytic	23	27	32	18	0	0	6.0	4.6
Tantalum	9	35	43	13	0	0	6.2	6.9
<b>INDUCTORS</b>								
	9	46	36	9	0	0	5.3	5.0

Source: Electronics Purchasing magazine's electronics business survey



# In the final analysis you'll choose Philips!



## Philips' PM 3551 A and PM 3632 Logic Analyzers

Choose the PM3551 A, the world's fastest transitional timing analyzer. With simultaneous state and timing analysis. Plus powerful performance analysis with unique features. Measure recursive routines, and obtain undistorted data even if subroutines are interrupted. Up to 16 on-screen timing channels. Unmatched trigger facilities. Pure power!

Pure power, too, with the PM3632 Personal Logic Analyzer. And at a price that lets you put one on every bench. Handles 32

channels at speeds up to 100 MHz. Adapts to any popular  $\mu$ P. Optional ROM emulator and plug-in Set-up and non-volatile Data Memory.

Both feature a simple, powerful menu system with soft-key entry that puts you in charge from the first day. The choice is yours! Get the details on the PM 3551 A logic timing, state and performance analyzer and the PM3632 Personal Logic Analyzer. In the final analysis you'll choose Philips. Contact your local Philips Sales organisation or:

Philips I&E, T&M Department,  
TQ III-4-62  
5600 MDEINDHOVEN, The Netherlands.  
Germany (0561) 501518  
Great Britain 0223-358866  
France 01-8301111  
Netherlands 040-783238  
Italy 039/3635.240 (or 248)  
Sweden 08-7821810.

PM3632 not available in Australia, Canada, Hong Kong, Japan, Singapore and Taiwan.



**Test &  
Measurement**

# PHILIPS



# POWER SUPPLIES



## MULTI-OUTPUTS FOR THE WORLD MARKET

KEC offers a full-line of multi-output switching power supplies designed expressly for use in OEM equipment that is targeted for sale in the world marketplace.

This new KFD World Class Series of power supplies includes 23 standard models in 7 different wattages: 25W, 40W, 60W, 80W, 100W, 130W, and 200W—plus customer specials. All are designed to meet VDE, IEC, UL, and CSA safety requirements; and EMI emissions are in compliance with VDE/FCC specifications. The KFD Series is the reliable, cost effective solution to your power supply needs.

For full specifications, send for the KEC KFD Series product brochure.



## NEW 100 kHz SINGLE- OUTPUTS FOR HIGHEST OUTPUT/CU.IN.

The KRV Series of single-output switching power supplies operate at 100kHz switching speed instead of the usual 20kHz, resulting in very small, space-efficient packages that provide more wattage per cubic inch.

This new KRV high-frequency series includes standard models in 5VDC, 12VDC, 15VDC, and 24VDC in 5 different wattages: 30W, 60W, 100W, 160W, and 300W—plus customer specials. All are designed to conform to UL safety requirements and to FCC class B on EMI; and they are dual source selectable—85-132V or 170-264V.

For full specifications, send for the KEC KRV Data Sheet.

**20817 Western Ave., Torrance, CA 90501 (213) 320-3902**



# WRING THE POWER FROM YOUR LOW OFFSET OP AMP ...

without reducing performance.

Teledyne's new TSC900 operational amplifier uses just 200  $\mu$ A maximum supply current—15 times less power than demanded by the pin-compatible TSC7650. But the TSC900 retains all of the low offset and drift performance of the industry-standard TSC7650 CMOS op amp. Both amplifiers feature an offset of only 5 $\mu$ V and  $V_{os}$  drift of less than 0.05 $\mu$ V/ $^{\circ}$ C, eliminating the need for adjustment potentiometers and costly trim procedures. Special chopper-stabilized error correction circuitry keeps offset voltage errors near zero throughout the entire operating temperature range.

Other advanced features for both amplifiers include a high open-loop voltage gain of 120dB minimum, and a low input bias current of 50pA. The TSC7650 has a 2.5 V/ $\mu$ sec slew rate. The TSC900 achieves a 0.2V/ $\mu$ sec slew rate despite its minimal power consumption. It's ideal for thermocouple and strain gauge applications—and the perfect choice as a preamplifier in low-power analog-to-digital converter systems.

The TSC7650—A precision chopper-stabilized op amp. The TSC900—The ultra-low-power alternative for precision op amp applications.

For more information on the TSC900 or TSC7650 call (415) 988-9241 or use the convenient coupon below.

 **TELEDYNE SEMICONDUCTOR**

1300 Terra Bella Avenue • P.O. Box 7267 • Mountain View, CA 94039-7267 • (415) 988-9241

☐ Please send me more information on the TSC900. ☐ Please send me more information on the TSC7650.

☐ Please have a Teledyne salesperson call me. Name \_\_\_\_\_ Title \_\_\_\_\_  
Company \_\_\_\_\_ Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_ Tel: (\_\_\_\_) \_\_\_\_\_ - \_\_\_\_\_

CIRCLE NO 193

386EDN900



# MORE BANG. LESS BUCK.

Why weapons systems designers are using Rantec standard military power supplies.

Rantec's standard military power supplies save weapons systems programs money. No costly non-recurring engineering expenses. No costly retooling. And, with over 600 different models to choose from, no costly design compromises on your part.

Also, no costly time delays waiting for product to develop or for manufacture. Which is very important when you consider it takes from 13 to 18 months and between \$125,000 and \$300,000 to get a custom military power supply.\*

Giving up reliability by going standard? No way. First of all, our quality program complies with MIL-I-

45208 and meets the intent of MIL-Q-9858. Secondly, all of our power supplies meet or exceed MIL-E-5400, MIL-E-16400, MIL-STD-704, MIL-STD-1399, MIL-I-6181, and MIL-STD-461.

This extensive product line includes single and three phase AC input power supplies and DC-DC converters in single and multiple output power ratings to 1KW.



To find out how you can save money like your contemporaries by using Rantec standard power supplies which are qualified for airborne, shipboard, ground-fixed and ground-mobile use, contact us today.

CIRCLE NO 194



Division of Emerson Electric Co.  
9401 Oso Avenue, Chatsworth, CA 91311 • Tel: (213) 885-8223 TWX: 910-493-1247

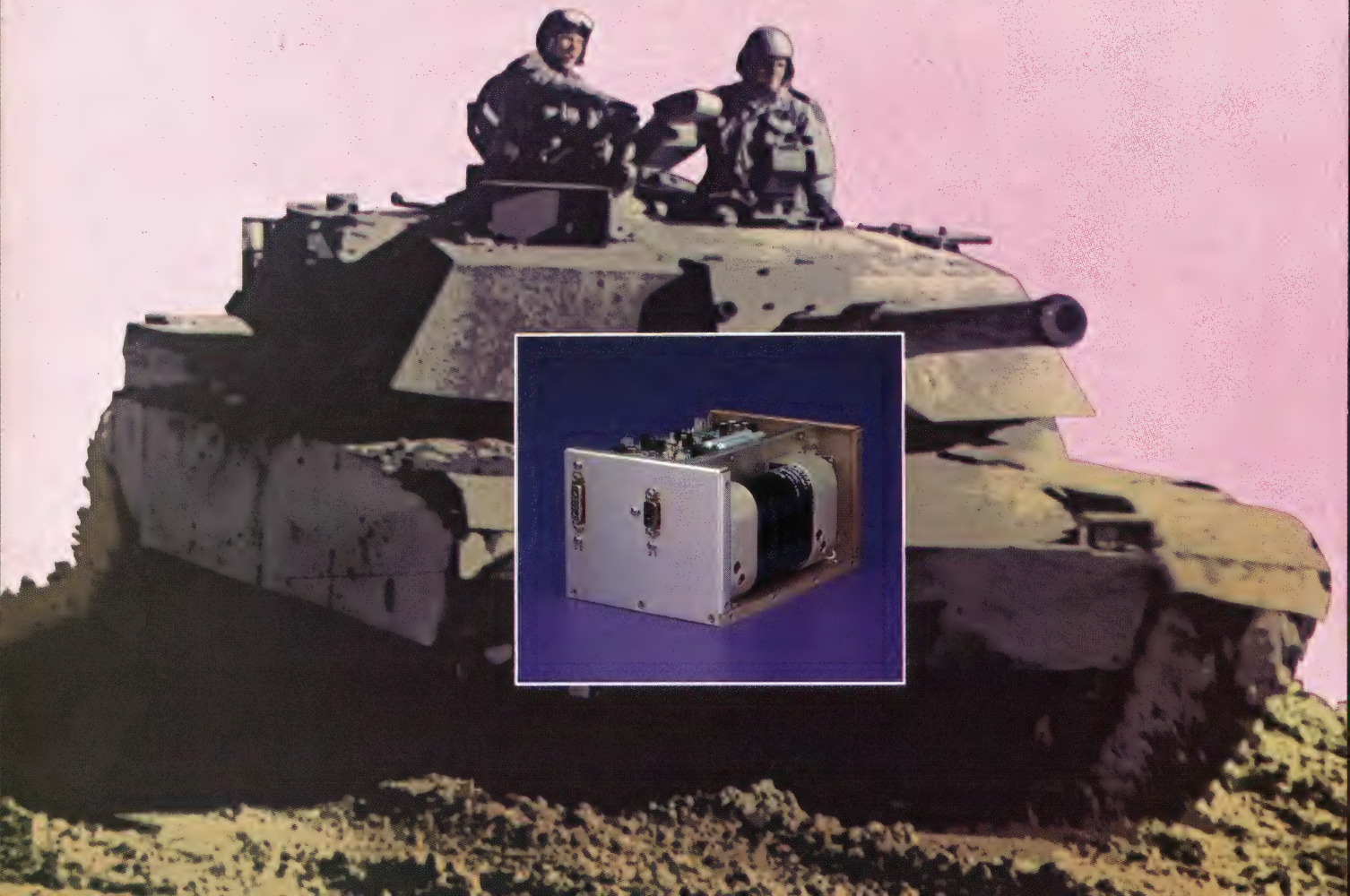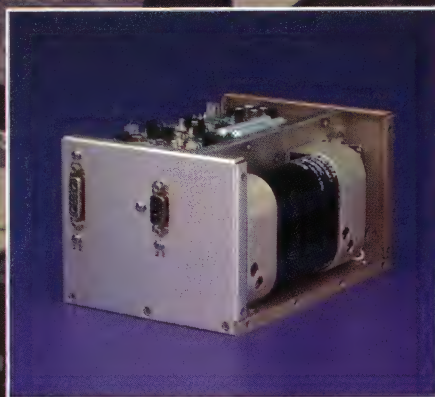\*U.S. Navy/Industry Power Supply Ad Hoc Committee Estimates for Time and Cost.






**You  
design  
the product.**


**Let Advance  
supply the  
power.**



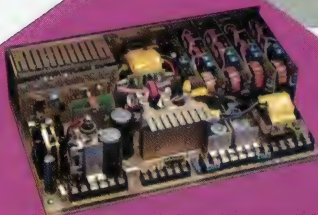**5/300 High Power** — 5" x 8" x 11" ■ 5V/300A/1500 watts ■ Built-in load sharing and paralleling circuit.



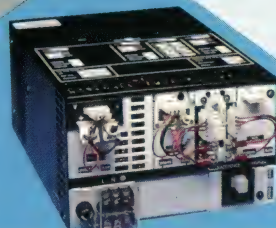**Powerflex** — Up to 5 outputs ■ 500 watts continuous / 750 watts surge ■ Inputs of 115/230 VAC or 48 VDC




**Hiflex** — 5" x 8" x 11" ■ Up to 6 independent outputs ■ To 1000 watts



**MG** — Demonstrated MTBF in excess of 125,000 hours  
■ Single outputs from 5V-60V/100 watts to 500 watts  
■ High-density convection cooled packaging



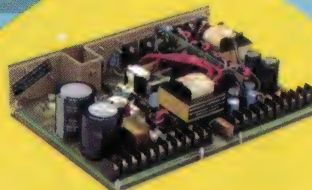**Multi High Power** — 5" x 8" x 11" ■ Mix and match up to 5 outputs ■ To 1000 watts



**Open Frames** — 100 KHZ high-efficiency switching  
■ Cost effective ■ Multiple outputs

The electronic systems  
you design are complicated  
enough without designing your own DC  
switching power supply — a system in itself. So  
go ahead. Do what you do best. And let Advance supply  
the power.

When designing around any one of the single- or multiple-output, open or closed Advance switching power supplies, you won't have to worry about compromising the overall quality of your product. These reliable switchers deliver from 180 to 1500 watts of full power in any voltage combination you may require.

Built to the highest standards, these units meet UL, CSA, VDE, IEC, and FCC requirements. With MTBF ratings that generally exceed others in their class.

When you need precise, dependable power for a well-designed instrument, computer or control, call 1-216-349-0755 for more information.



Advance Power Supplies  
32111 Aurora Road  
Solon, OH 44139

 **ADVANCE  
POWER SUPPLIES**

CIRCLE NO 196


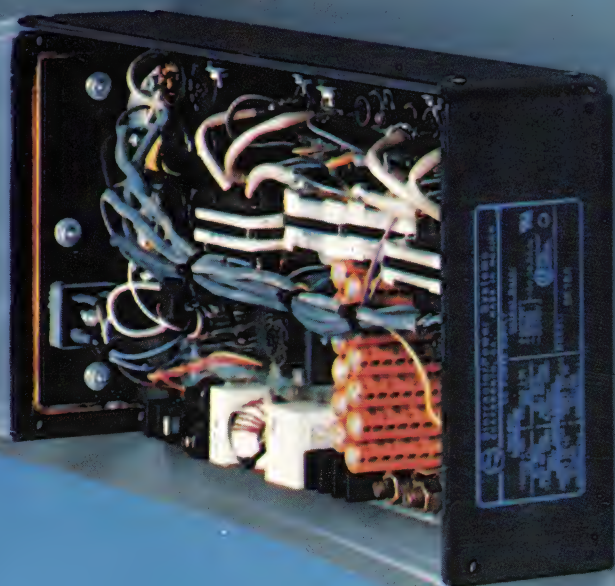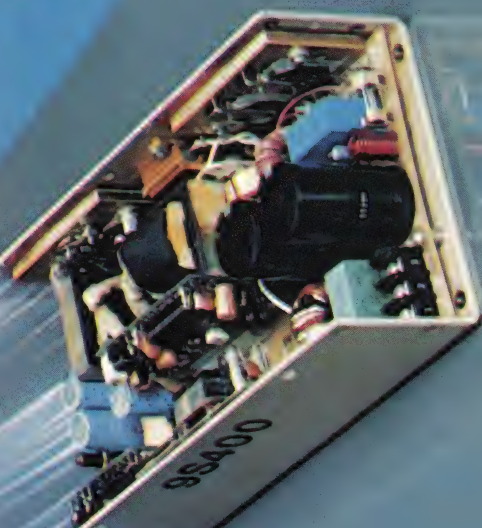
# High-frequency off-line switching power supplies





---

*Today's faster switching circuitry allows manufacturers to build smaller off-line switching power supplies. The smaller the supply, however, the greater its potential for internal heating and safety problems. Manufacturers avoid these potential problems by employing innovative thermal designs and packaging methods.*

---

Chris Everett, *Western Editor*

This year, you'll be able to put smaller power supplies into your designs without sacrificing power. As quickly as component manufacturers introduce faster switching transistors, diodes, and other components, power-supply manufacturers are incorporating them into off-line power supplies. Because these newer supplies operate at higher switching frequencies—50 kHz and higher—manufacturers can use smaller capacitive and inductive components, thereby reducing the supplies' package sizes and increasing their power densities. In the last year, off-line switchers' power densities have increased from less than 1W/in<sup>3</sup> to more than 4W/in<sup>3</sup>.

To solve the heat-dissipation problems that accompany this reduction in package size, companies are using new materials, components, and component-packaging techniques. In its MDT-400 Series, for instance, Todd Products uses both a higher switching frequency and surface-mount components to produce smaller power supplies than its earlier products. The 400W units come in a 144-in<sup>3</sup> package.

The MDT-400 Series includes models having a 50 to 60A, 5V primary output with  $\pm 1\%$  line and load regulation. You can choose a 12V or 24V secondary output to power disk drives or tape drives. You can also select 5V, 12V, or 24V floating auxiliary outputs.

The MDT-400 supplies, which typically operate with 75% efficiency, use bipolar transistors that switch at 60 kHz. Although they don't switch as fast as MOSFETs do, bipolar transistors are 50 to 80% less expensive than are MOSFETs with comparable ratings, and bipolars can handle higher power requirements.

Summit Electronics also employs bipolar switching transistors in its supplies. The firm's 750W switcher,

which operates at 50 kHz, has five outputs and a power density of 3.2W/in<sup>3</sup>. The company's GX500, also a 5-output supply, is a 500W switcher in a 1-piece extended chassis. At 10×5×2.75 in., the supply is smaller than many 200W power supplies. Its primary 5V output is rated at 75A.

You can select either  $\pm 12$  or  $\pm 15$ V each for the high-power auxiliary outputs. The low-power auxiliary outputs are set at the factory at +24 and -5V, but you can adjust them to any value between 2 and 48V. The GX500 includes an EMI filter, an ac fan output, an ac power-fail indicator, and a remote sense for the primary 5V output. The company expects qualification testing for UL, CSA, and VDE safety requirements to be complete this spring.

Some manufacturers are building smaller supplies by using MOSFET switching transistors, which can switch at higher frequencies than can bipolars. At present, some MOSFETs can operate to 1 GHz. These high frequencies let you use smaller filters to limit the EMI emitted from the input of the power supply.

Further, when a supply's operating frequency doubles, the volume necessary for its capacitive and inductive energy-storage elements is cut in half. CEI Corp, for example, reduced the size of the magnetics in its 100-kHz switching power supplies by 50%. CEI's 150W Model XL150 quad-output switcher has a power density of over 2W/in<sup>3</sup>. The single-output model in the 250W XL250 Series has a power-density rating of 3.2W/in<sup>3</sup> and comes in an 8.5×4.6×2-in. package.

The company's quad switchers are available with full regulation on each of the four outputs. The 5V primary output holds load regulation to within  $\pm 1\%$ . Cross-regulation, which is needed to limit load interaction during disk-drive start-up, for example, is held to a maximum of 0.5%.

CEI uses its own low-dropout regulator-circuitry design. This high-efficiency regulator circuit provides full regulation while allowing the power supplies to retain 70 to 80% efficiency levels.

The auxiliary outputs offer true current-foldback overload protection. Under a short-circuit condition, not only will the power supply's output voltage drop, but the output current will be reduced proportionately. The supply uses a single-ended forward converter design. You can change the individual output to meet your needs by replacing just a few components. You can also adjust the current-foldback points individually on each high-current output.

Other standard features of CEI's 100-kHz switchers include dynamic inrush protection, a built-in line filter (FCC class A), remote sensing on the 5V primary output, and horizontal or vertical heat-sink fins. Op-

---

*A 200-kHz switching frequency allows a state-of-the-art switching power supply to speed past its low-frequency predecessor. Today's high-frequency switchers not only offer higher performance, they also take up less space in your equipment. (Photo courtesy Sierracin/Power Systems)*



---

*Companies are using new materials, components, and component-packaging techniques to solve the heat-dissipation problems in small power-supply packages.*


---

tionally, you can add ac-okay and power-fail signals to the supplies.


Because MOSFETs use simpler external drive circuitry, the calculated MTBF figure for power supplies incorporating them is higher than that for supplies incorporating bipolars. Note, however, that a high calculated MTBF doesn't necessarily indicate a high actual MTBF. MIL-STD-217 MTBF calculations, for instance, are heavily weighted by the number of parts in a system.

Further, MOSFETs have proven to be more reliable than the older bipolar devices in power-supply designs. But it's not certain whether MOSFETs are intrinsically more reliable than bipolars, or whether MOSFET devices are more reliable because they're made in newer production facilities and with newer processing techniques. Bipolar-device manufacturers are currently upgrading their production facilities and processes; it remains to be seen whether MOSFETs will prove to be more reliable than new bipolar devices.

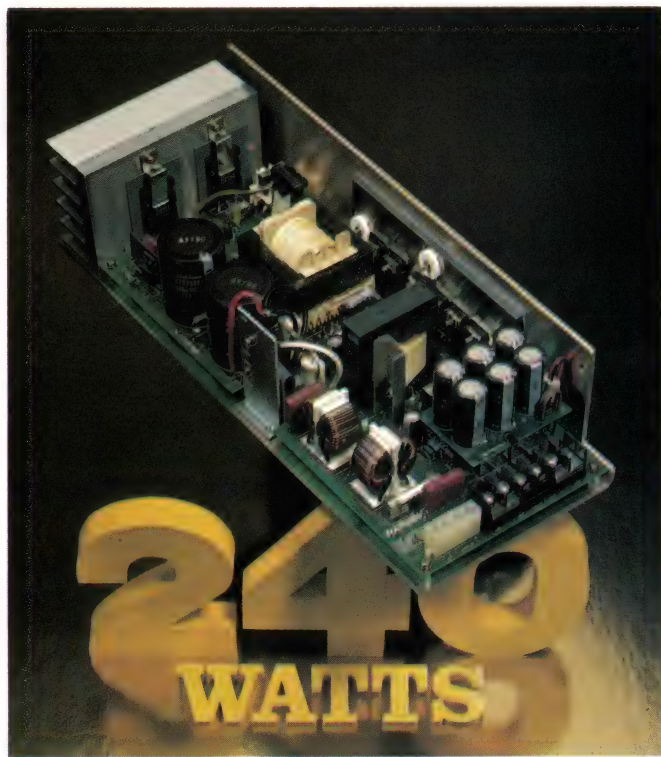Most of the switching power supplies using high-frequency architectures are low- to medium-power,



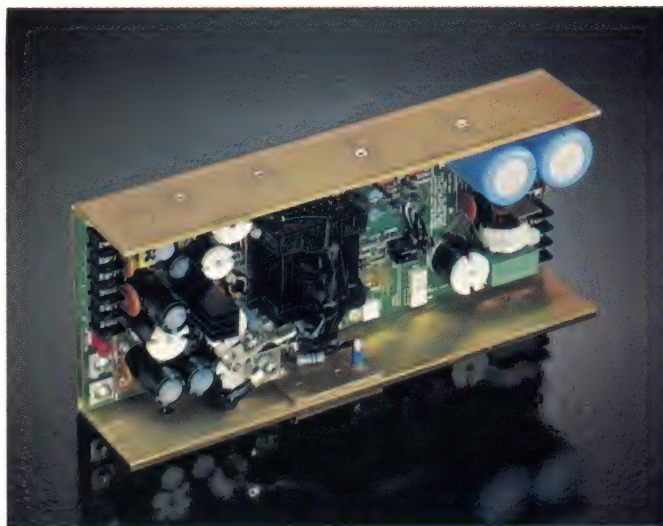**Rectangular current limiting lets you drive nonlinear loads or use multiple Kepco ERX power supplies in series. A monitor warns you of ac power loss within a half cycle, so you typically have 30 msec to shut down your system.**



**To put its 400W, 60-kHz open-frame supplies into a 144-in<sup>3</sup> package, Todd Products mounts components in surface-mount packages on the underside of the pc board.**

open-frame products geared for the high-volume computer industry. However, these supplies are not the only ones that realize the benefits of high-frequency MOSFET-based designs. For example, HC Power offers the HC Series 500 to 1500W single- and multiple-output supplies in industry-standard (5×8-in.) packages. Supplies in the HC Series include single-output units rated from 2V to 48V at 11A to 340A. Dual-, triple-, quad-, and penta-output supplies have primary outputs of 5V at as much as 230A.

You can order secondary outputs of 2V to 48V at 6A to 30A and auxiliary outputs of 2V to 48V at 2A to 10A. The fifth output on the penta-output supply is available as a 12V or 24V disk-drive supply. It provides continuous current ratings of 5A to 10A and peak loading current of 8A to 15A.

Instead of using the more popular voltage-mode control in its switchers, HC uses current-mode control. Both control schemes are based on feeding an error voltage back to one of the comparator's two inputs. In the voltage-mode control circuit, a fixed oscillator is connected to the second comparator input. In the current-mode control circuit, a voltage that's proportional to the output current is fed to the second input.

Current-mode control offers several advantages over voltage-mode control. First, a power supply that uses current-mode control can react more quickly to input voltage changes. In such a power supply, the drive logic monitors each switching-transistor pulse. In comparison, a voltage-mode unit can take five to 10 cycles



before responding to an input change. The current-mode-control supply, therefore, instantaneously rejects input-voltage transients and noise, which are the primary causes of switching-element failures in power supplies. Current-mode-control supplies also exhibit better transient response to large step-load changes than do voltage-mode supplies. For the HC Series, this transient response is typically less than 50  $\mu$ sec. In comparison, voltage-mode supplies typically respond in 100 to 150 msec.

Because current-mode-control supplies monitor output current, you can connect them in parallel without having to match their output voltages precisely. Further, when you're using the supplies in redundant-operation modes, you don't have to match load cables to compensate for IR drop. In a current-mode-control design, the paralleled outputs are forced to share current to within 1%. The HC devices incorporate a current monitor, which provides a calibrated voltage proportional to the output current. Other logic and control functions in the supplies include a remote sense, power-fail warning, and remote margin control.

### High-frequency switching has some drawbacks


Although supplies that switch at high speeds can use smaller inductive and capacitive components, they also experience increased power losses in choke and transformer cores. To solve this problem, Kepco/TDK uses a new ferrite material, H7C4, in all of its Series RBX chokes and transformers. H7C4 has lower loss-vs-frequency and loss-vs-temperature characteristics than do many other materials. High switching frequencies also cause power losses in the transformers' copper windings because of skin effect. To reduce these losses, Kepco uses Litz-type stranded wire in its transformers.

Another manufacturer, Theta-J, experienced a similar problem when it increased the switching frequency of its 50W supply to 350 kHz and the frequency of its 100W unit to more than 750 kHz. To minimize power losses caused by interwinding capacitive variations and skin losses, Theta-J uses smaller inductive components with fewer turns. The 5V transformer, for example, uses a 1-turn secondary.

High-frequency switching also reduces the filtering efficiencies of the capacitors in a power supply's output filters. To counter this problem, Kepco/TDK stacks the filter capacitors on both sides of the forward converter's output choke, thus minimizing the capacitors' inherent equivalent series inductance and resistance and improving efficiencies (Fig 1).



*Transient-response characteristics approaching those of linear power supplies and low conducted EMI are two results of the harmonic-resonant design of Sierracin/Power Systems' 400W switcher. Switching at 200 kHz, the supply offers a 2.9W/in<sup>3</sup> power density.*

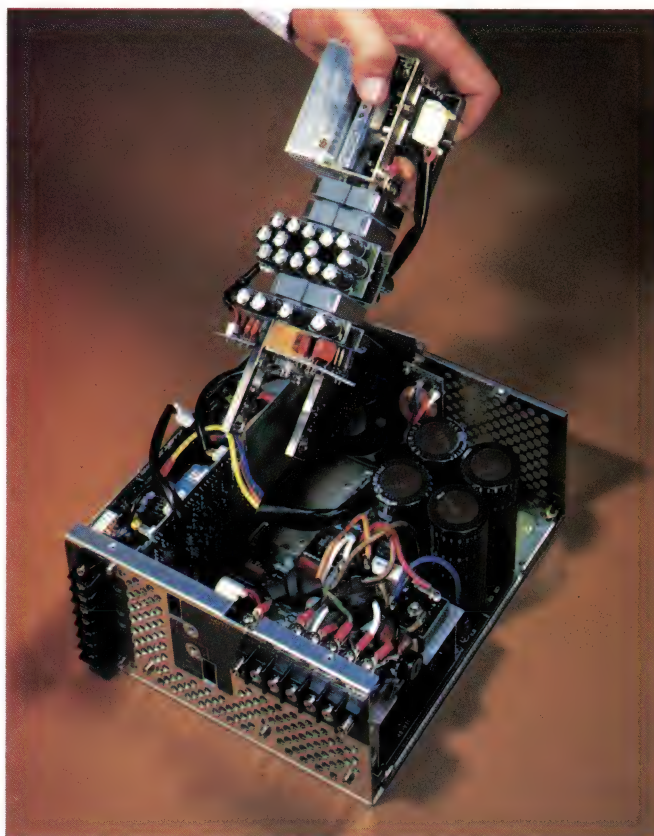


*Fig 1—To reduce high-frequency filter-efficiency losses in its RBX power supplies, Kepco stacks as many as 39 filter capacitors on either side of the forward converter's output choke.*



*When a supply's operating frequency doubles, the volume necessary for its capacitive and inductive energy-storage elements is cut in half.*

In addition, high frequencies cause inefficiency in switching transistors. In nonzero-current-switchers, current flowing through the switching transistor during turn-on and turn-off generates losses. As the operating frequency increases, a higher proportion of the energy flowing through the switching transistor is lost as heat. Theta-J solves this problem by employing a zero-current resonant-mode switching scheme in its supplies. By controlling the time that the resonant primary circuit can transfer energy to the secondary circuit, the zero-current resonant switching scheme forces the current to zero at the switching transition time, thereby reducing switching losses.

Besides using smaller inductive components in its high-frequency supplies, Theta-J reduced the size of some of the control circuitry in its supplies. The company uses a power-monitor IC and a driver IC to ensure repeatable control and operation of its supplies from unit to unit. The power-monitor IC includes a custom high-voltage circuit, and the driver IC controls the MOSFET switching circuitry. The MOSFET switching

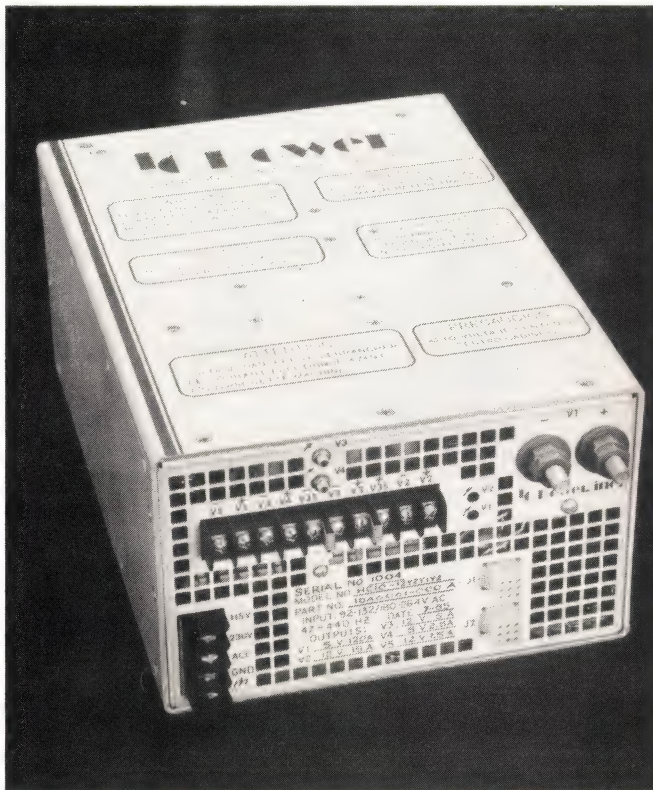

**The current-mode switching technology of this 5-output 1000W supply from HC Power improves the supply's transient response to large step changes. The switcher's outputs return to steady state within 50  $\mu$ sec.**



**Designed to meet the reliability guidelines of the Navy's NAV/MAT P-4855, these Technipower triple-output supplies can operate in harsh environments under moderate shock conditions.**

transistors are packaged with other circuitry in a custom power hybrid with both primary and secondary side functions.

Of course, high-frequency switching also causes noise problems. One manufacturer, Sierracin/Power Systems, reduces noise in its 200-kHz supplies by using a proprietary harmonic-resonant design. The company's 9S400 single-output supplies are rated at 400W (2.9W/in<sup>3</sup>).

The harmonic-resonant design closely resembles a half-bridge design whose MOSFET switching transistors operate at 200 kHz. The resonant circuit includes an inductor in the primary and a resonating capacitor in the secondary. The resonant circuit oscillates at 1.2 MHz. Because the resulting waveform is sinusoidal, the circuit generates very little switching noise, so the 9S400 switchers meet the conducted-noise requirements of both FCC Docket 20780 level B and VDE 0871 level B regulations, including the recent modifications that restrict noise above 10 kHz. The 9S400's transient-response characteristics ( $\pm 2\%$  deviation for a 75% to 100% to 75% step-load change with recovery in 100  $\mu$ sec) approach those of linear supplies.

Both the HC Power and Sierracin power supplies shut down automatically when their internal-temperature safety limits are exceeded. To operate at full load, the Sierracin 9S400 requires additional cooling either through conduction or forced air.

#### **New thermal designs counter heat troubles**

Kepco/TDK uses built-in fans to cool its RBX Series supplies. If the fan fails, a monitor circuit inhibits the power-MOSFET drive and turns the output off. The




RBX switchers are 600W single-output units. They're available with 2V, 5V, or 24V outputs, and their operating efficiencies range from 65% (for the 2V model) to 85% (for the 24V model).

Theta-J's 50W and 100W supplies both feature 4.5W/in<sup>3</sup> power densities. To counter the internal heating problems associated with such a high density, the company uses a common-surface thermal design that eliminates the use of individual heat sinks. In the design, all the dissipative components (the dissipative core materials, the primary-side power switch module, and the secondary rectifiers) are attached to a metal baseplate through selected heat-resistant insulators. All other components that must be kept cool are mounted so that they have maximum thermal resistance to the baseplate and minimum thermal resistance to the ambient.

Theta-J's power supplies represent the highest frequency off-line switchers. You can, however, use dc/dc modules such as Vicor's (Andover, MA) VI-100 models to build off-line switching supplies that operate at higher frequencies. (See **box**, "Use dc/dc modules to build an off-line power supply.")

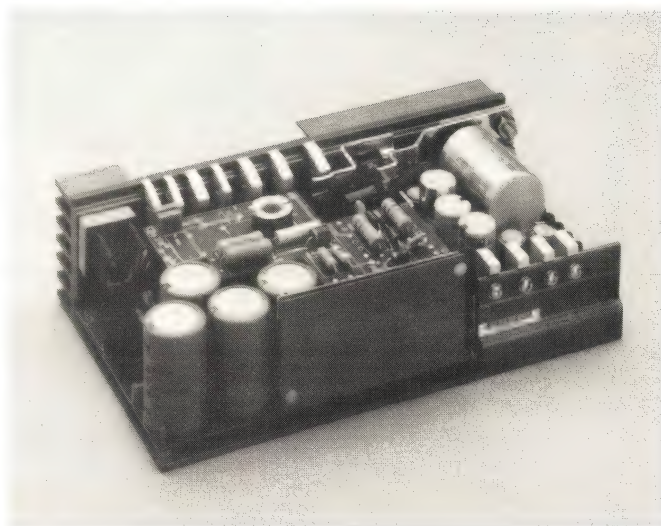You can choose a 75W module with a 5V output, or you can select one of four 100W modules with either a 12V, 15V, 24V, or 48V output. For more power, you can add booster modules. Each booster module doubles the power of its master. You can add as many boosters as you need to reach the power level you desire or to build




*At 10×5×2.75 in., this 500W power supply from Summit Electronics is smaller than many 200W power supplies. It offers a power density of 3.6W/in<sup>3</sup>.*


system redundancy into your design.

The Vicor switching modules are based on a 1-MHz, zero-current-switching forward-converter topology. Unlike Theta-J, Vicor doesn't use a resonant scheme to zero the current at the power transistors' switching times. The modules feature power densities of 13 to 51W/in<sup>3</sup> and good dynamic-load-regulation characteristics. The output voltage returns to within 1% of steady state within 100  $\mu$ sec after a 10% to 100% load change.

*Text continued on pg 138*

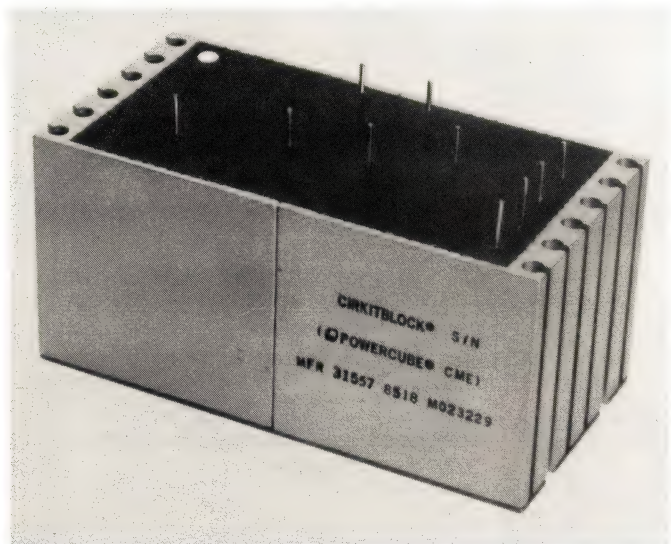

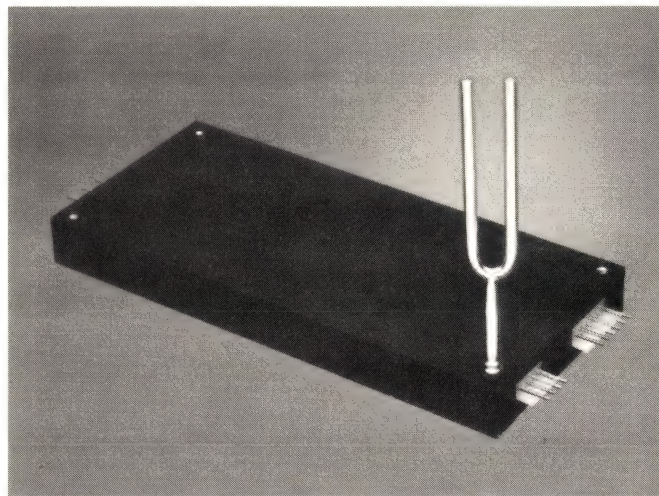*You provide the rectified ac input to generate a 50W, 5V output from Powercube's Icecube. To obtain more power, you can connect two or more Icecubes in parallel.*



*Operating to more than 750 kHz, this 100W switcher, the Q100ADAD from Theta-J, achieves a power density of 4.5W/in<sup>3</sup>. To counter the internal heating problems associated with such a high density, the company uses a common-surface thermal design that eliminates the use of individual heat sinks.*



## Use dc/dc modules to build an off-line power supply

Steven D Cogger, *Vicor Corp*

Until recently, when you needed a power supply with more +5V power than a power-supply manufacturer offered or when you needed a voltage other than the standard  $\pm 5$  or  $\pm 12$ V, you either had to buy a special power supply (by paying a nonrecurring engineering charge and making a volume commitment) or you had to design your own supply. Now, however, you have a third option: You can use dc/dc modules to design your own supply.

All off-line switching power supplies are dc/dc converters with ac-to-dc conversion circuitry on the front end. Designing your own power supply with dc/dc converter modules (such as Vicor's 1-MHz modules) is an easy task. Your main task is to


design the ac-to-dc front end and select heat-sink components. By using modules with high power densities, you can design power supplies having energy densities of  $3.9\text{W/in}^3$  without using surface-mount devices or special manufacturing techniques.

For example, assume you need a supply with outputs of +5V at 15A, +12V at 7A, and -12V at 5A. You can configure this supply with a Model V1-160 and two Model V1-161 modules from Vicor. The outputs are isolated, so you can obtain positive and negative outputs by wiring the modules' outputs as shown in Fig A.

First, you calculate the total output power of the supply by adding the output power from each module. The total output of the modules in this example is


219W. The total power required from the ac-to-dc rectifier is the total output power divided by the efficiency of the modules. The modules employ a zero-current-switching topology, so their minimum efficiency is 80%. The total input power required is  $219\text{W} \div 0.8$ , or 273.75W.

Next, you calculate the input current to determine the value of filter capacitors  $C_4$  and  $C_5$ . This calculation is the total input power, 273.75W, divided by the nominal line voltage. Because the front end is a voltage doubler, comprising  $C_4$ ,  $C_5$ , and a full-wave bridge (B), the voltage is  $2(115 \times 1.4)$  or 320V dc. The power supply's nominal input current is 0.86A. You calculate the value of the capacitors by using this equation  $c = it \div V$ , where  $i$  is the nominal input current,  $t = 8.33$  msec for a 60-Hz

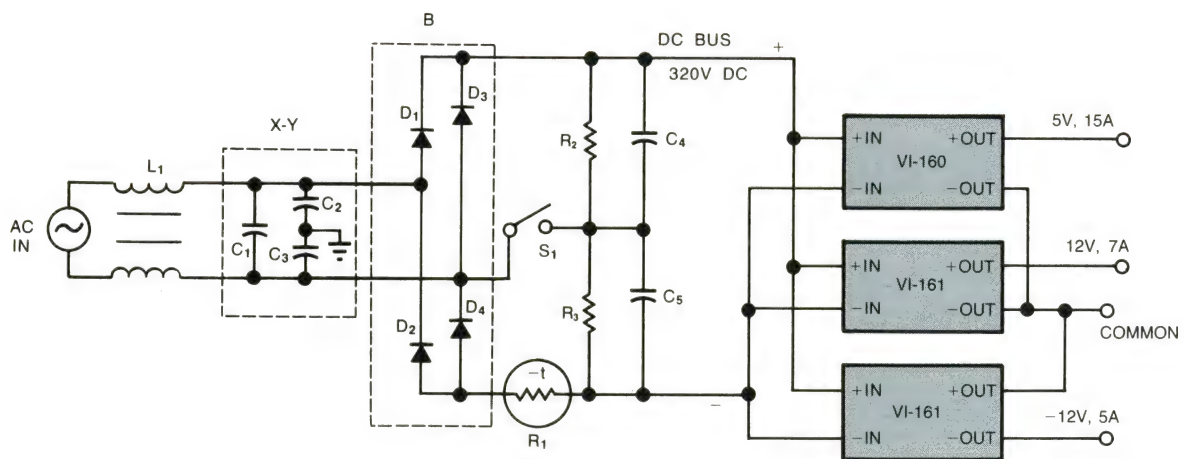

**Fig A**—The circuitry you add to Vicor's VI-160/161 dc/dc modules provides the ac/dc conversion, filtering, and in-rush current-limiting functions of a high-frequency off-line switcher.



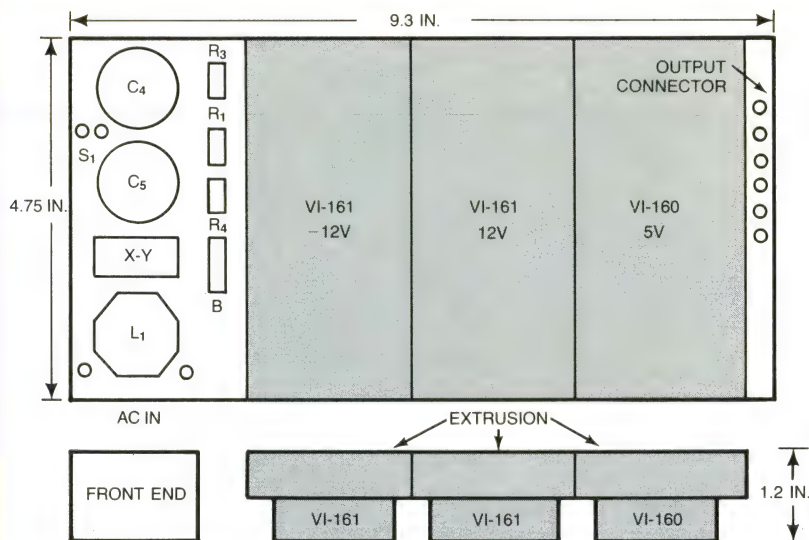

**Fig B**—To dissipate heat from your  $3.9\text{W/in}^3$  power-supply design, you should select an extrusion that has a thermal resistance to air of about  $2.4^\circ\text{C/W}$ .

line, and  $V$  is 30V (a design parameter of the modules).

The total capacitor value is  $237\ \mu\text{F}$ . Because the input is a voltage doubler and the capacitors are in series, you multiply the total input capacitance by 2 and choose the closest standard value. In this design,  $C_4$  and  $C_5$  must be  $470\text{-}\mu\text{F}$ , 200V capacitors.

The negative-temperature-coefficient (NTC) thermistor ( $R_1$ ) limits inrush current. For this design,  $R_1$ 's cold value is  $10\Omega$ , which limits the turn-on surge current to 32A on the first cycle. The rectifiers,  $D_1$  through  $D_4$ , must handle the peak inrush current and the peak current needed to charge the filter capacitors every cycle. A safe design value for the diode current

rating is five times the steady-state dc current. This design uses 5A diodes. You can buy a full-wave bridge in a single assembly instead of using four separate diodes.

To meet VDE and FCC noise specifications, you need the input filter, which comprises  $L_1$  and  $C_1$ ,  $C_2$ , and  $C_3$  (the X-Y assembly). Because the modules' operating frequency is so high, the filter elements are much smaller than those required for a 20-kHz power supply. When you lay out the front end, be sure to observe UL and VDE spacing requirements.

Finally, the design requires heat sinking. Overall conversion efficiency is an important factor in heat-sink calculation. Consider two 100W supplies, one with

70% efficiency, the other with 80% efficiency. The supply with 70% efficiency dissipates 42.9W, the one with 80% efficiency dissipates 25W, for a difference of 17.9W. Although this difference doesn't seem large, it represents an extra  $35.8^\circ\text{C}$  in a  $2^\circ\text{C/W}$  heat sink.

You can mount the modules in any direction. In some cases, you can mount the modules on an inner wall or on a baffle in your system. If you use an inner wall, the heat sink will essentially be free and will require no extra power-supply volume. Assuming the ambient air temperature is  $40^\circ\text{C}$  max, and the air is not moving, each module will require a heat sink to keep its baseplate temperature below  $85^\circ\text{C}$ .

The module that provides 12V at 7A can operate at 82% efficiency, so it will dissipate 18.4W at full load. You should choose a heat sink with a thermal resistance to air of about  $2.4^\circ\text{C/W}$  or less. A common extrusion that's 4.56 in. long and 0.750 in. high with 19 fins on 0.250-in. centers has a thermal resistance of  $2.0^\circ\text{C/W}$  and is a good choice for this application. You can use the same extrusion on all modules.

**Fig B** shows the space that your power-supply components will require. All parts shown are available from stock. The volume of the package is  $53.89\text{ in}^3$ , so its power density is  $3.9\text{W/in}^3$ .

*The author is an applications engineer for the Andover, MA, firm.*



---

*A high calculated MTBF doesn't necessarily indicate a high actual MTBF. Often, the calculations are heavily weighted by the number of parts in a system.*

---

The calculated MTBF for the modules is 214,000 hours. This high calculated value is due in part to the low parts count (less than 50) and the lack of aluminum electrolytic capacitors in the Vicor design.

Powercube (Billerica, MA) also offers high-frequency dc-input modules to which you supply a rectified input. The 4×2×1.9-in. 50W model costs \$880; the 7.5×4.9×7.8-in. 500W version costs \$3750. Both enclosed models furnish a single 5V output (line and load regulation each spec at ±0.5%) and employ MOS transistors that switch at 100 kHz. The supplies meet MIL-STD-461. (Several companies offer high-frequency dc/dc switchers that accept low-voltage inputs; see, for example, pg 118.)

#### **Check regulations when choosing supplies**

When you're choosing a power supply for your system, don't overlook the safety regulations that will apply to your product. If you want to sell your system abroad, for example, you'll have to have it certified to

international regulations, so the power supply you choose must be able to meet these regulations.

Because safety regulations limit the space between components in a supply, manufacturers of these smaller supplies will find it harder to certify their products. Keep the applicable regulations in mind when you specify one of these supplies.

Currently, more than 25 national and multinational agencies exist to decide whether your products can be sold within their countries or areas of influence. The most familiar agencies are Underwriters Laboratories in the US, Canadian Standards Association in Canada, and Verband Deutscher Elektrotechniker (VDE) in Germany.

In many countries, you're not permitted to sell your products unless they meet the requirements of a specific standard or standards. For example, Telecom equipment attached to the British phone system must meet the requirements of the British Telecom (formerly British Post Office) Technical Guide No 26. Telecom and

## **External power supplies**

Bob Marks, *Ault Inc*

For designs requiring 100W or less, you needn't resort to a compact high-frequency switching power supply in order to accommodate limited space requirements within your equipment; an external switching power supply can be a cost-effective alternative. External supplies are especially suitable for powering computer peripherals, disk drives, CRT displays, microprocessors, telephone key sets, multiplexers, modems, and other data-communications equipment.

External power supplies offer several advantages over internal supplies. First, they save you the time and trouble of designing an internal power source. They'll also save space in your

system, so you can either reduce the size of your design or add extra features. And because an external supply won't contribute to heat buildup inside your design, your system will undergo less stress during operation, so it may achieve a higher MTBF. You may be able to eliminate fans and even vents from your system. Finally, if your external supply ever fails in the field, you can simply unplug it and plug in a new one.

Currently, triple-output external switchers can deliver as much as 50W; 100W units are still under development. External supplies come in two basic styles. The smaller, lower-power units plug directly into ac wall outlets. Higher-power switchers plug into the ac outlet via a line cord and sit out of the way on a

desktop or the floor.


External switching power supplies typically employ either off-line or secondary switching. Off-line switching is suitable for systems requiring high power and performance. Less-expensive secondary switchers provide lower power levels.

External switching power supplies come in a range of outputs and case sizes. For example, Ault's off-line switchers supply either 25 or 50W and come in 6.5×3.75×2.25-in. cases; they cost less than \$90. The company's secondary switchers are rated at about 16W and come in 4.7×2.7×2.2-in. cases. The supplies use surface-mount components.

*The author is director of design engineering for the Minneapolis, MN, firm.*



# Eye-Tech

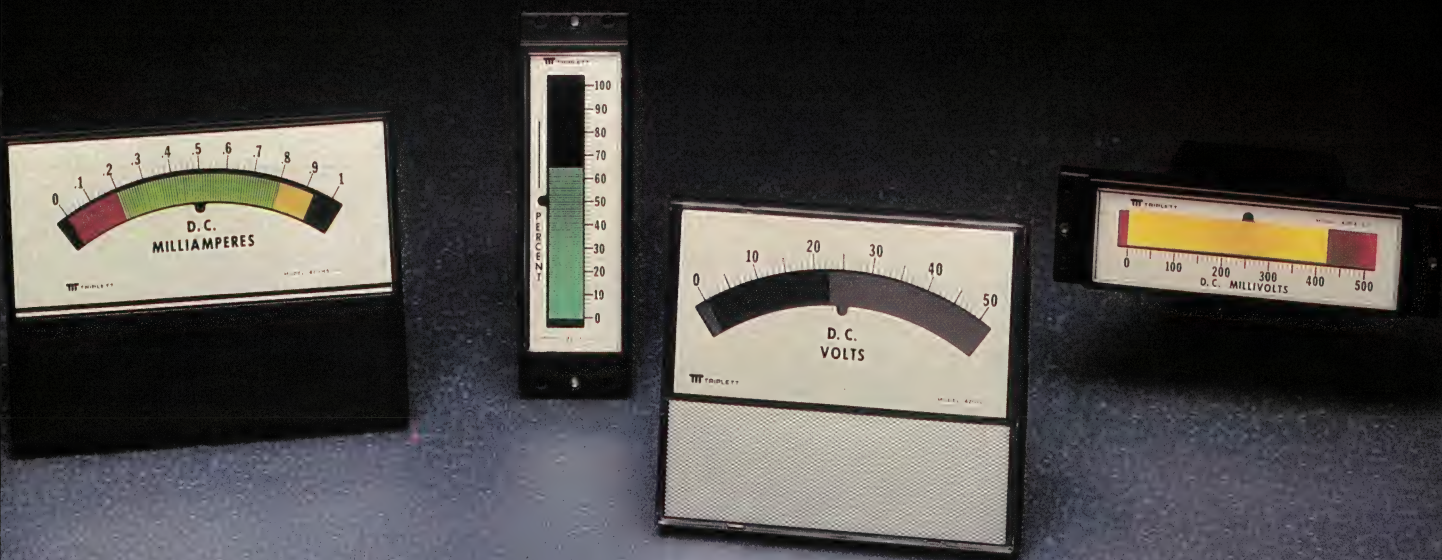

## See Triplett Technology in a Different Light. Versatile Panel Instrumentation

Triplett announces a revolution in high-tech panel instrumentation: innovative, readable LCD bar graphs. These exciting panel meters further establish Triplett as the worldwide leader in the design and manufacture of panel instruments and test equipment.

**Versatile.** Computer-compatible panel meters come in 16 models and 13 modes. The 103-segment bar graphs are specifically designed as replacements for the popular 3.5 and 4.5 inch analog instruments, as well as for new installations.

**Advanced.** Triplett's technology offers you panel instrumentation that indicates data, high set point, low set point, both set points, peak, valley, both peak and valley and alternate between data and the six modes of display. The bar graphs are highly visible from a distance of 20 feet.

Colorful, back-lit displays are available in red, green, amber or blue. You may also choose any combination of these colors. Black on gray is standard.

**Adaptable.** Panel meters are available in the "G" Series curved display; the "WS" Series curved display and in the Edgewise Series, vertical or horizontal with a front or rear mount.

When you are looking for the finest in high-tech panel instrumentation, look to Triplett, the Company America has trusted for more than 80 years.

For more information, call 1-800-TRI-PLET ext. 40.



**TRIPLETT CORPORATION**  
A Penril Company

Circle 99 for FREE demonstration



*Some manufacturers are building smaller supplies by using MOSFET switching transistors, which can switch at higher frequencies than can bipolars.*

data-processing equipment sold in Germany must be designed and built to VDE 0804/3.77 standards.

In some countries, power supplies must be certified twice. First they must meet the requirements of the standard for power supplies, and then they must meet the standard for the product in which the power supply will be used. In the US, a power supply must first meet the requirements of UL standard 1012 for power supplies. Then, depending on the system the supply is designed for, the supply might have to meet UL 114 (for electronic office appliances and business machines), UL 478 (for electronic data-processing units and systems), or UL 508 (for electric industrial-control equipment). In Canada, power supplies must meet the requirements of CSA standard C22.2, No 107-1957, which governs rectifying equipment, as well as requirements governing the end product.

It takes from six to eight weeks to have a power supply tested and recognized by UL. VDE certification could take as long as a year. It's a good idea, then, to find out during your design stage which standards will

apply to your product and plan to have the required certification testing performed. You can, however, shorten the German certification process by using the TUV-Rheinland testing agency; its US office is located at 50 Main St, Mount Kisco, NY, 10549; phone (914) 241-2400.

Further, when you select a power supply, you must know whether the supply is actually certified to the necessary standards or whether it's only designed to meet the requirements of specific standards. For example, NCR Power Systems' supplies are UL recognized, VDE approved through testing by TUV, CSA certified and compliant with IEC 380 (IEC does not have a certification program). ACDC's RH Series supplies are UL recognized and CSA certified. The company's Model RH101 is a 100W single-output open-frame supply operating at 100 kHz. Before being shipped, all RH101 supplies are burned in for 24 hours with ac cycling and then computer tested. Test results are shipped with each unit.

Panasonic's 75W MR Series and 100W MS Series

## Manufacturers of high-frequency off-line switching power supplies

For more information on high-frequency switching off-line power supplies, contact the following manufacturers directly or circle the appropriate numbers on the Information Retrieval Service card.

### Abbott Transistor Laboratories Inc

Power Supply Div  
5200 W Jefferson Blvd  
Los Angeles, CA 90016  
(213) 936-8185  
Circle No 676

### ACDC Electronics

401 Jones Rd  
Oceanside, CA 92054  
(619) 757-1880  
Circle No 677

### CEI Corp

Box 501  
Londonderry, NH 03053  
(603) 623-8888  
Circle No 678

### Deltron Inc

Box 1369, Wissahickon Ave  
North Wales, PA 19454  
(215) 699-9261  
Circle No 679

### Energetic Systems Inc

130 E St Charles Rd  
Carol Stream, IL 60188  
(312) 653-1920  
Circle No 680

### HC Power Inc

1571 Parkway Loop, Suite D  
Tustin, CA 92680  
(714) 259-0788  
Circle No 681

### Kepeco Inc

131-38 Sanford Ave  
Flushing, NY 11352  
(718) 461-7000  
Circle No 682

### Lambda Electronics

515 Broad Hollow Rd  
Melville, NY 11747  
(516) 694-4200  
Circle No 683

### Modern Power Conversion Inc

7100 Warden Ave, Unit 3  
Markham, Ontario, Canada L3R 5M7  
(416) 477-3387  
Circle No 684

### NCR Corp

Power Systems  
584 S Lake Emma Rd  
Lake Mary, FL 32746  
(305) 323-9250  
Circle No 685

### Panasonic Industrial Co

Computer Components Div  
One Panasonic Way  
Secaucus, NJ 07094  
(201) 392-4290  
Circle No 686

### Qualidyne Systems Inc

3055 Del Sol Blvd  
San Diego, CA 92154  
(619) 575-1100  
Circle No 687

### RTE Power/mate

2875 S 171 St  
New Berlin, WI 53151  
(201) 440-3100  
Circle No 688

### Sierracin/Power Systems

20500 Plummer St  
Chatsworth, CA 91311  
(818) 998-9873  
Circle No 689

### Summit Electronics Inc

855 E Collins Blvd  
Richardson, TX 75081  
(214) 231-1456  
Circle No 690

### Technipower

Box 222, Commerce Park  
Danbury, CT 06810  
(203) 748-7001  
Circle No 691

### Theta-J Corp

107 Audubon Rd  
Wakefield, MA 01880  
(617) 246-4000  
Circle No 692

### Todd Products Corp

50 Emjay Blvd  
Brentwood, NY 11717  
(516) 231-3366  
Circle No 693

### Total Power International Inc

418 Bridge St  
Lowell, MA 01850  
(617) 453-7272  
Circle No 694

### Xentek


297 S Pacific St  
San Marcos, CA 92069  
(619) 744-3346  
Circle No 695



# More switcher choices with more reliability...



## from the name no one knows.

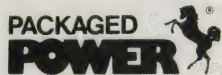

One company lays claim to the industry's broadest line of high-performance, high-reliability switching power supplies: Computer Products, Inc.

Our 36 to 200 watt models — with single, dual, triple and quad outputs — feature a reliable flyback or forward converter topology and yield minimum 70% efficiencies. With 115/230 VAC jumper selectable inputs.

When more power is the order, specify our 500 to 1500 watt switchers. Available with single, dual, triple and quad outputs, they offer field selectable 115/230 VAC inputs and efficiencies to 75%. Overload, OVP and thermal protection are built in.

Power Products' switchers are UL and CSA listed and meet EMI standards of FCC and VDE. They're perfect for building-in more performance and reliability in modems and minicomputers, CAD/CAM and telecom systems, in ATEs and industrial process control applications.

### There's No Power Supply Problem We Can't Solve

The Power Conversion Group of Computer Products Inc. now combines the resources of six separate business units — Boschert, Power Products, Stevens-Arnold, Tecnetics, Power Products Ltd. (Ireland), and Computer Products Asia-Pacific Ltd. (Hong Kong). This means we can produce virtually any type and size power supply you will ever need, from ½ watt to 2000 watts:

- AC/DC Linears and Switchers
- DC/DC Converters
- AC/DC Uninterruptible Power Systems
- Standard, Special and Custom
- Commercial, Industrial and Mil-Spec

All have guaranteed reliability, and most are backed by our no-hassle two-year warranty. And we offer high-quality design and application assistance, plus prototype services and a host of other supports we call **PACKAGED POWER**.

Contact us now for free product literature.



2981 Gateway Drive • Pompano Beach, FL 33069 • Phone (305) 974-2442 • TWX 510-956-3098

CIRCLE NO 135



# Brown Boveri Power Semi- conductors

## Diodes and thyristors in plastic and stud housings

- Up to 295 A
- Products of quality manufactured in West Germany
- Technical Service and application support


**Your way  
to the right  
Power  
Semicon-  
ductors**



For further information please contact:

Brown Boveri & Cie · Aktiengesellschaft  
Geschäftsbereich Halbleiter, HL/MA 1  
Semiconductor Division  
P.O. Box 1180, D-6840 Lampertheim  
Phone (0 62 06) 503-1, Telex 462 411 602 bbd

**BBC**  
BROWN BOVERI

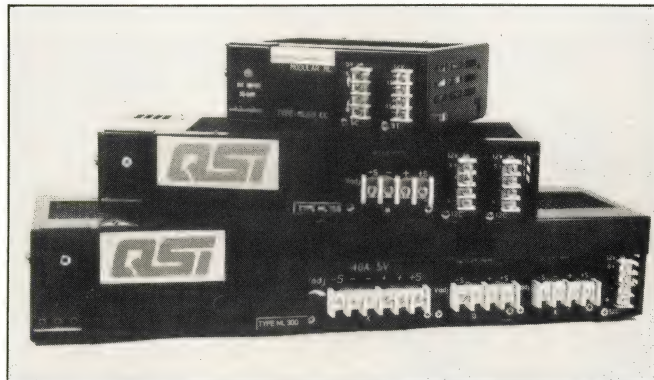

*You can build your own power supply by selecting from Qualidyne's power modules, post regulator modules, and enclosures.*

supplies are recognized by UL, certified by CSA, and approved by TUV to VDE standards. The supplies also conform to IEC 380 and BS 5850.

Because of the long certification cycle, many power-supply manufacturers offer supplies for sale before they've been certified. Deltron's V Series is an example. The V Series is designed to meet VDE, IEC, UL, CSA, BT, ECMA (European Computer Manufacturers Association), and CEE (International Commission on Rules for the Approval of Electrical Equipment) specifications. The supplies feature 3750V ac isolation, 8-mm spacing between primaries and secondaries, 4-mm spacing between primaries and ground, and a 0.75-mA leakage current between line and ground. The manufacturer is in the process of having the supplies certified.

For supplies that the manufacturer claims are "designed to meet" a certain standard, you'll have to determine on your own whether they'll actually meet the requirements when put to the test.

**EDN**

Table begins on pg 146

## References

1. Pressman, A, *Switching and Linear Power Supply, Power Converter Design*, Hayden Book Co, Rochelle Park, NJ, 1977.
2. Wright, M, "Special Report: Switchers," *EDN*, May 2, 1985, pg 102.
3. *Regulatories in the Electronics Marketplace*, Sierracin/Power Systems, Chatsworth, CA, 1984.

Article Interest Quotient (Circle One)  
High 470 Medium 471 Low 472




# THE SMALLEST COMMERCIAL SWITCHERS IN THE WORLD


**GX 500 (500 Watts)**  
10" x 5" x 3"




**GX 750 (750 Watts)**  
15.5" x 5" x 3"

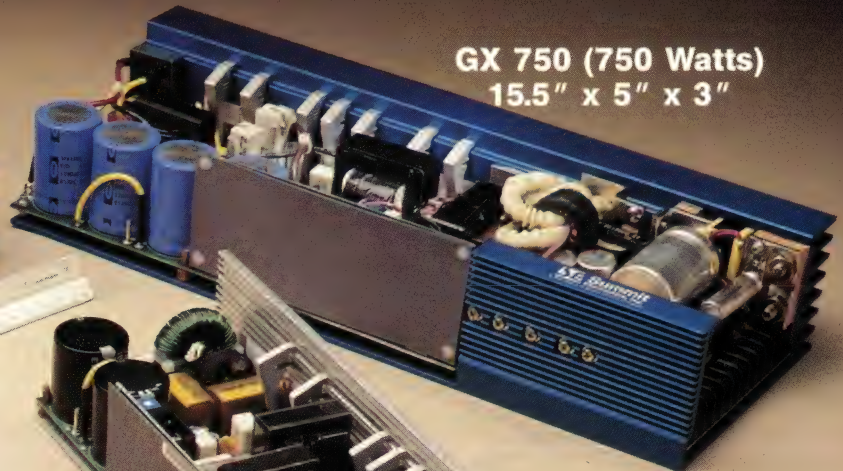

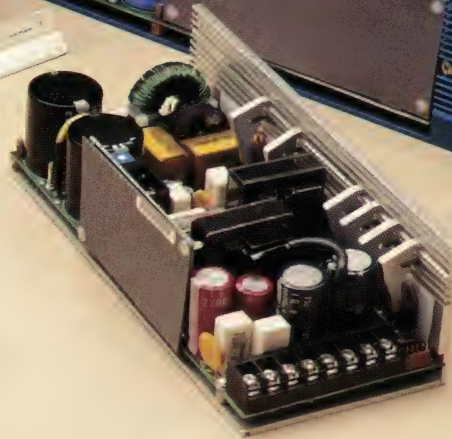**FX 300 (300 Watts)**  
4.5" x 9" x 2.5"



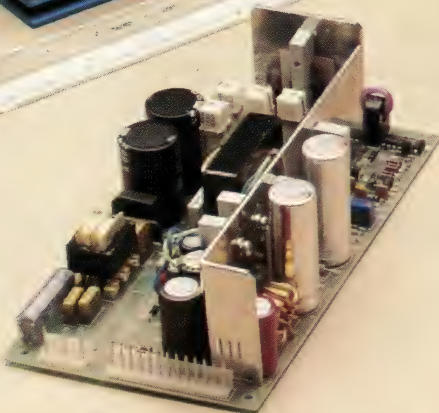**FX 150 (150 Watts)**  
4.25" x 8.25" x 2.75"



## New FX Series and GX Series of Switching Power Supplies.

- Up to 3.6 watts per cubic inch
- 50¢ per watt in volume
- Three to five outputs
- Adjustable auxiliary outputs
- 100 watt output
- FCC EMI filters
- UL / CSA / IEC / VDE approvals pending.

**GX Series Ruggedized to MIL-STD-810D**

**Call Our Toll Free  
Information Hot Line Today!  
(800) 645-2074**

In Texas Call (214) 231-1456  
Jack Barry, Vice President Marketing  
Steve Mole, Sales Manager  
Bryan Bristol, Customer Service

**SE Summit<sup>®</sup>**  
**Electronics, Inc.**

A subsidiary of Basler Electric Company, Highland, Illinois

855 East Collins Boulevard  
Richardson, Texas 75081



# OUR QUARTER-POUNDER OF POWER

## Military 100 Watt DC-DC Converters

- Weight: 1/4 pound
- Size: 4 cubic inches
- Power: 100 Watts
- Density: 400W/lb & 25W/in<sup>3</sup>
- Switching Frequency: 1 Megahertz



Inland Power Technology serves up state-of-the-art DC to DC converter technology. Encapsulated 4 ounce, 4 cubic inch modules that supply up to 100 Watts of low noise, tightly regulated DC power.

They're built to meet the requirements of MIL-STD-810A for shock, acceleration, vibration, altitude, humidity and salt spray. Reliability is exceptional with a calculated MTBF of over 200,000 hours at 80°C per MIL-HDBK-217D.

These mighty 100W modules are designed especially for portable, vehicle and airborne applications where high efficiency and small size and weight are important. Standard input voltages which cover the range from 10Vdc to 370Vdc are available with outputs from 2Vdc to 100Vdc.

We can also configure complete power systems with output powers in excess of 2KW and power densities up to 47 W/in<sup>3</sup>. For example, a triple output system with 5V @ 105 A &  $\pm 15V$  @ 6.7A has a volume of only 24 in<sup>3</sup> and weighs a mere 1 1/2 lb.

Call us for complete information on our full line of military quarter-pounders — the most significant improvement in power supply technology since the advent of the switcher.



Power Technology Group  
**Inland Motor Division**  
Kollmorgen Corporation

4020 E. Inland Road • Sierra Vista, AZ 85635  
Phone: (602) 459-1150 • TWX: 910-973-9869




# How to design a power supply in 2½ minutes.

Immediate shipment on 57 standard models.

Do what IBM, Control Data, Sperry, Xerox, and AT&T do. Spin your Rolodex to "P" and phone Pioneer.

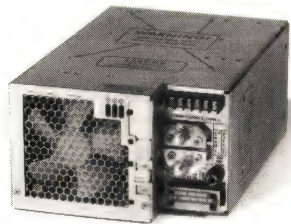In less time than it takes for a cup of coffee, you



can have Number One in high power switchers working on your power supply. And you can get back to work on your system.

Pioneer starts by taking you through our QuickCheck Spec List. Is your input AC or DC? How many watts of output power—from 375 up to 2000—do you need? How many channels? What tolerances? Does your unit need to meet International EMI specs? Or International Safety specs to the SELV level? Need built-in Volatile Memory Backup (or any of three dozen other options)?

**Pioneer Magnetics**  
"#1 In High Power Switching Supplies."

1745 Berkeley Street, Santa Monica, Ca 90404  
(800) 233-1745 outside California  
or (800) 848-1745 in California

No matter how unique the specs on your unit, chances are excellent that Pioneer has built one like it—not once but many times. (We should have; we've shipped well over a quarter million units.)

So you don't have to worry about expensive one-of-a-kind pricing. Or reliability. One customer put 333 Pioneer units through a million-hour cumulative evaluation. Result: MTBF's in excess of 115,000 hours!

Call Pioneer toll-free at 800-233-1745. In California, 800-848-1745. And turn your design needs over to us. Or if you'd just like to know more, we'll send a full Information Pack on our complete line of high power switchers with no obligation.



**Pioneer Magnetics. Because systems designers should design systems, not power supplies.**

CIRCLE NO 140



# REPRESENTATIVE HIGH-FREQUENCY OFF-LINE SWITCHING POWER SUPPLIES


MANUFACTURER	MODEL NUMBER	OUTPUT POWER (W)	OUTPUT VOLTAGES (V)	ENCLOSED (E) OPEN FRAME (O)	DIMENSIONS (IN.)	POWER DENSITY (W/IN.)	EFFICIENCY (%)
ABBOTT	MB100T	100	5, $\pm 12$ ; 5, $\pm 15$	E	1.875 x 3.5 x 7.5	2.0	65
ACDC	RH101	100	5	E	8 x 4 x 2.2	1.4	75-85
CEI	XL150	150	$\pm 5$ , $\pm 12$ ; 5, $\pm 12$ ; 5, $\pm 15$	O	8 x 4.6 x 1.9	2.2	70-85
	XL250	250	5; 5, $\pm 12$ ; 5, $\pm 12$ , +24; $\pm 5$ , $\pm 15$	O	10 x 5 x 2.125 (MULTI-OUTPUT VERSIONS)	2.4	70-85
DELTRON	V120A	120	5	O	2.5 x 8.5 x 7	0.8	80
	V360D	360	24	O	2.5 x 10.5 x 9	1.5	80
	V500A	500	$\pm 5$ , $\pm 12$	O	2.75 x 13 x 11.5	1.2	80
ENERGETIC SYSTEMS	ALPHA	50	5; 12; 24	O	4 x 4 x 1.6	2.0	80
	BETA	60	24; 48	E	5.7 x 5.9 x 1.5	1.2	80
	DELTA	60	5, $\pm 12$ ; 5, $\pm 15$	O, E	5 x 4 x 1.5	2.0	75
HC POWER	HC15-1	1500	5	E	5 x 8 x 11.25	3.3	75
KEPCO/TDK	ERX 5-48	240	5	O	12.9 x 3.5 x 2.8	1.9	68-80
	RBX 05-120K	600	5	E	3.74 x 7.87 x 8.66	2.4	80
	RBX 24-25K	600	24	E	3.74 x 7.87 x 8.66	2.4	85
	MRM 270KV	120	+5; $\pm 12$ ; -12; -5	O	10.5 x 5 x 2.5	0.6	75
LAMBDA	LRS-52-5	75	5	E	2 x 4.9 x 6.25	1.2	67
	LRS-56-5	450	5	E	4.4 x 4.9 x 11.5	1.8	75
MODERN POWER CONVERSION	150B/200	200	5, $\pm 12$ ; $\pm 5$ , $\pm 12$ ; 5, $\pm 12$ , +24; 5, $\pm 12$ , +28; 5, $\pm 12$ , +8	O	10 x 5 x 2.3	1.7	80
NCR	HZNNL05121205	230	5, $\pm 12$ , -5	O	11.5 x 6 x 2	1.7	70
PANASONIC	ETU-5V120U	60	5	O	3.9 x 8.1 x 2.2	0.9	65
QUALIDYNE SYSTEMS	ML 100 A1	100	5	E	2.36 x 5.17 x 9.25	0.9	70-85
	ML 300 K6	300	5, $\pm 12$ , +24, -5	E	3.15 x 5.17 x 15.75	1.2	70-85
RTE POWER/MATE	EV-H	200	5; 12; 15; 24	O	4.9 x 2.3 x 9	2.0	75
SIERRACIN/POWER SYSTEMS	9S300	300	5; 12; 15; 24	O	10 x 5 x 2.5	2.4	72
	9S400	400	5; 12; 15; 24	O	11 x 5 x 2.5	2.9	72
SUMMIT	GX500 5001	500	$\pm 5$ , $\pm 12$ , +24	O	10 x 5 x 2.75	3.6	75
	GX650 5004	650	$\pm 5$ , $\pm 15$ , +12	O	14 x 6 x 3	2.6	75
TECHNIPOWER	TVC/12-40/4.2	300	5, $\pm 12$	E	15 x 7 x 3	1.0	60-80
THETA-J	P7ADD	7.5	5, $\pm 12$	E	4.4 x 2.2 x 0.65	1.2	70
	P50ADD	50	5, $\pm 12$	E	2.8 x 5 x 0.8	4.5	80
	Q100ADAD	100	5, $\pm 12$ , -5	E	3.5 x 7.8 x 0.8	4.5	80
TODD PRODUCTS	MDT-400	400	5, $\pm 12$	O	11.5 x 5 x 2.5	2.8	75
	MDX-400	400	5, $\pm 12$	O	11.5 x 5 x 2.5	2.8	75
TOTAL POWER	KSY054506	1000	5	O	5 x 13.4 x 12.6	2.7	70



OUTPUT RIPPLE/NOISE	LINE REGULATION	LOAD REGULATION	BIPOLAR (BI) OR MOSFET (MOS)	SWITCHING FREQUENCY (kHz)	SAFETY AND EMISSIONS STANDARDS MET	PRICE (QUANTITY)	COMMENTS
100 mV p-p	10 mV	10 mV	MOS	200	MIL-STD-461B, MIL-S-901C	\$1300 (1)	3-PHASE/WYE OPTION
100 mV p-p	0.2%	0.2%	MOS	100	UL, CSA, IEC, VDE	\$172 (1)	
25 mV rms	± 0.5%	± 0.5% TO ± 1.0%	MOS	100	DESIGNED TO UL, CSA, FCC-A	\$195 (1)	INRUSH PROTECTION, LINE FILTER
25 mV rms	± 0.5%	± 0.5% TO ± 1.0%	MOS	100	DESIGNED TO UL, CSA, FCC-A	\$335 (1)	OPTIONAL AC-OK SIGNAL AND REMOTE SHUTDOWN
100 mV p-p	± 0.1%	± 0.2%	MOS	80	UL, CSA, IEC, VDE	\$180 (1)	3-YEAR WARRANTY
100 mV p-p	± 0.1%	± 0.2%	MOS	80	UL, CSA, IEC, VDE	\$360 (1)	OPTIONAL POWER-FAILURE MONITOR
100 mV p-p	± 0.1%	± 0.2%	MOS	80	UL, CSA, IEC, VDE	\$545 (1)	OPTIONAL THERMAL SHUTDOWN
70 mV p-p	± 0.2%	± 0.3%	MOS	100	DESIGNED TO UL, CSA, FCC-A	\$89.50 (1)	
50 mV p-p	± 0.1%	± 2.3%	MOS	100	DESIGNED TO UL, CSA, FCC	\$114 (1)	RACK-MOUNT ENCLOSURE
50 mV p-p	± 0.25%	± 0.2%	MOS	100	DESIGNED TO UL, CSA, FCC	\$134 (1)	
1% p-p	± 0.2%	± 0.4%	MOS	160	UL, CSA, IEC, VDE	\$1000 (1)	5-YEAR WARRANTY; MULTIPLE- OUTPUT MODELS AVAILABLE
50 mV p-p	± 1%	± 1%	MOS	100	UL, CSA, VDE	\$179 (1)	OPTIONAL STEEL COVER CAN PARALLEL 3 UNITS. 5-YEAR WARRANTY
20 mV p-p	± 0.8%	± 0.4%	MOS	150	UL, CSA	\$599 (1)	
25 mV p-p	± 0.6%	± 0.3%	MOS	150	UL, CSA	\$599 (1)	
100 mV p-p	± 1.5%	± 0.3%	MOS	100	UL, CSA, FCC-B	\$185 (1)	
35 mV p-p	± 0.1%	± 0.1%	MOS	100	DESIGNED TO MIL-STD-810C, UL, CSA, FCC-A	\$275 (1)	5-YEAR WARRANTY
35 mV p-p	± 0.1%	± 0.1%	MOS	100	DESIGNED TO MIL-STD-810C, UL, CSA, FCC-A	\$725 (1)	CONVECTION COOLING
1% p-p	± 0.6%	< 4%	MOS	100	UL, CSA	\$315 (1)	OPTIONAL POSITIVE AND NEG- ATIVE LINEAR REGULATORS
1% p-p	± 0.4%	± 0.4%	MOS	100	UL, CSA, VDE, IEC	\$310 (1)	
1% p-p	± 0.2%	± 0.5%	MOS	100	UL, CSA, VDE	\$110 (1)	
50 mV p-p	± 0.01%	± 0.05%	MOS	75	DESIGNED TO UL, CSA, VDE, BT	\$193 (1)	MODULAR CONSTRUCTION
50 mV p-p	± 0.01%	± 0.05%	MOS	75	DESIGNED TO UL, CSA, VDE, BT	\$405 (1)	
0.7% p-p	± 0.2%	± 0.2%	MOS	100	UL, CSA	\$240 (1)	CONVECTION COOLING
50 mV p-p	± 0.2%	± 0.2%	MOS	200	UL, CSA, VDE, FCC-B, VDE (EMI)	\$225 (1)	
50 mV p-p	± 0.2%	± 0.2%	MOS	200	UL, CSA, VDE FCC-B, VDE-B	\$300 (500)	
1% p-p	± 0.2%	± 3%	BI	80	UL, CSA, VDE, FCC, VDE (EMI)	\$749 (1)	
1% p-p	± 0.2%	± 3%	BI	60	UL, CSA, VDE, FCC, VDE (EMI)	\$974 (1)	
0.2% + 5 mV rms	± 0.4%	± 0.4%	MOS	100	MIL-STD-461, VDE	\$3795 (1)	MILITARY APPLICATIONS
100 mV p-p	± 1%	± 2.5%	MOS	300	UL, CSA, FCC	\$51 (1)	INCLUDES LINE CORD AND CAN BE PC-BOARD MOUNTED
100 mV p-p	± 1%	± 3%	MOS	300	UL, CSA, FCC	\$120 (1)	
100 mV p-p	± 0.5%	± 2%	MOS	750	UL, CSA, VDE, ECI FCC, VDE (EMI)	\$210 (1)	
1% p-p	± 1%	± 1%	BI	60	UL, CSA, IEC, VDE FCC, VDE (EMI)	\$535 (5)	
1% p-p	± 1%	± 1%	BI	60	UL, CSA, IEC, VDE FCC, VDE (EMI)	\$535 (5)	TIGHTER REGULATION ON AUX OUTPUTS. THIRD OUTPUT IS DRIVEN BY MAGNETIC AMP
1% p-p	± 2%	± 2%	MOS	100	UL, FCC-A	\$566 (1)	



# SOLA SWITCHERS. THE POWERS THAT BE.

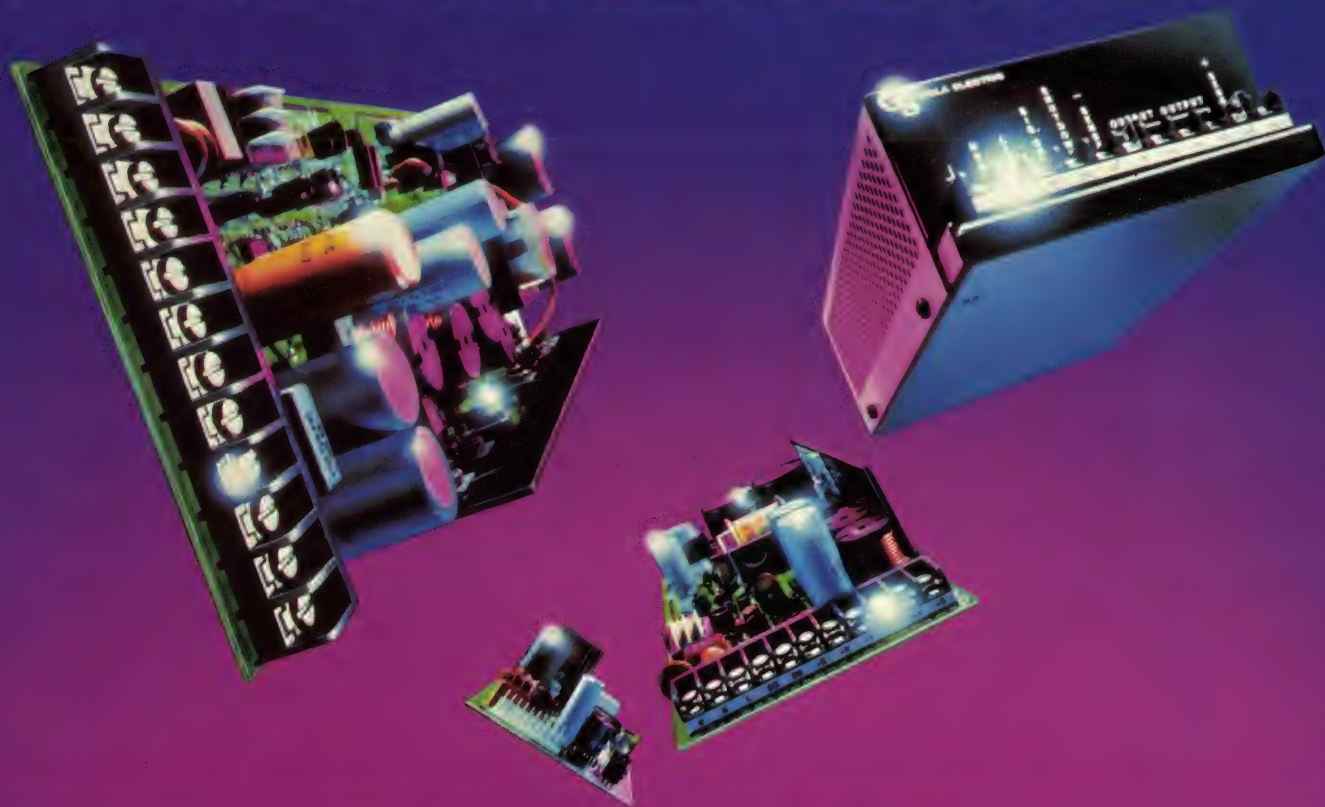

Sola, long recognized as the industry leader in power conditioning and uninterruptible power systems, announces the availability of switching power supplies through industrial distribution.

We offer twenty-nine different models for virtually every electronic application.

Ranging from 15 to 150 watts of regulated dc power, all switchers, featuring single, triple or quadruple outputs, are designed to meet or exceed the most stringent industry safety requirements, including UL and CSA approval.

Why such a diversified line? Because Sola doesn't feel that it's right for you to make do with what's available. So instead, we make available what's right for you.

The end result is your electronic products continue to perform dependably and cost-effectively. And if your OEM designs require modification or customizing, Sola will put its team of experts to work for you.

Switch to Sola switchers. After all, it only makes sense to deal with the powers that be.

A UNIT OF GENERAL SIGNAL 

**SOLA**

Write for free literature. 1717 Busse Rd., Elk Grove Village, IL 60007, (312) 439-2800.



# 200 WATT DC TO DC CONVERTERS 24V OR 48V DC INPUT



## THE CHOICE IS YOURS!

- 24V DC Input 2400 Series or 48V DC Input 1100 Series
- 200 Watts of Multiple Outputs (Up To 5 Outputs)
- High Efficiency Secondaries (MAG AMP Control)
- 3:1 Size Advantage over Single Output Supplies
- Surge Capability for Disk Drives
- *110VAC Input Available in the Same Package*

Ideal for Telecommunications, Cellular Radio  
and Distributed Power Applications.

Call or write today for a free brochure: RO ASSOCIATES, INC.  
246 Caspian Drive, Sunnyvale, CA • Telephone (408) 744-1450 • Twx: 910-339-9304

CIRCLE NO 142





**acdc's 750-1500  
watt power supply  
operates today...  
the next day...  
2,773 next  
days...**



**and  
counting.**

The demonstrated MTBF for acdc's 750-1500 Watt supplies is in excess of 7½ years! Already.

That's > 66,000 Hrs. And the burn-in test is still continuing.

And burn-in at acdc is harsh.

- 50°C
- full load
- AC cycling once a minute

This emphasis on testing is acdc's charter. It insures that specs are met or exceeded before units are approved for shipment.

acdc's new JF Series offers more than rugged reliability. Advanced technology such as Current Mode

Control allows superior Transient Response:

- < 100 mv output excursion following a 50% load step (< 400mv following a 100% load step)
- output recovery to within 1% in < 300ms

Features:

- VDE 0806 licensed by TUV
- direct paralleling
- precise current sharing—option
- minimum hold-over storage 40 ms
- standard 5" x 8" profile

- 750W, 1000W, 1500W Single output models

- 2, 5, 12, 15, 24, 28 and 48 V models available

- UL, CSA, IEC 380

For immediate assistance call (619) 439-4200. Or circle reader card for more technical information.

**acdc**  
electronics

401 Jones Road, Oceanside, CA 92054. Tel: 619/757-1880. TLX: 350227.

CIRCLE NO 143



# Don't buy any I/O Module

## until you evaluate Grayhill!



You'll find outstanding specs, performance, pricing and availability in these new I/O Modules... from Grayhill or your local Grayhill distributor, in all standard configurations. All are compatible with 5, 15 or 24V logic circuits.

AC output	120V or 240V	black case
DC output	3V to 60V	red case
AC input	120V or 240V	yellow case
DC input	3V to 32V	white case

Prove it to yourself... ask us for free literature with complete product specifications and prices.

**Grayhill**  
INC

561 Hillgrove Avenue, P.O. Box 10373  
LaGrange, Illinois 60525-0373 USA  
Phone: (312) 354-1040 TLX: 6871375  
TWX: 910-683-1850 FAX: (312) 354-2820

#### AVAILABLE LOCALLY THROUGH THESE REPRESENTATIVES

**AUSTRALIA/NEW GUINEA** Acme Engineering  
Kilsyth, Victoria • Tel: (03) 890-0900  
**BELGIUM/LUXEMBOURG** Rodelco SA/NV Electronics  
Brussels • Tel: 02-2166330  
**CHINA, REPUBLIC OF** Morihan International  
Taipei • Tel: (02) 752-2200  
**DENMARK** E.V. Johanssen Elektronik A-S  
Copenhagen • Tel: (01) 83 90 22  
**FRANCE** Radio Television Francaise  
Gentilly • Tel: (01) 664.11.01

**FINLAND** OY Flinkenberg & Co., AB  
Helsinki • Tel: (90) 647-311  
**GERMANY** Data Modul GmbH  
München • Tel: (089) 56 01 70  
**HONG KONG** Components Agent Ltd.  
Hong Kong • Tel: (0) 4992688  
**INDIA** Hindco Corporation  
Bombay • Tel: (22) 493-1544  
**ISRAEL** Rapac Electronics, Ltd.  
Tel Aviv • Tel: (03) 477115

**ITALY** Microelit s.r.l.  
Milano • Tel: (02) 46 90 444  
Rome • Tel: (06) 890892  
**JAPAN** Jepico Corp.  
Tokyo • Tel: (03) 348-0611  
**NETHERLANDS** Rodelco BV Electronics  
Breda • Tel: (076) 784911  
**NEW ZEALAND** S.D. Mandeno  
Auckland • Tel: (09) 600-008

**NORWAY** Hans H. Schive A/S  
Nesbru • Tel: (02) 84 51 60  
**SINGAPORE, REPUBLIC OF** Microtronics Associates Ltd.  
Singapore • Tel: 7481835  
**SOUTH AFRICA, REPUBLIC OF** Liberty Electronics Ltd.  
Boksburg • Tel: (11) 52-7637  
**SOUTH KOREA** Unistandard Corporation  
Seoul • Tel: (02) 532-6815  
**SPAIN** Unifronics SA  
Madrid • Tel: (01) 242 52 04

**SWEDEN** Bo Palmblad Aktieförsäkrings  
Bromma • Tel: (08) 25 27 20  
**SWITZERLAND** Walter Blum AG  
Zürich • Tel: (01) 312 68 72  
**UNITED KINGDOM** Highland Electronics, Ltd.  
Brighton • Tel: (0273) 69 36 88  
Dunfermline • Tel: (0383) 822911  
Burgess Hill, West Sussex • Tel: (044 46) 45021





**This  
publication is  
available in  
microform.**

University Microfilms International reproduces this publication in microform: microfiche and 16mm or 35mm film. For information about this publication or any of the more than 13,000 titles we offer, complete and mail the coupon to: University Microfilms International, 300 N. Zeeb Road, Ann Arbor, MI 48106. Call us toll-free for an immediate response: 800-521-3044. Or call collect in Michigan, Alaska and Hawaii: 313-761-4700.

**University  
Microfilms  
International**

☐

Please send information about these titles:

Name \_\_\_\_\_

Company/Institution \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_

Zip \_\_\_\_\_

Phone (     ) \_\_\_\_\_



# Feed analog signals to IBM PC-compatible personal computers

---

*A personal-computer-based data-acquisition system converts analog signals from low-level sensors—first, to a level an analog-I/O system can use, and second, to the digital ones and zeros the computer can use. Some guidelines can help you implement hardware and software solutions to the sometimes thorny interface problem.*

---

John Croteau, Doug Grant, and Scott Wurcer,  
*Analog Devices Inc*

By building a custom analog-I/O card for your IBM PC or compatible system, you can save money (as compared with commercially available cards) and realize a system that meets the particular requirements of your analog-input application. When building analog-I/O cards for personal computers, however, you must be aware of environmental influences and design trade-offs. This article reviews those design considerations, offers some simple software-driver routines, and gives examples that demonstrate how various blocks in an analog-I/O system interconnect. The emphasis is on systems needing 12-bit accuracy.

The availability of low-cost, programmable hardware (the personal computer) allows you to build systems that collect, store, communicate, summarize, plot, and analyze data—and you can do all these tasks without incurring major capital expenditures (see **box**, “Should you buy or build?”). Such data might come from an electronic system that measures physical parameters—for example, pressure, temperature, flow, force, and light intensity. Inexpensive software tools are available for many of the mentioned tasks, and specialized tools are easy to develop with the aid of the high-level languages now available.

A transducer's analog electrical output requires some signal conditioning in order to produce an output that's useful to a system. In no case does a transducer deliver either a digital output or a clean, buffered, filtered, precisely scaled, 0 to 10V output that an A/D converter can use. The real world contains many deviations from the laboratory's ideal environment: Temperature fluctuates, noise intrudes, and signal transmission is rarely perfect. Furthermore, transducers used to measure physical phenomena don't offer zero output impedance or convenient output levels. Consequently, there is a need to convert these signals from the original analog format to a *useful* analog format, then finally to a digital format that a personal computer can interpret.

Depending on your specific application, you have several alternatives in system-design philosophy—alternatives that entail tradeoffs in speed, accuracy, and



---

*A custom analog-I/O card for personal computers can save money and at the same time serve a particular application better than would a commercially available board.*

---

cost. For instance, to monitor several slowly varying temperatures by using similar transducers, you might build a system that uses identical fixed-gain stages and a single accurate A/D converter preceded by a multiplexer. On the other hand, a system that needs high versatility (for example, one that monitors several types of signal sources) might require a software-programmable-gain amplifier (SPGA) in order to ac-

commodate a wide range of input levels.

In either case, bear in mind that an analog system is only as good as the components it comprises. The multiplexer, SPGA, sample/hold amplifier, and A/D converter all contribute offset, gain, and linearity errors that degrade system accuracy. Although you can trim your circuits to reduce offset and gain errors, integral and differential nonlinearities and noise ulti-

---

## Should you buy or build?

The possibilities for effecting an interface between analog signals and a personal computer can entail an expense of anywhere from a few tens of dollars to a few tens of thousands, depending on the hardware you choose. At one end of the spectrum are complete analog-I/O systems that connect to the PC through a standard RS-232C interface.

Such systems can perform not only the signal conditioning and analog-to-digital conversion, but also store the data, scale it, and communicate it to the host PC in a form fully converted to engineering units. Many such systems use fairly high-level commands to communicate with the host; these systems have probably the simplest interface requirements.

The disadvantage attached to such systems (besides their high prices) is that they sometimes contain so much intelligence that you must learn a new operating system or command set, which can be quite different from the PC's software. For laboratory-experiment applications, it's unfair to ask a lab technician to become a computer scientist merely to automate a data-gath-

ering task.

One step down the cost ladder are board-level I/O subsystems, which can be attractive alternatives to large systems. Many I/O boards include a powerful subset of the features of the larger systems—for example, effective analog-signal-conditioning and data-conversion functions as well as some intelligence.

Some of these board-level subsystems offer interchangeable modules to adapt the board to various transducer types. These general-purpose board solutions typically represent an investment of a few thousand dollars, and are flexible enough to work with any host PC or minicomputer (because communication usually takes place through an RS-232 or similar port).

### Machine-specific I/O

Another solution to the analog-world/digital-computer interface challenge is to use a machine-specific I/O card. Such boards are available from many vendors (often including the computer manufacturer itself), and include various combinations of analog and digital I/O. These boards represent a good invest-

ment, for several reasons.

First, the cost of a machine-specific board is generally much lower than that of a general-purpose, one-size-fits-all board. Second, the tight coupling of the I/O board to the bus allows fast communication of the digital data to the PC's memory, without the intervention of a slow communications link. Finally, you can control the board's operation in the native operating system or the PC's language; you therefore don't have to learn a new language or operating system.

Because the dedicated I/O board is most often the best choice, you must make the decision whether to buy or build the board. The advantage of buying a board is that no design or construction efforts are necessary. On the other hand, a custom-built board can include exactly the features needed in the application, and you can easily modify the board without concern for voiding a warranty. Such modifications might include upgrades for higher-performance components or additional channels, or an interface to a different transducer type.




mately limit system performance. In addition to using proper layout, bypassing, and grounding practices, you must scrutinize seemingly unimportant specs when you choose signal-conditioning components.

In systems using high values of gain, even small, second-order errors in the signal-conditioning chain become important when the errors enter the system prior to a gain stage. Such error sources are sometimes hard to find. It's useful to analyze each stage in an analog-input system to determine the stage's error contribution. You can then take steps during the design process to minimize the errors in each stage.

The front end, or analog-signal-conditioning part, of a data-acquisition system (DAS) might resemble the configuration shown in Fig 1. The system can accept

signals from several different transducer types; each channel has its own amplifier. This remote-amplifier approach is often more desirable than one in which you send low-level signals around a noisy industrial environment or a noisy computer cabinet. The amplifier-per-channel approach has historically been prohibitively expensive, however, particularly in systems having many channels.

Newer-generation instrumentation amplifiers—for example, the AD524/624/625 family—make it possible to realize a cost-effective implementation of a high-accuracy, amplifier-per-channel data-acquisition front end. The availability of plastic-packaged versions of the amplifiers further enhances cost effectiveness. The AD524 and AD624 both have pin-programmable gain;

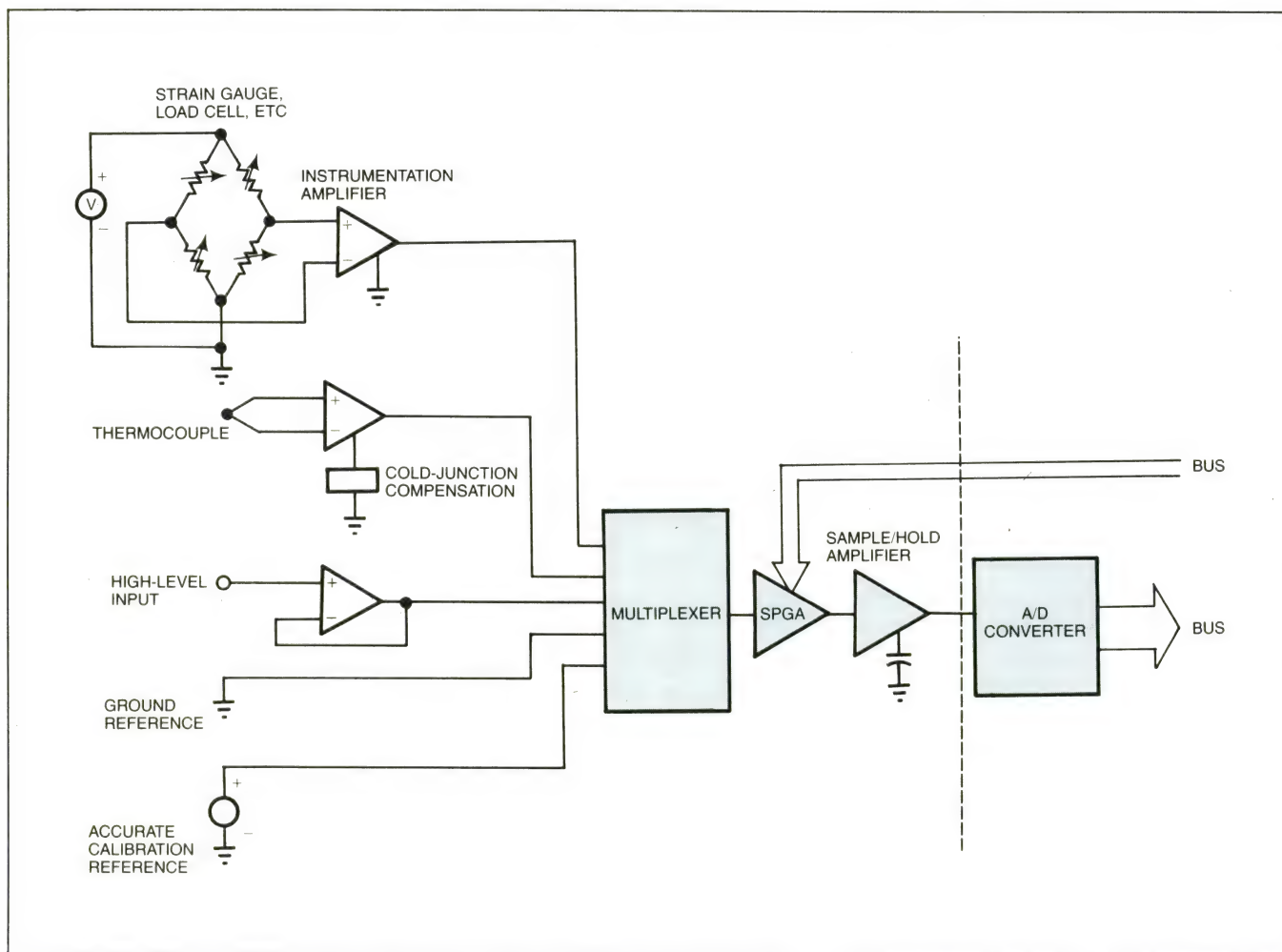

**Fig 1—In this typical data-acquisition system, a multiplexer routes the various analog-input signals to a software-programmable-gain amplifier. The sample/hold amplifier retains the value of a sampled signal while the A/D converter performs the conversion. The software signals to the SPGA adjust the amplifier's gain in accordance with the signal levels of the different input channels.**



you can use them without external components in fixed-gain applications. Instrumentation amplifiers offer several attractive advantages, such as true differential inputs and ground isolation (within the limits of the supplies).


To understand the benefits offered by an instrumentation amplifier in data acquisition, consider Fig 1's interface to the strain-gauge load cell. Strain gauges use a resistive-bridge configuration and are extremely linear and accurate, at the expense of yielding a very low full-scale output voltage (usually 10 to 40 mV). The AD624 is a good choice in this application; it offers pin-programmable gains of 1, 100, 200, 500, and 1000, thereby allowing the amplifier to raise the transducer's signals to several volts full scale.

Mounting the instrumentation amp right next to the transducer results in high rejection of potential noise sources and a low output impedance. If you need gains other than the mentioned fixed values, the AD625 is a better choice. This amplifier offers a 1 to 10,000 gain range that's determined by three external resistors. The amp can therefore accommodate virtually all standard industrial transducers. Resistance temperature devices and thermocouples are examples of other transducers that can benefit from precise signal conditioning at the transducer site.

The family of instrumentation amps employed here allows the use of an external power buffer inside the gain loop, thereby simplifying the task of driving very long cables between the transducer and the system. Such a buffer can prevent loss of bandwidth and preserve the signal's integrity. Without a buffer, most monolithic amplifiers oscillate when driving the large capacitive load of a long shielded cable. Furthermore, without the amp's sense connection, the inaccuracy of an outside-the-loop buffer can degrade signal accuracy. Instrumentation amplifiers having on-chip power-output stages tend to suffer from errors induced by the additional power dissipation.

### Choosing a multiplexer

An input multiplexer can greatly enhance the cost effectiveness of a data-acquisition system by allowing a single A/D converter to serve many input channels. The most precise multiplexers usually use relay switching elements, and the best commercial signal multiplexers use reed relays. High-quality reed relays have a very large (about  $10^{15}$ ) ratio of off- to on-resistance, as well as very low leakage current (about  $10^{-14}$  A) and offset voltage (about 2  $\mu$ V). However, cost, size, speed, and

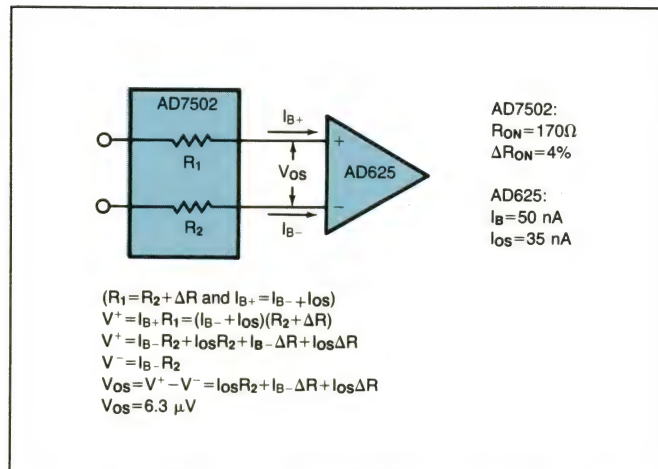

**Fig 2—Multiplexer-induced errors come from two sources:** multiplexer on-resistance, and the instrumentation amplifier's input-bias currents. More accurately, the major sources of error are the disparity between the on-resistances of the multiplexer's different channels and the difference between the amplifier's two bias currents.

power consumption are all problems inherent in the use of relays to multiplex analog signals.

If you can design around their shortcomings, JFET or CMOS multiplexers are preferable. JFET (including BiFET) multiplexers have on-resistances that are higher than those of relays, and the on-resistances are nonlinear with current and voltage. JFET multiplexers also have higher leakage currents than relays, and these currents are very temperature sensitive. MOSFETs have even higher on-resistances, as well as back-gate-to-substrate leakage. This leakage results in high off-current errors.

Another key difference between JFET and MOSFET multiplexers is their behavior in supply-sequencing situations. JFET multiplexers have the annoying (and potentially problematic) characteristic of turning all channels on upon loss of power. Multiple, separately powered signal sources sharing a JFET multiplexer could thus find themselves all shorted together upon the loss of power to the multiplexer. Furthermore, JFET and junction-isolated CMOS devices are prone to latch-up if signal levels exceed the supply voltages. Dielectrically isolated CMOS multiplexers are immune to this latch-up effect.

### Reduce multiplexer errors

To obtain maximum signal-transmission integrity, your system should provide the multiplexer with a low-impedance source and a high-impedance load.



*You must tailor the signal-conditioning function at the front end of your data-acquisition system to suit the requirements of the transducers.*

These conditions prevent leakage errors from exerting a large effect and ensure that leakage currents through the multiplexer are small (resulting in low offset). You shouldn't multiplex very-low-level signals with JFET or MOSFET multiplexers, because any errors in the multiplexer will be large with respect to those signals.

**Fig 2**, for example, shows a configuration in which a differential analog input is multiplexed into a programmable-gain amplifier (PGA). The PGA's offset current (the difference in the bias currents of the two inputs) produces a small offset voltage as the current flows through the multiplexer's on-resistances. A second offset error arises from the difference in on-resistances between the multiplexer's channels and the PGA's bias currents. In a system with a gain of 1000, the 6.3- $\mu$ V input offset, calculated in **Fig 2** for an AD7502 and AD625, would yield a trimmable output offset voltage of 6.3 mV.

You must trim the described offsets—and all others prior to the gain stage—at a point in the circuit *before* the gain stage if you wish to select multiple gain settings using software control. Otherwise, the offsets take on different values with each gain setting and as a consequence prevent your trimming them at a later point.


To make optimum use of the dynamic range of an A/D converter, it's necessary to adjust the front-end gain

for each input. You must adjust the gain so that the full-scale voltage for each input is as close as possible to the full-scale input of the converter. A system that must handle inputs over a very wide dynamic range could use an SPGA to accomplish the gain adjustments. The AD625 SPGA building block, combined with a resistor network and a CMOS switch, forms a versatile SPGA (**Fig 3**). This SPGA could provide just a few bits of dynamic range, or an entire 512-to-1 gain prescaling.

The AD625 exhibits no signal-related change in current in the sense inputs, so the gain network simply becomes a switchable feedback attenuator in which the switch resistance causes only second-order errors. CMOS switches are adequate in this application for 12-bit performance. Gain accuracy and temperature coefficients are primarily functions of the quality of the external resistors. The gain network should therefore comprise resistors that furnish a low temperature coefficient and  $\leq 1\%$  tolerance, or a packaged resistor network.

### Noise and other gremlins

In general terms, noise is anything that interferes with a measurement, whether the interference be random or periodic. It's beyond the scope of this article to do complete justice to the subject of noise, but some major topics are worthy of brief mention.

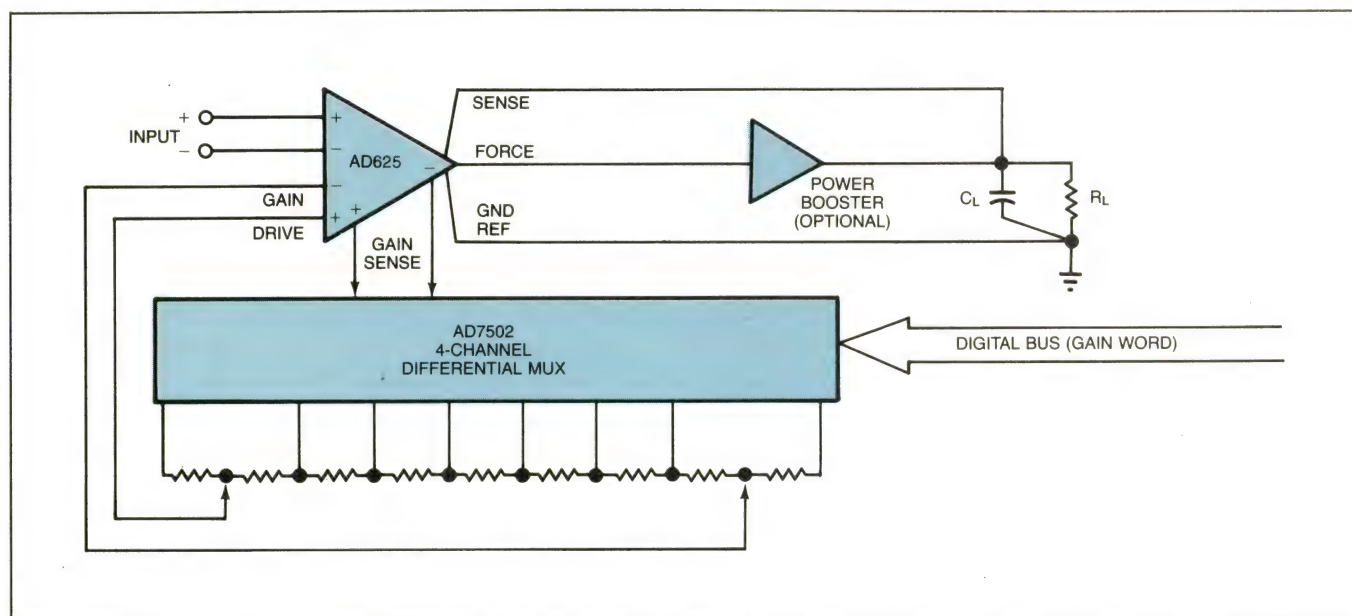

**Fig 3**—You can build your own software-programmable-gain amplifier using readily available IC building blocks. Here, the 4-channel multiplexer selects the gain-setting resistors for the instrumentation amplifier. Note that the optional power booster is inside the gain loop, thereby eliminating errors that could arise from the booster's nonlinearities.




*In designing a front end for an analog-I/O system, you should be aware of the various error sources and how they affect total system accuracy and linearity.*

Thermal, or Johnson, noise is a fundamental limiting factor in the accuracy of many measurements. Take, for instance, the quasistatic case of a mass on a load cell. Even a perfect  $350\Omega$  load cell has  $2.4 \text{ nV}/\sqrt{\text{Hz}}$  of noise that, in a 10-Hz bandwidth, contributes approximately 2.3 ppm p-p of a 20-mV full-scale output.

Bandwidth reduction is one way to reduce the effects of noise. You'd typically use a multipole filter with a low cutoff frequency (say, 3 Hz) to prevent as much as possible of the non-dc information from arriving at the A/D converter. The actual circuit noise eventually assumes a  $1/f$  nature, and additional filtering offers diminishing returns. The AD624 specs  $0.2\text{-}\mu\text{V}$  p-p noise

in a 0.1- to 10-Hz bandwidth. This spec results in a 10-ppm resolution limit for a 20-mV full-scale input.

Proper attention to grounding, shielding, and supply bypassing can result in considerably improved performance before you do any filtering, which only reduces undesired effects after the fact. **Fig 4a** shows some of the interference-type noise existing in a differential-amplifier circuit. Shielded twisted-pair cables offer good noise rejection; the twist prevents the formation of a magnetic loop, and the balanced nature of the line holds electrostatic pickup to the status of a common-mode error. In the schematic in **Fig 4a**, the op amp senses ground remotely. This connection maintains a

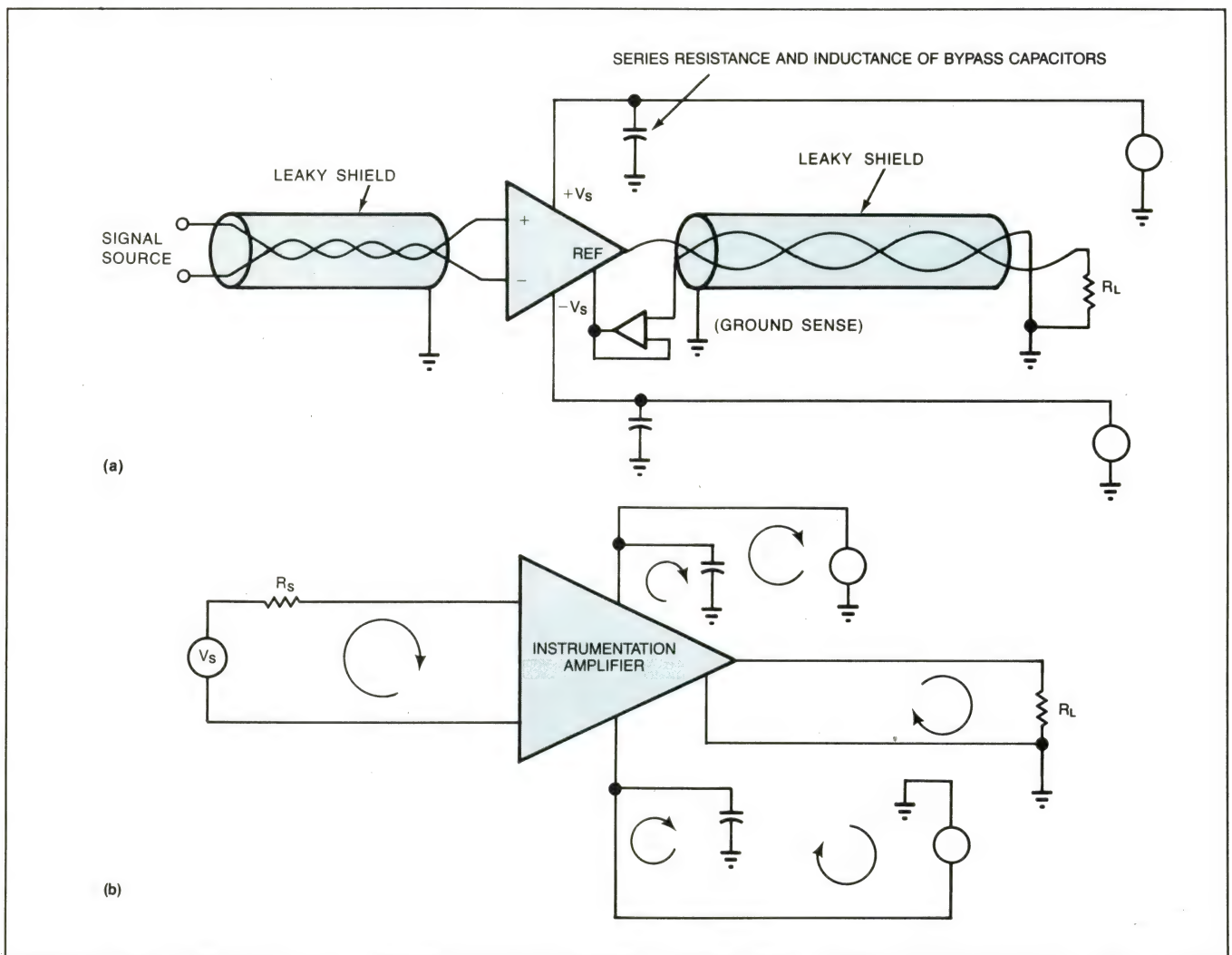

**Fig 4—A high-gain amplifier circuit contains several sources of error. In a, leaky shields and imperfect bypass capacitors produce interference-type noise. The op amp senses ground remotely, resulting in a large difference between input and output grounds. Transformer coupling is the gremlin in b; electromagnetic fields can couple line harmonics and load currents back into the amplifier's inputs.**




considerable difference between the input and output grounds, a difference that causes no error.

Current delivered to a load from the supply lines can cause coupling of a signal back into the circuit through transformer action. Similarly, transformer action can couple any of the loops shown in Fig 4b back into the input loop. Furthermore, power-supply transformers can couple line harmonics as well as signal current back into these sensitive inputs. Most amplifiers exhibit decreasing supply rejection with increasing frequency, making them particularly susceptible to high-frequency electromagnetic coupling. It's good practice to decouple all supplies using capacitors that provide efficient by-

passing to frequencies well beyond the signal-frequency range.

Noise and coupling phenomena are not the only problems that beset data-acquisition systems. Thermal-EMF effects can seriously degrade the dc performance of a data-acquisition system, especially at high gains. Any junction of dissimilar metals generates a potential that varies with temperature. The junction of a gold-plated Kovar IC lead with a copper pc-board run can have as much as  $50 \mu\text{V}/^\circ\text{C}$  of thermocouple voltage. You should, therefore, take care to balance all thermocouples in a dc circuit.

Be sure to keep all sensitive circuitry at equal

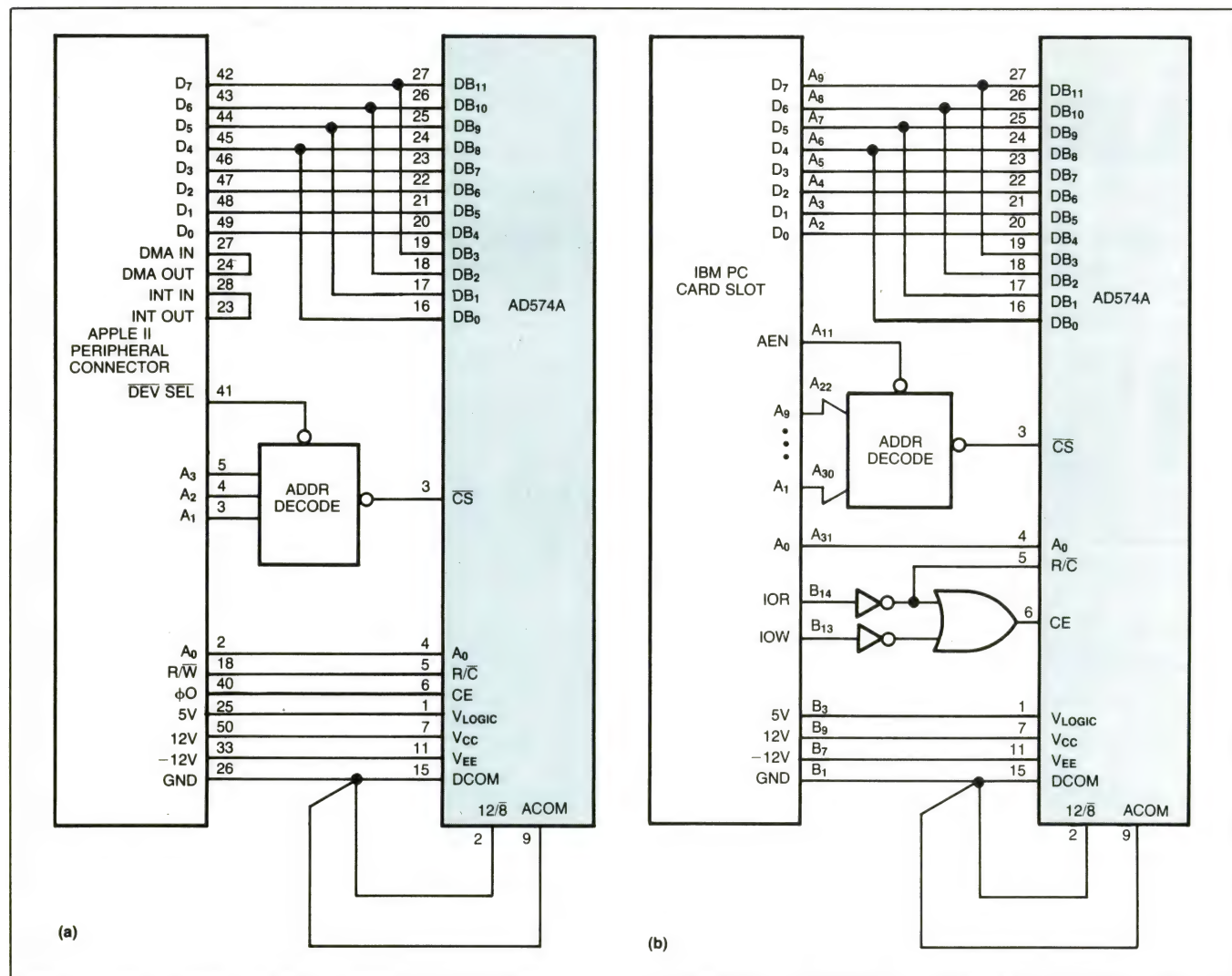

**Fig 5—It's easy to interface an A/D converter to a personal computer.** Here, the 12-bit AD574A interfaces with an Apple (a) and an IBM PC (b). Although the interfacing schemes are similar in several respects, the address-decoding requirements differ.



## An input multiplexer can greatly enhance the cost effectiveness of a data-acquisition system by allowing a single A/D converter to serve many input channels.

temperatures. You must also consider the positioning of heat-generating components and the heat-sinking effects of large pc-board runs. Air currents from fans or from convection will differentially excite even the most carefully balanced junctions, thereby causing spurious low-frequency noise. Because of the mentioned error sources, it's good practice to physically (and therefore thermally) isolate a system's front end.

High-impedance circuitry suffers from its own set of error sources. In this case, charge coupled into high resistances is the major culprit. Vibrating wires and capacitors exhibit microphonic behavior, which is particularly difficult to track down and eliminate. Because the vibration varies the spacing of conductors, thereby varying their capacitance, the voltage observed between the conductors varies. Because much of the vibration in electronic systems comes from cooling fans whose rotation speeds are synchronized with the ac line, you could mistake such microphonic-type errors for electromagnetic pickup. Avoid loose connectors and unsecured signal-carrying leads; tying or gluing down the offending components can make a big difference in performance.

Assuming you've implemented all the preceding error-reduction suggestions, and a properly buffered, filtered, and scaled analog signal is now present in the system, you still must get the signal into the system's A/D converter. The task is more difficult than you might expect. Sample/hold (S/H) amplifiers are often used to avoid dynamic errors in conversion systems. In a multichannel system, an S/H amplifier allows the analog front end to begin settling to the next channel during the time one channel is undergoing conversion. Even in single-channel systems, an S/H amplifier can increase a converter's signal bandwidth, by reducing the converter's effective aperture time.

Because the S/H amplifier acts as an analog storage unit during a conversion cycle, its dynamic output impedance must be low enough to maintain an accurate output in the presence of the dynamic load presented by a successive-approximation A/D converter. An S/H amplifier exhibits a sample-to-hold offset, or pedestal, arising from charge transfer from the switch to the hold capacitor. In some S/H units, the amount of charge varies with the applied signal voltage, resulting in a nonlinearity that can seriously degrade system accuracy.

```

5 DEF SEG = &H1700
10 SCREEN 1: COLOR 9,1: KEY OFF: CLS
20 REM INPUT TRIGGERING AND SCALING INFORMATION
30 PRINT "DIGITAL OSCILLOSCOPE":PRINT
35 PRINT "INPUT RANGE IS +/-5V, WITH 2.44mV RESOLUTION"
36 PRINT "INPUT SINGLE- OR CONTINUOUS-SWEEP (s,c)":E$
37 PRINT "INPUT NORMAL OR AUTOMATIC TRIGGER (n,a)":D$
39 IF D$="a" THEN GOTO 52
40 IF D$="A" THEN GOTO 52
45 PRINT "INPUT TRIGGER ON POS OR NEG SLOPE (p,n)":A$
46 PN$=1
48 IF A$="n" THEN PN$=0
49 IF A$="N" THEN PN$=0
50 GOTO 55
52 PN$=2
55 PRINT "INPUT SCREEN'S CENTER VALUE (+/-V)":CTR
70 PRINT "INPUT OFFSET TRIGGER PT FROM CTR SCREEN (y,n)":A$
80 IF A$="y" THEN GOTO 100
85 IF A$="Y" THEN GOTO 100
90 OFFSET=0: GOTO 110
100 PRINT "INPUT OFFSET BY HOW MUCH (+/-mV)":OFFSET
110 IF (CTR+OFFSET/999.99) > 4.998 THEN GOTO 135
120 TRVAL$=INT(409.6*CTR+OFFSET/2.4414+.5)*16
130 GOTO 140
135 TRVAL$=32752
140 PRINT "INPUT HOW MANY mV/div":DIV:PRINT
150 RNG=INT(3.2768*DIV+.5)
170 INPUT "HOW MANY ms/div (2.1ms MINIMUM)":MS:PRINT
175 IF MS < 2.1 THEN MS=2.1
180 DLY$=INT(MS/.15016-.7.4914)
190 BX$=TRVAL$-1
200 IF PN$=1 THEN BX$=TRVAL$+1
201 REM SPECIFY SCALES AND DRAW GRATICULES
203 CLS: LOCATE 2,4:PRINT DIV;"mV"
205 LOCATE 2,30:PRINT MS;"ms"
210 FOR J=25 TO 175 STEP 25
220 FOR I=1 TO 320
230 PSET (I,J),1
240 NEXT I: NEXT J
270 FOR I=40 TO 280 STEP 40
280 FOR J=1 TO 200
290 PSET (I,J),1
300 NEXT J: NEXT I
305 Q=200/RNG
306 FX=INT(409.6*CTR-RNG/2+2048.5)
310 IX=400: JX=1050
315 REM EXCHANGE MEMORY RANGES AND CALL SUBROUTINE
320 LX=IX: IX=JX: JX=LX
340 P=0
350 CALL P(BX$,IX,TRVAL$,PN$,DLY$)
355 REM SCAN SCREEN ERASING OLD AND DRAWING NEW WAVEFORM
360 FOR X=0 TO 560 STEP 80
370 FOR Y=2 TO 78 STEP 2
380 W=200-INT(Q*(PEEK(JX+X+Y)/16+PEEK(JX+X+Y+1)*16-FX)+.5)
390 IF INT(W/25)=W/25 THEN GOTO 410
400 PRESET ((X+Y)/2,W)
410 W=200-INT(Q*(PEEK(IX+X+Y)/16+PEEK(IX+X+Y+1)*16-FX)+.5)
420 IF INT(W/25)=W/25 THEN GOTO 440
430 PSET ((X+Y)/2,W),2
440 NEXT Y: NEXT X
442 REM CONTINUE IF CONTINUOUS SCAN, OTHERWISE PROMPT FOR RE-SCAN
444 IF E$="S" THEN GOTO 460
446 IF E$="s" THEN GOTO 460
450 GOTO 320
460 LOCATE 22,1
465 INPUT "AGAIN (y,n)":T$
470 IF T$="N" THEN END
480 IF T$="n" THEN END
490 LOCATE 22,1:PRINT "-----"
500 GOTO 320

```

**Fig 6—High-level languages are useful in data acquisition.** This Basic routine turns an IBM PC into a digital oscilloscope. The program allows you to enter trigger data and time and voltage scales. It also draws the screen's graticules and displays the scales. The program works with the PC's assembly language, via CALL statements. The oscilloscope system needs only a sample/hold amplifier and an A/D converter as hardware.



cy, especially if the S/H amplifier resides at a point prior to a gain stage.

The pedestal effect is prevalent in high-throughput systems that require small hold capacitors for quick signal acquisition and settling. High throughput also requires short sampling periods and long hold times, a combination that can produce a memory effect because of dielectric absorption in the hold capacitor. An untrimmable error results from charge left on the capacitor from the previous hold period. Teflon, polystyrene, and MOS capacitors offer the best performance; their dielectric-absorption coefficients are on the order of 0.02% or less.

### The A/D converter at last

With the buffering, filtering, scaling, sampling, and holding accomplished, the remaining task is to select an A/D converter that has the speed, resolution, and accuracy suitable for your application. For the examples discussed here, the chosen converter is the AD574A. This 12-bit A/D converter offers a 25- $\mu$ sec conversion time and 12-bit linearity, and it comes with a guarantee of no missing codes over its full operating-temperature range.

Essentially an analog-input port, the A/D converter resides in the PC's address space just as any other I/O port would. It can accept either memory-mapped or isolated-I/O modes of access, and it can lie in one or more locations, depending on the number of cycles needed to read its digital output. Signals generated from the decoded address (or addresses), the read/write line (lines), and assorted control signals supply the converter's control inputs. The control inputs signal the converter when to begin a conversion and when to put its output on the data bus.

Once the A/D converter completes the conversion cycle, it must communicate its digital output to the PC. Many converters offer onboard, 3-state output buffers, which allow the units to interface directly with the PC's data bus. The output format and logic depend on the converter's resolution relative to the width of the data bus. If the bus is wider than the data word, a single cycle can read the input "broadside" (ie, all bits at once), but if the word is wider than the data bus, multiple cycles must read the word in portions.

The data format becomes a concern if the output word's length is larger than, but not an exact multiple of, the width of the data bus. For instance, when the AD574A interfaces with an 8-bit system, as in **Figs 5a** and **5b**, the system must read the 12-bit output as one

```

PUSH BP           ; SAVE BP
MOV DX, 0309      ; SET ADC ADDRESS
MOV BP, SP        ; SET BASE PARM LIST
MOV S1, [BP] + 14 ; GET ADDR OF BX%
MOV BX, [S1]      ; GET VALUE OF BX%
MOV S1, [BP] + 12 ; GET ADDR OF 1%
MOV D1, [S1]      ; GET VALUE OF 1%
JMP START        ; JUMP TO BEGIN
NOTRIG MOV BX, AX  ; SAVE AS LAST CONVERSION
START OUT DX, AL   ; START CONVERSION CYCLE
WAIT MOV CX, 7     ; SET UP DELAY
      LOOP WAIT    ; LOOP TO WAIT FOR ADC
      MOV S1, [BP] + 10 ; GET ADDR OF TRVAL%
      MOV CX, [S1]    ; GET VALUE OF TRVAL%
      MOV S1, [BP] + 8 ; GET ADDR OF PN%
      DEC DX
      IN AX, DX      ; RETRIEVE CONV RESULT
      INC DX
      XOR AX, 8000   ; CHANGE TO 2's COMP
      CMP [S1], 2    ; AUTO OR NORMAL TRIGGER?
      JE TRIG        ; IF AUTO, TRIGGER
      CMP [S1], 1    ; POS OR NEG TRIGGER?
      JNE NEGTR      ; JUMP IF NEG, ELSE POS
      CMP BX, CX     ; LAST CONV > TRVAL%?
      JG NOTRIG      ; IF NOT, TRY AGAIN
      CMP AX, CX     ; THIS CONV < TRVAL%?
      JL NOTRIG      ; IF NOT, TRY AGAIN
      JMP TRIG       ; ELSE, TRIGGER
NEGTR CMP BX, CX    ; LAST CONV < TRVAL%?
      JL NOTRIG      ; IF NOT, TRY AGAIN
      CMP AX, CX     ; THIS CONV > TRVAL%?
      JG NOTRIG      ; IF NOT, TRY AGAIN
TRIG MOV BX, 0      ; INITIALIZE MEMORY FLAG
NXTPT XOR AX, 8000  ; CHANGE TO BINARY
      OUT DX, AL     ; START CONVERSION CYCLE
      MOV S1, [BP] + 6 ; GET ADDR OF DLY%
      MOV CX, [S1]    ; GET VALUE OF DLY%
      DLY LOOP DLY   ; LOOP TO DELAY FOR ADC
      MOV [D1], AX    ; STORE LAST CONV RESULT
      INC D1          ; INCREMENT TO NEXT
      INC D1          ; STORAGE ADDRESS
      INC BX          ; INCREMENT MEMORY FLAG
      DEC DX
      IN AX, DX      ; RETRIEVE CONV RESULT
      INC DX
      CMP BX, 0140   ; 320 POINTS YET?
      JNE NXTPT     ; IF NOT, INPUT NEXT PT
      POP BP         ; RESTORE BP
      RET 10         ; FAR RETURN TO BASIC

```

**Fig 7**—This IBM-PC-based assembly-language subroutine works in conjunction with **Fig 6**'s Basic program. The subroutine accepts five arguments, which control triggering and timing data.

8-bit byte and one 4-bit nibble. One read cycle obtains the eight MSBs, and a subsequent cycle obtains the four LSBs (with four trailing zeros for the unused bits). Data in such a form is said to be left justified. Alternatively, if the eight LSBs are in one byte and the four MSBs are in another, the data is right justified.

### Rely on general-purpose converters

General-purpose converters usually offer flexible interfaces and various pin- and software-programmable options. For example, the AD574A has a software-



*Proper attention to grounding, shielding, and supply bypassing can improve system performance considerably.*

programmable output-word length (eight or 12 bits) and a pin-selectable output format (**Table 1**). If you apply a one and a zero to CE and CS, respectively, and a zero to R/C, a 12- or 8-bit conversion results, depending on the status of A<sub>0</sub>. Holding R/C high, however, enables the 3-state outputs.


During the read cycle, 12/8 defines which bits are enabled; if this line is high, all 12 bits are read broad-side. If 12/8 is low, only the eight MSBs or the four LSBs are enabled, depending on the status of A<sub>0</sub>. Timing diagrams in the AD574A's data sheet define all control inputs and outline certain setup, hold, and bus-access times. You must take into account the PC's bus-timing and propagation delays when you specify control signals and decoding/logic schemes.

The interfaces in **Figs 5a** and **5b** satisfy all timing requirements for the AD574A and the two indicated

personal computers. In **Fig 5a**, the Apple's Device Select control signal acts as an upper-address decode for the particular card slot and limits the number of I/O addresses per slot to 16. If none of the other 16 possible addresses are used in that slot, you can connect the Device Select pin directly to the AD574A's CS input.

You can treat the AD574A either in memory-mapped mode or as isolated I/O for the IBM PC. In **Fig 5b**, the computer uses its IOR and IOW lines to treat the converter as isolated I/O. Isolated-I/O address decoding and troubleshooting are easy with the IBM PC, because the computer uses only the lower 10 address lines (A<sub>9</sub> to A<sub>0</sub>). However, you need AEN to mask out DMA cycles that use the same address space.

You can use any language to execute the read and write cycles that control the A/D converter. In Basic, you use PEEK and POKE commands if the device is

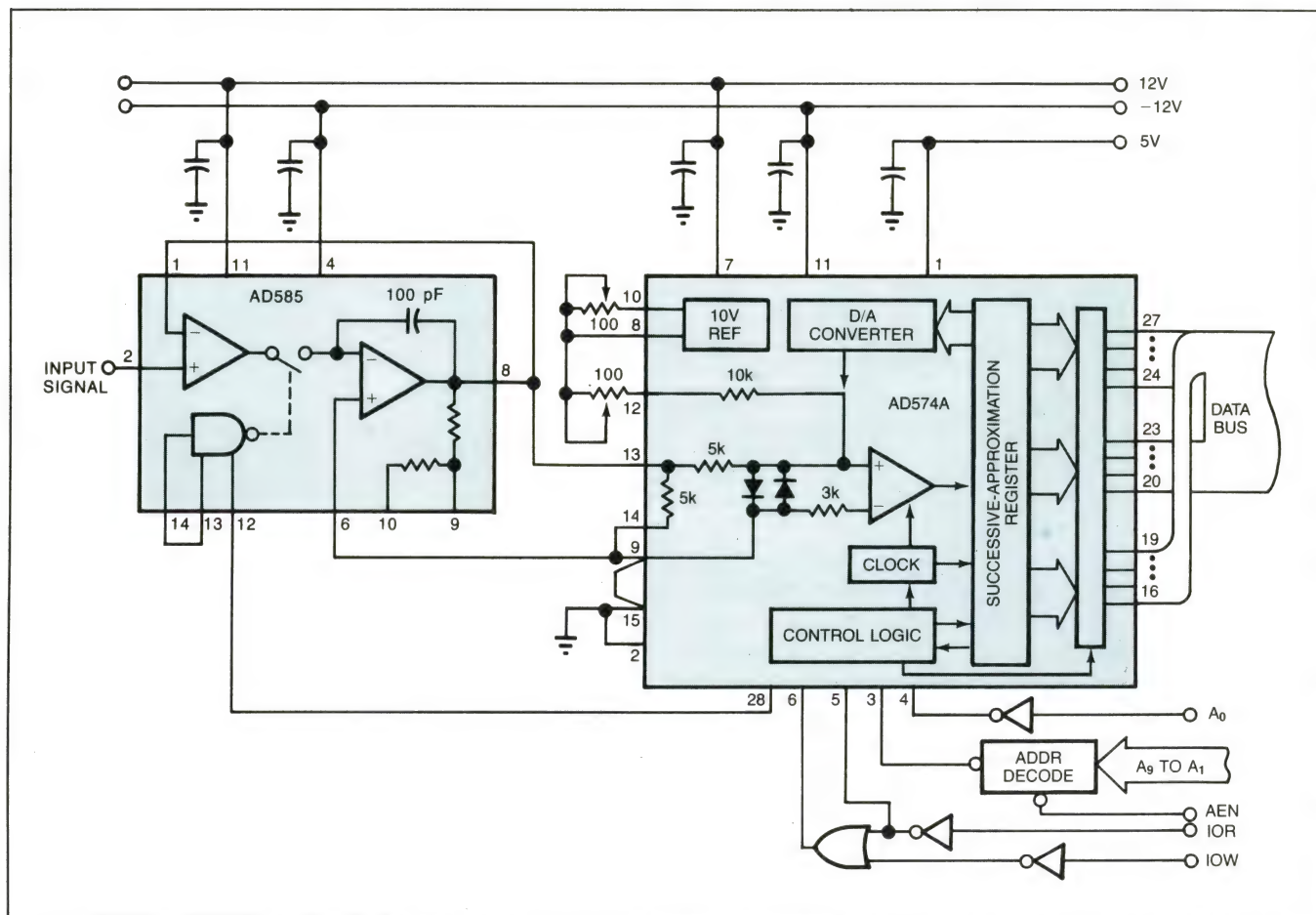

**Fig 8—You increase the effective signal bandwidth of an A/D converter by using a sample/hold amplifier to freeze signals during conversions. In this configuration, the AD585 S/H device drives an AD574A. Note that few external components are required; the two potentiometers shown adjust offset and gain errors in the A/D converter.**



# How to computerize your measurements without compromising results.

Now there's a faster, more repeatable and more productive way to make waveform measurements—and not surprisingly, it comes from Tektronix. Tek's library of waveform acquisition and processing software combines the best of computer-aided measurement with the high interactivity and accuracy you enjoy in Tek scopes.


Whatever your application, whatever your front-end processor—IBM PC, H-P Series 200 or Tek's own 4041 controller—Tek software

can help you store and retrieve data, process, analyze, display and document results.

Powerful, flexible operation is common to all Tek packages: we accommodate your way of working; you don't have to conform to ours.

**For more information contact the nearest Tektronix Office.**  
Tektronix, Inc.  
P.O. Box 1700  
Beaverton, OR 97075

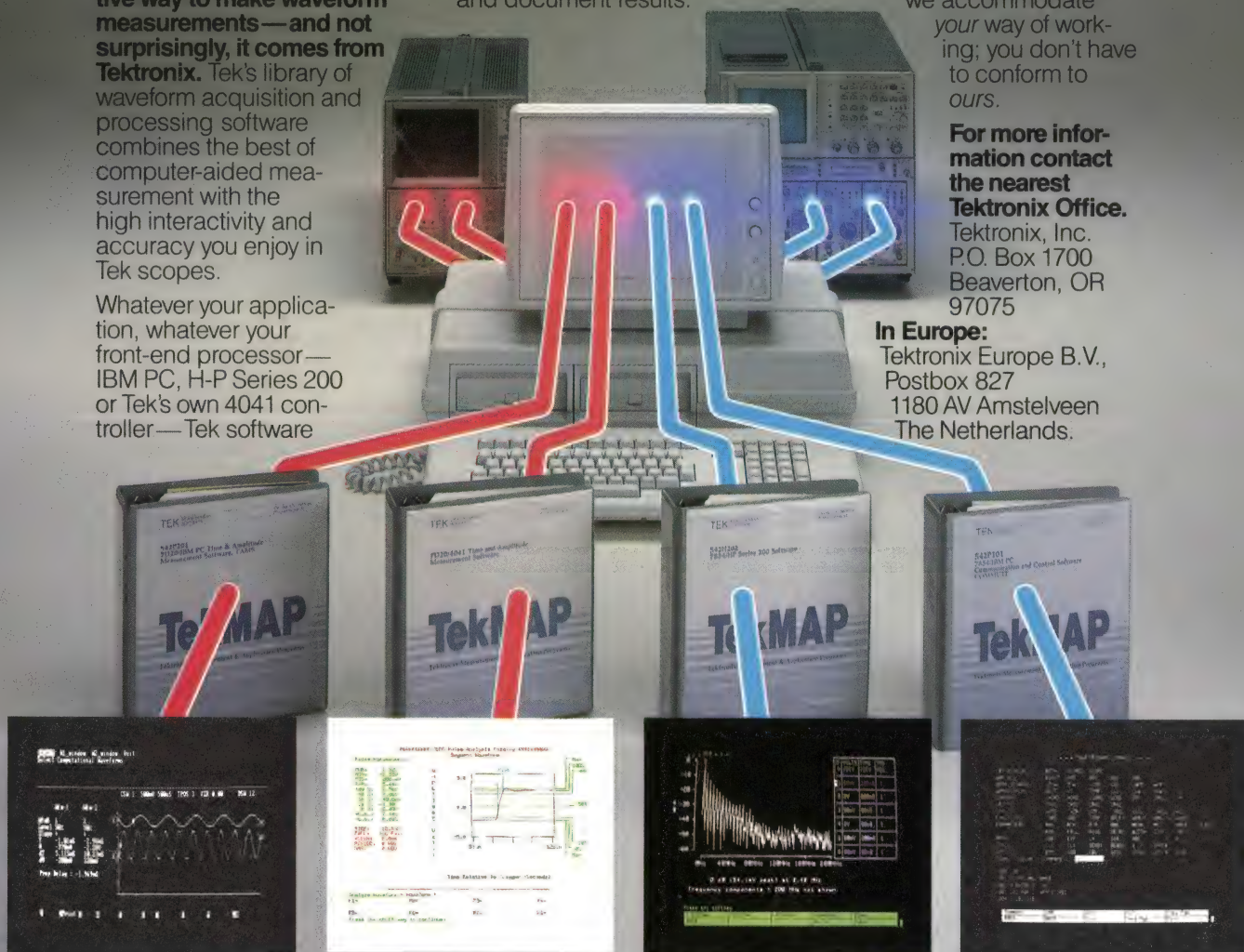**In Europe:**  
Tektronix Europe B.V.,  
Postbox 827  
1180 AV Amstelveen  
The Netherlands.



**Delay time measurement** using an IBM PC/XT/AT as controller with Tek's Time and Amplitude Measurement Software. Instruments: the Tek 7D20 Programmable Digitizer and Tek 7603 oscilloscope.

**Automated pulse parameter analysis** using a Tek 4041 Controller and Tek Time and Amplitude Measurement Software to direct the efforts of the 7D20 in a 7603 mainframe. Hard copy generated by a Tek 4695 Color Copier.

**Computing and displaying frequency domain data (FFT)**, using an HP Series 200 Technical Computer as controller. Tek software for these results accommodates the HP Series 200 with the Tek 7D20 or the Tek 7854 Waveform Processing Oscilloscope.

**Editing a Tek 7854 RPN program**, including comments, for downloading to the 7854 or archiving to disk. Performed with the HP 200 Series Technical Computer, the Tek 7854, and Tek 7854/HP Series 200 Software. Similar facility available in COMMUTE.

**Tektronix®**  
COMMITTED TO EXCELLENCE

CIRCLE NO 197



To communicate the results of A/D conversions to a personal computer, you can use both high-level- and assembly-language programs.

TABLE 1—AD574A TRUTH TABLE

CE	$\overline{CS}$	R/ $\overline{C}$	12/ $\overline{B}$	A <sub>0</sub>	OPERATION
0	X	X	X	X	NONE
X	1	X	X	X	NONE
1	0	0	X	0	INITIATE 12-BIT CONVERSION
1	0	0	X	1	INITIATE 8-BIT CONVERSION
1	0	1	5V	X	ENABLE 12-BIT PARALLEL OUTPUT
1	0	1	GND	0	ENABLE 8 MOST SIGNIFICANT BITS
1	0	1	GND	1	ENABLE 4 LSBs + 4 TRAILING ZEROS

memory mapped, while INP and OUT statements apply if the converter is operating as isolated I/O. In addition, most PCs offer the capability to call machine-language subroutines from Basic. The fast execution times of assembly-language commands offer the designer higher throughput per channel and a faster number-crunching capability.

By integrating assembly-language routines into high-level programs, you can take advantage of both the speed of the assembly language and the programming ease of the high-level languages. For example, the program in Fig 6, written in Basic for the IBM PC, uses the PC's graphics capability to configure a digital oscilloscope, using the medium-resolution mode on a color monitor. The first portion of the program, written in Basic, prompts the user to enter the trigger data and the time and voltage scales. It then draws the gratitudes on the screen and displays the scales.

The program then calls the Fig 7 assembly-language subroutine with five arguments that supply the triggering and timing data. The subroutine returns with 320 data points stored in one of two memory ranges. The other range contains the previous scan's points. The final portion of the program scans the screen while scaling both sets of data points, erasing the previous waveform and displaying the new waveform. In the single-scan mode, you can request additional scans after each sweep. In the continuous-scan mode, however, the program proceeds to trigger, acquire, erase, and display until you enter Control-Break.

### Scope hardware requirements are minimal

The only hardware requirements for the digital oscilloscope are an AD574A and an AD585, connected as shown in Fig 8. The configuration accepts a  $\pm 5V$  input (perhaps from a transducer-input front end as described earlier). Because the IBM PC's 8088  $\mu P$  reads a 2-byte word whose most significant byte is at the lower address, the IN command in the subroutine requires

the inversion of address line A<sub>0</sub> in the interface shown in Fig 5a. In contrast, an INP statement in Basic is an 8-bit operation, so you can eliminate the need for the inverter by accessing the converter with the MSB at the higher address.

The CALL statement in Fig 6's line 350 transfers control to the subroutine found in segment &H1700, as defined in the previous DEF SEG statement. The arguments BX%, TRVAL%, and PN%, passed to the Fig 7 subroutine, communicate the triggering information, while I% indicates which of the two ranges of memory to use. The final argument, DLY%, controls a variable delay between conversions, thereby setting the time scale. The subroutine continuously samples the input until the triggering conditions are met, and it then proceeds to the bottom portion of the program, which enters 319 more points and stores all 320 in memory. Throughout the subroutine, the stack stores the branch pointer (BP), and the intersegment return at the end transfers control back to the Basic program.

### Calibrating the system

All dynamic and static errors introduced by the system's individual components combine to define the system's accuracy. Most often, you can trim the offset and gain errors at each component. However, if the square root of the sum of the squares of the offset and gain errors is small enough, you can effect the entire system's calibration at the A/D converter. You can use either a hardware- or software-based trimming approach to eliminate errors.

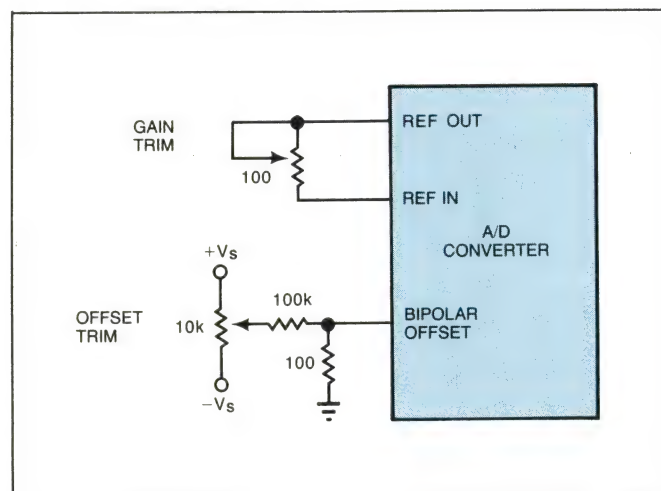


Fig 9—Trimming an A/D converter's offset and gain is easy, but beware: Trimming potentiometers might not offer enough resolution to make up for errors arising in other parts of the system.



# At last, comprehensive software that solves symbolic mathematical computations.

## In seconds.

If it is still taking you weeks or months to handle rudimentary algebraic problems and extremely complex analyses, then make it your business to find out about MACSYMA™.

MACSYMA is the most comprehensive approach to symbolic mathematics ever created. Originally designed at MIT through research in Artificial Intelligence, MACSYMA has been continuously developed and enhanced since 1969.

But for all its sophistication, you can put MACSYMA to work on computers ranging from workstations to mainframes. Without previous programming experience. In fact, you can interact with it in an almost conversational way while you use it to explore problems in basic or advanced mathematics that you couldn't begin to approach using a pencil, chalk or numerical software. This comprehensive program can then generate FORTRAN code from derived MACSYMA expressions and answers.

### 3 weeks vs. 10 seconds.

For example, an engineer working for a major aerospace company was stopped by an integral dealing with turbulence and boundary layers. Pencil and paper in hand, he had been looking at:

$$\int (k \log(x) - 2x^3 + 3x^2 + b)^4 dx$$

for more than three weeks. He always arrived at a different solution, never knowing which was the right one.

Less than 10 seconds after entering the problem into the computer, MACSYMA gave him the correct answer. Not just numerically, but in symbolic terms that gave him real insight into the physical nature of the problem.

How long would it take you or your staff to factor this expression?

$$3w^2z^6 + 2w^3z^4 - 10w^2y^2z^3 + 141xyz^3 + 45w^2x^3z^3 - 3w^2z^3 + 94wxyz - 2w^3z - 470xy^3 + 10w^2y^2 + 2115x^4y - 45w^2x^3$$

MACSYMA gives you the answer. In seconds.

$$(3z^3 + 2wz - 10y^2 + 45x^3)(w^2z^3 + 47xy - w^2)$$

### What MACSYMA can do. For you.

MACSYMA arms you with hundreds of practical and real-world applications. It can:

- Do algebra, trigonometry and calculus
- Provide standard numerical techniques
- Generate FORTRAN output from MACSYMA expressions
- Simplify, factor or expand expressions
- Solve equations analytically or numerically
- Expand functions in Taylor or Laurent series
- Compute Laplace transforms
- Manipulate matrices and tensors
- Plot functions in 2 or 3 dimensions
- Much, much more

Throughout the world, thousands of scientists, engineers and mathematicians are using MACSYMA in such diversified applications as electronics, structural engineering, CAD, acoustics, plasma physics, antenna theory, VLSI circuit design, control theory, numerical analysis, fluid mechanics, genetic studies, ship hull design, maximum likelihood estimation, ballistic missile defense systems design, underwater shock wave analysis, helicopter blade

motion studies, and atomic scattering cross section analysis. And the range of use is expanding every day.

### Easy computer algebra starts here.

MACSYMA is available right now from Symbolics™, the leader in Symbolic processing. For a complete kit including a full capabilities brochure, just clip and mail the coupon or call (617) 577-7600.

**MACSYMA™**  
The most comprehensive software approach to symbolic mathematical computations.

*symbolics™*  
Your next step in computing.™

MACSYMA and SYMBOLICS are trademarks of Symbolics, Inc. Copyright 1986 Symbolics, Inc.

Symbolics, Inc. Dept. M-ED1  
11 Cambridge Center  
Cambridge, MA 02142

Name

Title

Company

Address

City  State  Zip

Telephone  Extension

MACSYMA is available to colleges and universities at special rates. EDN041786



*General-purpose A/D converters usually offer flexible interfaces and various pin- and software-programmable options.*


Most often, you trim offset by injecting or draining a small amount of current into or from the A/D converter's input at the high-impedance summing node. Because an A/D converter produces an output that's proportional to the analog input relative to a full-scale (reference) voltage, you can trim gain errors by either varying the reference voltage or adjusting the gain of a preceding stage. Calibration then requires the application of two known analog voltages. The first voltage, near zero, trims the offset. You apply this voltage to the converter's input and trim the offset-trim current until the converter's output matches the desired code. You then apply the second known voltage, near full scale, and adjust the gain until the output matches the correct, near-full-scale code.

## Hardware vs software trims

Hardware-based trimming schemes (**Fig 9**) have traditionally used potentiometers for the offset and gain adjustments. However, a trimming potentiometer

might not offer sufficient resolution to trim several components' offset and gain errors at a single point in the system, because in single-point trimming the trim range can become quite large. For instance, a  $\pm 20\%$  offset-trim range in a 12-bit system would span 819 LSBs. A 10-turn potentiometer would trim 82 LSBs per turn, and thus offer  $4.4^\circ/\text{LSB}$  resolution. Such fine resolution requires precise calibration and risks both mechanical instability and the temptation on the part of untrained personnel to inadvertently recalibrate the system.

Instead of using hardware to calibrate the system, you can correct gain and offset errors entirely in software. To do so, you might need to offset (and possibly expand) the A/D converter's input range to accommodate a signal that has worst-case offset and gain errors. Begin the trimming algorithm by performing a conversion of a known analog voltage near zero scale. Because gain errors in the lower portion of the transfer function are negligible, the measured input's

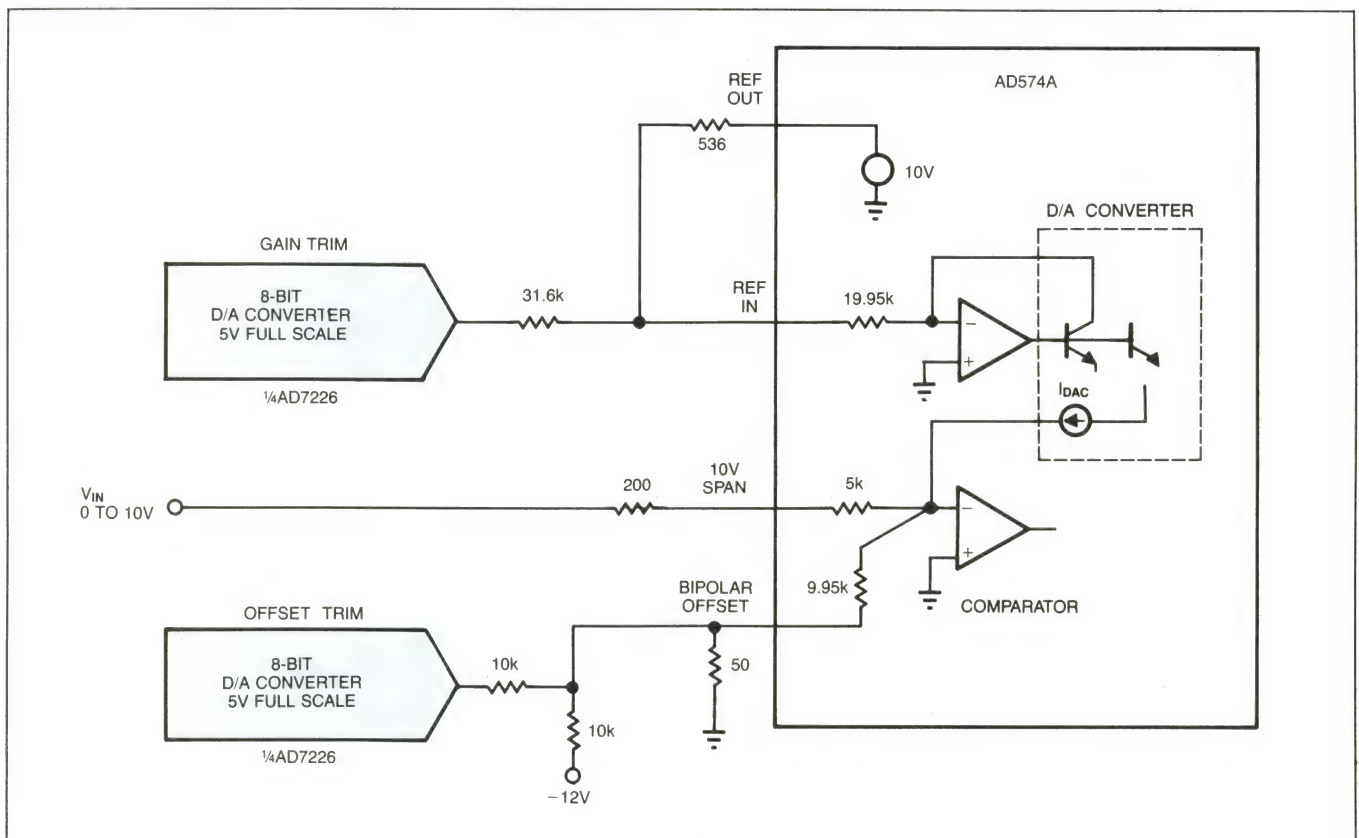


**Fig 10—A software-controlled hardware trimming scheme** uses D/A converters to trim the A/D converter's offset and gain errors. Depending on the software, you could use such a scheme to perform periodic calibration in a data-acquisition system. The attenuators at the outputs of the D/A converters control the resolution of the trim.


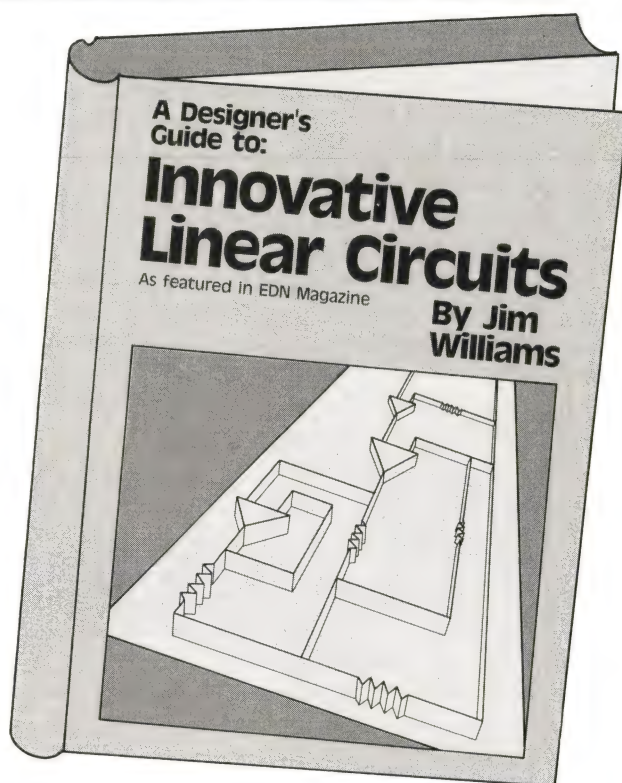
# ANALOG IS ALIVE AND WELL IN: A Designer's Guide to Innovative Linear Circuits

As exciting as digital technology is, you still need analog circuitry to operate on signals from real-world sources. Now, EDN is offering a wealth of analog design information in *A Designer's Guide to Innovative Linear Circuits*.

This 186-page collection of articles was developed by Jim Williams, one of America's foremost linear-circuit designers. It includes practical and efficient ways to use op amps, comparators, data converters, and other analog ICs, and discusses the theories behind all the design techniques presented.



Mail coupon to:

Linear Circuits Reprints  
EDN Magazine  
Cahners Building  
275 Washington Street  
Newton, MA 02158-1630

Please send \_\_\_\_ copies of **A Designer's Guide to Innovative Linear Circuits**

☐ \$14.95 UPS   ☐ \$17.95 non USA

Check or money order made out to  
EDN REPRINTS must accompany  
each order. No COD. Mass. residents  
add 5% sales tax.

**Please print clearly. This is your  
mailing label.**

NAME \_\_\_\_\_

TITLE \_\_\_\_\_

COMPANY \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_



---

*You can trim offset-voltage and gain errors by using either a hardware or software approach; in many systems a combined software-controlled hardware method is best.*

---

deviation from its desired value is stored as the system's offset. Next, the algorithm performs a conversion of a known, near-full-scale analog voltage. This time, the software calculates a gain-correction factor, defined as the input's desired value divided by the converted, measured value less the previously measured offset. The routine trims the digital result from each subsequent conversion by first subtracting the offset and then multiplying by the gain-correction factor.

Clearly, performing these calculations as each conversion's result is retrieved reduces system throughput and limits the system's maximum input frequency. To avoid this loss of speed, you can use a trimming subroutine or a signal-processing algorithm to trim a batch of samples in memory at a later time. Also, if the sampling routine is written in assembly language, the processor can perform the trimming calculations while awaiting the next conversion's completion.

In a system using such software-trimming schemes, the offset and gain errors limit the converter's dynamic range and as a consequence effectively limit its resolution. Assume, for instance, a 0 to 5V signal whose worst-case offset and gain errors (in stages prior to the converter) are  $\pm 30\%$ . In the worst case, the input signal can range from a minimum of  $-1.5\text{V}$  to a maximum of  $8\text{V}$ . The A/D converter would need to use a  $10\text{V}$  range, offset by  $-1.5\text{V}$ , to avoid code saturation under worst-case conditions. If the system's gain error is  $-30\%$ , the 0 to  $5\text{V}$  signal would then use only  $3.5\text{V}$  of the converter's  $10\text{V}$  range. So, under worst-case conditions, only 1434 (35%) of the converter's 4096 codes would span the input range; the converter would therefore offer only 10.5 bits of resolution.

### Hybrid trimming schemes become popular

D/A converters used in hybrid combinations of software and hardware trimming have recently become popular for software-controlled calibration (**Fig 10**). Depending on the trimming range required, an attenuator at the output of a D/A converter of minimal resolution can provide trim resolution of a fraction of the A/D converter's code width. Some sort of iterative comparison algorithm in software can thereby calibrate the A/D converter.

For example, a staircase algorithm might begin by setting the offset-trim D/A converter to half scale (with a near-zero signal applied to the A/D converter) and continue by performing an A/D conversion. Depending on the measured output's digital value relative to the desired value, the algorithm would then increment or

decrement the code of the offset-trim D/A converter and repeat the previous steps. This process would continue until the A/D converter's output matches the desired code. The next step is to apply a known, near-full-scale voltage to the A/D converter's input; the algorithm would then manipulate the gain-trim D/A converter to trim the gain error.

The beauty of software-trim D/A-converter schemes becomes evident when you consider the software-controlled application of the two known trimming voltages. If you apply the voltages through two dedicated multiplexer channels, you could use software routines for periodic system calibration. The accuracy of the two known voltages is therefore the only factor limiting the system's offset and gain accuracy over time and temperature.

**EDN**


---
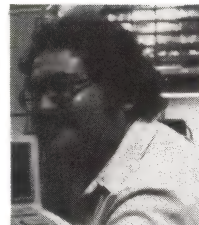
### Authors' biographies

*John Croteau, a product-marketing specialist at Analog Devices Semiconductor (Wilmington, MA), is engaged in product development for the company's bipolar and BiMOS D/A converters. John holds a BS in engineering science from Penn State University; he's now pursuing an MBA at Boston University. He's an IEEE member.*



*Doug Grant is new-product marketing manager at Analog Devices Semiconductor, where he's involved in product planning for data converters. Nine years at his present company, he previously worked at Hybrid Systems and Adams-Smith. He's a BSEE graduate from the University of Lowell and an IEEE member. His hobbies are amateur radio and collecting antique radio and electronics books.*



*Scott Wurcer, a senior design engineer at Analog Devices Semiconductor, has engaged in IC design at the company for the 11 years since he obtained a BSEE degree from Massachusetts Institute of Technology. Scott is an IEEE member.*



---

Article Interest Quotient (Circle One)  
High 473 Medium 474 Low 475



# How to beat the high cost of cheap meters.



You get what you pay for.  
**So get the Fluke 70 Series.**

You'll get more meter for your money, whether you choose the affordable 73, the feature-packed 75 or the deluxe 77.

All of them will give you years of performance, long after cheaper meters have pegged their fishhook needles for the last time.

That's because they're built to last, inside and out. So they're tough to break. They don't blow fuses all the time. You don't even have to replace batteries as often.

And they're backed by a 3-year warranty. Not the usual 1-year.

Of course, you may only care that the world-champion 70 Series combines digital and analog displays with more automatic features, greater accuracy and easier operation than any other meters in their class.

You may not care that they have a lower overall cost of ownership than all the other "bargain" meters out there.

But just in case, now you know.

For a free brochure or your nearest distributor, call toll-free **1-800-227-3800**, ext. 229.

FROM THE WORLD LEADER  
IN DIGITAL MULTIMETERS.



**FLUKE 73**

\$79\*  
Analog/digital display  
Volts, ohms, 10A, diode test  
Audible continuity  
0.7% basic dc accuracy  
2000+ hour battery life  
3-year warranty



**FLUKE 75**

\$99\*  
Analog/digital display  
Volts, ohms, 10A, mA, diode test  
Audible continuity  
Autorange/range hold  
0.5% basic dc accuracy  
2000+ hour battery life  
3-year warranty



**FLUKE 77**

\$139\*  
Analog/digital display  
Volts, ohms, 10A, mA, diode test  
Audible continuity  
"Touch Hold" function  
Autorange/range hold  
0.3% basic dc accuracy  
2000+ hour battery life  
3-year warranty  
Multipurpose holster


\* Suggested U.S. list price, effective November 1, 1985  
\*\* Patent pending.



IN THE U.S. AND NON-EUROPEAN COUNTRIES: John Fluke Mfg. Co., Inc., P.O. Box C9090, M/S 250C, Everett, WA 98206. Sales: (206) 356-5400, Other: (206) 347-6100.  
EUROPEAN HEADQUARTERS: Fluke (Holland) B.V., P.O. Box 2269, 5600 CG Eindhoven, The Netherlands, (040) 458045, TLX: 51846.  
© Copyright 1985 John Fluke Mfg. Co., Inc. All rights reserved. Ad No. 4714-70

CIRCLE NO 199



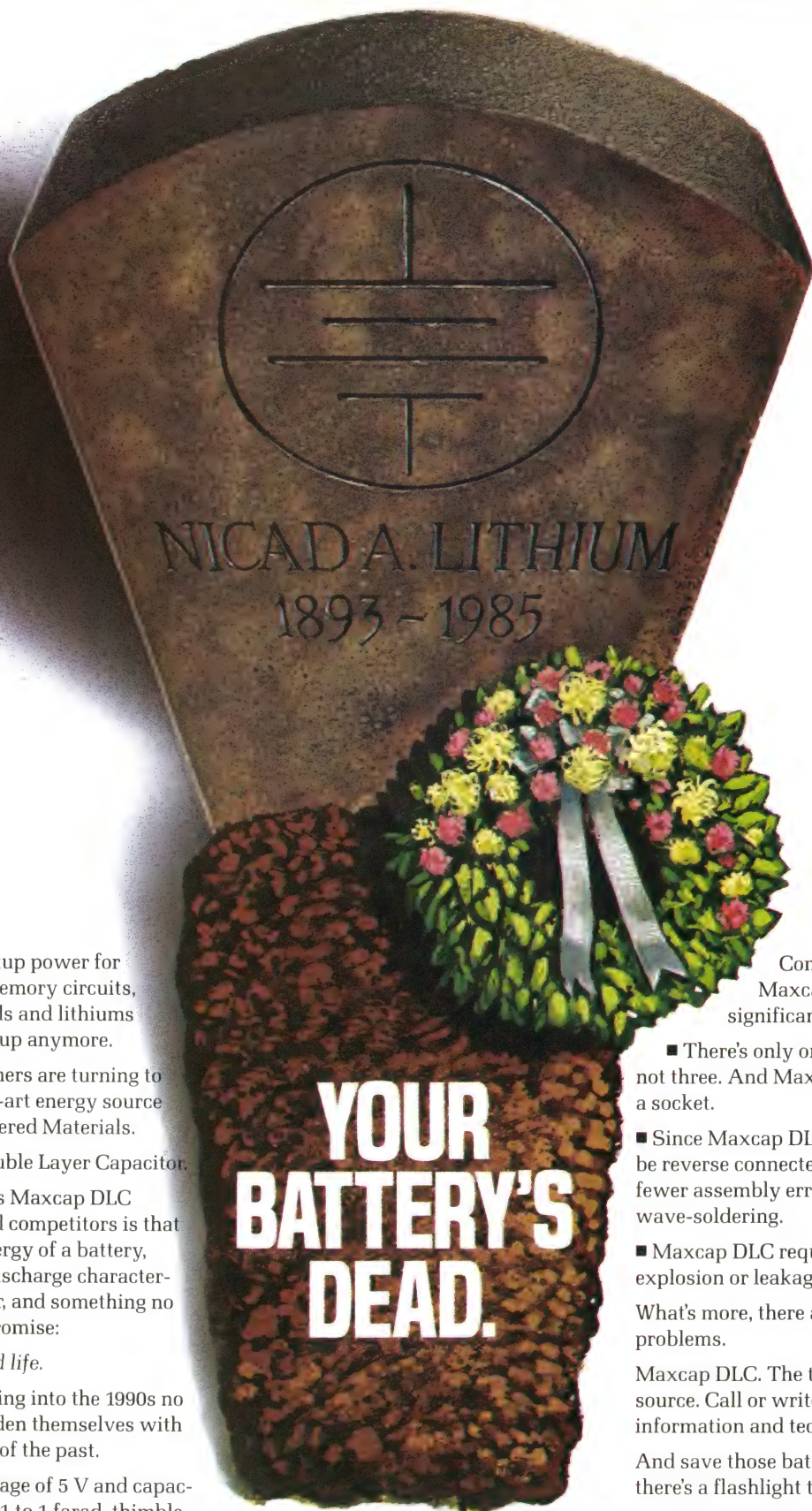

As backup power for CMOS memory circuits, the ni-cads and lithiums just don't measure up anymore.

Now, circuit designers are turning to a new, state-of-the-art energy source from Sohio Engineered Materials.

The Maxcap™ Double Layer Capacitor.

What distinguishes Maxcap DLC from its antiquated competitors is that it gives you the energy of a battery, the rapid charge-discharge characteristics of a capacitor, and something no battery can ever promise:

*Virtually unlimited life.*

So designers working into the 1990s no longer have to burden themselves with power sources out of the past.

At its nominal voltage of 5 V and capacitance values of 0.01 to 1 farad, thimble-size Maxcap DLC can be charged and discharged indefinitely without maintenance or replacement. Since there's no need for access, equipment can be

## YOUR BATTERY'S DEAD.

made smaller and simplified. You can also reduce backup circuit and assembly costs.

Compared to batteries, Maxcap DLC delivers these significant cost savings:

- There's only one extra component, not three. And Maxcap DLC doesn't need a socket.

- Since Maxcap DLC is nonpolar, it can't be reverse connected, so you'll have fewer assembly errors. And you can use wave-soldering.

- Maxcap DLC requires no toxicity, explosion or leakage safeguards.

What's more, there are no disposal problems.

Maxcap DLC. The timeless energy source. Call or write for complete information and technical details.

And save those batteries. Somewhere, there's a flashlight that can use them.

Sohio Engineered Materials Company  
Semiconductor Products Division  
P.O. Box 664  
Niagara Falls, NY 14302  
716/278-3954

**Sohio  
Engineered Materials  
Company**

Maxcap DLC shown actual size above.




CIRCLE NO 200



# Protect Your Power

## Surge Protectors

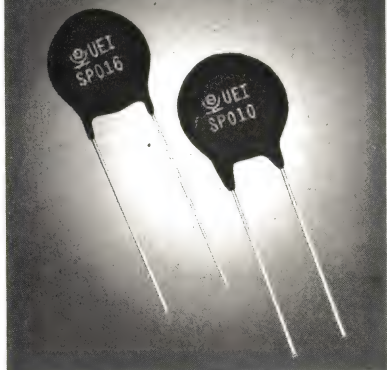

Inrush current suppressing devices specially designed for switching power supplies.




**UPPERMOST Electronic Industries Co., Ltd.**  
59, Wen Hua Road, Kaohsiung, Taiwan, R.O.C.  
Tel. (07) 201-0175 Fax. (07) 282-0935  
Telex. 71520 YUNLOON

CIRCLE NO 70
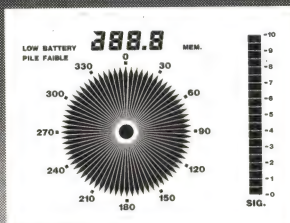
# LCD

**CUSTOM/STANDARD  
BEST QUALITY/SERVICE  
U. S. MANUFACTURING**



BAT  
1.8:8.8

- -40°C TO 95°C STORAGE/OPERATION TEMPERATURE
- LOW POWER/HIGH CONTRAST/WIDE VIEWING
- DICHROIC/PHASE CHANGE TYPES
- PLASTIC PROTOTYPE/GLASS PRODUCTION/DOT MATRIX
- COMMERCIAL/MILITARY STANDARDS
- CUSTOM MODULES
- 2 TO 4 WEEKS DELIVERY

**POLYTRONIX, INC.**  
P. O. BOX 833024, RICHARDSON, TX 75083  
(214) 238-7045



CIRCLE NO 71





# Power Your Communications. Communicate Your Power. With TDK Ferrite Cores.

As telecom technology switches to digital, and power supplies switch to switchers, quality and features of ferrite cores take on added importance while generating new reasons to talk to the undisputed leaders, TDK.

Next time you're in our neighborhood, come and take a look at the world's largest production of ferrite materials. TDK manufactures ferrite cores from the raw materials on up, with totally automated production systems. 50 years of experience and a continuous R & D program are reflected in unique features and unsurpassed quality levels.

*For telecom and power supply applications, TDK ferrite cores include:*

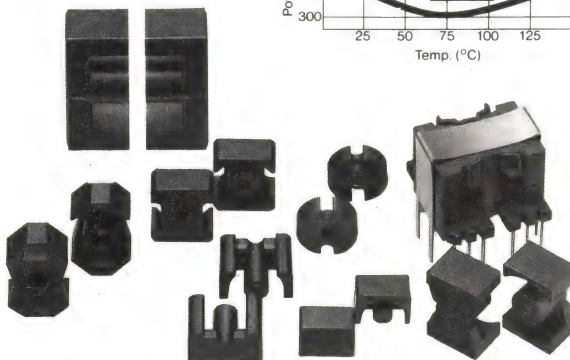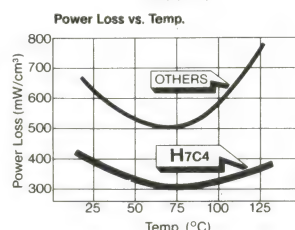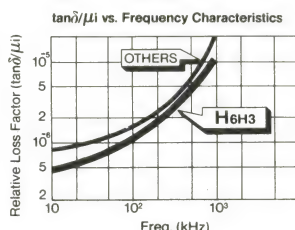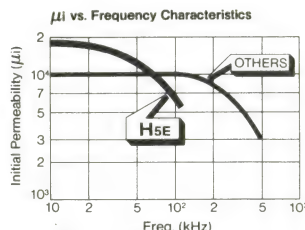- High permeability types such as our H5E
- Low loss types with significantly reduced loss factors up into the MHz range;
- Extremely low power loss and reduced temperature surge types (H7C4);
- TDK original cores, EEC, EP, LP and PQ as well as IEC standard core shapes including EEC, POT, RM, etc.



**TDK CORPORATION OF AMERICA** HEAD OFFICE 4711 West Golf Road, Skokie, IL 60076, U.S.A. Phone: (312) 679-8200  
**TDK CORPORATION** Tokyo, Japan.  
**MH&W INTERNATIONAL CORP.** 14 Leighton Place, Mahwah, New Jersey 07430 U.S.A. Phone: (201) 891-8800  
**MH&W INTERNATIONAL (CANADA) LTD.** Phone: (416) 676-9401

CIRCLE NO 80



<i>Device</i>	<i>Peak Vf at 1000A</i>	<i>Rel. Eff% at 5kW output</i>	<i>Input V at 1000A</i>	<i>Relative dc ripple mV</i>
<i>Germanium</i>	<i>0.60</i>	<i>86.5</i>	<i>188.8</i>	<i>80</i>
<i>Schottky</i>	<i>1.00</i>	<i>85.0</i>	<i>190.0</i>	<i>150</i>
<i>Silicon in use</i>	<i>1.20</i>	<i>76.0</i>	<i>200.0</i>	<i>100</i>
<i>Silicon alt. mfr.</i>	<i>1.25</i>	<i>74.0</i>	<i>202.0</i>	<i>95</i>

The figures on the blackboard came to us from the manufacturer of some of the world's largest computers.

As you see, they compare the performance of Germanium diodes with Silicon Schottky, with a Silicon Device already in use, and another Silicon product from another source.

After extensive laboratory and field tests, Germanium was clearly the first choice.

If you use Silicon for rectification, send for the GPD catalogue. It also contains many other devices from small signal to 500 Amps, in which the inherent advantages of Germanium are combined with the GPD's high standard of manufacture.

CIRCLE NO 201

**Germanium  
Rectifiers:  
Oliver  
gives you  
the facts.**

## Germanium Power Devices Corporation

**Australia** Eastern Crest (Pty) Ltd., 21 Shierlaw Avenue, Room 4, Canterbury, Victoria 3126. Tel: (03) 836 6818. Tlx: 790-38783 EAST. **Austria** Omni Ray GmbH, Vertriebsbüro Wien, Prinz Eugen-Strasse 36, A-1040 Wien. Tel: 0222-65 64 31. Tlx: 132712 omray a. **Benelux** BV DIODE Laboratorium Voor Electronentechniek, Hollandlaan 22, 3526 AM Utrecht, Holland. Tel: 030-884214. Tlx: 47388/Rue Picard Str. 202, 1020 Bruxelles, Belgium. Tel: 02-4285105. Tlx: 25903. **Denmark** E. V. Johansen Elektronik A/S, Titangade 15, DK 2200 Copenhagen N. Tel: 0451-83 90 22. Tlx: 16522. **France** Davum, Dept TMC, 11 Rue Racine, PO Box 28, 93121 La Courneuve. Tel: 836-84-01. Tlx: 210311F (PUBLI). **West Germany** Protec GmbH, Margreider Platz D8012 Ottobrun. Tel: 089-6097001. Tlx: 529298. **Italy** Esco Italiana Spa, 20099 Milano, Via Modena, 1. Tel: (02) 2409241/2409251. Tlx: ESCOMI 322383./Eurelettronica SRL, Sede, 20145 Milano, Via Mascheroni 19. Tel: 049-81 851. Tlx: 39102 THOMELEC. **Norway** Nordisk Elektronik (Norge) A/S, Mustadsvei 1, Postboks 91-Lilleaker, Oslo 2. Tel: 0752-13300. Tlx: 856-16963 (AJCO NM). **Sweden** Satt Electronics AB, Agency Sales Division, PO Box 32006, S-l: 08/8126 11 Stockholm. Tel: 08/81 01 00. Tlx: 10884. **Switzerland** Omni Ray AG, Industriestrasse 31, CH-8305 Dietlikon. Tel: 01-835 21 11. Tlx: 53239 omni ch. **UK Representative** Winslow International, Rassau Industrial Estate, Ebbw Vale, Gwent NP3 5SD. Tel: 0495 309117 Tlx: 498903.

GPD Box 3065, Shawsheen Village Station, Andover, Mass 01810.


Telephone: (617) 475-5982. Telex: 94-7150 GPD Andr.



# WOULD YOU SETTLE FOR $15\mu\text{s}$ ? GUARANTEED?

PMI guarantees 12-bit settling-time for its AMP-05 Instrumentation Amplifier.

At all gains.

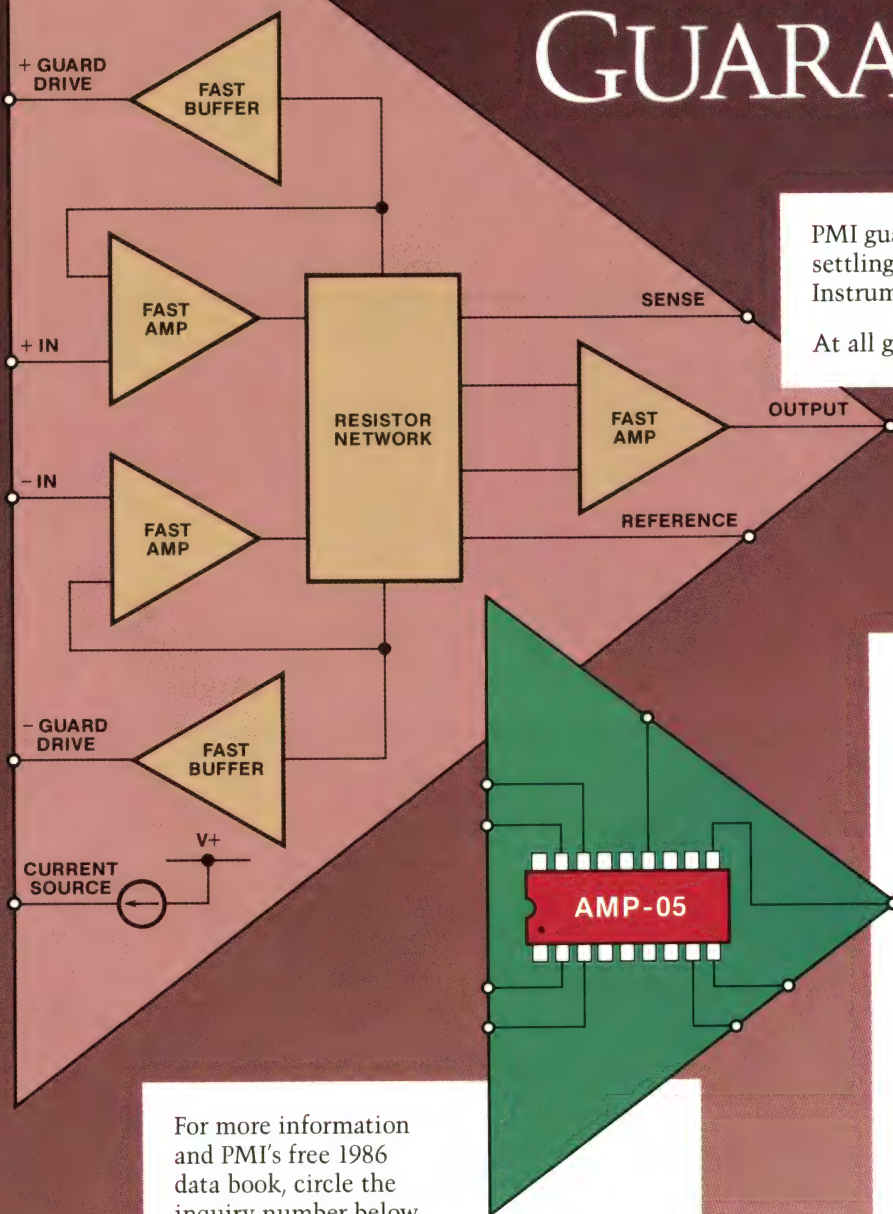

$15\mu\text{s}$  settling-time and  $15\mu\text{s}$  overload recovery time set the stage for high-speed data acquisition. On-board guard drivers and a  $100\mu\text{A}$  precision current source minimize components, save board space, and increase versatility.

Like PMI's industry standard AMP-01, the monolithic AMP-05 provides a high and stable common-mode rejection of 105dB MIN. over temperature. JFET inputs reduce bias currents to 50pA MAX. (20nA MAX. at  $125^\circ\text{C}$ ), for high impedance applications.

The AMP-05's output is guaranteed stable with 2nF loads, slews at  $5\text{V}/\mu\text{s}$ , and has a gain-bandwidth product of 120MHz.

For more information and PMI's free 1986 data book, circle the inquiry number below.

Precision Monolithics Inc.  
A Bourns Company  
1500 Space Park Drive  
Santa Clara, CA  
95054-3499  
(408) 727-9222

1-800-843-1515  
or, in California  
1-800-826-9664

FRANCE: 01-42 03 96 33, GERMANY: 0711-22 93 0, NETHERLANDS: 070 87 54 04, SWITZERLAND: 042-33 33 33,  
UNITED KINGDOM: 01-572 65 31, HONG KONG: 0-4992688, JAPAN: (03) 234-1411, ARGENTINA: 46-5776/0628/0864/2214,  
AUSTRALIA: (02) 570-8122, AUSTRIA: 0222-43 26 39, DENMARK: 02-98 63 33, EASTERN EUROPE: 0222-24 71 37,  
FINLAND: 90-75 06 00, GREECE: 01-821 58 25, INDIA: 222-999, ISRAEL: 03-49 44 50, ITALY: 02-569 57 46, KOREA: (02) 244-7492,  
NORWAY: 02-83 02 20, PORTUGAL: 19-68 60 72, SINGAPORE: 747-6188, SOUTH AFRICA: 52 86 61 OR 011-839 18 24,  
SPAIN: 01-405 42 13, SWEDEN: 08-768 05 60, TURKEY: 041-30 15 10, YUGOSLAVIA: 041-42 37 46.



*The precision solution.*



# The High Performance CASE for PCB design.



## From Design to Production

CASE Technology's new VANGUARD™ PCB design system includes schematic capture, CADAT logic simulation, worst case timing verification, and PCB layout. Nowhere else in the industry can you find as complete a set of professional PCB design tools on the desktop for only \$15,000. The entire system operates on standard IBM PC/XT/ATs, MicroVAX workstations and VAX mini-computers.

The VANGUARD PCB design system can be used as a stand-alone, interactive PCB design station for schematic capture, component placement, routing and final artwork generation. The system allows for interactive 45 degree routing, rats nesting capability, pin and gate swapping, automatic packaging, and on-line netlist consistency checking between the schematic and the physical board design. It is by far the highest performance PCB design system on the desktop.

## The CAE Price/Performance Leader

With more than 1500 installed systems, CASE Technology has developed a solid reputation as the CAE price/performance leader. If you haven't seen what CASE has to offer, then now's the time.

CASE Technology, Inc., 633 Menlo Avenue, Menlo Park, CA 94025. Phone: (415) 322-4057; Telex 506513.



# PC-based programs aid analog-circuit design and analysis

---

*You can use analog-circuit simulation software that runs on the IBM PC and compatible computers to analyze circuit designs. The programs, which augment (rather than replace) your circuit-design knowledge, let you analyze a circuit's ac and dc performance and conduct transient, Fourier, and Monte Carlo analyses.*

---

Richard E Kiefer, *Consultant*

Using circuit-simulation programs that run on the IBM PC and compatible computers, you can evaluate analog-circuit designs. Although you'll still need to understand thoroughly the principles of analog-circuit design, the programs can provide additional information and enhance your confidence that your designs will work. These analog-circuit simulation programs let you perform dc and ac analysis, transient analysis, Fourier analysis, and Monte Carlo (worst-case) analysis. Whether you are just starting your design or evaluating its implementation, you'll find these PC-based design tools useful.

**Table 1** (pg 188) lists the features and specs of five analog-design software tools. The tools have similar

capabilities, so a general description suffices to explain them all. For each type of analysis, one simulation program is described; the description of the analysis, however, holds true for all the packages.

For any type of circuit analysis on a personal computer, you must enter the design into the PC, run an analysis program, and then produce the results of the program in a format that you can understand. In most cases, you enter a design by creating an ASCII input file with a text editor or word processor. Some analysis programs include graphics-input capabilities that let you draw the circuit on the screen by using graphical representations of circuit elements. You then interconnect these elements with lines that represent wires. The program compiles the graphical description into an input file for analysis. To use the file in conjunction with the analysis program, you must identify it as the input file.

After the analysis program has analyzed your input file, you'll want to create output files and graphs to format the results for evaluation. Programs that format analysis results are called postprocessing utility programs; they can plot 2-dimensional graphs with the axes defined in linear or logarithmic steps. If you define the X axis to represent time, the postprocessors create diagrams that are organized like waveforms on a multi-channel scope. By setting different zero points and changing the scale of the axes, you can zoom into any part of the plot.




*Postprocessing utility programs can plot 2-D graphs with the axes defined in linear or logarithmic steps.*

The first step in evaluating your design is dc analysis, which checks the overall biasing voltages of the circuit to verify that resistor values and input common-mode ranges are correct. You can also determine if transistors in your amplifier stages are becoming saturated, if your current sources don't comply with specified ranges, and if your output signals contain nonlinear aberrations caused by inadequate drive capability. You


should check all of these conditions over the product's temperature range.

For dc analysis, consider E/Z CAD's Circuitpro program. To use it, you create via a text editor or word processor an ASCII file that describes your circuit. You initiate the analysis by starting the program and submitting the ASCII file from text editor to the Circuitpro program. In this type of analysis, capacitors

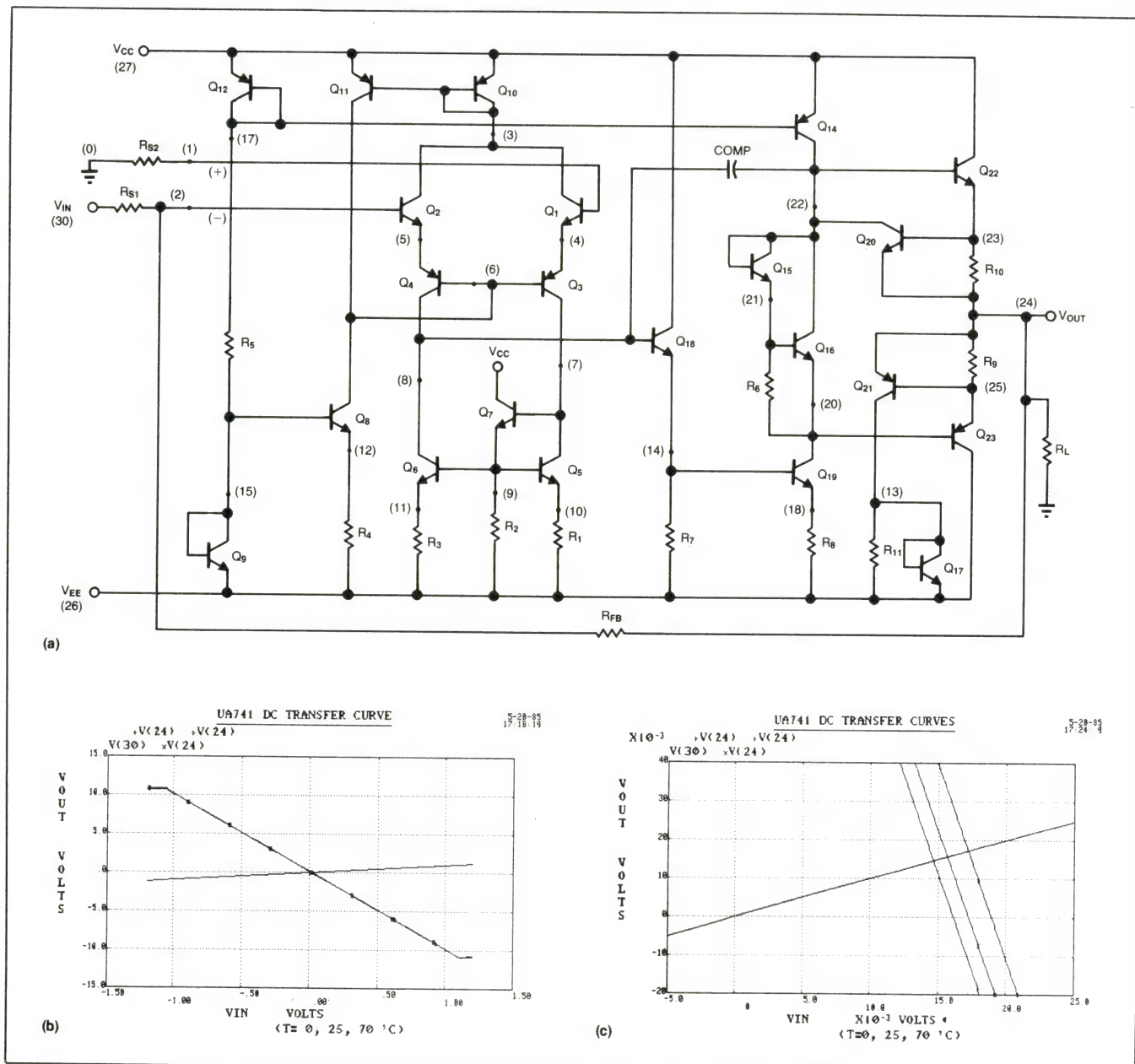

**Fig 1—The dc response of an op amp (a) over its input-voltage range appears in b. The plot expands in c to show an offset-voltage drift of 30 mV over 0 to 70°C.**



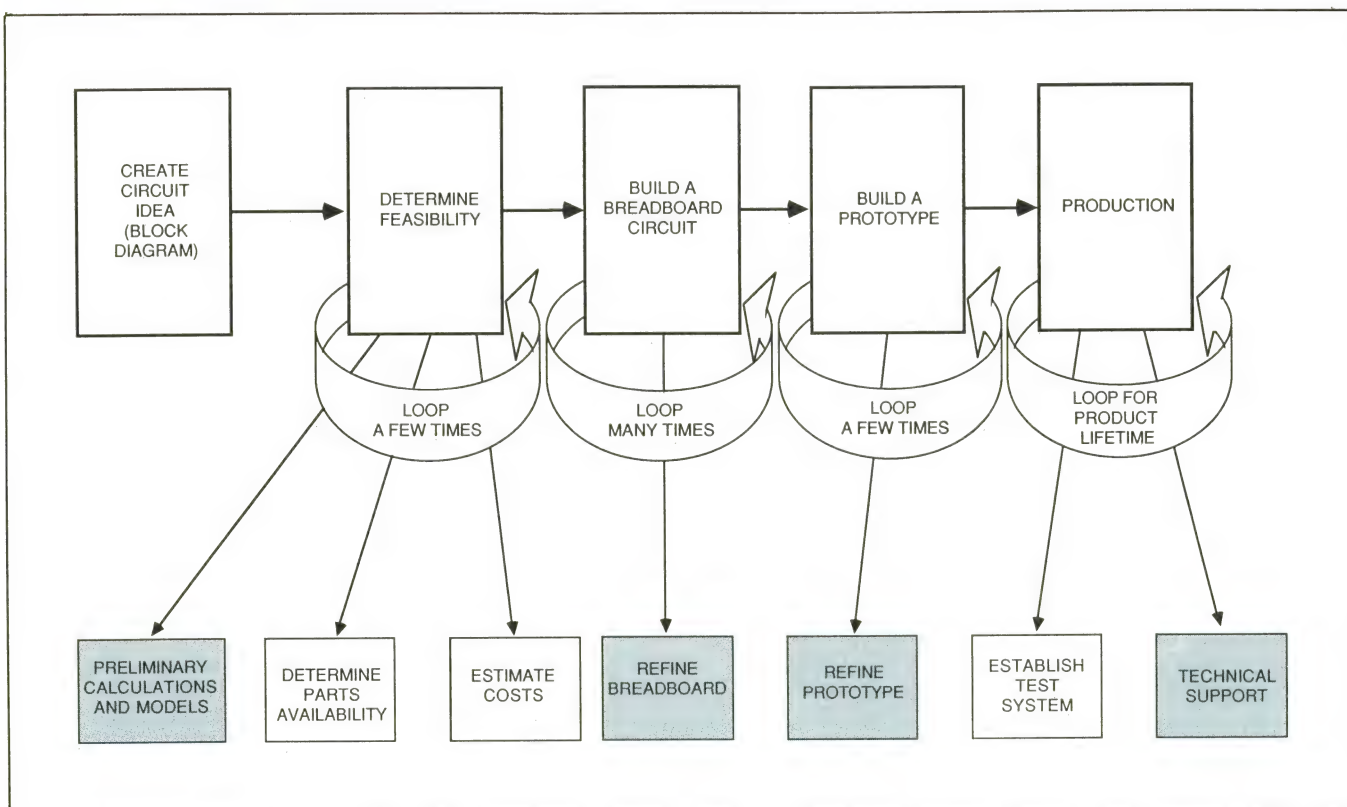

*Simulation assists in several steps of the analog-design cycle (shaded areas). It performs preliminary calculations, helps analyze breadboard and prototype performance, and supports production.*

appear as open circuits, and inductors have zero resistance.

Upon completion, you plot the results using E/Z CAD's Viewplot program. Viewplot can create plots of simulation waveforms on your PC's screen; to create hard copies, use the MS-DOS Graphics.com utility (by depressing the Shift and Shift-Print keys) to send the image to a printer. Through menus, you can scale the X and Y axes for either scalar or logarithmic units. To create waveform plots that resemble a multichannel-oscilloscope display, use the X axis to designate time. The program allows you to save the scaling data of your plot. Viewplot is a general-purpose plotting program that can plot any data as long as the data is in the output format of Circuitpro.

### DC-analysis example

To illustrate the result of Circuitpro's dc analysis, consider the 741 op-amp circuit in **Fig 1a**. You want to examine the output voltage as the input voltage varies from  $-1.2$  to  $+1.2$ V, stepped in 400 6-mV increments. To determine the effect of temperature on the output voltage, you can run the 400-step simulation at several temperatures. The results of a simulation run at 0, 25, and 70°C appear in **Fig 1b** and **1c**, plotted at different scales.

The three waveforms nearly overwrite each other in **Fig 1b**. The amplifier drives from a positive rail of approximately  $+11$ V to a negative rail of about  $-11$ V as the input voltage rises from  $-1.2$  to  $+1.2$ V. To see the effect of temperature on the offset voltage, you

need to expand the plot in order to get a closer look at the absolute values of the waveforms.

**Fig 1c** shows the center of the plot of **Fig 1b** with the units changed from volts to millivolts—in essence expanding the resolution of the plot in **Fig 1b**. Viewplot allows you to redefine the units along the X and Y axis to create this expansion. In the expanded version, the voltage for the 0°C plot is roughly 30 mV lower than the voltage for the 70°C plot, indicating that the offset voltage drifts 30 mV over 0 to 70°C.


### AC analysis ignores nonlinear responses

The next type of analysis, ac analysis, examines the effects of operating frequency on the amplitude and phase of voltage signals in your circuit. Programs that perform this analysis examine the effect of small ac signals that are juxtaposed on a dc operating point. As a result, this small-signal analysis ignores nonlinear responses that your circuit might exhibit during dc analysis.

You create a description of your circuit in a way similar to that used for the dc-analysis program. You then execute one of the ac-analysis programs such as Acirc from FB Circuit Products. This program allows you to examine any ac node voltage and ac branch current and to calculate Thevenin-equivalent input resistances for the nodes. You can also modify your input file and simulation parameters while you run Acirc without having to use a text editor, and you can save the changes you make.

**Fig 2** shows a bandpass-filter schematic in addition to



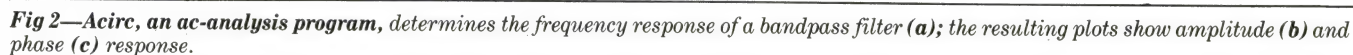




*In dc analysis, capacitors appear as open circuits, and inductors have zero resistance.*

two plots produced using the Acirc program. The filter uses stagger tuning to isolate a 600-Hz signal; this type of filter is often used in Bell-212A modems to isolate a 600-Hz carrier frequency. Stagger tuning, which reduces the overall temperature drift of the filter, requires you to adjust the value of  $R_8$  to pinpoint the 600-Hz response of the filter (at which point the output signal is exactly  $180^\circ$  out of phase with the input signal

at 600 Hz). You use Acirc and estimated values of  $R_8$  to plot the response of the filter and find the best value for  $R_8$ .

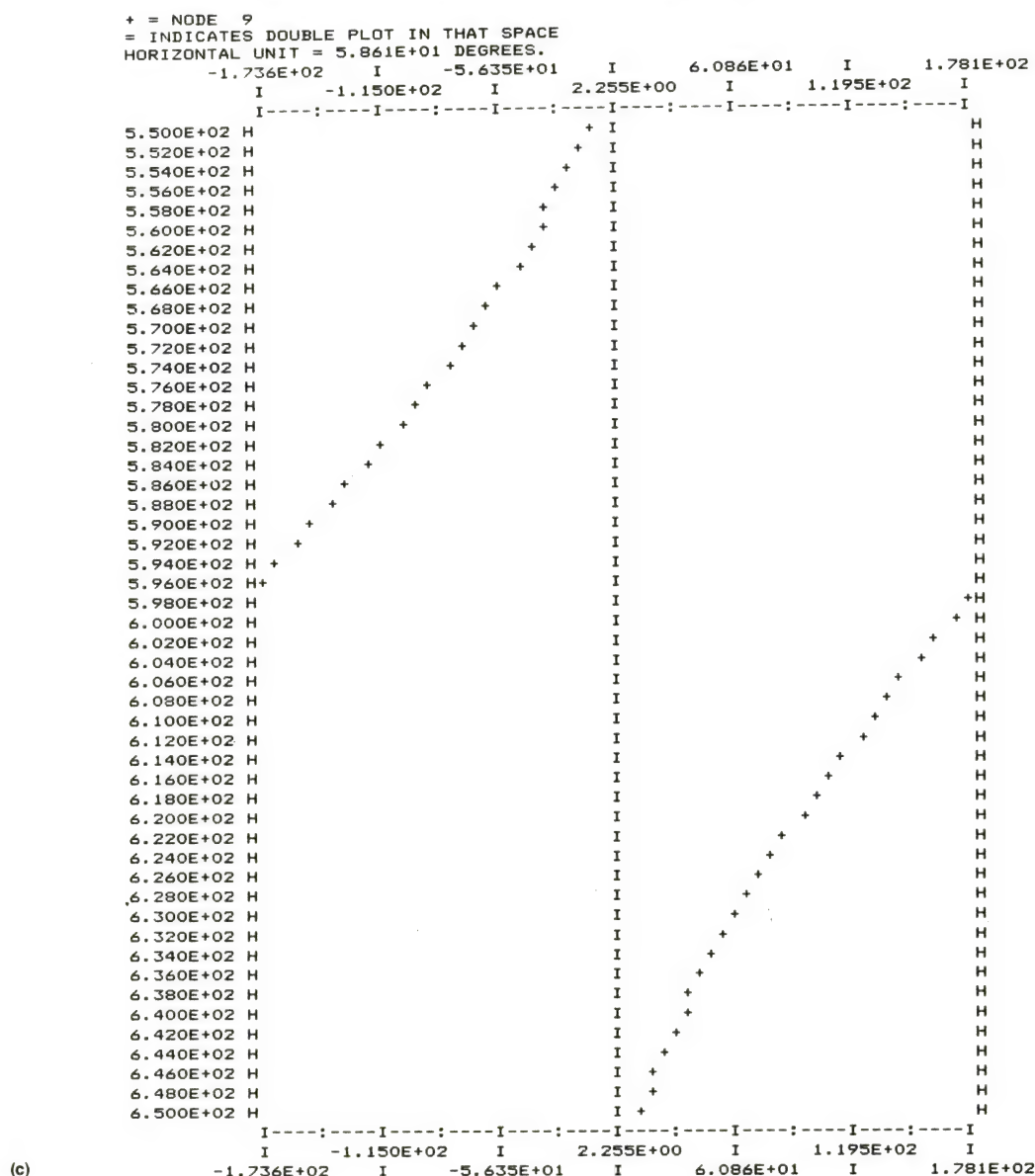**Figs 2b and 2c** show the output of an ac analysis of the filter in **Fig 2a**. Acirc automatically scales the outputs and can send them to the PC's screen, a disk file, or a printer. You can plot the values of one or two of the nodes in the circuit, and the node's values can be in





---

## *AC analysis ignores nonlinear responses that could appear during dc analysis.*

---

either decibels of gain from the input or in volts. For the filter in **Fig 2a**, **Fig 2b** shows a maximum output-node voltage of about 16V. The center frequency lies between 596 and 598 Hz. You determine the center frequency by noting the discontinuity in the phase response (**Fig 2c**). To ascertain the center frequency more accurately, you can resimulate the filter using smaller time increments, such as 0.1 Hz, between 596 and 598 Hz.

### **Transient analysis measures slew rate**

Transient analysis (large-scale analysis) can determine such parameters as slew rate, rise time (from which you determine 3-dB bandwidth), overshoot, and settling time, all of which you cannot determine using small-signal ac analysis. Transient analysis looks at the time-domain response of a circuit to an input waveform: usually a step, ramp, or sinusoid. Large input-signal swings induce the nonlinear and reactive behavior of the simulated circuit.

To perform transient analysis using Spectrum Software's MicrocapII program, you enter the circuit, describe the input waveform, set up the parameters of the analysis, and then execute the program. MicrocapII uses graphical entry, and so you use icons to represent such premodeled components as transistors, resistors, capacitors, inductors, diodes, current and voltage sources, and transformers. As you build your circuit on the PC's screen, the program automatically assigns node numbers and displays them on your schematic. You save your completed schematic in a file for input to the simulator.

### **Program calculates transient circuit values**

As an example of MicrocapII at work, consider the analysis of a circuit that uses a step waveform. First, you respond to the program's prompt to insert a model of a pulse generator at the circuit input. You enter such pulse-generator parameters as voltage step, rise time, fall time, and period. Then you specify simulation parameters, including total simulation time over which the program calculates the transient circuit values. You also specify the time step between calculations of circuit values. The program often calculates nodal voltage more frequently than specified by the time step to maintain a minimum accuracy of 5%.

At this time, you can indicate the nodes whose values you want the program to display and the initial values of conditions of components. Assigning initial component values frees you from having to use additional

initializing waveforms. For example, if you want a capacitor in your circuit to have a charge on it when the analysis begins, you can simply set the value of that charge.

### **Program generates output waveforms**

As an example of MicrocapII's capability, consider the analysis of a 733-equivalent video amplifier. In **Fig 3a**, the amplifier appears with a pulse generator attached and node numbers assigned. Given the simulation constraints displayed in **Fig 3b**, the transient response appears as shown in **Fig 3c**. Values for  $V_{CC}$  and  $V_{EE}$  are 6 and -6V, respectively, and  $R_1$  equals 2 k $\Omega$ .

The two graphs in **Fig 3c** show the response of the amplifier to a square pulse. The upper plot shows the differential output voltage across the first stage of the amplifier—between nodes 2 and 6. Three output waveforms result from three simulations at different temperatures between 0 and 70°C. The square waveform in the upper plot represents the 80-mV input waveform from the pulse generator. The waveforms on the lower trace show the voltage across  $R_L$ . The overshoot and undershoot for all waveforms is evident. In addition, the rise time of the signal from 10 to 90% of its final value is 6 nsec, which corresponds to a 3-dB bandwidth of 58 MHz for the amplifier.

### **Fourier analysis determines linearity**

The fourth type of analysis—Fourier analysis—determines the linearity of an analog circuit. In this analysis, you apply an arbitrary waveform to the circuit's input and examine the output waveform for harmonic and intermodulation distortion. You compare the harmonic content of the output with that of the input; when the output differs from the input, the circuit is distorting the waveform.

Like its progenitor, Spice, PSpice from MicroSim Corp requires an input file that contains a description of your circuit and program-analysis commands. The circuit description is similar to a Spice input file, and you can include special active-component model parameters such as the ideal values of the forward and reverse betas and junction capacitance. In addition to commands for controlling the limits of the simulation, you can insert plot and print commands into the input file to direct PSpice to place output data in an intermediate disk file (it's not generally the final file because you'll probably perform postprocessing).


When the simulation is finished, you can use the



Probe postprocessing program to format the output data. Alternatively, you can view the results on your screen or print them directly. Probe allows you to view the data in graphical format, with linear or logarithmic units on the axes. You can expand or contract the scale of the axes as well. Furthermore, you can plot traces of

the values at several nodes in your circuit, adding or subtracting traces at will. Because Probe is a general-purpose plotting program, you can use it to create plots from any database that has the same output format as PSpice.

A 5-MHz sinusoidal input to the broadband differen-

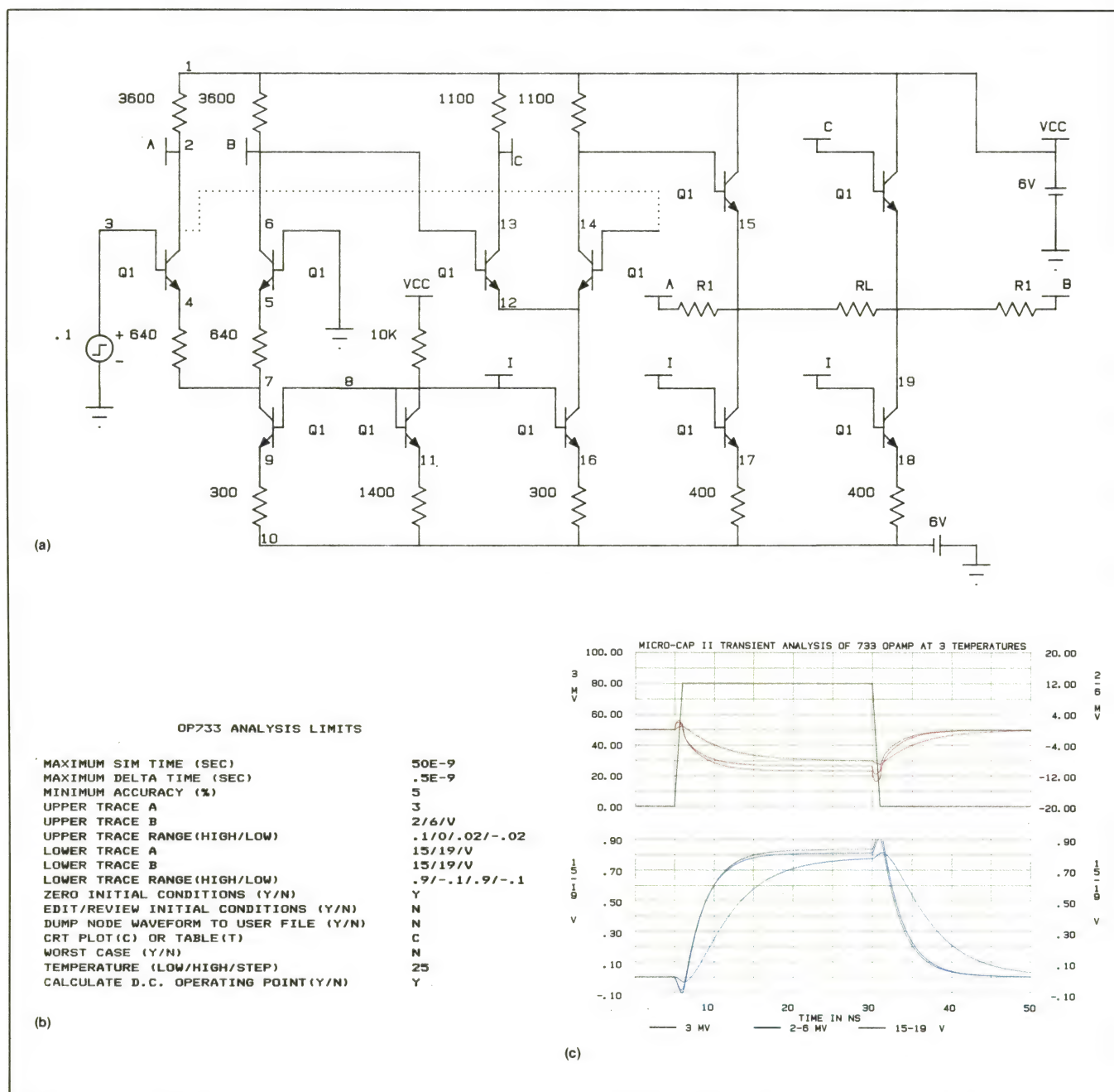

**Fig 3—Transient analysis reveals circuit response to a step or sinusoidal input waveform. For the amplifier in a, the analysis limits in b result in the plots shown in c. Overshoot and undershoot are evident, and the 6-nsec rise time indicates a 58-MHz bandwidth.**




*Transient analysis can determine such parameters as slew rate, rise time, overshoot, and settling time.*

tial amplifier in **Fig 4a** produces the larger of the two sinusoidal waveforms in the **Fig 4b** Probe plot when run through PSpice. The output waveform appears between nodes 4 and 5 in the schematic. The irregular shape of the output shows the presence of harmonic distortion. PSpice calculates the Fourier analysis of the waveform and presents the results in a tabular format (**Fig 4c**). The results include the total harmonic distortion as a percentage of the output waveform plus the amplitude and phase of each harmonic component.


You may also use the PSpice Fourier-analysis capability to construct piecewise-linear or polynomial-shaped waveforms from a current or voltage (or combined) signal. In this way, you can investigate arbitrary input and output waveforms during design.
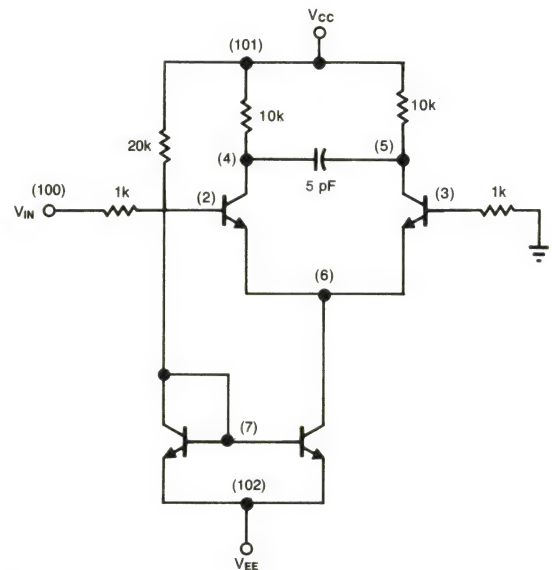
#### Consider components' tolerances

The final simulation appropriate to analog-circuit design involves assessing variations in performance that are caused by the tolerances of the components in the circuit. Called Monte Carlo analysis, this simulation



(a)

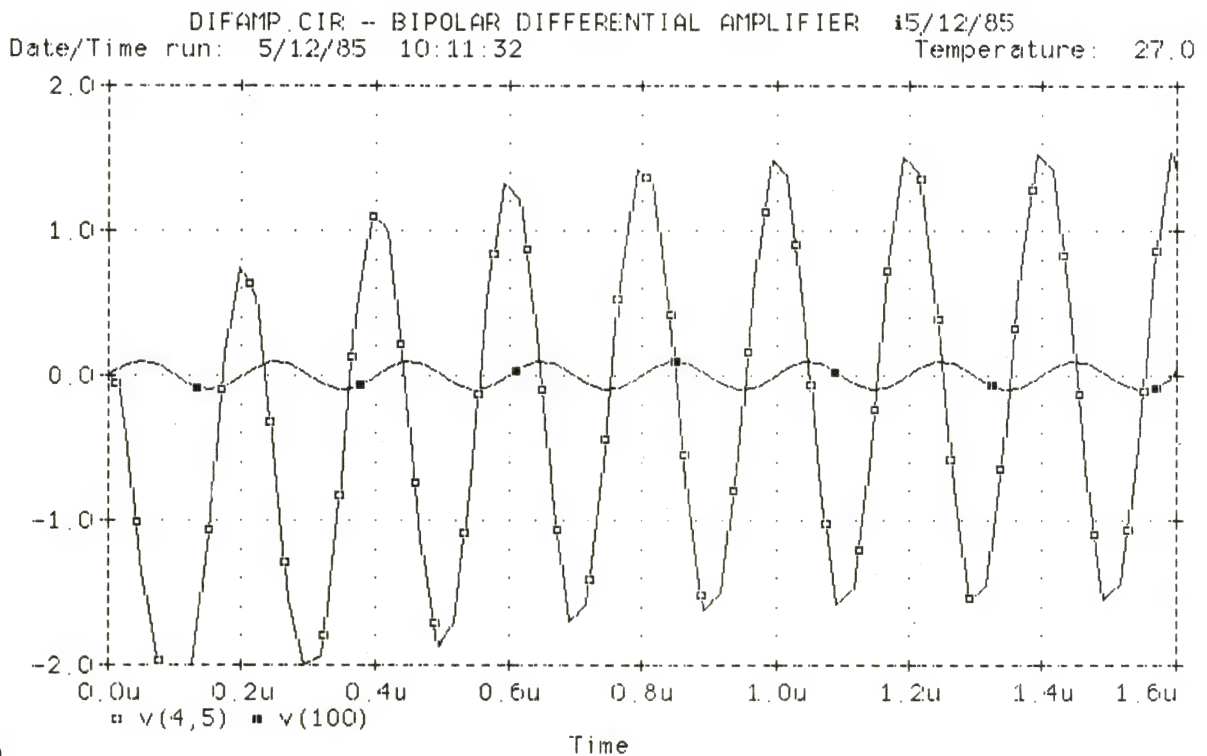

(b)

**Fig 4—A PSpice Fourier analysis of a differential amplifier (a) can be indicated in graphic (b) or tabular (c) form. The tabulation reveals 2.58% total harmonic distortion.**



\*\*\*\*\* 5/12/85\*\*\*\*\* PSpice 2.02 (Mar. 1985)\*\*\*\*\*10:11:32\*\*\*\*\*

DIFAMP.CIR - BIPOLAR DIFFERENTIAL AMPLIFIER 5/12/85

\*\*\*\* FOURIER ANALYSIS TEMPERATURE = 27.000 DEG C

\*\*\*\*\*

FOURIER COMPONENTS OF TRANSIENT RESPONSE V(4,5)

DC COMPONENT = -1.722D-04

HARMONIC NO	FREQUENCY (HZ)	FOURIER COMPONENT	NORMALIZED COMPONENT	PHASE (DEG)	NORMALIZED PHASE (DEG)
1	5.000D+06	1.533D+00	1.000000	87.591	.000
2	1.000D+07	5.229D-03	.003410	121.442	33.851
3	1.500D+07	4.699D-03	.003065	95.086	7.496
4	2.000D+07	3.769D-03	.002458	118.711	31.120
5	2.500D+07	3.267D-03	.002131	131.764	44.173
6	3.000D+07	3.817D-03	.002489	128.756	41.165
7	3.500D+07	3.215D-02	.020969	-153.941	-241.532
8	4.000D+07	3.369D-03	.002197	140.577	52.986
9	4.500D+07	2.071D-02	.013505	-160.956	-248.547

TOTAL HARMONIC DISTORTION = 2.578233 PERCENT

(c)



*In Fourier analysis, you apply a sinusoidal signal to your circuit and observe the output waveform for distortion.*


indicates whether you can execute your circuit design to meet your specifications, given the tolerances in components and operating conditions.

To run Monte Carlo analysis, you enter a circuit description as you would for ac simulation. Then you enter the tolerances and parasitics of the components you'll use to build the circuit. In the ECA2 program from Tatum Labs, you have the choice of either a text editor or the program's integral circuit editor. Component tolerances and temperature coefficients are part of the component description, but you have to introduce

parasitic impedances as additional components. For example, you model a capacitor so that it includes the inductance of the leads.

### Analyze a Chebyshev filter

The 10-MHz bandpass filter in **Fig 5a** exhibits a 10-MHz center frequency, a passband ripple of 0.1 dB, and a 3-dB bandwidth of 400 kHz during ac analysis. To analyze this Chebyshev filter, you enter the tolerances and parasitic impedances for the components you'll use to build the circuit. The capacitors will be silver mica

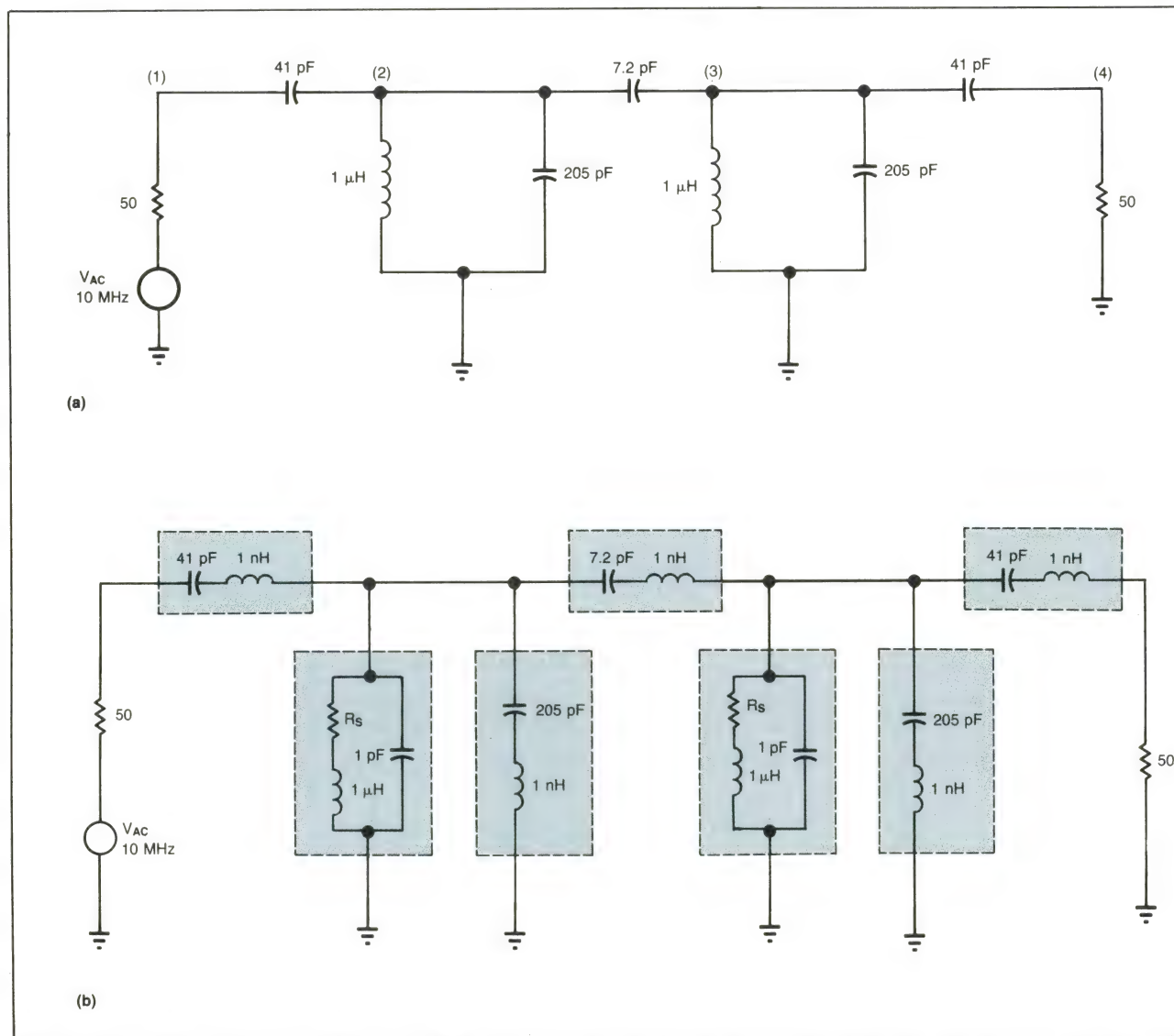

**Fig 5—Monte Carlo analysis** shows mean and standard deviation using several ac-analysis simulations at each frequency. You enter components' tolerances and temperature coefficients for the filter (a) into the program, and you model parasitic impedances into the schematic (b). The results of the analysis (c) show maximum gain at 9.3 MHz for average production instances of the design.



-->ac 8.2m 10.2m .1m random 10

# AC Monte Carlo Analysis

10 trials		----- max / min -----			----- mean / std.dev. -----		
freq	probe	value	dB	phase	value	dB	phase
8.2M	V:4	0.0085808	-41.329	69.189	0.0078564	-42.130	68.083
		0.006574	-43.643	67.412	720.47u	0.828	0.573
8.3M	V:4	0.011381	-38.876	67.854	0.010291	-39.795	66.466
		0.0084051	-41.509	65.639	0.0010558	0.930	0.718
8.4M	V:4	0.015516	-36.185	66.242	0.013813	-37.250	64.453
		0.010946	-39.215	63.403	0.001604	1.058	0.927
8.5M	V:4	0.021919	-33.184	64.247	0.019133	-34.439	61.856
		0.014584	-36.722	60.453	0.0025509	1.223	1.245
8.6M	V:4	0.032483	-29.767	61.697	0.027631	-31.275	58.350
		0.020004	-33.978	56.338	0.0043064	1.441	1.758
8.7M	V:4	0.051471	-25.769	58.298	0.042272	-27.629	53.298
		0.028497	-30.904	50.186	0.0078801	1.743	2.666
8.8M	V:4	0.089872	-20.928	53.500	0.070275	-23.295	45.270
		0.042725	-27.386	39.872	0.016108	2.178	4.495
8.9M	V:4	0.17854	-14.965	46.135	0.1313	-18.005	30.432
		0.068824	-23.245	19.303	0.03753	2.783	8.913
9.M	V:4	0.3443	-9.261	33.310	0.25877	-12.171	-1.439
		0.1227	-18.223	-26.044	0.077761	3.034	20.076
9.1M	V:4	0.39875	-7.986	6.875	0.35766	-9.026	-50.939
		0.24299	-12.288	-80.073	0.051995	1.402	29.088
9.2M	V:4	0.39462	-8.076	-43.718	0.37748	-8.494	-94.525
		0.29174	-10.700	-118.960	0.031687	0.808	23.857
9.3M	V:4	0.40417	-7.869	-89.703	0.38226	-8.376	-135.151
		0.30958	-10.184	-165.665	0.02804	0.687	25.371
9.4M	V:4	0.40323	-7.889	-125.274	0.32596	-9.864	-179.508
		0.24617	-12.175	149.160	0.058109	1.576	29.067
9.5M	V:4	0.38734	-8.238	-169.760	0.22181	-13.541	144.853
		0.1416	-16.979	125.523	0.079466	2.926	20.670
9.6M	V:4	0.2562	-11.828	149.122	0.13665	-17.757	123.924
		0.090058	-20.910	113.551	0.051356	2.901	11.204
9.7M	V:4	0.15373	-16.265	126.780	0.088801	-21.366	112.688
		0.062937	-24.022	106.536	0.027951	2.456	6.413
9.8M	V:4	0.1004	-19.965	114.981	0.062806	-24.276	106.035
		0.047086	-26.542	101.931	0.016426	2.077	4.160
9.9M	V:4	0.071334	-22.934	107.915	0.047431	-26.654	101.642
		0.037015	-28.632	98.664	0.010582	1.796	2.963
10.M	V:4	0.053966	-25.358	103.223	0.037578	-28.637	98.508
		0.030197	-30.401	96.214	0.0073325	1.587	2.252
10.1M	V:4	0.042768	-27.378	99.871	0.030859	-30.322	96.146
		0.025353	-31.919	94.302	0.0053731	1.427	1.794
10.2M	V:4	0.035108	-29.092	97.349	0.026054	-31.773	94.295
		0.021778	-33.240	92.763	0.0041127	1.302	1.480

(c)



*For Monte Carlo analysis, you construct several circuits on the computer without building any actual hardware.*

## Glossary of analog-circuit simulation terms

**AC noise contributions**—the relative amplitude of signal noise at a node in a circuit caused by noise sources within the circuit.

**AC transfer characteristic**—the relative gain, phase, or delay of the signal at a node with respect to a reference node. The term also refers to absolute measurement of ac voltage, current, or power at a particular frequency.

**AC voltage/phase/delay sensitivity**—relative response of a node's voltage, phase, or delay at a particular frequency to a change in some device parameter.

**Arbitrary-programmed voltage or current source**—an ideal source whose output you can describe in any mathematical or tabular form.

**Component macro model**—a user-defined collection of circuit elements that performs a specific function.

**Current-controlled current source (CCCS)**—an ideal current source whose output current is a linear function of an input current.

**Current-controlled voltage source (CCVS)**—an ideal voltage source whose output is a linear function of an input current.

**DC quiescent bias condition**—the values of all node voltages, currents, and power dissipations in a circuit, taking into account the nonlinearities of solid-state components in the circuit.

**DC transfer characteristic**—the response of a circuit to dc operating conditions and inputs with all reactive components eliminated (capacitors are open circuits, inductors are short circuits).

**DC voltage/current sensitivity**—the relative response of a node voltage or branch current to a change in some device parameter.

**Fourier response**—the magnitude of harmonic frequencies in the output signal of a circuit. The signal can be voltage, current, or power.

**Independent current source**—an ideal current source with infinite output impedance and infinite voltage compliance.

**Independent voltage source**—an ideal voltage source with zero output impedance and infinite current capability.

**Monte Carlo statistical analysis**—an analysis technique that determines the mean and standard deviation of circuit response. It requires many simulations using ac, dc, or transient analysis in which the component parameters are selected randomly from specified ranges of values.

**Piecewise linear voltage or current source**—an ideal source that has different gains at opposite input polarities or at different frequencies, with intermediate polarities and frequencies interpolated linearly.

**Polynomial voltage or current source**—an ideal source whose output is a polynomial function of an input voltage.

**Programmable voltage or current source**—an ideal source whose output you can program, eg, a pulse generator.

**Random-parameter evaluation**—an ac, dc, or transient-response calculation based on a random selection of component values from a uniformly distributed set of possible values.

**Temperature analysis**—the output of a circuit calculated as a function of temperature, determined by including temperature coefficients.

**Transient response**—the response of a circuit to one or more changing input sources, taking into account nonlinear behavior of solid-state devices and reactive components.

**Voltage-controlled current source (VCCS)**—an ideal current source whose output current is a linear function of an input voltage.

**Voltage-controlled voltage source (VCVS)**—an ideal voltage source whose output voltage is a linear function of an input voltage.

**Worst-case parameter evaluation**—an ac, dc, or transient analysis in which you vary the values of components within their tolerance ranges to produce the widest fluctuation in output.



## For more information . . .

For more information on the analog-circuit simulation programs described in this article, circle the appropriate numbers on the Information Retrieval Service card, or contact the following manufacturers directly.

**E/Z CAD Inc**  
5589 Starcrest Dr  
San Jose, CA 95123  
(415) 582-2009  
**Circle No 534**

**Spectrum Software**  
1021 S Wolfe Rd  
Sunnyvale, CA 94087  
(408) 738-4387  
**Circle No 537**

**FB Circuit Products Inc**  
5234 Longfellow Way  
Oxnard, CA 93033  
(805) 986-2276  
**Circle No 535**

**Tatum Labs**  
Box 698  
Sandy Hook, CT 06482  
(203) 426-2184  
**Circle No 538**

**MicroSim Corp**  
23175 La Cadena Dr  
Laguna Hills, CA 92653  
(714) 770-3022  
**Circle No 536**

devices that exhibit a temperature coefficient of 50 ppm/°C, a 5% tolerance, and a series lead inductance of 1 nH. The inductors, built from #6 material wound around a T-50-6 iron core, demonstrate a temperature coefficient of 35 ppm/°C, a stray parallel capacitance measuring 1 pF, and a 10% tolerance. The value of  $Q$  for the inductors varies from 170 at 4 MHz to 205 at 12 MHz. The program uses the value of  $Q$  to calculate the equivalent series resistance  $R_s$  of the inductor for each analyzed frequency. For frequencies between 4 and 12 MHz, the program calculates  $R_s$  using a straight-line interpolation shown in the equation  $R = 2\pi fL/Q$ , where  $f$  is frequency and  $L$  is the inductance measured in henrys.

The results of the analysis at each of the sample frequencies appears in **Fig 5c**. The first column on the left lists the frequency of the simulation, and the second column shows the node sampled. The middle three columns show the maximum and minimum gain of the circuit as measured at the frequency on the left. To determine the effect of variations in component values at each frequency, the program randomly selects values for the components within the components' listed tolerances and simulates the circuit 10 times. The filter has its highest mean gain at 9.3 MHz, which is the average center frequency if you use the components detailed in the previous paragraph. Minimum and maximum values tell you the widest range of responses you can expect when you start building the filter.

The program also lists the mean and standard deviations in the frequency response in the right-hand columns in **Fig 5c**. The program calculates the variations over the 10 simulations. At 9.3 MHz, the mean value of the circuit's attenuation is -8.376 dB with a standard deviation of 0.687 dB. Therefore, 68% of the filters built with these components will demonstrate an attenuation of  $-8.376 \pm 0.687$  dB at their 9.3-MHz center frequency.

**EDN**

## References

1. Cohen, Ellis, "Program Reference for SPICE2," EECS Industrial Liaison Program, Memorandum No. ERL-M520, University of California, Berkeley, CA.
2. Getreu, Ian, *Modeling the Bipolar Transistor*, Tektronix Part No 062-2841-00, Tektronix Inc, Beaverton, OR.
3. Nagel, Lawrence, "Spice: A Computer Program to Simulate Semiconductor Circuits," EECS Industrial Liaison Program, Memorandum No ERL-M520, University of California, Berkeley, CA.
4. Vlach, Jiri and Singhal, Kishore, *Computer Methods for Circuit Analysis and Design*, Van Nostrand and Reinholdt, New York, NY.

## Author's biography

*Richard E Kiefer is an independent design consultant for analog, RF, and EMI electronics. Based in Boulder, CO, he has worked with Martin Marietta, IBM, Hewlett-Packard, and Armco Autometrics. He holds BSEE and MSEE degrees from the Lawrence Institute of Technology and the University of Colorado. His hobbies include listening to classical music, operating a ham radio, cross-country skiing, backpacking, Scandinavian folk dancing, and reading historical novels.*



**Article Interest Quotient (Circle One)**  
High 476 Medium 477 Low 478



**TABLE 1—FEATURES OF REPRESENTATIVE  
ANALOG-CIRCUIT-SIMULATION SOFTWARE PACKAGES**

	E/Z CAD INC's CIRCUITPRO v 2.02 AND VIEWPLOT v 1.0	FB CIRCUIT PRODUCTS' DCIRC, ACIRC, AND TCIRC v 1.3	MICROSIM CORP's PSPICE v 2.02 AND PROBE v 1.0	SPECTRUM SOFTWARE's MICROCAPII v 2.0	TATUM LABS' ECA2 v 2.04
<b>CIRCUIT ANALYSIS TYPES</b>					
DC-TRANSFER CHARACTERISTICS	•		•	•	•
DC QUIESCIENT BIAS CONDITION	•	•	•	•	•
DC VOLTAGE/CURRENT SENSITIVITIES	•	•	•		•
AC-TRANSFER CHARACTERISTICS	•	•	•	•	•
AC-NOISE CONTRIBUTIONS	•		•		
AC-VOLTAGE/PHASE/DELAY SENSITIVITIES					•
TRANSIENT RESPONSE	•	•	•	•	•
FOURIER RESPONSE	•		•	•	
WORST-CASE PARAMETER EVALUATION					•
RANDOM-PARAMETER EVALUATION				•	•
MONTE CARLO STATISTICS					•
TEMPERATURE-VARIATION EVALUATION	•		•	•	•
DC-COMPONENT OPTIMIZATION		•			
<b>PARAMETER SWEEPS</b>					
LINEAR	•	•	•	•	•
LOGARITHMIC	•	•	•	•	•
BY MULTIPLIER		•			•
<b>COMPONENTS (BUILT-IN MODELS)</b>					
<b>PASSIVE</b>					
RESISTOR	•	•	•	•	•
CONDUCTANCE ELEMENT				•	•
CAPACITOR	•	•	•	•	•
INDUCTOR	•	•	•	•	•
TRANSFORMER	•	•	•	•	•
TRANSMISSION LINE	•		•	•	•
SWITCH				•	•
NONLINEAR CHARACTERISTIC					•
<b>SEMICONDUCTOR</b>					
DIODE	•	•	•	•	•
BIPOLAR TRANSISTOR	•	•	•	•	
JFET	•	•	•		
MOSFET	•		•	•	
OP AMP		•		•	•
<b>POWER SOURCES</b>					
BATTERY				•	•
INDEPENDENT VOLTAGE SOURCE	•	•	•	•	•
VCVS	•		•	•	•
VCCS	•		•	•	•
INDEPENDENT CURRENT SOURCE	•	•	•	•	•
CCVS	•		•	•	
CCCS	•		•	•	
PROGRAMMABLE				•	•
POLYNOMIAL	•		•	•	•
PIECEWISE LINEAR					•
ARBITRARY				•	
<b>CIRCUIT MACRO MODELS</b>	•		•	•	•

Continued on pg 190



# SURVIVAL OF THE FASTEST.

The fast succeed. The slow succumb. You can't change that, but you *can* change your system.

It starts by adding a faster controller.

Take our ACB-5585. It's the first full SCSI controller for ESMD drives. And with a data transfer rate of 15 Mb/s, it's as fast as they come.

The ACB-5585 also comes with features like 1:1 Interleave,

© 1986 Adaptec, Inc. MULTIBUS is a registered trademark of Intel Corp.

Multithreaded I/O and, of course, it supports the SCSI Common Command Set.

If ESDI is more your speed, there's our 10 Mb/s ACB-4520. It's the first noninterleaved SCSI to ESDI controller. Which makes it twice as fast as its closest competitor.

To complete the set, we offer the fastest MULTIBUS® to SCSI host adapter: the AHA-1530. It works

with either controller. And any drive.

You can put all of this speed to work for you just as soon as you get our brochure.

For your copy, call 408/946-8600, ext. 400.

Or write Adaptec, 580 Cottonwood Drive, Milpitas, CA 95035.

The faster the better.


**adaptec**



**TABLE 1—FEATURES OF REPRESENTATIVE  
ANALOG-CIRCUIT-SIMULATION SOFTWARE PACKAGES**

	E/Z CAD INC's CIRCUITPRO v 2.02 AND VIEWPLOT v 1.0	FB CIRCUIT PRODUCTS' DCIRC, ACIRC, AND TCIRC v 1.3	MICROSIM CORP's PSPICE v 2.02 AND PROBE v 1.0	SPECTRUM SOFTWARE's MICROCAPII v 2.0	TATUM LABS' ECA2 v 2.04
<b>COMPONENT-MODEL LIBRARY AVAILABLE</b>			•	•	
<b>OPERATOR INPUTS</b>					
<b>CIRCUIT DESCRIPTION</b>					
BATCH DISK FILE	•	•	•	•	•
ONLINE KEYBOARD					•
CRT SCHEMATIC				•	
<b>CIRCUIT CHANGES</b>					
BATCH DISK FILE	•	•	•	•	•
ONLINE KEYBOARD		•			•
CRT SCHEMATIC				•	
<b>ANALYSIS COMMANDS</b>					
BATCH DISK FILE	•		•		•
KEYBOARD		•		•	•
<b>SIMULATOR OUTPUTS</b>					
DISK DATA FILE	•		•	•	•
PRINTER DATA	•	•	•	•	•
PRINTER GRAPHS	•	•	•	•	•
CRT-SCREEN DATA	•	•	•	•	•
CRT-SCREEN GRAPHS	•	•	•	•	•
PLOTTER GRAPHS			•	•	
PLOTTER SCHEMATICS				•	
<b>ONLINE HELP</b>		•		•	•
<b>8087-COPROCESSOR SUPPORT AVAILABLE</b>	•	•	•		•
<b>HARDWARE ACCELERATOR AVAILABLE</b>			•		
<b>FULL NONLINEAR CALCULATIONS</b>	•		•	•	•
<b>APPROXIMATE MAX CIRCUIT SIZE</b>					
NODES, DC ANALYSIS		40		100	500
NODES, AC ANALYSIS		40		50	500
NODES, TRANSIENT ANALYSIS		40		100	500
NET-LIST ITEMS				256	2500
TRANSISTORS	120		120		
<b>LANGUAGE</b>	FORTRAN	FORTRAN	FORTRAN	BASIC	COMPILED C
<b>COPY PROTECTION</b>	•		•		
<b>MINIMUM SYSTEM REQUIREMENTS</b>					
MEMORY (BYTES)	512k	192k	512k	256k	256k
FLOPPY DISKS	1	1	1	1	1
OPERATING SYSTEM	DOS 2.0	DOS 1.1	DOS 2.0	DOS 1.1	DOS 2.0
IBM COLOR-GRAPHICS CARD	•		•	•	
8087 COPROCESSOR	•		•		
<b>PRICE</b>	\$1200	\$120	\$1400	\$895	\$450





## Put any one of our boards up against these.

Put any Hamilton Standard Digital Systems VMEbus board up against the boards in any other VME system and you'll discover the same thing we did when the architecture was designed. 100% compatibility.

Moreover, 100% flexibility.

At Hamilton Standard, we offer and service a broad, fully compatible line, including MPCPU: A multiprocessing card based on 68010 CPU that operates at 10 and 12.5 MHz. VME-I/O: An input/output user-configurable board with 512K DRAM that is based on 68000 CPU. VME 1, 2 & 4MB DRAM: Boards that utilize the latest SIP technology and provide greater density and byte parity with diagnostic support. VME-ECC: An error-checking and correcting subsystem. VME-SMD: A 68000 processor-based, storage module device controller and formatter used to interface VME systems to SMD-compatible disk drives.

For more specific needs, we also provide board- and system-customization, as well as surface-mount capabilities.

For more information, call 1-800-635-0200. Or write 1419 Dunn Dr., Carrollton, Texas 75006.





# How to convert a VAX<sup>TM</sup> Tektronix Aided Engineering



WorkSystem is a trademark of Tektronix.  
DEC, VAX, VMS, and MicroVAX are trademarks of Digital  
Equipment Corporation.  
Copyright 1985. All rights reserved.



# computer into a powerful design and test system.

A complete, fully integrated electronic design system. Running on one of the world's most popular engineering computers. Imagine what you could do with a tool like that.

And it's just one phone call away. Thanks to Tektronix.

We've implemented the entire Tektronix WorkSystem™ family on the full spectrum of VAX computers. To give you complete development support—from design capture and verification through test—all within DEC's™ VMS™ environment. That's Tektronix Aided Engineering.

The family includes WorkSystems for design, simulation and layout of standard cells, gate arrays, structured custom and full custom circuits, even PC boards. Other WorkSystems support test and measurement, and software development.

Every WorkSystem shares our unique Designer's Database that lets you partition your design, making team engineering a reality. The open architecture design of the database also allows you to interface any of your existing tools with our WorkSystems. So your prior investments in hardware and software are protected.

For all their power, Tektronix WorkSystems are surprisingly easy to learn, easy to use. And they're backed by the kind of service and support programs that you've come to expect from Tektronix.

If you haven't selected your CAE tools yet, let us help you put together the best system for your needs. Or if you already have a DEC MicroVAX II™, VAXstation II, VAX 11/750, VAX 11/780 or VAX 8600, let us turn it into a Tektronix Aided Engineering tool, right now.

Either way, the right buttons to push are 800/547-1512 (in Oregon, 800/542-1877). Or write Tektronix, CAE Systems Division, 5302 Betsy Ross Drive, Santa Clara, CA 95054.


## Push a button.



**Tektronix**  
COMMITTED TO EXCELLENCE


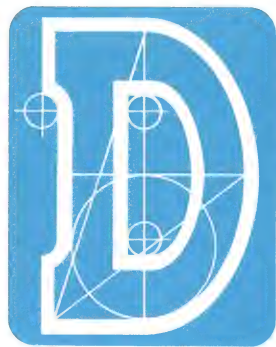
# 9 Important Reasons Why You Should Attend...



**Fall  
National Design  
Engineering Show  
& Conference™**

Jacob K. Javits  
Convention Center  
New York City  
September 16-18, 1986





# In just one day, you can:

## 1. See what's new in:

- CAD/CAM
- Mechanical components
- Electrical/electronic components
- Plastics, metals and alloys
- Fasteners and adhesives
- Power transmission
- Fluid power
- Shapes and forms
- Engineering services/equipment

## 2. Discover new ideas for improving your product designs.

Not only will you see what's new, you can discuss specific applications with technical experts at each exhibit. You'll have a rare opportunity to evaluate products through "hands-on" demonstrations and see if they satisfy your demanding design needs.

## 3. Find new sources of supply.

Meet over 400 leading original equipment manufacturers and suppliers. Shop and compare — finding just one new vendor who can save you time and money will make your trip to the Show a day well spent.

## 4. Sharpen your design skills.

Attend the ASME sponsored Conference for sessions, tutorials and ½ day short courses. Topics covered include: CAD/CAM/CAE, Finite Elements, Value Engineering, Expert Systems, Product Liability, CAE in Medical Devices and Sports Equipment, Designing with Plastics, Project Management and more!

## 5. Attend two Conference keynote sessions FREE.

All show visitors are invited to hear Diamond Star Motors' Chairman, G. Glenn Gardner, and CEO Yoichi Nakame, discuss this new Chrysler/Mitsubishi joint venture. Then, see what the future holds for CAD/CAM/CAE/CIM as Laura Conigliaro, Vice President of Prudential Bache Securities provides an in-depth analysis of this growing industry.

## 6. Visit the CAD/CAM Theatre... FREE on the Show floor.

Relax to large screen video presentations of the latest micro CAD and other computer-based systems while you take a break from visiting exhibits. Videos will run continuously each day of the Show for your viewing convenience.

## 7. Your admission to the Show is FREE!

Simply complete and mail the coupon below for your **Free Show Admission** tickets. When you arrive at the Show on September 16-18, 1986, you'll receive a **Free Show Directory** — a handy reference guide to all the exhibitors and their products.

## 8. Pick-up your Special Show Bonus!

All Show visitors will also receive a complimentary copy of the "Design Engineering Outlook," a forecast of major design engineering trends, and the effect they'll have on labor, supplies, prices, production and spending throughout the OEM.

## 9. There are *hundreds* of reasons to attend...

Clip and mail the coupon below *today* for your **Free Show Admission** tickets and discover *all* the reasons why you should attend the Fall National Design Engineering Show & Conference.™

**Don't delay — mail this coupon now for free Show admission**

(Save the \$15.00 on-site Show registration fee.)

**Mail to:**



**Fall National  
Design Engineering  
Show & Conference™**

999 Summer Street  
P.O. Box 3833  
Stamford, CT 06905-0833

☐ **YES**, please rush me \_\_\_\_\_ **free admission** Show registration tickets.

☐ I'm interested in attending the ASME Sponsored Fall National Design Engineering Conference. Please send me complete program details.

Name \_\_\_\_\_

Company \_\_\_\_\_

Street \_\_\_\_\_


City \_\_\_\_\_

State \_\_\_\_\_

Zip \_\_\_\_\_

Telephone \_\_\_\_\_



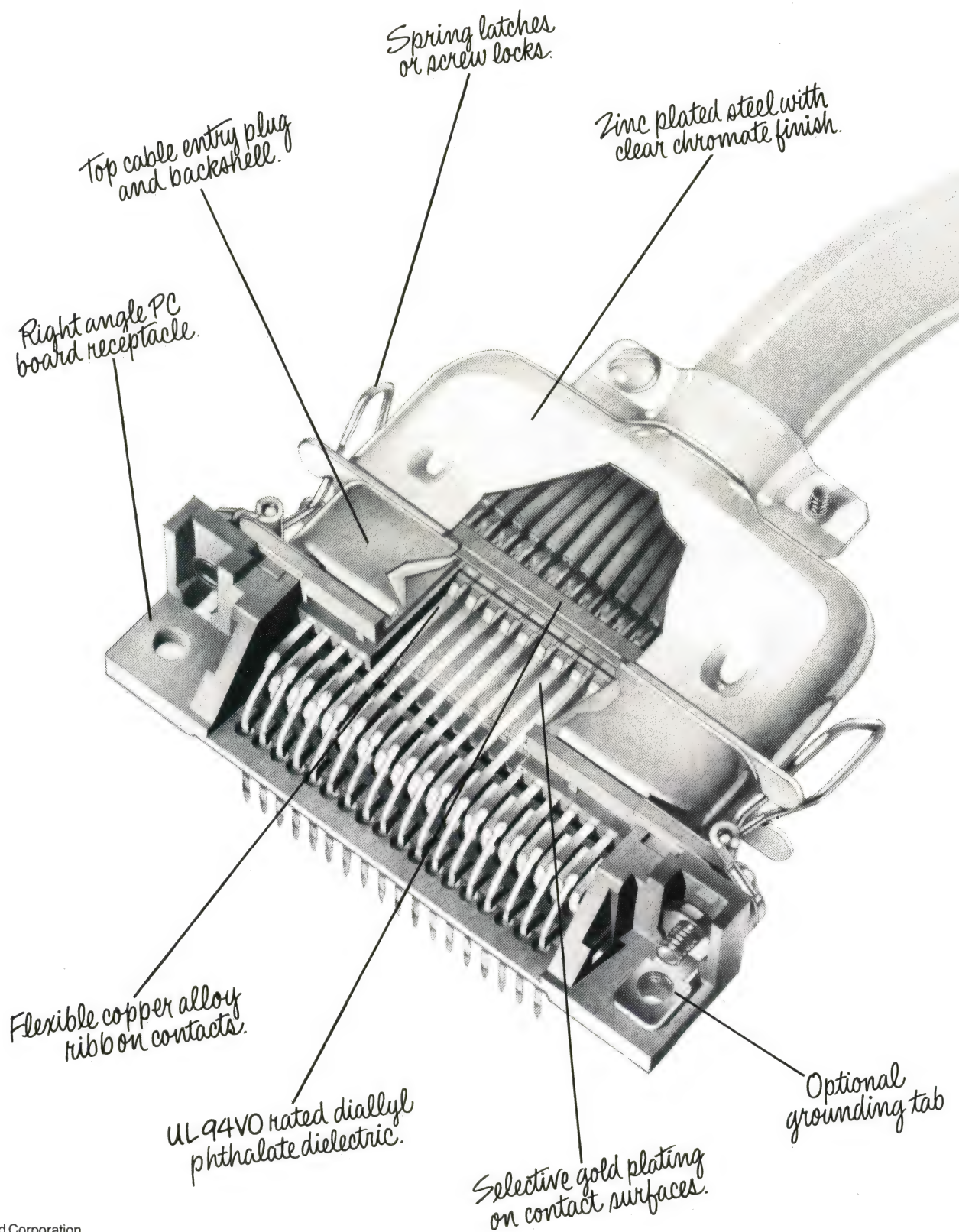



# Wrapped up: High density packaging.

## Low cost Amphenol® miniature ribbon connectors mass terminate, shield or filter up to 64 contacts.

The wide choice of miniature ribbon connectors available from Amphenol Products makes it easy for you to secure the right input/output connection for telecommunication, computer, business and test equipment.

When durability and EMI/RFI shielding are required choose steel shelled 57 Series Micro Ribbon® connectors for solder termination, or 157 Series Micro-Pierce® connectors for solderless IDC termination.

To meet tough EMI/RFI requirements like FCC Docket 20780, choose Amphenol FCC Micro Ribbon filter connectors. With chip capacitors that shunt EMI/RFI noise to ground and remove it from the signal, these connectors save up to half the cost of competitive models.

When economy and easy assembly are prime considerations, low cost Amphenol plastic body connectors are your logical choice.

Our new 50 contact, running cable IDC connector, for example, features an all plastic body and hood plus a snap-in latching mechanism that secures without screws.

Other models combine plastic with metal front shell construction for economy and shielding capabilities.

All feature time-proven flexing action contacts with selective gold plating for easy mating and reliable electrical continuity.

For more information, contact your nearest Amphenol Products sales office.

**Amphenol Products world headquarters:**  
Lisle, IL 60532—USA—Telex: 190-215

**CANADA:** Montreal, (514) 482-5520 • Ottawa, (613) 226-2727 • Toronto, (416) 291-4401 • Vancouver, (604) 278-7636

**EUROPE:** Austria—Vienna, (0222) 925166. • England—Whitstable, (0227) 264411. • France—Paris, (01) 5888682. • W. Germany—Heilbronn, (07131) 4861. • Italy—Arese, (02) 9385161. • Netherlands—IJsselstein, (03408) 87844. • Sweden—Upplands Väsby, (0760) 88035.

**FAREAST:** Hong Kong—Kowloon, (3) 681283. • India—Poona, 83363. • Japan—Tokyo, (03) 379-2111.




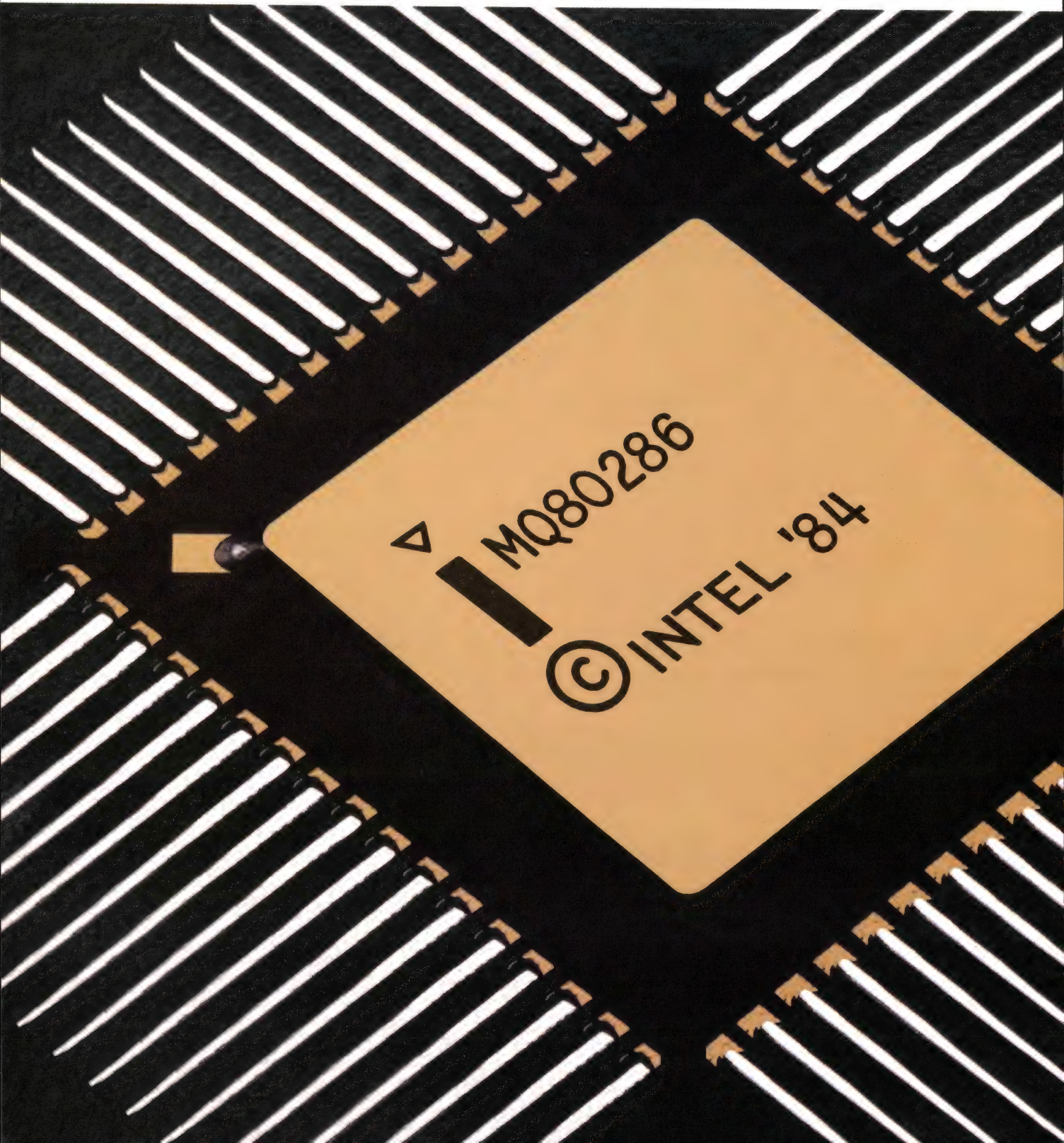**ALLIED**

**Amphenol  
Products**



**HOW TO RESPOND  
978 MICROSECONDS FASTER  
THAN THE ENEMY.**





It's only the blink of an eye. Not even that.

But an awful lot can happen in the blink of an eye these days.

And to get that crucial edge is very easy. Just see to it that the military grade microprocessor you design

in has complete hardware support for multitasking built right into the chip.

Ours does. So it's lots faster than trying to do task switching in software.

978 microseconds faster, to be exact.

Which means you can complete a full task switch in 22 microseconds flat (at 8 MHz). Instead of the millisecond it can take with a software solution.

98 percent more time for your system to respond. Giving you the advantage you need in an increasingly demanding tactical environment.

And because our M80286 chip is based on Intel's high-performance M8086 microprocessor architecture, you are assured of the most powerful and easily upgradable engine available for military designs.

Included in the CPU is a memory management unit that equips the M80286 with hardware support for virtual memory and software protection. Making it ideal for military applications that require processing of massive amounts of information.

Performance is enhanced by exclusive pipelining features that eliminate delays in execution time. So the M80286 can do more instructions per clock than


any other CPU.

System throughput can be further increased with our broad base of peripheral products. Such as our 80287 coprocessor and 82720 graphics controller. These chips are specifically designed to offload the numerics and graphics functions from the CPU.


In addition, the M80286 is optimized for higher level languages such as ADA.

#### ACHIEVING PERFORMANCE MEMORY MANAGEMENT

Traditional Technique

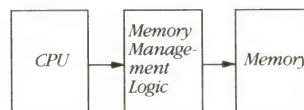

M80286 Technique

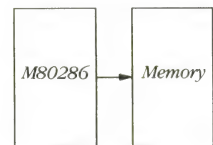

*M80286 integrated Context Switch, memory management and protection offers a fast, consistent, and highly portable multitasking solution.*

With ADA 286, designers can get greater systems flexibility and maximum performance.

And tomorrow? As your military system requirements grow, an upgrade path based on the same high performance architecture of our M80286 will be available with our 32-bit M80386 microprocessor.

For further information, call toll-free (800) 548-4725. Or write Intel Corporation, Lit. Dept. W281, 3065 Bowers Ave., Santa Clara, CA 95051.

We'll get back to you. Faster than you can blink an eye.

**intel®**



# EPLD macrocells and feedback signals ease circuit design

---

*The AND arrays, programmable macrocells, and feedback paths of an erasable programmable-logic device augment your ability to design general-purpose logic circuits. Designs based on the device can perform their functions with fewer components than corresponding discrete-IC implementations.*

---

Don Faria, Altera Corp

New erasable programmable-logic devices (EPLDs) contain several design features that now let you implement sequential circuits in addition to combinatorial circuits. Among these features are AND arrays for combinatorial logic, programmable output cells for flip-flops and drivers, and feedback paths. The programmable feedback and output features enhance the basic product-term array common to many PLDs, allowing the EPLD to implement such noncombinatorial circuits as counters and state machines. An implementation of an EPLD as a motor controller illustrates the use of EPLD features.

Of course, before you decide that your design is a suitable candidate for an EPLD, you must determine whether a sufficiently large EPLD exists to support your design. EPLDs come in many sizes, varying in the number of inputs, outputs, product terms, and macrocells available. You first compare your I/O, flip-flop, and clock-frequency requirements with the specifications of


available devices. If you find an EPLD that looks promising, you then attempt to complete the design using PLD-design software. This software attempts to compile your design into EPLD code. When you have corrected any design errors identified by the compiler, the EPLD can implement your design. Design compilation takes minutes, so you can attempt several iterations of your design in pursuit of a fit to a particular EPLD.

EPLD circuitry consists of macrocells that contain an AND/OR array, output and feedback selection, and interconnecting signals. The AND/OR array consists of input signals that form product terms (AND gates) connected to an OR gate. An EPLD designer creates the pattern in each macrocell that realizes the desired logic function. The designer switches an interconnecting transistor by applying a charge to the transistor's floating gate, and this action controls the connection between an input signal and a product term. Typical EPLDs have 18 to 64 inputs and 74 to 480 product terms.

EPLD I/O circuitry contains a flip-flop, feedback, and output-selection circuitry. You program outputs from the logic array so that they connect to the macrocell I/O architecture. The macrocell I/O can store the values of the logic array and also drive the value back into the logic array via feedback circuitry. You can also program the macrocells to drive values to output pins via output circuits.

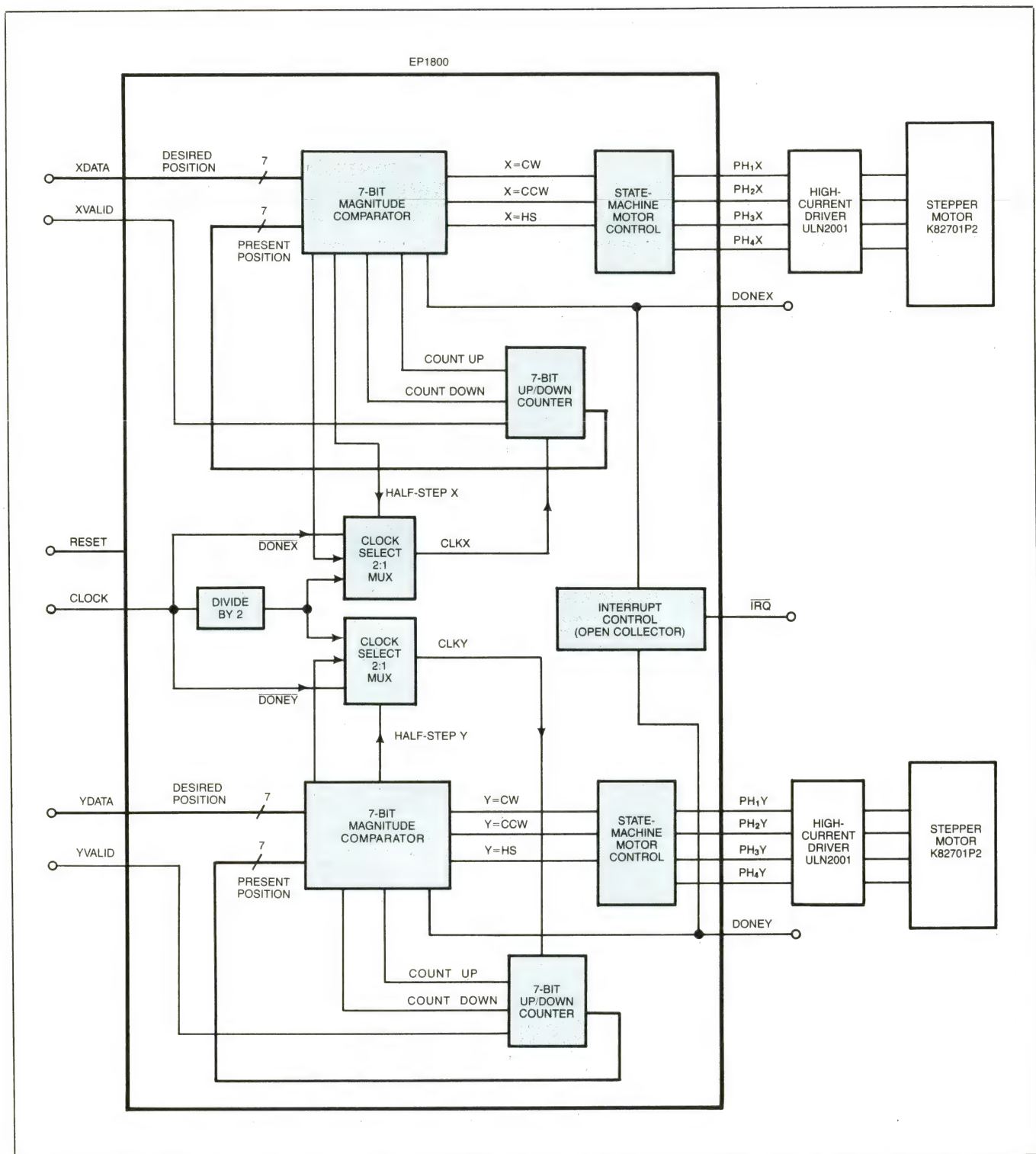The motor-positioning circuit shown in **Fig 1** illustrates how a logic design can employ the macrocell circuits of an EPLD. The motor controller is called an X-Y positioner because, in a 2-D plane of motion, it

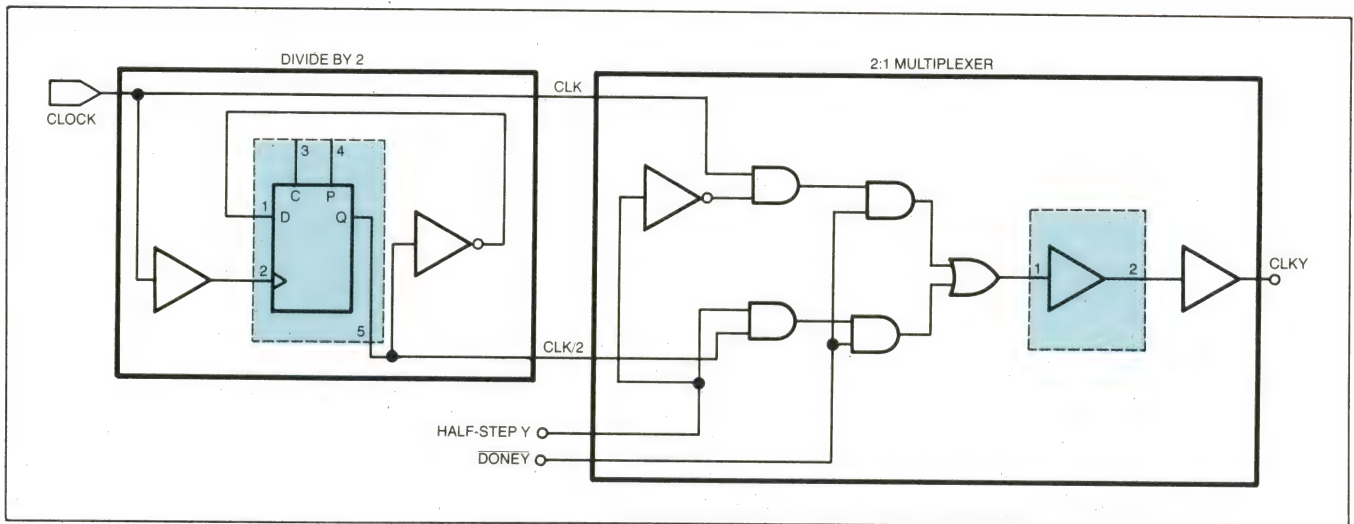




**Fig 1—An EPLD implementation of a motor-positioning circuit** illustrates the use of many features of the EPLD. The circuit compares desired stepper-motor coordinates with actual coordinates and generates the appropriate signals to drive the motors to the desired coordinates. The EPLD's logic plane, feedback features, and output selection can implement all of the circuitry of the positioner on one chip.



*The feedback macrocell features enhance the basic logic array to implement such non-combinatorial circuits as counters and state machines.*



**Fig 2—The macrocells' input and feedback options, exploited in this clock circuit, allow you to connect an input directly to a macrocell and to feed back a macrocell output to the EPLD's logic array. This figure shows the Y-axis clock circuit; the X-axis clock circuit is identical.**

controls one motor on the X axis and one on the Y axis. The positioner accepts inputs, from a  $\mu P$ , that describe the desired X and Y coordinates, and it also determines the necessary action of the motors. It then drives control signals to two 4-phase stepper motors to achieve the new position. In addition, the positioner requires a 500-Hz clock input and a reset signal to indicate the initial "0,0" position.

The positioner circuit in this example is an Altera EP1800 EPLD (see **box**, "Programmable macrocells yield flexible EPLDs"). The positioner drives the two stepper motors through ULN2001 high-current drivers. The drivers convert the controller's TTL-level outputs to the drive signals required for the motor control. The stepper motors, Airpax K82701P2s, step in 7.5° increments. To implement full and half steps, the controller must designate 96 distinct motor positions for each axis. To distinguish 96 positions, the minimum number of control bits for the X and the Y axes is seven ( $2^7=128$ ).

In addition to motor-control signals, the controller furnishes two outputs, DONEX and DONEY, that indicate when the positioner has driven the motors to the desired X and Y coordinates, respectively. When this action is complete, the interrupt output (IRQ) sends signals to the system controlling the positioner. The positioner is then ready to accept the next set of desired coordinates.

Within the controller, two identical logic circuits keep track of the positioner's actual coordinates, compare the actual and desired coordinates, and translate the

required movement into the appropriate 4-phase stepper-motor signals. A clock circuit supplies a 500-Hz clock signal for full-step movement and a 250-Hz clock signal for half-step movement.

**Fig 2** shows the Y-axis clock circuitry in the position controller (the X-axis clock circuit is identical). The circuitry consists of divide-by-2 logic and a 2:1 multiplexer. The clock signals drive the flip-flops in the controller's up/down counter. In half-step mode, the 250-Hz clock signal slows the change of position reflected in the counter compared with the rate of change dictated by the 500-Hz clock. At any given time, the multiplexer routes one of the two clock signals to the counter, depending on whether the controller is in half-step or full-step mode.

### Macrocells make versatile clock circuit

The clock circuitry exploits two features of the EPLD's macrocells: Inputs to macrocells can be chip inputs or internal feedback paths, and the macrocells can drive signals back into the logic plane. (The solidly lined boxes in **Fig 2** show EPLD macrocells.) The clock input comes straight into the divide-by-2 circuit's macrocell through the logic plane. Alternatively, you could connect the signal with other signals via an AND gate to create a composite clock. The circuit routes the output of the divide-by-2 flip-flop back into the logic plane to form one of the clock inputs (CLK/2) to the multiplexer. The output also feeds back through an inverter to the D input of the flip-flop.


The multiplexer logic, unlike the divide-by-2 logic,

*Text continued on pg 207*







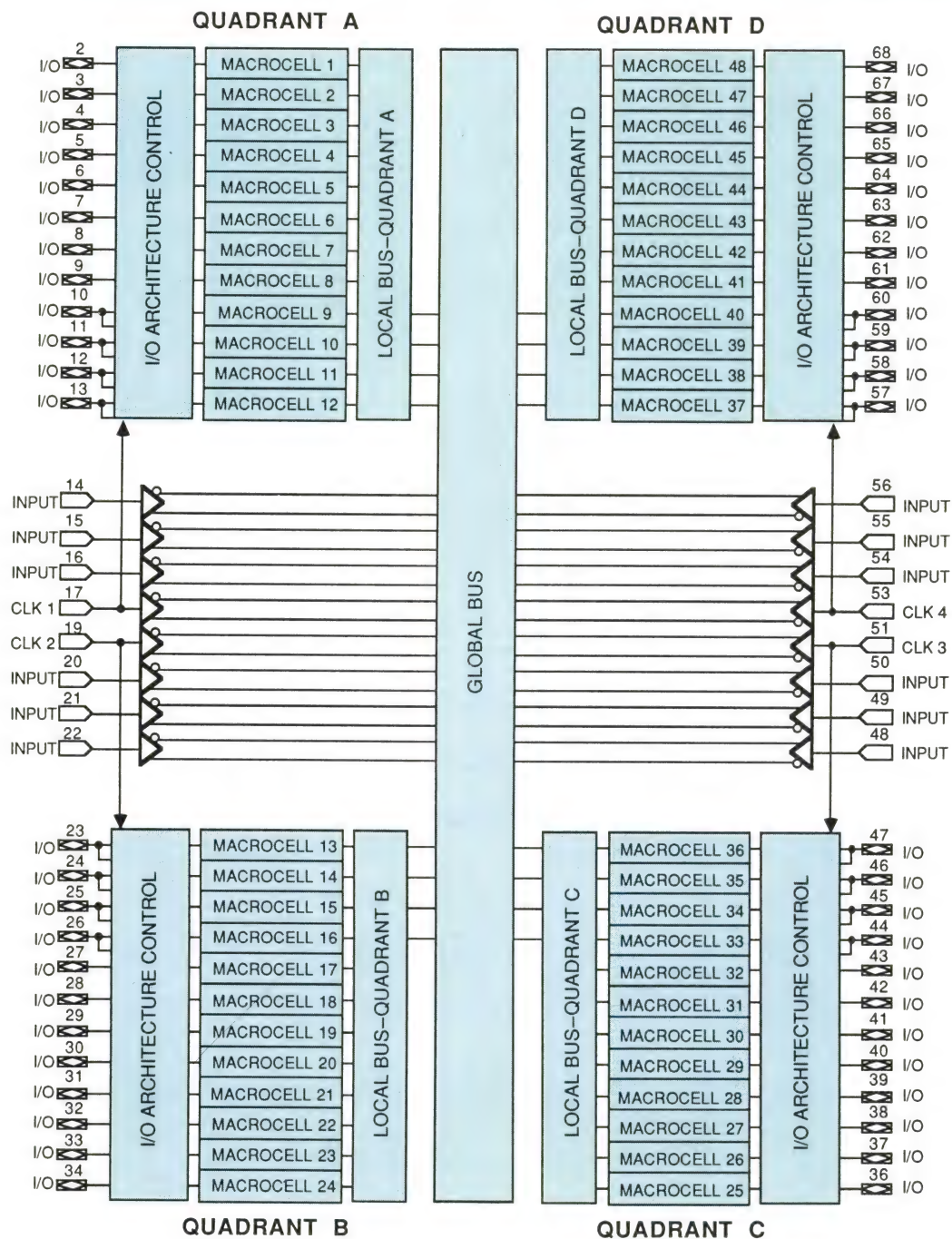

**Fig A—Buses, macrocells, and I/O control logic** combine to form the EP1800 architecture. All inputs travel to all macrocells through the global bus; macrocells contain logic arrays and storage elements. Feedback within quadrants occurs via the local bus and global bus. Feedback and output circuits reside in the I/O-architecture control logic.



## Programmable macrocells yield flexible EPLDs

The EP1800 EPLD comprises a logic array and programmable macrocells. It contains circuitry that's equivalent to approximately 2100 2-input gates, a degree of complexity normally associated with gate arrays. In addition to having an order of magnitude more logic than traditional 20- and 24-pin fuse programmable bipolar PLDs, the EP1800 includes programmable features that make it more flexible than the bipolar PLDs for implementing general-purpose logic circuits:


- Transition-sensitive input circuits allow the internal circuitry of the device to remain in a quiescent mode when the inputs aren't changing. The quiescent mode consumes less power than circuits that are continuously in an on state.
- You can program each of the EP1800's 48 macrocells to operate as a D, J-K, set-reset, or T flip-flop.
- You can program the macrocells to implement a variety of feedback paths. Sixteen of the macrocells can implement two feedback paths, providing both a flip-flop and a connection to an input pin.
- You can program the chip's four clock circuits for synchronous or asynchronous operation.
- Some macrocells provide feedback paths to nearby macrocells, and some

macrocells provide feedback to all macrocells. The global feedback helps to minimize the propagation delay required when one signal must drive all of the macrocells.

The diagram of the chip's architecture (**Fig A**) shows the interconnections of the device's circuitry. A global bus connects the input signals and global feedback lines to four macrocell quadrants. Each quadrant contains 12 macrocells, a local bus, and I/O-architecture control logic. The local bus connects signals from the macrocells to establish feedback lines within each quadrant. I/O architecture


can create combinatorial logic or one of four types of flip-flops for output circuitry.

The EP1800's 68-pin J-lead carrier incorporates a window for ultraviolet light erasure (**Fig B**). The EPLD in this package costs \$90. You can order one-time-programmable devices in plastic, windowless packages for \$42 each. Both prices are for 100-piece quantities. Production volumes will be available in the third quarter of 1986.

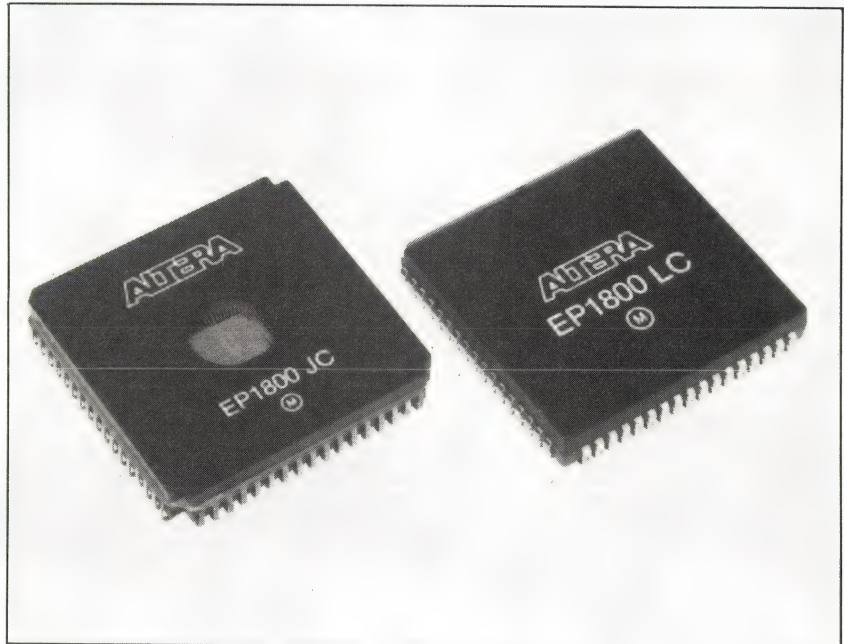

**Fig B**—A 68-pin J-lead carrier with a window (left) allows you to erase the EP1800 under an ultraviolet lamp. A less-expensive carrier without a window (right) is available for production volumes.



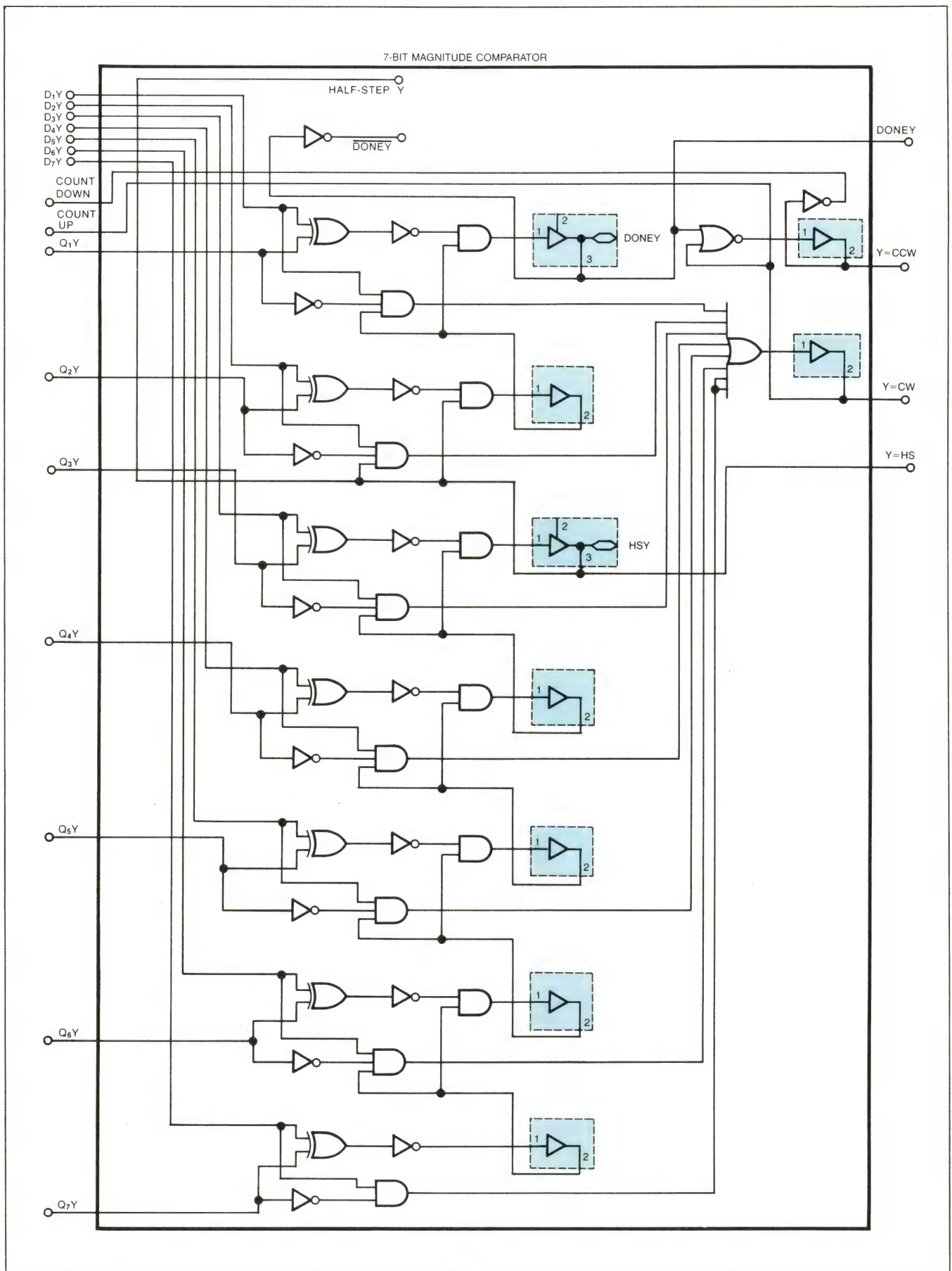

**Fig 4—When actual and desired motor positions are unequal, the magnitude comparators generate a CW or CCW signal to actuate the motor-control state machine. The half-step signal (HS) indicates that the five MSBs are equal; DONEY indicates that all bits are equal (ie, the motor is at the desired position).**



*A design for a motor-positioning circuit illustrates how your logic design can exploit the logic and I/O circuits of an EPLD.*

uses the combinatorial nature of the logic array. All of the logic between the multiplexer's clock inputs and the OR gate's output maps onto the logic array. Because both true and inverted versions of all inputs are available, Boolean logic guarantees that all combinatorial logic can be reduced to two levels of gates, allowing you to implement the logic in sums of products in the logic plane. The A+Plus support software does this logic reduction automatically. The multiplexer macrocell, unlike the macrocell in the divide-by-2 logic, serves only to select either the CLK or the CLK/2 signal for the CLKY output.


### Counter uses feedback capability

The positioner's up/down counter keeps track of the actual position of the motors with respect to the desired position (**Fig 3** shows the counter for the Y axis). Like the multiplexer, the counter makes use of the EPLD's logic array. The counter begins at zero and counts up or down, depending on whether the count-up or count-down input is valid. Remember that the positioner's clock signal toggles only when the desired position is not the same as the actual position. Also, the data-valid input for Y-axis positioning, DVALIDY, enables the first flip-flop in the counter only when new data is valid at the Y-data input.

When DVALIDY goes high, the counter begins to count. The flip-flop at the top of the figure toggles and supplies both the LSB of the position and a signal that enables the rest of the counter's stages. The count-up and count-down inputs control these stages as well, designating which flip-flop in the counter will toggle next. As is the case with the multiplexer, the EPLD's logic array implements the combinatorial logic. Although the last stage contains the most inputs to an AND gate—eight—of any stage in this counter, the EPLD can implement more than 10 times that number of inputs to one AND term.

The reset signal in the counter presents an application of the dual-feedback capability of the EPLD. In the counter circuit, the reset signal connects to all of the flip-flops. The macrocell distributes the reset signal internally to all the flip-flops. In addition, within the macrocell, one of the counter's flip-flops feeds its Q output back into the logic array. Thus, a single macrocell is used for internal logic functions (counter-stage) and also for a dedicated input function (reset).

The positioner's magnitude comparators compare the desired motor position with the actual motor position (**Fig 4** shows the Y-axis comparator). When the desired

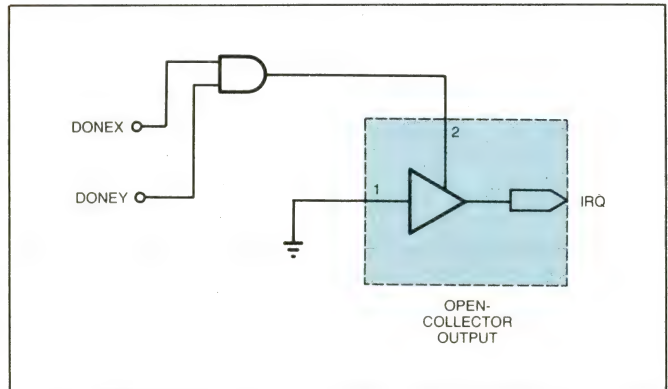

**Fig 5—Any macrocell can implement an open-collector output, allowing direct connection to a controller. The connection is typically a microprocessor interrupt-request line.**


position of the Y-axis motor (designated as inputs  $D_1Y$  through  $D_7Y$ ), for example, is different from the actual position recorded in the up/down counter ( $Q_1Y$  through  $Q_7Y$ ), the comparator generates signals that indicate the required motor movement:  $Y=CW$  for clockwise movement,  $Y=CCW$  for counterclockwise rotation,  $Y=HS$  for half-step rotation, and DONEY, of course, to indicate that the rotation is done and the actual and desired positions are the same.

The XOR gates in the comparator compare all of the bits from the desired and actual position inputs in order from the MSBs ( $D_7Y$  and  $Q_7Y$ ) to the LSBs ( $D_1Y$  and  $Q_1Y$ ). If, for example, all bits but the LSBs are equal, the XOR gates in each stage ripple an enable signal through to the last stage, enabling comparison of the LSBs. The difference between the actual and desired LSBs forces the positioner to generate one more signal. Once all bits are equal, the comparator generates the DONEY signal.

The circuit also compares the relative magnitude of the desired and actual positions. Thus, to move the motor toward higher desired values, the comparator circuit generates a CW signal. If the desired position has a lower value than the actual position, the comparator generates a CCW signal. As you can see from **Fig 4**, the logic that determines whether the comparator will generate a CW or a CCW signal begins with the connection of the desired MSB ( $D_7Y$ ) and the complement of the actual MSB ( $Q_7Y$ ).

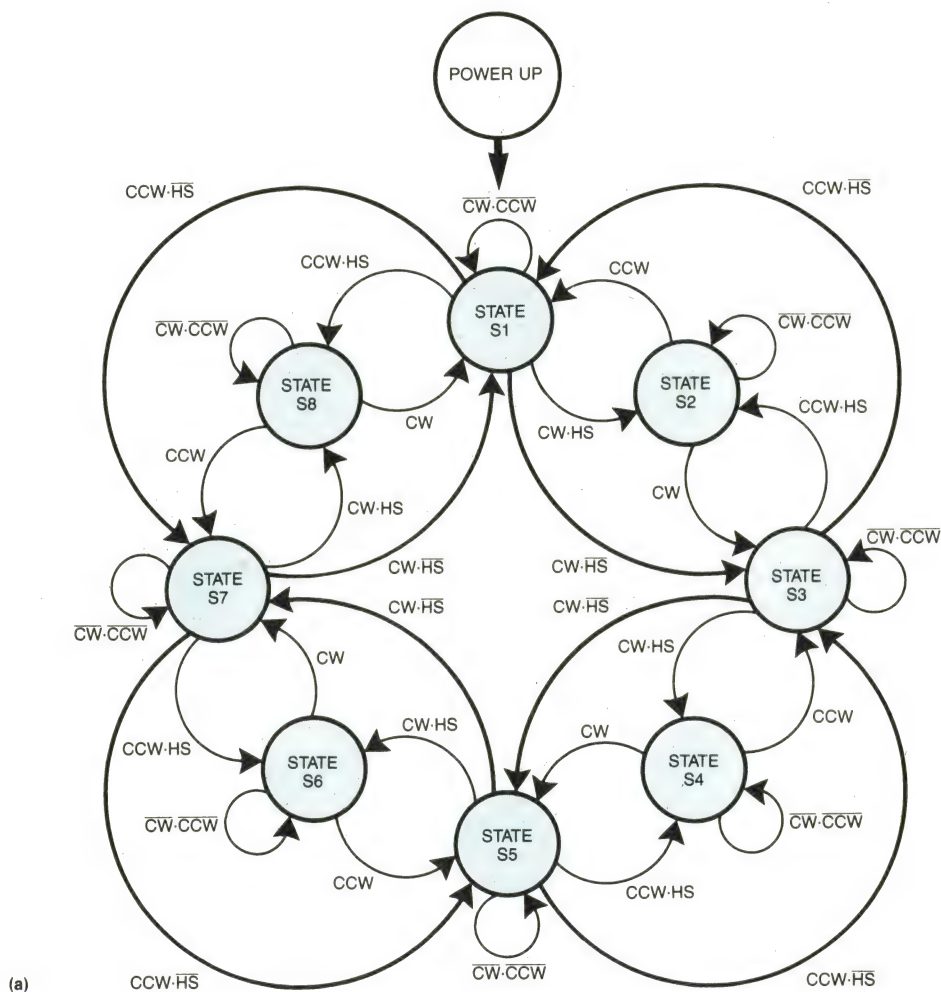The comparator also generates a half-step signal (HS) that slows the rotation of the motors as they near their desired positions. The signal goes high when the five MSBs are the same. HS connects to the clock multiplexer and allows the half-step clock signal, in-





(b)

# STEPPER MOTOR CONTROLLER

PART: EP1800

INPUTS: CW % CLOCKWISE ROTATION ENABLE %  
 CCW % COUNTER CLOCKWISE ROTATION ENABLE %  
 HS % ROTATE 3.75 DEGREE STEPS %  
 CLKY % CLOCK %

OUTPUTS: PH1Y PH2Y PH3Y PH4Y % MOTOR WINDINGS %

MACHINE: STEPPER\_MOTOR\_CONTROLLER

CLOCK: CLKY

STATES: PH1Y PH2Y PH3Y PH4Y

PU	0	0	0	0
S1	1	0	1	0
S2	1	0	0	0
S3	1	0	0	1
S4	0	0	0	1
S5	0	1	0	1
S6	0	1	0	0
S7	0	1	1	0
S8	0	0	1	0

% FOLLOWING ARE STATE TRANSITIONS DEFINITIONS.  
 IN ALL CASES AN ELSE HOLD IS IMPLICIT. %

```

PU:
S1:
  IF CW*/HS THEN S3
  IF CW*/HS THEN S2
  IF CCW*/HS THEN S7
  IF CCW*/HS THEN S8

S2:
  IF CW THEN S3
  IF CCW THEN S1

S3:
  IF CW*/HS THEN S5
  IF CW*/HS THEN S4
  IF CCW*/HS THEN S1
  IF CCW*/HS THEN S2

S4:
  IF CW*/HS THEN S5
  IF CW*/HS THEN S3

S5:
  IF CW*/HS THEN S7
  IF CW*/HS THEN S6
  IF CCW*/HS THEN S3
  IF CCW*/HS THEN S4

S6:
  IF CW THEN S7
  IF CCW THEN S5

S7:
  IF CW*/HS THEN S1
  IF CW*/HS THEN S8
  IF CCW*/HS THEN S5
  IF CCW*/HS THEN S6

S8:
  IF CW THEN S1
  IF CCW THEN S7

ENDS
  
```

**Fig 6—A state diagram (a) describes the motor-control logic, and EPLD-design software A+Plus automatically converts the state-diagram description (b) into appropriate programming to implement the logic in the EPLD. The logic converts the outputs of the comparator ( $Y=CW$ ,  $Y=CCW$ , and  $Y=HS$ ) into the control signals that drive the stepper motor.**



*The clock input comes straight into a macrocell through the logic plane. You could also connect the signal with other signals via an AND gate.*



**Fig 7—A pinout drawing of the completed design** is one output of the EPLD design software, A+Plus. Once you've completed your logic design, the software automatically assigns signals to pins and creates a hard-copy report on chip utilization.

stead of the system clock signal, to pass through the multiplexer.

An AND gate generates an interrupt signal ( $\overline{IRQ}$  in Fig 5) when the DONE<sub>X</sub> and DONE<sub>Y</sub> signals from the positioner's two comparators are both high. The  $\overline{IRQ}$  logic is unremarkable except that, because it connects directly to a microprocessor or controller, it's the only positioner signal that requires an open-collector output. Therefore, the macrocell that drives the  $\overline{IRQ}$  signal off chip implements a grounded driver to provide the open-collector output.

### State machine describes motor control

The final part of the positioner's circuitry translates the outputs of the comparator—CW, CCW, and HS—into the control signals that are required to drive the stepper motor. Control of the stepper motor is highly sequential: The motor has clearly defined operational states that the positioner must control in order to rotate the motor to the desired position. You can describe these sequential circuits as a state machine that accepts the comparator outputs and generates the

four phase signals that control the stepper motor. The state-machine design can be an easier approach to designing sequential circuits than trying to create a logic diagram.

The positioner's state machine (Fig 6a) contains all of the states and transitions possible for the stepper motors (as defined in the motor's specifications). You can follow the operation of the motors by starting in any state and tracing the next state depending on the inputs from the comparator. For example, the positioner initializes to the first state (S1), and it can then go to one of five possible states, depending on the values of CW, CCW, and HS. Each state represents a specific combination of the outputs (PH<sub>1</sub>Y through PH<sub>4</sub>Y and PH<sub>1</sub>X through PH<sub>4</sub>X). Available personal-computer-based software, A+Plus, accepts this state-machine description (Fig 6b) and converts it into the appropriate programming code to implement the state machine on the EPLD.

Once you've entered the entire design (as logic schematics and a state machine), the design software creates an output that automatically assigns pins and produces a hard copy of the device's pinouts (Fig 7). The software also produces a report that describes the utilization of the chip's resources. The positioner example uses 47 of the chip's 48 macrocells, a relatively good utilization of the chip. Also, your savings in board real estate are significant: A discrete-IC implementation of this stepper-motor controller would contain six MSI functions—the counters, comparators, and multiplexers—and dozens of SSI devices that the EPLD implementation does not require.

**EDN**

### Author's biography

Don Faria is an applications engineer with Altera Corp (Santa Clara, CA). He holds a BSEE degree from the University of Massachusetts and is currently pursuing an MSEE degree at the University of Santa Clara. Prior to joining Altera, he spent three years at Hewlett-Packard, where he was involved in semicustom-IC development. Don enjoys skiing, white-water rafting, and tracing the southern migration of elephant seals.




Article Interest Quotient (Circle One)  
High 479 Medium 480 Low 481





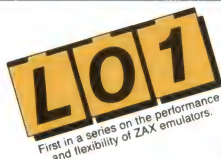CART/PPG World Champion Al Unser and his Pennzoil Z-7/Penske Racing March 85C. Photo by Doug Peacock.




## How The Brakes On This Race Car Helped Us Design The Brakes On Our Emulator

### Beware The Brakes of March

Al Unser's winning March 85C is an incredible piece of racing machinery that's as fast as the wind. But to repetitively slow the yellow bullet from speeds over 200 mph requires the presence of a supreme braking system. One that's infinitely adjustable by the user, easy to maintain and utterly dependable. Fortunately, racecars don't have a lock on superior design parameters, so we at ZAX duplicated the same ideas when we engineered the breakpoint system of our ICD-series in-circuit emulators.
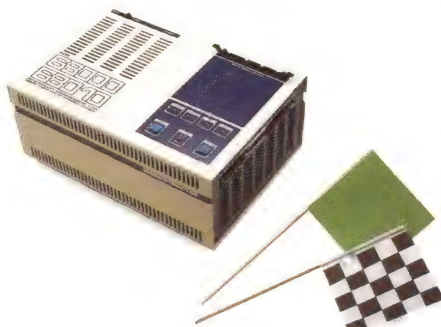
### Breakpoints: Making an Emulator Stop as Well as It Goes

Most emulators are fine at executing prototype software programs and testing hardware—until a bug rears its head. Then it gets tough. But a flexible breakpoint system can help eliminate the time and tedium involved in tracking down the deepest bugs. The problem is, most emulator's breakpoint mechanisms just don't grab you. But ours are different.



"Simplicity to start fast,  
Power to finish first"

### ZAX Emulators: The Definition of a Flexible Breakpoint System

Each of our ICD-series emulators feature a breakpoint system that lets you run your prototype in real time and then stop on a variety of parameters to pinpoint the trouble fast. You can specify to break on a single address or address range, data or memory type; in sequential priority; on the Nth occurrence; when accessing a non-memory area; when writing to a read-only area; when an interrupt occurs; on different wait-states; and from sensing an external trigger. Four hardware and eight software breakpoints can be named, and an unlimited number of breakpoints can be assembled into the user program as well. Now that's flexibility!

For information on other ZAX emulator features and news about our entire product line, call us at ZAX Corporation, 800-421-0982, 714-474-1170 in California. Or write: ZAX Corporation, 2572 White Road, Irvine, CA 92714.

**ZAX**  
Zax Corporation

CIRCLE NO 152




**"WHAT'S NEW FROM TEXAS INSTRUMENTS?"**

# IMPACT PROMs that boost speed by 29% or cut power by 43%.

- New PAL ICs, interface devices, "flash" shifter also utilize high-speed, low-power IMPACT process.
- New EPROM microcomputer, cost-effective replacement for masked ROM, slashes prototype cycle time.
- New list of 681 military ICs compliant with MIL-STD-883C, Paragraph 1.2.1.

And much more, inside ►

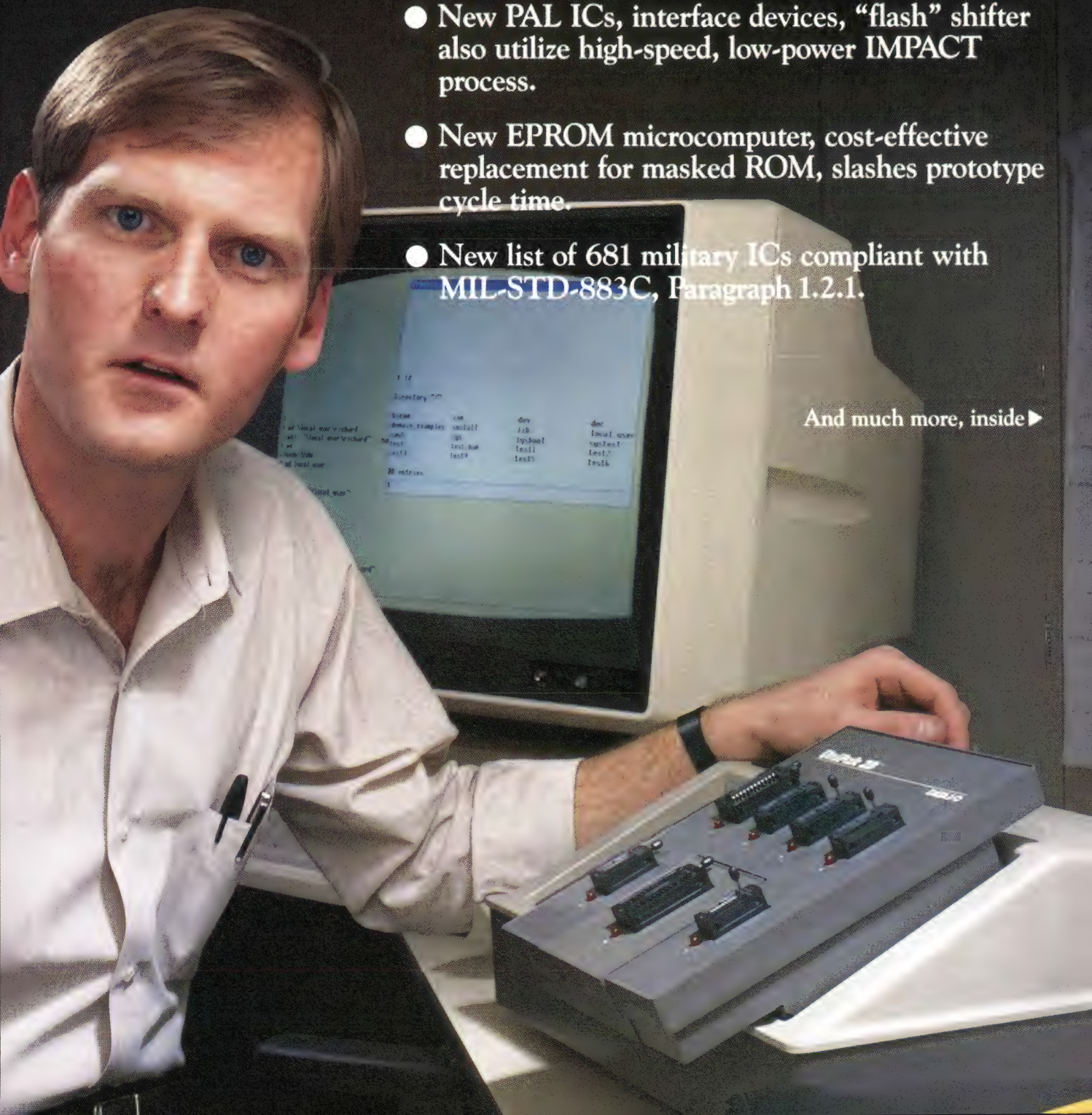



# IMPACT PROMs deliver 25-ns speed at industry-standard power.

New Series 3 IMPACT™ PROMs from Texas Instruments make 16K-memory performance upgrades quick and easy. If speed is your most critical parameter in a high-complexity PROM, you can achieve it now without paying a power penalty. Just design in TI's new 25-ns, 175-mA IMPACT PROMs: The TBP38S165-25 (2K × 8) or the TBP34S162-25 (4K × 4).

Or use the world's fastest 16K registered PROMs. TI's TBP34R165-18 (2K × 8), with a minimum address-to-clock setup time ( $t_{su}$ ) of only 18 ns, is nearly  $2\frac{1}{4}$  times faster than the closest competitor. And the TBP34R162-30 ( $t_{su}$  = 30 ns) is the only 4K × 4 registered PROM on the market.

## Standard speed at 43% less power

You can also cut power without sacrificing speed, using TI's new TBP38L165-35 IMPACT PROM. It is pin-for-pin compatible with existing 2K × 8 PROMs and operates at the same 35-ns speed, but instead of 175 mA, it draws only 100 mA. TI's broad family of Series 3 IMPACT PROMs also includes 256-bit, 1K and 2K devices.

## Reliability built in

IMPACT PROMs are designed by TI for exceptional reliability. Current densities, metal spacing, and contact sizes are all conservatively designed. Electrostatic-discharge tolerance up to 4,000 V

is designed in. During programming, TI-developed titanium-tungsten fuse links insulate themselves with titanium-oxide caps. Electromigration is eliminated by copper-doped aluminum in the first-level interconnection. And you can program any of TI's new Series 3 PROMs on widely available commercial equipment, using TI's standard Series 3 programming algorithm.

## Shift 32 positions in less than 29 nanoseconds.

Now TI's 2- $\mu$ m IMPACT technology also brings you high-speed "flash-shift" operations — with the new 74AS8838 32-bit barrel shifter. Shifting as many as 32 positions in a single 29-ns instruction cycle, it can dramatically increase throughput in such applications as graphics systems, wide-word CPUs, and array processors. At an energy cost of less than 1.5 W, you get higher speed with lower power, in a single 84-pin ceramic pin-grid-array package.

You can program the 74AS8838 for logical, circular, or arithmetic shifts. Its two 3-state, 16-bit outputs give it the versatility to be configured as a 32-bit-in, 32-bit-out barrel shifter, as a 16-bit funnel shifter, or as a 16-bit shifting transceiver. And it can drive buses directly with 24-mA low-level output — with no additional circuitry.

The 74AS8838 barrel shifter, first

device in TI's 74AS88XX 32-bit processor chip set, is available today through your local authorized Texas Instruments distributor.

## IMPACT technology doubles speed of new PAL ICs.

Four new exclusive-OR programmable-array logic (PAL®) ICs from TI feature the highest speed available today. Their 20-ns propagation delay at 180 mA makes them twice as fast as any comparable devices.


These devices — TIBPAL20L10-20, TIBPAL20X4-20, TIBPAL20X8-20, and TIBPAL20X10-20 — are designed primarily for counter-intensive applications. The exclusive-OR feature suits them ideally to digital voice applications and video-screen information correction. They can also be useful in memory addressing and mapping.

## Programmable logic sequencer is 250% faster because of IMPACT processing.

Still another new product in TI's growing line of high-speed programmable logic devices is the TIB82S105B. At 50 MHz, it is  $2\frac{1}{2}$  times as fast as functionally equivalent  $16 \times 48 \times 4$  field-programmable logic sequencers — at the same 180-mA power. Unlike them, however, it maintains that speed even when using many product terms.

Because of its improved clocking scheme, the IMPACT TIB82S105B is not a direct replacement for the TI or Signetics N82S105A. But it is ideal for those new high-speed state machines designed to control peripheral I/O, dynamic memory systems, and video blanking systems.

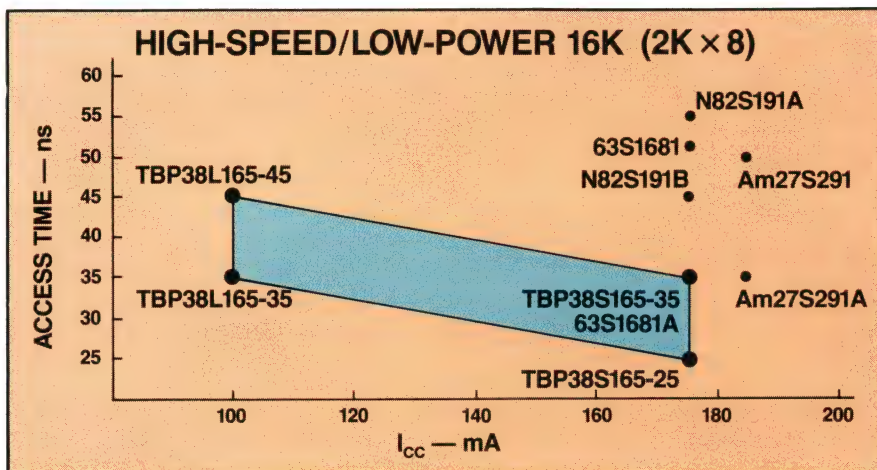For more detailed information about any of TI's growing line of high-speed, low-power IMPACT products, just check the appropriate box on the attached reply card and return it to TI.



Bracketing the speed/power spectrum, TI's IMPACT PROMs cut power requirements from 180 to 100 mA for "standard" 35- to 45-ns access time. Or at 180 mA, they can give you 25-ns speed.



# High-density IMPACT circuits speed logic, memory access.


**TI's** unique *Im*planted *Ad*vanced *Com*posed *Techn*ology (IMPACT) capitalizes on the advantages of ion implantation, oxide isolation, and composed-masking techniques to increase the speed and density of bipolar ICs.

This innovative technology dramatically reduces the size and the sidewall capacitance of circuit elements (see diagram). As a result, speed/power ratios are significantly improved: In PROMs that cut power consumption by 43%, or more than double the speed (see story opposite). In PAL ICs that reduce propagation delay by as much as 40% — to only 15 ns at 180 mA.

With the high speed and low power that TI's IMPACT process makes feasible, its potential for large-scale integration will reduce package counts in many high-complexity circuits.
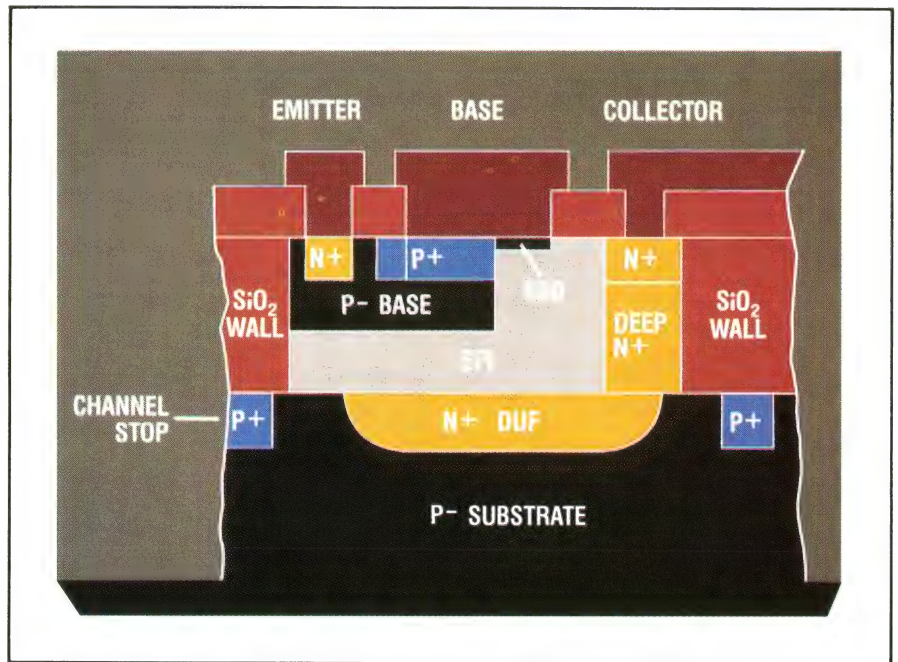
## Composed masking yields high density

In composed masking, critical components are defined on the chip with a minimum number of masks. Thus they can be more tightly defined and more densely spaced than by conventional masking.



A major reduction in capacitance results from the 2- $\mu$ m feature size which TI's IMPACT processing makes possible. Silicon dioxide is the isolation material. Switching speed is further enhanced by utilizing this silicon dioxide for emitter and base sidewalls.

The IMPACT process also makes it possible to insulate critical base and emitter components with oxide walls. This insulation reduces sidewall capacitance, which, at the 2- $\mu$ m dimensions of IMPACT features, can represent as much as half the overall capacitance. Small size and oxide walling together contribute significantly to

the increase in switching speed.

## DRAM technology spurs IMPACT growth

The IMPACT process is not a direct descendant of DRAM technology. Nevertheless, TI's commitment to DRAM production has provided IMPACT technology with vital processes.

It was the DRAM effort, for example, that drove photolithography to its present advanced state and contributed key dry-etching processes. Ion implanters designed to produce CMOS DRAM ICs enhance the quality — and the economy — of TI's bipolar IMPACT ICs. And this vital "cross-fertilization" from VLSI memory is one reason Texas Instruments — almost alone among U.S. semiconductor manufacturers — is committed to the development and manufacture of DRAM devices.

◀ **More chips per slice** help cut costs. The 150-mm wafers now used on TI's advanced MOS 256K DRAM wafer-fabrication line have 125% more area than the 100-mm slices formerly used.





# your competitive edge.

6

## Keeping you competitive: ASICs and TI.

If you're looking for increased system-level integration and performance, shorter design-cycle time, and reduced VLSI development costs, take a hard look at application-specific integrated circuits (ASICs). And a long look at TI.

### Broad choice lets you pick the right implementation

Texas Instruments supports an extensive library of 3- $\mu$ m CMOS standard cells — more than 200 of the standard SN54/74 TTL functions you have designed with for years — including MSI, analog, and procedural LSI functions like RAM, ROM, PLA, and ALU. In addition, high-drive cells (up to 48 mA) are true TTL replacements.

From TI's new family of advanced standard cells you'll be able to choose among more than 280 functions and achieve increased system integration and performance.

Or for the performance you need, and quick turnaround to get your product to market fast, there's TI's DLM TAC-H and TAC-VH silicon-gate CMOS gate-array family. These devices, fully alternate-sourced, offer complexities from 440 to 8,000 gates.

### Extensive design support

Whatever level of help you need, you get it from TI. In your design cycle as well as in meeting your prototype and production requirements *on time*. TI's proven expertise and worldwide manufacturing facilities are your assurance of dedicated support and products in the volume you require. And you have a wide range of package options: DIPs, SOs, PLCCs, pin-grid arrays — from 8 to 179 pins.

### Design your own way

You can reduce your costs and speed your ASIC design with TI because you don't need special proprietary software or design tools. And you can do it at a TI regional design center or at your own work station. Because TI's cell libraries are supported by most work stations, including Daisy LOGICIAN®, MEGALOGICIAN®, and

GATEMASTER®, Mentor IDEA 1000®, Valid SCALDSYSTEM®, and P-CAD® and FutureNet® in IBM PC® environments.

TI's worldwide network of 13 training and design centers, staffed with experienced ASIC design engineers, can provide access to work stations, as well as mainframe capability. And you can learn ASIC design in one of TI's unique hands-on workshops. Using TI's semicustom libraries with a real-world standard-cell example, you'll learn every phase of design from schematic capture through test-pattern generation and simulation.

Select TI distributors can also give you local access to TI's leading-edge ASIC options, with dedicated facilities, tools, and trained engineers.


To find out more about what TI ASICs can mean to you, check the appropriate box on the return card.

8
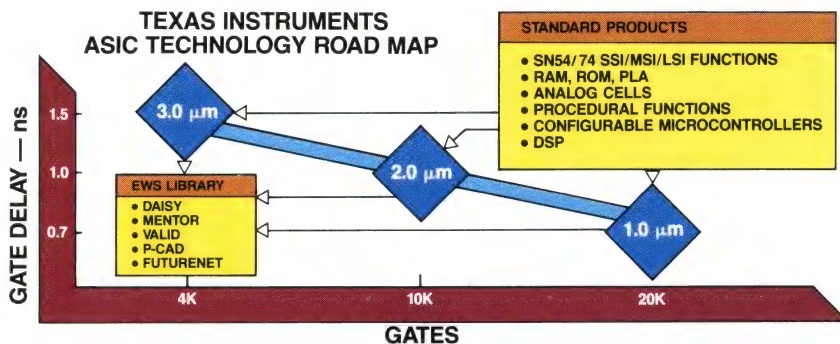
## And now, a new, easy-to-use EPROM microcomputer.

TI's new TMS7742 EPROM microcomputer can cut to zero your lead time for development, prototyping, field tests, and product qualification. And it bridges the gap to ROM-based volume production. For low-volume applications, it can be a cost-effective alternative to mask-programmed ROM. Its 4K bytes of on-chip EPROM are identical to TI's TMS2732A — transferred into the chip area vacated by masked ROM. So if you can program the TMS2732A you can program the TMS7742. This new microcomputer provides EPROM capability for the TMS7020, the TMS7040, and the new TMS7042 ROM microcomputer.

Also new to TI's TMS7000 family is the ROM-less TMS7002 microprocessor. Both the TMS7002 and the TMS7042 feature 256 bytes of RAM, a serial port for USART and serial I/O functions, 32 I/O lines, and three timers. And with their 60% performance increase over earlier TMS7000 ICs, they can improve system performance in such applications as disk and tape drives, printers, and industrial and motor controls.



Advancing technology in ASICs need not demand new rules and tools. Your investment in hardware and training is protected when you move up with Texas Instruments to faster, more complex ASIC functions.

7

## New series of input-latched and registered PAL ICs lowers parts counts.

Eight new 30 MHz PAL devices from TI are the first input-latched (TIBPALT19XX) and input-registered

(TIBPALR19XX) PAL ICs in the marketplace. Functionally similar to TI's TIBPAL20XX series, they include either 11 D-type transparent latches or 11 D-type input registers on chip. This added circuitry allows you to synchronize inputs without external registers or latches. These devices can reduce your parts counts and simplify your design task in a wide range of applications such as random logic, bus-interface logic, and input synchronization to custom controllers.



# 8 new ways TI can help sharpen


## 1 New alternative for memory-systems design: TI SIP DRAM modules.

Memory-intensive packaging for the future is available today — in TI's highly reliable modules in single-in-line packages (SIPs). With them you can have the many advantages of surface-mount technology (SMT) — while using through-hole-mounted or socketable packages. Thus without changing your manufacturing technology, you can increase memory density by a factor of up to 3.5 over dual-in-line packages (DIPs). And you can simplify board layout while facilitating replacement and future upgrades. Each SIP module uses DRAM chips in plastic leaded chip carriers (PLCCs),

surface-mounted along with decoupling capacitors on an epoxy substrate. Since all connection points are on one edge of the substrate, the module "stands on end" to make the most of your board area.

TI's full line of SIP memory modules — from 64K × 4 to 256K × 9 and 1M × 1 — includes standard DRAMs and Multiport Video RAMs in various organizations. And all are available through your authorized TI distributor.

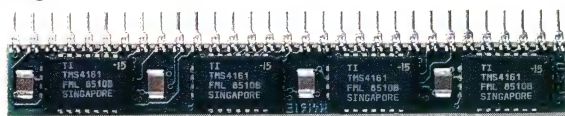For more information, just check the appropriate box on the reply card.



Memory can be 3.5 times denser using fully-qualified, production-proven RAMs configured in SIP modules. TI SIPs combine the density of surface-mount technology with economies of through-hole insertion.

## 2 Interface performance enhanced by TI.

Also new from Texas Instruments is an improved direct replacement for the JCN5812 vacuum fluorescent display driver. TI's TL5812 is 11% faster and

draws 60% less current. With an output voltage swing of 70 V and an output source-current capability of 40 mA.

Only TI's patented BIDFET technology — combining bipolar, double-diffused MOS (DMOS) and N-channel and P-channel CMOS transistors on the same chip — makes these improvements possible. And at a competitive price.


## 3 Fast line drivers and bus transceivers from TI.

In the new SN75ALS192/194 quadruple EIA Standard RS-422-A differential line drivers, TI's exclusive ALS 1.5 process technology (oxide-isolated Advanced Low-power Schottky) yields the best speed/power ratio in the industry: At approximately half the power consumption, these devices are 30% faster than the competition.

A new family of differential bus transceivers, SN75176B, 177B, 178B, and 179B, are faster than earlier versions. Designed for bidirectional communication on multipoint transmission lines in noisy environments, they meet

EIA Standards RS-422-A and RS-485. Typical propagation time is only 22 ns.

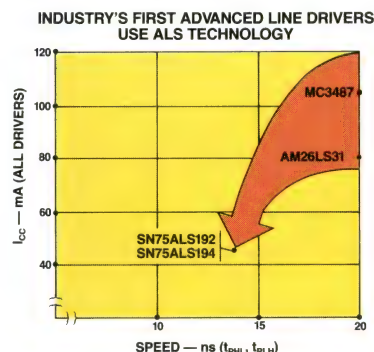Want to know more about these new interface products from TI? Just check the appropriate box on the reply card.



Advanced TI line drivers are 30% faster, typically draw only half the power of the devices they are designed to replace.

## 4 Fast, economical new 8-bit SAR A/D converters.

Now Texas Instruments offers 8-bit SAR (serial-approximation resolution) A/D converters that are as economical as any you can use. And because they use LinCMOS™ polysilicon-gate-process technology, they are unsurpassed in speed. TI's TLC549 analog-to-digital converter performs 40,000 conversion cycles per second (cps), while the new TLC548 pushes speed to an unprecedented 45,500 cps. At any supply voltage between 3 and 6 V. And typical power consumption is only 6 mW.

Performance of the serial-approximation algorithm is not only fast. It's accurate: Conversions are performed with the guaranteed low error rate of  $\pm 0.5$  LSB (least significant bit) across the temperature range from  $-55^{\circ}$  to  $125^{\circ}\text{C}$ .

## 5 681 military TI devices comply with 1.2.1.

Now designers of military electronics have the broadest choice ever of devices that comply with the requirements of MIL-STD-883C, Paragraph 1.2.1. The vast majority of TI's military ICs — 681 different devices — now qualify:

Product Type	Number
ALS/AS	83
TTL	131
LS/S	238
HCMOS	80
PAL ICs	16
Linear	113
Memory/LSI	19
MOS DSP	1
TOTAL:	681

For more detailed information on specific TI military devices, just check the appropriate box on the reply card.



# Texas Instruments quality recognized in Tokyo and Detroit.

Outstanding Texas Instruments quality-assurance programs were lauded during 1985 both at home and abroad. In June, Ford Motor Company granted TI linear products the coveted Q1 Award. And in November, TI's wholly owned Japanese semiconductor operation received the prestigious Deming Prize. Both awards recognize exceptional levels of quality and reliability, achieved through aggressive defect-prevention programs.



## First Ford Q1 Award to a semiconductor supplier

Ford Motor Company's Q1 Award to Texas Instruments Linear is the first ever to a major U.S. semiconductor manufacturer.

Qualification is based on a demonstrated defect-prevention program,

along with Ford's review of warranty returns, specifically keying part numbers to failures. Thus it recognizes both initial product quality and continuing reliability.

Both quality and reliability are attributes that TI Linear has pursued aggressively through its "monitor program," begun in 1979. The goal of the program has been to achieve levels of quality and reliability equal to or better than the best worldwide competition. And the Ford Q1 Award is one visible token of its success.

## First U.S. winner of Japan's Deming Prize

At ceremonies on November 11 in Tokyo, the Japanese Union of Scientists and Engineers awarded the prestigious Deming Prize for total quality control to TI's bipolar semiconductor operation in Japan.

The prize, never before won by a wholly U.S.-owned company, recognizes outstanding quality-control achievement in all aspects of business — including marketing, engineering, manufacturing, and support. It is named for W. Edwards Deming, the American statistician whose work in defining and measuring quality control in Japan after World War II became the basis for the legendary Japanese commitment to quality. In 35 years, the Deming Prize has been awarded to only 48 individuals and 111 institutions. Texas Instruments Japan, Ltd. was one of only eight companies so honored in 1985.



As is the case with the Ford Q1 Award, sensitivity to customers' requirements is a key factor in selecting winners of the Deming Prize. TI's successful commitment to quality and reliability in support of all our customers' needs has been demonstrated twice again. And TI is justifiably proud of this achievement.

IMPACT and LinCMOS are trademarks of Texas Instruments Incorporated.

PAL is a registered trademark of Monolithic Memories, Inc.

LOGICIAN, MEGALOGICIAN, and GATEMASTER are registered trademarks of Daisy Systems Corporation.

IDEA 1000 is a registered trademark of Mentor Graphics.

SCALDSYSTEM is a registered trademark of Valid Logic Systems Incorporated.

PCAD is a registered trademark of Personal CAD Systems Inc.

FutureNet is a registered trademark of FutureNet Corporation.

IBM PC is a registered trademark of International Business Machines Corp.

## More news upcoming from TI in the next issue:

- A new CMOS version of TI's trend-setting TMS320 Digital Signal Processor.
- New CMOS standard cells and gate arrays that augment TI's leadership in Application-specific Integrated Circuits (ASICs).
- And more ...

## For more information...

Check the appropriate square on the reply card, or write **Texas Instruments Incorporated, Department SY093, P.O. Box 809066, Dallas, Texas 75380-9066.**

  
**TEXAS  
INSTRUMENTS**

Creating useful products  
and services for you.



# Dynamic signal analyzers simplify measurement of linear control systems

---

*Advanced dynamic signal analyzers (DSAs) give designers a wide choice of techniques for measuring a system's open-loop frequency response. This article, part 2 of a 3-part series, considers the effect of DSAs on the graphical measurement techniques of linear control-system theory. Part 1 of the series presented an overview of classical linear control theory. Part 3 will explore the expanded role of DSAs in the control-system design process.*

---

Steve Asbjornsen and Owen Brown,  
*Hewlett-Packard Co*

You can use a variety of graphical techniques to analyze a negative-feedback, closed-loop control system (Ref 1). Bode plots, Nichols diagrams, and Nyquist diagrams are three distinct tools that allow you to determine a system's amplitude and phase characteristics (and, therefore, its stability) as functions of frequency. Typical test instruments make use of these tools, and a dynamic signal analyzer (DSA) is no exception—it allows you to view and plot frequency-response data in all three formats.

The internal analysis functions of modern DSAs,

however, alter the relative usefulness of these three graphical techniques. Understanding these DSA functions gives you an idea of how a DSA's computational power can expand your test options.

## Waveform math and Nyquist diagrams

A DSA's waveform-math capability, for example, limits the Nyquist diagram's usefulness to providing a complete check of a system's stability and a 1-trace representation of its frequency response. The waveform-math utility is a built-in calculator that allows you to add, subtract, multiply, divide, or use any of the other operators shown in **Table 1** to manipulate frequency responses, recorded waveforms, and complex constants.

The Nyquist diagram lets you easily determine the stability of all types of systems, including absolutely and conditionally stable systems. You can also directly calculate the closed-loop frequency response of a unity-feedback control system. However, the diagram doesn't facilitate calculation of composite frequency responses, and its linear scales can't accommodate both adequate gain ranges and acceptable resolution around the unity-gain point. Reading phase margin is more difficult with the Nyquist diagram than with other diagrams, and reading the open-loop bandwidth is



*A DSA's built-in calculator uses waveform math to perform arithmetic operations and to manipulate frequency responses, waveforms, and complex constants.*

**TABLE 1—WAVEFORM-MATH  
FUNCTIONS IN A DSA**

ADD	SQUARE ROOT	MULTIPLY BY $j\omega$	$T/(1-T)$
SUBTRACT	RECIPROCAL	FFT	REAL PART
MULTIPLY	NEGATE	INVERSE FFT	COMPLEX CONJUGATE
DIVIDE	DIFFERENTIATE		LOG DATA

impossible unless the frequency at which the gain becomes unity is recorded on the plot. Finally, you can't use the Nyquist diagram to estimate the transfer function of a system from its measured frequency response, or vice versa.

A DSA's waveform-math utility, however, lets you calculate a system's closed-loop response precisely, in any format, using the equation

$$C(j\omega)/R(j\omega) = G(j\omega)/\{1 + G(j\omega)\}.$$

Using waveform math, you can calculate closed-loop frequency response independently of the display format. Linear scales are not a problem when you're using a DSA, because the DSA's display can easily rescale the data. The DSA's marker readouts make the measurement of gain margin, phase margin, and open-loop bandwidth much easier.

### Code plots

DSAs also alter the usefulness of the Bode plot, which designers have traditionally favored because they could use it to estimate composite frequency responses quickly. The Bode plot's logarithmic units offer a large dynamic range of gains, and the plot makes it easy to measure gain margin, phase margin, and open-loop bandwidth. Finally, unlike the Nyquist diagram, the Bode diagram lets you estimate a transfer function from a frequency response and vice-versa.

The Bode plot's major drawbacks are that you have to plot traces for both gain and phase, and that you can't estimate the closed-loop frequency response from the open-loop frequency response. A DSA's waveform-math utility makes it easy to calculate the closed-loop frequency response, however. Further, the DSA's frequency-response-synthesis and curve-fitting functions automate the transition between frequency responses and transfer functions.

The Bode plot is still useful in that it helps you intuitively understand the frequency-response/transfer-function transition. The Bode plot also helps you


estimate composite waveforms, and its logarithmic gain units provide both range and resolution.

Although the Bode plot and Nyquist diagram are still useful to designers who perform system analysis on DSAs, Nichols diagrams are not. The Nichols diagram's only advantage over the other diagrams is that it lets you calculate closed-loop frequency responses. Because the waveform-math capability of DSAs solves this problem, it renders the Nichols diagram obsolete.

### The root-locus plot

The newest method of making control-system measurements is root-locus analysis, which was developed in the late 1940s and early 1950s by Walter R Evans. All previous methods of analysis had used open-loop frequency response solely to determine whether closed-loop poles with positive real parts existed. These methods yielded no additional information concerning the actual value of  $s$  for the poles. The root-locus technique, however, lets you examine the actual values of  $s$  for the closed-loop poles graphically, based on the known values of  $s$  for the open-loop poles and zeros.

The root-locus diagram could not have been conceived without the development (in the late 1940s) of the  $s$ -plane. The  $s$ -plane is a 2-dimensional plane that represents all possible values of the Laplace variable  $s$ . The plane's ordinate is the imaginary part ( $\omega$  of  $s = \sigma + j\omega$ ), and its abscissa is the real part ( $\sigma$  of  $s = \sigma + j\omega$ ), of  $s$  (Fig 1).

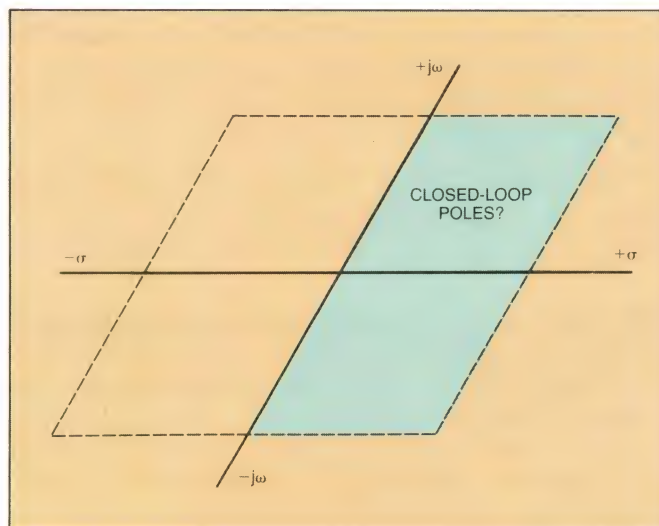

**Fig 1—The  $s$ -plane represents all possible values of  $s$  in two dimensions. This plot allows you to locate the poles and zeros of a closed-loop transfer function and thereby determine the stability of the system characterized by the transfer function.**



Each value of  $s$ , therefore, has a unique position in the  $s$ -plane. If you can determine the poles and zeros of a ratio of polynomials (such as the open- and closed-loop transfer functions of a control system) in  $s$ , you can plot the location of these poles and zeros in the  $s$ -plane. Any closed-loop pole that exists in the right half of the  $s$ -plane represents poles with positive real parts and therefore indicates an unstable system.

In measuring the open-loop frequency response of a system, you're collecting the same data you would if you were evaluating  $GH(s)$  for values of  $s$  that lie on the positive ordinate of the  $s$ -plane ( $s=0+j\omega$  for  $\omega=0$  to  $+\infty$ ). From the open-loop information, Nyquist—without using the idea of the  $s$ -plane—made the conceptual leap that allowed him to determine whether there were any values of  $s$  with positive real parts that solved the equation  $GH(s)=-1$ . His observation was not an obvious one, to say the least.


Consider a control loop that has been opened so that the open-loop frequency response ( $GH(j\omega)$ ) is measurable. If you alter just the gain of the loop, you won't affect the value of the open-loop poles and zeros. As a result, the open-loop transfer function can be expressed as  $GH(s)=KGH(s)$ , where  $K$  represents a proportional gain constant that's independent of  $s$ .

Although varying  $K$  has no effect on the position of the open-loop poles and zeros, it can have a tremendous effect on the closed-loop poles. This effect becomes apparent if you substitute  $KGH(s)$  in the denominator of the closed-loop transfer function  $G(s)/\{1+GH(s)\}$  and solve the equation for the poles. The resulting expression is  $1+KGH(s)=0$ .

The closed-loop poles, therefore, are values of  $s$  that are solutions to the equation  $GH(s)=-1/K$ . To locate the closed-loop poles, you must, whenever  $K$  changes, find new values of  $s$  that satisfy the equation  $GH(s)=-1/K$ . It was this relationship—between the stationary poles and zeros of the open-loop transfer function, and the closed-loop poles that vary with pure gain—that provided the basis for Evans's root-locus technique.
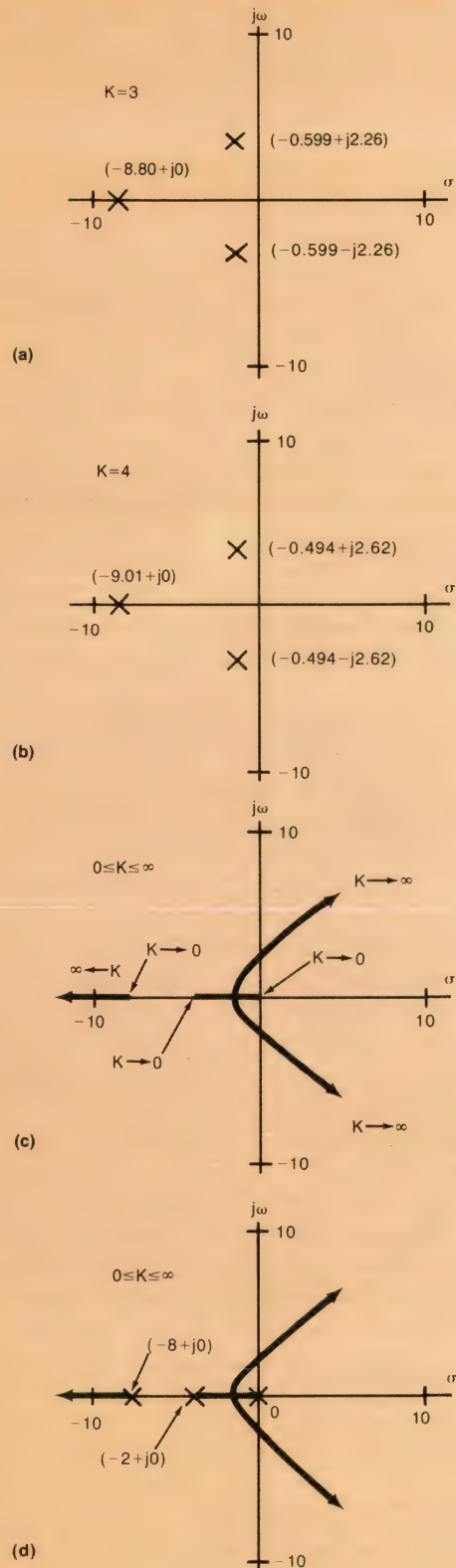
### Using the root locus

The root-locus technique plots the open-loop poles and zeros in the  $s$ -plane. You can obtain the open-loop pole and zero locations from a mathematical derivation of the open-loop transfer function or by using Bode's techniques to extract the transfer function from a measured frequency response. If you plot the open-loop poles and zeros on the  $s$ -plane (Figs 2a and 2b), you can



NOTE:  
 $GH(s) = \frac{K}{s(1+0.125s)(1+0.5s)} = -1$

**Fig 2—A powerful graphical technique, the root-locus plot, allows you to determine the location of poles in a closed-loop system without actually measuring the closed-loop response. This method depicts the migration of poles as the system's frequency-independent gain ( $K$ ) varies.**



use Evans's graphical techniques to draw a trace that represents the migration of the closed-loop poles (or root loci) as the frequency-independent gain varies (Figs 2c and 2d).

The advantage of this technique lies in its ability to give the actual location of closed-loop poles without actually measuring the closed-loop response. However, using graphical techniques to determine the root loci doesn't give you the actual value of the frequency-independent gain ( $K$ ) at any particular point in a locus. You must return to the equations and calculate the closed-loop pole locations for several values of  $K$  until you discover the value of  $K$  that corresponds to some point on a locus.

The root-locus technique also requires that you know the number and location of the open-loop poles and zeros before you can estimate the position of the closed-loop poles. The technique is, therefore, less flexible than the Nyquist or Bode diagrams, which let you predict stability, measure performance, and obtain design information, but allow you to measure only the open-loop frequency response. The root-locus method, however, provides you with more information during the initial design process, and it's better suited to the design of the complex compensation networks typically associated with complex systems. Also, because you know the position of the closed-loop poles, you can derive the time-domain response for a given value of gain ( $K$ ).

Almost all linear control-system analysis, and much of the subsequent designs, depends on obtaining an accurate estimate of a system's open-loop characteristics, either in the form of a frequency response  $GH(j\omega)$  or the closed-loop transfer function  $GH(s)$ . No matter how these open-loop characteristics are expressed, designers must always perform the actual physical frequency-response measurements, whether to help construct system models or to verify them.

### Measurement techniques

In the past, engineers had to choose between two types of analyzers for making low-frequency control-system measurements. They could choose either the classic frequency-response analyzers (FRA), which provide swept-sine measurements, or fast-Fourier-transform analyzers (FFTA), which can measure a whole spectrum in one measurement.

The two analyzers have different advantages and disadvantages. For example, although the FFTA has the potential for faster measurement times, it entails


complex set-up procedures. And although the FRA is familiar to engineers, who understand its swept-sine method of measurement, its measurement times are slow. However, because DSAs offer both measurement techniques, designers no longer have to accept the tradeoffs that accompany choosing an FFTA or an FRA.

### Frequency-response analyzers

FRAs operate in much the same way as do heterodyne network analyzers, and they're limited to taking measurements at low frequencies. They generally possess two channels, each of which uses a discrete Fourier transform to emulate a single bandpass filter. The Fourier integration time controls the filter's bandwidth to values in the low microhertz range, and an integrated sine-wave source (Fig 3) synchronizes the filter's center frequency.

A stimulus signal from the FRA drives the device under test. The analyzer's two channels connect to the input and output of the device, and the signal each channel receives undergoes comparison with the stimulus signal as a function of the discrete Fourier transform. The result is a complex value containing the magnitude and phase (with reference to the stimulus signal) of the measured signal.

The FRA then compares the two channels' results, deriving the gain and phase-shift relationships between the two channels' signals. This process occurs several

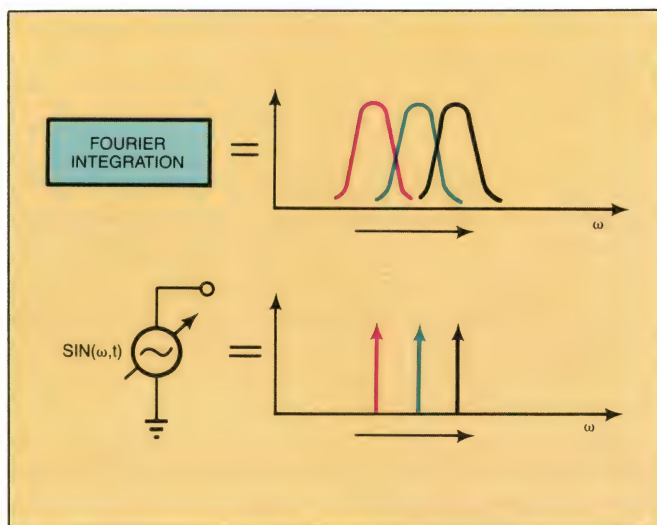

**Fig 3—The integration time of a Fourier transform controls filter bandwidth, and a sine-wave signal source sets the filter's center frequency. Each discrete Fourier transform emulates a single band-pass filter.**



---

*A root-locus diagram allows you to examine the values of  $s$  for a system's closed-loop poles, based on the known values of  $s$  for the open-loop poles and zeros.*

---

times between the start and stop frequencies being analyzed, thereby producing a series of discrete gain and phase values. When you connect these points graphically, you obtain the gain and phase curves of the frequency response. Note that this measurement process has two implementations, and the difference between them can be important to the designer who uses computer-aided analysis.

The primary distinction between the two implementations lies in the sources. An FRA whose source sweeps continuously can integrate the signal while the source is actually sweeping. Each integration period, therefore, covers a small part of the total measurement span. The result of that integration is then available at the end of each integration period.

This continuous-sweep technique creates a potential ambiguity between the phase and magnitude values for the displayed frequency, and the exact frequency at which they occurred. The ambiguity becomes especially serious when the integration period covers large frequency spans. Because the integration period is typically fixed, you can generally minimize this problem by reducing the sweep speed—and therefore the frequency span covered—during integration. The ambiguity won't interfere with graphical analysis, but it can create difficulties in computer analysis.

### Sweep-and-dwell sources

The alternative to the continuous-sweep implementation is a sweep-and-dwell sine-wave source. In this type of analyzer, the sine-wave source dwells at a discrete frequency during the integration process and then performs a phase-continuous sweep to the next analysis frequency.

Because a sweep-and-dwell analysis occurs at a discrete frequency, the phase and gain analyses apply only for the frequency point at which the measurement was made; therefore, no ambiguity exists. DSAs incorporate this sweep-and-dwell form of swept-sine analysis, which optimizes the accuracy of their integrated computer-aided-analysis functions.

One possible drawback to the sweep-and-dwell technique is that the analyzer might miss valuable information between measurement points. However, by simply decreasing the sweep rate of these analyzers, you increase the number of measurement points between the start and stop frequencies and provide better resolution.


Newer analyzers offer an autoresolution function that monitors the gain and phase shift between mea-

surement points and automatically adjusts the resolution (ie, sweep rate) during the sweep, thereby preventing the loss of valuable data. This function can also minimize total sweep time by increasing the sweep rate in portions of the frequency response that are relatively flat in both gain and phase.

### FFT analyzers

Fast-Fourier-transform analyzers (FFTAs) are similar to FRAs in that they use a type of Fourier transform to achieve narrow analysis bandwidths. Their method of signal generation and use of two channels to compare a device's input and output are also the same as those of the FRAs. However, instead of emulating a single bandpass filter and tracking it over the spectrum of interest, FFTAs emulate hundreds of bandpass filters (Fig 4) and provide complete coverage of an entire spectrum in one integration period. FFTAs can usually perform measurements much more quickly than can FRAs.

In addition to the increased number of analysis bands, the FFT process can also use a wide range of

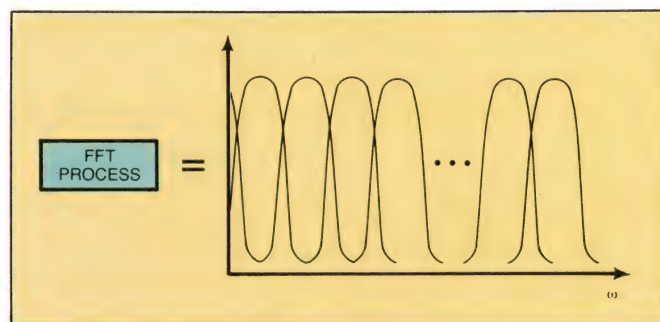

**Fig 4—FFT analyzers emulate hundreds of bandpass filters.** One integration period, therefore, provides complete coverage of an entire spectrum. The FFTA can use a wide variety of stimulus signals, including random noise.

stimulus signals. They typically use stimulus signals (such as random noise) that provide energy over the entire analysis span, thus taking full advantage of the analysis power.

FFTAs and FRAs use different methods to reduce measurement noise. If you don't know what the differences in the methods are and how they affect the measurement process, you can very easily misuse an FFT analyzer. Designers lacking this information have sometimes concluded—mistakenly—that FFT analyzers can't make control-system measurements.

Although the term "swept-sine analysis" describes the FRA's stimulus signal, it doesn't describe the



*The sweep-and-dwell sine-wave stimulus is better than any other type of stimulus for measuring noisy systems.*

FRA's unique analysis process comprehensively (heterodyne analyzers also use a swept-sine stimulus). The term "swept Fourier analysis" (SFA) describes the FRA's measurement process more specifically. The differences between FFT and SFA measurement processes lie mainly in their stimulus signal, single- versus multiple-band analysis, and noise-reduction techniques.

### Stimulus signals in SFAs and FFTs

The SFA measurement process uses a swept-sine-wave stimulus, and the FFT process uses stimuli that produce energy at all the analysis frequencies within a single integration period. When you're measuring extremely noisy systems, the type of stimulus itself can have a profound effect upon the measurement.

The sweep-and-dwell sine-wave stimulus is better than any other type of stimulus for measuring noisy systems, because the power of the stimulus is concentrated at one discrete frequency. This concentrated-power approach automatically provides the best possible signal-to-noise ratio without any signal processing. A random-noise stimulus, on the other hand, must distribute its energy over a wider bandwidth, providing less power at any one discrete frequency than would a dwelling sine wave (ie, its power spectral density is much lower than a sinusoid's) (Fig 5).

A random-noise stimulus also has advantages, however. One of the key strengths of this type of stimulus is that it provides a linear estimate of the operation of a nonlinear system. For example, many systems experience changes in their frequency response relative to the drive level or relative to the direction of a sine-wave

sweep. Random noise, which has no sweep direction and has random amplitudes at all frequency components, provides an average of the drive-level and sweep-direction effects, so it usually provides a good approximation of a system's operation.


In situations in which initial measurements indicate that the energy level of the random-noise stimulus is too low, you can improve the relative power spectral density of the stimulus by reducing the frequency span of the measurement (if the analyzer uses a band-limited random-noise source). However, to cover the original frequency span of interest, you must take more measurements.

### Single- vs multiple-band analysis


The SFA's single-filter measurement process is slower than the FFT process, which provides hundreds of filters. However, the use of a single filter does have its advantages. If you use a single filter, you can make all the signals produced by distortion products (such as harmonic distortion and intermodulation distortion) lie outside the analysis bandwidth of a single filter, thus removing the products from the measurement.

By increasing the Fourier integration time, you can always reduce the filter's bandwidth to exclude distortion products (Fig 6). The only time you can't remove a disturbance signal is when a spur at a fixed frequency occurs at exactly the same frequency as that of the SFA's stimulus. Because of its many filters, the FFT process can be affected by distortion products, depending on the stimulus used.

For example, if you use a sine-wave stimulus in a

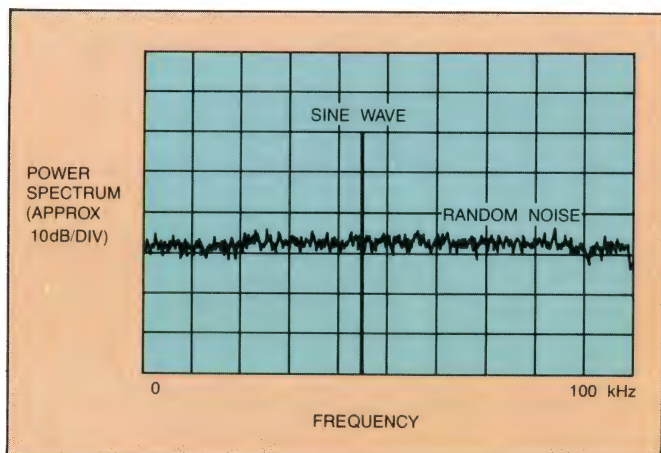

**Fig 5—Power-spectrum density for a random-noise signal is much lower than that for a sine wave, as this plot shows. The random-noise signal distributes its energy over a much wider bandwidth than does a sine wave.**

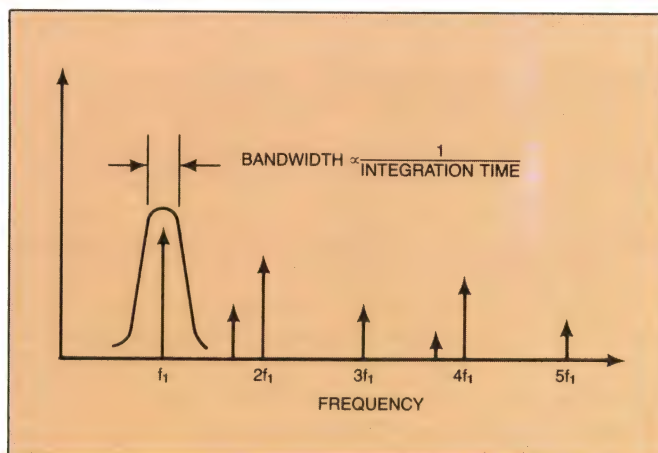

**Fig 6—Reducing the analysis band of an SFA's measurement process excludes distortion products from the measurement. The analysis band is inversely proportional to the Fourier integration time.**





# WHAT TO DO WHEN IT TURNS INTO A CAN OF WORMS.

You face the pressure everyday. On almost every project. To reduce weight. Reduce material and labor costs. Improve product performance and appearance.

All against the clock!

So, you look for outside suppliers to add to your own resources.

That's why so many engineers like you turn to MACtac. For fresh new solutions to product design...assembly...decoration...and protection.

Because MACtac brings you the broadest line of performance-rated pressure sensitive adhesives. Foams, films and free films in rolls and sheets. For permanent parts bonding,

temporary spot adhesion, wide area lamination, durable decoration, etc.

Plus unique optically clear pressure sensitive films for a host of exotic applications. And much more.



**CALL MACtac, 1-800-323-3439.**

Schedule a Materials Specification Meeting in your plant now—to review our standard and custom capabilities, and quickly focus in on problems/solutions. Contact: MACtac Industrial Products, 4560 Darrow Rd., Stow, Ohio 44224. In Ohio, 216-688-1111.


**Adhesives Systems Engineering**




A Bemis Company



*A DSA combines the advantages of classic frequency-response (swept-sine) analyzers and fast-Fourier-transform analyzers.*

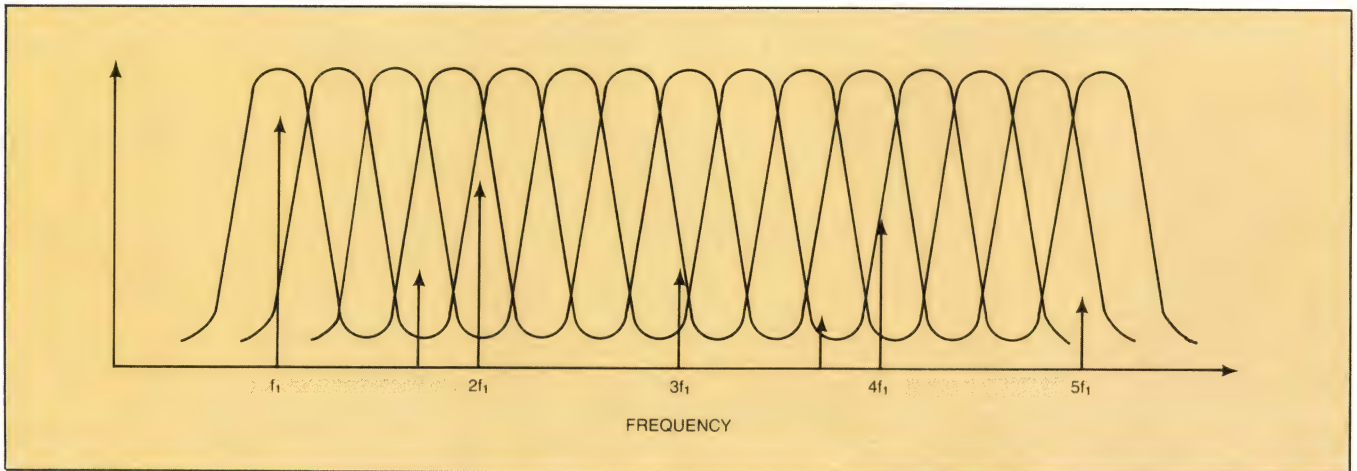

**Fig 7—A sine-wave stimulus in a measurement using the FFT process** can cause distortion products to appear within the filters produced by the transforms. The products would thus be recorded as part of the system's response.

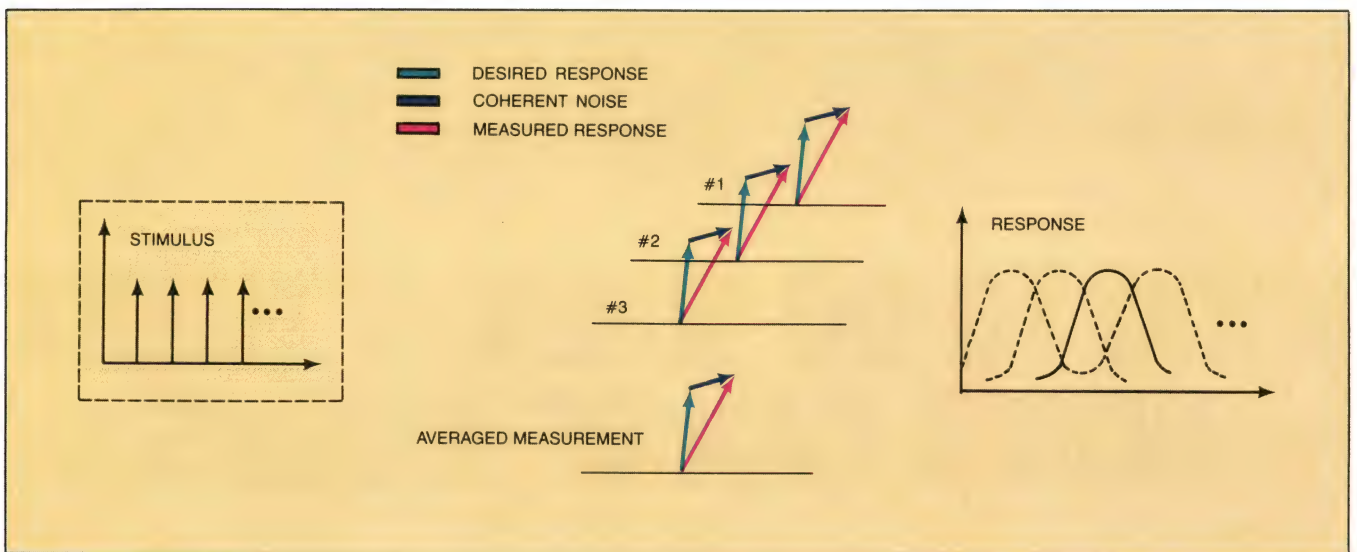

**Fig 8—Periodic stimuli allow harmonics to maintain a constant phase relationship** with desired signals. It's impossible, therefore, to average these components to zero, thereby reducing the effect of the nonlinearity on a measurement. A random stimulus eliminates this distortion-induced problem; averaging causes the nonlinear portion of the response in each filter to dwindle to zero.

system that produces harmonic distortion, the distortion products can appear within one or more of the FFT's filters and be recorded as part of the system's response (Fig 7).

Distortion products can also affect the FFT process when you use a pseudorandom signal as a stimulus. You can characterize this pseudorandom signal as a summation of discrete sine waves, each of which is tuned to the center frequency of a unique filter. If you separate the response in each filter into the portion of the response that results from the intended stimulus (the desired response) and the portion of the response that arises

from a harmonic product of a lower frequency, you'll never see a change in the relationship between the desired response and the distortion product from measurement to measurement. Therefore, even if you were to average the results of several measurements, you wouldn't reduce the effect of the nonlinearity on the measurement (Fig 8).

A random stimulus, however, eliminates this distortion-induced problem by letting the nonlinear portion of the response in each filter decay to zero with averaging, even if the nonlinearity is a fixed spur at the center frequency of a filter. A swept-sine-wave stimulus





## BECAUSE NO TWO ENGINEERS ARE EXACTLY ALIKE, DIALIGHT OFFERS THE LARGEST OPTOELECTRONICS VARIETY.

With everything electronic getting smaller, PC boards and front panels are getting more complicated and difficult to service.

Fortunately, Dialight optoelectronics can help throw some light on the subject. And that's why using this technology is becoming the mark of a good design engineer.

### **THE ABCs OF DESIGNING WITH LEDs.**

Suppose you want to backlight a front panel from an internal PC board.

You could use value-added Dialight LEDs. They plug right into the board and hold the light steady at exactly the right distance from the panel.

Or you can make troubleshooting a circuit board easy by designing in a Dialight LED that will indicate a faulty component.

Dialight packages LEDs to make them easier to insert. With no need to bend, trim, and possibly break, delicate leads.

Of course, you could buy individual LEDs for less. And have somebody bend, trim and insert them by



hand. But think of what all that hand labor costs. Not to mention the cost of a service call if your light fails in the field.

That's what made the value-added LED such a good idea when we came up with it almost 15 years ago. And why we still 100% test every single LED before we ship it.

### **AN IDEA THAT'S 4 TIMES BRIGHTER.**

Today Dialight is still lighting the way. Our new Super Brights, for example, are 4 times brighter than ordinary LEDs. So they're easier to see. Even in the high ambient light of a computer room. And if you're short on power, they operate on one-fourth the current.

Call 718-497-7600 or write Dialight Corporation, 203 Harrison Place, Brooklyn, NY 11237-1587 and we'll send you copies of our catalogs.

Keep them handy. They'll put hundreds of great ideas at your fingertips.



A North American Phillips Company

# **DIALIGHT OPTOELECTRONICS**

*Products of your imagination.*

CIRCLE NO 168

See us at Electro '86 Booth #523-7



---

*An FFT analyzer uses two channels to compare input and output and emulates hundreds of bandpass filters to provide complete coverage of an entire spectrum.*

---

doesn't permit such averaging. The explanation of distortion phenomena leads directly to the topic of noise reduction.

#### Noise reduction in SFAs and FFTs

The noise-reduction process of SFAs is fairly straightforward. If you increase the integration time in each channel, the analysis bandwidth in each channel becomes smaller and smaller while remaining centered on the frequency of the stimulus. As the bandwidth becomes smaller, the noise power (of the measured system) within the filter lessens. Moreover, any spurs close to the center frequency become located farther down the stop band of the analysis bandwidth until they receive sufficient rejection.

The only type of distortion that can't be rejected is a spur that has the same frequency as the stimulus and that maintains a constant phase relationship with the stimulus. In this case, the spur is said to be coherent with the stimulus. A key aspect of this type of noise reduction is that the noise in each channel is reduced before the gain and phase relationship (ie, the frequen-


cy response) between channels is calculated.

The FFT process makes two types of noise reduction available: time averaging (a form of linear averaging) and power-spectrum averaging. Time averaging is very similar to the SFA's averaging process in that it improves the S/N ratio of the signal in each channel before the frequency response is calculated. The time-averaging method gathers the samples of the signal normally considered by the FFT into blocks of data called time records, and then averages the time records.

To keep averaging from reducing the signal of interest, you must make sure that the signal is a periodic one (such as the pseudorandom signal mentioned above) and that the phase of the signal is the same in each time record. You must also supply a trigger signal to the analyzer to indicate when data collection should begin.

#### Power-spectrum averaging

The second, and more commonly used, form of noise reduction in FFT measurements is power-spectrum averaging. The fundamental difference between this technique and time averaging is that relatively little

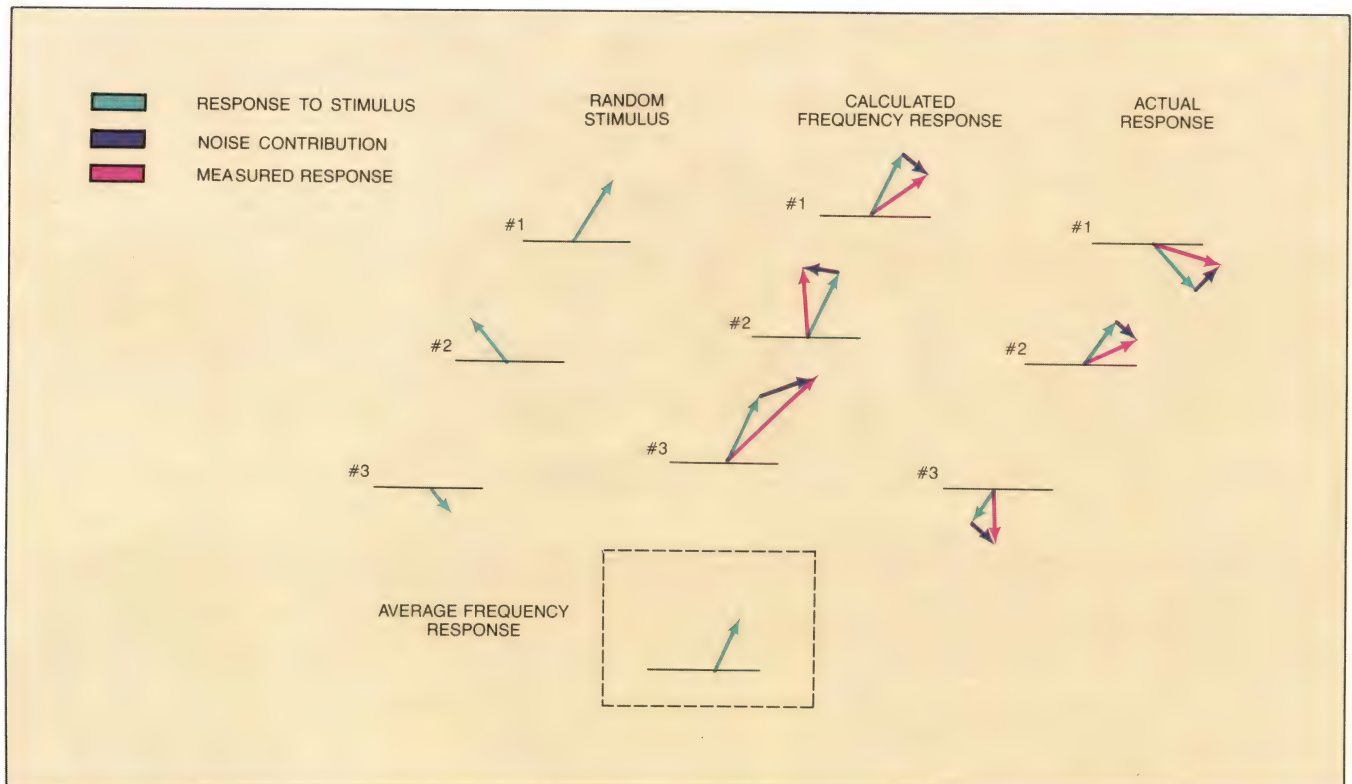

**Fig 9—If you average frequency-response calculations, you can use random noise as a stimulus. The stimulus-response relationship remains constant, while the noise contribution in both channels averages to zero. The averaged frequency response thus converges in a linear representation of the system's frequency response.**



# Win the board game, with smart real-estate decisions!

## Choose our monolithic buffer amps for more reliability, less cost.

When you go for high-performance buffer amps, go to the high-performance leader...Harris.

New HA-5002 and HA-5033 monolithic buffers use our proven Dielectric Isolation technology to produce both PNP and NPN high-frequency transistors. The result: wider bandwidth and more speed than you get from many hybrids.

And that means some impressive performance characteristics!

HA-5002 performance:

- High slew rate: 1300 V/ $\mu$ s
- Bandwidth: 110 MHz
- Voltage gain: 0.995 V/V
- Output current: 200 mA
- LH0002 pin compatibility (cans)

Beyond great performance, our buffer amps offer single-chip reliability no hybrid can match, and accompanying savings in board space, design time and system costs. Choose our buffer amps for military systems such as sonar, radar, avionics and ECM; for cable and line drivers, medical scanners — and broadcast video equipment.

The HA-5002 comes in 8-pin cerdip and plastic DIP, leadless chip carrier and TO-99 can pin-compatible with LH0002. The HA-5033 comes in an 8-pin plastic DIP and 12-lead TO-8 can.

To improve the performance of your real-estate investment, specify monolithic high-speed buffer amps from Harris.

Find out more; contact:  
Harris/MHS Semiconductor  
Sales Ltd., Eskdale Road,  
Winnersh, Wokingham,  
Berks, RG11 5TR,  
England.

Harris Semiconductor:  
Analog · CMOS Digital  
Gallium Arsenide · Semicustom  
Custom · Hybrids



Used by permission of Parker Brothers. ©1935, Parker Brothers.

# For your information, our name is Harris.

CIRCLE NO 167



---

*If you don't understand the differences in the ways an FFTA and an FRA effect measurement-noise reduction, you could misuse the FFTA.*

---

noise reduction occurs in each channel. Instead, the method removes noise by averaging frequency-response data from each measurement.

The benefit of this noise-reduction technique is that it doesn't matter how much the stimulus signal differs from one measurement to the next, as long as the gain and phase relationship from measurement to measurement remains the same. You can thus use random noise in an averaged measurement.

For example, assume you allow the random-noise stimulus to maintain the same frequency components as the pseudorandom-noise signal discussed earlier, but let the phase of the discrete sine waves vary randomly (a poor representation of random noise, but useful for this example). In this case, the stimulus signal within each filter will have a different phase orientation in each measurement.

If you were to examine a filter whose output is composed of a linear response to the intended stimulus signal and a nonlinearity-induced harmonic product, you'd see a change from measurement to measurement in the relationship between the linear response and the harmonic. The disparity exists because the phase of the harmonic's fundamental and the intended stimulus would have changed between measurements.

If, over several measurements, you examine a vector representing the computed frequency-response data for each measurement, you'll see that the distortion product appears as a vector that rotates about the end of a stationary frequency-response vector (**Fig 9**). When you average several frequency-response vectors, the contribution from the distortion product falls to zero. The averaged frequency-response vector thus gives you the best linear estimate of the device's frequency response. If you use a random-noise stimulus in this type of averaging scheme, you'll find that even a spur at the center frequency of a filter would be noncoherent with the stimulus and would average to zero.

Although power-spectrum averaging, combined with a random-noise stimulus, reduces the effects of all forms of distortion products from a measurement, you wouldn't benefit from using power-spectrum averaging with a periodic stimulus. Using a periodic stimulus would allow distortion products to be coherent with the stimulus, so they'd be unaffected by averaging. Further, certain control-system measurements don't allow the use of power-spectrum measurement.

The FFT analyzer is always better than a swept-frequency analyzer for measuring a basically linear system with poor to good S/N conditions. Both analyz-

ers (FFTA and SFA) will provide the same response, but the FFT process will provide it much more quickly. The SFA, on the other hand, gives you the best possible S/N ratio, so it's more suitable for use in difficult measurement situations. Having both techniques available is clearly preferable, as in a DSA, so you can use them to handle different measurement problems. **EDN**

---


## Reference

1. Asbjornsen, Steve, and Brown, Owen, "Apply control-system theory to analyze closed-loop system," *EDN*, April 3, 1986, pg 173.


---
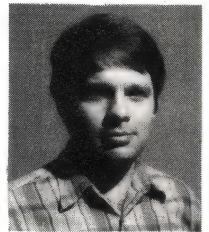
## Authors' biographies

*Steven W S Asbjornsen is a product-marketing engineer at Hewlett-Packard (Everett, WA), where he's responsible for control-system application and market development. He received a BSEE from the University of Washington and has been with HP for five years. Steven, who is a musician in his spare time, also enjoys hiking and waterskiing.*



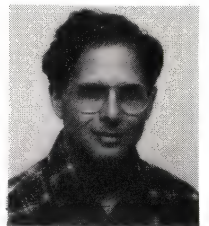*Owen Brown, who is in charge of product publicity for Hewlett-Packard (Palo Alto, CA), has worked for H-P for two years. He has a bachelor's degree from Yale University and an MBA from the University of Chicago. His spare-time pursuits include painting and aikido.*



---

Article Interest Quotient (Circle One)  
High 482 Medium 483 Low 484



# the NEW VFC100

## Synchronized V/F Converter



## Simply the Best

VFC100 is easy to use and offers the best voltage-to-frequency conversion performance. Output frequency is determined solely by the system clock:  $f_{out} = V_{in}/20 \cdot f_{clock}$ . It's that simple!

0.1% max nonlinearity at 1MHz, best available in a VFC.  
0.5% max total error, eliminating the need for trimming in

many applications. 50ppm/°C drift, highest stability and no external resistors or capacitors to degrade drift performance. Compact 16-pin DIP. VFC100, unique and simply better than any other voltage-to-frequency converter design. Call, write, or use the reader service number for more information on this exciting new part.



Putting Technology To Work For You





# Integral one-step shielding. Very friendly I/O. From AMP.

*Round shielded  
cable terminates  
in just two steps.  
Optional insulation  
boot protects  
against ESD.*

AMP is a trademark of AMP Incorporated.







Our latest idea in I/O: a good-looking, hard-working shielded connector that attaches to flat cable in a single operation.

One step mass-terminates the cable, applies two-point strain relief, and terminates the cable shield to the connector shield.

Our Shielded Data Link connector comes in a one-piece assembly,

already shielded, all ready to go. With selective gold plating for high cycle life, user-friendly design for easy insertion, secure retention and simple release.

Sensible? You bet: the shielding you need, in an economical connector with unbeatably


economical one-step application.

Cost effective? No question about it: it's from AMP.


**Call (717) 780-4400 to find out more. Ask for the AMP SDL Information Desk. AMP Incorporated, Harrisburg, PA 17105-3608.**
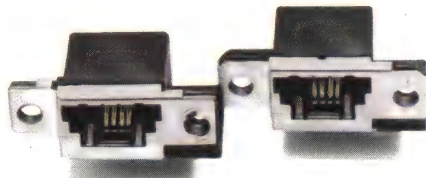
# AMP Interconnecting ideas

*SDL connectors in 4, 6, 8 and 16 contact configurations. Insulation-displacing design, built-in polarization and keying.*



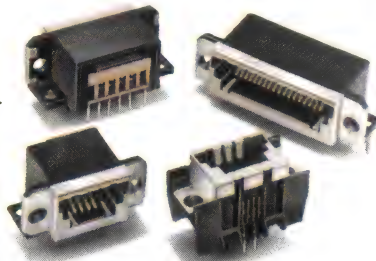*Top or side entry pcb receptacles. Integral shunt versions and side-entry versions with offset mounting ears for close spacing also available.*



CIRCLE NO 163



# MILITARY MODULES AND MONOLITHICS



## MILITARY Cerdips/LCC's Static RAM

SIZE	PIN	SPEED
16Kx1	DP9167	35ns
4Kx4	DP9168	35ns
2Kx8	DP9116	35ns
64Kx1	DP9287	35ns
16Kx4	DP9788	35ns
8Kx8	DP9264	65ns
1Kx8	DP9130*	85ns
2Kx8	DP9132*	85ns
32Kx8	DP92256	65ns
64Kx4	DP9186	35ns

\*Dual Ported

## Dynamic RAM

SIZE	PIN	SPEED
64Kx1	DP9164	100ns
256Kx1	DP91256	100ns
1Mx1	DP9001	100ns

## EPROMS, EEPROMS and HI-REL

M68000 (-55 to +125°C)  
now available

Dense-Pac currently supplies over 80% of the top 25 defense contractors in the United States with their military MIL-STD 883 semiconductor requirements.

Dense-Pac continues to offer the widest range family of high density million bit memory modules. The technologies included in the above modules are SRAM, EEPROM, EPROM, DRAM, VIDEO RAM and NOVRAM.

Dense-Pac also provides complete form, fit and function compatibility with existing memory modules from IDT and EDI. CMOS CPU modules are currently being designed for the **80C31**, **80CX86**, **9450** and **290X** families which include memory and support chips. Challenge the Future - Join the Family!

Contact Sales at:



## ***Dense-Pac Microsystems, Inc.***

7321 Lincoln Way • Garden Grove, California 92641

(714) 898-0007 • (800) 356-2690 (Outside CA)

TWX: 5106011045 • Answerback: DENSE PAC UQ


CIRCLE NO 164


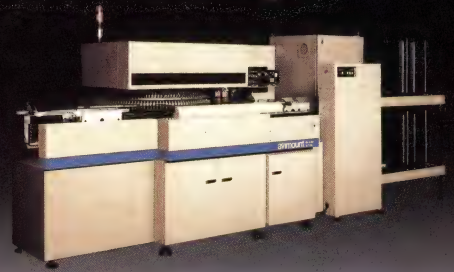
# In Surface Mountable Chip Components. TDK Quality Is More Than Skin Deep.

As boards are getting thinner, TDK is helping that diet succeed by providing a variety of extra-slim surface mountable components. Nourished by TDK's expertise in ferrite and ceramic materials, these miniaturized components feed on TDK-developed multi-layerization and multi-functionalism.

How we know the exact needs of high-quality automated board production? Well, a fair share of the world's automatic mounting equipment—the Avimount series—comes from TDK.




## Multi-layer Ceramic Chip Capacitors

A wide range of capacitances and high dimensional accuracy are instrumental in the production of slim, high-density, quality boards.

Dimensions: A x B x C (mm)	Class I (50V)						
	CH	PH	RH	SH	TH	UJ	SL
3.2 x 1.6 x 0.6-1.1	0.5- 680pF	0.5- 820pF	0.5- 1,000pF	0.5- 1,200pF	0.5- 1,520pF	0.5- 1,500pF	0.5- 2,700pF
2.0 x 1.25 x 0.6-1.1	0.5- 430pF	0.5- 560pF	0.5- 680pF	0.5- 750pF	0.5- 820pF	0.5- 1,000pF	0.5- 1,800pF


Dimensions: A x B x C (mm)	Class II	
	50V	25V
3.2 x 1.6 x 0.6-1.1	1,000- 100,000pF	12,000- 220,000pF
2.0 x 1.25 x 0.6-1.1	470- 47,000pF	6,800- 100,000pF

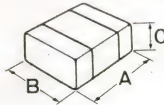

## Multi-layer Chip Inductors (MLF Series)

Coilless chip inductors utilizing TDK's multi-layer ferrite technology. Closed magnetic paths for perfect shielding.


Dimensions: A x B x C (mm)	Inductance (μH)
3.2 x 1.6 x 0.6	0.1~1.2
3.2 x 1.6 x 1.1	0.39~27
3.2 x 2.5 x 1.1	33~56
3.2 x 2.5 x 2.5	68~220

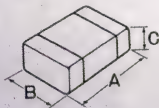

## Multi-layer Chip Transformers, IFT, LC Traps

With the world's smallest transformers, IFT and LC traps (series 4532), TDK advances automated surface mounting by another significant step. Monolithic IFT and LC traps incorporating non-adjustable transformers and capacitors in a single, sintered, multi-layer block. Another world's first from TDK.


Series designation Dimensions: A x B x C (mm)	Applicable frequency range	Characteristics
MTT (transformers) 4.5 x 3.2 x 2.8	300kHz~1MHz	L: 10~200μH
MIA (AM IFT) 4.5 x 3.2 x 2.5	455kHz, 459kHz 464kHz	Q: above 40
MIF (FM IFT) 4.5 x 3.2 x 2.0	10.7MHz	Q: above 40
MXT (LC traps) 4.5 x 3.2 x 2.2	in-series type parallel type	F±2% Attenuation over 20dB

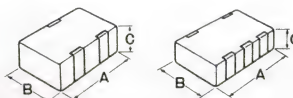

## Leadless Inductors (NL & NLF Series)

Especially suitable for automatic high-density mounting. Epoxy sealed, excellent dimensional accuracy, large inductance, steep Q. High temperature and humidity resistance.


Series designation, Dimensions: A x B x C (mm)	Inductance range (μH)	Q
NL 3.2 x 2.5 x 2.2	0.12~100	20~30
NL 4.5 x 3.2 x 3.2	1.0~1,000	30~50
NLF (shielded) 4.5 x 3.2 x 3.2	1.0~1,000	30~50

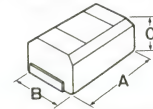

## Ferrite-chip Type Microbeads (CB Series)

Effectively eliminate EMI/RFI and parasitic oscillation vibrations. Suitable for easy, automated surface mounting. Your new, reliable anti-noise (EMI/RFI) weapon. Mounted on circuit board, no need for lead wires.

Dimensions: A x B x C (mm)	Impedance (Ω) at 100MHz	DC resistance Rdc (Ω)
2.0 x 1.25 x 0.9	5~9	0.030~0.033
3.2 x 1.6 x 1.1	14~26	0.048~0.055
3.2 x 2.5 x 1.3	37~77	0.105~0.121
4.5 x 3.2 x 1.5	55~130	0.193~0.212

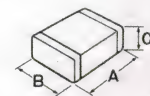

See our Chip Components and other fine products at Electro/86 May 13-15, Bayside Exposition Center, Boston.



CIRCLE NO 204



TDK CORPORATION OF AMERICA HEAD OFFICE 4711 West Golf Road, Skokie, IL 60076, U.S.A. Phone: (312) 679-8200 Telex: 9102230220 (TDK SKO) CHICAGO REGIONAL OFFICE 4711 West Golf Road, Skokie, IL 60076 Phone: (312) 679-8200 Telex: 9102230220 (TDK SKO) INDIANAPOLIS REGIONAL OFFICE 4015 West Vincennes Road, Indianapolis, IN 46268 Phone: (317) 872-0370 LOS ANGELES REGIONAL OFFICE 3102 Kashiwa Street, Torrance, CA 90505 Phone: (213) 539-6631 Telex: 9103496968 NEW YORK REGIONAL OFFICE 12 Harbor Park Drive, Port Washington, NY 11050 Phone: (516) 625-0100 Telex: 144535 (TDK ELECT GRCY) DETROIT DISTRICT OFFICE 3000 Town Center, Suite 2239, Southfield, MI 48075 Phone: (313) 353-9393 HUNTSVILLE DISTRICT OFFICE 303 Williams, Suite 1032, Huntsville, AL 35801 Phone: (205) 539-4551 SAN FRANCISCO DISTRICT OFFICE 2254 North First Street, San Jose, CA 95131 Phone: (408) 435-8565 TDK CORPORATION, TOKYO, JAPAN.



# Feller Power Line Module



K181 USC

*The Power Line Module is based on the Feller Universal Combicon and complies with current multi-function modules. Besides an inlet it contains a voltage selector, with a small PC-board, which may be inserted from the front side of the module. The line voltage is selectable between 100, 120, 220 and 240 V, following the insert position. Incorporated are one or two fuseholders for American respectively European fuses which makes the product especially suitable for export purposes.*

*The dimensions of the cut-out of the new Feller Power Line Module are compatible with others. It is available in both snap-in or screw-mounting types. Its installation is simple and cost-effective.*

*Most of the countries have their own safety standards. For this reason, Feller Power Line Modules have been approved by all important test agencies.*

*Feller PCC, CH-8810 Horgen (Switzerland), Telex 826926  
Telephone 01/725 65 65, Telecopier 01/725 70 12*



*Feller*

**PCC** Primary  
Circuit Components




Dallas Convention Center  
Dallas, Texas  
August 18-22, 1986

A combination of the highest standards in technical achievement, creative artistry and today's most advanced graphics systems.

13th Annual Conference  
on Computer Graphics and  
Interactive Techniques

Sponsored by the Association  
for Computing Machinery's  
Special Interest Group on  
Computer Graphics in  
cooperation with the IEEE  
Technical Committee on  
Computer Graphics.

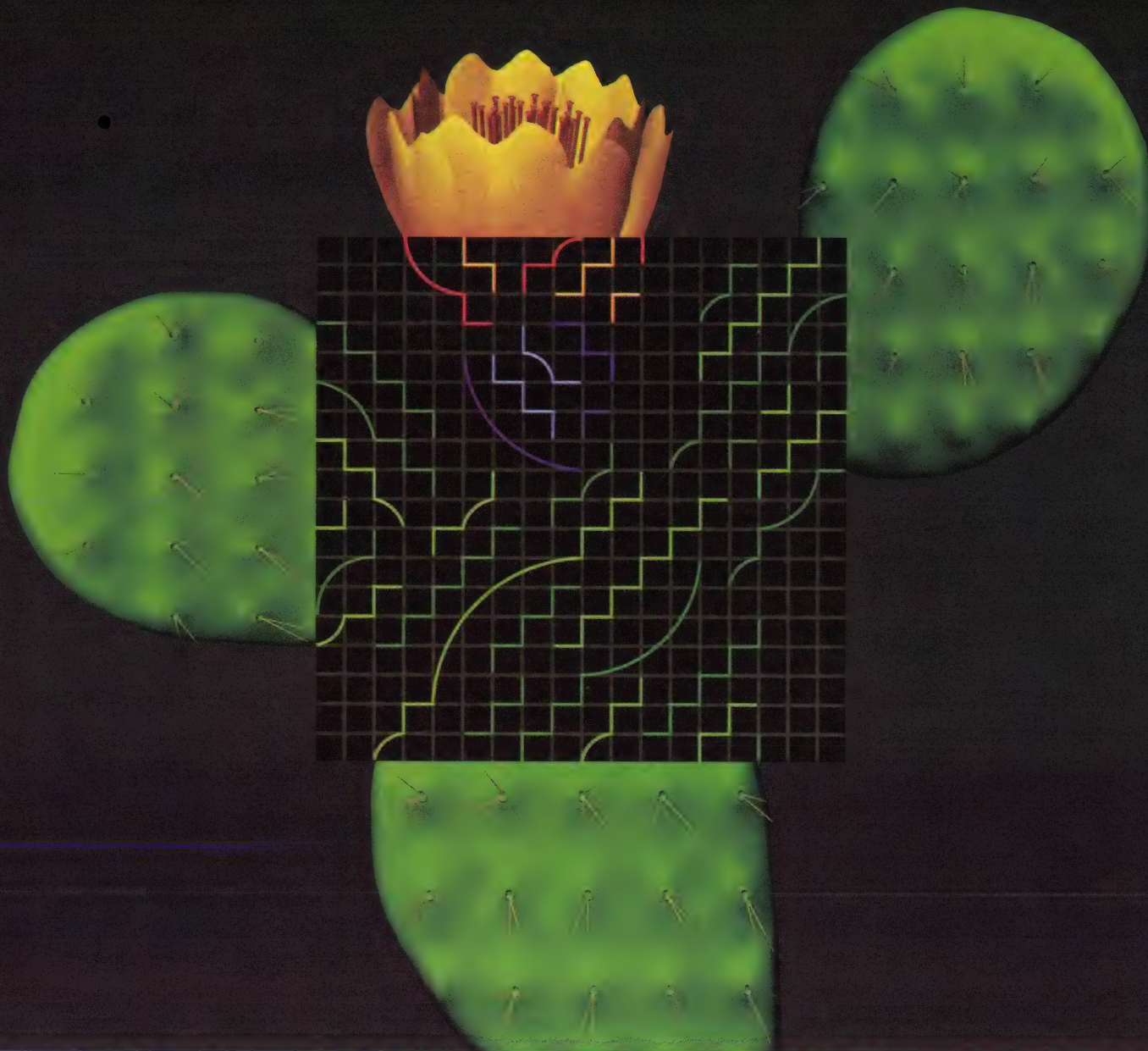Technical Papers  
Panel Sessions  
Courses  
Industry Exhibition  
Art Show  
Electronic Theatre



## ACM SIGGRAPH 86

Conference Management  
111 East Wacker Drive #600  
Chicago, IL 60601  
312/644-6610

Please send a copy of the SIGGRAPH '86 advance program to:

NAME

COMPANY

ADDRESS

CITY/STATE/COUNTRY

ZIP

TELEPHONE

EDN041786

Members of ACM SIGGRAPH will automatically receive these materials in the mail in April and need NOT return this coupon.

8

CIRCLE NO 206

237





# SUDDENLY IT ALL WORKS TOGETHER.

Dallas Semiconductor has simplified design, by providing orderly shutdown and automatic restart for the microprocessor-based system. A power disruption no longer has to mean chaos.

Integrated Battery Backup is an easy three-part solution. The DS1231, power monitor, warns the processor of impending power failure. Then the DS1212, nonvolatile controller, protects the threatened data in up to 16 CMOS RAMs from being garbled during power transients. Simultaneously the DS1260, SmartBattery, secures the data with uninterrupted power from a Lithium source.


The Result? Whether the power flickers or goes out for 10 years your system stays intact.

Call us now for more information

 **DALLAS  
SEMICONDUCTOR**


4350 Beltwood Parkway  
Dallas, TX 75244  
(214) 450-0400

CIRCLE NO 207

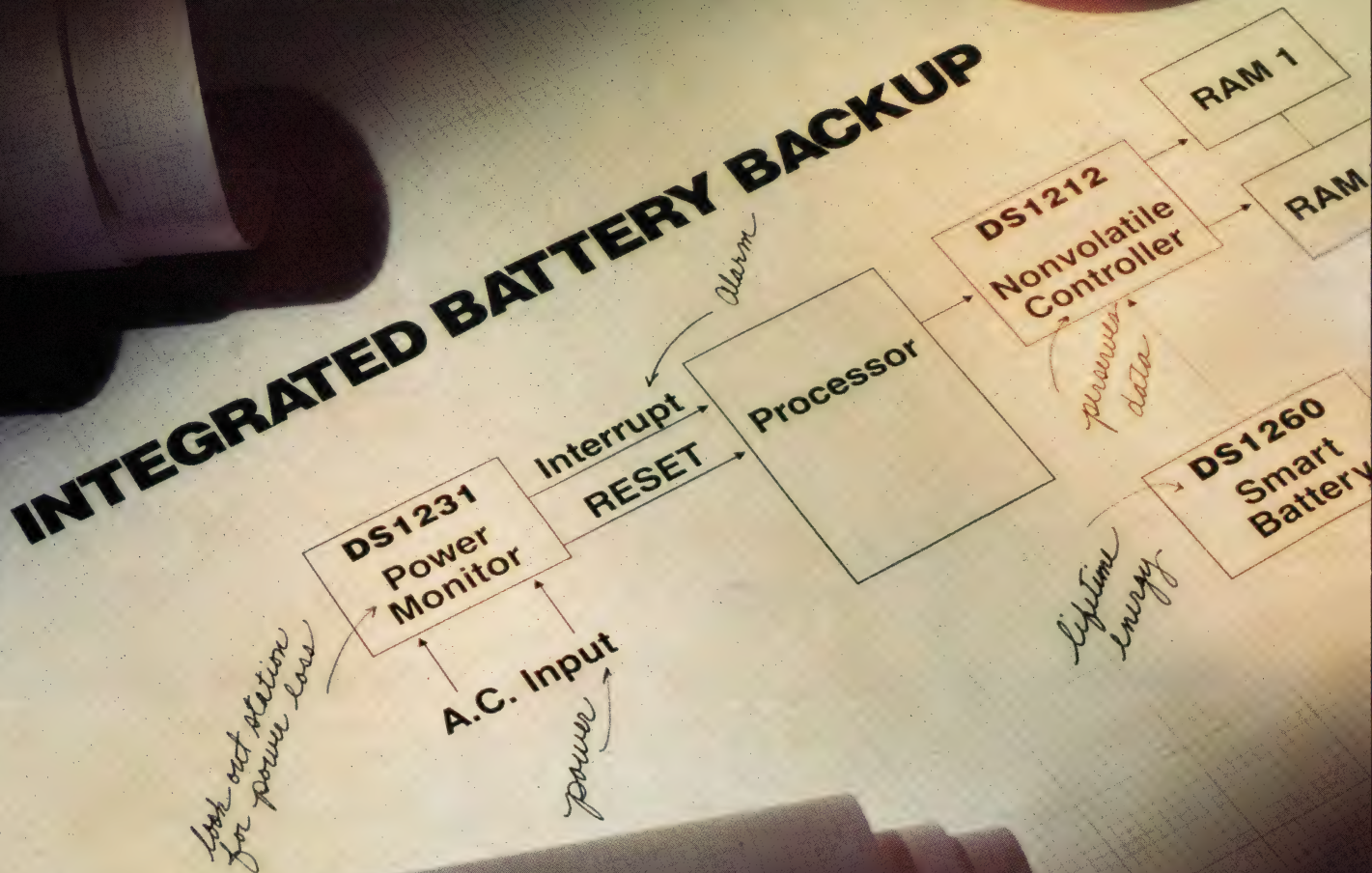



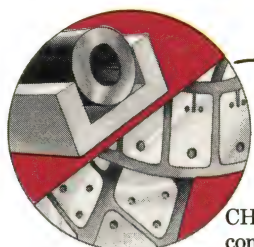
# TODAY'S COMMUNICATIONS ELECTRONICS HAVE CHOMERICS WRITTEN ALL OVER THEM.



**CHO-SEAL®**  
conductive

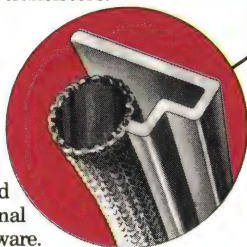elastomers combine EMI and environmental sealing in cellular phone transceivers. CHO-THERM® materials dissipate heat and electrically isolate power transistors.




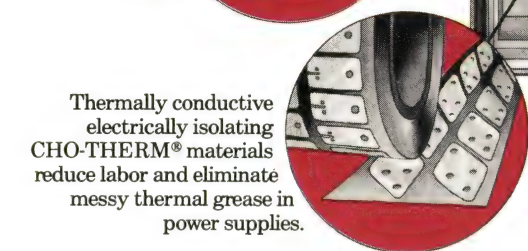**MESHKLIP™**


EMI gasketing with integral mounting clip eliminates riveting, punching, and additional mounting hardware.




Chomerics custom engineered laminates include CHO-STRAP™ insulated ground straps, and cable and PC board shields.



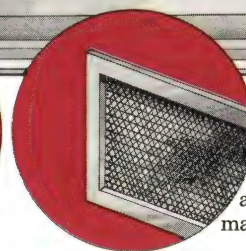
Thermally conductive electrically isolating CHO-THERM® materials reduce labor and eliminate messy thermal grease in power supplies.



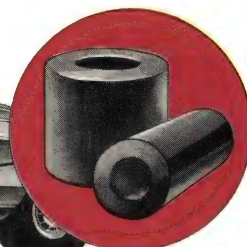Shielded vents and filters attenuate EMI while maximizing air flow.




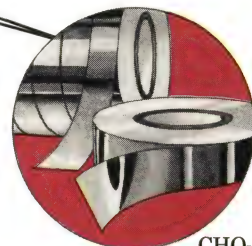**CHO-SORB®** EMI absorbers attenuate 10-15dB on unshielded cables.



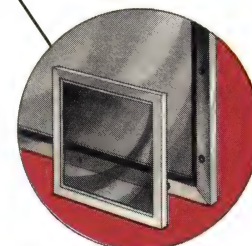**CHO-MASK™**

EMI foil tape with peel-off mask replaces chromate conversion coating, plating, and conductive paints.



Chomerics EMI shielded windows allow viewing inside cabinetry.

Today's rapidly evolving voice, data, and video transmission systems all have one goal in common - to transmit and receive the cleanest signal possible.

At Chomerics, we've been helping design engineers guarantee the performance and integrity of their communications electronics designs through materials technology.

Over the past 25 years our full line of materials and product forms have been incor-

porated into modems, mobile radios, PBX systems, microwave radios, and cellular phone systems.

The signal is clear: for your next communications system design, make sure EMI shielding, sealing, bonding, grounding, and heat transfer components have Chomerics written all over them.

Circle the number or call (617) 935-4850 for additional information.

**CHOMERICS**  
a GRACE company

**THE LEADER IN SHIELDING INNOVATION, DESIGN, AND TESTING TECHNOLOGY.**

77 Dragon Court  
Woburn, MA 01888  
TEL: (617) 935-4850  
TWX: 710-393-0173

Chomerics Europe, Inc.  
First Avenue  
Globe Park Estate  
Marlow, Bucks  
SL7 1YA ENGLAND  
TEL: (06284) 6030





# THE SHORTEST ROUTE TO SOFTWARE DEVELOPMENT.

**Tek's Language Development System (LANDS) is a complete, proven pathway from design to final hardware/software integration.**

Available in "C" or Pascal for the DEC VAX™ under VMS or UNIX,™ LANDS lets you edit, compile, link and debug code for Motorola 68000 and Intel 8086/80186 embedded processors.

**Integrated by methodology and language, LANDS can pare development costs, speed market entry and improve product quality.** A unique Language Editor excludes syntax errors from the compiler. The compiler thus accepts edited code without the cumbersome rechecking delays required by conventional systems.

**An Integration Control System dramatically shortens distances between coding and emulation.** By automating the

error-prone task of assembly language coding for initialization and interrupt handling, it allows you to work swiftly in your high-level language. And it automatically generates the linker command file, correctly assigning constants, variables and instructions from your parameters.



**With LANDS' high-level language debugger, you debug your "C" or Pascal program while it executes**

**in your prototype.** You readily detect program errors; corrections are rapid and precise. Throughout the LANDS environment, tasks that once took days now take hours.

**LANDS is an integral component of Tek's Computer Aided Software Engineering (CASE) program.** This growing toolset cluster from Tek's Software Development Products Division demonstrates Tek's commitment to software technology. For information on LANDS or other CASE products, call 1-800-342-5548, or your Tek representative today.

**CASE: From concept to code, Tek's tools take you all the way.**



# DESIGN IDEAS

EDITED BY TARLTON FLEMING

## Dual one-shot forms frequency discriminator

Gordon F Rogers  
Bradenton, FL

Circuits that include a dual, retriggerable, monostable multivibrator let you sense a frequency threshold (Fig 1) or sense when a frequency  $f_{IN}$  is within preset bounds (Fig 2).

For threshold sensing, you configure  $IC_{1A}$  (Fig 1) as a retriggerable pulse generator of frequency  $f_R$  by selection of an external resistor and capacitor ( $f_R=30$  Hz in this case).  $V_{OUT}$  is low when  $f_{IN}$  is less than  $f_R$ , but the duty cycle of  $IC_{1A}$ 's  $Q_1$  output increases to 100% (dc) as  $f_{IN}$  increases. For this dc condition,  $Q_1$  is high and  $\bar{Q}_2$  is high, so  $V_{OUT}$  is high, indicating  $f_{IN}$  is greater than  $f_R$ .

The 1-k $\Omega$  resistor delays the  $Q_1$  output slightly to compensate for the propagation delay through  $IC_{1B}$ , which will otherwise cause brief output pulses at the  $f_{IN}$  frequency. (Ed Note: To get enough delay, you may need a small capacitor ( $C$ ) as well.)

EDN

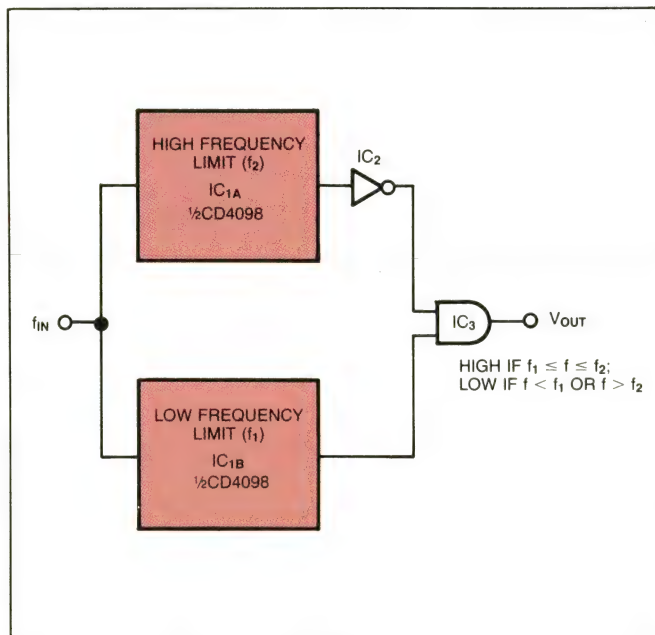


Fig 2—Parallel one-shots form an indicator circuit that determines whether  $f_{IN}$  is in band or out of band.

To Vote For This Design, Circle No 750

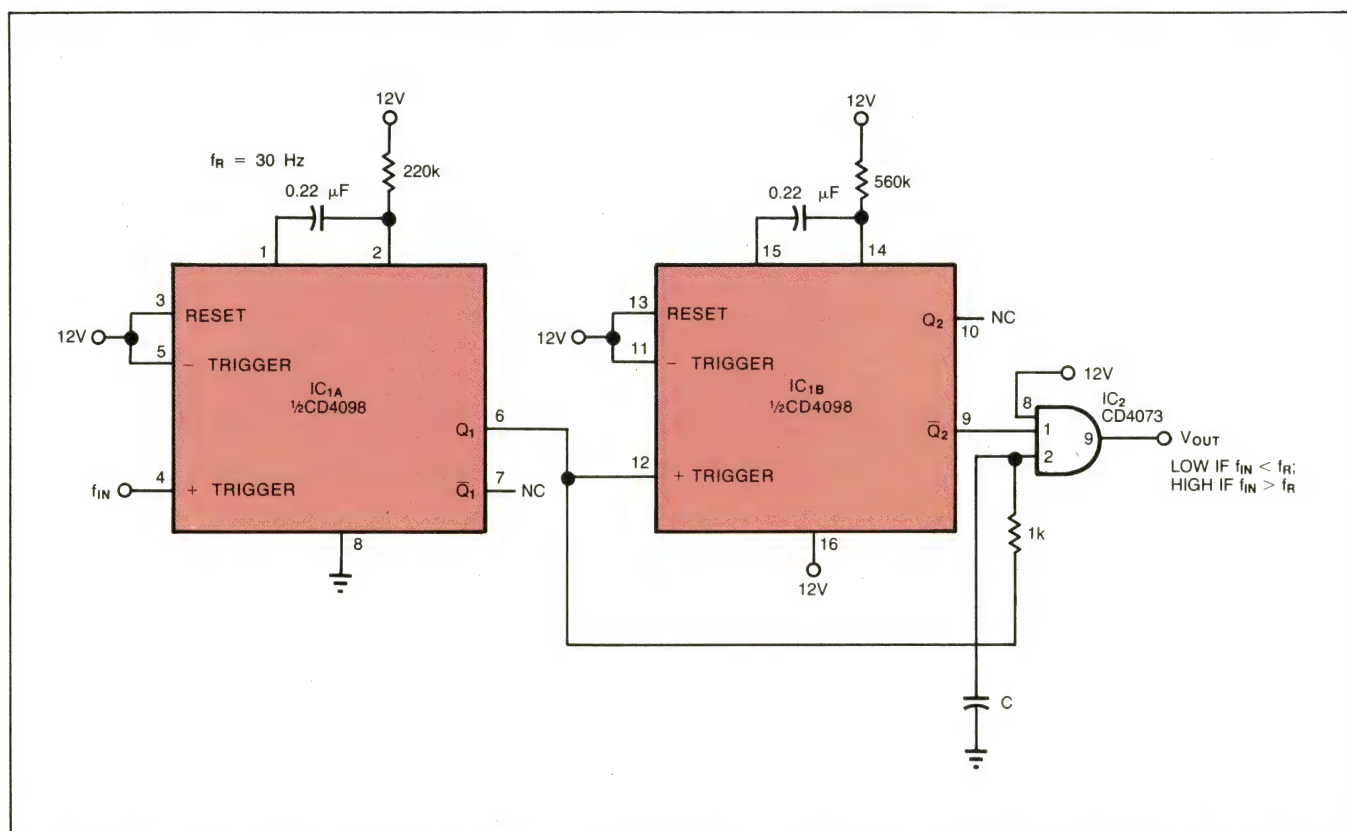


Fig 1—Two retriggerable one-shots form a frequency limit detector.



## Matched FETs provide balanced modulator

Richard C Cabot  
Audio Precision, Beaverton, OR

The balanced modulator circuit of **Fig 1** is suitable for use with two audio-frequency signals. You can apply the carrier to either input (drain or gate port), and you apply the lower-frequency amplitude-modulating signal to the remaining input. Your choice will depend on your application; the drain input provides better feedthrough performance ( $-80$  vs  $-60$  dB), but is less linear than the gate input. The output is zero with either or both inputs removed.

A matched pair of FETs serves as voltage-controlled input resistors for the inverting op-amp stages  $IC_3$  and  $IC_4$ . Because the FETs' on-resistance is inversely proportional to their gate voltage and because the op amps' gain is inversely proportional to the input-resistor value, the op-amp gain is proportional to the FET gate voltage. Further, the two  $2\text{-k}\Omega$  dividers provide a standard method of enhancing the linearity of on-resistance with respect to gate voltage. Feeding  $IC_3$ 's output to  $IC_4$ 's summing junction subtracts the FET source currents. And, because the same signal connects to each drain, the even-order nonlinearity products


cancel—provided that the FETs are properly matched. ( $IC_1$  buffers the drain voltage for use in this linearity compensation. You can eliminate the buffer with only a small increase in intermodulation distortion between the two port signals.)

To compensate for different pinch-off voltages in the FETs, you adjust overall gain using the  $1\text{-k}\Omega$  potentiometer in the output stage. Similarly, you compensate for small mismatches in the FETs' on-resistance by adjusting the  $20\Omega$  potentiometer near  $IC_3$  for minimum drain-signal feedthrough while maintaining  $0\text{V}$  at the gate port. A large resistance ( $2.80\text{ k}\Omega$ ) in series with the FET drains helps to mask further changes in on-resistance.

Intermodulation products between the two ports measure less than  $-90$  dB with the signal levels shown. The gate signal's harmonic distortion is typically  $-60$  dB and predominantly third order. You can reduce this distortion further by tying the  $100\text{-k}\Omega$  resistor to a negative voltage instead of ground, which applies negative bias to the FET gates.

EDN

To Vote For This Design, Circle No 749

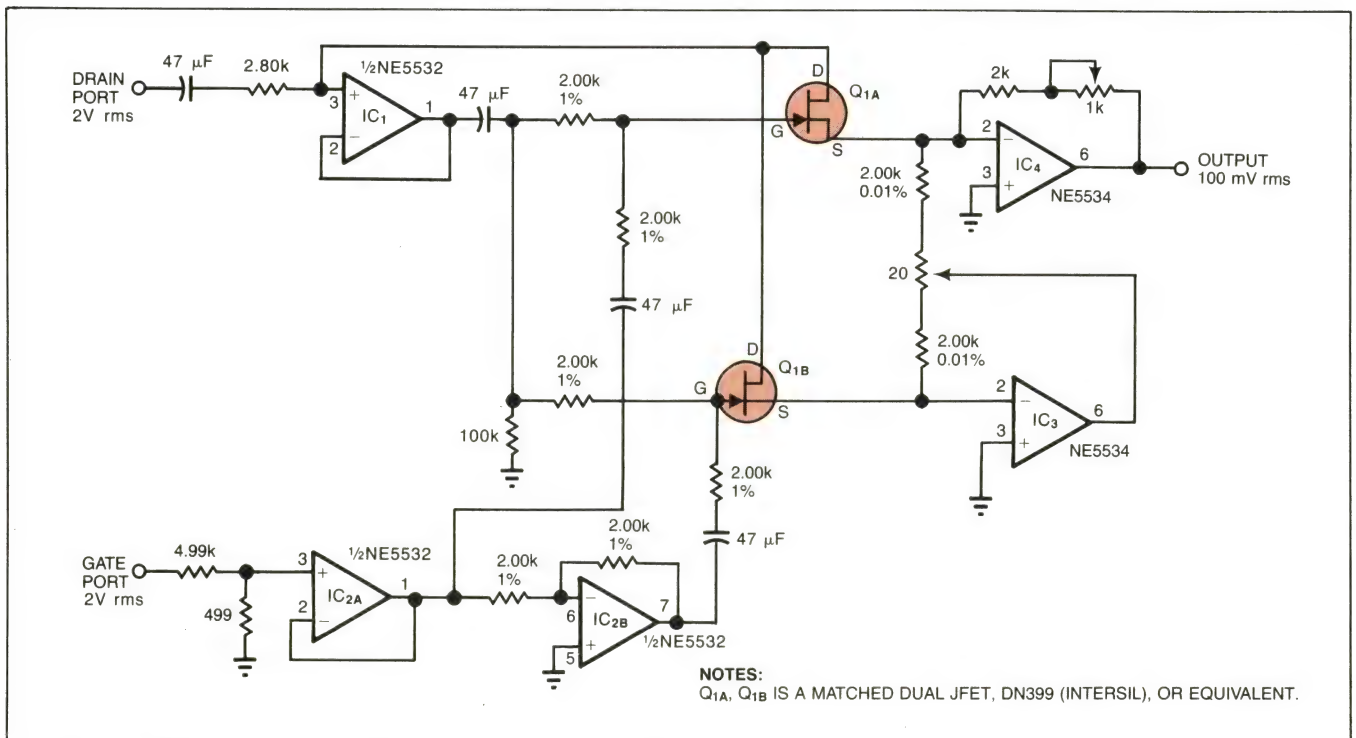

**Fig 1—This balanced modulator for audio frequencies** uses the on-resistance of matched FETs as gain-control elements. Intermodulation distortion (linearity) is better than  $-90$  dB.





# *value-packed* filters **\$9.95** from

dc to 3GHz

- less than 1dB insertion loss over entire passband
- greater than 40dB stopband rejection
- 5 section, 30dB per octave roll-off
- VSWR less than 1.7 (typ)
- over 100 models, immediate delivery
- meets MIL-STD-202
- rugged hermetically sealed package (0.4 x 0.8 x 0.4 in.)
- BNC, Type N, SMA available

finding new ways ...  
setting higher standards

**Mini-Circuits**

A Division of Scientific Components Corporation  
P.O. Box 166, Brooklyn, New York 11235 (718) 934-4500  
Domestic and International Telexes: 6852844 or 620156

LOW PASS	Model	*LP-	10.7	50	100	150	200	300	450	550	600	750	850	1000
Min. Pass Band (MHz)	DC to		10.7	48	98	140	190	270	400	520	580	700	780	900
Max. 20dB Stop Frequency (MHz)			19	70	147	210	290	410	580	750	840	1000	1100	1340
Prices (ea.): P \$9.95 (6-49), B \$24.95 (1-49), N \$27.95 (1-49), S \$26.95 (1-49)														

HIGH PASS	Model	*HP-	50	100	150	200	300	400	500	600	700	800	900	1000
Pass Band (MHz)	start, max.		41	90	133	185	290	395	500	600	700	780	910	1000
	end, min.		200	400	600	800	1200	1600	1600	1600	1800	2000	2100	2200
Min. 20dB Stop Frequency (MHz)			26	55	95	116	190	290	365	460	520	570	660	720
Prices (ea.): P \$12.95 (6-49), B \$27.95 (1-49), N \$30.95 (1-49), S \$29.95 (1-49)														

\* Prefix P for pins, B for BNC, N for Type N, S for SMA

example: PLP-10.7

CIRCLE NO 209

C105 REV. ORIG.



## Lamps improve solenoid-driver efficiency

John A Haase


Colorado State University, Fort Collins, CO

A simple solenoid driver (**Fig 1**) uses incandescent-lamp filaments to limit power consumption. As a welcome side effect, the lamps also serve as on-indicators.

High magnetic reluctance (opposition to flux) in the coil of an armature-driven device (solenoid, relay, etc) calls for a surge of activation current, followed by a lower dc level to remain on (surge to on-current ratio is typically 5:1). You can roughly approximate this current requirement by connecting a lamp filament in series with the coil. The cold filament allows a surge of coil-activation current to pass through; as the filament heats up, it throttles the current to a more reasonable hold value.

The solenoid driver circuit in **Fig 1** offers these features:

- 5V logic swings turn the power-MOSFET switch ( $Q_1$ ) fully on and off.
- Two low-cost flashlight lamps in parallel handle the peak current. Because their dc current is only 50% of peak and because they operate at 60% of their rated voltage, the lamps have an operating life of 12,000 hours. Further, the lamp filaments' positive temperature coefficients raise each fila-

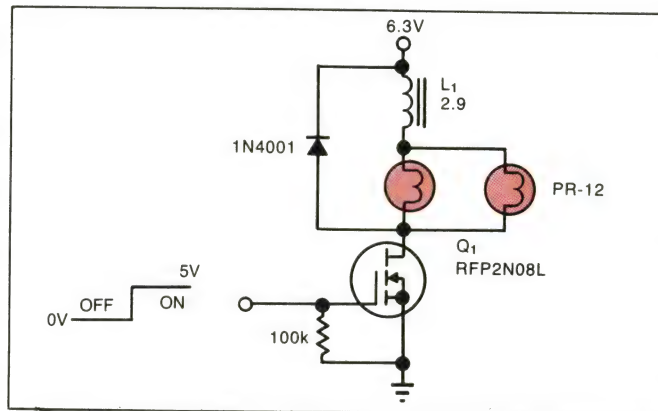

**Fig 1**—This solenoid driver uses PR-12 flashlight lamps to limit the coil's on-current. Five-volt logic swings control power MOSFET  $Q_1$ .

ment's resistance, which eliminates current-hogging problems and provides short-circuit protection.

- Steady-state on-current is 700 mA (vs 1700 mA without the lamps).
- A 4.6V min supply rating allows battery operation.

**EDN**

To Vote For This Design, Circle No 746

## Switching supply is small and efficient

Doug Farrar

Apple Computer Inc, Cupertino, CA

Using inexpensive components, you can build a 15W (3A at 5V) switching supply (**Fig 1**) that fits easily on a 2×3-in. area of a pc board. The circuit converts 12V to 5V±2% and has an efficiency greater than 85%. Further, a bootstrap technique ("Circuit improves switcher's efficiency," EDN, September 19, 1985, pg 242) allows the use of an efficient n-channel power MOSFET as the switching transistor.

Components  $R_1$  and  $C_1$  set the operating frequency (100 kHz) of PWM switching regulator  $IC_1$ . This regulator controls the switching transistor ( $Q_1$ ) via a bootstrap

network consisting of  $Q_2$ ,  $Q_3$ ,  $R_2$ ,  $R_3$ ,  $D_1$ ,  $D_2$ , and  $C_2$ . Bootstrapping provides approximately 23V of gate drive and thus permits use of a MOSFET ( $Q_1$ ).

The main output filter consists of the lowpass network  $L_1$ ,  $C_6$ ,  $C_7$ , and  $C_8$ .  $L_2$  and  $C_9$  provide additional lowpass filtering for higher frequencies, and the resulting output ripple is less than 100 mV p-p. The inductors are wound on low-cost powdered-iron torroids to minimize the generation of external magnetic fields.


If  $Q_1$ 's source current exceeds 4A (corresponding to a dc load current of about 3.5A), the voltage across  $R_3$  and  $R_4$  causes  $IC_1$  to enter its current-limit mode. The Schottky rectifier  $D_3$  functions as a catch diode to improve regulation efficiency.




# MICRO CAP and MICRO LOGIC put your engineers on line... not in line.



## MY OWN WORKSTATION

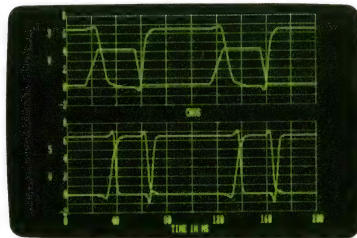

"Typical MICROCAP Transient Analysis"

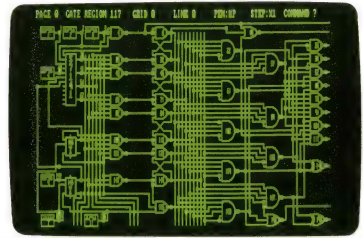

"Typical MICROLOGIC Diagram"

How many long unproductive hours have you spent "in line" for your simulation? Well, no more. MICROCAP and MICROLOGIC can put you on line by turning your PC into a productive and cost-effective engineering workstation.

Both of these sophisticated engineering tools provide you with quick and efficient solutions to your simulation problems. And here's how.

## MICROCAP: Your Analog Solution

MICROCAP is an interactive analog circuit drawing and simulation system. It allows you to sketch a circuit diagram right on the CRT screen, then run an AC, DC, or Transient analysis. While providing you with libraries for defined models of bipolar and MOS devices, Opamps, transformers, diodes, and much more, MICROCAP also includes features not even found in SPICE.

MICROCAP II lets you be even more productive. As an advanced version, it employs sparse matrix techniques for faster simulation speed and larger net-

works. In addition, you get even more advanced device models, worst case capabilities, temperature stepping, Fourier analysis, and macro capability.

## MICROLOGIC: Your Digital Solution

MICROLOGIC provides you with a similar interactive drawing and analysis environment for digital work. Using standard PC hardware, you can create logic diagrams of up to 9 pages with each containing up to 200 gates. The system automatically creates the netlist required for a timing simulation and will handle networks of up to 1800 gates. It provides you with libraries for 36 user-defined basic gate types, 36 data channels of 256 bits each, 10 user-defined clock waveforms, and up to 50 macros in each network. MICROLOGIC produces high-resolution timing diagrams showing selected waveforms and associated delays, glitches, and spikes—just like the real thing.

## Reviewers Love These Solutions

Regarding MICROCAP... "A highly recommended analog design program" (PC Tech Journal 3/84). "A valuable tool for circuit designers" (Personal Software Magazine 11/83).

Regarding MICROLOGIC... "An efficient design system that does what it is supposed to do at a reasonable price" (Byte 4/84).

MICROCAP and MICROLOGIC are available for the Apple II (64k), IBM PC (128k), and HP-150 computers and priced at \$475 and \$450 respectively. Demo versions are available for \$75.

MICROCAP II is available for the Macintosh, IBM PC (256k), and HP-150 systems and is priced at \$895. Demo versions are available for \$100.

Demo prices are credited to the purchase price of the actual system.

Now, to get on line, call or write today!

## Spectrum Software

1021 S. Wolfe Road, Dept. E  
Sunnyvale, CA 94087  
(408) 738-4387




# DESIGN IDEAS

An RC network ( $R_5$ ,  $R_6$ ,  $R_7$ ,  $C_3$ ,  $C_4$ , and  $C_5$ ) provides frequency compensation for the regulator loop. Loop gain is 36 dB at 60 Hz, 30 dB at 120 Hz; phase margin is 60° at unity gain (4.5 kHz).

The regulator generates little heat. Without a heat sink,  $Q_1$ 's case temperature rises about 14.5°C/A of load

current. With a small heat sink (in this case a Thermalloy THM 6025), the rise is about 9°C/A. **EDN**

To Vote For This Design, Circle No 747

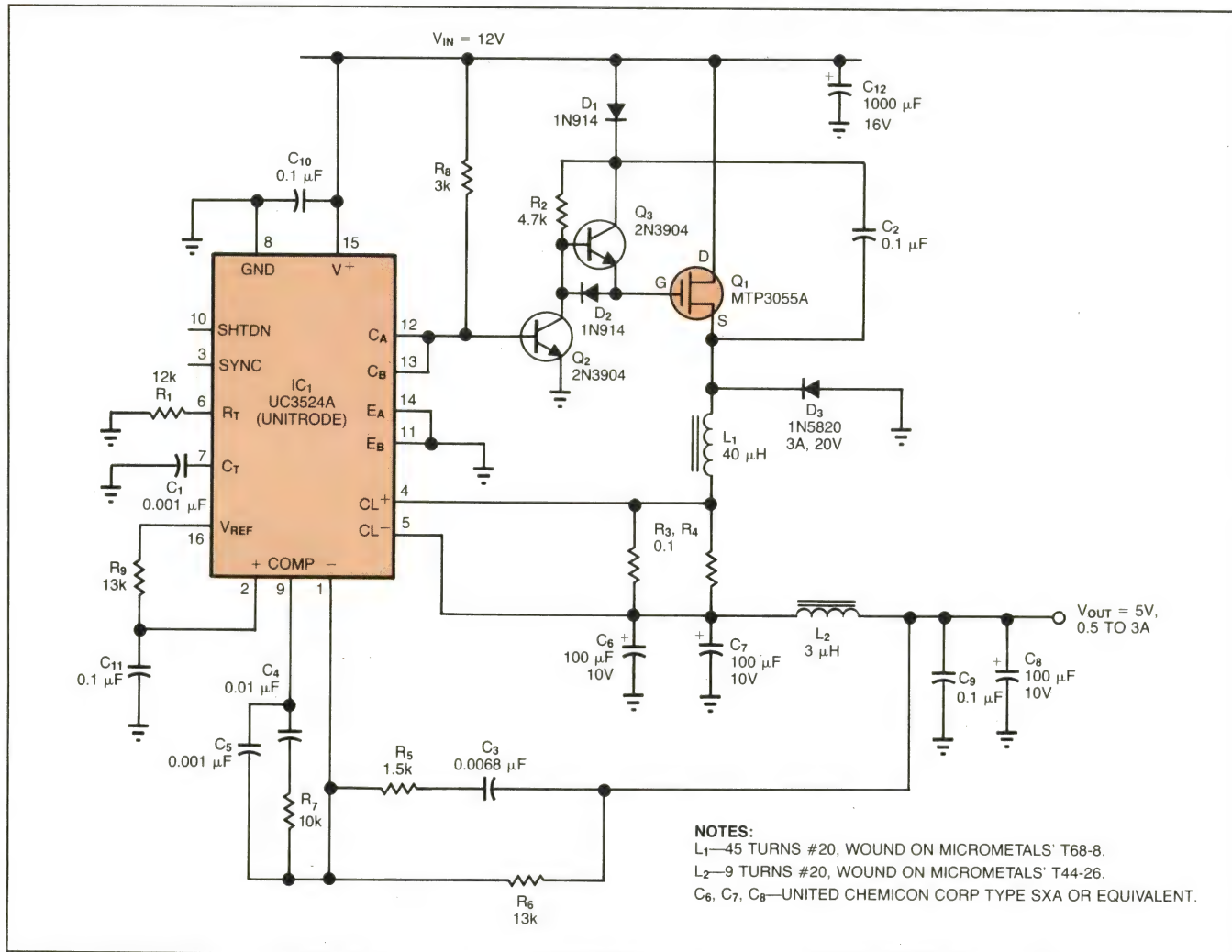

**Fig 1—A switching regulator** uses a PWM regulator IC and, for the switching transistor, an efficient n-channel MOSFET. The circuit converts 12V to 5V  $\pm 2\%$  and boasts better than 85% efficiency. (At 1A, efficiency is about 88%.)

## Square-root algorithm is fast and simple

Robert D Grappel  
MIT Lincoln Laboratory, Lexington, MA

Most software routines for the calculation of square roots are based on the Newtonian-iteration algorithm

or the shift-and-subtract algorithm. Shift-and-subtract routines are usually written in assembly language and are therefore fast, whereas the Newtonian-iteration routines are easy to express in high-level languages, but run somewhat slower. A third algorithm, however,



# How to turn your mounting problems into mounting profits.

**The need to mount LED indicators onto printed circuit boards can create costly production problems. General Instrument Lamp Division offers a whole family of time-saving, profit-making solutions.**

Our pre-assembled LED indicator packages, delivered on-time, on-spec and ready for ONE-STEP installation, can increase your production rates while reducing the cost of inventory, equipment and labor.

**1** Here's a new angle on right angle LED mounting. Our StatusPak™ system lets you mount from one to 12 right angle LEDs as a single unit. Choose from over 500,000 combinations of 10 LED colors, brightness intensities up to 60mcd, wide or narrow viewing angles and positioning. Select T-1 or T-1½ LEDs.



Each StatusPak is unitized and vibration resistant to ensure maximum stability during and after mounting. Housings are black to provide high contrast with LEDs.

**2** StatusPak also is available with rectangular LEDs, in your choice of vertical or horizontal positioning. Ideal for bar graphs, function and status modes, and back-lighting.



**3** Where vertical mounting is needed, our SpaceSetter™ system reaches new heights in convenience and economy. Individual T-1 and T-1½ LEDs feature an integral mounting spacer, provided to the exact length from .200" to .900", and ready for easy mounting. No more trouble with assembling separate LEDs and "doughnut" type spacers.



**4** And when you need to mount from two to 12 LEDs at a preset height, use our SpaceSetter MultiPak. We'll ship these units to you pre-assembled, arranged in any color sequence, with single-in-line or dual-in-line packaging. Perfect for through panel displays.



**5** It is easy to see how StatusPak and SpaceSetter Circuit board indicators can help you turn mounting problems into mounting profits. Call General Instrument Lamp Division today at 312/784-1020 or write Mr. Dan Savocchia at 4411 N. Ravenswood Ave., Chicago, IL 60640. We'll send you complete information and the names of authorized distributors in your area.



**GENERAL  
INSTRUMENT**  
Lamp Division

The reasons to switch are mounting.



# DESIGN IDEAS

## Design Entry Blank

**\$75 Cash Award for all entries selected by editors. An additional \$100 Cash Award for winning design each issue, determined by vote of readers. Additional \$1500 Cash Award for annual Grand Prize Design, selected among biweekly winners by vote of editors.**

To: Design Ideas Editor  
EDN  
Cahners Publishing Co  
275 Washington St, Newton, MA 02158

I hereby submit my entry for  
EDN's Design Ideas program.

Name \_\_\_\_\_

Title \_\_\_\_\_ Phone \_\_\_\_\_

Company \_\_\_\_\_

Division (if any) \_\_\_\_\_

Street \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Design Title \_\_\_\_\_

Home Address \_\_\_\_\_

Social Security No \_\_\_\_\_

**Entry blank must accompany all entries.** Design entered must be submitted exclusively to EDN, must be original with author(s), must not have been previously published (limited-distribution house organs excepted), and must have been constructed and tested.

Exclusive publishing rights remain with Cahners Publishing Co unless entry is returned to author or editor gives written permission for publication elsewhere.

In submitting my entry, I agree to abide by the rules of the Design Ideas Program.

Signed \_\_\_\_\_

Date \_\_\_\_\_

**Your vote determines** this issue's winner. All designs published win \$75 cash. All issue winners receive an additional \$100 and become eligible for the annual \$1500 Grand Prize.

**Vote now**, by circling the appropriate number on the reader inquiry card.

**Submit your own design**, too. Mail entries to Design Ideas Editor, EDN, 275 Washington St, Newton, MA 02158.

is fast and is easy to express in a high-level language as well.

The basis for this algorithm is a mathematical theorem stating that a perfect square is equal to the sum of a sequence of odd integers, and the number of terms in the sequence gives the integer square root. (For example, the sum of the first five odd integers is 25.) The following C function shows how easily you can express this algorithm in high-level form:

```
int square_root(arg) int arg;
{
    int sq;

    if (arg <= 0) return 0; /* special cases */
    for (sq = 1; sq < arg; sq += 2)
        arg -= sq;
    return ((sq + 1)/2); /* round count */
}
```

This routine returns a square-root value quickly for small arguments, but slows as you increase the size of the argument.

You can also code this algorithm very efficiently in assembly language, as illustrated in the following subroutine for the 68000  $\mu$ P:

SQRT	TST.L D0	ARGUMENT == 0?
	BEQ.S SQRTN	YES, RETURN-IT
*		
	MOVE.L D1, -(A7)	SAVE D1
	MOVEQ #-1, D1	INIT. ODD
*		
LOOP	ADDQ.L #2, D1	NEXT ODD INTEGER
	SUB.L D1, D0	DONE YET?
	BGT.S LOOP	IF NOT, LOOP
*		
	ADDQ.L #1, D1	ROUND UP
	LSR.L #1, D1	
	MOVE.L D1, D0	RETURN IN D0
	MOVE.L (A7)+, D1	RESTORE D1
SQRTN	RTS	

The calling routine passes the unsigned 32-bit argument to the subroutine in register D0, and the subroutine returns the square root in that same register; all other registers are preserved. This routine requires about 100 clock periods for an argument of 4, 290 periods for an argument of 100, and 1480 periods for an argument of 4096. For comparison, a 68000 shift-and-subtract routine (*Dr Dobb's Journal*, May 1985, pg 122) requires between 1480 and 1832 periods, depending on the size of the argument, and it doesn't preserve the working registers.

**EDN**

**To Vote For This Design, Circle No 748**



# IN OPTO COUPLERS, TOSHIBA'S 600% CURRENT TRANSFER RATIO IS THE DIFFERENCE BETWEEN BLACK & WHITE.

White mold — Toshiba's patented material — makes possible the highest current transfer ratio available — up to 600% for transistor output. With correspondingly lower driving current, longer life and greater reliability.

This kind of technological superiority is one reason why Toshiba is the world's largest maker of opto couplers.

But whether you want high CTR, isolation voltage up to 5000V AC — or speed up to 10 MHz — with UL and VDE/BSI approvals, you want Toshiba.

Call or write today for Toshiba's Opto Coupler product summary.

**SOME TYPICAL PHOTOCOUPLER APPLICATIONS**  
(Call for Information on Additional Products)

	PROGRAMMABLE CONTROLLER	SSR	POWER SUPPLY	INVERTER	OFFICE AUTOMATION	TELE- COMMUNICATION
TR OUTPUT	TLP620-4 4N35 TLP535	4N35 TLP535	TLP581 TLP633	4N25	4N35 TLP535	4N35 TLP504A
DARLINGTON TR OUTPUT	TLP571 4N32				TLP571 4N32	TLP571
HIGH SPEED	TLP2601 6N135			TLP2601 6N137		
THYRISTOR OUTPUT	TLP545J TLP641J	TLP545J TLP641J				TLP541G
TRIAC OUTPUT	TLP560G TLP561G		TLP760G		TLP560G TLP561G	

**TOSHIBA OPTO COUPLERS.**  
**THE DIFFERENCE BETWEEN BLACK AND WHITE.**  
**TOSHIBA AMERICA, INC.**

TOSHIBA AMERICA, INC., 2692 DOW AVENUE, TUSTIN, CALIFORNIA 92680. AREA SALES OFFICES: WESTERN AREA, TOSHIBA AMERICA, INC., (714) 832-6300; CENTRAL AREA, TOSHIBA AMERICA, INC., (312) 945-1500; EASTERN AREA, TOSHIBA AMERICA, INC., (617) 272-4352.

DISTRIBUTED NATIONWIDE BY TIME ELECTRONICS, INC.: ARIZONA, TIME ELECTRONICS, (602) 967-2000; CALIFORNIA, ITAL ELECTRONICS, (714) 990-0922, TIME ELECTRONICS, (714) 937-0911, (818) 998-7200, (619) 586-1331, (408) 734-9888, (213) 320-0880; COLORADO, TIME ELECTRONICS, (303) 799-8851; CONNECTICUT, TIME ELECTRONICS, (203) 271-3200; FLORIDA, TIME ELECTRONICS, (305) 974-4800, (305) 841-6565; GEORGIA, TIME ELECTRONICS (ELECTRO AIR), (404) 351-3545, (404) 448-4448; ILLINOIS, TIME ELECTRONICS, (312) 350-0610; MARYLAND, TIME ELECTRONICS, (301) 964-3090; MASSACHUSETTS, TIME ELECTRONICS, (617) 532-6200; MINNESOTA, TIME ELECTRONICS, (612) 944-9192; MISSOURI, TIME ELECTRONICS, (314) 391-6444; NORTH CAROLINA, TIME ELECTRONICS, (704) 522-7600; NEW YORK, TIME ELECTRONICS, (516) 273-0100, (315) 432-0355; OHIO, TIME ELECTRONICS, (614) 761-1100; OREGON, TIME ELECTRONICS, (503) 684-3780; PENNSYLVANIA, TIME ELECTRONICS, (215) 337-0900; TEXAS, TIME ELECTRONICS, (214) 241-7441, (713) 530-0800; UTAH, TIME ELECTRONICS, (801) 973-8181; WASHINGTON, TIME ELECTRONICS, (206) 882-1600.

© 1986 Toshiba America, Inc.




# DC/DC CONVERTERS. SMALL IN SIZE. BIG IN POWER.

## COMPACT DC/DC CONVERTER UNITS

The PKA Series of 25-40W DC/DC converters are extremely lightweight, compact units, having single, dual and triple outputs with +24V or -48V inputs.


## BEAUTIFULLY SIMPLE

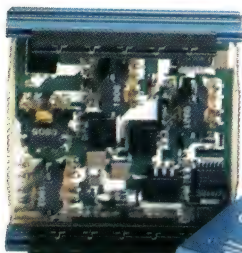

Complete units which are simple to use and are directly pc board or chassis mountable. No extra components. And no extra cooling.
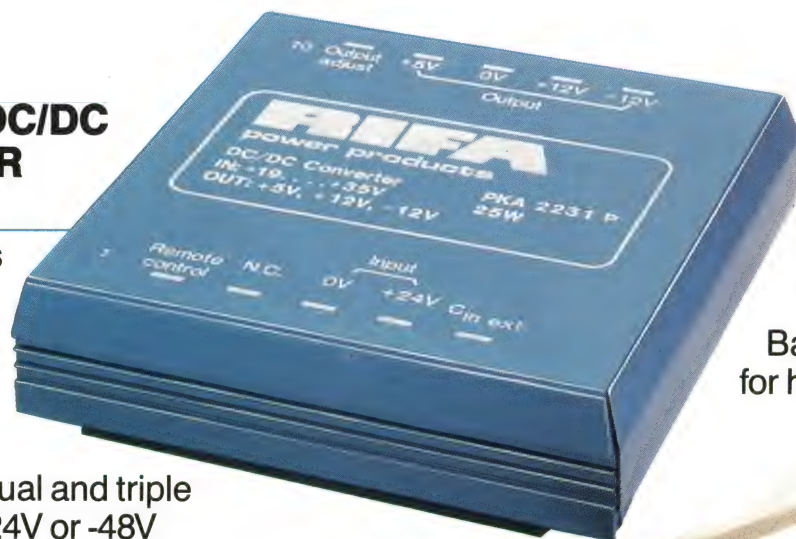
## POWER PLUS

With a switching frequency of 300 KHz, the PKA Series



results in a MTBF in excess of 200 years.

## EASILY PARALLELED

Balanced load sharing for higher, more flexible or redundant power.

## AUTOMATED MANUFACTURE AND TEST

Automated production, assembly and test procedures provide continuity of manufacture, ensuring consistent

## MATCHLESS PRICE, PERFORMANCE, DELIVERY.

offers very high power density in a cost-effective package. Highly efficient, with no derating of the output power from -45°C to +85°C.

## ULTRA RELIABILITY

The unique hybrid design and production techniques employed yield extremely cool operation and low component stress, which



reliability, performance and availability. This series of standard DC/DC converters is

available off-the-shelf. For a free, life-size mechanical sample, write Rifa Inc., Greenwich Office Park 3, P.O. Box 3110, Greenwich, CT. 06836-3110. Or call (203) 625-7300.

# RIFA INC.

ERICSSON  RIFA is a member of the Ericsson Group.

See us at Electro Show Booths 1612-1617





# Who brings you even more designer enclosures than ever before?

**Who but Hoffman. We've added more sizes and styles to give you even more flexibility in your enclosure specification.**

Things haven't changed. You still need to protect those delicate components from dust, dirt and other contaminants. But you still want that protection to blend aesthetically with your high-tech equipment design.

Hoffman engineers have expanded their DesignLine™ series to include more sizes of Instrument Enclosures and NEMA Type 13 units. They have also added five new Electronic Rack Enclosures to accommodate 19 inch or 24 inch rack mounted electronic equipment. Plus six modular and gasketed Environmental Electronic Enclosures with functional openings on all sides,

including top and bottom.

All DesignLine Enclosures provide a number of unique features:

1. Covers and doors are easily removable and interchangeable.
2. Doors are held closed by

nearly flush, oil-tight latches.

3. Oil-resistant gaskets are held in place with oil-resistant adhesive.
4. Textured beige polyester powder coating is electrostatically applied on phosphatized metal surfaces.
5. Wide choice of options and accessories.

For complete specifications and applications information, contact your Hoffman representative. Or contact us.



**Your informed source.**

## *Hoffman*®

HOFFMAN ENGINEERING COMPANY  
Division of Federal Cartridge Corporation  
Anoka, Minnesota 55303. (612) 421-2240  
Dept. EDN-852



# How to put a whole new light on your next product design.

This EL Shopping Guide comes to you courtesy of Endicott Research Group, Inc., innovators of commercially feasible Smart Force™ power for electroluminescent lighting.



## EL Lamps

Wafer-thin, energy-efficient electroluminescent lamps, made in a variety of shapes and colors, have opened the doors on virtually limitless design options for automotive, architectural, aviation instrumentation, marine, safety, and novelty products. They're used both for primary and secondary light sources, and for signaling and decorating in a host of consumer, industrial and military applications. Throw a whole new light on your product design with EL — electroluminescence.




## Liquid Crystal Displays

Against EL backlighting, LCD (transmissive or transreflective) characters can be seen in low ambient light conditions. Particularly useful in instrument panel applications! LCD's can be ganged against large scale EL panels for multiple alphanumeric information displays which offer design and economy advantages versus CRT and screened image information displays.


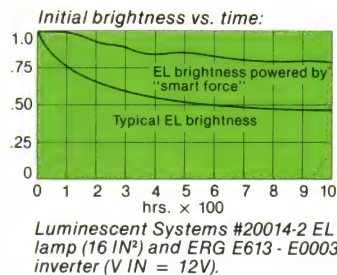
## "Membrane" Switches

EL backlighting enhances the aesthetics of touch-activated switches and keyboards. Creates better legibility in low ambient light conditions, too. Choose the "membrane" switch format which suits your design: flat, bubble top or keytop.



Made in U.S.A.

Patent pending

## Smart Force™ Power Inverter

This DC-to-AC inverter overcomes the brightness loss characteristic of EL lamps. Because it automatically adapts its own voltage and frequency over the course of EL lamp life, this Smart Force™ DC-to-AC inverter delivers constant power output, maintaining essentially constant lamp brightness. We'll be glad to help you determine the specs on your DC-to-AC inverter needs. Refer to our EL power "spec starter" sheet.




EL power starts here!



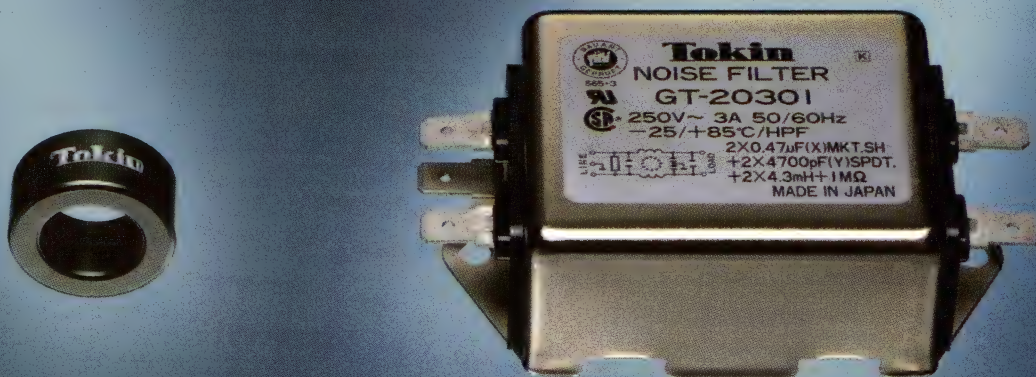**Endicott Research Group, Inc.**

2601 Wayne Street, PO Box 269, Endicott, NY 13760  
607-754-9187 TWW510-252-0155





# You are looking at the source behind Tokin's expanding EMC services.

All technology at Tokin begins with basics, in the very materials that make electronic progress possible. The EMC product on the right is a direct beneficiary of that slice of ferrite on the left.

This solid background in magnetic materials and devices coupled with an irresistible urge to move forward, has made Tokin one of the premier exponents in the war against electronic noise.

Our EMI/EMC Power-line Filters and Data-line Filters have achieved compliance with exceedingly strict

standards. The EMC standards including the FCC, CISPR and VDE, as well as the safety standards of the UL, CSA and VDE/TÜV.

Achievements worthy of quiet satisfaction.

## ANNOUNCEMENT: OPENING OF NEW LABORATORY IN U.S.A.

### ETCL (EMC Test and Component Laboratory)

The EMC technical services available through our ETCL in San Jose, Calif. include measurement and countermeasures conforming to international standards such as FCC and CISPR in addition to Japanese and other standards, also the prototype development of EMC and Transformers/Inductors Components. For details contact Tokin America Inc.

## EMI/EMC Power-line Filters



GL-EP type



MA type



GL-F type



SC-J type



SU-Coil

## EMI/EMC Data-line Filters




ST-Series



DIP-Filter



Filter Capacitor

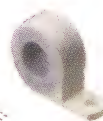

ESD-R type



Bead Inductors



ESD-FPL type

## Tokin Corporation

Head Office: Hazama Bldg., 5-8, Ni-chome, Kita-aoyama, Minato-ku, Tokyo 107, Japan  
Tel.: Tokyo (03) 402-6166 Telex: 02422695 TOKIN J

### Tokin America Inc.

2261 Fortune Drive, San Jose, California 95131 U.S.A. Tel.: 408-946-4887

### You can reach our agents by phone:

London (01) 837-2701; Paris (1) 534-7535; Milan (0331) 67-8058; Munich (089) 59-4621; Seoul (02) 777-5767; Taipei (02) 731-1425; Hong Kong (3) 31-5769; Singapore 747-8668; Sydney (2) 922-7566

# Tokin



# WE THINK YOUR CAREER NEEDS SOME CLOSE ATTENTION.



That's why we've created **EDN Career News**. It's the one publication focused entirely on the career concerns of electronics engineers. And it's the added source you need to find new career opportunities.

**EDN Career News** expands **EDN's** career coverage with the same first-rate editorial that's made **EDN** first among electronics engineering publications. **Career News** looks at the legal and government-related issues affecting the electronics industry. And at personal growth issues to help you reach your professional potential.

Join the 300,000 electronics engineers and engineering managers who pay attention to **EDN Career News** each month. It will make a difference in your career.

**EDN**  
CareerNews

**For Professional Growth and Development**


Roberta Renard, National Sales Manager  
475 Park Avenue South, New York, N.Y. 10016 (212) 576-8045

**Cahners Publishing Company**

- Publishers of 35 specialized business magazines in Building & Construction
- Electronics & Computers • Foodservice • Manufacturing • Medical/Health Care


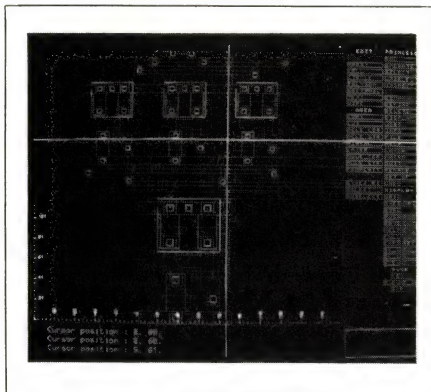
# NEW PRODUCTS: COMPUTER-AIDED ENGINEERING




## IC LAYOUT

The Princess system provides an integrated package, from schematic entry to layout, for full-custom, semicustom, standard-cell, and gate-array designs. When using the software, you perform normal input via hierarchical on-screen menus or via the keyboard. You can customize the package with programmable function keys, macrocommands, or batch files. An interface to the NCA's FDR format facilitates mask data preparation. The system runs on DEC minicomputers and workstations and on Apollo workstations. \$25,000.

**Silvar-Lisco**, 1080 Marsh Rd, Menlo Park, CA 94025. Phone (415) 324-0700.

Circle No 350

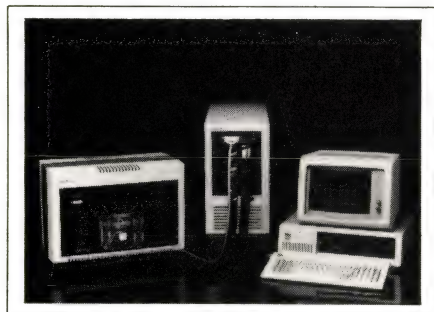

## IC TESTER

A parametric measurement unit (PMU) incorporated into the Logic Master Series allows you to measure and verify physical parameters of prototype ICs. Parameters include input current, output voltage levels, output current or drive capability, and input-voltage level sensitivity for high and low logic levels.

The unit includes a switching matrix-verification station for creating a fixture for the device under test. The matrix allows the user, under program control, to disconnect the tester's drivers and receivers from the device and then connect the unit's sockets to the desired pins of the IC for measurement. A software feature, Auto-Measure, automatically develops a parametric test sequence covering every pin on the device under test. After the test has run, a report is issued with the measurement results. Two versions of the unit are available: The PMU-1001 provides a switching matrix to support as many as 192 channels; the PMU-2001 provides a matrix for as many as 384 channels. Both systems permit the user to force voltage and measure current, or to measure voltage and force current on any pin of the IC under test. PMU-1001, \$19,200; PMU-2001, \$31,200. Delivery, 16 weeks ARO.

**Integrated Measurement Systems Inc.**, 9525 SW Gemini Dr, Beaverton, OR 97005. Phone (503) 626-7117.

Circle No 351

## GRAPHICS DISPLAY

The 9250 terminal interfaces to the MicroVAX II. The terminal provides translucent and opaque surfaces; X-, Y-, and Z-axis clipping of objects; flat shading; depth cuing; perspective; homogeneous transformations; and surface textures, patterns, and meshes. It also edits display lists, emulates DEC's VT 100, and highlights objects. \$55,000.

**Megatek Corp.**, 9645 Scranton Rd, San Diego, CA 92121. Phone (619) 455-5590.

Circle No 352


## GRAPHICS EDITOR

Rgraph performs schematic capture and physical layout of pc boards and ICs. The software supports both 1024x768-pixel and 640x400-pixel monitors and offers a selection of 16

colors from a palette of 4096. This graphics editor uses 2-letter mnemonics that relate to the English commands they represent. Libraries include TTL, CMOS, analog, and ECL. Each database can have nine libraries for source entities; each library can contain 600 entities. The package also features rubberbanding and three types of cursor controls: mouse, graphics tablet, and keyboard. It can generate output to plotters manufactured by Houston Instruments, Hewlett-Packard, CalComp, Nicolet, and Gerber. A digital simulation package is optional. \$3000.

**Aptos Systems Corp.**, 4113 Scotts Valley Dr, Scotts Valley, CA 95066. Phone (408) 438-2199.

Circle No 353

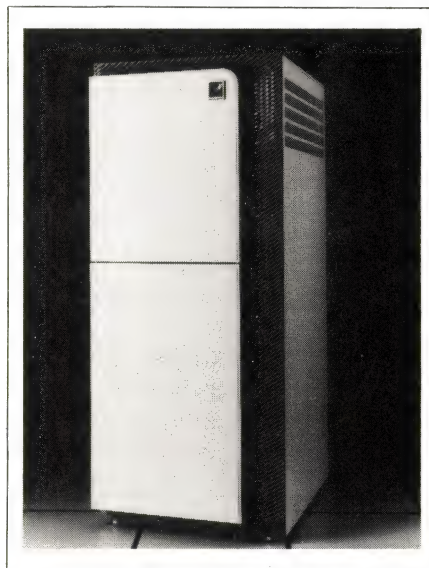

## PARALLEL COMPUTER

Configurations of the Balance 21000 can include as many as thirty 32-bit processors. The computer can also include as much as 48M bytes of memory, 10G bytes of disk storage, and as many as 256 terminal lines. The system runs at speeds ranging from 2.8 to 21 MIPS. The speed of the computer increases almost linearly with the addition of processors. The Dynix operating system, a version of Unix 4.2, supports the Unix System V interface standard and user interface. \$139,000 to



# Iwatsu translates 30 years of leadership into a line-up of unlimited scope



**Presenting multi-channel, multi-function instruments delivering extraordinary intelligence, speed and ease of operation.**

**CAPTURE SIGNALS UP TO 12.4 GHz** with Iwatsu SAS-8130 Sampling Oscilloscope. Features 2 plug-in sampling heads, 10-bit 1k-word memory per channel, standard GP-IB, automatic waveform search and auto ranging. Also saves 15 programs and executes sequentially.

**DIGITALLY STORE 100-MHz SINGLE SHOT SIGNALS** with Iwatsu TS-8123 Storage Scope. Features 3000 cm/ $\mu$ s

writing speed, 8-bit vertical resolution, standard GP-IB and digitizing speed of 1200 cm/ $\mu$ s [equivalent to 40 ps (25 GHz) clock].

**OBSERVE TWO SIGNALS SIMULTANEOUSLY** with Iwatsu DS-8122 Dual Beam Oscilloscope with 3 plug-in compartments. The oscilloscope features 1-gun, 2-beam high luminance CRT, 100 MHz Bandwidth and digital display of data.

**USE IWATSU'S GENERAL PURPOSE MAIN-FRAME SS-8120** as a 4-channel 100 MHz oscilloscope, a 4-channel 1 GHz sampling oscilloscope or as an 11 MHz spectrum analyzer, depending on plug-in selections.

**PLUG-INS** include vertical dual-trace amplifier, horizontal dual timebase, delay line, vertical and horizontal sampling units and digital measuring unit.



**IWATSU INSTRUMENTS INC.**

**Instruments of your success.**

See us at Electro Booth #'s 192 — 194 Bay Side

430 COMMERCE BOULEVARD, CARLSTADT, NJ 07072 PHONE: (201) 935-5220, TLX. 710-989-0255




## COMPUTER-AIDED ENGINEERING

\$500,000; upgrade of the Balance 8000, \$39,000.

**Sequent Computer Systems Inc.**, 15450 SW Koll Parkway, Beaverton, OR 97006. Phone (503) 626-5700.

Circle No 354

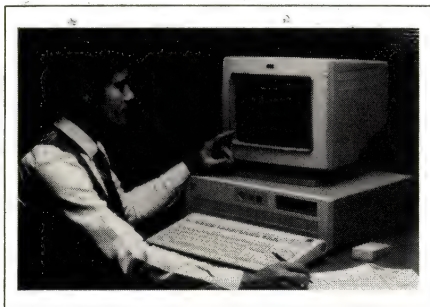

### CAE WORKSTATIONS

The RT PC line of 32-bit workstations includes one desktop and three floor-standing models. The units contain a 32-bit  $\mu$ P that uses a RISC architecture. The workstations use the company's Advanced Interactive Executive (AIX) operating system. As many as eight users can share a single workstation's CPU. By adding a PC/AT coprocessor card and a coprocessor program, you can run programs that run on a PC and you can share the RT PC's disk files and displays with a PC. The workstation offers a choice of three graphics monitors, an 8-pen color plotter, and a tape drive. Typical stand-alone desktop unit, \$16,485; typical high-end floor-standing model, \$19,730.

**IBM Corp.**, Information Systems Group, 900 King St, Rye Brook, NY 10573. Phone local office.

Circle No 355

### SCHEMATIC CAPTURE

The Computer-Integrated Electrical Design Series (Cieds) runs on the manufacturer's 30XX, 43XX, PC/AT, and RT PC computers. This program, which is a port of Silvar-Lisco's schematic-capture package (Schematic Design System), can develop hierarchical logic designs on a 5080 that you have connected to a

host computer. The package lets you create, edit, and list schematics and symbols. It offers multiwindow interactive graphics, net-list manipulation, and hierarchical-design expansion. Interfaces are available to other automated design tools, including this company's Circuit Board Design System. Single license for mainframes, \$75,000; for

PC/AT, \$6000; for RT PC, \$8000.


**IBM Corp.**, Information Systems Group, 900 King St, Rye Brook, NY 10573. Phone local office.

Circle No 356
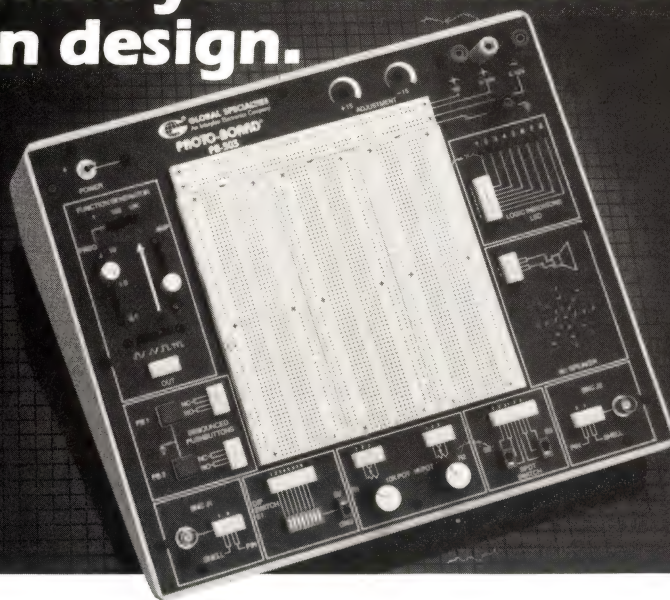
### SMD ANALYSIS

An SMD analysis program projects the design feasibility of an SMD

**Our new proto-station  
does the dog work  
while you concentrate  
on design.**



The new Global PB-503 PROTO-BOARD station eliminates the tedious building of redundant circuits and connections. The designer is free to devote time and energy to the circuit being designed and tested.

The PB-503 contains a large three-socket breadboarding area, plus a function generator, a variable output power supply and eight-LED logic indicators. Also built in are debounced push-buttons, eight-position DIP switch, SPDT switch, 1K and 10K pots, a speaker and two BNC connections. Everything is connected to the breadboarding area through a

PC board, and access is quick and convenient.

Priced at \$275, the PB-503 will pay for itself many times over.

For details and the name of your Global distributor, call our Customer Service Department, toll-free 1-800-572-1028 or write Interplex Electronics, Inc., Global Specialties Division, 70 Fulton Terrace, New Haven, CT 06512.

 **Global  
Specialties**  
An Interplex Electronics Company

CIRCLE NO 27



project and establishes fabrication requirements, manufacturing techniques, and design parameters. It runs on any IBM PC or compatible MS-DOS system that includes 512k bytes of RAM. \$695.

**Animat/USA**, 200 Brown Rd, Suite 300, Fremont, CA 94539. Phone (415) 659-0105.

Circle No 357


### PC-BOARD ROUTER

According to the vendor, the Look Out router completed the routing of a 6-layer 11×7.6-in. board that had 429 components, 1699 connections, and a 0.33 equivalent-IC density in just over 10 minutes. The router, which is part of the Scicards package, features a gridless algorithm and can route one, two, three, or more traces between pin pads. To set the channel and spacing, you specify only the component pad size. The program can bend traces in

channels; it doesn't violate layer-direction preference rules. Before it places any traces, the router explores all routes, analyzes all channels, and determines the best via locations. \$25,000 for Scicards package.

**Scientific Calculations Inc**, 7635 Main St, Fishers, NY 14453. Phone (716) 385-6790. TWX 510-254-8546.

Circle No 358

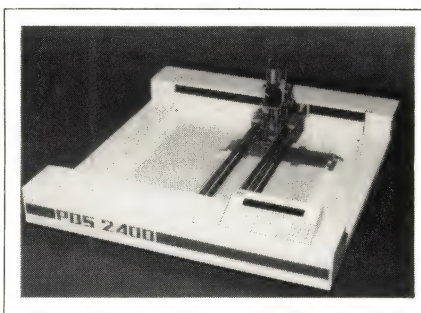

### WIRE-WRAP SYSTEM

The PDS 2400 automatic wire-wrapping system accepts Future-

Net schematics. With a wrapping speed of 300 wraps/hour, the system features daisy-chaining and automatic error detection and correction. The system can handle several boards concurrently. An RS-232C serial port lets you interface computers to the system. To use Convert, the FutureNet translation package, you identify the components that you want to use and specify the positions of those components. This system accommodates 30- and 26-gauge wire. PDS 2400, \$39,950; Convert, \$950.

**Mind to Matter Robotics Corp**, 2810 de Miniac, Montreal, Quebec, Canada H4S 1K9.

Circle No 359

### 68020 WORKSTATIONS

The Sun-3/50M desktop workstation and the -3/52M stand-alone system both operate under Unix. The -3/50M is a diskless node that inter-





## COMPUTER-AIDED ENGINEERING



disk drive and a 60M-byte, 1/4-in. streaming-tape drive. -3/50M, \$7900; -3/52M, \$13,900. Delivery, 60 days ARO.

**Sun Microsystems Inc.**, 2250 Garcia Ave, Mountain View, CA 94043. Phone (415) 960-7533.

Circle No 360


### AUTOMATIC ROUTER

Based on the 68020  $\mu$ P, the CDX-75000 Route Engine-Plus has a memory subsystem, which contains a 32-bit data path to dual-ported RAM and a memory-address capacity to 16M bytes. The expanded memory capacity of this version accommodates the routing of boards that contain 700 or more equivalent ICs. This router uses a multilayer routing algorithm, which has been implemented in microcode and thus accelerates the performance of the routing technique. Because the router evaluates all layers simulta-

neously, it can rapidly find an optimum trace path for making the connection. Fewer vias are necessary, and traces are shorter than those generated by layer-pair routers. \$77,000.

**Cadnetix Corp.**, 5757 Central Ave, Boulder, CO 80301. Phone (303) 444-8075.

Circle No 361

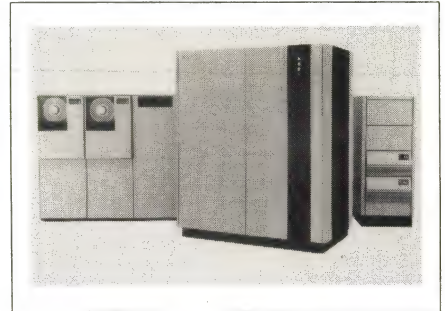

### PARALLEL PROCESSOR

This expanded version of the System 6400 is a 12-processor computer that performs 72 Whetstone MIPS.

# Y PAPER?

For RFI suppression, RIFA Metallized Paper Capacitors are accepted all over the world as the industry standard.

Here are a few of the reasons.

Metallized Paper is self-healing, temperature-stable and gives excellent pulse-handling capability.

What other technique could withstand pulses up to 2000V/ $\mu$ sec, ten times a day?

This means maximum protection for your circuit, maximum safety for your equipment and maximum assurance against subsequent liabilities.

Now, the PME series comes in even better packaging, with smaller overall size, better mechanical stability, better flame resistance and complete suitability for automatic insertion.

If you design equipment needing RFI suppression, send for full data on our Metallized Paper Capacitors.

RIFA Inc., Greenwich Office Park 3, P.O. Box 3110, Greenwich, CT 06836-3110.  
☎ 203 625 7300. Fax 203 625 7087. Tx (23) 221976 ERIAN UR.

Full marketing, applications and technical service in N. America from  
World Products Inc. P.O. Box 517, Sonoma CA95476. ☎ 707 996 5201. Tx 171715. Fax 707 996 3380.  
Deskin Sales, 77D Steelcase Rd. W, Markham, Ontario. L3R 2M4. ☎ 416 475 1412. Tx 6966559.

**RIFA INC.**  
quality for the future

See us at Electro Show Booths 1612-1617





Designed for such applications as VLSI chip design, it features a parallel-processing architecture, which offers modular expansion. Because the system uses ECL and LSI gate arrays, it can package a single 6-MIPS CPU on three circuit boards. The system provides as much as 4G bytes of virtual addressing space per process. You can expand the central computer memory to 192M bytes. The system bus, Gigabus, is a synchronous, 64-bit-wide channel that specs a system bandwidth of 320M bytes/sec. The system incorporates three operating systems: EMBOS, this company's proprietary operating system; Unix BSD 4.3; and Unix system V. The computer can compile Fortran, Pascal, Cobol, and Mainsail programs. \$3,000,000.

**Elxsi**, 2334 Lundy Pl, San Jose, CA 95131. Phone (408) 942-0900. TLX 172320.

Circle No 522

## PC-BOARD ANALYSIS

The Printed Circuit Board Analysis Program runs on any IBM-compatible MS-DOS system. The program estimates the board requirements, costs, and manufacturing parameters of pc boards. It includes file utilities for printing, storage, and retrieval from hard disk. The program will report IC equivalency, density, and feasibility of the design, and specifically define the level of difficulty using 2-, 4-, 6-, 8-, or 10-layer boards. Job-cost estimates and models can be reviewed. \$99.

**Animat/USA**, 200 Brown Rd, Suite 300, Fremont, CA 94539. Phone (415) 659-0105.

Circle No 523


## TAPE EMULATOR

Disk-A-Tape, a punched-tape emulator, is available in a ruggedized 5¼-in. disk version and a 3½-in.

protected rigid-disk configuration. Both versions feature a positive air-flow filtration system that prevents contamination from foreign matter. The tape emulator replaces both paper-tape readers and punchers. You can attach the tape emulator to numerically controlled machines without adding any hardware. The 5¼-in. disks can store as much data as 3000 ft of punched tape; the 3½-in. version stores as much as 6000 ft. The emulator reads and punches data at 1500 cps when operating as a parallel reader or puncher. Both versions fit on 19-in. instrument racks and include parallel and RS-232C ports. 5¼-in. version, \$2995; 3½-in. version, \$3095.

**Wire Graphics Inc**, 95 Sherwood Ave, Farmingdale, NY 11735. Phone (516) 293-1525.

Circle No 524

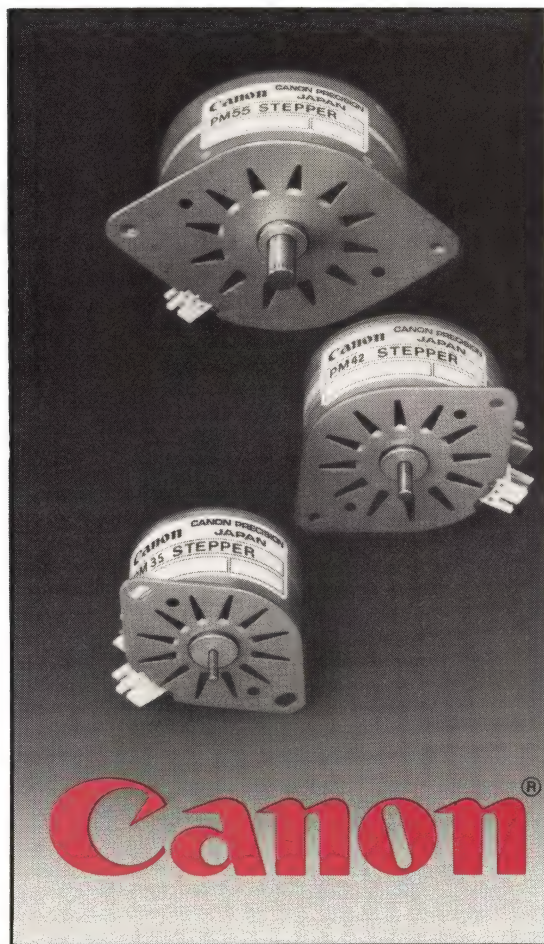

## Need a Stepper?

We have three new frame sizes to offer!

- Low in cost, high in performance
- Modifications of standard units available in OEM quantities
- Step angle 7.5 degrees
- 35mm, 42mm and 55mm diameters
- Non grain-oriented, radial grain-oriented and multi-pole grain-oriented magnets
- 4 phase, operating in a 2-2 driving mode
- Rated voltages of 12 or 24 volts
- Maximum pull-in pulse rates 250 to 600 pps
- Maximum pull-out pulse rates 260 to 720 pps
- Holding torques 110 to 1500 g-cm
- Detent torques 30 to 150 g-cm
- Rotor Inertia 4 to 40 g-cm<sup>2</sup>
- Weights 100 to 280 grams

For complete technical information, call or write

CANON U.S.A. INC. Components Division

New York Office/Headquarters  
One Canon Plaza  
Lake Success, NY 11042  
(516) 488-6700 • Telex 96-1333

Santa Clara Office  
4000 Burton Drive  
Santa Clara, CA 95054  
(408) 986-8780 • Telex 17-1961


See us at **ELECTRO 86** at Booth #2941-2943


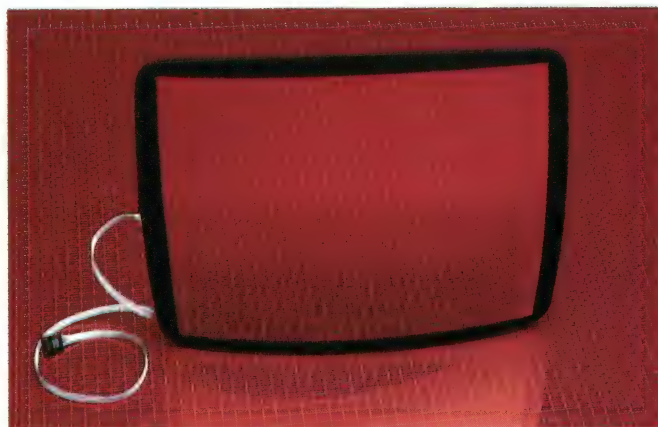
# Give Your Computer System the Right Touch



With the  
Elographics  
E274  
Touch  
Screen



Your customers are looking for improved human-computer interfaces. With the E274 Touch Screen, your computer system will offer just that. And people will want to use it again and again.

Why? Because the E274 is a natural operator-computer interface. It responds to your finger's slight pressure exactly the way you expect. Without delayed, premature, or accidental triggering. With any pointing device you choose — finger, gloved finger, ball-point pen, or stylus.

And you won't need to redesign your system. Elographics has touch screens to fit most CRT's from 5 to 25" diagonal and makes custom shapes and sizes. Both RS232 and PC bus controllers are available.

To find out more about the E274 and its million-touch durability, harsh-environment reliability, and .003" resolution, get in touch with us.

We'll give your computer system the right touch.


## ELOGRAPHICS


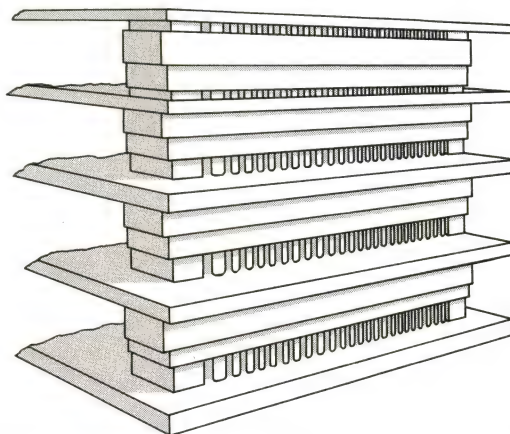
# STACK THE CARDS IN YOUR FAVOR

Average contact insertion forces of one ounce ease the task of parallel board stacking.

The KS Series connectors incorporate sockets on one side and socket tails serving as mating pins on the other. Printed circuit boards can be placed one on top of another with all electrical connections between boards routed through the stacking connectors.



Hypertronics' connectors utilize the Hypertac® contact design, a hyperboloid shaped socket. The Hypertac® is formed by multiple wires that stretch and wrap around the mating pin to create multiple contact paths. This design results in several major advantages:


- contact resistance as low as .0005 ohms
- extremely low insertion/extraction force (as low as 1/2 ounce)
- absolute continuity under extremes of shock and vibration (tested below 10 n.s.)
- extended life exceeding 100,000 cycles with consistent repeatability

For more information on these versatile connectors, call Toll Free 1-800-225-9228, or write for a copy of our complete 1986 catalog.

 **HYPERTRONICS  
CORPORATION**


16 Brent Dr., Hudson, MA 01749-2904  
Telex 95-1152 Canada & MA 617-568-0451  
Toll Free 800-225-9228

"NEW HORIZONS IN CONNECTORS"

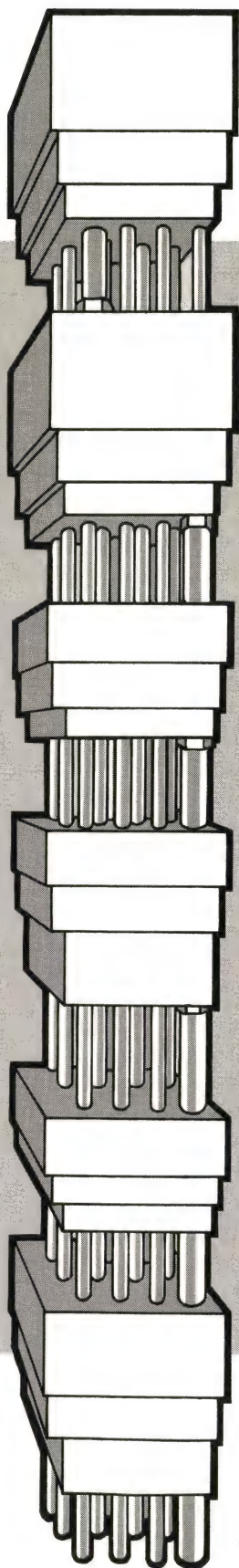



## NEW PRODUCTS: COMPUTERS & PERIPHERALS

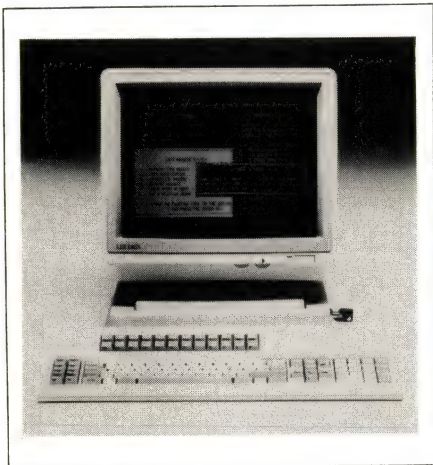

### TERMINAL

The Model 1222 display terminal features windowing capabilities and a variety of terminal emulations. One windowing function lets you store data in two small windows; another function indicates the arrival of electronic-mail messages. You can also store more than 1000 characters in any of the terminal's four windows. The unit has a key lock for

security; for even greater protection, you can use an optional software-based password to prevent unauthorized access to programs. You can specify either coaxial-cable or twisted-pair wire connections. The Model 1222 provides asynchronous communications through optional terminal emulations, including DEC VT 100, HP 2624B, Hazeltine 1510, and Televideo 950. Keyboard is included. \$2866.

**Lee Data Corp.**, 7075 Flying Cloud Dr, Minneapolis, MN 55344. Phone (612) 828-0300.

Circle No 362


### INK-JET PRINTER

The JX-720 color ink-jet printer uses four ink cartridges to produce as many as 256 color combinations. An automatic printhead cleaning station minimizes nozzle clogging. The design of the ink reservoirs prevents you from splashing ink

when you refill them. The printer uses 8½×11-in. cut sheets, overhead-projector transparencies, or roll paper. The JX-720 prints text at 35 cps and fills a 1024×1024-dot color-image page in 2.2 minutes with a 120-dots/in. resolution. You can connect the printer to your computer via a Centronics parallel interface. \$1495.

**Sharp Electronics Corp.**, Systems Div, 10 Sharp Plaza, Paramus, NJ 07652. Phone (201) 599-3856.


Circle No 363

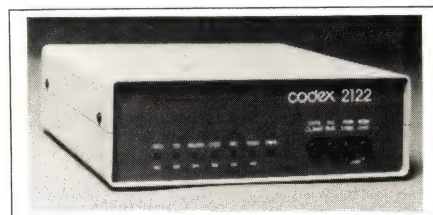

### NETWORK CONTROLLER

The Model 2122 features data-transmission speeds that reach 56k bps
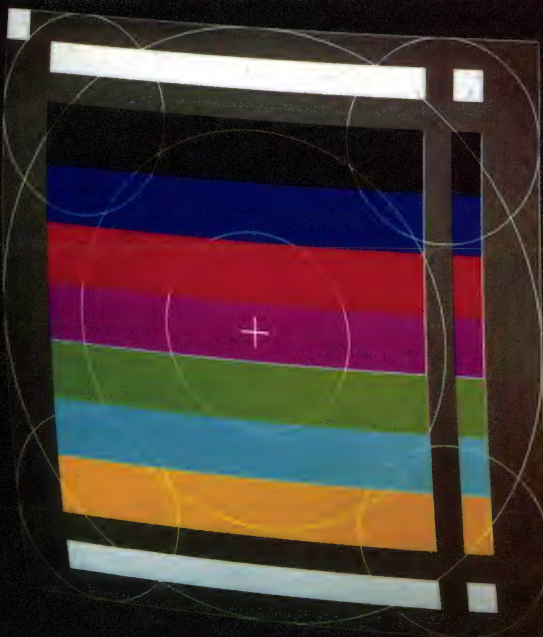
## You Don't Need a Thousand Words When You Have a Picture Like This!



**The** image quality demonstrated here is required by your customers... and will be appreciated! They expect THE BEST from original equipment manufacturers. You can provide it! While other video monitor vendors claim, "about 100 + MHz" video bandwidth,\* **Video Monitors, Inc.** provides it! While other vendors claim, "full gray-scale color capability," **VMI** delivers it!

And if your customers or you need semi-custom or custom designs, **VMI** can provide this service. These are just a few of the reasons why **Video Monitors, Inc.** should be your supplier of very high resolution monitors.

**Video Monitors Inc**

3933 North White Avenue  
Eau Claire, Wisconsin 54703  
(715) 834-7785


\*5.5 NS max rise & fall time measured at CRT cathode



Large Image Area



Ergonomic Design

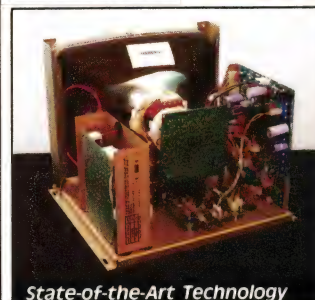

State-of-the-Art Technology





# How to build Rome in a day.

## Use the best project management software for empires of all sizes.

Whether you're launching a new product, constructing an office complex or planning to make history, Harvard™ Total Project Manager (HTPM) is the complete PC software program for anyone who wants to manage more effectively.

Successful project management starts with HTPM's intuitive roadmap (PERT Chart) which graphically demonstrates relationships between tasks and offers a clear view of the critical path. HTPM's Gantt Charts allow you to modify the project for the most


efficient scheduling and resource allocation. You can also budget each task and compare actual costs to planned costs. If necessary, cost data can be transferred easily to Lotus™ spreadsheets. The flexible Project Calendar gives you the ability to define your workdays and tailor a project to fit your schedule.

Because most managers must juggle more than one project at a time, HTPM supplies a special feature that alerts you to over-committed resources, both within a project and across multiple projects, and helps you reallocate resources accordingly.

When a project requires the coordination of many people, good communication is vital. With HTPM you can produce comprehensive,

presentation quality reports to keep the entire organization informed of the latest developments.

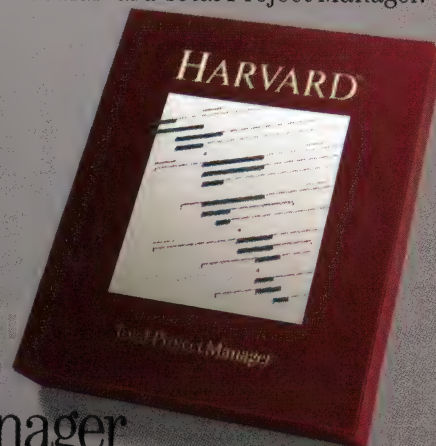Any project can take on epic proportions when *you* are responsible for bringing it in on time and on budget. That's why every project manager needs HTPM. For planning, scheduling, controlling, and reporting, no PC software is as effective as Harvard Total Project Manager.



## Graduate to Harvard Total Project Manager

Runs on IBM PC, Compaq, Leading Edge, AT&T and other compatible MS DOS computers. A product of Software Publishing Corporation.

**CIRCLE NO 158**



for distances ranging as far as 7.5 mi. The 2122 supports 4-wire networks in both full- and half-duplex communications, as well as 2-wire, half-duplex networks. You can select synchronous operating speeds of 40k, 48k, 56k, and 64k bps. To ensure accurate data transmission, an automatic equalizer compensates for circuit distortion. The unit also features remote and local diagnostics and can generate internal test patterns. It is available in a stand-alone and a card version. \$875.

**Codex Corp.**, 20 Cabot Blvd, Mansfield, MA 02048. Phone (617) 364-2000.

Circle No 364



## IMAGE PROCESSOR

The Imag 100 real-time image-processing workstation includes an IBM PC, a video camera, an RGB monitor, a mouse, a digital frame grabber, and software. With these components, you can perform more than 40 interactive image-processing and -analysis functions. By using the mouse and menu commands, you



## HANDHELD COMPUTER

Weighing less than 2 lbs, the HP-94 handheld industrial computer features an 80C88  $\mu$ P that supports programming in Basic and assembly language. Its 4-line $\times$ 20-character LCD lets you monitor the computer's operation. The ruggedized unit runs on batteries. Its built-in RS-232C interface lets you communicate with a host computer. The unit also supports bar-code wands for data entry. The standard model comes with 64k bytes of RAM, expandable to 256k bytes; you can also add ROM and EPROM to a maximum of 128k bytes. An optional electroluminescent display lets you use the HP-94 in the dark. \$1295.


**Hewlett-Packard Co.**, 1020 NE Circle Blvd, Corvallis, OR 97330. Phone local office.

Circle No 365


## GENTRON'S NEW
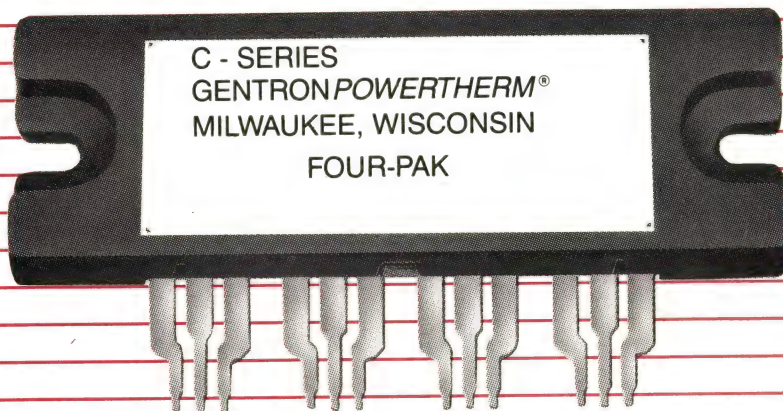
# C SERIES MOSFET FOUR-PAK

- SPECIFICALLY DESIGNED WITH LOW CIRCUIT INDUCTANCE FOR HIGH SPEED SWITCHING TO 5 N.S.
- CONSTRUCTION YIELDS 2500 VOLTS(RMS) OF ELECTRICAL ISOLATION TO THE HEATSINK
- LOW THERMAL RESISTANCE JUNCTION TO CASE
- PACKAGE HAS PRINTED CIRCUIT PINS (OPTIONAL 90° BEND)



V <sub>oss</sub> Drain-Source Voltage (volts)	I <sub>D</sub> Drain Current (amps)	R <sub>DS</sub> Drain-Source Max. Resist. (ohms)	GENTRON PART NO.
100	27	0.09	CM07
200	18	0.18	CM05
400	10	0.55	CM03
500	8	0.85	CM01

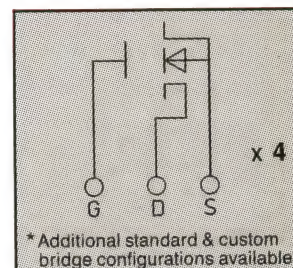

To find out more about Gentron's transistor series, contact:



**Gentron Corporation**

6667 North Sidney Place, Milwaukee, WI 53209  
(414) 351-1660 Telex: 26881




can capture a video signal at the rate of 30 frames per sec and store the image in the computer's 512×512×8-bit frame memory while simultaneously displaying the stored image on the system monitor. An optional pseudocolor module allows you to transform the monochrome input into a colored display for increased image analysis. Or you can order a full-color system with three frame-grabbing modules and an RGB camera to produce 24 bits per pixel of RGB data. \$10,499.

**SSE Products Inc.**, 791 Meacham Ave, Elmont, NY 11003. Phone (516) 872-9001. TWX 510-223-0417.

Circle No 366
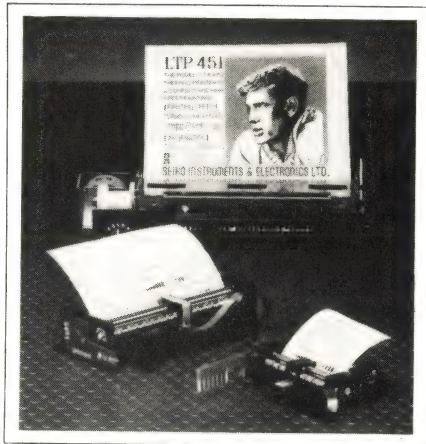
## THERMAL PRINTER

The LTP451 produces 7×5-dot matrix characters in 42 columns at the rate of 210 cps. Using a thermal printhead, it prints both alphanumeric and graphics characters. The




device measures 6.1×2.2×1.1 in., weighs 12 oz, and requires a 5V dc and a 24V dc power source. The unit operates from 0 to 50°C. Print resolution is 76 dots/in. It uses 4.4-in. heat-sensitive paper, covering a print width of 3.5-in. per line. \$83 (1000).

**Seiko Instruments USA Inc.**, 2990 W Lomita Blvd, Torrance, CA 90505. Phone (213) 530-8777.

Circle No 367

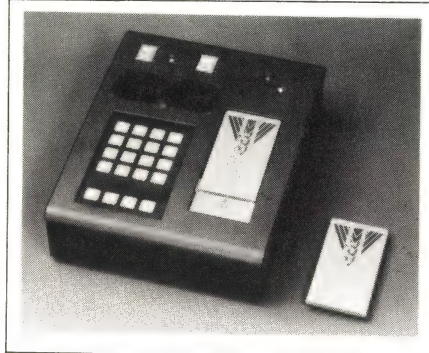
## MEMORY CARDS

You can use the LSI Card with an LSI Card Reader for access-control applications, computer timesharing, and programmable control. Incorporating four nonvolatile memory coils in a device that is about the size of a credit card, each card has read/write memory embedded in a



plastic resin and hermetically sealed to exclude dirt, moisture, and oil. Each card comes with either 64k bytes or 256k bytes of CMOS static RAM and a lithium battery. The

## Highly Visible

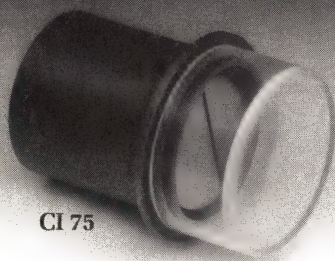

CI 75

**New 3/4" Reflective Display Indicator visible at great distance in bright or dim light.**

- Large 3/4" display uses reflective flag.
- No bulbs to replace, magnetic operation.
- Low power usage, pulse to "Set" or "Reset", no power needed when latched in either position.
- "Remembers" last "Set" or "Reset" signal, even with power outage or dip.

For large display panels, fault warning systems, outdoor applications or other brightly lit areas, and where low power drain is required.

**Call or write today for complete information.**

Minelco Inc. Talley Industries  
135 South Main Street,  
Thomaston, CT 06787-0459  
Phone (203) 283-8261  
TWX 710-475-1091

**MINELCO INC. Talley Industries**

CIRCLE NO 32

## DID YOU KNOW?

Ten times a year EDN publishes *EDN Career News*, the fastest-growing newspaper focused solely on the career and professional development concerns of engineers in electronics.

**EDN**



**Just when you thought all  
connectors were alike...**

# There's Welcon!®


**J**ust when all connectors begin to look the same, cost the same, and perform the same, Welcon adds a difference.

**W**elcon combines the service and responsiveness of a small company with the product performance and technology of a major manufacturer.

**T**he result is obvious when you choose Welcon connectors. You get more than a part. You get a partnership. Fast delivery, comprehensive service—the attention you get only from a company that cares.

**A** company like Welcon.

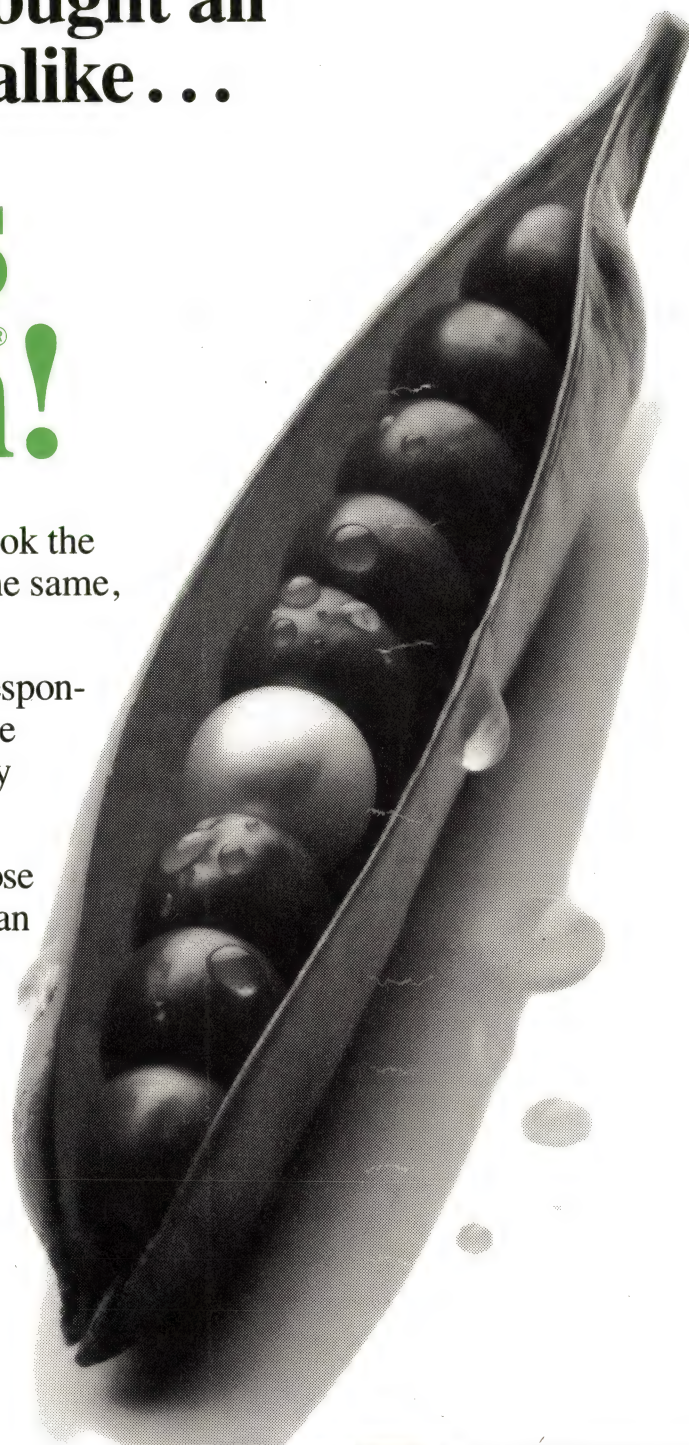- 
- Card Edge Connectors
  - D-Sub Connectors
  - Pin Headers • Shunts
  - DIP Production Sockets
  - Leadless Chip Carrier Sockets
  - ZIF Sockets
  - Burn-In/Test Sockets
  - Contactors • Carriers



**WELLS ELECTRONICS, INC.**  
1701 SOUTH MAIN STREET  
SOUTH BEND, IN 46613. U.S.A.  
219-287-5941 TELEX 25-8325  
FAX 219-287-0356




# YOUR DISCRETE AND ELECTRO-MECHANICAL MOTOR DRIVE DESIGN DILEMMAS ARE OVER!

*If you use discrete semiconductor components in motor drive circuits, Solitron's new power hybrids allow reduction of space and weight and resolve complex wiring problems.*

*If you're not using Solid State components, these "Mini" packages give you the opportunity of moving into proven state-of-the art power hybrid motor drive circuitry.*

Just imagine. Power MOSFET or Bipolar hybrid circuits in copper "Mini" packages with the necessary interconnects including flyback diodes. Today it's a reality. With Solitron's new half bridges, single phase and three phase full bridges, all the components are electrically isolated from the package so that it may be directly attached to the heat sink. Electrical insulators are eliminated, improving mechanical stability of the system with reduced thermal resistance.

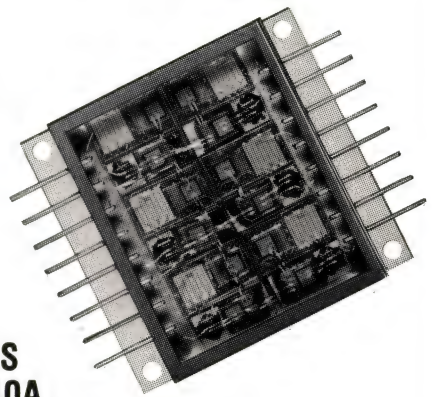

**POWER RATINGS FOR HALF BRIDGES, SINGLE PHASE FULL BRIDGES AND THREE PHASE FULL BRIDGES ARE 500V/13A; 400V/15A; 200V/30A; AND 100V/40A. SPECIAL CIRCUIT CONFIGURATIONS ARE AVAILABLE ON REQUEST.**

Solitron's energy saving motor speed controllers have numerous aerospace, military and industrial applications where brush and brushless motors are employed and where high reliability and high efficiency are design criteria. They can replace conventional hydraulic control systems presently used on aircraft for steering, flaps and landing gear with increased efficiency and reliability. Other applications include drives in Automation, Robotics and portable equipment where limited source of power, weight, size and high reliability are very critical factors.

All Solitron circuits, whether custom designed or standard types, can be tested to MIL-STD-883 requirements. For specific information, call our Sales Department toll-free 1-800-327-8462.

*"The Problem Solvers"*

**Solitron**  
DEVICES, INC.

1177 Blue Heron Blvd. Riviera Beach, Florida 33404 (305) 848-4311/TWX: (510) 952-7610/TLX: 51-3435




## COMPUTERS & PERIPHERALS

Card Reader has RS-232C, current-loop, and parallel outputs for computer interfacing. Card Reader, \$1000; Card, \$15 (OEM qty).

**Orientation Inc.**, 101 Coolidge St, Hudson, MA 01749. Phone (617) 568-0509.

Circle No 368

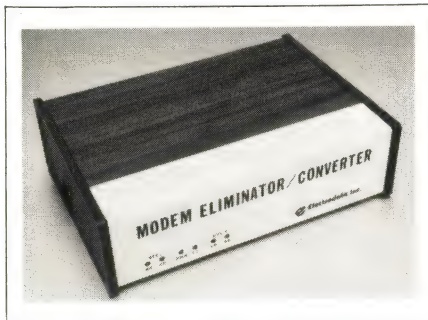

crystal-controlled data rates. Or you can drive the unit externally from a terminal or computer. Diagnostic features include front-panel indicators and a digital loop-back switch. \$475.

**Electrodata Inc.**, 23020 Miles Rd, Bedford Heights, OH 44128. Phone (216) 663-3333. TWX 810-427-2280.

Circle No 370



### HARD-DISK DRIVES

The 9133L is a 40M-byte hard-disk drive in a stand-alone cabinet. The 9134L is similar to the 9133L but also includes a 3½-in. floppy-disk drive in its cabinet. Both drives feature a 40-msec access time and allow you to partition the hard disk into as many as eight volumes. (This latter feature is particularly useful for storing multiple operating systems on one drive.) Among the computers that accept these drives are the manufacturer's 9000 workstations, its Models 250 and 260 computers, the Touchscreen II, and the IBM PC family. 9133L, \$4450; 9134L, \$4050.


**Hewlett-Packard Co.**, 3000 Hano-ver St, Palo Alto, CA 94304. Phone local office.

Circle No 369

### INTERFACE CONVERTER

Supporting the RS-232C and CCITT V.35 interfaces, the ME 3 allows you to directly connect two terminals or computers without using modems. The device provides interface conversion for data communication at speeds ranging from 14.4k to 896k bps. You can set the unit's internal clock to any of 19
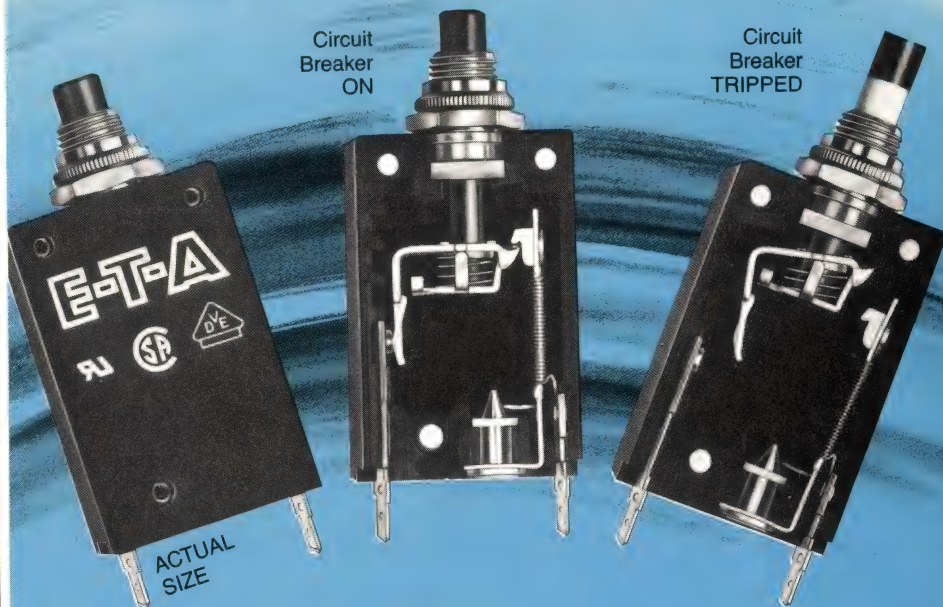
## See why **E-T-A<sup>®</sup> CIRCUIT BREAKERS** provide better protection



CIRCLE NO 34


It's really the same concept as a magnetic circuit breaker! In the ON position, a spring loaded latching mechanism keeps the contacts closed until an overload is detected.

The tripped position shows the sensing element deflected and the contacts open. The E-T-A design can handle high inrush currents without nuisance trips. It is not shock or vibration sensitive.

100% of E-T-A's Circuit Breakers are calibrated and tested. They not only meet requirements for, but carry **UL** **SP** **VDE** and other worldwide approvals. E-T-A Circuit Breakers are ideally suited for a wide variety of applications in equipment such as Data Processing, Medical Instruments, Communication, Power Supplies, Marine and Automotive.

*For Better Protection, Economical Prices, and Delivery you can depend on, please call (312) 647-8303.*

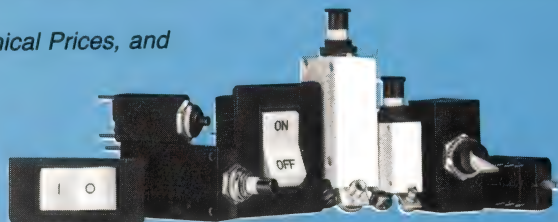**E-T-A<sup>®</sup>**  
**CIRCUIT**  
**BREAKERS**




**setting the pace for circuit protection**

7400 North Croname Road, Chicago IL 60648  
312/647-8303 • TELEX: 253780 • FAX: 312/647-7494



## COMPUTERS & PERIPHERALS

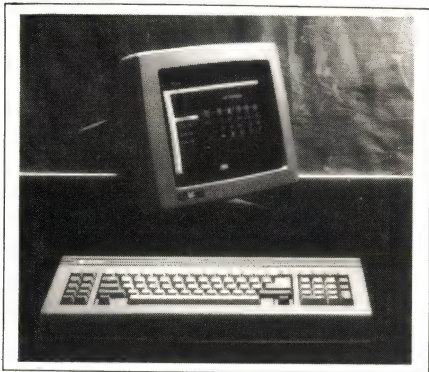


### MULTIUSER TERMINAL

You can use PCTerm, a multiuser terminal, with your IBM PC or compatible computer. Its 14-in. green or amber CRT displays a 256-character set in the IBM PC-style font. It supports 80- and 132-column displays, and its keyboard resembles that of an IBM PC/AT. The terminal has two bidirectional RS-232C ports: You can simultaneously connect one port to an IBM PC and the other to another host computer. In addition to its native IBM PC mode,

the terminal emulates a WY-50 and a TeleVideo 925. \$649.

**Link Technologies Inc.**, 2260 Paragon Dr, San Jose, CA 95131. Phone (800) 223-8626; in CA, (408) 943-0143. TWX 910-338-2143.

Circle No 371

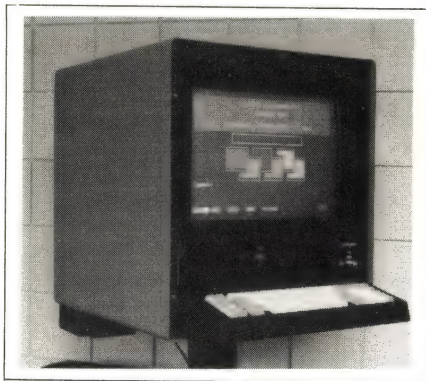

### INDUSTRIAL COMPUTER

The Expert computer, designed for use in a factory environment, is enclosed in a ruggedized NEMA 12 enclosure. It features a thermostati-

cally controlled dynamic heat exchanger for use in high-temperature locations. The unit has a membrane keyboard, an 80286 CPU, 640k bytes of RAM, eight I-Bus expansion slots, and a 19-in. color CRT. You can order an 8088  $\mu$ P as an option. \$1995.

**Comark Corp.**, Box 474, Medfield, MA 02052. Phone (617) 359-8161. TLX 703156.

Circle No 372


### COLOR PLOTTER

The Spectrum can serve either as an electrostatic color plotter or as a line printer. It produces both A-size (8.5 $\times$ 11-in.) and B-size (11 $\times$ 17-in.) drawings. When used with an optional video interface, it produces hard copy directly from a CRT image. The machine uses either paper or polyester film; print speed is 2 ips with a 200-dot/in. resolution. Using this plotter, you can produce
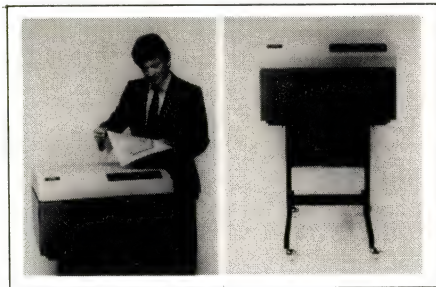
# $\mu$ PAK. <sup>©</sup> A Sm

Our 607C31 series, 80C31 systems compatible, turns 80C31  $\mu$ C s into full CMOS micro-a logic control unit. All on a 40 pin (600 mil pin spacing) ceramic substrate. Available






### UNIX COMPUTER

Based on a 68020  $\mu$ P, the P/75 computer supports as many as 80 terminals with its Unix-based operating system. You can configure the system with as much as 16M bytes of RAM and 6.5G bytes of disk storage. The system also uses dedicated

card cage, 1M byte of error-correcting RAM, a 60M-byte cartridge tape drive, a mass-storage processor, and a 145M-byte, 8-in. Winchester drive. The system also comes with a built-in 110-, 300-, and 1200-baud autodial, autoanswer modem. From \$36,000.

**Plexus Computers Inc**, 3833 N First St, San Jose, CA 95134. Phone (408) 943-9433. TWX 910-338-2223.

Circle No 374

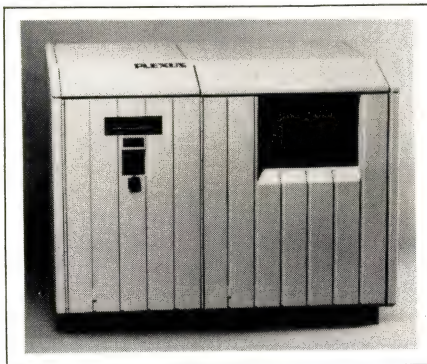

communication processors that relieve the CPU of I/O functions. Each communication-processor board includes a 35-channel DMA processor and a 2M-byte buffer memory. Standard features include a 15-slot

an A-size monochrome drawing in 5 sec or color drawing in 60 sec. A B-size monochrome plot takes 10 sec and a color version <90 sec. This unit also emulates the manufacturer's V-80 printer/plotter in monochrome mode, printing text with 132 cpl at 1000 lpm. A built-in raster-data translator converts 100-dots/in. data to 200-dots/in. density; the translator thus lets the host computer generate less data and thereby plot faster. \$11,950.

**Versatec**, 2710 Walsh Ave, Santa Clara, CA 95051. Phone (800) 538-6477; in CA, (800) 341-6060.

Circle No 373



### BAR-CODE READER

The EZ Reader provides automatic recognition and decoding. This bar-

# all Wonder.

computers. With 8K/32K x8 SRAM and on-board programmable 8K/32K x8 EPROM. Plus to MIL STD 883 specifications. Maybe you'll wonder how. But, you won't wonder who.



# EDI

## The future...today.



# ROCKWELL SEMICONDUCTOR TECHNOLOGY SOLVES T-1/CEPT IMPLEMENTATION IN A CMOS CHIP.

**Replace up to 100 MSI devices with the world's first single-chip PCM transceiver.**

Designed for worldwide primary rate applications, the R8070 from Rockwell International is a telephony breakthrough. This single-chip solution accommodates all primary telephone carrier requirements in both North America and Europe. The R8070 T-1/CEPT operates with AT&T extended framing, Clear Channel, and European CEPT formats.

**Save on power, design engineering and component costs.**

As a single-chip, CMOS transceiver, the R8070 minimizes board space requirements with its VLSI implementation. It significantly reduces power consumption, saves on component costs and reduces engineering design investment as well. To find out how the R8070 can help you build your next generation T-1/CEPT communications system, talk to your Rockwell distributor or sales representative or send for complete technical literature today.

**Semiconductor Products Division**

Rockwell International, P.O. Box C,  
M.S. 501-300, Newport Beach, CA 92658-8902  
(800) 854-8099. In California (800) 422-4230.



**Rockwell  
International**

...where science gets down to business




## COMPUTERS & PERIPHERALS

code reader interprets several formats, including Code 39, UPC A/E, Codabar, Codabar/ABC, and Interleaved 2 of 5. The wand uses a decoding algorithm that incorporates error-checking routines to ensure accurate decoding for both dot-matrix and preprinted labels. The scanner comes with either an RS-232C interface or an IBM PC/XT keyboard interface. The keyboard-interface model requires no software modifications and permits full use of the keyboard at all times. You can also order optional IBM PC/AT and Tektronix 4100 keyboard interfaces. From \$635.

**Percon Connections Inc.**, 2190 W 11th St, Eugene, OR 97402. Phone (503) 344-1189.

Circle No 375

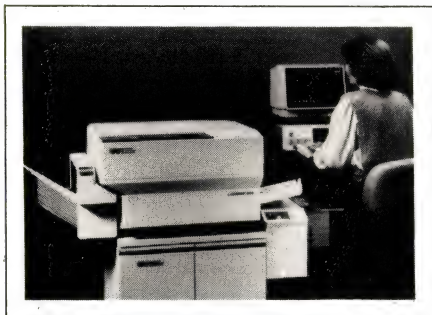

### LASER PRINTER

The Laserprint 2670 produces letter-quality documents at speeds reaching 1500 lpm. You can use this printer to emulate a plotter, or a line or daisy-wheel printer. Its 300-dots/in. resolution lets you create bar codes and bit-mapped graphics. You can specify a plug that's compatible with IBM, DEC, or Wang computers. You can load this printer with 2000 pages for continuous production workloads. Its dual input cut-sheet feeder accepts paper as large as 11×17 in. The manufacturer estimates a cost per page of \$0.018. \$11,400.

**Advanced Technologies International Inc.**, 2041 Mission College Blvd, Santa Clara, CA 95054. Phone (408) 748-1688.

Circle No 376

## PROGRAM 68000-68020

on your  
**VAX**  
and IBM PC

**NOW SHIPPING**

### Professional Development Systems for PC's, VAX/VMS and IBM VM/CMS

- PC compatible 68020/68000 evaluation, test board provided
- Professional quality high performance tools
- Optimizing C and Pascal compilers
- Assembler and linker/locator
- In-Circuit Emulators supported
- VRTX, PSOS, MTOS Supported
- Rugged, reliable and field-proven for over 3 years
- Unequaled customer support services
- The choice of leading software professionals for the development of consumer and industrial products

Cost Effective Solutions for Motorola microprocessor development . . .

Call Today: (303) 449-6809



4885 Riverbend Road, Boulder, Colorado 80301 (303) 449-6809 Telex: ITT 4992706  
VAX is a trademark of Digital Equipment Corp.

CIRCLE NO 36

## Be An Author!

When you write for EDN, you earn professional recognition. And you earn \$75 per published magazine page.

EDN publishes how-to design application information that is read by more than 137,000 electronic engineers and engineering managers worldwide. That's an audience that could belong to you.


If you have an appropriate article idea, please phone Jon Titus, Senior Editor, at (617) 964-3030 or send a proposal and outline to him at 275 Washington Street, Newton, MA 02158-1630. For a FREE EDN Writer's Guide—with tips on how to write for EDN and other technical publications—please circle number 301.



**First in Readership among Design Engineers  
and Engineering Managers in Electronics**



## NEW PRODUCTS: COMPONENTS & PACKAGING

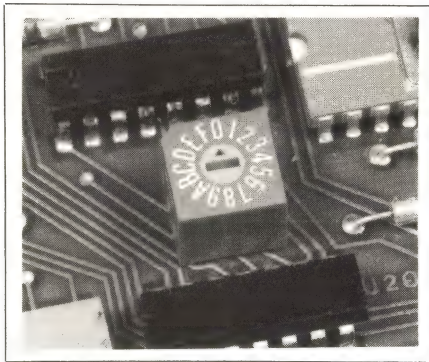

### DIP SWITCHES

The Series 74 16-position hexadecimal and 10-position BCD rotary DIP switches provide direct input to logic circuitry without a coding interface. The switches provide single-setting accuracy and measure 0.38×0.38×0.295 in. Terminals are located on DIP centers with a common lead on each side. Common leads are internally connected. A standard epoxy-sealed base protects the bottoms of the switches during board assembly and cleaning processes.

For a complete seal, a factory-applied top-tape seal is available as an option. \$3.28 (100).

**Grayhill Inc.**, Box 10373, La-Grange, IL 60525. Phone (312) 354-1040. TWX 970-683-1850.

Circle No 377



### CRYSTAL OSCILLATORS

The Models KTXO and KTVXO temperature-compensated crystal

oscillators are compatible with 14-pin DIP ICs and TTL and CMOS circuits. The KTXO has a frequency range of 4 to 50 MHz; the KTVXO has a frequency range of 10 to 20 MHz. You can obtain a fine frequency adjustment with 1 to 5V on pin 1. Modulation sensitivity for the KTVXO is 10 ppm/V min. Both oscillators are available in the temperature range of -20 to +70°C with an aging rate of 1 ppm/year. Frequency tolerance is 3 ppm. From \$15 (1000). Delivery, six to eight weeks ARO.

**Kyocera International Inc.**, Electronic Components Group, 11425 Sorrento Valley Rd, San Diego, CA 92121. Phone (619) 454-1800.


Circle No 378

### MULTIPLEXER

The MX327 multiplexes as many as 32 channels of the IBM 3272's I/O on
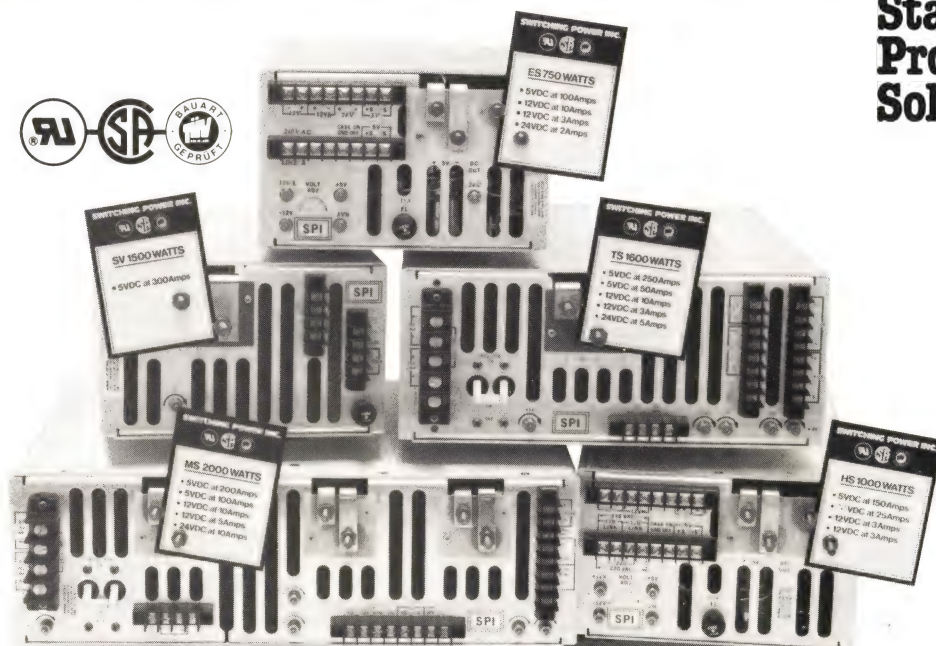
# Unique, Complex Power Requirements?

...Medical Systems--Telecommunication Systems--Graphic Systems--Mainframe Systems--Minicomputer Systems--CAE Workstations



### Standard Product Solutions!

- Up to five outputs
- Up to 3000 Watts
- Up to 300 Amps
- AC to DC
- DC to DC
- 50° C Power Ratings
- Paralleling
- High Efficiency
- Proven Products
- Wide Range AC Input
- Reliability
- Versatility



## SWITCHING POWER INC

3601 Veterans Highway, Ronkonkoma, NY 11779  
Telephone 516 / 981-7231 TWX 510 220 1528

CIRCLE NO 37



# CURRENT MODE CONTROL

The Right Way From Cherry Semiconductor

Cherry Semiconductor's new CS-3842A and CS-3843A current mode control ICs deliver enhanced off-line switching power supply performance. Incorporating a new precision temperature-controlled oscillator and maximum duty-cycle clamp, CSC current mode circuits reduce external component count, and system cost, to a minimum.

Special logic ensures that  $V_{ref}$  is stabilized before the output stage is enabled. Ion-implant resistors provide tighter control of under-voltage lockout. Other features include low start-up current, pulse-by-pulse current limiting, and a high-current totem pole output for driving capacitive loads.


The CS-3842A family of current mode ICs are available now in surface-mount SO-8 packages as well as 8-pin DIP.

PWM CONTROL CIRCUITS	
CS-593	CS-1527A
CS-594	CS-2527A
CS-595	CS-3527A
CS-1524	CS-5560
CS-2524	CS-5561
CS-3524	
CS-1524A	<b>NEW</b>
CS-2524A	<b>CURRENT</b>
CS-3524A	<b>MODE</b>
CS-1525A	CS-2842A
CS-2525A	CS-2843A
CS-3525A	CS-3842A
	CS-3843A

CSC circuit design and packaging.

Current mode control . . . **The right way!**

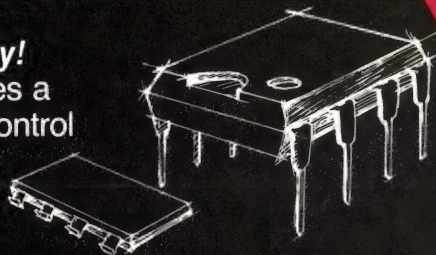Cherry Semiconductor manufactures a wide range of switching power supply control ICs. A Designers Guide describing the complete line is available on request.



## CHERRY SEMICONDUCTOR


CHERRY SEMICONDUCTOR CORPORATION • 2000 South County Trail, East Greenwich, Rhode Island 02818 / (401) 885-3600

CIRCLE NO 171


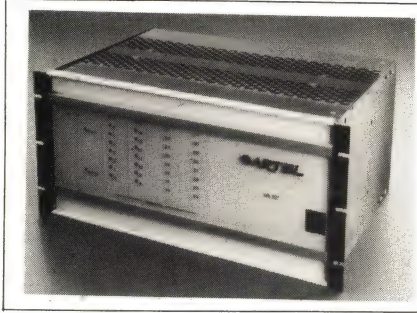
## COMPONENTS & PACKAGING

one optical or coaxial cable. It connects a 3272 controller to 3270 terminals and 3280 printers as far away as 5000 ft. The multiplexer accepts the inputs and multiplexes them into a signal that is then converted into light (for fiber-optic cable) or electrical pulses (for coaxial cable). At the far end, the signal is demultiplexed by a second MX327 into its



original form. The 19-in. rack-mounted unit is designed for synchronous applications at data rates to 2.3587M bps. Each modular unit contains four cards; additional cards can be added to reach the 32-channel capability. The multiplexer features diagnostic indicators on the front. It is plug compatible with standard BNC connectors for data-transmission and SMA-type connectors for optical transmission. Two 32-channel units, \$7600.

**Artel Communications Corp.**  
Box 100, West Side Station, Worcester, MA 01602. Phone (617) 752-5690.


Circle No 379
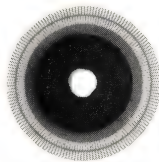
# Try Our Low Cost Solution To Your 1.5" Problem

When the fit is tight, the light-weight, low inertia V70 Series modular optical encoder fits in easily and provides top quality, performance at the lowest cost. Easy to install, these Honeywell units include a high stability polycarbonate photo-head, hermetically sealed light source and sensors, and a custom square-wave output comparator chip, just like its big brother,



the 2-inch Modular V90 Series. The V70 is designed for such tasks as pick-and-place robotic axis positioning, capstan tape drive velocity feedback, plotter pen position drives, etc. The V70 and V90 are available immediately in lower priced OEM quantities.



**SINGLE EVALUATION UNIT  
AT \$19.95 TO QUALIFIED  
O.E.M. CUSTOMERS  
CONTACT THE FACTORY  
FOR DETAILS OF OFFER!!**

## V70 Series

# Honeywell

Disc Instruments Subsidiary

102 East Baker Street, Costa Mesa, CA 92626  
714-979-5300 • TWX (910) 595-1987 DISC CSMA

CIRCLE NO 38




## FLAT CABLE

The AC Series gray flat cable and CSK Series multicolored cable are both available in 100-ft reels. The AC line spans 10 to 64 conductors, and the CSK covers 9 to 64 conductors, all on 0.05-in. center spacings. Wire gauge is 28 AWG, and maximum operating rating equals 105°C. Both series accommodate currents of 1A. Voltage rating equals 300 and 250V for the AC and CSK cables, respectively. 26-conductor AC, \$17.63; 26-conductor CSK cable, \$33.97. Delivery, stock to six weeks ARO.

**Amlan Inc.**, 97 Thornwood Rd, Stamford, CT 06903. Phone (203) 322-1913.

Circle No 380



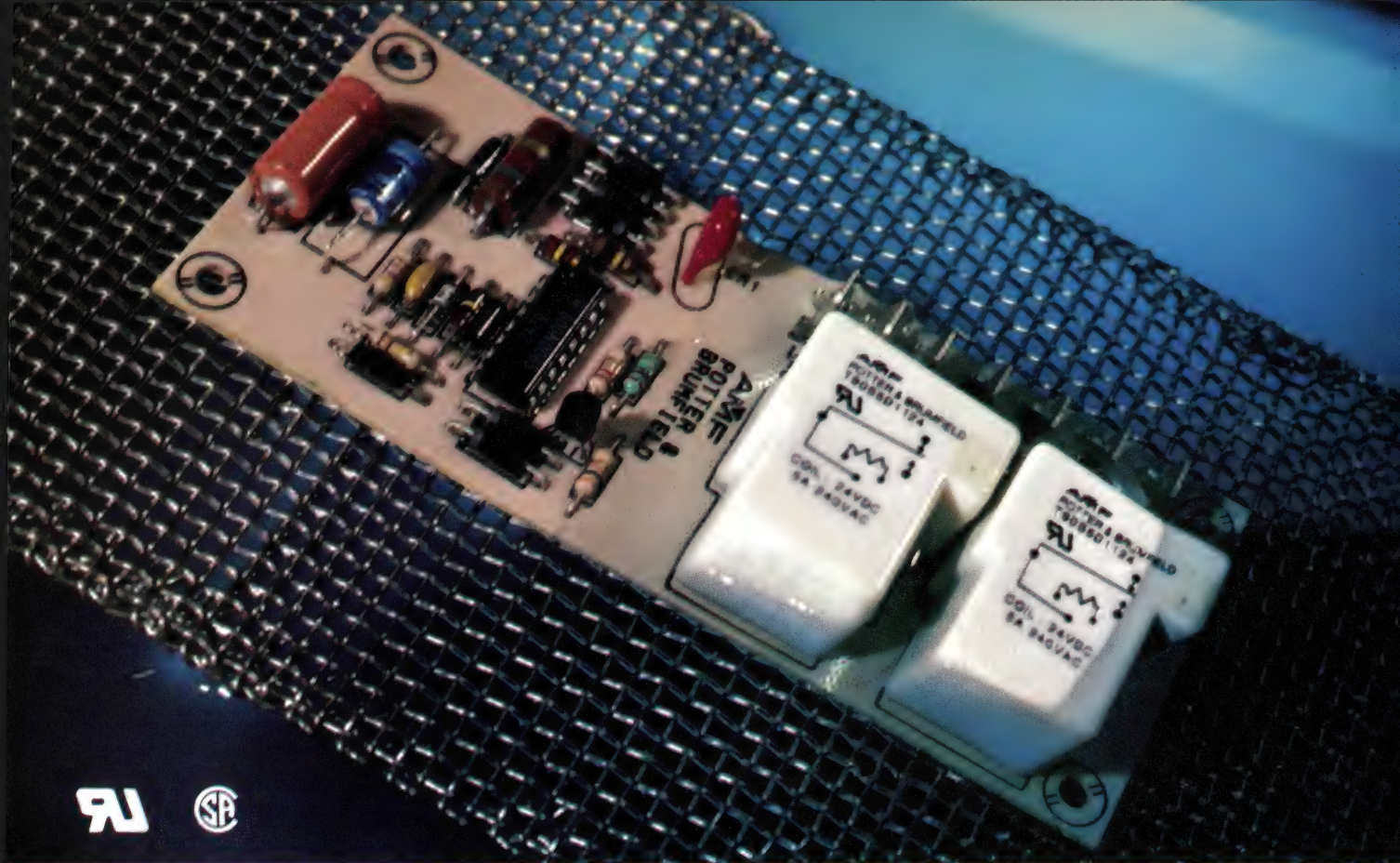

# P&B's T90 relay available for immediate delivery from stock!!!

## Low cost...

Now you can design low cost power switching into your products with Potter & Brumfield's T90 relay.

## Switches .5—30A...


Its small size and low coil power requirement (less than 1W) make the T90 the ideal printed circuit board mounted interface between your solid state devices and power loads.

## Open or sealed...

The T90 is available as an open-style relay, with an optional, snap-on dust cover or sealed to withstand immersion cleaning.
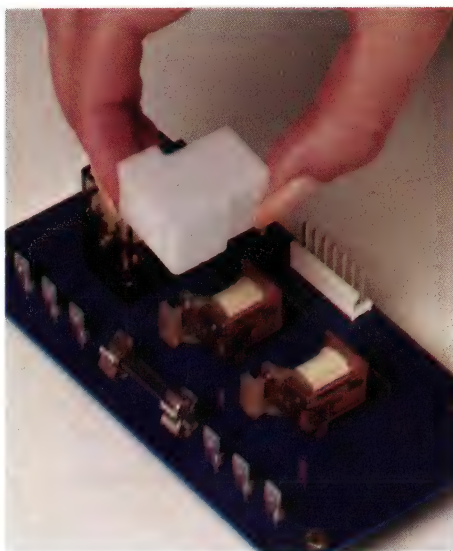
## Meets your design needs...

The T90 series offers the combination of features you've demanded for new generations of appliances, load management controls, business machines, HVAC equipment and similar applications.



## Consistent quality...

Our totally automated production under tight process control assures you of consistent, high quality relays, minimizing your needs for incoming inspection.

CIRCLE NO 170

## Find out more...


For more details on the T90, call our toll free number for the name of your authorized Potter & Brumfield distributor or your local P&B sales representative: **800/255-2550.**

Potter & Brumfield,  
A Siemens Company,  
200 South Richland Creek Drive,  
Princeton, Indiana 47671-0001.

**Regional Sales:** Oak Brook, IL, 312/887-0811;  
Braintree, MA, 617/848-6550;  
San Juan Capistrano, CA, 714/493-4503;  
Princeton, IN, 812/386-2130.

# Potter & Brumfield



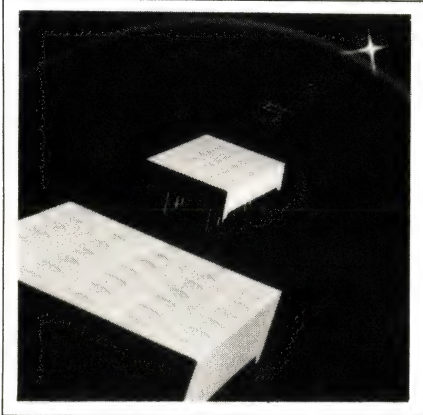

### LED DISPLAYS

With high-efficiency red characters measuring 1.05 in. high, HDSP-4500 displays are readable at distances to 60 ft. The displays feature a 5×7 dot-matrix font and are available in common-anode-row and common-cathode-row models. The units are housed in DIPs to facilitate mounting on pc boards. The displays can be stacked end to end, or side by side to satisfy graphics

panel applications. Luminous intensity (for 10-mA drive) equals 3.5 mcd/dot. \$6.65 (1000).

**Hewlett-Packard Co.**, 1820 Embarcadero Rd, Palo Alto, CA 94303. Phone local office.

Circle No 381

### MULTIPLEXER

The CDS-372 general-purpose, fiber-optic multiplexer is compatible with Datalog, AT&T's virtual circuit switch. The CDS-372 is available with 36 or 72 channels, each channel with one data and one control line. It handles asynchronous data at rates to 100k bps and synchronous data to 76.8k bps. The basic 36-channel model can be expanded to the 72-channel model. The unit features mass-terminated 50-pin connectors with each connector handling six RS-232C channels. The unit includes diagnostic capabilities to determine synchronization and

local and remote loopback functions. Features also include a choice of stand-alone or rack-mounted versions, full-duplex operation, bit-error rate of  $1 \times 10^{-9}$  or better, and code transparency. From \$3950.

**Canoga-Perkins**, 6635 Independence Ave, Canoga Park, CA 91303. Phone (818) 887-1897.


Circle No 382



### PANEL METER

Mini Versameters feature a low-profile package to save panel space. They are available in voltage and current models. Decimal points are

# Power in numbers.

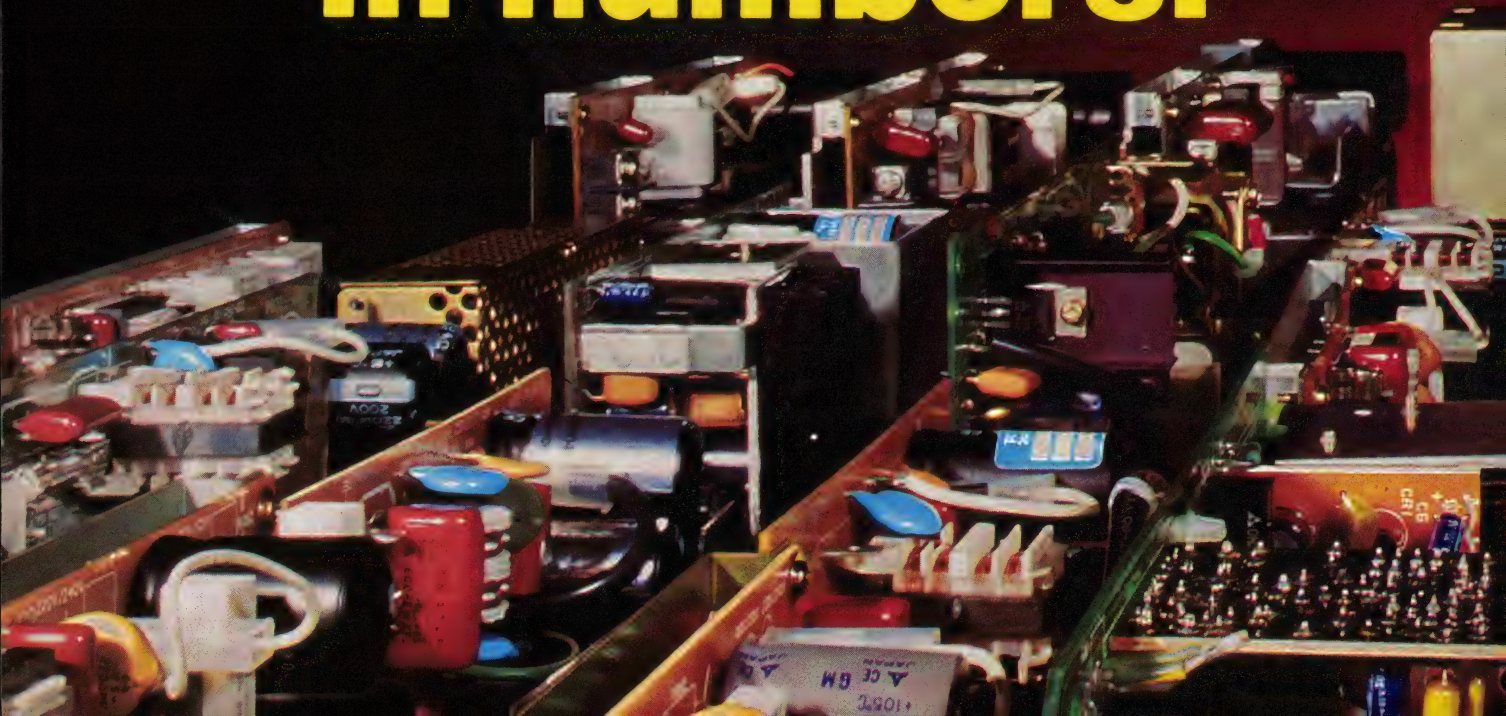



## COMPONENTS & PACKAGING


selectable via rear-panel connections. The voltage and current models accept inputs from 200 mV to 100V dc and 200  $\mu$ A to 2A, respectively. Model G922DA allows users to program and display a 4- to 20-mA process signal generated by a transducer. All meters feature a 0.5-in.-high, 3½-digit LED display. From \$69.

**Extech Instruments Corp.**, 150 Bear Hill Rd, Waltham, MA 02154. Phone (617) 890-7440.

Circle No 383
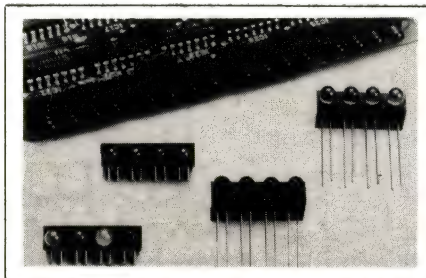
### LED ARRAYS

The PCL1904/2004 Series quad LED arrays offer a choice of four colors—red, yellow, amber, or green. The units feature T-1¾-size LEDs and are available in either standard-bright, medium-bright, high-efficiency or super-bright versions. Bicolor versions are also available. Offering good alignment



and matched color, these arrays come in mitered packages with horizontally mounted LEDs. \$0.74 (1000). Delivery, four to six weeks ARO.


**Data Display Products**, 301 Coral Circle, El Segundo, CA 90245. Phone (800) 421-6815; in CA, (213) 640-0442.

Circle No 384
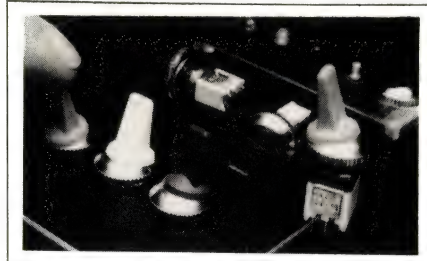
### PADDLE SWITCH

The Tiny Paddle Switch is designed for panel mounting. The actuator is available in red, black, white, blue, and custom colors, all with matte

finish. The switch mounts in a ¼-in. hole that allows simple retrofitting, and it features wire-lug, pc-board, or wire-wrap terminals. Contact ratings are 3A at 125V ac or 28V dc, or 0.4 VA at 20V ac or dc. The on-on model has a life expectancy of 80,000 cycles at full load. You can choose either silver or gold contacts. A typical on-on wire-lug ver-



sion costs approximately \$3 (2500). Delivery, six weeks ARO.

**Alco Electronic Products Inc.**, 1551 Osgood St, North Andover, MA 01845. Phone (617) 685-4371. TWX 710-342-0552.

Circle No 385

## Panasonic® Switching Power Supplies

And they're available now for immediate off-the-shelf delivery.


Just tell us what you need. Single or dual inputs. Up to four outputs. Outputs ranging from 5V to 24V. And 0.1 to 30.0 amps.

Of course, Panasonic switching power supplies meet the necessary safety approvals of UL, CSA and TUV plus noise specifications ratings from FCC Class A to VDE Class B.

So, now that you've got our number, get the rest of the story. Panasonic Industrial Company, Computer Components Division, One Panasonic Way, Secaucus, NJ 07094. (201) 392-4290.

## Panasonic Industrial Company

CIRCLE NO 39

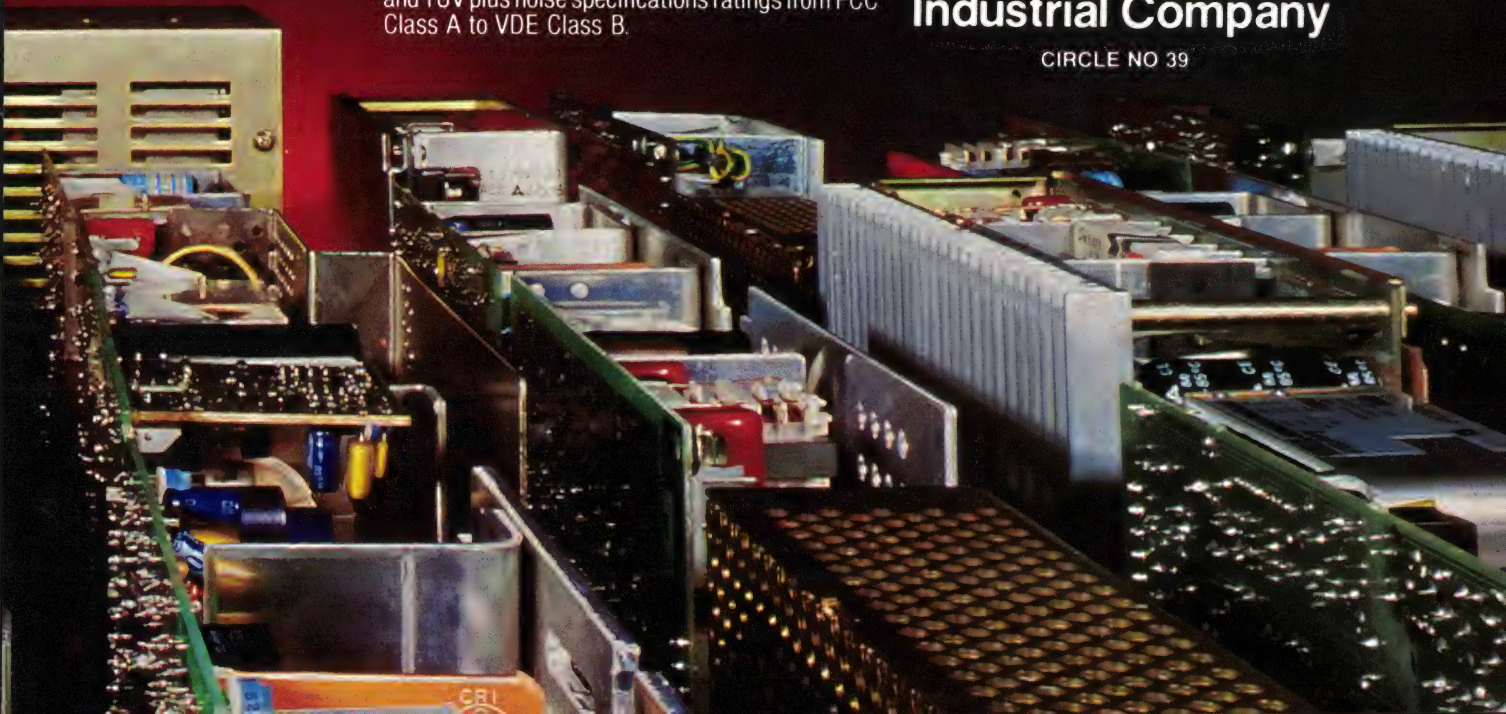



# Activate Your System —



## with PEP™ — the Touch Entry Panel

Make your system easy-to-use with the touch-activated PEP™ from IEE. **Training costs and input errors are reduced** when the operator can concentrate on the task at hand, not on complicated protocol.

PEP **goes where a CRT can't**—it's less than 3.4 inches (87mm) deep.

PEP is available in **two sizes**—a compact 12×40 character format (480 PEP) and a larger-character 8×32 (256 PEP). Both come in a choice of display colors—Orange, Green or Red.

Four **standard interface** modes make communication a snap—choose RS-232-C, 20mA current loop, RS-422-A, or parallel data bus.

IEE has a special **evaluation kit offer** so you can see how a PEP will look and work in your system. Call or write us today!




Industrial Products Division  
**Industrial Electronic Engineers, Inc.**  
7740 Lemona Ave., Van Nuys, CA 91405  
Tel. (818) 787-0311 - Ext. 418  
FAX: (818) 902-3723

Circle 7 for Immediate Application

Circle 46 for Reference Material



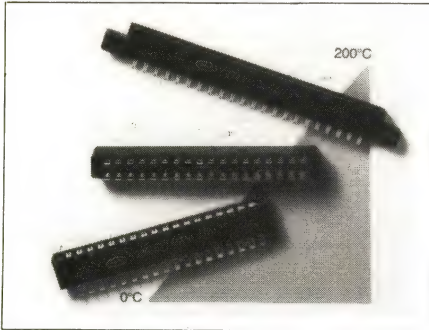

## CONNECTORS

A high-temperature thermosetting molding compound used for the connector body and beryllium copper used for the contacts allow the EB7D and EB8 Series edgeboard connectors to withstand operating temperatures of 200°C. The connectors feature 0.156-in. center-to-center spacings on 0.140- and 0.200-in. grids, respectively. Selective gold plating of the contacts is standard. The devices are available with a variety of terminals including dip-


solder, solder-eyelet, and card-extender styles. You can order the EB7D with six, 10, 12, 15, 22, 36, or 43 contacts per side; the EB8 has a choice of six, 10, 12, 15, 18, 22, 24, or 25 contacts per side. Approximately \$4.80 (1000) for an EB8 with two rows of 22 or 44 contact positions and card-extender terminals. Delivery, four to six weeks ARO.

**Dale Electronics Inc.**, Box 609, Columbus, NE 68601. Phone (605) 665-9301.

Circle No 386
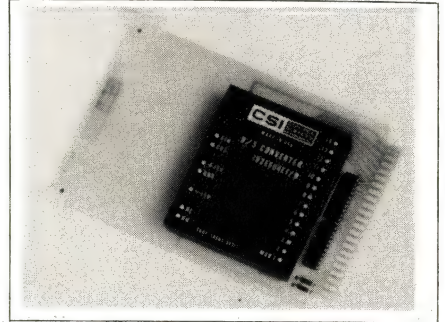
## D/S CONVERTERS

The SCB-22 Series of card-mounted digital-to-synchro (resolver) converters provide 1.5 or 5W of output power to drive size 11 torque receivers or control transformer loads for simulator or trainer applications. All outputs are short-circuit and overload protected; the 5W units



include thermal cutoff with automatic recovery from locked-rotor conditions. Standard transformer-isolated outputs are 11.8 or 90V line-to-line with 26 or 115V rms reference at 400 Hz. Twelve- or 14-bit digital inputs are stored in a set of TTL-compatible latches. The cards measure 4.24×6.25 in. From \$470. Delivery, four to six weeks ARO.

**Control Sciences Inc.**, 9509 Vassar Ave, Chatsworth, CA 91311. Phone (818) 709-5510.

Circle No 387

## Would you support a 32 bit project with a 2 bit operating system? Of course you wouldn't!

# MTOS

We wouldn't either. That's why we developed the MTOS family of sophisticated but user-friendly real-time, multi-tasking, multi-processor operating systems.

Rather than making MTOS small for the sake of smallness, we put a lot of very useful features in MTOS, so you wouldn't have to re-invent them. Take MTOS-UX, for example. It supports multiple processors on the bus, links to UNIX™\*, mailboxes, signals, event flags, semaphores and a completely dynamic set of system objects.

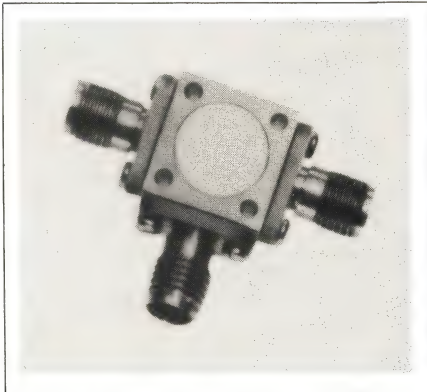
**ipi Industrial Programming Inc.**

For detailed information on any of our systems, call or write (800) 228-MTOS, Industrial Programming, Inc., 100 Jericho Quadrangle, Jericho, NY 11753, (516) 938-6600, Telex: 429808 (ITT).

\*UNIX is a trademark of AT&T Information Systems







## MINIATURE MIXER

Housed in a 0.5×0.5×0.2-in. package, the Model DCM4-26 mixer features ground tabs that facilitate soldering to both coplanar and microstrip ground planes. The mixer was designed to meet small-size requirements for wideband electronic-counter-measure mixers and to provide shielding and low VSWR connections. Removable SMA connectors are provided for testing prior to solder-in installation.


Typical specifications in the 4- to 26-GHz band include RF range of 4 to 26 GHz, local-oscillator (LO) range of 4 to 26 GHz, IF range of 1 to 10 GHz (−1 dB), and LO injection of 10 to 13 dBm. Typical conversion loss is 9 dB from 2 to 18 GHz and 10 dB from 18 to 26 GHz. \$995. Delivery, 120 days ARO.

**RHG Electronics Laboratory Inc.**, 161 E Industry Ct, Deer Park, NY 11729. Phone (516) 242-1100. TWX 510-227-6083.

Circle No 388
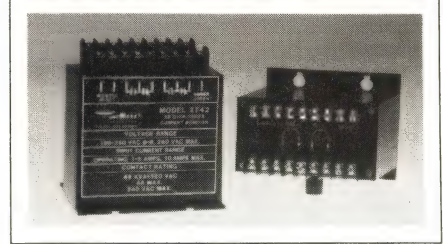
## CURRENT SENSOR

The Model 2742 current-sensing relay is designed for 3-phase applications. You can use it to monitor for undercurrent or overcurrent conditions: As shipped, the device will monitor undercurrent conditions; by adding a wire, you can adapt it to monitor overcurrent conditions. You can also add a NC pushbutton to the



relay if manual reset is required. The device is housed in a high-impact ABS plastic, machine-tooled case. Versions are available for 24, 120, and 240V ac sources. The sensor can monitor to 480V ac, 5A; you can extend the range by using current transformers. \$133.75.

**Time Mark Corp.**, 11440 E Pine St, Tulsa, OK 74116. Phone (918) 438-1220.

Circle No 389

## IC SOCKETS

The 2300 and 2400 Series sockets accommodate 70-mil-lead spacing ICs, thereby accommodating  $\mu$ Ps,

# AT LAST! 500,000 DIRECT REPLACEMENTS PLUS 500,000 SUGGESTED REPLACEMENTS.

From over 400 electronic component manufacturers worldwide--The **NEW Alternate Source and Replacement Series** from D.A.T.A. is the most complete and up-to-date reference source available for locating solid-state electronic devices.

Designed for easy use by engineers, purchasing agents and others, this series can help you:


- Locate alternate sources to complete your design.
- Find replacements for unavailable parts.
- Search for replacement parts by generic types.

In four authoritative Guides, the complete series includes:

**DISCRETE SEMICONDUCTORS**  
Replacement information on transistors, diodes, thyristors, optoelectronic and microwave devices.

**Direct Replacement Guide**  
identifies over 350,000 direct replacements from 352 manufacturers.

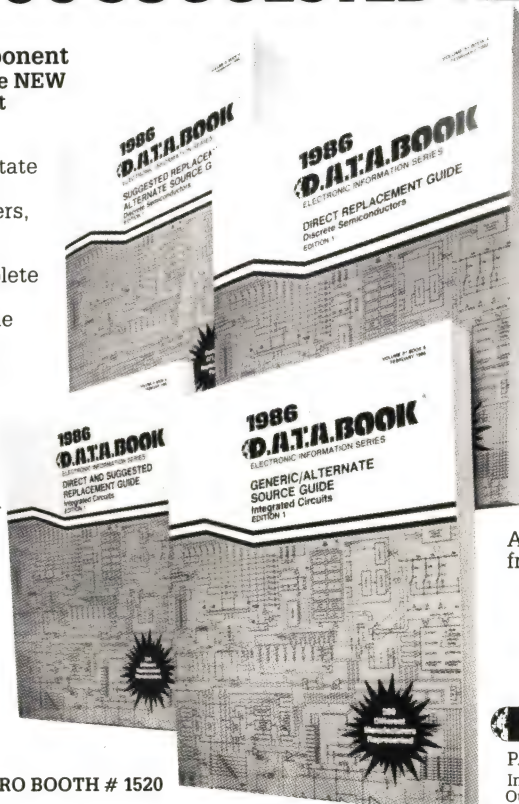**Suggested Replacement/Alternate Source Guide**  
identifies more than 470,000 suggested replacements from 92 manufacturers.



## INTEGRATED CIRCUITS

Replacement information on digital, interface, microprocessor, audio/video, linear and memory ICs.

**Direct & Suggested Replacement Guide** identifies more than 150,000 direct and suggested replacements from 127 manufacturers.

**Generic/Alternate Source Guide** organized by generic family, identifies over 110,000 alternate sources from 289 manufacturers.

**\$95 EACH (U.S.)**

- Price includes two complete semiannual editions of each guide.

**SPECIAL OFFER! Purchase any two guides together for \$150 and save \$40.** There's never been a better time to find more direct and suggested replacement information than with this special introductory offer! To place your order or receive a **FREE** brochure on the

Alternate Source and Replacement Series from D.A.T.A., call TOLL-FREE

**1-800-854-7030**

(In CA call 1-800-421-0159)

**30-Day Money-Back Guarantee**

Complete Series also available on magnetic tape.

**D.A.T.A. INC.** A Cordura Company

P. O. Box 26875, Dept. S0746, San Diego, CA 92126

In Canada: Call 416-674-1717

Outside U.S. and Canada: Telex (England) 95671


VISIT US AT ELECTRO BOOTH # 1520



μCs, and video controllers from Hitachi, Mitsubishi, Fujitsu, and NEC. They have a machined sleeve, a machined inner contact, and solid- and open-ladder glass insulators. The sockets are available in 28-, 30-, 40-, 42-, 52-, and 64-pin versions. The sockets are tested to standards such as MIL-STD-1344A and MIL-STD-202. Gold-plated (30-μin.) and tin/lead-plated contact versions are available. Gold contact, \$5.32; tin/lead contact, \$4.48 (100).

**Augat Inc.**, Box 779, Attleboro, MA 02703. Phone (617) 222-2202.

Circle No 391

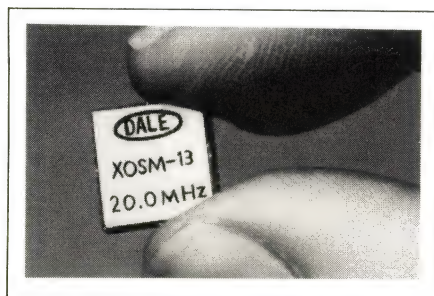

## CLOCK OSCILLATOR

The XOSM-13, a TTL-compatible clock oscillator, is available in a frequency range from 16 to 24 MHz. Frequency stability is  $\pm 100$  ppm over  $-55$  to  $+125^\circ\text{C}$ . Supplied in a 40-pin leadless chip carrier, it occupies  $0.48 \times 0.48$  in. of board space. It's hermetically sealed to meet MIL-STD-883, Method 1014 and is designed for reflow soldering. A typical 16-MHz XOSM-13, \$48.26 (100).

**Dale Electronics Inc.**, 2064 12th Ave, Columbus, NE 68601. Phone (602) 967-7874.

Circle No 392

## OPTOCOUPERS

A 16-pin, dual-channel, line-receiver family of optocouplers provides a guaranteed common-mode transient immunity of  $\pm 1000\text{V}/\mu\text{sec}$ . The hermetically sealed devices are available either as standard products (HCPL-1930) or with full MIL-STD-883, level B testing (HCPL-1931). Both types are specified over the

full military temperature range. In line-receiver applications, an input-current regulator serves as a line termination to clamp line voltage and to regulate the LED current. The regulator also minimizes the effect of line reflections and shunts excess current (above a typical LED current of 12.5 mA). Optocouplers can accept inputs to 10M bps. Prop-

agation delay time to both high- and low-output levels is 100 nsec max. At an input current of 10 mA, the output will sink six TTL gates. HCPL-1931, \$92; HCPL-1930, \$50.75 (50).

**Hewlett-Packard Co.**, 1820 Embarcadero Rd, Palo Alto, CA 94303. Phone local office.

Circle No 393

## Answers for today's engineers, educators and researchers.

**S**AMS books provide the most current information and the latest developments in technology today. They discuss theories, provide practical applications, and explore every level of electronics from the basics to state-of-the-art equipment.

### Reference Data for Engineers: Radio, Electronics, Computer, and Communications (7th Edition)

Edward C. Jordan, Editor-in-Chief

Previously a limited private edition, now an internationally accepted handbook for engineers. Includes over 1300 pages of data compiled by more than seventy engineers, scientists, educators and other eminent specialists in a wide range of disciplines. Presents information essential to engineers, covering such topics as: digital, analog, and optical communications; lasers; logic design; computer organization and programming, and computer communications networks. An indispensable reference tool for all technical professionals. No. 21563, \$69.95.

### Image Tubes

Illes P. Csorba

This text provides a wealth of valuable, hard-to-find data on electron optics, imaging, and image intensification systems. Renowned scientist-engineer-inventor Illes Csorba explains every detail of image tube theory, design, construction, and components. He includes material on the design and operation of camera tubes, power components and secondary electron emitters, as well as data on photomultiplier tubes and electron guns. Engineering students, practitioners, and managers will find this book invaluable for developing a better understanding of electronic imaging. No. 22023, \$44.95.

### Principles of Solid-State Power Conversion


Ralph E. Tarter, Editor-in-Chief

This comprehensive manual puts all the essential information about solid-state power conversion in an easy-to-use format. The author explores such fundamentals as vital protection and efficiency considerations, semiconductor, and component selection. He explains how to increase product efficiency and safety, improve performance, and achieve high-packing densities. Every facet of power conversion is detailed — switching systems, system operation and design, and passive devices. Over 20 years of hands-on experience is outlined in this excellent reference book. No. 22018, \$44.95.
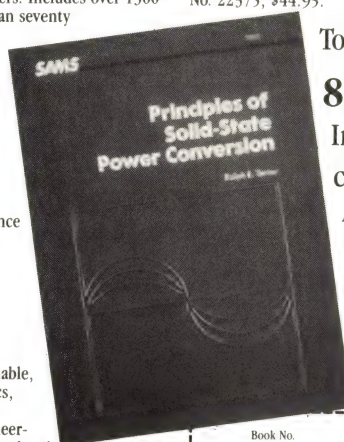
### Gallium Arsenide Technology

David K. Ferry, Editor-in-Chief

Gallium arsenide has replaced silicon in the design of optoelectronic devices. This comprehensive introduction to the structure and properties of this wonder compound also explores its application in analog and digital technology. Editorial contributions by leading experts document applications in chip design, integration levels, and monolithic microwave integrated circuits (MMICs). They examine the new bandgap engineering and the uses of gallium arsenide in MESFET integrated circuits, photodetectors, and optical sources. An essential library edition for professionals in electronics-related fields. No. 22375, \$44.95.



To order call

**800-428-SAMS**

In Indiana

call 317-298-5566

Ask For Operator 819

**SAMS**

A Division of Macmillan, Inc.

Book No.	Quantity	Price
Shipping & Handling		\$ 2.50
AR, CA, FL, IN, NC, NY, OH, TN, WV residents add local sales tax		\$
Total		\$
Name _____		
Company _____		
Address _____		
City _____		
State _____ Zip _____		
Daytime Telephone No. _____		
<input type="checkbox"/> Bill my credit card <input type="checkbox"/> VISA <input type="checkbox"/> MC <input type="checkbox"/> AE		
<div style="border: 1px solid black; width: 100px; height: 20px;"></div> Account No.		<div style="border: 1px solid black; width: 50px; height: 20px;"></div> Exp. Date
Signature (required) _____		
<input type="checkbox"/> Check or money order enclosed. Make checks payable to Howard W. Sams & Co. Mail this form with payment to: Howard W. Sams & Co., Inc., Dept. DM • 4300 West 62nd Street • Indianapolis, IN 46268		
EDN041786		DM819


Prices subject to change without notice

CIRCLE NO 45





# Gives You More

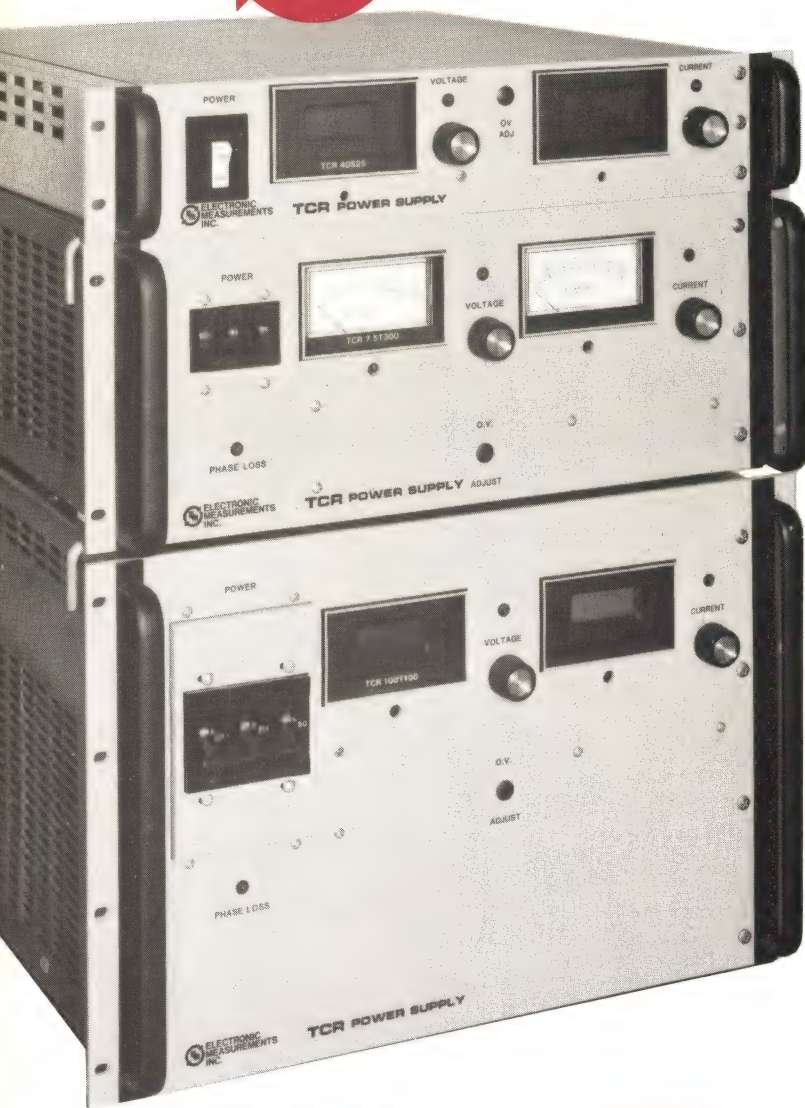

## In 10 and 30 SCR High Power DC Power Supplies!

■ *More Watts per \$ . . .* for the **BEST PRICE/ PERFORMANCE VALUE** in SCR type power supplies anywhere!

■ *More Power per Cubic Inch . . .* to conserve vital space.

■ *More Models . . .* 101 models to select from to give you exactly what you need.

■ *More Reliability . . .* backed by a 5 Year Warranty on both parts and labor and world wide service.

■ Plus . . . everything you expect from the leader in SCR High Power DC Power Supplies. Compliance to VDE-875 Level N and VDE-871 Level A for line conducted RFI • Fully Programmable • Local or Remote Sense • High Efficiency • Fully adjustable from 0 to max. value • CV/CC Automatic Cross-over • Fan Cooled — FOR GREATER RACKING DENSITY . . . and much, much more.

Partial listing of 10 models

Model	Output Voltage	Output Current	Price
TCR 150-S4	0-150V	0-4A	\$785
TCR 60-S18	0-60V	0-18A	\$985
TCR 7.5-S200	0-7.5V	0-200A	\$1350
TCR 600-S4.5	0-600V	0-4.5A	\$1650
TCR 10-S50	0-10V	0-50A	\$785
TCR 300-S3	0-300V	0-3A	\$985
TCR 40-S45	0-40V	0-45A	\$1350
TCR 20-S135	0-20V	0-135A	\$1650
TCR 20-S90	0-20V	0-90A	\$1350
TCR 10-S240	0-10V	0-240A	\$1650

Partial listing of 30 models

Model	Output Voltage	Output Current	Price
TCR 7.5-T300	0-7.5V	0-300A	\$2295
TCR 10-T500	0-10V	0-500A	\$2800
TCR 100-T100	0-100V	0-100A	\$3890
TRC 30-T100	0-30V	0-100A	\$2295
TCR 20-T250	0-20V	0-250A	\$2800
TCR 20-T500	0-20V	0-500A	\$3890
TCR 160-T30	0-160V	0-30A	\$2800
TCR 10-T750	0-10V	0-750A	\$3890
TCR 120-T40	0-120V	0-40A	\$2800
TCR 500-T5	0-500V	0-5A	\$2295

To order or obtain more information, **CALL TOLL-FREE 800-631-4298.\*** or contact:


 **ELECTRONIC MEASUREMENTS INC.**  
405 Essex Road,  
Neptune, N.J. 07753

\*In NJ, AL, HI and Canada, call 201-922-9300.

CIRCLE NO 157



## NEW PRODUCTS: ICs & SEMICONDUCTORS

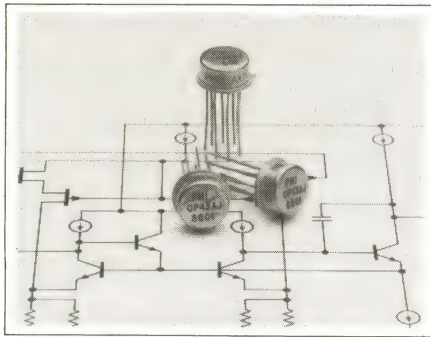


### OP AMP

Offering the same dc specifications and 5-pA bias current as the OP-41, the OP-43 features a slew rate of 5V/ $\mu$ sec min and a gain-bandwidth product of 2.4 MHz typ. It achieves this speed while drawing a supply current of only 1 mA max. CMR is 100 dB min, and the op amp is stable with closed-loop gains of  $-1$  or  $+2$ . A cascode input stage stabilizes bias current against changing common-mode voltages, and improves common-mode-rejection linearity. The device drives a 100-pF load

without oscillation and has power-supply rejection of 92 dB min and supply-current consumption of 1 mA max. In an 8-lead, TO-99 metal can, \$3.50 (100).

**Precision Monolithics Inc.**, 1500 Space Park Dr, Santa Clara, CA 95052. Phone (408) 727-9222.

Circle No 394

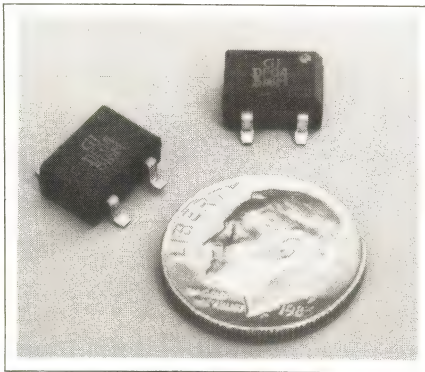

### BRIDGES

The DF-S Series of miniature single-phase surface-mount bridge rec-

tifiers includes seven 1A devices that have glass-passivated junctions and a surge overload rating of 50A pk. They exceed MIL-STD-19500 environmental standards and have voltage ratings ranging from 50 to 1000V. In molded plastic cases, \$0.30 (1000).

**General Instrument Corp.**, Discrete Semiconductor Div, 600 W John St, Hicksville, NY 11802. Phone (516) 933-3333.

Circle No 395

### VIDEO DACs

The NE5150/5151 triple 4-bit video DACs include composite-video functions to make output waveforms meet RS-170 and RS-343 industry standards. The NE5150 has an onboard voltage reference that provides immunity to power-supply variations. The chip has a refresh rate of 110 MHz; you can thus use it in applications having high-resolu-

*Continued on page 295*

# VMEbus TO SCSI INTERFACE

## TO: OPTICAL-MAGNETIC-DISC-TAPEDRIVERS, LASERPRINTERS AND OTHER INTELLIGENT PERIPHERALS


### COMPCONTROL

COMPCONTROL INC.  
15466 Los Gatos Blvd. Suite 109-365  
LOS GATOS, CALIFORNIA 95030  
Phone: 408-356-3817  
Twx: 510-601-2895

Member of  
the VMEbus International Trade Association



CIRCLE NO 54

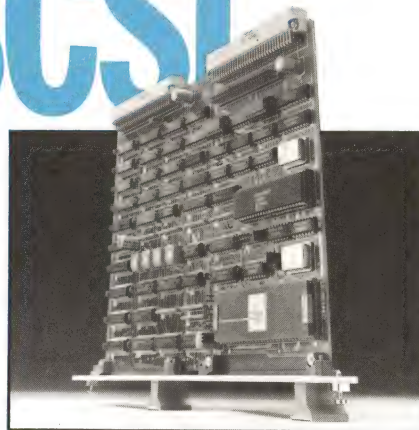

Application of the NCR 5386 guarantees conformance to the SCSI specifications. The four channel DMA controller gives additional power to your systems.

### VMEbus

COMPCONTROL B.V. EUROPE  
Stratumseindijk 31, P.O. Box 193  
5600 AD Eindhoven, Holland  
Telefoon (040) 12 49 55  
Telex 51603 comp nl



# 1986: THE YEAR OF THE COMET<sup>®</sup> MEMORIES

COMET<sup>®</sup> CMOS Overfast MEmory Technology

**New from MHS:**  
The Ultrafast memory  
family, that meets all  
your high speed data-  
processing requirements.

**25/35/45 ns.** Three figures tell it all.

PERFORMANCES		
	ORGANIZATION	ACCESS-TIME
HM 65747	4 K x 1	25/35/45
HM 65748/49	1 K x 4	25/35/45
HM 65767	16 K x 1	25/35/45
HM 65728/29	2 K x 8	35/45/55
HM 65768/69	4 K x 4	25/35/45
HM 65770	4 K x 4	35/45
HM 65787*	64 K x 1	35/45
HM 65788*	16 K x 4	35/45

\* Available late 86

They're the access times of the new ultra-fast advanced CMOS COMET<sup>®</sup> memories from MHS. These speeds are the fastest available on the CMOS market. Other COMET<sup>®</sup> features include a wide operating temperature range, CMOS consumption, automatic power down mode, and outstanding resistance to electrostatic discharge. COMET<sup>®</sup> memories are thus an effective

state-of-the-art replacement for bipolar or ECL technology products.

**MHS**  
MATRA HARRIS SEMICONDUCTOR

**FRANCE**  
"Les Quadrants"  
3, avenue du Centre  
78182 St-Quentin-en-Yvelines.  
Tel.: (33) 1 - 30 43 62 72


**ITALY**  
Via Fratelli Gracchi 48  
I-20092 Cinisello Balsamo  
Tel.: (39) 2-6188282

**SWEDEN**  
Stockholmsvägen 116  
S-183 38 Täby  
Tel.: (46) 8-7921240

**UNITED KINGDOM**  
Eskdale Road Winnersh  
Triangle, Berkshire  
Wokingham RG11 5TR  
Tel.: (44) 734-698787

**GERMANY**  
Erfurterstrasse 29  
D-8057 Eching  
Tel.: (49) 89-3190050

CIRCLE NO 173

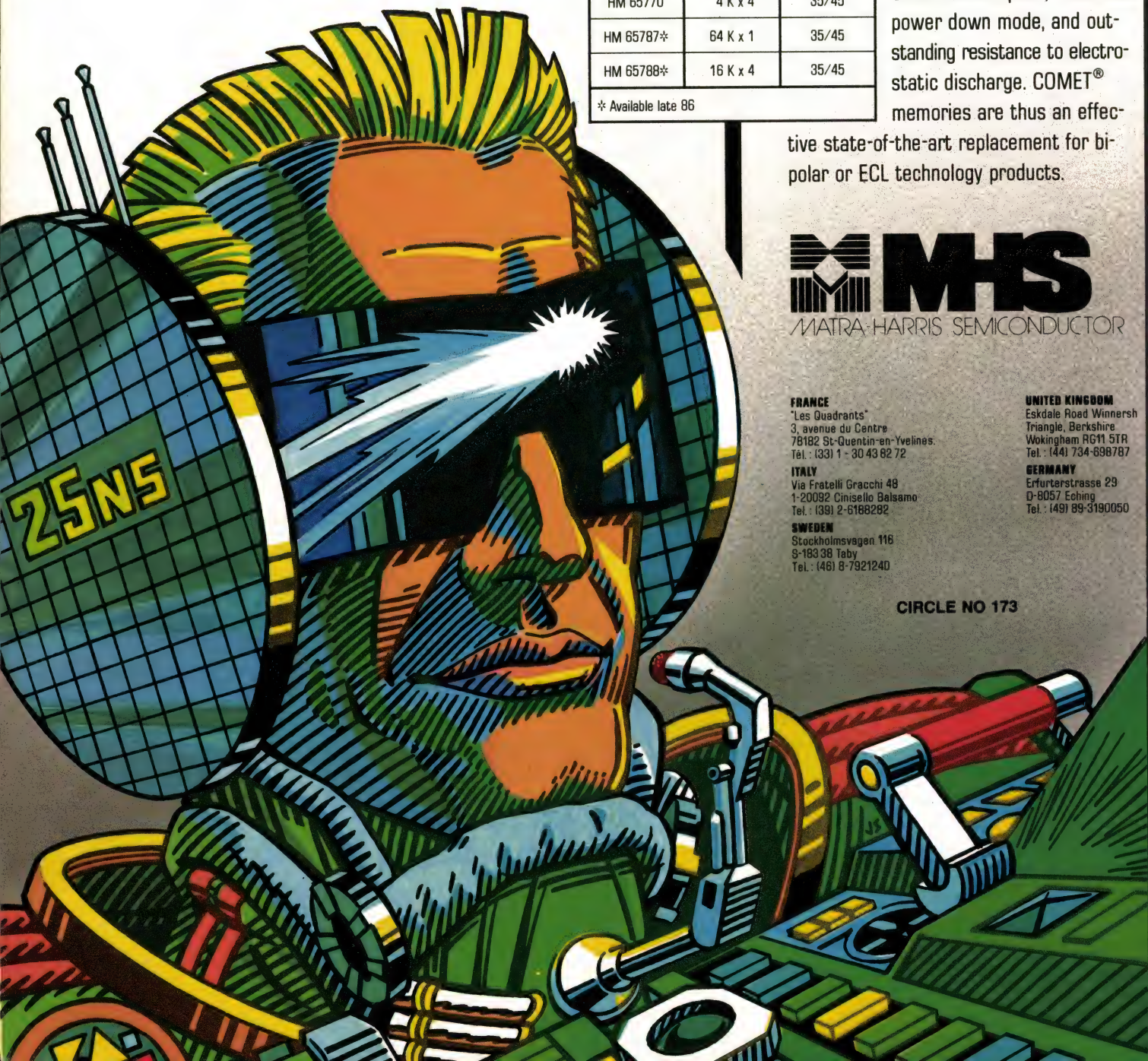





# Memory Magic.

## No illusions. Just vastly superior memory boards from Plessey Microsystems.

There are no tricks involved in building memory boards that work like magic. All it takes is advanced technology, painstaking attention to quality and a knack for knowing just what the marketplace needs. At Plessey Microsystems, we've got it all . . . for your systems.

Every Plessey memory is built in a facility that meets U.S. (AQAP 1&2) and U.K. (DEF. STAN. 05-21) military standards. So you get mil spec quality at the best commercial pricing.

Plus a full year guarantee, double sourcing by Plessey in America and England and a range of memories to meet your every need.

### Work Wonders for Your Micro.

You don't need tricks to bring the wizardry of superior memory technology to your system. All you really need is Plessey Microsystems. Memory Magic without the tricks. Call us today or use the coupon below.

### Plessey Microsystems Memories

	Capacity/Slot	Parity	EDC	Data Bits	Write Access	Read Access	Volatile	Non-Volatile
Multibus*	2 Mbyte DRAM	•	•	8/16	200nS	200nS	•	•
VMEbus	4 Mbyte DRAM	•	•	8/16/32	150nS	270nS	•	•
VERSAbus†	4 Mbyte DRAM	•	•	8/16/32	300nS	300nS	•	
iLBX	2 Mbyte DRAM		•	8/16	200nS	200nS	•	
Bubble	2 Mbyte		•	—	36mS	36mS		•

\*TM Intel. †TM Motorola

Plessey and the Plessey symbol are registered trademarks of The Plessey Company plc.



# PLESSEY

**England**  
Water Lane  
Towcester  
Northants  
NN12 7JN  
(0327) 50312

**France**  
BP 74  
7-9 rue Denis Papin  
78194 Trappes Cedex  
(3) 0514952

**Germany**  
Bahnhofstraße 38  
D-6090 Russelsheim  
(0 61 42) 6 80 04

**United States**  
One Blue Hill Plaza  
Pearl River  
NY 10965  
(914) 735-4661

**CIRCLE NO 219**

For additional information, clip and mail to Plessey Microsystems Ltd., Water Lane, Towcester, Northants, UK NN12 7JN

Name \_\_\_\_\_ Title \_\_\_\_\_  
Company \_\_\_\_\_ Address \_\_\_\_\_  
Phone \_\_\_\_\_ Postcode \_\_\_\_\_  
EDN041786



# The INMOS 25ns Static RAM Family.

## Because some designers prefer life in the fast lane.


INMOS just gave you a passing lane for high-speed Static RAMs. You're no longer stuck in low gear with slow-speed memories. Simply shift into over-drive with our advanced high-performance CMOS products.

You can accelerate to access times of 25, 35 and 45ns with our IMS1423 (4Kx4) and 35, 45 and 55ns with our IMS1600 (64Kx1). Our IMS1620 (16K x 4) offers 45, 55 and 70ns access times.


Our fast memories are fuel efficient; perfect for your power requirements. With E high, they can be placed in a low standby condition. And for even higher efficiency, you can reduce the standby power by using CMOS input levels.

Soup-up your system design with our IMS1423, IMS1620 and IMS1600. And let the competition eat dust.

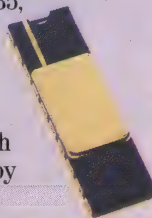INMOS Corporation, Colorado Springs, Colorado. Tel. (303) 630-4000 Bristol, England. Tel. 0272-290-861 Paris, France. Tel. (1) 687-2201 Munich, Germany. Tel. (089) 319-1028



Device	Access Times	Max Power (mW)		Process
		act	stby	
IMS1400 16K x 1	35,45,55	660	110	NMOS
IMS1420 4K x 4	45,55	605	165	NMOS
IMS1423 4K x 4	25,35,45	660	33 CMOS	CMOS
IMS1600 64K x 1	45,55,70	440	77 CMOS	CMOS
IMS1620 16K x 4	45,55,70	440	77 CMOS	CMOS

INMOS,  and IMS are trademarks of the INMOS Group of Companies.

CIRCLE NO 220



When you're ready to make tracks, not follow them, call INMOS.





tion graphics and imaging. The device resolves 16 gray-scale levels. Also, it contains three separate ECL memory look-up tables with read/write controls—the tables consist of 16×4-bit RAMs for the red, green, and blue channels. The device contains four composite-video controls: blanking, sync, reference white, and 10% bright. On-chip registers latch these signals to prevent screen-edge distortions. All logic inputs to the chip are TTL and ECL compatible. The NE5151 has no memory look-up tables, but it can select colors from look-up tables in external-memory and access the three 4-bit DACs at update rates of 150 MHz. Both devices use  $\pm 5V$  supplies and operate over a 0 to 70°C range. \$43 (100).

**Signetics Corp**, Box 3409, Sunnyvale, CA 94088. Phone (408) 991-4516.

Circle No 396


transistors' reverse-biased safe operating area permits inductive-load switching to 500V at 30A with no degradation. 2N6922, \$12.60; 2N6923, \$14.50 (100).

**General Semiconductor Industries Inc**, Box 3078, Tempe, AZ 85281. Phone (602) 968-3101. TWX 910-950-1942.

Circle No 397

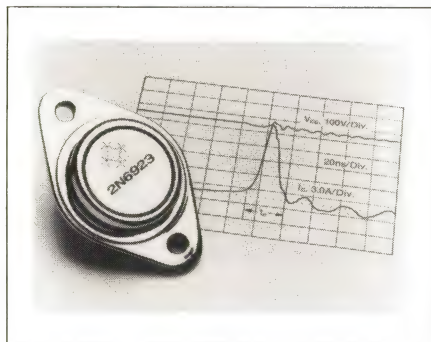
## SENSOR ICs

This line of ICs combines temperature monitors and heaters that allow monitoring airflow velocity past the device's package. Programming a power level to be dissipated by the internal heater will cause the die temperature to rise by an amount dependent on the thermal resistance between the die and the sur-


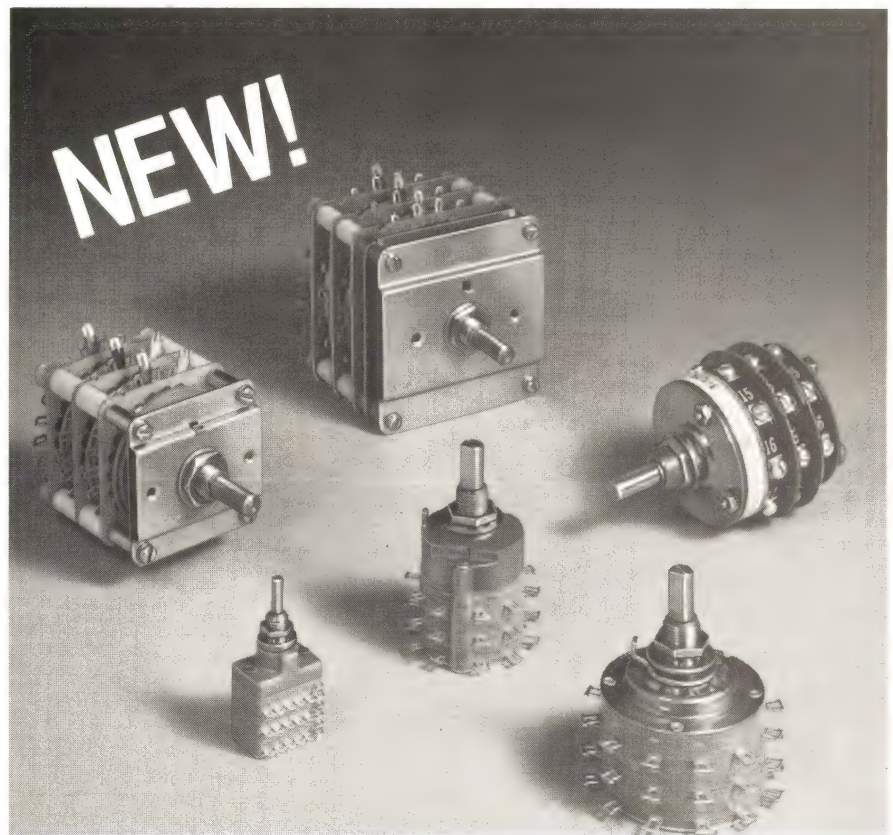
## NPN TRANSISTORS

The 2N6922 and 2N6923 bipolar switching transistors, which are members of the Switch Plus III family, offer guaranteed performance specs at 100°C; they also feature 15A nominal operating currents. The 2N6922 specs a  $V_{CE0}$  of 400V; the 2N6923 has a  $V_{CE0}$  of 450V. Typical  $V_{CE(sat)}$  is 0.8V at 100°C. The JEDEC-registered transistors suit 120/220V ac off-line switching applications at frequencies to 100 kHz. At 25°C, typical rise time is 32 nsec, fall time is 30 nsec, and storage time is 900 nsec. Operating and storage junction-temperature range is -65 to +200°C. The



## A Full Range of ELECTRONIC ROTARY SWITCHES from low-level to power applications

**Interrupt Ratings:** to 10 amps. **Continuous Ratings:** to 25 amps. Up to 48 Positions. **Applications include:** Communications Systems... Computers & Peripherals... Test Equipment... Power Supplies... Medical Electronics... Industrial Controls... etc. **Available with:** Special Contacting (encoded, shorting/non-short-ing, etc.); Special Terminals (PC mounts, solder & quick-connect); Dual Concentric Shafts; Key-operated; Spring-return; Field Adjustable Stops; etc.




180 King Avenue Weymouth, Massachusetts 02188

617/335/5200 • TWX: 710/388/0377

CIRCLE NO 55



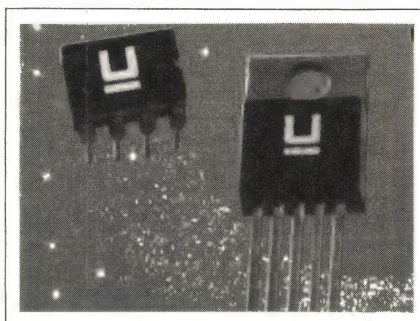rounding air. The effective thermal resistance is strongly dependent on the velocity of any airflow passing the package. As a result, the reported die temperature varies as a function of airflow. You can set a threshold using an onboard alarm comparator that results in an alarm output either if ambient temperatures rise above a specified level, or



if airflow in the surrounding environment diminishes to a set level. The devices come in three packages and satisfy a variety of applications. The UC3730N (in an 8-pin DIP) monitors ambient temperatures. The UC3730T (in a 5-pin TO-220) monitors surface temperatures, and the UC3730W (in a 12-pin "batwing": a 16-pin outline with protruding tabs) monitors airflow in power supplies or anywhere fan cooling is critical. \$1.75 (100).

**Unitrode Integrated Circuits Corp.**, 7 Continental Blvd, Merrimack, NH 03054. Phone (603) 424-2410.


Circle No 398

## Electron & Ion Beam high voltage applications...

**the  
BERTAN  
answer!**
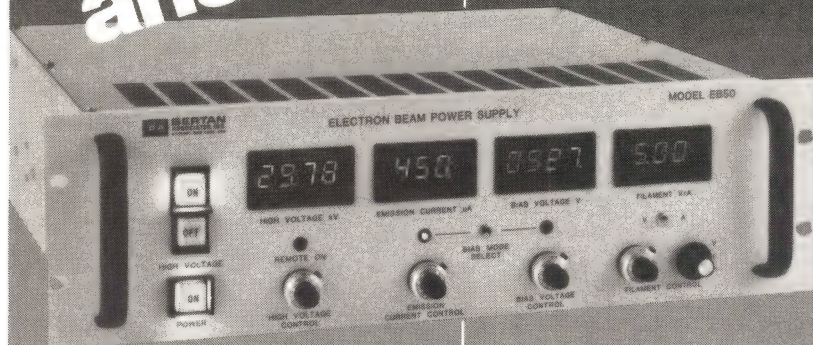
### BERTAN EB and IB Series

- Research and Material Analysis (Auger Microprobe, Scanning Electron Microscopes)
- Lithography-IC Manufacturing
- Testing of Chips and Wafers
- Microscopic Milling Machine (IB only)
- IC Mask Repair



Series EB and IB units contain three independently adjustable power supplies for beam acceleration, bias and filament. Series EB and IB have 3 user selectable filament regulation modes. Series EB has 2 selectable bias regulation modes including constant beam current. Both units feature remote analog programming, monitoring and are arc protected.

Send for the BERTAN EB Brochure and Catalog for additional information on this series. BERTAN also has a line of Single Output High Voltage Power Supplies for EB and IB applications.


**A BERTAN Applications Engineer is ready to assist you in satisfying your requirements.**

In addition to the models described above, BERTAN has designed units to meet special control, programming or monitoring circuits requirements and tight performance specifications.

See EEM or GOLD BOOK for specifications on over 100 standard products available from stock

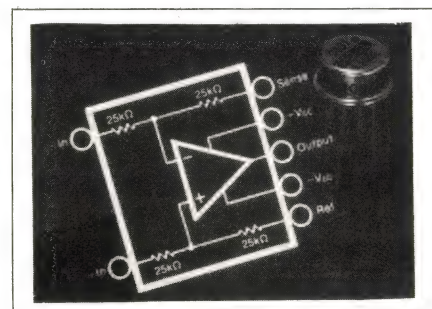**BERTAN ASSOCIATES, Inc.**

121 New South Rd., Hicksville, NY 11801 • (516) 433-3110 • TWX 510-221-2144



### DIFF AMP

The INA105 combines a premium op amp and a precision, low-drift resistor network on a single chip. Laser trimming ensures accuracy (gain error, nonlinearity, offsets, and CMR) of better than  $\pm 0.015\%$ , thus eliminating the need for external adjustments. The device can draw 20 mA from the positive supply, thereby simplifying 4- to 20-mA current-source and transmitter designs. Other features include CMR of 86 dB min, 5- $\mu$ sec settling to 0.01%, and 2-mA max quiescent current. In a metal TO-99 package, \$5.75 (100).

**Burr-Brown**, Box 11400, Tucson, AZ 85734. Phone (602) 746-1111.

Circle No 399

### ROMs

The LH5300 CMOS ROMs specify 30- $\mu$ A standby current and maximum operating currents as low as 30 mA. The LH2300 Series is the





# Development System Catches Bugs Before They Become Beasts.

## Orion's UniLab II<sup>™</sup> is four instruments in one.

Here's an **Advanced 48-Channel Bus-state Analyzer**, a real-time, real-world, **In-Circuit Emulator**, a **Stimulus Generator** for your special test cases, and a built-in **EPROM Programmer**, all in one small, \$2,995 powerhouse.

To find causes of software and hardware problems, Orion's "Non-intrusive Analysis"<sup>™</sup> concept triggers on bug symptoms you specify. This mature product supports 46

microprocessors with one easy-to-use instrument. Personality Paks get you started fast, and if you need them, Orion's team of Applications Engineers is only a toll-free call away.

You'll gain new development efficiency with our extensible language macro capability not found even in more expensive systems. UniLab II's disk-based intelligence in your PC, VAX<sup>™</sup>, or PDP-11 means much more for your money than in any stand-alone development system.

You've suffered long enough, call Orion today!

**CALL TOLL FREE: 1-800-245-8500**

415-361-8883 in California

VAX trademark of Digital Equipment Corp. UniLab is an Orion trademark.

EDN April 17, 1986

CIRCLE NO 221

### ACTION COUPON

Send me info on UniLab II and your No-Risk 10 Day Evaluation!

Name: \_\_\_\_\_ Title: \_\_\_\_\_

Company: \_\_\_\_\_

Address: \_\_\_\_\_


City: \_\_\_\_\_

State/ZIP: \_\_\_\_\_

Tel.: \_\_\_\_\_ Ext. \_\_\_\_\_

UniLab II EDN041786

Universal Development Laboratory

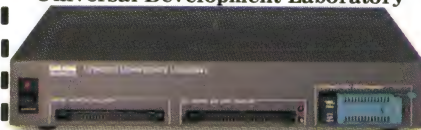

Orion Instruments, Inc.

**ORION**

702 Marshall Street  
Redwood City, California 94063




NMOS counterpart of the LH5300 devices. Both families offer densities ranging from 32k to 256k bits. For example, the LH23257 and LH53257 256k-bit (organized as 32k×8 bits) ROMs have 250-nsec max access times and are TTL compatible. Lower speed, lower power CMOS devices in the LH5300 Series offer densities from 32k to 512k bits. In JEDEC-standard, 28-pin plastic DIP, the LH23257 and LH53257 cost \$4.34 and \$6.18, respectively (5000). Delivery, eight weeks ARO.

**Sharp Electronics Corp.**, Sharp Plaza, Mahwah, NJ 07430. Phone (201) 529-8757.

Circle No 400
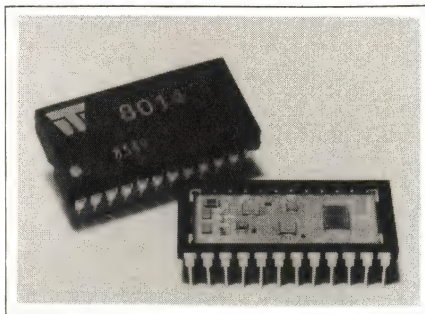
### EEPROM

The 8014 is a 16,384-bit programmable hybrid EEPROM that has a 2k×8-bit format and 3-state outputs. The device operates from -55 to +200°C. You can reprogram it at



temperatures as high as 150°C and read it at temperatures through 200°C. The EEPROM includes on-chip address latches and a separate output-enable control. At 200°C, the device offers a 250-nsec access time, an operating power-supply current of 30 mA/MHz, and a standby power-supply current of 20 mA. In a 0.600-in.-wide, 24-pin ceramic DIP, \$121 (100). Delivery, eight weeks ARO.

**White Technology Inc.**, 4246 E Wood St, Phoenix, AZ 85040. Phone (602) 437-1520. TWX 910-951-4203.

Circle No 401

### CMOS 8-BIT $\mu$ P

The MSM80C85A-2 operates at 5 MHz and draws less than 20 mA from a power supply. According to the manufacturer, this device is the industry's fastest CMOS version of the 8085A-type 8-bit  $\mu$ P. It uses a multiplexed address/data bus. The device provides direct interface to the on-chip address latches of the MSM81C55 CMOS static RAM/timer and I/O chip and also to the MSM83C55 CMOS 2k×8-bit ROM and I/O chip. The MSM80C85A-2 operates on a 4 to 6V supply and over -40 to +85°C. Other features include full compatibility with the NMOS 8085A; a 0.8- $\mu$ sec instruction cycle; an on-chip clock generator with external crystal; an on-chip controller; advance cycle-status information available for large-system control; four vectored interrupt inputs; a serial-in/serial-out port; decimal, binary, and double-precision arithmetic; and addressing capability.



# Everything is

Throughout the disk drive industry, the Fujitsu name stands for proven technology, superior performance and unmatched reliability.

Throughout the world, the name represents a company that comes through with products instead of promises.

And when it comes to 5¼" Winchester disk drives, Fujitsu America has a new 172MB drive, with units available today for your evaluation.

It's the newest member of our 5¼" disk drive family—and it's based on the same proven technologies. It's fully compatible with industry standards. And it gives you a significant price/performance advantage.


This drive represents a major step in the evolution of your multi-user system. And Fujitsu America has the technology, the strength and the experience to help you continue on that growth path.



ty of as many as 64k bytes of memory. In a 40-pin DIP, \$7.30 (100).

**Oki Semiconductor**, 650 N Mary Ave, Sunnyvale, CA 94086. Phone (408) 720-1900. TWX 910-338-0508.

Circle No 402

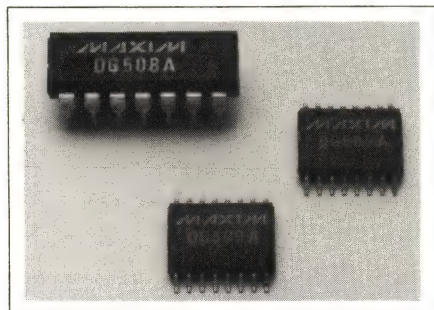

## MULTIPLEXERS

The DG508A and DG509A symmetrical analog multiplexers are 8-channel and 4-channel devices, respectively. The company guarantees these devices have break-before-make switching and that they will not latch up if the power supplies


are turned off with the input signals still connected. Improved specifications, as compared with industry-standard devices, include lower positive and negative supply currents ( $\pm 0.2$  vs  $\pm 2.4$  mA), lower drain-off and drain-on leakage currents (5 vs 20 nA max), lower source-off leakage current (1 vs 5 nA), and a lower drain-to-source On resistance (130 vs 230 $\Omega$ ). These devices are 100% burned-in at 150°C. In a 16-pin plastic DIP, \$4.30 (100).

**Maxim Integrated Products**, 510 N Pastoria Ave, Sunnyvale, CA 94086. Phone (408) 737-7600.

Circle No 403
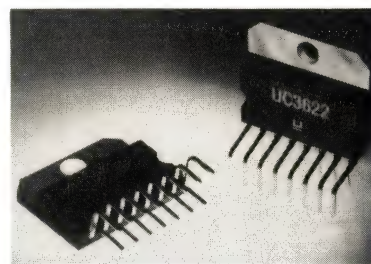
## MOTOR DRIVERS

The UC3620 and UC3622 motor-drive ICs feature decode logic that interfaces directly with TTL-compatible, Hall-effect position sensors; moreover, the devices have internal high-gain amplifiers and employ



switch-mode operation that minimizes power dissipation. The UC3620 uses fixed-off-time, current-mode control; the UC3622 has fixed-frequency, voltage-mode control. The devices are rated at 2A dc (3A pk), 40V. In a 25W, 15-lead package, \$7.40 (100). Delivery, eight weeks ARO.

**Unitrode**, 7 Continental Blvd, Merrimack, NH 03054. Phone (603) 424-2410.

Circle No 404

# this name represents built into these 5¼" drives.

So no matter what capacity 5¼" drive you need, you can be sure of its performance, reliability and delivery. We keep close control of all three by manufacturing virtually every component of our drives ourselves. And we recently opened a plant that adds 220,000 square feet to our 5¼" and 3½" manufacturing capacity.

For more information about Fujitsu's full family of 5¼" drives, call (408) 946-8777. Or write Fujitsu America, Inc., Storage Products Division, 3055 Orchard Drive, San Jose, CA 95134-2017.

When you want the best in data storage technology—and you want it now—just remember our name.

**We're developing technology for you.**

Model	M2233	M2235	M2243	M2246E
Capacity (MB) (unformatted)	13	27	86	172
Access Time (msec)	95	83	33	25
Interface	ST506/412	ST506/412	ST506/412	ESDI
Transfer Rate (KB/sec)	625	625	625	1250
Technology	Composite ferrite heads, Oxide media			



**FUJITSU AMERICA**



# NOW BUBBLE MEMORY CARRIES MORE WEIGHT

**With Intel's New Development Tool for PCs.** Hamilton/Avnet is proud to announce that the most reliable form of data storage is now even easier to use. We now offer the Intel PC-BUBBLE\* Design Kit, to show you the fastest path to bubble memory design. It features the world's highest density bubble memory (Intel's 4 Mbit 7114) and Intel's special 4-SITE\* development software.

To quickly evaluate Intel's 4 Mbit bubble memory, just install the add-on card and load the 4-SITE tutorial software into your IBM\* PC or compatible. As in all Intel design kits, complete design literature is included. After developing your prototype, leave the card in your PC to expand your mass storage!

Call the Hamilton/Avnet location nearest you and ask for kit PCB75-1 (512KB card) at just \$495 or kit PCB75-2 (1MB card) at \$945.\*\* We're also ready to deliver volume quantities of bubble memory components and boards. All good reasons for you to take a new look at bubble memory now!

\*PC-BUBBLE and 4-SITE are trademarks of Intel Corporation. IBM is a registered trademark of International Business Machines Corporation.

\*\*Limited time offer. Available on first come, first served basis.

**Hamilton**  **Avnet**  
ELECTRONICS AN AVNET COMPANY

**United States**

**1-800-521-3387**

**California**


**1-800-521-7088**

# INTEL from HAMILTON/AVNET

CIRCLE NO 222


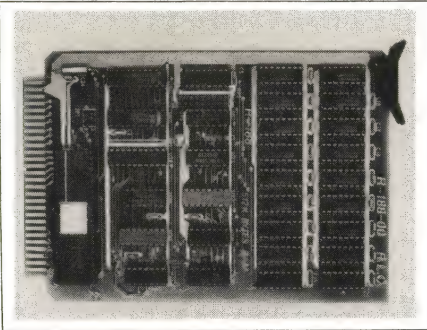
## NEW PRODUCTS: COMPUTER-SYSTEM SUBASSEMBLIES



### STD BUS CARD

The R-188, a 512k-byte dynamic-RAM card, works with 8-MHz CPUs and supports STD Bus 20-bit 8088 memory addressing. You can map the two 256k-byte blocks of memory into the 1M-byte address space on any jumper-selectable 256k-byte boundary. A RAM-controller chip performs onboard memory refresh. The card fully supports high-speed DMA to onboard memory in the byte, burst, or continuous modes. Onboard parity generation and checking will produce an inter-


rupt on detected parity errors; strap options allow nonmaskable interrupts on parity errors. LEDs indicate onboard errors for each confirmation. 256k-byte board, \$376.

**RLC Enterprises**, 1117 Hillview Dr, Milpitas, CA 95035. Phone (408) 946-7471.

Circle No 405
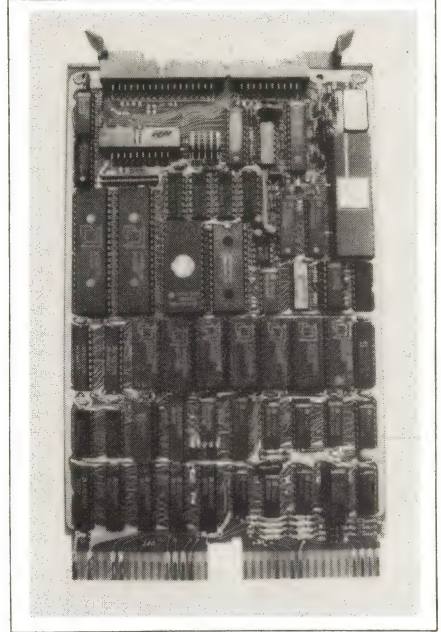
### ST506 CONTROLLER

The SDC-RQD11-B Winchester controller uses the industry-standard ST506 disk-drive interface and communicates with the host computer via DEC's mass-storage control protocol (MSCP). You can connect two ST506-compatible, 5¼-in. Winchester disk drives to each controller; as many as three controllers can operate in one system. Using DEC's MSCP, this controller runs on standard operating systems without software modification. The



device is hardware compatible with DEC's LSI-11 Series and MicroVAX I and II CPUs as well as Motorola 68000 and National 32032 Q Bus CPU designs. The module implements current Q Bus enhance-

## Around the world Ion Implantation Equipment is being powered by the new 4800 Series HV Power Supplies.

The 4800 kW system has been designed to the leading edge of HV technology, and offers hitherto unattainable standards of flexibility and stability.

It provides a controlled continuous d.c. output, with either positive or negative polarity, rated from 20 kV-200 kV as standard. Yet units are so compact, they may be hand-carried for either bench or rack mounting.

So if you need a supreme HV power supply for ion implantation or other demanding applications, get full details of the Series 4800 today! They'll make a world of difference.



**HUNTING  
HIVOLT**

**YOUR POWERFUL PARTNER**

**Hunting Hivolt**, 1008 West Ninth Avenue, King of Prussia, PA 19406, USA. Tel: (215) 265 7462. Fax: (215) 265 1982.

**Hunting Hivolt Limited**, Riverbank Works, Old Shoreham Road, Shoreham-by-Sea, West Sussex, England BN4 5FL. Tel: (0273) 454511. Telex: 87466. Facsimile: (0273) 454471.

EDN April 17, 1986



**Our international customers include:** Balzers, Switzerland; Eaton Nova, USA; UKAEA Harwell, UK; Applied Materials, USA and UK; Tecvac, UK; Whickham Engineering, UK and many more.

First European High Voltage Manufacturer to hold Defence Standard 05-21/AQAP1.

CIRCLE NO 58

301



## COMPUTER-SYSTEM SUBASSEMBLIES

ments, including 22-bit addressing and block-mode DMA transfers. Other features include 32-bit error checking and correction, bad-block replacement, transparent read retry, automatic onboard bootstrap, data buffer, and LED indicators. \$1295.


**Sigma Information Systems,**  
3401 E La Palma Ave, Anaheim, CA

92806. Phone (714) 630-6553. TLX 298607.


Circle No 406
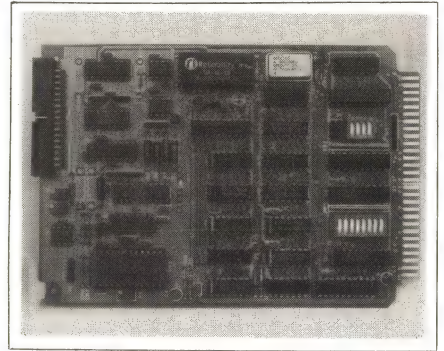
### STD A/D CONVERTERS

Models 7110 and 7120, based on National Semiconductor's ADC 1205, are available for the STD Bus. These A/D converters feature high



## The IQ-400A has the highest IQ in its class

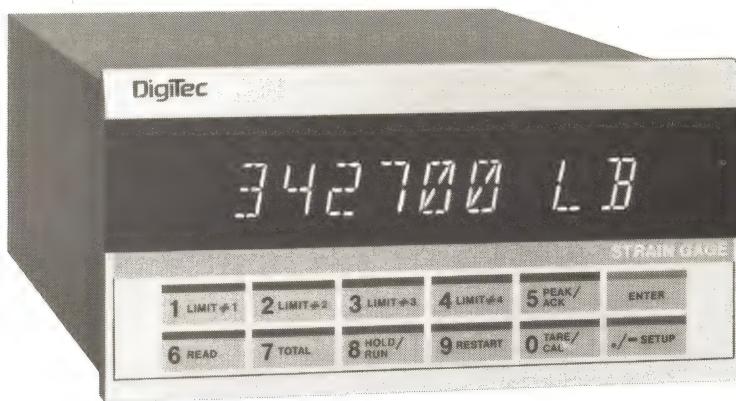

Program IQ-400A from the front panel with step by step prompts.

Low cost IQ-400A panel monitors with on-off control provide application flexibility and fully prompted front panel setup. Design them into new or replacement equipment.

#### **IQ-400A Features:**

- Four setpoints for alarm/control.
- Interfaces with Digitec printers and other equipment.
- Industrially rugged standard DIN case NEMA 12 sealed to panel.
- Display readings, minimums, maximums, averages, totals, and setpoints.
- Bright nine character alphanumeric display with user-definable labeling.
- Assured high accuracy with SelfCal™ digital autocalibration.
- Optional outputs include additional open collectors, an RS-232 serial communications port, or offset and scalable analog interface.

#### **Get Monitor/Control**

**versatility with these models:**  
**Strain Gage/Load Cell**—Select input. Program balance and span. Display peaks, totals, limits, counts, net, gross, etc. Front panel auto-tare key.  
**Thermocouple (TC) Temperature**—Select °C/°F and TC type (J, K, T, E).  
**RTD Temperature**—Select °C/°F and 3-/4-wire 100 ohm Pt RTD input.  
**Process Variable**—Easily program offset and scale. Display any process variable in any unit of measure.

**Digitec Corporation**  
918 Woodley Road, P.O. Box 458  
Dayton, Ohio 45401-0458  
Phone: 513-254-6251  
Telex: 6874219-W.U.I.


Flexibility/ Economy/ Service/ Quality



noise immunity, low power consumption, and 13-bit resolution (12 bits plus sign). Conversion time is 108  $\mu$ sec. You can configure the inputs as 16 single-ended or eight differential channels; the input voltage range is -5 to +5V. Two channels can handle 4- to 20-mA or 10- to 50-mA inputs. Gain is hardware or software selectable. Prices start at \$385.

**Cubit,** 190 S Whisman Rd, Mountain View, CA 94041. Phone (415) 962-8237.


Circle No 407

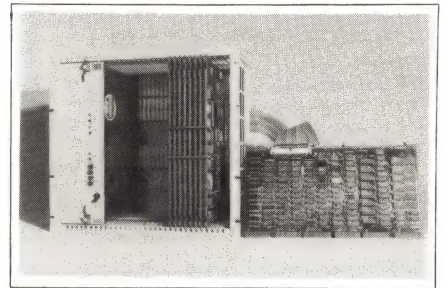
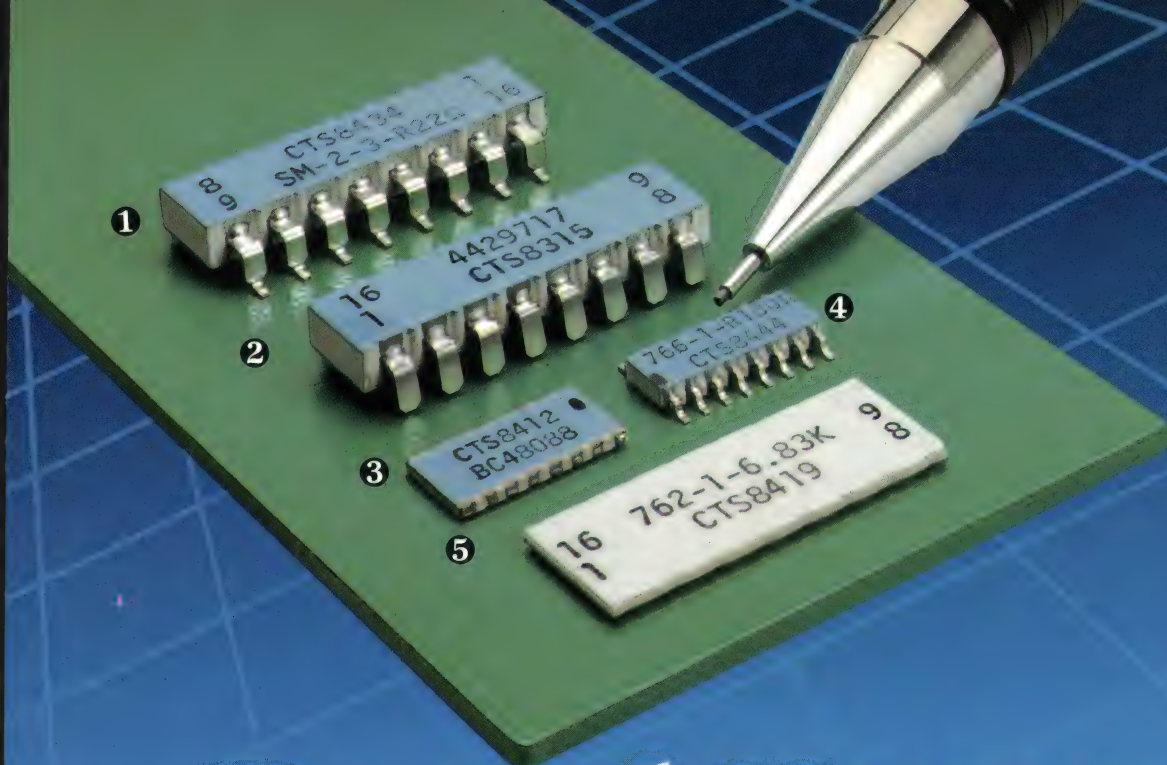
### UNIBUS RAM DISK

The N7000 semiconductor-based, disk-emulating memory specs an access time of 200  $\mu$ sec, which increases memory access in Unibus-based computers tenfold, according to the manufacturer. The memory consists of a card cage that holds 4M-byte memory boards, allowing you to increase storage from 28M to 224M bytes. Two Unibus processors can access the dual-ported memory simultaneously, and the memory can transfer data at 1M byte/sec. The memory, which emulates DEC's RK07 disk system, is compatible with all DEC operating systems that operate with the RK611 Unibus disk controller. You can add





# Board Huggers

## New! Space saving Surface Mount Resistor Networks with proven CTS reliability

These new CTS "board hugger" surface mount networks reduce board space requirements by over 50% in comparison with discrete resistors. In addition, your total installed costs are greatly reduced by eliminating discrete inventory costs as well as labor costs in attaching discretes to PC boards.

Reliability? CTS resistor network reliability has set industry standards for decades! Our network reliability is backed by 148,000 element years of continuous life testing—unmatched anywhere. These new surface mount networks meet the same exacting quality standards you've come to expect from CTS.

### BOARD HUGGER RESISTOR PACS shown on board above.

- ① **Gull-Wing Series 760**  
Available with 8, 14, 16 or 18 leads.
- ② **Stub Lead Series 760**  
Available with 8, 14, 16 or 18 leads.
- ③ **Leadless Series 765**  
Available with 8, 14, 16 or 18 solder pads.
- ④ **Small Outline Series 766**  
Available with 14 or 16 leads.
- ⑤ **Leadless Series 762**  
Available with 8, 14, 16 or 18 solder pads.

Packaging: Tube or bulk with optional reel packages where applicable.

**WRITE TODAY** for Test Report and detailed specifications on the new CTS "board hugger" Surface Mount Resistor Networks. Contact: CTS Corporation, 406 Parr Road, Berne, IN 46711. Phone: (219) 589-8220.

**CIRCLE NO 10**

### Engineer's Experimentation Kit for CTS Surface Mount Resistor Networks

Develop your own surface mount resistor network circuits with this handy CTS Board Hugger Kit. You get 5 samples of each resistor pac shown here—total 25 units in random values. *Introductory Offer—Only \$59.95.* Send check, money order, or purchase order to:

**CTS Corporation**, Berne Division  
406 Parr Road, Berne, IN 46711

EDN041786

Name \_\_\_\_\_

Company \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_



# CTS® MEANS RELIABILITY


CTS CORPORATION • ELKHART, INDIANA



**Series 207—Surface mount,**  
process compatible  
AUTO-DIP™ Switches  
Phone: (805) 238-0350  
**CIRCLE NO 49**



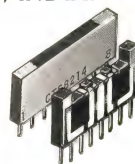**Series SMXO-55 Surface mount**  
hybrid clock oscillator  
Phone: (815) 786-8411  
**CIRCLE NO 88**



**Series 750 R/C Machine**  
insertable Resistor/Capacitor  
SIP networks  
Phone: (219) 589-8220  
**CIRCLE NO 127**



**Series CCXO-140 Leadless**  
chip carrier crystal oscillator  
for surface mounting  
Phone: (815) 786-8411  
**CIRCLE NO 166**





Need switches  
that look as good  
to purchasing  
agents as they  
do to design  
engineers?

Just ask us!

Unimax switches deliver the appearance, performance and price that make everyone look good. Out front, that quality is easy to see. Handsome chrome bezels and a range of lens colors, sizes and shapes deliver the good looks your customers want. And there's even more quality behind the panel.

Like switches designed for maximum versatility and fast delivery. Modular LPB's and keylocks with interchangeable prewirable switch elements that reduce inventory requirements and speed installation.

Switches that convert from alternate to momentary at the flick of a lever. Models with minimum behind-panel depth to solve any space problems. Multi-position, interlock and key-operated oil-tight models.

For a free sample that matches your needs, send us your specs and a description of your application on your letterhead. Or call for the location of your nearest distributor or sales representative.

To discover why Unimax should be your complete source for switches, just ask us!

**Unimax**  **Switch**

Ives Road, Wallingford, CT 06492. (203) 269-8701.




## COMPUTER-SYSTEM SUBASSEMBLIES

battery backup. Including a 1-year warranty, a 28M-byte version costs \$39,500.

**Nissho Electronics (USA) Corp.**, Inwood Park, Suite 200, 17310 Red Hill Ave, Irvine, CA 92714. Phone (714) 261-8811.

Circle No 408

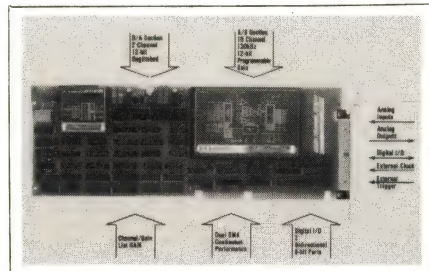

### DATA ACQUISITION

The DT2821-F data-acquisition board for the IBM PC/AT samples 16 single-ended or eight differential analog inputs at 130 kHz and specs 12-bit resolution. In addition, two 12-bit D/A-converter channels provide analog outputs at a 130-kHz throughput rate. For digital I/O, the board includes 16 I/O lines. The board supports five levels of interrupts and DMA transactions for communications with the PC/AT. You specify the sampled channels and the order of sampling in the board's channel-gain-list RAM. You can use a library of subroutines in the manufacturer's Atlab software package to write your applications software. DT2821-F, \$1595; Atlab package, \$449.

**Data Translation Inc.**, 100 Locke Dr, Marlboro, MA 01752. Phone (617) 481-3700. TLX 951646.

Circle No 409

### PC D/A CONVERTER


The PCI20021M-1 instrumentation module fits into the manufacturer's carrier boards, which plug into the IBM PC, PC/XT, or PC/AT. It provides eight channels of 12-bit D/A conversion, 1/2-LSB linearity, and 500-μsec settling time. Onboard RAM holds eight voltage values that a D/A converter consecutively



converts and stores in an S/H amplifier in one of the channels. The D/A converter refreshes data automatically. In addition, you can use on-board memory to store data setups. \$495.

**Burr-Brown Corp.**, Box 11400, Tucson, AZ 85734. Phone (602) 746-1111. TLX 666491.

Circle No 410

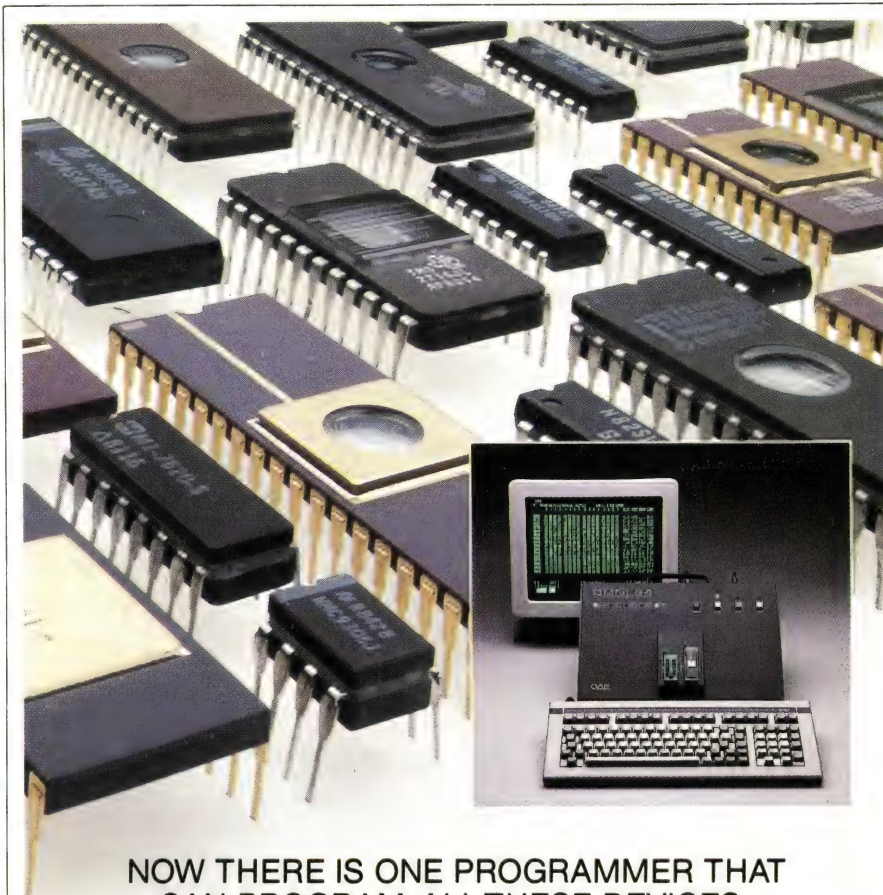

### NOW THERE IS ONE PROGRAMMER THAT CAN PROGRAM ALL THESE DEVICES.

The software configured OMNI 64. From little 8 pin MOS memories with serial I/O like the NMC9306 to the new 40 pin 16 bit wide one megabit EPROMs. From ECL PALs\* to single chip CMOS microprocessors. Because the only programmer with patented 80V, 10 amp bipolar pin drivers at every pin is the OMNI 64. Pin drivers with over 4000 steps of voltage resolution, current resolution down to 20uA per step, and timing resolution of 1 nanosecond per step. The result... There are no known devices

which these pin drivers cannot program.

But OAE doesn't just sell super programmers, we sell solutions. And the real solution to the exponential growth of the programmable semiconductor market includes direct access by modem to the largest data base of test and programming algorithms available today. A data base of over 1000 parts that is growing at the rate of more than 1 new device **per day**. And the icing on the cake... Every OMNI owner now has free access to this

data base for two years!

Victor Hugo once said that there is nothing so powerful as an idea whose time has come. Call today for more information on an idea whose time has come.

\*PAL is a registered trade mark of Monolithic Memories.

**OAE**

**Oliver Advanced Engineering, Inc.**  
676 West Wilson Avenue  
Glendale, CA 91203  
(818) 240-0080  
Telex: 194773  
Cable: OAEINC



# Our special designs... for your special designs.



## Special Pots from Spectrol

For more than 30 years, designers with application problems have turned to Spectrol for special pot solutions. They have come to us for • cermet, conductive plastic, and wirewound pots • linears and non-linears • special torque devices • concentric shafts • spring returns • linear motions • pot/switch combinations • element sectors • 1000°F pots • motion and position sensors.

So for help with your tough applications, come to Spectrol. Let us design a "Problem Solver" for you.



UNITED STATES • Spectrol Electronics, P.O. Box 1220, City of Industry, CA 91749, U.S.A. (818) 964-6565 • TWX (910) 584-1314


UNITED KINGDOM • Spectrol Reliance Ltd., Drakes Way, Swindon, Wiltshire, England • Swindon 21351 • TELEX: 44692

ITALY • SP Elettronica SpA, Via Monti, 23, 20016 Pero (Milan) Italy • (02) 35 30 241 • TELEX: 330091

GERMANY • Sales Office, Spectrol Electronics GmbH, Oberauerstrasse 15, 8000 Munich 70 West German (089) 7145096 • TELEX: 05-213014

CIRCLE NO 224



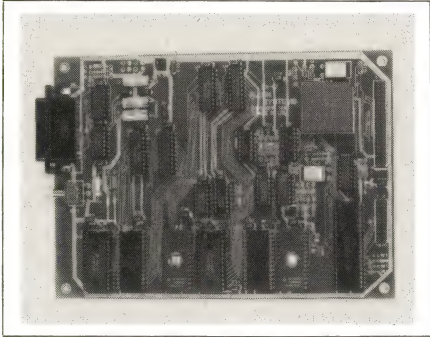


## SINGLE-BOARD $\mu$ C

The FX-97 single-board computer connects directly to a terminal and power supply so you can use it as a stand-alone system. The board includes two serial ports, eight analog inputs with 10-bit resolution, 32 parallel I/O lines, five counters, and 48k bytes of RAM, EPROM, or EEPROM. The 16-bit processor runs at 12 MHz. Available with the FX-97 is a system monitor to simplify program testing and debugging. The monitor lets you download software from a host computer. A resident interpretive Basic package is also available for writing programs without a host computer. The board measures 5.75x8 in. Assembled and tested, \$425; bare board, \$75.

**Allen Systems**, 2151 Fairfax Rd, Columbus, OH 43221. Phone (614) 488-7122.

Circle No 411

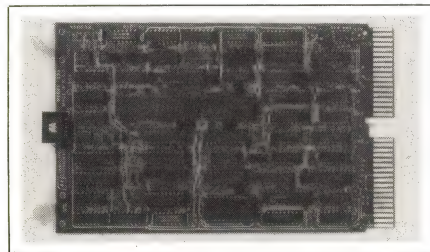

## SYSTEMS BOARD

The Model 305 multifunction systems board includes a DLV-equivalent console-interface port, a software-programmable watchdog timer, and time clock. Diagnostic bootstrap PROMs for such I/O and storage devices as DECnet, RK06, RL01/RL02, TU58, RX01, and RX02 are optional. The device also includes 4-level interrupt pro-

cessing and 22-bit addressing. Compatible with the DEC Q Bus micro-computer series, it comes on a dual-height board that measures 8.9x5.2 in. \$450.

**Computer Products**, Grant Technology Div, 11 Summer St, Chelmsford, MA 01824. Phone (617) 256-8881.

Circle No 412

## TAPE COUPLER

The DQ142 tape coupler connects 1/2-in. tape drives to DEC LSI-11 and Micro PDP-11 computers. It has a 4k-byte FIFO buffer and can switch-select DMA burst size to either two or four words. Users can attach virtually any 9-track, 1/2-in. magnetic tape drive to an LSI-11 system, and they can configure as



For over 25 years Arnold Magnetics has been building high reliability power supplies...it's been our specialty. Over the years our units have proven themselves in thousands of tough military/government and demanding industrial applications. They've been exceptional...and they keep getting better!

Our innovative pre-designed module concept offers many advantages:

- Predictable reliability that reduces the failure risk of custom circuits or package designs.
- Tailored "custom" units in 8 to 12 weeks without NRE charges.
- Choice of 1 to 8 DC outputs with AC or DC inputs.
- Performance to MIL-STD-810C, MIL-E-5400 and MIL-E-16400 specifications.
- High density (5.33 watts/cubic inch) encapsulated packages that are 50% to 75% smaller than other switching power supplies.



Send for our "Design-Your-Own" High Reliability Power Supply Catalog today. Better yet, call us toll free 1-800-421-8181 (in California 213/390-3537) and ask for it!



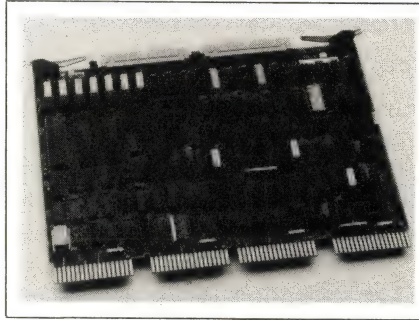
## ARNOLD MAGNETICS CORPORATION

11520 W. Jefferson Blvd., Culver City, CA 90230  
(213) 390-3537 • (213) 390-8837 • TWX 910-343-6486



many as four tape drives per coupler. The tape coupler can connect to 800-bpi NRZ drives, 1600-bpi phase-encoded drives, and 6250-bpi group-code-recording (GCR) drives, as well as dual-density (1600/3200 bpi) and tridensity (800/1600/3200 bpi) drives. A 2901 bipolar  $\mu$ P implements controller functions, and an automatic self-test



feature initiates onboard diagnostics at power-up. Operating over ambient temperatures between 50 and 140°F and humidity ranging from 10 to 90%, the quad-sized tape coupler draws 4A at 5V from the CPU power supply. It provides TS-11/TSV05 subsystem compatibility using DEC operating systems, including RT-11, RSX11M, and RSTS. \$1260 (OEM qty).

**Distributed Logic Corp.**, Box 6270, Anaheim, CA 92806. Phone (714) 937-5700. TLX 6836051.



Circle No 413
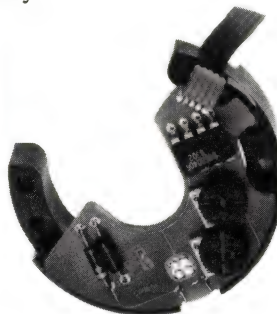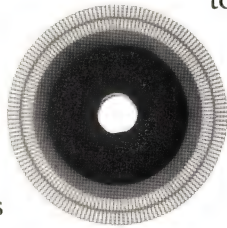
## Great Quality Greater Economy



Don't sacrifice quality for price. The V90 Series modular optical encoder provides lasting performance, and it's low priced. Easy to install on motor shafts, these Honeywell units include a high stability polycarbonate photohead complete with a custom square-wave output comparator chip. With its resolution from 200-1200 ppm, its many uses include—

streamer tape drive, velocity feed back, dot matrix print-head position, x-y positioning tables, plotter pen position drives. If size is a problem, try Honeywell's 1.5" V70 Series. Both are available immediately in low priced OEM quantities. Call today!



**SINGLE EVALUATION UNIT  
AT \$19.95 TO QUALIFIED  
O.E.M. CUSTOMERS  
CONTACT THE FACTORY  
FOR DETAILS OF OFFER!!**


### V90 Series

# Honeywell

Disc Instruments Subsidiary

102 East Baker Street, Costa Mesa, CA 92626  
714-979-5300 • TWX (910) 595-1987 DISC CSMA

CIRCLE NO 63

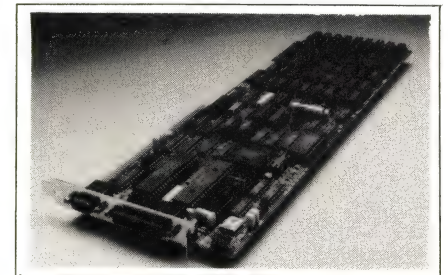

### PC/AT BOARDS

The Persyst Mono Combo/AT and Persyst Color Combo/AT boards supply I/O ports, memory, and a display adapter to the IBM PC/AT. The Mono Combo/AT module includes a parallel port, an asynchronous serial port, 128k to 1.5M bytes of memory, and a monochrome-display adapter. The adapter drives IBM's monochrome screen and is software compatible with IBM's Monochrome Display Adapter, according to the manufacturer. The Color Combo/AT module offers the same parallel port, serial port, and memory as the Mono Combo/AT but has a color-graphics-display adapter instead of monochrome. The color-graphics-display adapter is fully compatible with the IBM Color/Graphics Adapter. You can assign all of the 1.5M bytes of memory to the PC/AT's extended (more than 1M-byte) memory, or you can split the assignment between the extended and base (256k to 640k bytes) memory. This choice makes the Combo/ATs suitable for DOS applications, which use base memo-



**POWER  
GENERAL**

# Delivery

**DELIVERY.** Hundreds of reliable off-the-shelf standard products or a fast, experienced, response to your special/custom requirement. Advanced, yet economical products backed by a standard two (2) year warranty.

**SWITCHING POWER SUPPLIES** — The world's smallest, 1 to 5 outputs over a range of 25 to 200W. Features include UL, CSA, and VDE approval, input line filters, selectable inputs, and high efficiency operation.

**DC-DC CONVERTERS** — A full line of encapsulated and open board power converters featuring 1 to 60W, single, dual or triple outputs, high input/output isolation, 2:1 input voltage range, high efficiency, and remote on/off.

**UNINTERRUPTIBLE POWER SYSTEMS** — 200W and 420W models provide reliable back-up power to computer based equipment in the event of power failure. Features include 1.5mS transfer time, audible/visual alarms, internal battery and desk-top styling.

Product and performance, Power General delivers the total solution to your power requirements. Products that fit your needs.

For complete technical data contact your nearest **POWER GENERAL** sales office or call our Instant Literature Line:

617-828-6216 Ext 322

AL 205-539-8476	MA 800-336-3747	OK 214-437-4839
AZ 602-994-5153	MA 617-449-7400	OK 713-462-1432
CA 714-998-8200	ME 313-591-6112	OR 503-635-3540
CA 800-874-3821	MN 612-888-7011	PA 215-631-1414
CA 408-358-3861	MS 919-722-9445	PA 614-761-3177
CO 303-799-6063	MO 314-839-0800	RI 617-449-7400
CT 203-248-4380	MT 206-353-1833	SC 919-722-9445
DE 800-336-3747	NE 314-839-0800	SD 612-888-7011
FL 305-724-1027	NV 702-329-9440	TN 919-722-9445
FL 305-587-7146	NH 617-449-7400	TX 214-437-4833
FL 813-923-2804	NJ 201-340-1515	TX 713-462-1432
GA 919-722-9445	NM 602-994-5153	TX 512-459-0802
ID 206-353-1833	NY 315-662-7996	UT 801-546-4029
IL 312-991-2144	NY 518-274-4758	VT 617-449-7400
IN 614-761-3177	NY 607-756-6592	VA 703-478-2480
IA 319-365-8071	NY 716-223-1030	VA 800-239-8486
KS 816-229-4007	NC 919-722-9445	WA 206-353-1833
KY 614-761-3177	ND 612-888-7011	WV 614-761-3177
ME 617-449-7400	OH 614-761-3177	WI 312-991-2144

**POWER  
GENERAL**  
A SUBSIDIARY OF UNITRODE CORPORATION





# Elfab Introduces: The Four Row Box Pac.<sup>TM</sup>

## High Density Interconnection at its best.



FEMALE CONNECTOR

MALE CONNECTOR

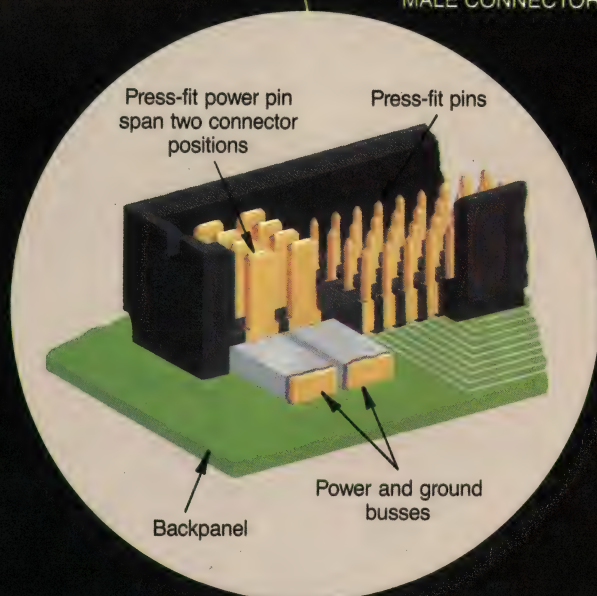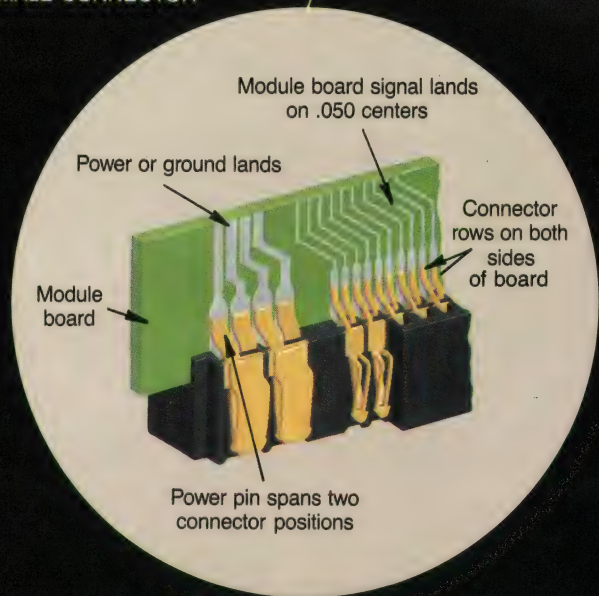

- High density interconnect system with 4 rows on .100" grid.
- Shortest conductor path between module board and backpanel, with consistency of distance between all four rows
- Optional power and ground busses
- Optional Keying
- Low insertion force
- Male press-fit design or solder tail
- Early mate power pins
- Female surface mount adapts to either vapor phase or reflow soldering

For a free brochure write to:  
Elfab Corporation  
1097 Yates  
Lewisville, Texas 75067  
214/221-8776  
or call toll free:  
1-800-527-0753

In Europe:  
Elfab Europe, B.V.  
Raheen Industrial Estates  
Limerick, Ireland  
(061)-27600 Telex: 70150






## COMPUTER-SYSTEM SUBASSEMBLIES

ry, and for operating systems that use the extended memory (eg, Xenix). Either board, including 128k bytes of RAM, \$595.

**Emulex Corp**, Box 6725, Costa Mesa, CA 92626. Phone (800) 368-5393; in CA, (714) 662-5600.

Circle No 414

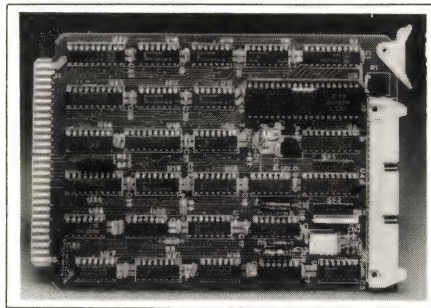

### STD BUS CONTROLLER

The FLP-380 floppy-disk-controller card for the STD Bus can control 6.6M-byte, 5¼-in.; 1M-byte, 3½-in.; and 8-in. floppy-disk drives. The controller is available in a CMOS


version for low-power applications. With read, write, and format functions that are software configurable, you can mix and match drive types and formats within the same system. Using a DMA circuit, this controller can interface to a Z80 CPU with clock speeds greater than 8 MHz. It can accommodate single- or double-sided drives, and single- or double-density operation. Software support includes the BIOS for CPM 2.2 and MP/M. \$232 (OEM qty).

**Computer Dynamics Inc**, 105 S Main St, Greer, SC 29651. Phone (803) 877-7471.

Circle No 415
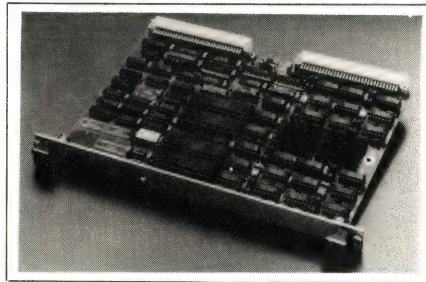
### SERIAL CONTROLLER

The V/SIO 3208 is a serial communications controller with eight independent, full-duplex RS-232C channels on a single VME Bus board. Four software-programmable inter-





rupts for each of the eight channels help to increase the throughput rate. The unit offers programmable baud rates from 50 to 19.2k bps; modem control; asynchronous, synchronous, and SDLC bit-synchronous modes; local loop-back; and auto-echo modes. It also provides 32- or 24-bit addressing. Two RS-232C ports, on individual headers on the card front and on the P2 standard DIN connector on the back, are provided. \$795.

**Interphase Corp**, 2925 Merrell Rd, Dallas, TX 75229. Phone (214) 350-9000. TLX 732561.

Circle No 416
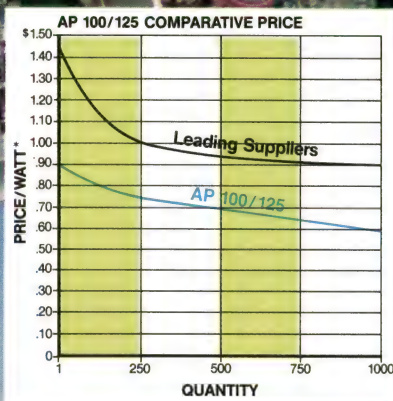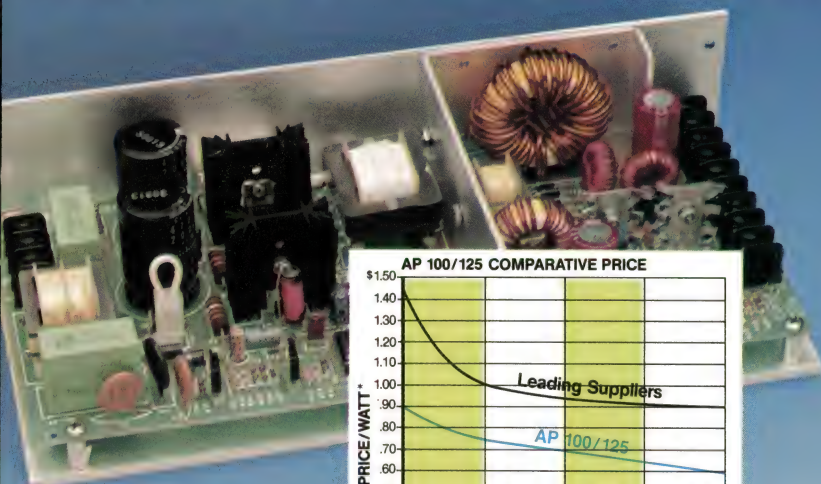
# First, we gave you 80% power supply efficiency. Now, it's lower cost per watt.



The new AP 100 and 125 Switching Power Supplies are at least 25% lower in cost than competitive units on the market. Plus they have the same high efficiency we introduced with the AP 8151. Small quantity buyers get this same pricing advantage and unit costs continue to decline with larger volumes.

All AP switchers have over-voltage and short-circuit protection and meet the safety standards of UL, CSA, VDE, and IEC. They also satisfy FCC and VDE requirements for conductive and radiated noise without the need of additional shielding or filtering.

Advanced Power offers you American design engineering and technical support plus an extremely advanced automated offshore manufacturing facility. Compare our performance, reliability and cost. You're in for a surprise—and there's more to come.



**ADVANCED POWER CORP.**

10440 N. Tantau Avenue, Cupertino, CA 95014. (408) 255-9955.

\* Subject to change without notice.



# TECHNOLOGY PLUS ECONOMY

FOR DISPLAY MONITOR AND POWER SUPPLY VALUE, NO ONE ADDS UP TO IKEGAMI

Ikegami's full line of display monitors are engineered for high performance and high value, while our impressive list of features score high marks with computer people, industry-users, lab technicians and R&D personnel. These features include:

- ☐ 1280 x 1024 pixels with greater than 100mHz of video frequency response.
- ☐ Horizontal deflection frequencies available from 15 to 64kHz on monitors with medium to ultra high resolution.
- ☐ A variety of sizes from 9" to 26", analog and TTL, monochrome and color.
- ☐ Both precision in-line gun and delta gun configurations.
- ☐ Neatly packaged for ease of maintenance, with or without an enclosure.
- ☐ Exceeds safety and emissions requirements: UL, CSA, FCC, IEC and VDE
- ☐ Precise geometry, superior linearity and color stability assure reliable and repeatable images.

Ikegami's power supplies also combine technology and economy, and the following superior features:

- ☐ Designed for a variety of applications, including computer and communications systems.
- ☐ Output ratings from 120 to 1000 watts with 4 or 5 user specified power outputs.
- ☐ Dual range AC inputs, user selectable for worldwide system applications.
- ☐ Meet international EMI and safety requirements: FCC, UL, CSA, IEC and VDE Standards
- ☐ 100% tested and burned-in to insure quality.
- ☐ Soft start with overload and overvoltage protection standard.
- ☐ Offered in both open frame and enclosed designs.

Together, or alone, when you consider great technology, at economical prices, the name to watch is Ikegami.



## Ikegami®

Ikegami Electronics (USA), Inc. 37 Brook Avenue Maywood, NJ 07607

Northeast: (617) 579-4992 East: (201) 368-9171 Northwest: (415) 449-1794 Southwest: (213) 534-0050

CIRCLE NO 227





STYLETTE™... latest in McGill's new generation of switches. With softer lines that enhance your product's styling. Backed by McGill's proven-in-use mechanical excellence. Plus statistical quality controlled manufacturing and just-in-time delivery. Featuring miniature size (.955" x .890" x .490"), plastic snap-in bezels for fast, easy installation, 12 amp capacity standard — 15 amp available, variety of circuit arrangements and rocker colors. STYLETTE... just one more reason it

will pay you to look at McGill's array of bright designs that work as good as they look. For the free bulletin 280A, call us at (219) 465-2200 or write McGill Manufacturing Co., Inc., Electrical Division, 1002 N. Campbell Street, Valparaiso, IN 46383.

ELECTRICAL/ELECTRONICS

**McGILL**  
PRECISION BEARINGS

# STYLETTE™

gives your designs style, reliability, just-in-time delivery

Circle 8 for Literature Only


Circle 47 for Contact by Manufacturer




# Looking For Reliable LOW PROFILE Machined Sockets Or Strips?




See what Samtec has!

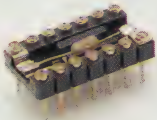


Low Profile Capacitor/IC Sockets

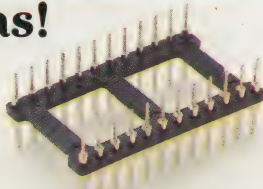


Low Profile Adaptors

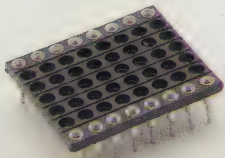


Low Profile Versatile IC Sockets

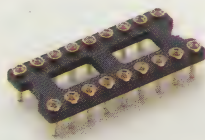


Low Profile IC Sockets

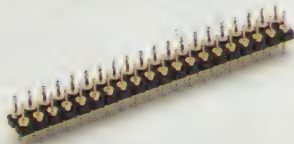


Low Profile Terminal Strips

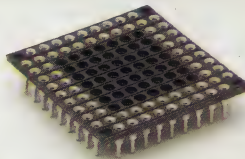

Low Profile Pin Grid Array

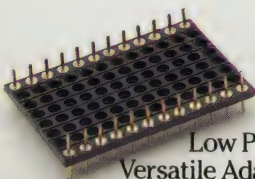

Low Profile  
Versatile Adaptors

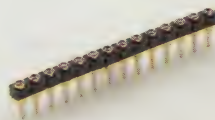

Low Profile Socket Strips

When it comes to  
**SUDDEN SERVICE**  
Samtec really *is*  
a different breed  
of cat!



**Low profile.** Today's design engineers require versatile, low profile parts to meet the requirements of high density packaging. Samtec offers a broad selection of DIPs, adaptor plugs and strips with sockets as low as .070" off the board. Custom designs on DIPs and pin grid arrays are available in low profile versions as well.

You can always rely on Samtec SUDDEN SERVICE for dependable low profile products.



**WRITE TODAY** for our new 72-page full line catalog. It has been revised and enlarged to include many new products. And it contains complete specification data for fast, easy ordering. Get yours today.

© Samtec, Inc. 1986

# samtec

## SUDDEN SERVICE

P.O. Box 1147 • 810 Progress Blvd., New Albany, IN 47150 U.S.A.  
Phone: (812) 944-6733 • TWX 810-540-4095 • TELEX 333-918

CIRCLE NO 228




software includes Grealstar for the generation of nonstandard tests, and Loadstar, which allows you to use the system in an interactive mode. Optional hardware includes a 750-VA solid-state ac source, a multichannel timing module, a module for measuring ripple and noise, and a 0 to 75V, 100W dc source. From approximately £20,000.

**Intepro Systems Ltd**, Plassey Technological Park, Castletroy, Limerick, Ireland. Phone (353) 61-332233. TLX 70110.

Circle No 421
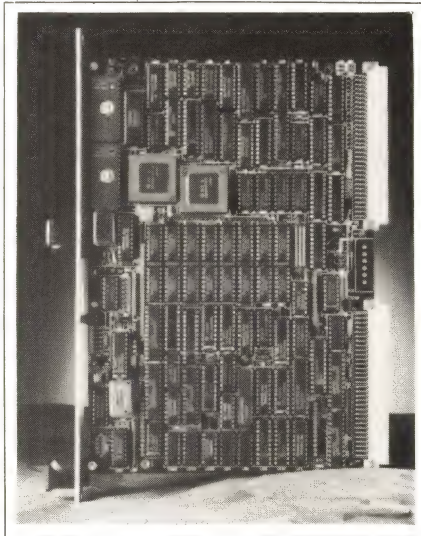
## DISK-CONTROL BOARD

The CT-68VIDC has an onboard 68000 or 68010  $\mu$ P that executes a firmware disk-caching algorithm for high-speed access to 5¼-in. disk drives on its SCSI interface. A 2- or 4-channel DMA controller allows SCSI bus data-transfer rates as high as 1.5M bytes/sec. Versions are available with either 128k or 512k




bytes of dual-ported memory, which you can expand to 2M bytes by adding a daughter board. Space is also provided for as much as 128k bytes of onboard EPROM. The board has an MMU and a VME Bus master-to-slave interface that includes a single-level bus arbiter and interrupt handler. A programmable

interval timer and self-test firmware are also included. \$2000.

**Integrated Micro Products Ltd**, Number One Industrial Estate, Medomsley Road, Consett, DH8 6TJ, UK. Phone (0207) 503481. TLX 53429.

Circle No 422

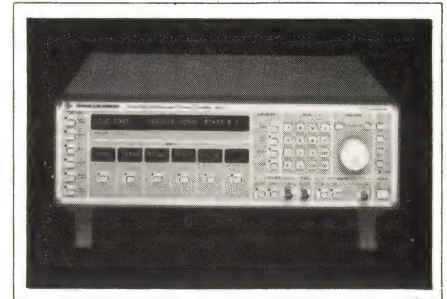

## FUNCTION GENERATOR


The AFG function generator, which incorporates a 40-digit alphanumeric display, provides a soft-key, menu-driven set-up procedure. It also has full IEEE-488 bus control. The generator produces sine, trian-

## MICROWATT COMPUTERS
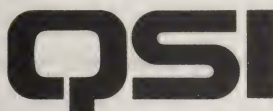
### Board-Level Microcomputers for Remote and Harsh Environments

- Ultralow Power Consumption
- -40° to 85°C Operating Temperature Range
- Unregulated 8 to 18 VDC Supply Voltage

Quartic Systems C-44 bus microcomputers feature low power consumption and ruggedness. Typical C-44 board-level systems use 50 to 200 times less power than competitive CMOS buses. Boards available include CPU, memory, analog and digital I/O, communications, data storage, and others. Under the ocean, on a mountain top, or on a factory floor, QSI's C-44 computers provide rugged, economical solutions.



Quartic Systems, Inc.  
3575 South West Temple, Suite 7  
Salt Lake City, UT 84115  
(801)268-9264 Telex: 887430

CIRCLE NO 66

## QUICK-MOUNT MODULAR ENCODERS



**OEMs.** Now you can save space, get high performance, and avoid assembly headaches with MCD's **NEW** Modular Encoders. All components are pre-aligned for fast, simple and trouble-free direct mounting on your motor shaft.

### M15

- ☐ 1/4 to 3/8" shafts
- ☐ Square wave output
- ☐ Up to 1000 PPR

### M21

- ☐ 1/4 to 5/8" shafts
- ☐ Square or sine wave
- ☐ Up to 1200 PPR

- ☐ Wire or ribbon cable terminations
- ☐ Differential line driver output option
- ☐ 18 month warranty

MCD's Quick-Mount modular encoders offer a low profile with low inertia and cost-effectiveness. No assembly and alignment problems commonly associated with kit encoders. Call or write for complete specifications today.

*New Dimensions in Motion Control*




Motion Control Devices, Inc.  
80 Stedman St., Lowell, MA 01851  
(617) 454-3407

CIRCLE NO 67



## NEW PRODUCTS: INTERNATIONAL

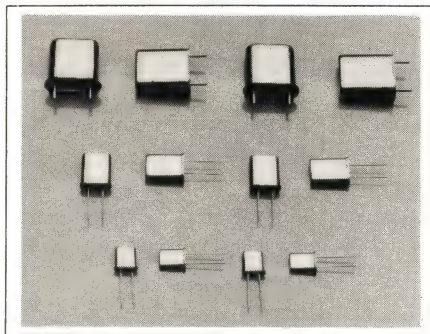

### CRYSTALS


The QCX Series crystals are available in the frequency range from 1 to 48 MHz. All of the crystals feature a frequency tolerance at 25°C of  $\pm 50$  ppm, a frequency stability of  $\pm 50$  ppm over a -20 to +70°C range, and an aging rate of 5 ppm/year. Maximum shunt capacitance equals 7 pF. Crystals with frequencies between 1 and 3.5 MHz are available in HC-33/U cases, between 2 and 48 MHz in HC-49/U cases, and between 6 and 24 MHz in UM-1 cases. £0.47 to £2.54 (1000).

**STC Components Ltd**, Quartz Crystal Unit, Edinburgh Way, Harlow, Essex CM20 2DE, UK. Phone (0279) 26811. TLX 818746.

Circle No 417

**Stantel Components**, 636 Remington Rd, Schaumburg, IL 60195. Phone (312) 490-7150.

Circle No 418

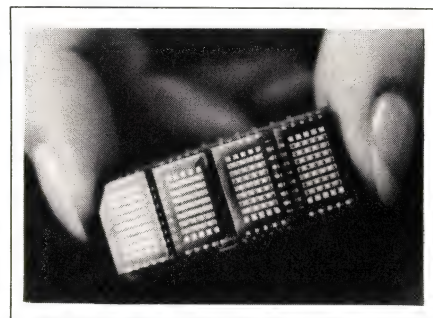

### LED DISPLAY

The PD-3435 and -3437 are orange and green versions, respectively, of a 4-digit, dot-matrix LED display. The 5x7-dot matrix has a character height of 7 mm. Integral character memory, character generator, display multiplexing, and driver circuitry allow you to display 96 char-


acters from the ASCII character set. Additional features include blinking, display testing, and programmable brightness control. PD3435, DM 107; PD3437, DM 117 (99).

**Siemens AG**, Zentralstelle für Information, Postfach 103, 8000 Munich 1, West Germany. Phone (089) 2340. TLX 5210025.

Circle No 419

**Siemens Components Inc**, 186 Wood Ave S, Iselin, NJ 08830. Phone (201) 321-3400.

Circle No 420

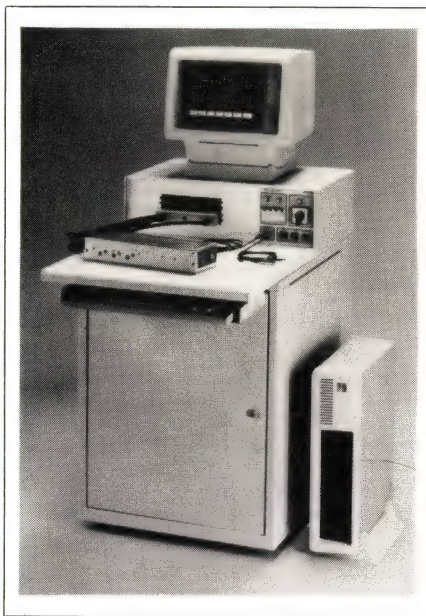


### SUPPLY TESTER

The Model 3600 includes the hardware and software necessary to test power supplies with ratings to 300W. Running on an IBM PC, the Powerstar software provides you with 38 standard power supply tests that you can set up by entering the required test limits. The system's hardware components include a 1-kVA motorized variac; four 30A/150W loads; a 5-digit DVM with rms ac current- and voltage-measurement capability; a counter/timer; a 14-channel DVM-input scanner and a 2-channel counter/timer-input scanner; and six free and configurable power relays. The unit's front panel includes test-fixture connectors and test-probe inputs. Optional

# YOUR SINGLE SOURCE
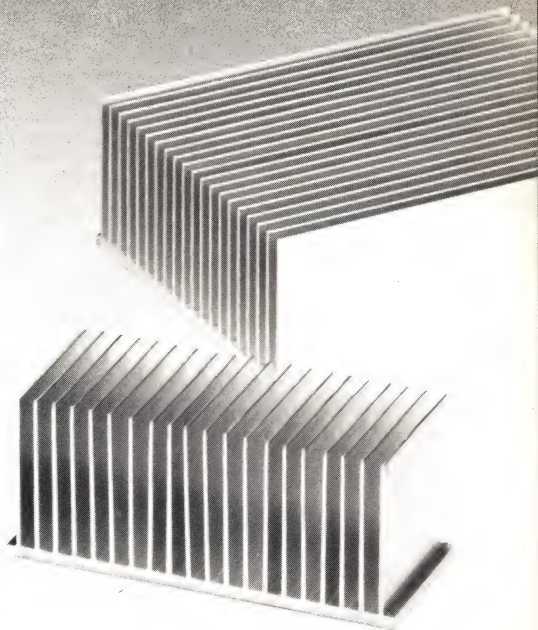
## HIGH FIN DENSITY EXTRUSIONS FOR NATURAL AND FORCED CONVECTION

- ★ These unique extrusions provide maximum cooling efficiency per unit volume
- ★ The High Fin Density family of heat sinks gives the same cooling performance as other heat sinks using nearly twice as much space
- ★ High Fin Density heat sinks provide maximum surface area and performance with relatively low weight
- ★ When used in a forced convection mode, these High Fin Density Extrusions become a cost effective alternative to mechanical fabrications
- ★ Choose from a variety of High Fin Density Extrusions to improve your cooling capabilities



For All Your Cooling Needs Call  
**EG&G Wakefield Engineering Today**  
617 245-5900

**EG&G**  
**WAKEFIELD ENGINEERING**

Components Division  
60 AUDUBON ROAD, WAKEFIELD, MA 01880  
(617) 245-5900 TWX 710-348-6713

CIRCLE NO 65




gle, and square waveforms in the 0.01-Hz to 20-MHz frequency range. It also produces trapezoidal and pulse signals. Its sine-wave harmonic ratio is >50 dB from 20 Hz to 100 kHz, and its triangular-wave linearity is <0.2% at frequencies to 1 kHz. You can set the 50Ω output level between 0 and 10V p-p and offset the output by as much as ±5V dc. In the 1 to 10V range, the output-amplitude accuracy at 10 kHz is 2%. Voltage control of the frequency is possible from an external source. In addition, you can amplitude-modulate, frequency-modulate, or pulse-modulate the output and generate an FSK output signal. You can control pulse modulation and FSK from either an internal or external source. DM 13,440.

**Rohde & Schwarz GmbH**, Mühlendorfstr 15, 8000 Munich 80, West Germany. Phone (089) 41290. TLX 523703.

Circle No 423

**Rohde & Schwarz Inc**, 13 Nevada Dr, Lake Success, NY 11042. Phone (516) 488-7300.

Circle No 424

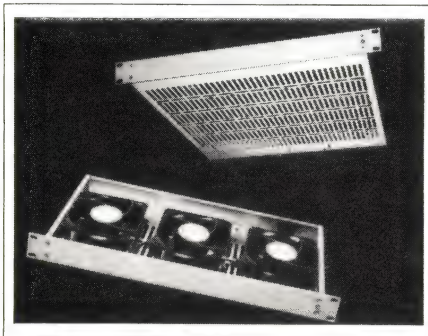

## FAN TRAY

This 1U-high fan or component tray for 19-in. rack-mounted systems comes in 208- and 460-mm-deep versions. The trays are prepunched with air vents that double as fan-mounting holes and finger guards. The 208-mm-deep version accommodates as many as three standard 120-mm<sup>2</sup> fans, and the 460-mm deep version holds as many as nine of those fans. Alternatively, you can use the trays for other assemblies,

such as pc boards or power sources. The trays are manufactured from zinc-plated steel with an anodized front panel and are supplied with a CEE22 power socket at the rear. Accessories include a filter unit and narrow slides that allow you to slide each tray in and out of the rack for maintenance. The 208-mm fan tray, including three ac fans, sells for

under £100.

**Bicc-Vero Electronics Ltd**, Flanders Rd, Hedge End, Southampton SO3 3LG, UK. Phone (04892) 81424. TLX 477984.

Circle No 425

**Bicc-Vero Electronics Inc**, 40 Lindeman Dr, Trumbull, CT 06611. Phone (203) 372-0038.

Circle No 426

# 90% Minimum Efficiency Guaranteed

## DC-DC Power Sources

**EFFICIENCY DUAL OUTPUT**

**7A/D12U12-12 LOAD REGULATION**

- Reliability Incorporated's New Z-Pac™ series of DC-DC power sources is designed to provide linear performance with switch-mode efficiencies.
- Guaranteed High Efficiency: 90% Minimum\*
- Low Noise: 1mV RMS
- 7-9 Watts, Single and Dual Outputs
- I/O Isolation: 500 VDC
- Operating Temperature: -40 to 85°C—No Derating
- Low Profile: 2" x 2" x .375"
- High Reliability

All units are 100% burned-in and tested before shipment, assuring extended reliability. Call or write for more information.

\*5v single output at 85% Minimum

**RELIABILITY INCORPORATED**  
Power Sources Division  
P.O. Box 218370  
Houston, Texas 77218  
(713) 492-0550  
TWX: 910-881-1739

**RELIABILITY EUROPE LTD.**  
22A Horseshoe Park  
Pangbourne, Berkshire  
England RG8 7JW  
0735 4947 / TLX: 846271

**RELIABILITY NEDERLAND B.V.**  
Gortlandroe Industrial Estate  
Nenagh, County Tipperary  
Republic of Ireland  
067-31897/TLX: 852-26833

"Quality is Reliability"

CIRCLE NO 68



# 2.

**Easy workability**  
Meets broad range of soldering equipments and automatic washing process thanks to

solderability of 10 sec/260 °C  
or 3.5 sec/350 °C  
and seal integrity for 10 min/75 °C  
or 20 sec/125 °C.


**MT Relay**  
For a reliable future.

For further information and address of your local sales representative please contact:  
Standard Telephone and Radio AG  
Components Division  
8027 Zurich/Switzerland  
Tel. 01 201 42 55, Telex 815 385

**ITT**

CIRCLE NO 69

## INTERNATIONAL

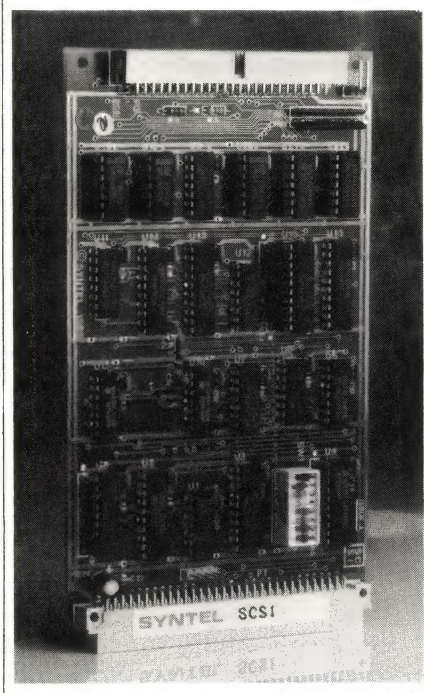

### SCSI BUS CARD

The Syn-SCSI single Eurocard board furnishes an interface for G64 Bus computer systems to SCSI bus peripherals such as hard-disk, floppy-disk, or tape drives. The board automatically acknowledges SCSI bus transfers, speeding data throughput. You can also accelerate the board's throughput by using it with a separate DMA controller. The SCSI bus interface provides only local access to one or more peripherals; it's configured as a single-ended communications option without parity or arbitration logic. £169.

Syntel Microsystems, Queens Mill Road, Huddersfield HD1 3PG, UK. Phone (0484) 535101. TLX 51194.

Circle No 427

### SEMICUSTOM SUPPLY

This semicustom supply comes on two universal pc boards and provides a range of voltage and power outputs. The primary side of the supply, an auxiliary regulation coil, and the first output winding are standard on one pc board; the other board accommodates the output op-



## DIE CAST ZINC NAMEPLATES

When "Typical" Product Identification  
Just Isn't Good Enough!

### ALSO FROM DOUGLAS

Molded Plastic Nameplates  
Graphic Overlay Panels  
Membrane Switches  
Decals  
Thermal Die Cut Emblems  
Aluminum Data Plates

No other nameplate process offers a greater opportunity for imaginative product identification. Rich electroplated raised surfaces. Contrasting baked enamels in recessed areas. Get striking variations tailored for your products alone. There's no better way to effectively prove your pride in the products you sell.  
Samples and Literature on Request.



**DOUGLAS CORPORATION**


620 12TH AVE. SO., MINNEAPOLIS, MN 55415 (612) 333-8911

WE HELP YOUR PRODUCTS STAND OUT FROM THE CROWD!

CIRCLE NO 96



# Avocet puts you in the chips!

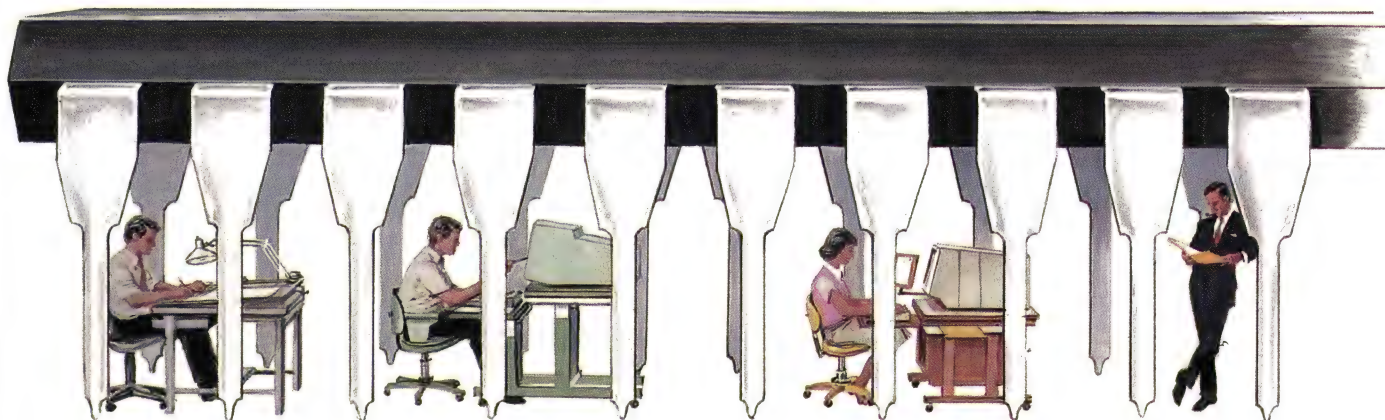

**Now you can use your PC to develop software for virtually any microprocessor. Quickly. Easily. Inexpensively.**

## THE AVOCET CROSS-ASSEMBLER FAMILY.

**AVMAC™ Macro Cross-Assembler**  
MSDOS™, PC DOS™ ..... \$349  
VAX™/UNIX™ ..... \$995

**XASM Cross-Assembler**  
CP/M™-80, CP/M-86 ..... \$249

**Target Microprocessors Supported:**

6804	6502/65C02	Z8
6805	6800/01, 6301	Z80
6809	NEC 7500	68HC11
1802/1805	8085	HD64180
8048/8041	COP400	68020
8051	F8/3870	68000/68010

**New AVMAC Macro Cross-assemblers** offer these important features: Powerful macro facility, relocatable code, linker and librarian, cross-reference by line and procedure, plain English error messages and much more.

™ Signifies manufacturer's trademark.

Avocet cross-assemblers, simulators, emulators and EPROM programmers will help put your design ideas into more chips than any other software development system on the market. You don't need a mainframe, or even a dedicated system. All you need is a PC, a good idea...and Avocet. It's as simple as that.

Avocet has been creating tools for software development since 1979 to help design engineers find easier and more productive ways to develop software for virtually any microprocessor—without

switching development systems.

Our customers turn ideas into real products. From data entry through assembly, debugging and final EPROMs, Avocet has everything you need to transform your personal computer into a fully integrated development system.

## Cross-assembler capabilities.

No matter what the application, our family of cross-assemblers runs on any computer with CP/M\* or DOS and processes assembly language for most microprocessors.

## Taking the bugs out.



Avocet's new debugging tools will eliminate "crash and burn" from your vocabulary in two ways.

First, AVSIM software simulator/debuggers allow you to test program modules on your PC. No special hardware is required for executing your target code interpretively in a crash-proof, interactive environment. AVSIM's full screen display lets you see at a glance what your program is doing.

When you're ready to test your program in a working model, Avocet's TRICE in-circuit emulators allow you to examine target memory and register, set breakpoints, single-step, trace and more. A standard serial interface lets you control emulation and download code from your PC.

And best of all, TRICE costs less than \$500.

## Progressive EPROM programming.

Avocet AVPROM programmers work with over 37 different devices including EPROMs through 27512, CMOS and E<sup>2</sup> PROMs, and MPU/EPROM combos using fast "adaptive" algorithms. These intelligent, self-contained units work with any personal computer using Avocet's GDX driver software.

## Made to order.

You don't have to come to Maine to get Avocet products (unless, of course, you want a really great lobster dinner). Just call, toll-free,

# 1-800-448-8500

(in the U.S. except Alaska and Hawaii)

and we'll rush out your order, send out more information, or, if you want, talk about some of your great ideas. Avocet Systems Inc., P.O. Box 490-N8, Rockport, Maine 04856. (207) 236-9055. Telex: 467210 AVOCET CI

**AVOCET SYSTEMS INC.™**





Full line of electrical connectors and switch components


## You'll never be in a pinch for a PGA LSI socket with JAE.

In Japan the name JAE is synonymous with connectors and quality. The industry's leader. We produce nearly every type of electrical connector. The PCPS Series of ZIF sockets for 100 mil Pin Grid Array (PGA) LSIs have pin counts ranging from 68 to 208 pins. And gold plating guarantees reliable signals. But don't overlook JAE's other IC/LSI sockets. JAE has a socket for each and every application. More state-of-the-art products from JAE.

Japan Aviation Electronics Industry, Limited's manufacturing activities span the full breadth of the electronics industry. Aerospace, Connector, Electro-optics, and Commercial/Industrial Components divisions bring you the most reliable electronic products. JAE is first an aviation electronics company. Much more than just a supplier. JAE's R & D expertise produces sophisticated aviation products including inertial navigation and automatic flight control systems. Component products range from connectors and switches to relays.
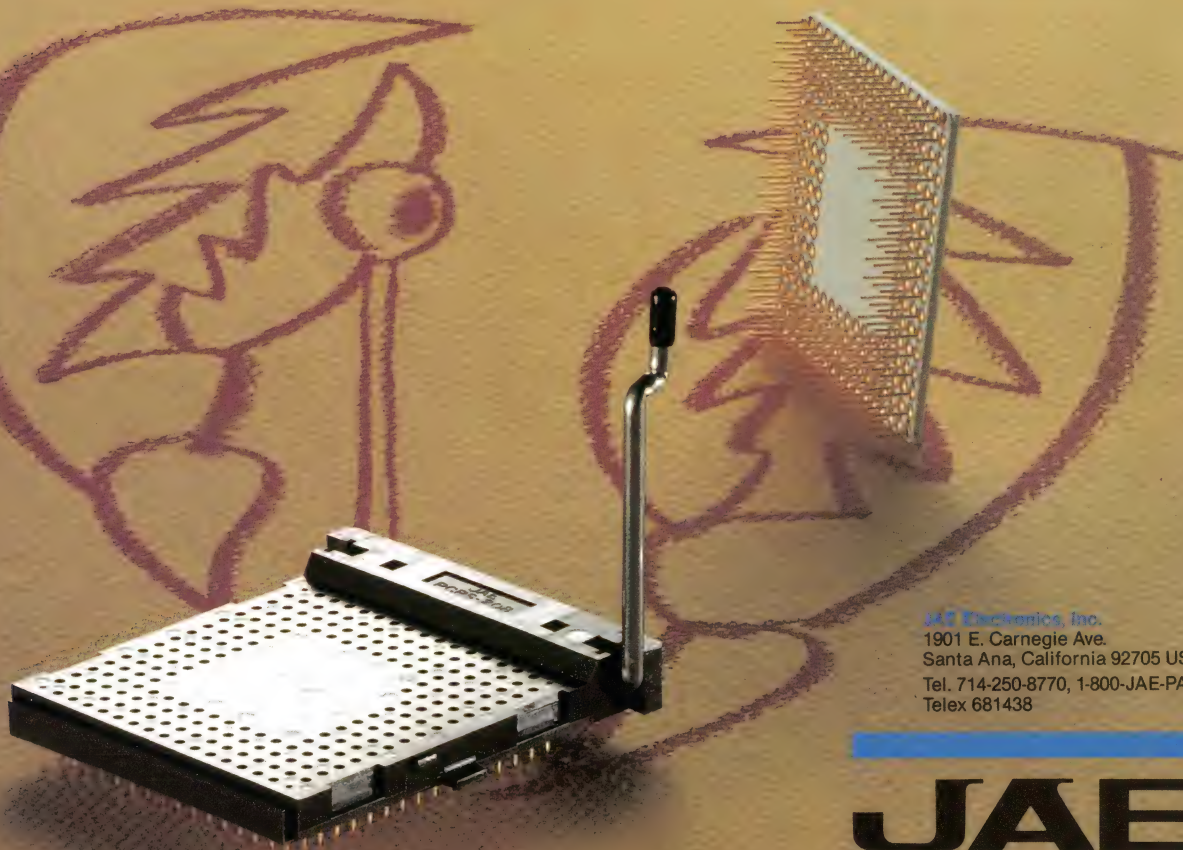
# EASY IN, EASY OUT

Whether you are looking for selection, reliability, innovation or prompt delivery. JAE. Call us today.



JAE Electronics, Inc.  
1901 E. Carnegie Ave.  
Santa Ana, California 92705 USA  
Tel. 714-250-8770, 1-800-JAE-PART  
Telex 681438

# JAE

 Japan Aviation Electronics Industry, Limited

21-6, 1-chome Dogenzaka  
Shibuya-ku, Tokyo 150, JAPAN  
Tel. 03-463-3111




tions. The supply comes in seven basic designs, including 100 to 150W, 100 to 300W, and >300W multiple-output units; 60W multiple- or single-output units; and 100 to 300W single-output units. The vendor also offers backup and standby supplies and 100 to 200W multiple-output dc/dc converters. Nonrecurring engineering costs for a typical design are around gld 15,000.

**Philips**, Electro-Acoustic Systems Div, Box 523, 5600 AM Eindhoven, The Netherlands. Phone (040) 757005. TLX 51573.

Circle No 428
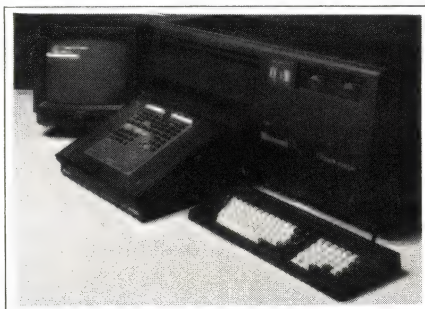
## BENCHTOP ATE

The Checkmate ATE system can perform digital tests, functional analog tests, and in-circuit tests. The modular tester, which includes a high-resolution color monitor and two 3½-in. floppy-disk drives, ac-



cepts as many as 21 analog and digital measurement or function cards. Dry-reed or mercury-wetted relay cards are provided for signal routing. You can configure the system with two or more independent sets of digital function cards to perform asynchronous testing. Six-wire guarded measurements allow you to diagnose faults at the component level. You program this system using the Climate ATE language. The unit accepts either vacuum-actuated bed-of-nails or platen-type test fixtures. £20,000 to £30,000.


**Marconi Instruments Ltd**,

Longacres, St Albans, Herts AL4 0JN, UK. Phone (0727) 59292. TLX 23350.

Circle No 429

**Marconi Instruments**, 3 Pearl Ct, Allendale, NJ 07401. Phone (201) 934-9050.

Circle No 430

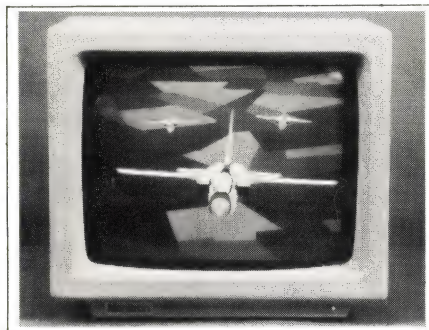

## COLOR MONITOR

Designed for high-resolution graphics applications, the CLR20 color monitor features a line-scan rate of 64 kHz and a usable resolution of



## Snap-Action Pushbuttons

Moisture and dust are sealed out with OTTO's new internal silicon rubber rolling sleeve at button; epoxy at case and terminals. Positive tactile feed-back actuation. High contact pressure patented design assures < .025  $\Omega$  contact resistance for dry circuits while offering a big 10 ampere rating. Available in a variety of bezels and contact arrangements, in MIL-S-8805 and commercial construction. Write for Catalogs P1 and P3. Call for samples.

**OTTO**  
CONTROLS

2 East Main Street, Carpentersville, Illinois 60110  
Phone: 312/428-7171 Telex: 72-2426

CIRCLE NO 72

**Honeywell, Always A Step Ahead..**

**VHSIC**

## 1.25-MICRON BIPOLAR VHSIC PROCESS TECHNOLOGY IS HERE!

Honeywell, the VHSIC Bipolar Phase 1 and 2 contractor, now offers this flexible, high density technology to the commercial market. Contact us today for complete information.

Honeywell  
Digital Product Center  
1150 E. Cheyenne Mtn. Blvd.  
Colorado Springs, CO 80906  
800-328-5111 (ext. 3404)

Together, we can find the answers.

**Honeywell**

CIRCLE NO 73



1280×1024 pixels. You can adjust the frame rate within the 50- to 120-Hz range; the monitor has a frame-blanking period of 800  $\mu$ sec and a line-blanking period of 3.7  $\mu$ sec. You can choose either an interlaced or a noninterlaced scan mode. The monitor's small-signal bandwidth is >100 MHz. You can synchronize the scan by using either

a composite synchronous input or separate TTL-compatible line and frame synchronous inputs. The monitor operates from a 190 to 265 V ac line input. £1800.

**Ficention Ltd**, Manitron Div, Bold Street, Sandbach, Cheshire CW11 9AR, UK. Phone (0270) 764171. TLX 367227.

Circle No 431

## MEMORY MODULES

The HM44256P1 and HM44257P1 are 256k×4-bit dynamic-RAM modules housed in 22-pin SIPs. The HM44256P1 has page-mode access, and the HM44257P1 has nibble-mode access. Both devices are available in 100-, 120-, or 150-nsec access-time versions. They are constructed from four dynamic RAMs, which are packaged in plastic leaded chip carriers and mounted on a fiber-glass mother board together with decoupling capacitors. The modules measure 61×11.4×5 mm and feature common I/O with early write, 256-cycle RAS-only refresh, and hidden refresh. They operate from one 5V supply. £26 (500).

**Hybrid Memory Products Ltd**, W Chirton Industrial Estate, North Shields, Tyne & Wear NE29 8SE, UK. Phone (0632) 580690. TLX 53206.

Circle No 432


## MODEM

The Tm512E autodial, autoanswer modem operates on CCITT standards V21 (300/300 bps full duplex), V23 (1200/75 bps, 75/1200 bps, and 1200/1200 bps half duplex), and Bell transmission standards. It includes the Epad (Error-Protected Packet Assembler/Disassembler) error-checking protocol for use on the Packet Switch Stream (PSS) network; the vendor claims this protocol allows for error-free data transfer to and from a terminal or computer and the packet assembler/disassembler. The Epad facility uses the Epad notes to enable transmission over the whole PSS network. The modem also features automatic baud rate, parity detection on the local terminal or computer link and on the telephone line, and automatic selection of pulse or tone dialing. £339.

**Tandata Marketing Ltd**, Albert Rd N, Malvern, Worcs WR14 2TL, UK. Phone (06845) 68421. TLX 337617.

Circle No 433
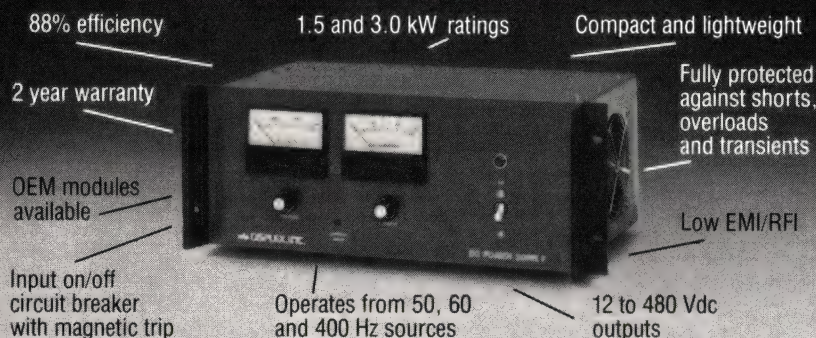
## THE NEXT TIME YOU NEED A 1.5 OR 3 KW DC REGULATED POWER SUPPLY, REMEMBER THIS AD.



Delivering 1.5 or 3kW at 12 to 480 Vdc, these units are especially designed for high-power applications where tight regulation, low-ripple and high efficiency are critical. Features include: light weight, low panel height and high MTBF. Unique modular design and circuitry permit custom modification. Available rack-mountable or as OEM modules. Single or 3-phase. Call for complete details and custom design capabilities: 516-671-4400.

### TYPICAL PERFORMANCE CHARACTERISTICS

Input voltage	117 Vrms, 220 Vrms 1-phase; 208 Vrms 3-phase
Input frequency	47 Hz to 63 Hz, 400 Hz
Output voltage	12 Vdc to 480 Vdc
Voltage adjustment range	+20%, -10% of nominal value, wider adjustment range available
Voltage regulation	< 1% line and load combined
Output current limit	Adjustable from 40% to 100% of nominal rating
Output voltage ripple	< 1% or 500 mV p-p, whichever is greater (lower ripple options available)
Transient response	Recovery time to normal range < 0.6 ms for 30% step load change
Temperature coefficient	< 0.02% per degree Centigrade
Ambient temp. (operating)	0 to 40 degrees Centigrade
EMI/RFI (conducted and radiated)	Per FCC Class A and VDE 0875 limits






**DISPLEX, INC.**

Subsidiary of North Hills Electronics  
1 Alexander Place, Glen Cove, New York 11542 (516) 671-4400. TELEX: 46-6886


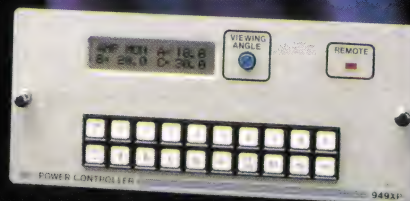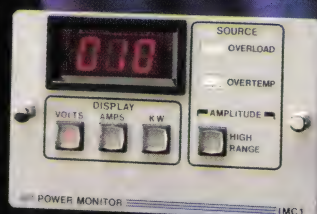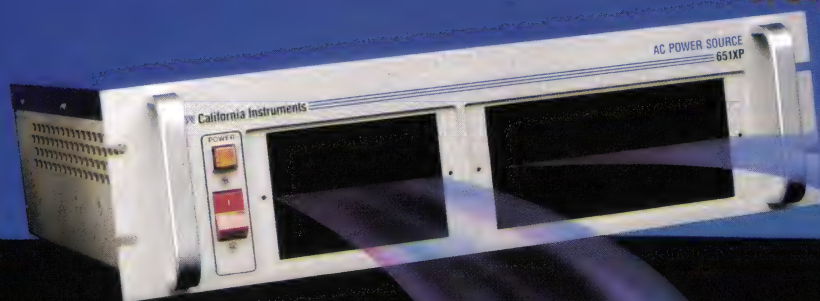
# ADVANCED PRECISION AC POWER SYSTEMS

for a Wide Range of Applications  
from Reliable Burn-In Power  
to Precision Testing



The important factors in the selection of an AC power supply: space, efficiency, safety, power bandwidth, modularity and cost have all been thoughtfully incorporated into the XP Series AC Power Systems.

The XP Series System is made up of three interchangeable components: power amplifier, power controller and power monitor.

## POWER AMPLIFIERS

Choose from four XP Series Power Amplifiers. All are compact and can be stacked in two-phase, three-phase open delta and three-phase WYE configurations.

- Wide range of VA ratings from 325VA to 1300 VA and multi-phase capability 7800VA.
- Selectable output voltage ranges 0 to 135V RMS or 0 to 270V RMS
- Full rated power from 45 Hz to 5,000 Hz and optional bandwidth to 10,000 Hz
- Guarded safe operating area
- Input and output isolation transformer
- Reduced panel height

## POWER CONTROLLERS

Five versatile power controllers cover the needs of every AC power source application. From the simplest, the 910XP which provides crystal-controlled fixed-frequency to the top of the line, the powerful 949XP which provides total control and programmability of the AC power System.


- Crystal-controlled, synthesized frequency in increments as fine as 0.1 Hz
- Talks measured voltage, current, kilowatts, power factor and error messages over IEEE-488 bus
- Non-volatile RAM stores turn-on parameters
- External sync capability
- Independent programming of phase angles and amplitudes
- Programmable current limits
- 32-character alphanumeric LCD display
- Harmonic distortion of <0.5% (948XP and 949XP <1%)

## POWER MONITORS


- Overload and overtemp indicators
- Gain pot (internal)

- Hi/Lo range switch/indicator
- 3-digit display of voltage, current and kilowatts

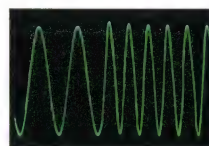With over 25 years of experience, California Instruments is unmatched in the precision AC power systems to meet stringent requirements. Get precision testing power into your applications by calling today for assistance and a complete catalog.



Programmable Frequency

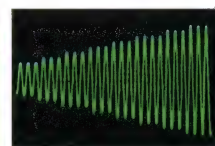

Amplitude Ramp/Step



Multi-Phase Waveform



Programmable Start-Point

An affiliate of



## California Instruments


A Division of  
Amstar Technical Products  
Company, Inc.

5125 Convoy Street  
San Diego, CA 92111

(619) 279-8620  
Telex 695047  
Call Toll Free: 800-356-2244  
In California: 800-821-1634


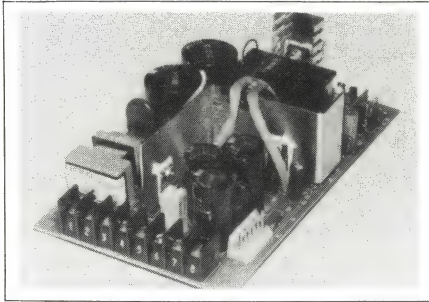
## NEW PRODUCTS: INSTRUMENTATION & POWER SOURCES




### 75W SWITCHERS

The 7S75 family of 75W open-frame switching power supplies provides regulated outputs of 5, 12, 15, or 24V dc. The supplies are recognized under UL 478, certified to CSA 22.2, and approved to VDE 0806 (IEC 380) for SELV applications. Conducted noise complies with FCC Docket 20780 level B and VDE 0871 level B. The supplies include protection against overload, short circuit, reverse polarity, and overvoltage. Output voltages are adjustable over  $\pm 5\%$ , and maximum output ripple and noise is 1% of the nominal out-

put. The supplies exhibit load and line regulation of 0.2%. The devices accept input voltages ranging from 90 to 132V ac and 180 to 264V ac (47 to 63 Hz) and measure 7.25 $\times$ 4.25 $\times$ 1.95 in. \$66 (1000). Delivery, 12 to 16 wks ARO.

**Sierracin/Power Systems**, 20500 Plummer St, Chatsworth, CA 91311. Phone (818) 998-9873.

Circle No 434

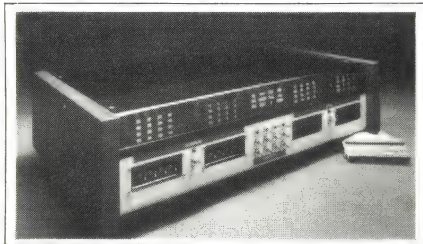

### STATIC STIMULATOR

With the CSA SSLA logic stimulator, you can manually exercise all the address, data, and control lines of your  $\mu$ P-based project. The CSA

has adapters for 68000/10/20 and 8086/186/286  $\mu$ Ps' sockets as well as the VME Bus, Multibus, and Versabus. The unit offers remote control via an RS-232C interface. The remote-control feature allows you to perform low-speed emulation. \$3850; additional adapter cables, \$180.

**Computer System Associates Inc.**, 7564 Trade St, San Diego, CA 92121. Phone (619) 566-3911. TLX 333693.

Circle No 435

### COIL CHECKER

The STT-4 detects shorted turns in coils and works with a large range of coil and wire sizes. A variety of probes are available to accommodate different coils and wire gauges. Probes from  $\frac{1}{16}$  in. in diameter for miniature sizes to  $\frac{1}{2}\times 4$  in. long are standard. You can control the go/no-go limit adjust and the volume of the

# THE SYSTEM SUPPLY



You say you want a choice of over 100 different system supplies? You want them all from one source, with OEM discounts, super-high MTBF's and nationwide service backup? Well...grab your shopping carts. Welcome to the Kik System Supply Supermarket.

#### A choice for every application.

Whether you need low noise, high current units for microprocessor systems, bipolar amps for servo control,

programmable loads for power output testing, or units for any one of hundreds of other applications, the Kik supermarket is the only source you need. And Kik backs every unit with a 30-day money back guarantee, so you can test your new Kik's at your leisure and in your own application—without risk or obligation.

#### One stop for all your system supply needs.

Down Aisle One you'll find Kik's low

noise, low ripple PAD series with .005% regulation. That's not 10 models or 20 models, but *forty five*—ranging in output from 8-1000 volts and 0.2 up to 500 amps, and a demonstrated 131,000 hours MTBF! (Incidentally, Kik is the only system supply maker to publish its MTBF's.)

If over-70% efficiency is what you need, the next Aisle has our PAL series (up to 60 amps @ 16V or 35V with .003%




## INSTRUMENTATION & POWER SOURCES

5-kHz alarm from the back panel. The device draws 30W from a 115V $\pm$ 10%, 50/60-Hz supply. \$850.

**International Electro-Magnetics Inc.**, 350 N Eric Dr, Palatine, IL 60067. Phone (312) 358-4622. TLX 726329.

Circle No 436

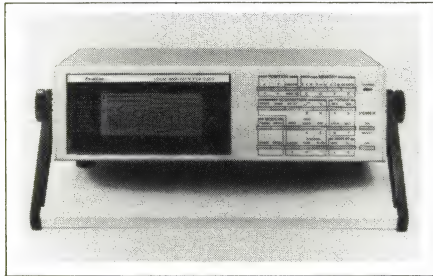

### LOGIC ANALYZER

The Primeline PLA-3300 logic analyzer performs state, timing, and signature analysis. It has an LCD readout and operates from line power without an ac adapter or from a built-in NiCd battery. The


device features a 10-MHz clock rate, 16 channels for data input with 256 bits/channel of acquisition memory, a reference memory of 256 bits/channel, 15-nsec glitch detection, and 100-nsec resolution. \$1995.

**Soltec Distribution**, Box 818, Sun Valley, CA 91353. Phone (818) 764-5400. TLX 4943094.

Circle No 437
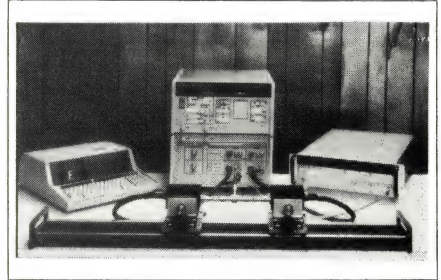
### SIGNAL GENERATOR

The VM-4B signal generator/calibrator features a 0.01- to 18.0-GHz frequency range (expandable to 40 GHz) and a dynamic range greater than 100 dB. The instrument provides dual- or single-channel operation; dual-channel measurement accuracy is  $\pm 0.02$  dB (per 10 dB, exclusive of mismatch uncertainty). You can select 0.1-, 0.01-, or 0.001-dB measurement resolution. For dual-channel phase measurements, the specs are:  $\pm 180^\circ$  range; 1.0, 0.1,



and  $0.01^\circ$  resolution; and  $\pm 2.5^\circ$  accuracy (exclusive of mismatch uncertainty). Typical measurement time for a -130-dBm signal is 18 msec. System repeatability for magnitude is  $\pm 0.015$  dB max,  $\pm 0.008$  dB typ; for phase, it's  $\pm 0.5^\circ$  max,  $\pm 0.25^\circ$  typ. Load VSWR is 1.27 at 18.0 GHz with a masking attenuator (1.15 typ); source VSWR is 1.15 at 18 GHz (less than 1.10 typ). \$74,700. Delivery, four months ARO.

**Weinschel Engineering**, 1 Weinschel Lane, Gaithersburg, MD 20877. Phone (301) 940-3434. TLX 440702.

Circle No 438

# SUPERMARKET.



line and load regulation). Yet another aisle for our new 0-10V, 0-150 amp high-efficiency PAK series designed for power burn-in and semiconductor aging—with  $3\frac{1}{2}$  digit resolution. Or keep going for our super flexible, compact PAR series with autoranging from 0-80 volts and 0-10 amps in three or four combinations, with remote or local programming, at a low, low price.

**One-stop for over a hundred different system supplies.**

And we've got aisles and aisles of more supplies.

### Next door and worldwide.

Kik is #2 worldwide in lab and system supplies sales, and #1 for breadth of line. Our supermarket-sized line lets you pick from 80 GPIB programmable system models and over fifty lab models—most of which are voltage- and current-programmable. With Kik you never

settle for a lesser unit than you require, and you never overbuy just to get the reliability and performance you need.

Give your local Kik rep a call, or send for our complete shopping list. Chances are we've got the supply you need—on the shelf and at a price that'll make you one happy shopper. 17819 S. Figueroa

**KIK**® Gardena, CA 90248  
(213) 515-6432  
(800) 421-5334

CIRCLE NO 75

© Kikusui International Corp. 1985  
Subsidiary of Kikusui Electronics Corp., Japan



# One half million more power supplies...



## now have the name no one knows.

**PACKAGED  
POWER**



**Adding Boschert makes us the Biggest Name in power supplies!**

Boschert, the leading name in open-frame switchers, will produce more than a half million units in 1986. Boschert is the newest member of the Power Conversion Group of Computer Products Inc. — the name no one knows.

Now, as the world's fastest-growing supplier of power conversion products, we have more ways than ever to meet all of your critical power supply requirements.

### **There's No Power Supply Problem We Can't Solve.**

We now combine the resources of six separate business units — Boschert (now including Compower), Power Products, Stevens-Arnold, Tecnetics, Power Products Ltd. (Ireland), and Computer Products Asia-Pacific Ltd. (Hong Kong).

Together, we can design and produce virtually any type and size power supply you will ever need, from ½ watt to 2000 watts:

- AC/DC Linears and Switchers
- DC/DC Converters
- AC/DC Uninterruptible Power Systems
- Standard, Special and Custom
- Commercial, Industrial and Mil-Spec

All have guaranteed reliability, and most are backed by our no-hassle two-year warranty. And we offer high-quality design and application assistance, plus prototype services and a host of other supports we call PACKAGED POWER.

**Contact us for our free informative booklet, "How to Get the Best Value for Your Power Supply Dollar," and literature covering our entire line of quality-built power conversion products.**



**COMPUTER  
PRODUCTS**  
POWER CONVERSION GROUP


**World leader in power supply technology.**

2900 Gateway Dr. • Pompano Beach, FL, 33069 • Phone (305) 974-5500 • TWX 510-956-3098  
Boschert Incorporated • Power Products Division • Stevens-Arnold Incorporated • Tecnetics Incorporated  
Power Products Limited (Ireland) • Computer Products Asia-Pacific Limited (Hong Kong)

CIRCLE NO 232



## INSTRUMENTATION & POWER SOURCES

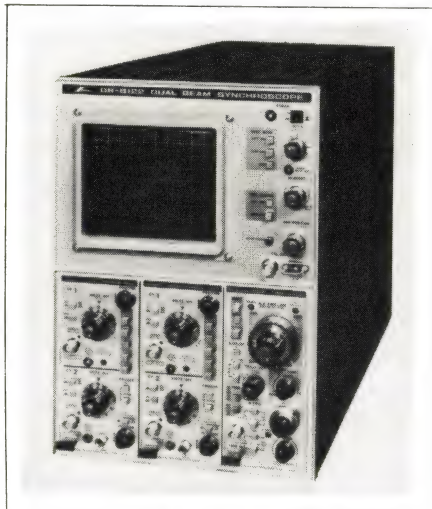

### SCOPE MAINFRAME

The DS-8122 accepts as many as three plug-in units. A 1-gun, 2-beam CRT makes it possible to observe two high-speed, single-shot events simultaneously or to observe four traces at the same time when two vertical dual-input units are plugged in. The mainframe incorporates a character generator to display the data from the plug-in units on a 6-in. CRT. Plug-ins include a dual-trace amplifier (100 MHz), differential-input amplifier (10- $\mu$ V/div sensitivity), dual timebase with delayed sweep, and a 1-GHz sampling front end. The device measures  $8\frac{3}{4} \times 12\frac{3}{8} \times 20\frac{1}{2}$  in. \$6920. Delivery, 10 to 12 weeks ARO.

**Iwatsu Instruments**, 430 Commerce Rd, Carlstadt, NJ 07072. Phone (201) 935-5220.

Circle No 439



### 29PL141 EMULATOR



The MM141 works with an IBM PC to support development of AMD's 29PL141 microcontroller. The emulator connects to the IBM PC via a flat cable. The package includes an

## CUSTOM POWER

**ONAN for a custom power supply...**from mainframes to micros, peripherals to systems, ONAN offers the exact switching power supply to fit your application.

**ONAN for quick, reliable prototypes...**Engineers using computerized workstations, modify proven circuits to meet your requirements. Zero Defect Programs and Statistical Process Control ensure consistent performance.

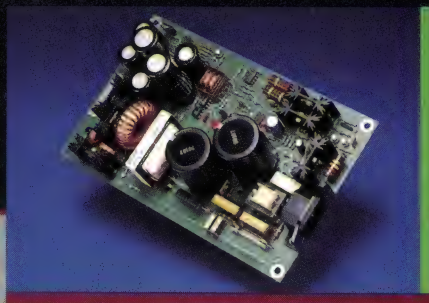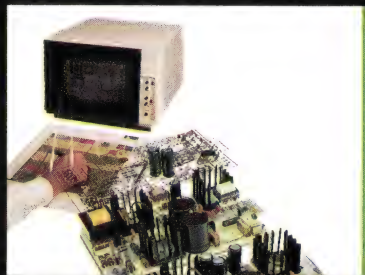**ONAN for manufacturing strength...**fifty years of power supply design and manufacturing experience—a worldwide, manufacturing capability that keeps our products cost competitive and delivered on time.



At ONAN,  
it's the  
"Power of Partnership."

**Onan**

ONAN Power/Electronics  
4801 West 81st Street  
Minneapolis, MN 55437  
612/921-5600

CIRCLE NO 76

### DYNAMIC MEMORY TIMER

- Triggered by a Single MREQ Pulse
- Rising-edge Triggered
- TTL Interfaced
- 14 Pins DIP
- Generates All Timing Pulses for DRAM Memory Board
- Precise and Stable Timing

**data delay devices, inc.**

385 Lakeview Avenue, Clifton, New Jersey 07011  
(201) 772-1106

CIRCLE NO 77



# An Invitation To Meet The IDRIS Team



## IDRIS OPERATING SYSTEM

Whitesmiths announces Version 3.0 of the IDRIS operating system. We've made IDRIS even more versatile and cost effective with new real-time features, greater UNIX compatibility, flexible packaging options, and an even higher level of customer support.

### REAL-TIME

Real-time enhancements include a high performance interprocess communications facility. Plus improved interrupt latency, context switching times, and serial I/O performance which make IDRIS faster than ever.

### STANDARDS

Our portable resident and interface libraries have been enhanced to support the 1984 /usr/group standard system calls, ensuring UNIX source code compatibility. IDRIS now supports environments, FIFO files and pipes, file locking, process groups, no delay I/O, System V style termio, curses, termcap and more.

### PACKAGING OPTIONS

- \* IDRIS DEVELOPMENT SYSTEM, for software development and general purpose computing, boasts the complete executive and all utilities, including Whitesmiths C and Pascal compilers and other sophisticated program development tools.
- \* IDRIS TARGET SYSTEM, a runtime environment for disk-based turnkey and dedicated systems, offers the complete executive and all utilities except program development tools.
- \* IDRIS DISK-BASED EXECUTIVE is the complete executive without the Whitesmiths-supported utilities.
- \* IDRIS EMBEDDED EXECUTIVE is a trimmed down executive designed for use in board-level products without a disk.

All IDRIS packages have the same open architecture. What's more, system developers can build custom device drivers and applications programs that work under all IDRIS configurations.

**RSVP**  
Whitesmiths, Ltd.  
1-800-225-1030  
97 Lowell Road, Concord, MA 01742

#### AVAILABLE NOW AT VERSION 3.0

	MC 68000	INTEL 80 x 86*	DEC VAX+
DEVELOPMENT SYSTEM	X	X	X
TARGET SYSTEM	X	X	X
DISK-BASED SYSTEM	X	X	X
EMBEDDED EXECUTIVE	X		

\* Cohabitates with DOS  
+ Cohabitates with VMS



## INSTRUMENTATION & POWER SOURCES

editor and assembler, a writable control store, a real-time emulator, and real-time trace. Given the 29PL141's fixed-instruction format, you need only fill in highlighted fields in edit mode to write programs. You enter emulator commands as single keystrokes. The error messages contain specific information about invalid entries, thus serving as an on-line help facility. Two maskable trace-point registers and a delay counter control operation of the 2k-word $\times$ 32-bit trace memory. \$4995. Delivery, 60 days ARO.

**HLA Instruments**, 5667 Snell Avenue, Suite 218, San Jose, CA 95123. Phone (408) 726-2050.

Circle No 440




### COMPONENT COOLER

The Cold Gun component cooler produces a stream of clean, cold air at  $-40^{\circ}\text{C}$  by passing compressed air through a vortex tube. The tube divides the compressed air into a hot and a cold stream, and an articulated nozzle directs the cold stream in a narrow pattern at the component under test. The cooler has no moving parts and requires no electricity or chemicals. An ordinary supply of compressed air is the only power source, and a thumb-actuated air valve permits intermittent use. The cooler eliminates the expense of Freon and the associated thermal-shock damage caused by cryogenic Freon temperatures when thermal
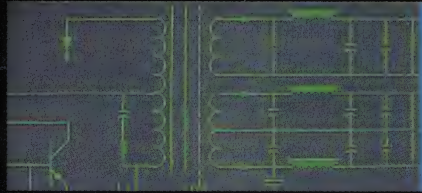
## RELIABLE POWER

**ONAN POWER SUPPLIES...** designed for your application. Our Engineers use computerized workstations to quickly turn proven circuits into prototypes for new applications.

**ONAN RELIABILITY...** from Zero Defects Programs and Statistical Process Control to conservative designs and a QA System based on Mil-Q-9858.



**ONAN TECHNOLOGY...** state-of-the-industry power, sophisticated, yet cost competitive, from MOSFET's and 100 KHz switchers, to "current-mode control." Compact, yet reliable power supplies that conform to your requirements.




At ONAN,  
it's the  
"Power of Partnership."

**Onan**

**ONAN Power/Electronics**  
4801 West 81st Street  
Minneapolis, MN 55437  
612/921-5600

CIRCLE NO 115
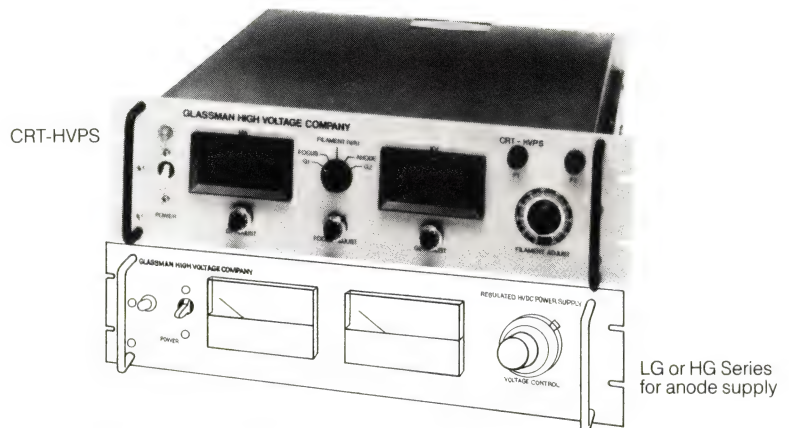
## A power supply package designed for CRT production testing and research



### The Glassman CRT-HVPS system plus anode supply

- HVPS provides G1, G2, Focus, and Filament voltages in one chassis
- Choose from 19 different Glassman anode voltage options, up to 100KV
- Economical — costs less than purchasing five separate power supplies
- Saves bench/rack space
- Saves time — no need to interface and debug separate units
- LED digital meters for accurate readings even in microampere range
- Other advanced design features include high efficiency, low stored energy, low ripple, excellent transient response and tight static regulation

*Innovations in high voltage power supply technology.*

**GLASSMAN HIGH VOLTAGE INC.**

Route #22 (East), Salem Industrial Park, P.O. Box 551, Whitehouse Station, N.J. 08889  
(201) 534-9007 • TWX 710-480-2839




CIRCLE NO 78



# WHAT IS AN INTERNATIONAL POWER SUPPLY WITHOUT AUTOMATIC VOLTAGE COMPENSATION?

## NOT QUITE WHAT IT SHOULD BE

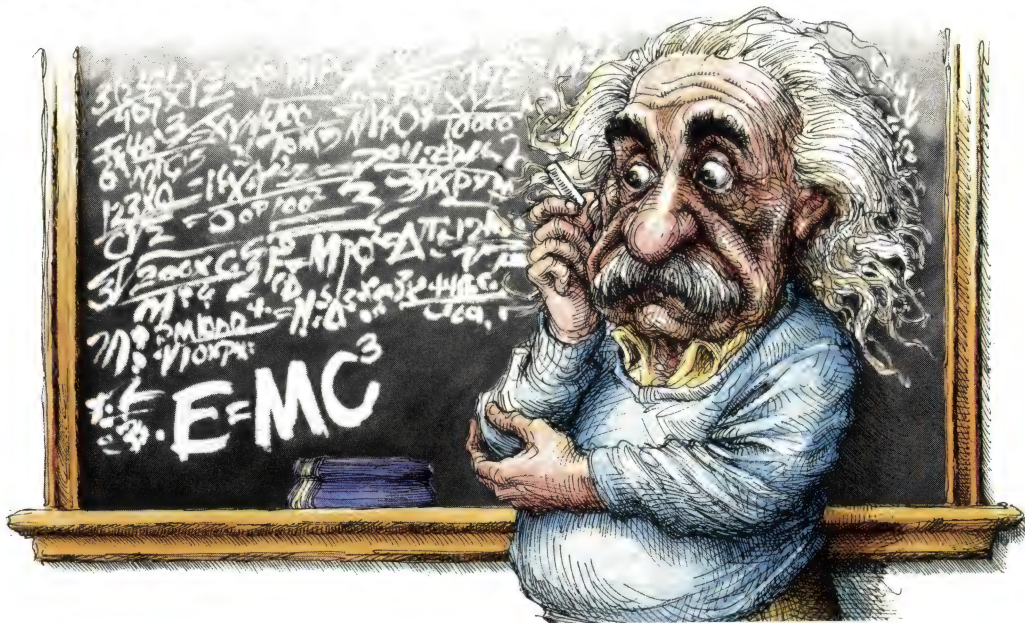

International safety and EMI standards are design benchmarks for certain power supply market segments. Most switcher OEM's that sell in international markets conform to VDE and IEC specs, thereby meeting less stringent standards.

So far so good. . .lot's of players. . .lots of selection. But isn't something missing? How many offer a truly *international* input voltage range? After all, you are buying a power supply that meets *international* standards because your product will be sold internationally. Right. Bear in mind that there are 150 countries worldwide with 30 unique operating frequency and voltage combinations.

### THEIR WAY

- Input: 90-132 VAC or 180-264 VAC, requires straps, taps or jumpers. User selectable.
- Designed to meet VDE 0804, 0806; IEC 380; UL 1012

### OUR WAY

- Input: 90-265 VAC or 100-380 VDC. Automatic input voltage compensation. No straps, taps or jumpers required.
- Meets VDE 0804, 0806, Class I SELV; IEC 380; UL 478, 1012
- 16 standard output configurations.
- 1 to 4 outputs.
- Overvoltage limit protection.
- Open or closed frame.
- Options available: Adjustable outputs, logic shutdown, overvoltage shutdown protection, power fail detect, remote sense, reverse polarity protection, ruggedized, thermal shutdown.

So why not select a power supply that can handle all those combinations automatically. . .without *straps, taps or jumpers*?

Now you can. Converter Concepts has designed its Versatron International (VI) Series to be truly *international*. Our ultra-wide input range will handle any AC input frequency and voltage combination worldwide.

Call Converter Concepts or our nearest representative for our 1986 catalog and a 30-day evaluation unit. If you value performance, you'll be glad you made the call.

**Phone: (800) 253-5227**

AL Alabama (205) 895-9160, AR Arkansas (501) 859-3105, Northern California (714) 859-3105, Eastern Canada (416) 675-4490, West-  
 orado (303) 773-2830, CT Connecticut  
 887-2310, FL Central Florida (305)  
 2211, Western Florida (813) 443-5214, GA Georgia (404) 263-9688, ID Idaho (801) 546-4837, IL Illinois (312) 398-5300, IN Eastern Indiana (616) 846-4980, Southcentral Indiana (513)  
 890-8322, KY Kentucky (513) 890-8322, LA Louisiana (214) 681-1376, MA Massachusetts (617) 655-6080, MD Maryland (215) 887-2310, ME Maine (617) 655-6080, MI Michigan (616)  
 846-4980, MS Mississippi (205) 895-9160, NC North Carolina (919) 833-8755, NH New Hampshire (617) 655-6080, NJ New Jersey (215) 887-2310, NY Upstate New York (315) 455-7346,  
 New York City (215) 887-2310, NV Northern Nevada (415) 887-1620, OH Ohio (216) 238-5905, OK Oklahoma (214) 681-1376, OR Oregon (503) 292-0820, PA Western Pennsylvania  
 (412) 823-5400, Eastern Pennsylvania (215) 887-2310, RI Rhode Island (617) 655-6080, SC South Carolina (919) 833-8755, TN Tennessee (404) 263-9688, TX Texas (214) 681-1376,  
 UT Utah (801) 546-4837, VA Virginia (215) 887-2310, VT Vermont (617) 655-6080, WA Washington (206) 743-6641, WI Wisconsin (414) 259-1771, WV West Virginia (412) 823-5400,  
 WY Wyoming (303) 773-2830

**CONVERTER CONCEPTS**  
 THE LEADER IN WIDE INPUT SWITCHER TECHNOLOGY

kansas (214) 681-1376, CA Southern  
 California (415) 887-1620, CANADA  
 ern Canada (604) 430-3680, CO Col-  
 (617) 655-6080, DE Delaware (215)  
 298-7748, Southern Florida (305) 792-  
 CONVERTER CONCEPTS, INC., INDUSTRIAL PKWY., PARDEEVILLE, WI (800) 253-5227



## INSTRUMENTATION & POWER SOURCES

testing ICs, resistors, and other electronic components. \$119.

**Exxair Corp.**, 419 Findlay St., Cincinnati, OH 45214. Phone (513) 381-4388.

Circle No 441



### FREQUENCY COUNTER

Model 1998 features a 1-sec response for 9-digit resolution over its 10-Hz to 1.3-GHz frequency range. Depending on the degree of resolution and speed of measurement required, you can vary displayed resolution from three to 10 digits. The counter features a burst-frequency capability that allows 6-digit resolution for signals as short as 2 msec. In addition, it offers period, ratio, and nulling capabilities. The nulling capability enables you to make measurements relative to any previously measured value. Other features include fixed-attenuator and variable-sensitivity controls. A rechargeable battery option for field operations includes an external 11 to 16V dc input for connection to a dc supply such as a vehicle battery. An IEEE-488 capability is also optional. \$1325.

**Racal-Dana Instruments Inc.**, Box C-19541, Irvine, CA 92713. Phone (714) 859-8999. TWX 910-595-1136.

Circle No 442

### 68020 SOFTWARE

The Oasys 68020 cross-development Toolkit features a set of compilers, assemblers, debuggers, simulators, profilers, a real-time operating system, and utilities for downloading

## POWER PARTNERSHIP

*At ONAN, every power supply we make comes with a partnership. A commitment.*

*In partnership, your deadlines become our deadlines. Your requirements become our requirements. It's what we call "Power Partnership." It's what cuts your own design and manufacturing costs, and frees you to focus on base technology and project management. It's a partnership that keeps you responsive to the demands of your marketplace.*



*Put the Power of Partnership behind your power supplies. Contact your ONAN Account Manager at 612/921-5600.*



**Onan**

**ONAN Power/Electronics**  
4801 West 81st Street  
Minneapolis, MN 55437  
612/921-5600

CIRCLE NO 154

## Technipower "Mil-Qual" Triple Output Switching Power Supplies




### Sealed or Field Repairable

The efficiency and size of a switcher, the output of a linear — all in a compact package! Available in AC/DC and DC/DC models, these "Mil-Qual" units are designed for severe shock and harsh environments. They feature a Mil-type input/output connector along with specially developed EMI/RFI filter circuitry. MTBF is 100,000 plus hours. Efficiency is 80%. Full power is provided at max operating temp., to 95°C, no derating.

Choose from 20 models which meet Mil-704, Mil-901 and other standards, have transient protection plus power ranges from 20 to 300W. 5 year warranty. Send for details.

*We Do The Job Right!*

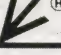**TECHNIPOWER**   
A **penfil** COMPANY

P.O. Box 222, Commerce Park, Danbury, Conn. 06810  
Phones: (203) 748-7001, In Calif. (805) 493-2244

See us at booth #118 Electro '86 Bayside Ctr., Boston

CIRCLE NO 79



# WE SATISFY YOUR PHYSICAL NEEDS



## MICOM-INTERLAN'S NT100 TRANSCEIVER FOR ETHERNET/IEEE 802.3 LANs

The NT100 offers all of the physical layer capabilities of an 802.3 transceiver:

- Sends and receives 10 Mbps
- Heartbeat test and collision detection
- Jabber control protects the network
- Electrical isolation to 500 volts

- Choice of three taps
- Installs in less than 5 minutes
- Calculated MTBF of more than 9 years

All of this at a price you'll find very satisfying. For details call 800-LAN TALK (or in Massachusetts call 800-TELL LAN) and ask for the Transceiver Manager.



MICOM-Interlan, 155 Swanson Road, Boxborough, MA 01719

CIRCLE NO 94

## INSTRUMENTATION & POWER SOURCES

programs. The compilers included are C, Pascal, and Fortran 77. The assemblers include linker, loaders, and librarian. In addition, the package supports the 68881 floating-point processor. The software runs on DEC VAX and MicroVAX (VMS, Ultrix, Unix), Sun, Apollo, Pyramid and other 68000- and 32000-based systems running Unix. \$3200.

**Oasys**, 60 Aberdeen Ave, Cambridge, MA 02138. Phone (617) 491-4180.

Circle No 443



### THERMOMETER

The Model 740 programmable scanning thermometer can linearize inputs from the seven thermocouple types (J, K, T, E, R, S, and B) and includes a separate microvolt range for nonstandard thermocouples. It supports as many as 81 channels, scans at 20 channels/sec, and includes a 100-reading, nonvolatile data memory. It features a built-in cold-junction reference, eight alphanumeric LED displays with °C or °F scale selection, a built-in IEEE-488 interface, digital calibration, a print feature, programmable alarm limits, and a real-time 24-hour clock. The device's accuracy is better than 0.5°C, and its resolution is 0.1°C or 0.1°F. You can use a selectable analog filter to provide an additional 20 dB of normal- and common-mode rejection at power-line frequencies. \$1350.

**Keithley Instruments**, Instruments Div, 28775 Aurora Rd, Cleveland, OH 44139. Phone (216) 248-0400.

Circle No 444



# When Choosing Quality The Choice Is LEMO Electronic Connectors



## LEMO B Series quality connectors available in multicontact from 2 to 64 contacts, or unique coaxial-multicontact, or high voltage multicontact configurations

**SPEED:** Connectors engage and disengage simply and quickly by pushing and pulling axially with the mated connector.

**SPACE SAVINGS:** Only finger clearance on two sides needed to engage and disengage connectors. No need to twist or turn locking ring.

**RELIABILITY:** Key/Keyway pattern provides mating exclusivity. Quick-Lok mechanism assures secure contact by audible click when lock is engaged. Color coding is available too.

**RUGGEDNESS:** Connector components are precision machined from brass bar and tubing stock, plated with copper and then nickel. Locking mechanism is totally protected by outer shell, virtually eliminating accidental disconnections, damage to locking mechanism, cables and contacts.

**AESTHETIC-FUNCTIONAL DESIGN:** Outer shell and back nut finished with matte chrome plating. Contacts are gold plated. LEMO connectors will complement any front panel application.

Over \$1 million inventory stocked in Santa Rosa, California, sold by a network of representatives in North America.

For technical data and catalog, as well as the name of your local representative, please call or write LEMO U.S.A., INC. [707] 578-8811, P.O. Box 11006, Santa Rosa, California 95406.




**LEMO USA INC**

See us at Electro booth #2856, 2858, World Trade Center

CIRCLE NO 288


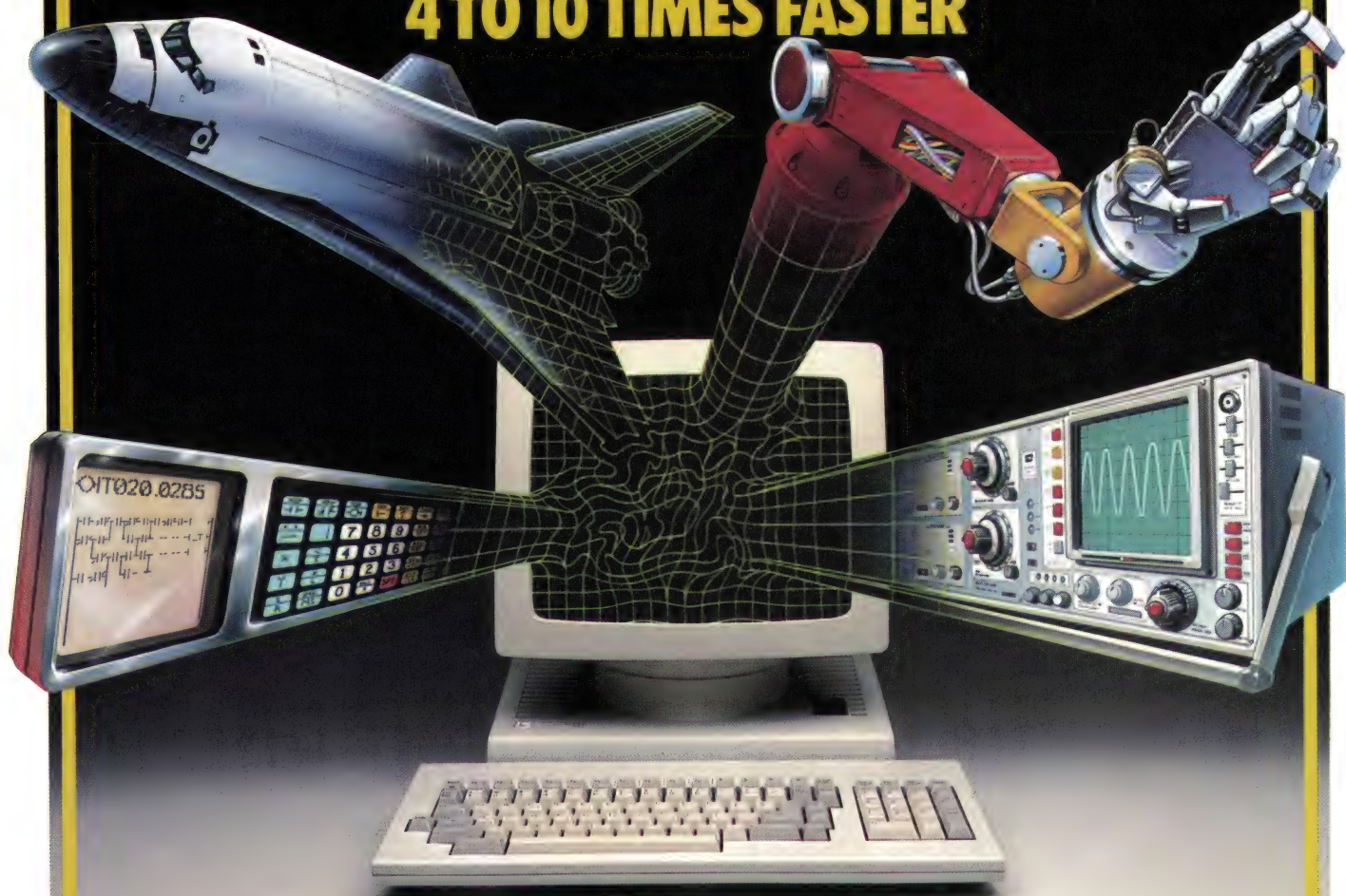
# polyFORTH GETS YOUR PROGRAM FROM CONCEPT TO REALITY 4 TO 10 TIMES FASTER



## THE ONLY INTEGRATED SOFTWARE DEVELOPMENT PACKAGE DESIGNED FOR REAL-TIME APPLICATIONS

If you're a real-time software developer, polyFORTH can be your best ally in getting your program up and running on time. In fact, on the average, you will develop a program 4 to 10 times faster than with traditional programming languages.

But you don't have to take our word for it—just ask our customers. We'll tell you who they are. They're some of the largest and most successful companies in high technology fields such as aerospace, robotics and machine vision, instrumentation, process control, and more.

polyFORTH shortens development time by making the best use of your time. There are no long waits while you load editors, compilers, assemblers, and other tools, not to mention the long waits while they run—because everything you need is in a single, easy-to-use, 100% resident system. Using polyFORTH, you take a raw idea to fast, compiled code in seconds—and then test it interactively.

polyFORTH's total programming environment has all the tools you need to develop real-time applications: fast multi-tasking, multi-user OS; FORTH compiler, interpreters, and assemblers; editor and utilities; and over 400 primitives and debugging aids. And because of its unique modular structure, polyFORTH even helps you test and debug custom hardware interactively.

polyFORTH is available for most 8, 16, and 32-bit computers. FORTH, Inc. stands behind its customers with complete professional support services including custom application programming, plus polyFORTH programming courses and the FORTH, Inc. "Hotline" to help programmers learn to use polyFORTH.

**For more information and a free brochure** on how you can cut development cycles 4 to 10 times, contact FORTH, Inc. today. FORTH, Inc., 111 N. Sepulveda Blvd., Manhattan Beach, CA 90266. Phone (213) 372-8493.



**FORTH, Inc.**



## NEW PRODUCTS: SOFTWARE

### IMAGE PACKAGES

Two additions to the Series 100 product line are the Itex 100 subroutine library and the Image-Pro 100 interactive program. Itex 100 routines are callable from applications written in the C programming language and provide image-processing, graphics, and hardware-control functions. The library uses uniform naming and calling conventions to minimize the amount of information the programmer must remember. It includes more than 100 different routines that perform, for example, initialization and hardware-control functions, pixel operations, and image and look-up table archiving. The Image-Pro 100 program uses Series 100 architecture to perform real-time image processing from a menu-driven user interface. It supports use of a variety of pointing devices. A report generator allows frame composition by merging image data with graphic

data from image-analysis functions. In addition, the program interfaces to most dot-matrix printers for hard-copy output of images captured, created, and/or manipulated. It includes the Halovision image editor for high-level graphics. Itex 100, \$995; Image-Pro 100, \$1495.

**Imaging Technology Inc.**, 600 W Cummings Park, Woburn, MA 01801. Phone (617) 938-8444. TLX 948263.

Circle No 445

### LISP

Using Lisp version 5.1, users can develop programs with as many as 8000 lines. This software offers more than 400 common Lisp functions, special forms, macros, and control variables. For greater speed, more than 300 of these functions are implemented in native machine code. The implementation has twice as many primitives as the

previous version, including selectors, constructors, modifiers, recognizers, and comparators. It also has twice the capacity of the previous version, allowing the development of programs using as many as 512k bytes of memory. A 2-pass garbage collector reallocates data-space boundaries during program execution. This version provides infinite-precision arithmetic for all rational numbers, including floating-point numbers. It comes with a symbolic debugger, a multilevel break-and-trace facility, and a profiling facility that identifies functions critical to program efficiency. Demonstration programs included on the disk illustrate AI techniques. System requirements include PC-DOS 2.0 or higher, 128k bytes of memory, and one disk drive. \$250.

**Microsoft Corp.**, Box 97200, Bellevue, WA 98009. Phone (206) 828-8080. TLX 328945.

Circle No 446

# FREE!



Here's the data you need on AC power for ATE systems, laboratories,

test facilities, robotics, quality control, data processing and more. It's all in our new full color catalog that features hundreds of AC Power Sources and Uninterruptible Power Systems. Call or write for your free copy.


**(805) 684-8311 COLLECT**

**BEHLMAN**  
Engineering  
Electronic Energy Conversion Sources & Systems

1142 Mark Avenue  
Carpinteria, CA 93013

CIRCLE NO 81
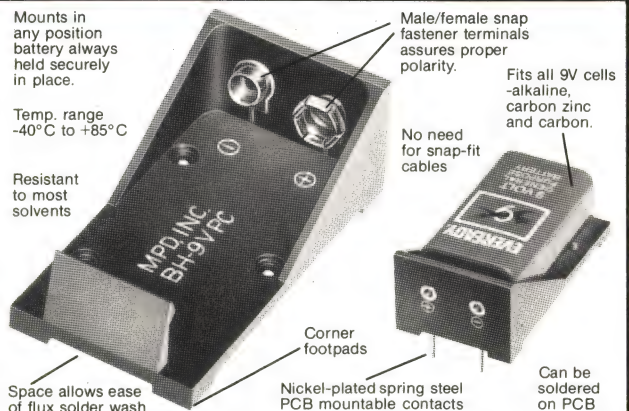
## NEW PCB MOUNTABLE 9V BATTERY HOLDER BH9V-PC



### For Memory Back-Up or Power Source

Use these handy BH9V-PC battery holders in microcomputer memory back-up systems, microprocessors, telecommunication equipment, etc.; or for power source in computer real time clocks, radios, smoke alarms and other appliances.

Black, high impact ABS plastic • Nickel-plated brass snap fastener terminals • Easy insertion and removal of batteries • Super efficient and economical • Custom holders available.

For all the details, call or write today.  
**Memory Protection Devices Inc.**  
320 Broad Hollow Road, Farmingdale, NY 11735 • 516-454-0340

CIRCLE NO 82



## CD-ROM LIBRARY

The Clasix Software Library Dataplate, which includes more than 8800 IBM PC programs on one CD-ROM disk, is included free with the purchase of the Clasix Series 500 CD-ROM Datadrive. An interface card and cable for the IBM PC and PC-compatible computers are also supplied. The library features executable programs and documentation from the PC Sig Library of public-domain and user-supplied software. An optional audio card allows the Datadrive to play compact audio disks and function alternately as the PC user's data-storage device or as a high-fidelity audio system component. Series 500 CD-ROM Datadrive plus software library, \$1595; audio card, \$149.

**Reference Technology Inc.**, 1832 N 55th St, Boulder, CO 80301. Phone (800) 225-2749; in CO, (800) 826-7873.

Circle No 447

## TURBO PASCAL TOOLS

Two packages of scientific programming tools, the IPC-TP-006 and the IPC-TP-007/008, provide the Turbo Pascal and Turbo-87 Pascal programmer with a variety of routines for applications programs. Both packages run on IBM PC, PC/XT,

PC/AT, and compatible computers. The general science and engineering package, IPC-TP-006, includes procedures for general statistics, multiple regression, curve fitting, integration, FFTs, file transfers to and from Lotus 1-2-3, solving simultaneous equations, matrix math, linear programming, and graphic display. The Turbo Pascal data-acquisition package, IPC-TP-007, operates with the IBM Data Acquisition Adapter and the Cyborg Isaac 411 and 911 hardware; the -008 version of this package operates with MetraByte Dash-8 and Dash-16 hardware. These data-acquisition packages include procedures for analog and digital input and output, thermocouple linearization, data logging, process control, and real-time graphics. Source code is provided for these programs. IPC-TP-006, \$69.95; IPC-TP-007/8, \$94.95.

**Quinn-Curtis**, Box 10, Newton Centre, MA 02159. Phone (617) 969-9343.

Circle No 448

## ENHANCED COMPILER

RM/Fortran V.2 is available for IBM PC/ATs and compatibles running under Xenix as well as for the Altos 2086. According to the manu-

facturer, it's the only program for personal computers that is a full Fortran-77, GSA-certified compiler that's error-free to the highest possible level. It also carries VAX, VS, and Fortran-66 language extensions frequently used in mainframe applications. The compiler boasts enhancements in execution speed, language features, ease-of-use upgrades, and new utilities. The Xenix implementation directly addresses more memory than DOS versions: Under Xenix, total program size is limited only by the computer's available memory. \$750.

**Ryan-McFarland Corp.**, 609 Deep Valley Dr, Rolling Hills Estates, CA 90274. Phone (213) 541-4828. TLX 294253.

Circle No 449

## DATA SIMULATOR

Picon, an on-line, real-time expert system for industrial-automation applications, now offers simulation capabilities. These capabilities enable users to simulate operating data to test their system's response to process upsets as well as standard operating conditions. In addition, these capabilities can help new operators learn their jobs prior to plant construction. The system's simulator supplies sensor values to

# TAKE THE HORROR OUT OF LED ASSEMBLY.

IDI takes the work and waste out of board assembly. With packaged LED solutions that save you more time and money - right off the shelf. Or, we'll

give you customizing help. Working with engineers is our specialty. Write for our data book, or call direct.

**BRIGHT IDEAS**




Industrial Devices, Inc., Edgewater, NJ 07020  
Telephone: (201) 224-4700




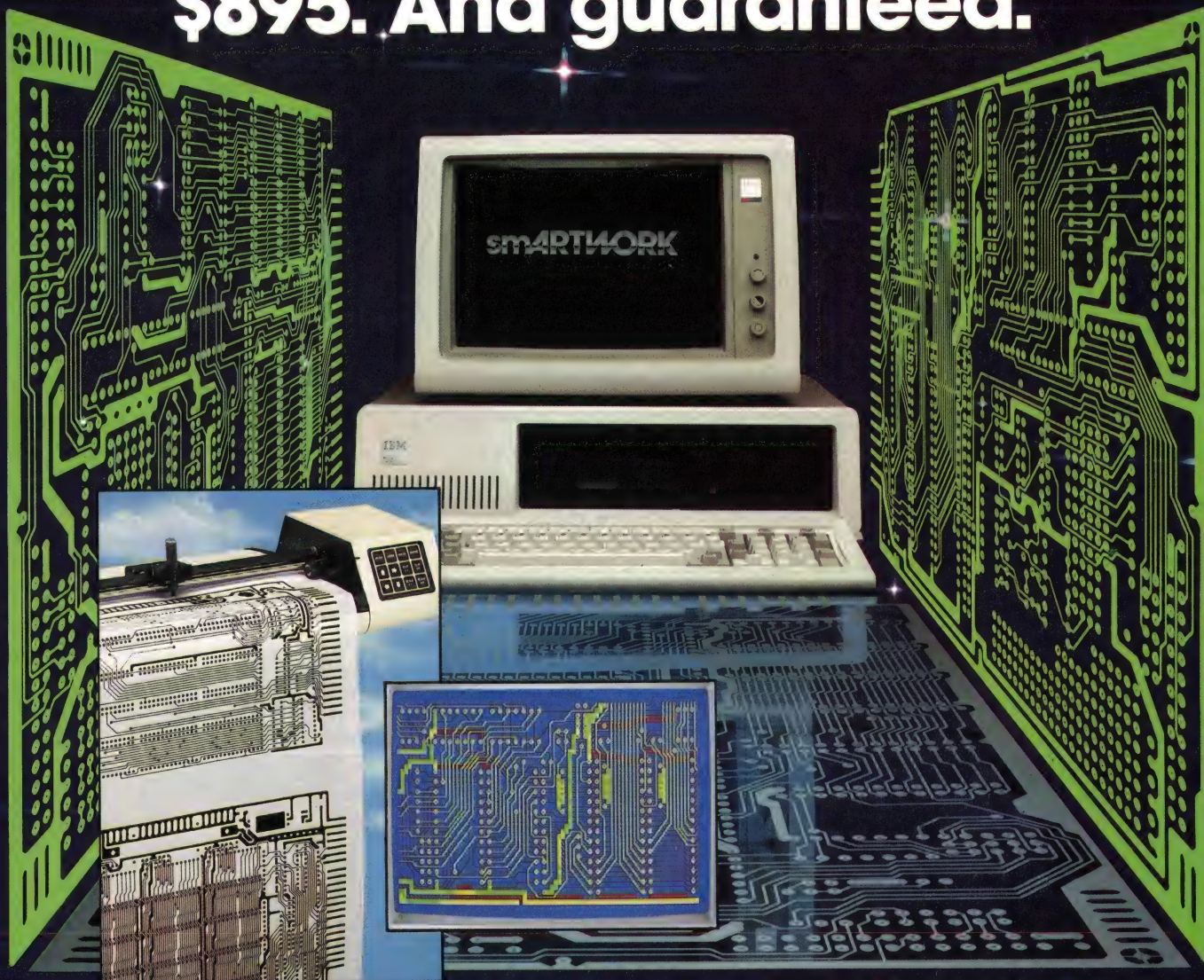
# Circuit-Board-Artwork Software: \$895. And guaranteed.



smARTWORK® lets the design engineer create and revise printed-circuit-board artwork on the IBM Personal Computer. You keep complete control over your circuit-board artwork — from start to finish.

And smARTWORK® is reliable. When we couldn't find a package that was convenient, fast, and affordable, we created smARTWORK® to help design our own microcomputer hardware. We've used it for over two years, so we know it does the job.

That's why we offer every design engineer a *thirty-day money-back no-nonsense guarantee*. smARTWORK® advantages:

- ☐ Complete interactive control over placement and routing
- ☐ Quick correction and revision
- ☐ Production-quality 2X artwork from a pen-and-ink plotter

- ☐ Prototype-quality 2X artwork from a dot-matrix printer
- ☐ Easy to learn and operate, yet capable of sophisticated layouts
- ☐ Single-sided and double-sided printed circuit boards up to 10 x 16 inches
- ☐ Multicolor or black-and-white display

#### System Requirements:

- ☐ IBM Personal Computer, XT, or AT with 320K RAM, 2 disk drives, and DOS Version 2.0 or later
- ☐ IBM Color/Graphics Adapter with RGB color or black-and-white monitor
- ☐ IBM Graphics Printer or Epson FX/MX/RX series dot-matrix printer
- ☐ Houston Instrument DMP-41 pen-and-ink plotter
- ☐ Microsoft Mouse (optional)

#### The Smart Buy

At \$895, smARTWORK® is proven, convenient, fast — *and guaranteed*. Call us today. And put smARTWORK® to work for yourself next week. Try it for 30 days at absolutely no risk. That's smart work.

Wintek Corporation  
1801 South Street  
Lafayette, IN 47904-2993  
Telephone: (317) 742-8428  
Telex: 70-9079 WINTEK CORP UD




In Europe contact: RIVA Terminals Limited,  
Woking, Surrey GU21 5JY ENGLAND,  
Telephone: 04862-71001, Telex: 859502

"smARTWORK", "Wintek" and the Wintek logo are registered trademarks of Wintek Corporation.



# MAGIC

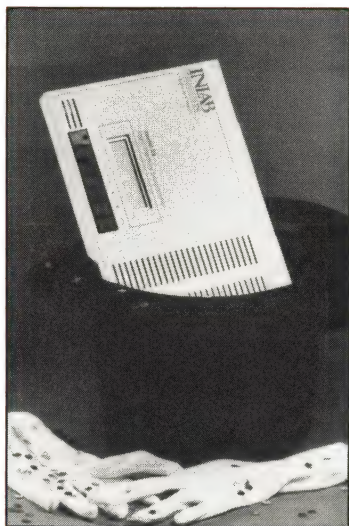

THE INLAB 28  
LOGIC/MEMORY  
PROGRAMMER

**I**t must be magic! How else could INLAB load all these features into such a small package:

- Capable of programming hundreds of logic and memory devices, including all of the most frequently used PLDs!
- Small and portable—less than 26 ounces!
- Completely software driven—ZIF Universal socket accepts all devices up to 28 pins!
- Available with CUPL™, the design software from Assisted Technology!
- Compatible with both JEDEC and Intel HEX download file formats!
- Standard RS232 interface links the Model 28 with most host systems!
- Inexpensive firmware updates ensure long instrument life!

What more could there be? How about EPROM programming and emulation, from 2716 up to 27256 (including CMOS)? Its like getting an EPROM programmer/emulator—for free!

It's no illusion! For only \$1995, we can make a Model 28 appear before your very eyes! Just give us a call at:

303/460-0103

We'd like to do some *magic* for you!

**INLAB**  
INC

A Hathaway Company

2150-I West 6th Avenue  
Broomfield, CO 80020

CUPL is a trademark of Assisted Technology; some elements of the Model 28 are manufactured and marketed under license from Digital Media, Inc.

CIRCLE NO 84

## SOFTWARE

the inference engine in lieu of data from the real process or factory. It can solve sets of difference equations, which allows it to realistically portray the changing conditions of a process over time. The user can switch the input to the inference engine from actual plant data to simulation and back again to allow incremental testing of the system's response to various scenarios. After the process is completed, the system responds with appropriate diagnoses or operator messages. The system runs on the manufacturer's Lambda Plus multiprocessor and costs \$60,000.

**Lisp Machine Inc.**, 6 Tech Dr., Andover, MA 01810. Phone (617) 689-3554.

Circle No 450

### VRTX FOR VME

This company has ported its VRTX real-time operating system to Motorola's VMEmodule board family. The MVME device support packages allow users of three VMEmodule units—the MC68010-based MVME117 and MC68020-based MVME130 single-board microcomputers and the MVM320 Winchester/floppy-disk controller—to interface the boards' hardware devices easily to the VRTX/OS. Because each MVME device support package is supplied in the form of source-code listings, users can modify variables, such as baud rate, to fit specific applications. The MVME117 and MVME130 packages provide driver support for onboard devices such as the MC68881 floating-point coprocessor, RS-232C ports, 8-bit parallel ports, the SCSI bus, the MC68B40 programmable timer, and the 8-bit software-readable front-panel switch. MVME117 and MVME130 device support packages, \$500 each; MVME320 package, \$1000.

**Hunter & Ready**, Box 11803, Palo Alto, CA 94306. Phone (415) 326-2950. TLX 278835.

Circle No 451

### IMAGE PROCESSING

The RTI-Station is an integrated digitizing, storing, and processing system for IBM PCs and PC-compatible systems. It digitizes a high-resolution (512×512-pixel, 8-plane) video signal in 1/40th of a second from an RS-170, RS-330, RS-343, or CCIR source. You can connect as many as four video sources to the processing system. In addition, the system's signal-conditioning hardware permits connections to VCRs and cameras. The system performs automatic input dc restoration; gain/level controls are programmable. Four programmable 256×8-bit transformation tables allow preprocessing of the input signal. RTI-Station's imaging-software library provides a driver interface, basic board-level control, high-level imaging algorithms for image enhancement, feature extraction, object recognition, and comprehensive board diagnostics. \$10,000 to \$23,500.

**Recognition Technology Inc.**, 335 Fiske St, Holliston, MA 01746. Phone (617) 429-7804.


Circle No 452

### FORTH TOOLS

An enhanced pf8086/MSD package for PolyForth programming operates under MS-DOS but provides multiuser, multitasking capabilities not available in standard MS-DOS systems. Included are an integrated graphics package and screen-oriented editor that runs with any standard IBM color monitor. The standard math package is supplemented by one that uses the 8087 math coprocessor and allows you to perform 32- and 64-bit floating-point math, matrix arithmetic, and trigonometric, log, and exponential functions. The package comes in several levels. Level 3 includes the multiuser, multitasking operating system, a compiler, an assembler, a high-level interpreter, a string editor, routines for database support, disk and print utilities, and source



# VDE APPROVED.

Only Airpax gives you real design freedom with  approved magnetic circuit breakers. From 50 milliamps to 50 amperes, in more than 50 configurations and styles. Only Airpax VDE approved breakers can help open your world markets. Airpax Corporation, Cambridge Division, Woods Road, Box 520, Cambridge, MD 21613. (301) 228-4600. A North American Philips Company.



## AIRPAX®

CAMBRIDGE DIVISION

CIRCLE NO 305

See Us At Booth 522-530



**...TO THE ENDS OF THE EARTH**

**ELECTROCHEM  
QUALITY LITHIUM  
POWER SOURCES**



*Sometimes you need power in the most remote, hostile environments... like data gathering stations in sub-zero climates. That's a service call nobody wants to make.*

*In extreme cases like this, specifiers rely on incredibly powerful, dependable and long lasting Electrochem lithium batteries.*

*But you don't have to operate on a frozen tundra to experience the advantages of lithium power sources... they work in critical everyday applications like metering devices, memory backup, telemetry and many more.*

***Why lithium?** Today lithium power sources represent a highly developed technology offering distinct advantages over other battery types... like high voltage, light in weight, adaptable to virtually any climatic condition, extremely reliable performance for years with no recharging required. In short, better overall operating efficiency.*

***Why Electrochem?** We're a leader in lithium power sources, and we'll go to the ends of the Earth to meet your power source needs. But chances are we won't have to because we have a wide range of lithium batteries, and packs, for almost every conceivable application... in stock.*

*Our team of power source experts is ready to take on your next challenge. They'll introduce you to our exclusive CELlection program... to determine your needs and provide the most effective and efficient solution.*

*When you need a reliable power source that will go to the ends of Earth, look no farther than Electrochem.*

*For more information on lithium power sources, and our CELlection program, call (716) 759-2828 and say "Hello, Electrochem!"*

**ELECTROCHEM  
INDUSTRIES**

**DIVISION OF WILSON GREATBATCH LTD.**  
10,000 WEHRLE DRIVE  
CLARENCE, NEW YORK 14031  
(716) 759-2828 TELEX: 91-386



## SOFTWARE

code for the elective utilities. Level 4 has all the facilities of Level 3 plus a target compiler and source code for the entire system. Level 3, \$600; Level 4, \$3200.

**Forth Inc.**, 111 N Sepulveda Blvd, Manhattan Beach, CA 90266. Phone (213) 372-8493. TLX 275182.

Circle No 453

### Z80 CROSSASSEMBLER

The AX Z-80 absolute crossassembler and the RX Z-80 relocatable crossassembler both run on the IBM PC and compatible computers. The AX Z-80 absolute crossassembler translates an assembly source file into a downloadable object file with absolute addresses in Intel hex format. The RX Z-80 relocatable version translates an assembly source file into a relocatable file, which you can then link with other relocatable files (by using the linker included in the package) to form a downloadable object file in Intel hex format. Both crossassemblers feature pseudo-ops and conditional assembly and include descriptive error messages and cross-reference tables. One-time fee for AX Z-80, \$250; for RX-Z80 with linker, \$400.

**United States Software Corp.**, 5470 NW Innisbrook Pl, Portland, OR 97229. Phone (503) 645-5043. TLX 4993875.

Circle No 454

### AI TOOLS

The Lisp Toolkit runs on any VAX, MicroVAX II, VAXstation II, or DEC AI Workstation that's configured to run VAX Lisp (version 1.2 or a later version). It also works in conjunction with Inference Corp's Automated Reasoning Tool (Art). This set of development tools includes five main modules: The FMS Module is a fourth-generation form-and-menu-display package layered on VAX FMS. The GKS Module allows the control, use, and generation of device-independent imaging and graphics from VAX Lisp or Art.

The RDB Module allows the tight integration of traditional database technology with AI technology. The CMS/MMS Module extends DEC/CMS and DEC/MMS to permit application maintenance of VAX Lisp and Art-based systems. The DECnet Module provides a VAX Lisp-based distributed communications environment for building cooperat-

ing expert systems or any other VAX Lisp-based distributed applications. License for VAX 8600, \$24,000; for 78/785, \$15,000; for VAX 750, \$8000; for DEC AI Workstation, \$6000.

**Composition Systems Inc.**, 570 Taxter Rd, Elmsford, NY 10523. Phone (914) 592-3600.

Circle No 455

## WEATHER FORECAST:

**Low Temperature,  
High Reliability  
For ETA Power Supplies**



That's what you'll be forecasting for your system when you use ETA high current, switchmode, DC power supplies. They maintain the lowest component-to-ambient temperature gradient in the industry. At least 15% lower.

ETA does it from 500 to 1800W; 1 to 5 outputs; to 360A. More power? Parallel-up and share current automatically — no master. Six new high density models deliver up to 1200W from a smaller 5" x 8" x 10" case.

Reliability is the priority with ETA. A unique hybrid thermal design (patent pending) maintains low component temperatures. High voltage transistor V-I reshaping enhances safe area operation. Fault tolerant designs provide protection for power supply and system alike. In-house stress tests "beat-up" the power supply

more than your system ever can. Then there's burn-in. The end result is high system reliability for you.

That's why ETA has become the vendor of choice for reliability sensitive applications with many Fortune 100 computer/electronic companies.

*Call or write for ETA's new full line power supply catalog. Judge the value for yourself.*


**ETA  
POWER  
SYSTEMS**

2675 Junipero Ave.  
Signal Hill, CA 90806  
(213) 427-0095

CIRCLE NO 85




## AMERICA'S BEST PROGRAMMERS

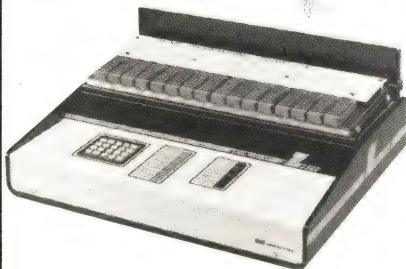
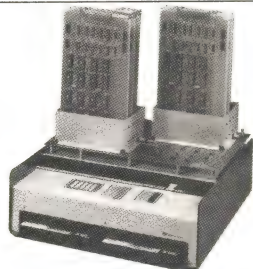
### Z-3000 HIGH VOLUME GANG/SET PROGRAMMER

- 14,000 27256s programmed per day.
- 32 EPROMs simultaneously with 1 to 8 DATA BLOCKS.
- 16 Intel or Motorola MCUs at a time.
- 64K to 256K bytes of DATA RAM.
- Simple one key programming operation.
- Two RS-232 ports with data transfer formats included.



### Z-2500B IN-CIRCUIT MEMORY CARD PROGRAMMER

- Programs up to 32 memory cards with EPROMs or microcomputers at a time.
- Two 1.2 Mbyte DSDD floppy disk drives. Optional 20 Mbyte hard disk.
- Turnkey systems include programmer, terminal, custom interface hardware and software.
- Simple menu driven operation.

### Z-1000B UNIVERSAL PROGRAMMER

- Over 600 PLDs, EPROMs, EEPROMs, bipolar PROMs and INTEL MCUs.
- Upgradeable PROM based software.
- Stand alone or PC/XT/AT operation.
- Two independent RS-232 ports.
- 64K or 256K bytes of DATA RAM.
- EXATRON handler interface is standard.

### Z-1200B TWELVE SOCKET GANG/SET PROGRAMMER

- 2716-27512, 1 to 4 DATA BLOCKS.
- 64K to 256K bytes of DATA RAM.
- Software personality. No plug-ins.

**ZAP SERIES** low cost programmers for EPROMs and single-chip MCUs.

**Z-400** for bipolar PROMs and EPROMs.



**SUNRISE ELECTRONICS, INC.**

524 South Vermont Avenue  
Glendora, California 91740  
(818) 914-1926

CIRCLE NO 86

## SOFTWARE

### PL/I COMPILER

The PL/I compiler for Prime Series 50 superminicomputers meets the requirements of the ANSI X3.53-1976 and ISO 6160 standards for the PL/I language. It also contains extensions, such as Select and Leave statements, to provide functional compatibility with IBM PL/I. The compiler is upward compatible with the extended version of PL/I Subset G offered by the company. Both compilers use the same run-time library, so that third-party programs compiled under either of them can be run without the presence of the compiler. Both compilers are compatible with the the company's Interactive Source Debugger and use the same interface to the PRIMOS operating system. For Prime office systems, \$4000; for Prime computer-room systems, \$7000.

**Prime Computer Inc.**, Prime Park, Natick, MA 01760. Phone (617) 655-8000.

Circle No 456

### PROCESS SIMULATOR

The Chemcad integrated PC software system provides process simulation and 2-D CAD. You can prepare process designs, quickly analyze design alternatives, predict the effects of changes on plant operating conditions, optimize energy consumption, and eliminate bottlenecks and increase throughput. The package can simulate flowsheets containing as many as 100 streams and 50 pieces of equipment, and it has 16 built-in equipment modules capable of modeling virtually all process plants. The same program that you use to perform the simulation allows you to produce the process flow diagram (PFD); you choose which calculated results appear on the PFD. You can obtain hard copy using an HP 7400 Series plotter or an Apple laser-jet printer. The program runs on an IBM PC or equivalent with 64k bytes of RAM, a hard disk, an Intel math

coprocessor, and an IBM enhanced color-graphics adapter. \$7350.

**Coade**, Div of International Thomson Information Inc, 8550 Katy Freeway, Suite 122, Houston, TX 77024. Phone (800) 231-0732; in TX, (713) 973-9060.

Circle No 457

### SCHEMATIC CAPTURE

Circuit Design Mate schematic-capture program allows editing of schematics in much the same way that a word processor handles text. The menu-driven, self-prompting program can retrieve often-used parts from libraries of user-created components or from the library of standard TTL parts that is supplied with the package. Files can contain multiple pages of schematics, and you can print schematics in A, B, or 11×14-in. sizes. The program requires an IBM PC, PC/XT, PC/AT or compatible system with 256k bytes of RAM; a 640×200-pixel IBM-compatible graphics card; two double-sided disk drives or one floppy-disk drive and one hard-disk drive; an Epson or compatible dot-matrix printer with graphics capability; and PC-DOS or MS-DOS 2.0 or higher. \$295.

**Midwest Micro-Tek Inc.**, Box 29376, Brooklyn Center, MN 55429. Phone (612) 560-6530.

Circle No 458

### BASIC COMPILER

The BC 204 Basic compiler is the first compiler available for HP Basic, version 4.0, according to this manufacturer. It's compatible with HP 9000 Series 200/300 workstations. Compiled programs operate directly with the manufacturer's FP 200 or FP 210 floating-point coprocessors as well as the HP 98635 floating-point coprocessor. \$880.

**Infotek Systems**, 1400 N Baxter St, Anaheim, CA 92806. Phone (714) 956-9300.

Circle No 459




# TAKE YOUR BEST SHOT WITH AIE'S T-CARRIER MAGNETICS



**DASH-BAK SERVICE GIVES YOU FAST ACCESS TO THE COMPONENTS YOU NEED.** When you need inductive components for data transmission circuits, count on AIE Magnetics' new lineup of T-carrier transformers. We've got the small pulse and wideband transformers and clock extractor coils to fit your needs—both in "stock" designs for sample quantities or custom-designed for your specific circuit requirements.

And no one brings it to you faster than AIE. With our DASH-BAK service, you receive "straight-from-the-catalog" orders within 72 hours and transformers that require design modifications within 5 days.

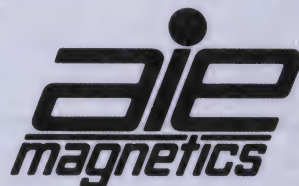Simply write or call us about your next design; we'll gladly send you our catalog and your own DASH-BAK service card. They'll give you the best shot at your goal.



701 Murfreesboro Road Nashville, TN 37210 615/244-9024  
"A Division of Vernitron Corporation"

CIRCLE NO 292








## 2,000 sharper-than-ever characters all on a portable LCD display.

Toshiba's newest LCD modules give you  $640 \times 200$  dot displays in a choice of two viewing sizes. One is approximately the size of a magazine, and the other about half that size.

Both sizes put an enormous amount of information on view... an array of 80 characters  $\times$  25 lines. But still bulk and power consumption are at a minimum. Battery powered, these slim modules interface with various systems through LCD controller without renewing software.

Toshiba's advanced technology has also eliminated surface reflection and developed a sharper contrast which gives a brighter and easier to read viewing screen. And for low light or dark viewing an optional backlightable LCD is available.

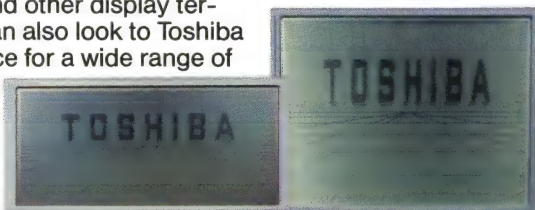These versatile LCDs are ideally suited for applications as displays for personal computers, POS terminals, portable word processors and other display terminals. You can also look to Toshiba with confidence for a wide range of sizes and display capacity to suit your LCD requirements.



TLC-363B

TLC-402

### Specifications

	TLC-402	TLC-363B
<b>Display</b>		
Number of Characters	80 $\times$ 25 (2,000 characters)	80 $\times$ 25 (2,000 characters)
Dot Format	8 $\times$ 8, alpha-numeric	8 $\times$ 8, alpha-numeric
Overall Dimensions (W $\times$ H $\times$ D)	274.8 $\times$ 240.6 $\times$ 17.0 mm	275.0 $\times$ 126.0 $\times$ 15.0 mm
<b>Maximum Ratings</b>		
Storage Temperature	-20° ~ 70° C	-20° ~ 70° C
Operating Temperature	0° ~ 50° C	0° ~ 50° C
Supply Voltage	VDD 7 V VDD - VEE 20 V	7 V 20 V
Input Voltage	0 $\leq$ VIN $\leq$ VDD	VSS $\leq$ VIN $\leq$ VDD
<b>Recommended Operating Conditions</b>		
Supply Voltage	VDD 5 $\pm$ 0.25 V VEE -11 $\pm$ 3 V Var.	5 $\pm$ 0.25 V -11 $\pm$ 3 V Var.
Input Voltage	High VDD - 0.5 V min. Low 0.5 V max.	VDD - 0.5 V min. 0.5 V max.
<b>Typical Characteristics (25°C)</b>		
Response Time	Turn ON 300 ms Turn OFF 300 ms	300 ms 300 ms
Contrast Ratio	3	3
Viewing Angle	15 - 35 degrees	15 - 35 degrees

Design and specifications are subject to change without notice.

# TOSHIBA

Toshiba America, Inc.: Electronic Components Business Sector: Head Office: 2692 Dow Avenue, Tustin, CA 92680, U.S.A. Tel. (714) 832-6300  
Chicago Office: 1101 A Lake Cook Road, Deerfield, IL 60015, U.S.A. Tel. (312) 945-1500

Toshiba Europa (I.E.) GmbH: Electronic Components Div.: Hammer Landstrasse 115, 4040 Neuss 1, F.R. Germany Tel. (02101) 1580

Toshiba (UK) Ltd.: Electronic Components Div.: Toshiba House, Frimley Road, Frimley, Camberley, Surrey GU 165JJ, England Tel. 0276 62222

Toshiba Electronics Scandinavia AB: Vasagatan 3, 5 TR S-111 20 Stockholm, Sweden Tel. 08-145600



# EDN PRODUCT MART

This advertising is for new and current products.

Please circle Reader Service number  
for additional information from manufacturers.

## PROGRAMMABLE CROSS HAIR GENERATOR

VISIT  
US AT  
ELECTRO '86  
MINI MICRO  
BOOTH #2629



**SPEEDS  
IMAGE  
ALIGNMENT  
AND  
MEASUREMENT  
PROCEDURES**


The AMS PCHG-8 Video Cross Hair Generator is a single board which features the ability to superimpose up to 4 horizontal and 4 vertical indicator lines anywhere on the screen and produce cross hairs, or a box under program control. Eliminating the need to manually set coordinates, it speeds image alignment and measurement procedures.

Available with RS232 input for stand-alone use or powered by the STD bus for systems use, the AMS PCHG-8 Video Indicator Generator provides a variety of signal outputs, including position data, making it ideal as a pattern recognition building block. The board provides a target mode as well as 1 to 8 black, white or dotted lines in any combination. A joy stick option in conjunction with position readout is useful in optical measurement applications.

**AMS**

9 Executive Drive  
Hudson, NH 03051  
(603)882-1447

CIRCLE NO 237

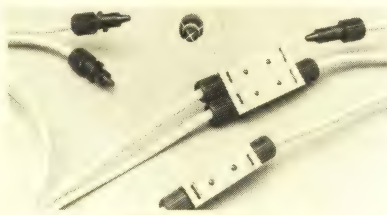

## NEW "LITE-LINK" MINIATURE FIBER OPTIC CONNECTOR

- Easy In-the-Field Installation
- Exclusive Quick-Disconnect

Series 808 provides a space-saving glass fiber optical connector for applications ranging from optical data links to LAN (Local Area Network) interface. It is field installable. Features bayonet type, twist lock for quick-disconnect. Has integral bushing and spring loading to assure proper fiber end-spacing and alignment.

Connector will terminate 50/125 or 100/140 micron multimode, glass fiber optic cable. Available in both single and duplex line configurations for cable-to-cable, cable-to-PCB and cable-to-wall mount interconnects. Application Kits are offered.



**METHODE ELECTRONICS, INC.**  
7447 W. Wilson Ave., Chicago, IL 60656  
(312) 867-9600 Outside IL: 1-800-323-6858

CIRCLE NO 239

## LOGIC PROGRAMMER... "and" DESIGN & TEST SYSTEM



### DIGELEC Model 803-LDC \$3450.

- Supports design & test in "STAND-ALONE" as well as computer control operation
- Built-in CRT display for entry and display
- Both Boolean equation & fuse map entry for PALs
- Exclusive Boolean equation DISASSEMBLER for PALs
- H&L Logic table entry for IFLs/FPLAs
- User defined JEDEC format vector testing entry
- Time-saving CRC TESTING using internal pseudo-random test pattern generator
- Programs 20, 24 & 28 pin PALs & IFLs, virtually all manufacturers and UPGRADEABLE

—Also manufacturers of EPROM, GANG, OEM, BOARD LEVEL & UNIVERSAL PROGRAMMERS—


**DIGELEC, INC.**

1602 Lawrence Ave., Ocean, NJ 07712  
For immediate action call: (201) 493-2420

CIRCLE NO 240

## 0 to 40 in 1 second!

Remarkable performance. A linear microstepping motor/drive system with a resolution of 12,500 steps per inch. Capable of speeds up to 40 inches per second. An interesting alternative to leadscrew, rack and pinion or belt drives.

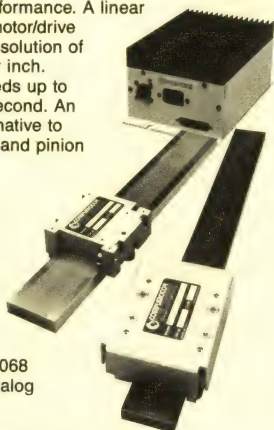

call 1-800-358-9068  
for our latest catalog

Another step forward from . . .

**COMPUMOTOR  
CORPORATION**  
1179 North McDowell Blvd., Petaluma, CA 94952

CIRCLE NO 241

## EXORbus/MICROMODULE® COMPATIBLE BOARDS FROM STOCK

**mikul™** offers a full line of EXORbus/Micromodule compatible boards including an enhanced MM17 replacement, I/O, memory and more.

For more information contact—

**mikul™**

A Division of TL Industries, Inc.  
2541 Tracy Road • Toledo, Ohio 43619 • (419) 666-8144

® TRADEMARK OF MOTOROLA


CIRCLE NO 242

## UNIVERSAL UP/DOWN COUNTER



It's a presettable, 4 digit up/down counter with optional DIGITAL LIMIT, with LARGE L.E.D. display and 5-150VDC or 115/230VAC power input housed in 1/8 DIN/NEMA metal or plastic case with screw connector. To it we plug in at your option RPM, FREQUENCY, RATE, QUADRATURE, DATUM ZERO, TIMER, CLOCK, PULSE DIVIDER and more and/or tristate opto isolated BCD, RELAYS and logic for zero and limit detection give you unlimited applications. One unit for all your counting needs.

"SERIES 270"

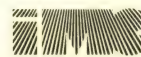


**I.M.C.**  
4016 Tennessee Street  
Tucson, AZ 85714  
(602) 748-7900

CIRCLE NO 243


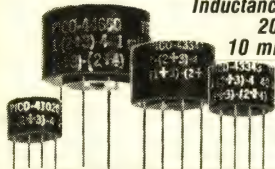
## PICO's Miniaturized Power Inductors

for Noise, Spike and Power Filtering  
Applications in Power Supplies, DC-DC  
Converters and Switching Regulators.  
Inductance values from  
20 millihenry to  
10 microhenry with  
DC currents  
to 6 Amps.




See us at Electro 86, Booth 1109

These units can  
be supplied as  
military standards.  
Contact factory  
for appropriate  
part numbers.  
(MIL-T-27/356-01  
thru MIL-T-27/356-63)

- Minimum possible size
- Meets MIL-T-27D (TF5S042Z)
- Special high frequency core material to insure low losses
- All units have split windings
- Large selection of sizes available

PICO Electronics, Inc., 453 N. MacQuesten Pkwy.,  
Mt. Vernon, NY 10552. In NY call 914-699-5514.  
Call Toll Free 800-431-1064

CIRCLE NO 244

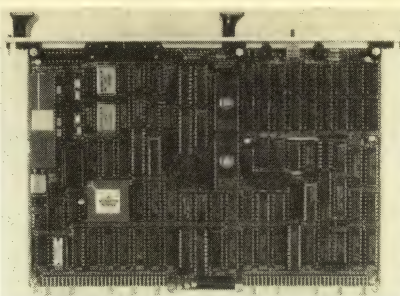

### SVME-101 Intelligent VMEbus Expansion Card

- 68000 (8, 10 MHz) processor
- 128/512 Kbytes tri-ported RAM
- High performance DYBX I/O channel (16D, 24A control)
- One RS-232C, four counter timers
- Two 28-pin byte-wide sockets
- Interrupt handler

For more information on the SVME-101 contact:


DY-4 Systems Inc.,  
1475 S. Bascom Ave., Suite 202,  
Campbell, CA 95008 (408) 377-9822



CIRCLE NO 245
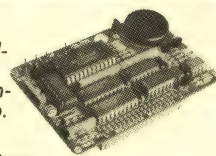
## MULTIBUS: Your Time Has Come!

The mSBX-241™  
Multimodule is a  
robust, precision Real-  
Time Clock/Calendar  
in SBX format with on-  
board battery backup.



### General Features:

- ☐ For high performance systems:  
no wait states or software overhead
- ☐ Attaches to all SBX and BLX compatible Multibus boards
- ☐ Programmable alarm clock and periodic interrupts
- ☐ 12 or 24 hour time modes, in both BCD and binary format
- ☐ Internal 100 year calendar with leap year compensation
- ☐ Selectable automatic Daylight Savings compensation
- ☐ Contains fifty bytes of general purpose non-volatile RAM
- ☐ RMX-86/286 drivers supplied on diskette

For more information contact:

Medinova Corporation  
Intelligent Systems Group  
244 West Court, Palatine, Illinois 60067  
Telephone (312) 934-4700

Multibus, Multimodule TM Intel Corp.


CIRCLE NO 246

## PRESSURE SENSORS

A complete line of solid state pressure transducers, sensors, and transmitters. PC Board-mountable or fully packaged. For both gases and corrosive liquids. Low cost, reliable. IC Sensors is a leading manufacturer of standard and custom pressure transducers.

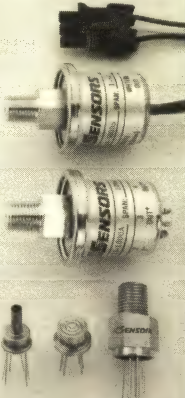
- 0-5 to 0-5000 PSI
- Gage, Absolute, Differential
- 3x Overpressure
- Temperature Compensated
- Piezoresistive
- 316 Stainless Steel Diaphragm
- Sensors: 100mV & 200mV
- Transducers: 1-5V
- Transmitters: 4-20mA

- Applications:
  - Medical Instrumentation
  - Liquid Levels
  - Air Conditioning
  - Robotics
  - Hydraulics
  - Process & Industrial Control
  - Avionics
  - Automotive
  - Environmental Control
  - Water Management
  - Machine Tools



**IC SENSORS** 1701 McCarthy Blvd., Milpitas  
CA 95035 (408) 946-6693

CIRCLE NO 247

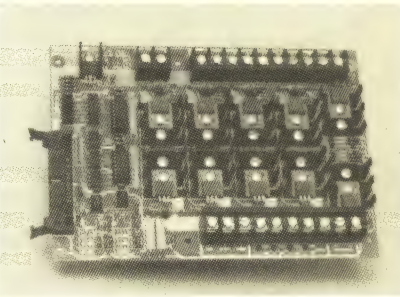

### DDB-10 DUAL AXIS STEPPER MOTOR DRIVER

Optically isolated interface board independently drives two four-phase unipolar steppers to 48V and 5A/phase. Simple connection to most computer I/O - one line for STEP, one for DIRECTION, two for encoder/limit sense inputs (each channel). All output drivers protected from inductive stepper spikes. Eight LEDs display step drive activity. Optional on-board voltage reference and linear voltage control. Controlled oscillators give analog speed control capability.

KINETICON SYSTEMS  
1079 Culloden Ct.  
San Jose, CA 95121  
(408) 365-7063

CIRCLE NO 248

## GET BIG RESULTS WITH PRODUCT MART ADS

REACH OVER 137,000  
READERS —  
ALL SPECIFIERS  
OF ELECTRONIC  
COMPONENTS, SYSTEMS  
AND EQUIPMENT!

CIRCLE NO 249



### PHILIPS DOT MATRIX LCD's

Amperex announces the availability of Philips Dot Matrix LCD displays in 1x16, 2x16, 2x40 characters and Graphics Panel configurations. Each of these displays features a built-in character generator and display controller. For detailed information and specifications call or write:

Amperex Electronic Corporation  
George Washington Highway  
Smithfield, RI 02917  
Telephone (401) 232-0500

CIRCLE NO 250

### CADD for \$99.95

GENERIC CADD is a sophisticated & easy to use Computer Aided Drafting/Design program for PCs.

### GENERIC CADD Features:

- Drawing Layers • Component Libraries
- Component Libraries • User-Defined Fonts
- Video & Digitizer Menus • Color Graphics

### Other Available GENERIC

#### Software:

AUTOCAD™ file conversion for \$24.95  
Dot Matrix printer/plotter option for \$24.95

Call 1-800-228-3601 to order  
No dealer calls, please.


MC, VISA, COD. Add \$3.00 for shipping  
60 day money back guarantee

### GENERIC SOFTWARE

13250 NE 40th St.  
Bellevue, WA 98005  
(206) 885-5307

CIRCLE NO 251

## \$91.00\* Single Board Computer

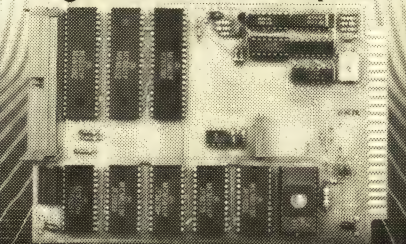

\*500 piece price, model MCI45 (shown)

6800 MPU, serial I/O, parallel I/O, RAM, EPROM,  
44-pin 4.5" x 6.5" PCB

EXPANSION MODULES: RAM, EPROM, CMOS RAM/  
battery, analog I/O, serial I/O, parallel I/O, counter/  
timer, IEEE-488, EPROM programmer, floppy disks,  
cassette, breadboard, keyboard/display.

**WINTEK** Wintek Corp.  
1801 South Street  
Lafayette, IN 47904  
317-742-8425  
(800) 742-8809

CIRCLE NO 252



## Schematic Capture \$495


Now a complete design tool for your IBM or compatible computer that includes everything you need to design, edit, and print electronic schematics. Compare these features and you will discover that OrCAD/SDT is the most powerful, complete, and cost effective schematic design tool available.

- Full color & monochrome graphics.
- Supports A through E size sheets.
- Unlimited level hierarchy.
- Powerful keyboard macros.
- Automatic panning.
- Part rotation & mirroring.
- Utility programs for post processing.
- Over 1600 library parts.
- Supports the most common PC graphic boards, printers and plotters.

BROCHURE and DEMO DISK — **NO CHARGE!**

OrCAD Systems Corporation  
23315 W. Baseline Road  
Hillsboro, Oregon 97123  
(503) 640-5007

CIRCLE NO 253

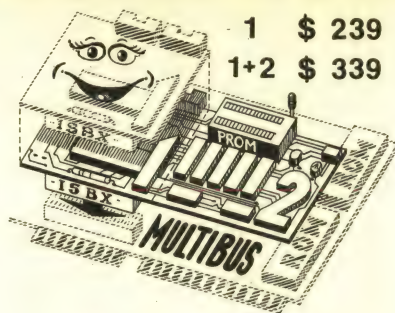

1 \$ 239  
1+2 \$ 339


### SBX 8086 DEVELOPMENT PACKAGE

- SOFT-EMULATOR firmware Executive
- IBM-PC interface (symbolic debug opt.)
- 2 channel RS-232/422, HDLC/SDLC
- DMA, 2 Interrupts, multidrop
- Fast on-line PROM programming
- EPROMS: 2716-27512, 1Mb workspace

#### MICRO-CRAFT

P.O. Box 124  
Boulder Creek, CA 95006  
(408) 338-4958

CIRCLE NO 254

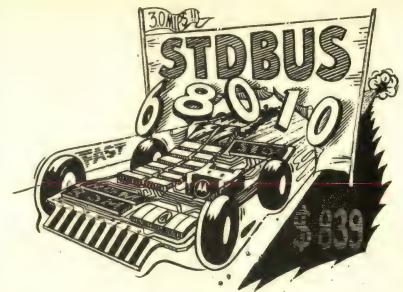


### STD BUS — Single board computer

- 68000/68010 @ 10/12.5MHz (C-MOS)
- 512k-DRAM 0-waits, 128k-EPROM
- MULTITASKING NUCLEUS, 16k-Rom
- RS-232. 16 bit parallel, 5 Timers
- EXPANSION: 2ch DMA, 768k-DRAM/ROM IEEE Numeric processor

#### MICRO-CRAFT

P.O. Box 124  
Boulder Creek, CA 95006  
(408) 338-4958

CIRCLE NO 255

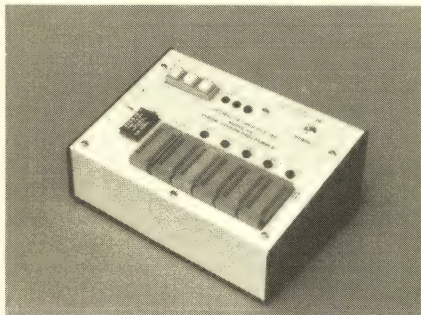

### EPROM DUPLICATOR WITH RS232

The Model 98 has stand-alone programming for 2716, 2732, 2732A, 2764, 27C64, 2764A, 27128, 27128A, 27256, 27C256, 27512, and 27C512 EPROMs, and 2816A, 2864A EEPROMs. Programming time for 27256 is 190 seconds. A serial interface provides file transfer to/from IBM PC, or PC compatible. Silicon identifiers are supported for Intel, AMD, and SEEQ. Price \$650. Software \$40. Copy modules \$18. **Optimal Technology**, Earlysville VA 22936. 804-973-5482


CIRCLE NO 256

### PRESTON QUALITY AT A NEW REMARKABLY LOW PRICE

Building Better Solutions With The New EM Series A-to-D Conversion Systems

Preston Scientific now brings you its new low-cost, high performance ADC Instrumentation Systems. The EM Series Three models give you 13-bit resolution and the conversion rate you need for your most critical applications. Three models: 1MHZ, 500 KHZ, 312 KHZ. All with the same performance and quality that has made Preston world-famous.

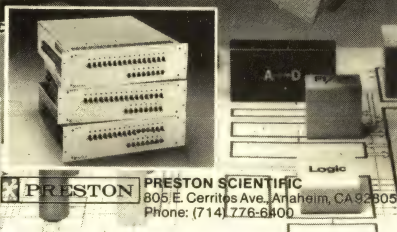The new EM Series provides: high quality, high resolution, and high speed. You buy only what you need and that saves you money. Best of all, the EM Series can be delivered quickly, 30 days ARO. Don't settle for less. For a better A-to-D solution, call or write today for details.



CIRCLE NO 257



### TEST COMPONENTS IN CIRCUIT, POWER OFF WITH THE NEW HUNTRON TRACKER 2000

Revolutionary Huntron Trackers find shorts, opens, leakage and bonding problems in analog, digital and hybrid components. Test capacitors, logic circuits, op amps, transistors and more. An excellent troubleshooting tool that finds the faults scopes, DMM's and logic analyzers miss. Tracker prices start at \$995.00.

For the nearest distributor, call  
1-800-426-9265, Dept. 270.

**HUNTRON INSTRUMENTS, INC.**  
15123 Highway 99 North  
Dept. 270, Lynnwood, WA 98037

**HUNTRON**

CIRCLE NO 258

## Custom "Hi-Rel" POWER/CURRENT/CONVERTER transformers




FOR REPEATABILITY OF PRODUCT...all specs translated into standardized format & language  
FOR IDENTICAL PROTOTYPE AND PRODUCTION PARTS...there's total documentation of production and Q.C.

ALL SIZES AND POWER LEVELS/MILITARY/INDUSTRIAL

**TORWICO** ELECTRONICS  
INCORPORATED

410 Oberlin Ave. South, Lakewood, NJ 08701 • (201) 364-1800

CIRCLE NO 259

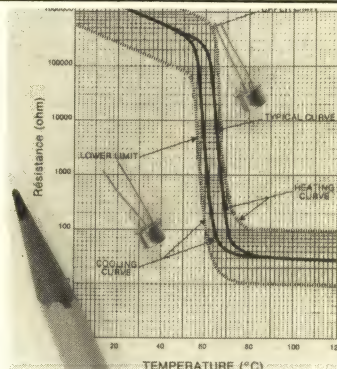

### SOLID STATE THERMAL SWITCH CANTHERM'S MOXIE™ THERMAL SENSOR

57°C, 65°C, 75°C, 85°C  
TCR max - 200%/°C  
Excellent stability  
Application information

Delivery from stock  
Optional housing  
Also in chip form  
Samples available upon request

Canadian Thermostats & Control Devices Ltd.  
8415 Mountain Sights Avenue  
Montreal, Quebec H4P 2B8  
(514) 739-3275 Tlx. 05-825619

CIRCLE NO 260

## NEW PRESSURE TRANSDUCER


FREE FOR OEM TEST

- Stainless steel
- Strain gage

Call free  
1-800-323-7115  
ext. 502

In Pennsylvania  
1-800-323-7114

**Robinson-Halpern**

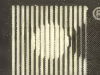

One Apollo Road  
Plymouth Meeting, PA 19462

CIRCLE NO 261

To advertise in Product Mart, call Joanne Dorian, 212/576-8015





### Capture and Analyze Waveforms with the IBM Personal Computer

Single card plug-in module and software package makes IBM PC (or compatible computer) a digital storage oscilloscope.


- 25 MHz real-time sampling rate, down to 250 Hz. Pre-trigger viewing of waveform.
- Dual input channels, gain from 0.005 V/Div to 5.0 V/Div.
- Software package provides full control, display, disk storage, print-out and analysis.
- Computes true RMS, frequency, power, mean volts, averaging and more.
- Interfaces with user's Basic program for use in test or control system.

From stock, \$1500 including software.  
OEM discounts available.

**Integrated Systems Products, Inc.**, 6028 Freemont Circle, Camarillo, CA 93010. Call for data sheet (805) 987-5125.

CIRCLE NO 262

### FREE Design Guide!

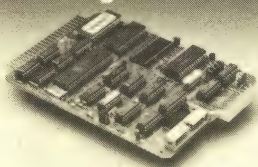

### CONTROL COMPUTER WITH BASIC - ONLY \$345

Versatile Z-80A data acquisition and control computer. Resident 16K Floating Point BASIC language for easy programming. Connect a CRT terminal, a 5V supply, and write programs. The SYS-2Z includes: 12-bit A/D converter, digital I/O, lamp/relay drivers, EPROM programmer, RS-232C port, 8K RAM, ROM-mable code, Auto-run operation, and Debug Monitor. Expandable. **Octagon Systems**, 6510 W. 91st Ave., Westminster, CO 80030. 303/426-8540.

CIRCLE NO 264

# 8051 8048

**SIMULATORS - CROSS ASSEMBLERS - PROGRAMMERS - SIM51 and SIM48** Software Simulators run on IBM-PC, CP/M-80, MS-DOS. Designed for validation & debugging application software. Simulation includes all on chip functions plus expansion chips. \$250, one year **FREE** updates. Formats: PC-DOS 2.x DSSD, CP/M-80 8" SSSD, many 5 1/4" formats. Cross Assemblers and EPROM pgmrs also available. **Logical Systems Corp.** 6184 Teall Station, Syr., NY 13217 (315) 478-0722

**Logical Systems**

CIRCLE NO 267

Ultraminiature ITT Schadow KSA switches have a low applied cost.




KSA switches lower your assembly costs with a sealed, auto-insertable design that resists processing contamination. Built-in contact straps, positioning studs, snap-in pins, and optional ESD protection further simplify assembly, and a size of only 7.62 x 10.16mm can save up to 50% on front panel space.

**ITT Schadow Inc.**  
8081 Wallace Road  
Eden Prairie, MN 55344  
(612) 934-4400

Circle No. 235 for an ITT Schadow Catalog  
Circle No. 236 for Sales Engineer Call/Samples

### ELIMINATE DECOUPLING CAPACITORS

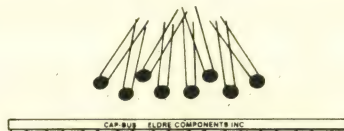


#### CAP-BUS® CAPACITOR/BUS BAR

Eliminate the decoupling capacitors and the power and ground traces from your PCB for more reliability. CAP-BUS® has a distributed capacitance of .05 micro-farads per lin. in., at 50 VDC with low inductance and low impedance. The capacitor and the bus bar have been joined together for CAP-BUS®, a more efficient capacitive decoupled power distribution system, increasing IC density on a two sided board.

**ELDRE COMPONENTS, INC.** 1500 Jefferson Rd.  
Rochester, NY 14623  
(716) 244-2570

CIRCLE NO 265

## ROEDERSTEIN

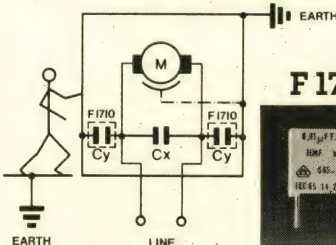

ROEDERSTEIN introduces F-1710 "Y class" suppression capacitor in a molded plastic case, 250 VAC, with value range from 1000 pF to 0.1 uF in 9 different case sizes. Designed to meet VDE O565 part 1/1279, and as a "safety capacitor" according to VDE O86O/8.81 para 142.

For more information contact:

**ROEDERSTEIN ELECTRONICS, INC.**

PO Box 5588, 2100 West Front St., Statesville, NC 28677

(704) 872-8101 TWX: 810-625-0786

CIRCLE NO 268

## C CROSS-COMPILERS MACRO CROSS-ASSEMBLERS

VAX

PDP-11

IBM PC

6801/6301

68HC11

6805

68000/10

6809

68020

VAX, PDP-11: TM of Digital Equip. Corp.  
IBM: TM of Int'l. Business Machines

## INTROL CORPORATION


647 W. Virginia St.  
Milwaukee, WI 53204  
(414) 276-2937

CIRCLE NO 263

# DISTRIBUTE YOUR LITERATURE AND CATALOGUES THROUGH THIS SPACE FOR ONLY

# \$725

CIRCLE NO 266

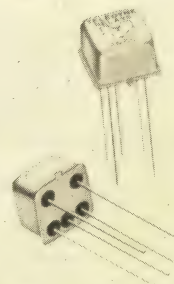


### RADIATION TESTED MIL OPTO-ISOLATOR

Teledyne's 4N50 isolator contains a gallium arsenide LED coupled to a silicon photo-diode detector which provides base bias for a high gain NPN transistor. Isolation of 1500 VRMS, output voltage of 40V, and current transfer ratio of 140% is provided in a hermetically sealed case 0.37" square by 0.275" high. Exceeds tactical radiation levels. Hybrid assembly complies with MIL-883B. \$20.50 ea. for 1000 pcs. **Teledyne Solid State**, 12525 Daphne Ave., Hawthorne, CA 90250 (213) 777-0077.

CIRCLE NO 269

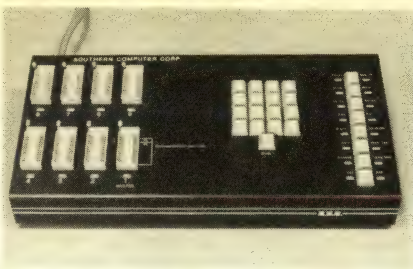To advertise in Product Mart, call Joanne Dorian, 212/576-8015





### The SCC Cost Efficient Programmer for EPROMS/EEPROMS.

Basic System \$1,195 includes:

Keypad, serial port, display, 8 gang programming, set programming, and device menu – **no personality modules**. 256K byte memory option – program 512 devices. UV Eraser \$395.



Southern Computer Corporation  
3684 Clearview Avenue  
Atlanta, Georgia 30340  
404/455-8018

CIRCLE NO 270



### REGISTERED INTEGRAL MODEM

Designing a modem into your product has never been easier—and quicker. Just plug Cermetek's 1770 FCC registered modem module onto your circuit card, connect it to power, your system's UART, and to the phone line via an RJ11C jack.

Cermetek Microelectronics, Inc.  
1308 Borregas Avenue  
Sunnyvale, CA 94088-3565 408/752-5055

CIRCLE NO 271




### TELEPHONE LINE INTERFACE

Cermetek's DAA module, the CH 1812, allows you to implement a registerable phone line interface right on your circuit card. All Cermetek DAA modules are compatible with today's modern components currently available from semiconductor manufacturers.

Cermetek Microelectronics, Inc.  
1308 Borregas Avenue  
Sunnyvale, CA 94088-3565 408/752-5055

CIRCLE NO 272
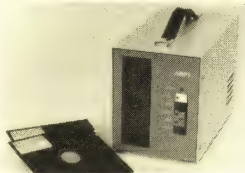
### IBM PC COMPATIBLE RS232 EASI-DISK 5 1/4" FLOPPY DATA STORAGE & TRANSFER SYSTEM



- Reads & Writes IBM PC DOS 5 1/4" Disks
- RS-232C I/O
- Rugged Portable Package
- Host and/or Manual Controls
- ASCII or Full Binary Operation
- Baud Rates 110 to 19.2 K Baud
- Automatic Data Verification
- Price \$1,095 in Singles - OEM Qtys. Less

28 other systems with storage from 100K to 35 megabytes  
ANALOG & DIGITAL PERIPHERALS INC



815 Diana Drive  
Troy, Ohio 45373  
513/339-2241  
TWX 810/450-2685

Branch Off: Oklahoma City, OK - Factory: Yucca Valley, CA

CIRCLE NO 273

### Your Helping Hand!



### Switch Mode Power Supply - Inductor Calculator-

Provides calculations for buck, boost and flyback mode power supplies. Also a section for output filter calculations.

TO RECEIVE YOUR COPY SEND \$39.00 TO:

**HURRICANE**  
Electronics LAB  
P.O. Box 1280, Hurricane, Utah 84737  
The source of all your magnetic needs  
(Request our full line catalog)

CIRCLE NO 274


### DC-DC CONVERTERS



This DC-DC converter series was developed by our own engineering and design team. The input/output circuits of the converter are completely isolated. The filter is built in so that ripple and spike noise are reduced to a minimum. Input voltage: DC 5, 12, 15, 24, 48V. Output voltage: DC 5, 12, 15, 24, 48V. High Efficiency, High Reliability, Low cost.

**P&C SHITEN ENTERPRISE CO., LTD.**  
Tel: (02) 395-1400 Telex: 19206 PCSHITEN  
Cable: PCSHITEN P.O. Box: 30-291 Taipei Taiwan


CIRCLE NO 275

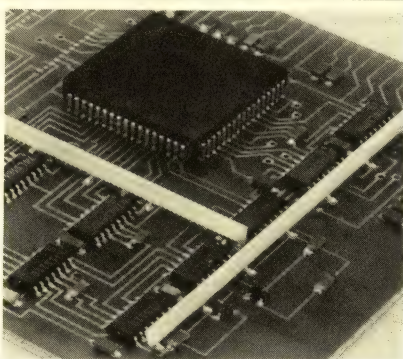

### HOW ROGERS MINI/BUS® BUS BARS REDUCE YOUR COSTS:

Move power distribution off-board; stay with 2-layer boards. MINI/BUS bars mount between rows of columns or nest under columns of IC's. Get more room without adding space or costs. Get rid of up to half the decoupling capacitors for many applications. **ROGERS CORP.**, 2400 S. Roosevelt St., Tempe, AZ 85282 (602) 967-0624

CIRCLE NO 276

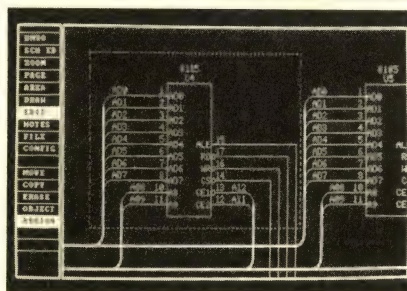

### FREE DEMO DISK

**SCHEMA** is a complete, integrated schematic drawing software package for IBM Personal Computers. Use **SCHEMA** with your PC to draw schematics and automatically generate design documentation such as Wire and Net Lists, Bills of Materials, Design Rule Checks, etc. **SCHEMA** is \$495 and supports most common PC hardware configurations. Call or write today for a free demo disk and brochure.

**OMATION INC.**  
1701 N. Greenville Ave., Suite 809  
Richardson, TX 75081  
(214) 231-5167

CIRCLE NO 277



### ANTI-STATIC Chair Covers

Just slip these covers over the seats and backs. Designed for your shop and lab chairs.

Available with or without padded cushions, in black only.

Laboratory Tested, the covers help control static and provide years of service.

Practical  
Efficient and  
Economical.


Call or write for more information.



Covercraft Co. Inc.  
PO Box 417, Goshen, IN 46526-0417  
Telephone - (219) 533-7960

CIRCLE NO 278



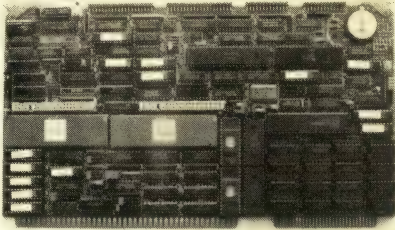

### 68000 Multibus Board

High performance 10 MHz 68000 processor based Multibus single board computer features four DMA channels, parallel interface, timers, real time clock, dual synchronous or asynchronous serial channels, up to 1 megabyte RAM, 256K EPROM or 128K EPROM and 64K battery backed up RAM, dual expansion connectors, on-board interface to Priam hard disk controllers.

AMTELCO

4800 Curtin Drive,  
McFarland, WI 53558


(608) 838-4194 (800) 356-9148

CIRCLE NO 279

## COOLSIL™

THERMALLY CONDUCTIVE  
INSULATORS

SILICONE COATED FABRIC

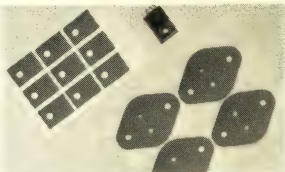

- Eliminates the use of messy grease and mica
- Saves assembly time
- Provides consistent thermal conductivity
- Puncture resistant
- Excellent dielectric properties
- Available in standard T03, T03P, T0220 and many other configurations.



Stockwell Rubber Company  
4749 Tolbut St./Philadelphia, Pa. 19136  
215-335-3005, 800-523-0123 outside Pa.

CIRCLE NO 282

## Computer Parts Mart


634 North 8th St.  
San Jose, CA 95112  
(408) 993-9011

### STEPPER ENSEMBLE

100 Step High Precision Motor

By Applied Motion. Stepper driver with bipolar windings, 26 ohms/15mh. 1/4" x 2.1" ground shaft with helical follower groove @ 0.182" pitch. This is an extremely high accuracy assembly good to better than 50 microns absolute. Ball bearings, 5.5gm/cm inertia, 10 oz. in. holding torque @ 400 ma. New, never used. Driver I.C.s: 3717 for P.W.M. Microstepping allows efficient use of any supply voltage up to 40v D.C. Motor and Two I.C.s including data sheets \$14.95

### STD-BUS

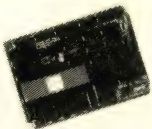

64K RAM Card expandable to 256K	\$ 99
256K Card	\$249
Votrax Card	\$149
SASI Interface Card	\$100
4-SIO Card	\$165
4-PIO Card	\$129
2-SIO & 2-PIO Card	\$125
Z80 CPU Card	\$ 79
6800 Proc. Card	\$300

Complete STD Systems available—Up to 10 slots, 10 MB Disk, etc.

### MULTI-BUS I

Now specializing in Multi-Bus I, we buy and sell boards, chassis, and development systems.

CIRCLE NO 285



## The Pulse of Dependable Communications


Crystek Crystals offers their new 16 page free catalog of crystals and oscillators. Offering state of the art crystal components manufactured by the latest automated technology. Custom designed or "off the shelf," Crystek meets the need, worldwide. Write or call today!

### CRYSTEK CRYSTALS

1000 Crystal Dr. • Ft. Myers, FL 33907  
P.O. Box 06135 • Ft. Myers, FL 33906-6135  
TOLL FREE 1-800-237-3061

CIRCLE NO 280
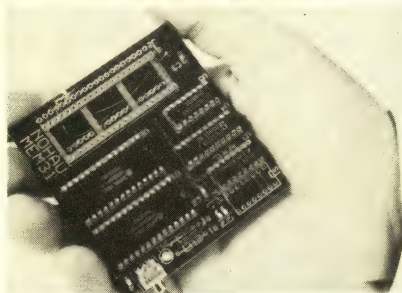
### MEMORY EXPANSION FOR INTEL EMV51 and ICE51



#### MEM31. MEMORY EXPANSION UNIT

Hardware: The MEM31 circuit board is installed between the emulator and the target system. The MEM31 board contains 16K of R/W memory. The memory can be expanded up to 64K. No external power supply is needed.

Software: The MEM31 software automatically splits your object file into emulatory loadable units. They are then loaded into the MEM31 via the emulator. The price is \$695 which includes PCB, floppy disk and documentation.

NOHAU CORPORATION, 164 Calle Larga, Los Gatos, CA 95030 (408)374-1594.

CIRCLE NO 283

### LOW COST PROCESS CONTROLLERS FOR COMMERCIAL AND SEMI TECHNICAL END USERS.



#### Automate your processing;

Controller programming requires only a power supply and dumb terminal. The programmer need only be familiar with 'BASIC' programming language.

#### CONFIGURED SYSTEMS AVAILABLE. Individual cards also available including;

- \* CPU card with nine 8-bit ports to the controlled environment
- \* Memory expansion cards
- \* Analog digital interface cards
- \* High current/voltage drive cards
- \* Real Time clock/calendar

#### Obtain automated controlling:

Contact technical representative:  
LASER VIDEO INC on (713) 850 4800  
Full Systems support available

CIRCLE NO 286

## CY525 3rd generation STEPPER MOTOR CONTROLLER

most intelligent controller offers  
linear ramping, 10,000 steps/sec,  
unlimited stepping, change  
rate on the fly, read  
position on the  
fly, and  
much  
more.



CY512  
compatible,  
40 pin, +5 volt  
TTL, 8 bit I/O interface  
to computer. \$195 ea (\$80/100)  
Prototyping board available.



Cybernetic Micro Systems

P.O. Box 3000, San Gregorio, CA 94074  
(415) 726-3000 Telex: 171-135 att: Cybernetic

CIRCLE NO 281

## BE REMEMBERED...



Enhance your visibility  
to EDN's 137,000  
EOEM circulation with  
a Product Mart Ad

CIRCLE NO 284

## Quelo® 68000 Software Development Tools

Quelo Assembler Packages are Motorola compatible. Each package includes a macro assembler, linker/locator, object librarian, utilities for producing ROMable code, extensive indexed typeset manuals and produces S-records, Intel hex, extended TEK hex, UNIX COFF and symbol cross references. Portable source written in "C" is available. It has been ported to a variety of mainframes and minis including VAX.

#### 68020 Assembler Package

For CP/M-86, -68K and MS/PC-DOS ..... \$ 750

#### 68000/68010 Assembler Package

For CP/M-80, -86, -68K and MS/PC-DOS ..... \$ 595

#### 68000 "C" Cross Compiler

For MS/PC-DOS by Lattice, Inc.  
With Quelo 68000/68010 Assembler Package \$1095  
With Quelo 68020 Assembler Package ..... \$1250

Call Patrick Adams today:

Quelo, Inc.  
2464 33rd W. Suite #173  
Seattle, WA USA 98199  
Phone 206/285-2528  
Telex 910-333-8171

COD, Visa, MasterCard


Trademarks: CP/M, Digital Research; MS, Microsoft Corporation; Quelo, Quelo, Inc.

CIRCLE NO 238

To advertise in Product Mart, call Joanne Dorian, 212/576-8015



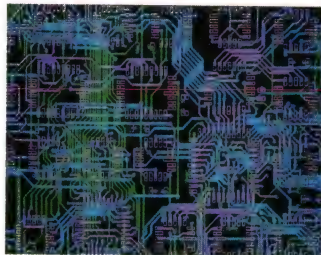
# TELESIS GIVES YOU MORE THAN ONE PATH TO THE FUTURE.



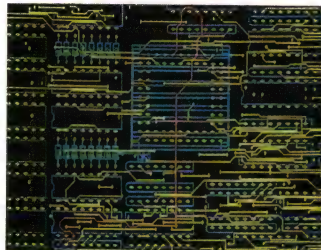
## SMD TOOLBOX

For surface-mounted and thick-film hybrid designs.



## ECL TOOLBOX

Automates design of transmission lines.

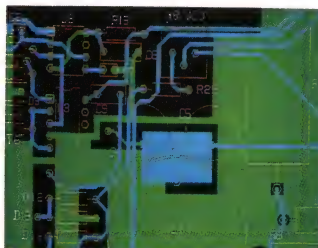

## ANALOG

Automatically handles non-uniform characteristics.



## DIGITAL


Over 1,000 components can be designed as a single data base.

## THE CAD WORKSTATION FOR EVERY PCB TECHNOLOGY.

Most CAD systems just can't handle today's complex PCB designs.

But the Telesis EDA-700 Design Workstation lets you follow any technology path—from digital to analog to ECL to SMD. It also gives you complete design tools. Like schematic creation. Automatic placement and routing. Design rules checking. Artwork generation. And it's so flexible it can even handle tomorrow's PCB designs, regardless of device technology, density or packaging technique.

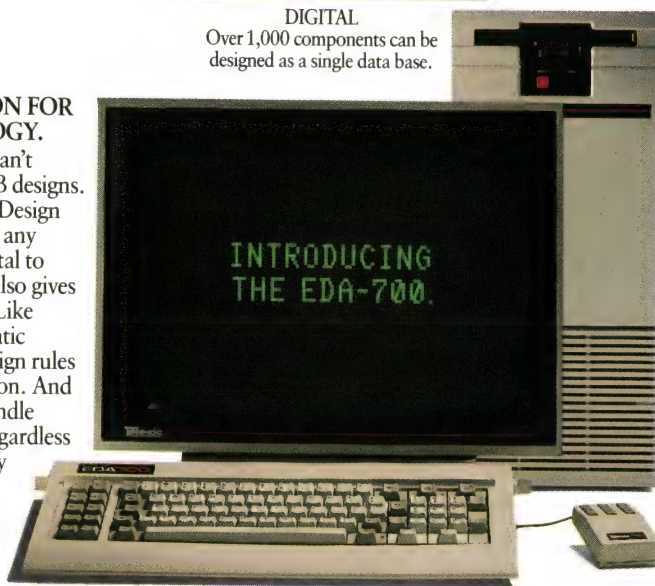Telesis takes you beyond conventional design solutions. Our unique



Thermal Analyzer software predicts thermal behavior prior to prototyping. And our fully integrated Design Capture System places low-cost productivity tools in the hands of the engineer.

With all this capability at an affordable price, it's no wonder that Telesis ships more PCB CAD workstations than anyone else in the U.S.

For complete information, call us at 617-256-2300. Or write Telesis, Two Omni Way, Chelmsford, MA 01824. We'll put you on the path to the future of PCB design.

# Telesis



# We run with a great crowd.

## Complete hardware/software compatibility.

Talk about easy interfacing. You can take a ZETA 824 or ZETA 836 plotter and plug it into virtually any computer made.

What's more, you'll be ready to run because our plotters understand a variety of computer protocols. Select the model for your application then just plug in and plot.

In fact, we're a plug compatible replacement for many plotters from HP, CalComp and Tektronix. Some models of our plotter can even run directly from your IBM cluster controller. Now that's easy interfacing.

When it comes to your favorite application packages, you'll be on safe ground too. Packages such as CADAM, TechniCAD, Euclid, P-CAD, AutoCAD and many more.

### *The most productive plotter for the money.*

You'll be getting the highest output plotters for the money with our new ZETA 824CS and ZETA 836CS. More

finished plots. More productivity. Plus, these "D" and "E" format plotters let you run either single sheet or roll media.

### *Easy-to-use touch controls.*

Your time is valuable. So we've made our touch controls simple – yet powerful. Set speed, pen pressure, liquid ink parameters, electronic limit sensing, windowing, scaling – all at the touch of a finger. Self-test and diagnostic plots too. Let us show you dozens of other time-saving operations in a brief demonstration.

### *Plotter specialists.*

We've been designing hardware interfaces, plotting language emulators and high performance pen plotters for over 14 years. Nicolet also provides you with worldwide sales and service support.

Give us a call. See how easy it is to join the crowd.

Call (415) 372-7568.


Nicolet Computer Graphics Division, 777 Arnold Drive, Martinez, CA 94553  
TWX 910-481-5951

**Nicolet**  
Computer Graphics Division

CADAM is a trademark of CADAM, Inc.  
TechniCAD is a trademark of Tektronix, Inc.  
Euclid is a trademark of MATRA DATAVISION, Inc.  
P-CAD is a trademark of Personal CAD Systems.  
AutoCAD is a trademark of Autodesk, Inc.

**CIRCLE NO 294**



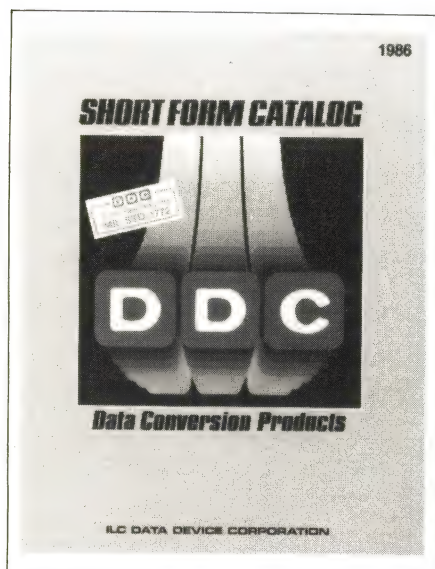

## Catalog depicts data converters, -1553 products

This 1986 8-pg short-form catalog describes more than 100 of the manufacturer's products, including numerous new devices. It provides specs and technical data for databus products, A/D and D/A converters, synchro-to-digital and digital-to-synchro converters, S/H and T/H amplifiers, synchro and resolver instruments, and MIL-STD-1553 components. The booklet also depicts units providing special functions such as control transformers, a synchro booster amplifier, and Inductosyn-to-digital converters. In addition, it describes the company's MIL-STD-1772-qualified facilities.

**ILC Data Device Corp.**, 105 Wilbur Pl, Bohemia, NY 11716.

Circle No 460


## App note explains remote temperature transducer

This 4-pg application note concentrates on minimizing the influence of noise in remote-temperature-measurement circuits. It outlines how to build a remote temperature-to-current transducer with a  $-55$  to  $+100^{\circ}\text{C}$  range and a  $100\text{-mV}/^{\circ}\text{C}$  output voltage using the AD590 linear current-output temperature transducer. The publication treats types of noise, initial noise effects, elements of noise, RF noise, and

shielding to eliminate electrostatic noise. Sixteen accompanying diagrams include graphs of RF noise, correct shielding, mutual inductance noise, and bypass capacitors to reduce RF noise effects.

**Analog Devices**, Literature Ctr, 70 Shawmut Rd, Canton, MA 02021.

Circle No 461

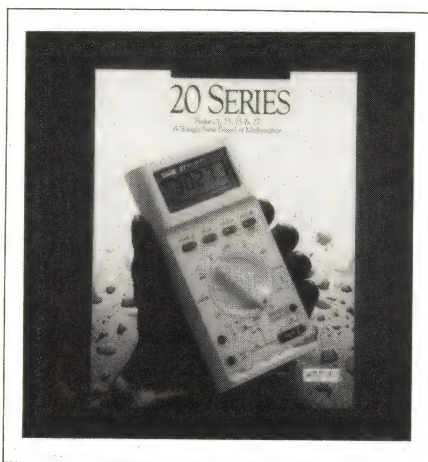

## Digital multimeters described

This 8-pg color brochure details Series 20 ruggedized digital multimeters and explains the design and construction of the instruments. It also includes information on typical applications, a specification table, and a listing of accessories for the meters.

**John Fluke Mfg Co Inc**, Box C9090, Everett, WA 98206.

Circle No 462

## Guide lists semiconductor and IC products

The *Designer Selection Guide* (#R15) describes the company's semiconductor and IC products. It details representative items in each product family, and one section details packaging options. Among the products covered are microprocessors, microcontrollers, peripheral devices, dynamic and static RAMs, and EPROMs. Also included are gate arrays, coder/decoders, bipolar and logic families, and linear ICs, as well as gate turn-off modules, power

**DIN 41612**  
• **USA Market**  
• **Leader**  
• **Broadest Product Line**

## Winchester Electronics

... for Euroconnectors conforming to DIN 41612 & VG95324

### INCLUDING

- Std. DIN • Inv. DIN •
- Multi-Purpose • Ribbon Cable
- American Expanded -
- Std. & Inv. • System 12
- 4 Row HD ...

available in Solder, Wire-Wrap & C-Press® compliant pin terminations.



**For more information, or a DIN catalog...**

CALL OR WRITE:  
(203) 755-5000  
1-800-262-2678

ADVERTISING Dept.

**WINCHESTER ELECTRONICS**  
Litton

400 Park Road, Watertown, CT 06795




## LITERATURE

MOSFETs, and optoelectronic devices.

**Hitachi America Ltd**, Semiconductor & IC Div, 2210 O'Toole Ave, San Jose, CA 95131.

Circle No 463

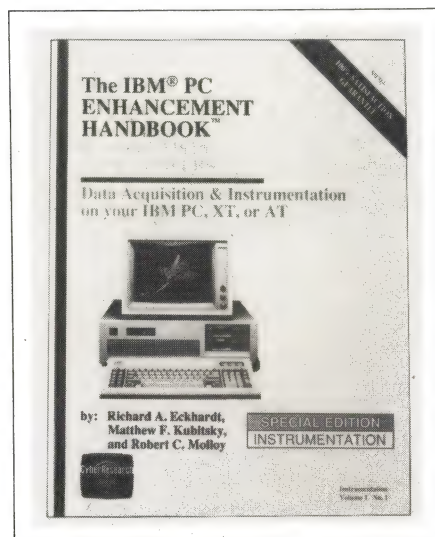


### Handbook features PC-based data-acquisition products

The data-acquisition and instrumentation special edition of *The IBM PC Enhancement Handbook for Scientists and Engineers* includes tutorial information and descriptions of products and systems for data acquisition, instrumentation control, and process control based on the IBM PC, PC/XT, and PC/AT.

The instrumentation section of the handbook covers such topics as controlling instruments through use of the IEEE-488 bus or through serial communications (RS-232C, -422, and -485). It also provides descriptions of hardware and software products that allow you to convert the IBM PC to various laboratory instruments. The data-acquisitions section of the handbook includes information on systems and components for both local and remote applications. \$9.95.

**CyberResearch Inc**, Box 9565, New Haven, CT 06536.

INQUIRE DIRECT

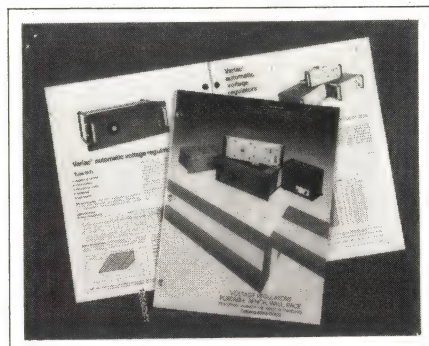


### Voltage-regulator catalog covers five categories

This voltage-regulator catalog provides specs, schematics, and applications information on the company's regulators. The multicolor

publication details products in portable, bench, wall-, rack-, and panel-mount versions. In addition, it describes how the standard units can be altered and provides information on custom items.

**Technipower**, Box 222, Commerce Park, Danbury, CT 06810.

Circle No 465

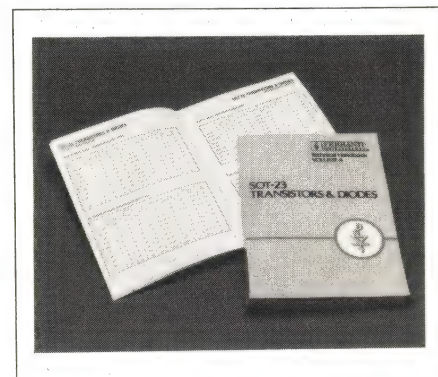

### SOT-23 parts highlighted

This 270-pg technical handbook, which covers the manufacturer's SOT-23 transistors and diodes, provides both general information on the SOT-23 package and product-specific information. The technical-data section provides fully characterized data on more than 140 device types. The handbook also includes a product index of JEDEC and Pro-Electron types, listing commercial and quality-assured parts.

## EPROM PRODUCTION EFFICIENCY: \$995.00

14 DAY FREE TRIAL  
OFFER



GANGPRO-8 - meets time-critical production needs. This upgraded unit simultaneously programs eight EE/EPROMs with speed, reliability, and accuracy. Non-technical personnel can efficiently learn to operate GANGPRO-8 within 30 minutes.

- Programs 2716-27512, 27513 (incl. A versions), 68764 & 87C64/128
- Verifies at 4.75, 5.00, and 5.25 VCC margins
- Isolates and displays the location of any failures

- Fast, intelligent algorithms
  - RS232 option for up/download to any computer/ includes IBM PC software
- Compare features, compare price; then make the Logical choice.

### IT'S LOGICAL

For details, write or call:  
1321 NW 65th Place  
Fort Lauderdale, FL 33309;  
(305) 974-0967;  
toll free 800-331-PROM  
TELEX 383142

## LOGICAL DEVICES INC.



# Now, Desktop Transceiver ATE From Anritsu.



## **MS555A Radio Communi- cation Analyzer**

The Anritsu MS555A puts ATE — for checking out radiotelephones, FM transceivers, wireless telephones and more — right on your desk.

To begin with, this one compact unit is packed with the programmable instruments you need for testing FM mobile radio; a 25 — 1000MHz signal generator that's perfect for checking out narrowband 400MHz and 900MHz systems. A frequency counter (10Hz — 1000MHz), FM deviation meter, and AF level meter. An RF power meter handles up to 60 watts CW, and there's also an AF

oscillator. There's even an auto-ranging 1mV to 50V DC voltmeter.

But the best part is that all this can be controlled *automatically*. You simply tell the Analyzer what tests you want performed. Then press the START key. The internal microprocessor handles everything from then on; the entire sequence is performed automatically. It's held in memory, too, so you can make the same tests over and over again, if you like. Add the optional printer to get hard-copy convenience.

Field use? Of course. GPIB option? You bet. Want to learn more? Contact Anritsu.

# Anritsu

**WE'RE ON THE MOVE. WORLDWIDE.**

**ANRITSU CORPORATION** 10-27, Minamiazabu 5 chome, Minato-ku, Tokyo 106, Japan Phone: (03) 446-1111 Telex: 0-242-2353 **ANRITSU ELETRÔNICA S.A.** Av. Passos, 91-Sobrelas 204/205-Centro, 20.051-Rio de Janeiro-RJ, Brasil Phone: 221-6086, 224-9448 Telex: 2131704 ANBR **ANRITSU AMERICA, INC.** 128 Bauer Drive, Oakland, NJ 07436, U.S.A. Phone: 201 337-1111 Telex: 642-141 ANRITSU OKLD **ANRITSU EUROPE LIMITED** Thistle Road, Windmill Trading Estate, Luton, Beds, LU1 3XJ, U.K. Phone: (STD0582)418853 Telex: 826750 ANRSEU G **ANRITSU ELEKTRONIK GmbH** Uhländstrasse 9, 4000 Düsseldorf 1, F.R. Germany Phone: (0211) 682424 Telex: 8584904



Short-form selector tables that group devices by application are provided. A section on quality and reliability and a description of tape-and-reel specifications conclude the treatment.

**Ferranti Electric**, Semiconductor Div, 87 Modular Ave, Commack, NY 11725.

**Circle No 466**

## Handbook offers 102 linear-IC ideas

*Circuit Ideas for Linear ICs*, a 34-pg handbook, offers 102 circuits based on linear ICs and MOSFETs. The handbook is divided into nine sections of ideas that can be applied to industrial and consumer equipment. Included are sections on timing, measurement, modulation,

power control, data conversion, communications, alarm monitoring, and other topics. A schematic illustrates each circuit, and a description of the circuit's function is provided.

**RCA Solid State Div**, Box 2900, Somerville, NJ 08876.

**Circle No 467**

## Guide aids in network planning

This planning and international-standards guide aids designers who use the manufacturer's local- and wide-area network products. The guide features planning information on PrimerNet, a distributed networking facility that provides local- and wide-area networking for all of the company's systems. Also provided is information on Ringnet, a local-area network, and guidelines on international LAN standards. The 16-pg guide is illustrated with schematics and charts.

**Prime Computer Inc**, Sales Leads Group, M/S 15-60, Prime Park, Natick, MA 01760.

**Circle No 468**

## Guide lists southern California businesses

Details of more than 2700 high-tech companies are included in the first edition of *Rich's High-Tech Business Guide to Southern California*. The guide, a sister publication to the Silicon Valley edition, provides the names of key executives, addresses, phone numbers, year established, product descriptions, and number of employees. Also included are more than 20 maps of areas between San Diego and Santa Barbara. \$98.50 includes shipping; in CA, add \$6.65 sales tax.

**Business Directories Inc**, 101 First St, Suite 426, Los Altos, CA 94022.

**INQUIRE DIRECT**



**Opening  
the door is not as  
hard as you think.**

You've heard that surface-mount technology is complicated, mysterious, frightening, expensive to get underway . . . and absolutely essential if you're going to compete with the smaller, better performing, lower cost electronic products that are being designed today.

But, don't despair. Now there's a one-stop surface-mount technology center: Interplex Technologies. We'll eliminate the complication, mystery, fear and most of the start-up expense of SMT for you, quickly and cost-effectively.

Our product lines include standard and custom memory modules, interconnects for changing LCCs to leaded chip carriers to eliminate TCE, and complete Type I, II, and III SMT assemblies. In addition, we offer comprehensive design, prototyping, and testing services, plus

the capability to supply small, medium, and large production quantities. When you're ready for in-house manufacturing, we'll assist you in developing the most efficient systems and even provide specialized automated assembly equipment, if you need it.

We'll make opening the door to SMT easier and less costly than you think. Call us for some straight-from-the-shoulder talk.


Contact Walter Bailey, Interplex Technologies Corporation, 381 Park Street, Hackensack, New Jersey 07602; 201/343-3156.

**Interplex  
Technologies**  
An Interplex Industries Company

**CIRCLE NO 91**



# Graphic proof of high-tech leadership.

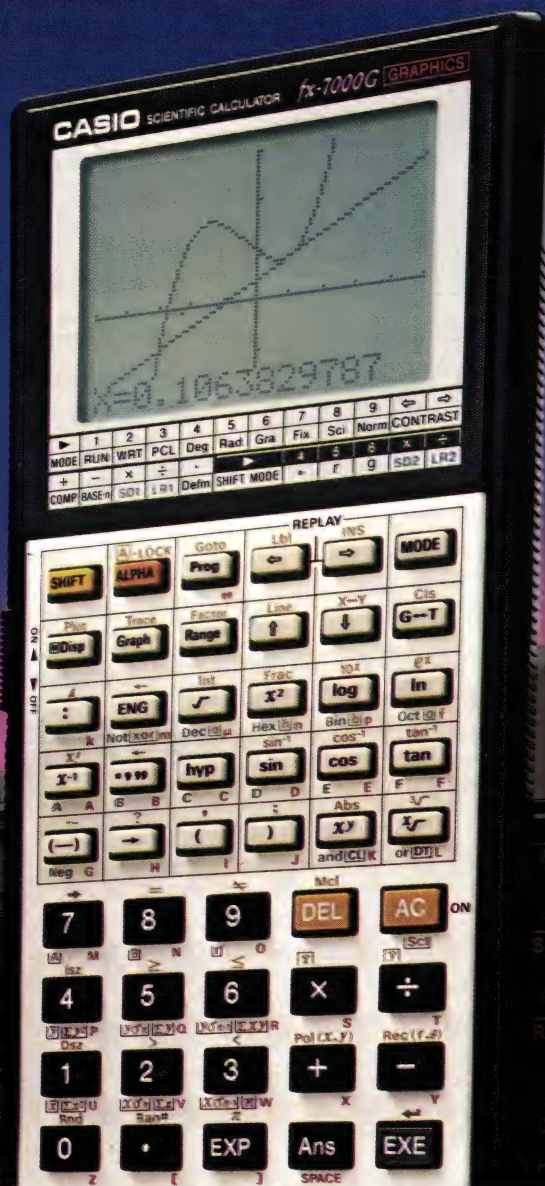

**The Casio fx-7000G \$79.95** It's the world's first programmable scientific calculator with a graphic display. The only calculator that can give form to your figures, instantly drawing graphs that represent your formulas and calculations on its big LCD screen.

And with a screen measuring 16 characters by 8 lines, the fx-7000G can display enough information for some of your biggest ideas. The formula or graph can then be stored and, when needed,

brought back for an instant replay.

The fx-7000G has 82 scientific functions—including linear regression, standard deviation, as well as binary, octal and hexadecimal calculations—making it useful in virtually any scientific or technical endeavor.

In fact, without requiring computer knowledge—or costing computer dollars—the fx-7000G, with its 422 step memory, performs many functions you'd otherwise find only on a computer.

There's ample evi-

dence of Casio's high-tech leadership throughout our entire line of scientific calculators. Our smaller-screen fx-6000G, for example, offers many of the features of our fx-7000G at even a smaller price.

If you have any doubt as to who's the leader in high-tech calculators, simply pick up an fx-7000G and draw your own conclusions.

For more information call 1 (800) 553-3338 Ext. 11.

**CASIO®**  
Where miracles never cease

Casio, Inc. Consumer Products Division: 15 Gardner Road, Fairfield, N.J. 07006

CIRCLE NO 295



# Toko Buffered Delay Lines

Protect  
your data and  
your reputation



Because the data your products will handle is priceless, Toko never shortcuts quality. Our automated assembly and 100% testing assure you of the highest reliability at the lowest possible cost.

- ☐ Available in SIP, DIP and SMT packages.
- ☐ Transfer-molded epoxy resin package provides superior environmental protection.
- ☐ Each delay line meets rigid quality control standards—100% testing with seven separate inspections during manufacture.
- ☐ Lumped Constant Delay Line and IC are integrated into one package for simplified design and assembly.
- ☐ Backed by Toko...one of the world's largest delay line manufacturers.
- ☐ Total delay times from 100 pico seconds up to 7 micro seconds  $\pm 5\%$ .
- ☐ Input/output buffering equivalent to 74SO4 (TTL compatible).

A broad range of delay values are available. For a free catalog, sample and application information contact Toko America today.

**TOKO**  
TOKO AMERICA, INC.

1250 Feehanville Drive  
Mount Prospect, Illinois 60056  
(312) 297-0070, TELEX: 724372  
FAX (Gill): (312) 699-7864

CIRCLE NO 92

# Engineered With Vision



## Built With Care

POWER-SONIC, a leading manufacturer of rechargeable batteries, offers a complete line of both sealed lead-acid and nickel-cadmium batteries, engineered to meet the toughest specifications. State-of-the-art design, meticulous quality control and time-proven performance are the reasons why engineers are specifying POWER-SONIC batteries; competitive prices and an outstanding track record for product reliability and on-time delivery have convinced buyers. For more information or a copy of our catalog, contact:

POWER-SONIC CORPORATION

3106 Spring Street, Redwood City, California 94063 USA (415) 364-5001

**POWER SONIC**

SEALED RECHARGEABLE BATTERIES

CIRCLE NO 306

## DID YOU KNOW?


1986 marks EDN's  
three decades of dedication to the  
electronics industry.

**EDN**



# Gold is second best to new RN plating technology!

**GOLD  
LOSES!**

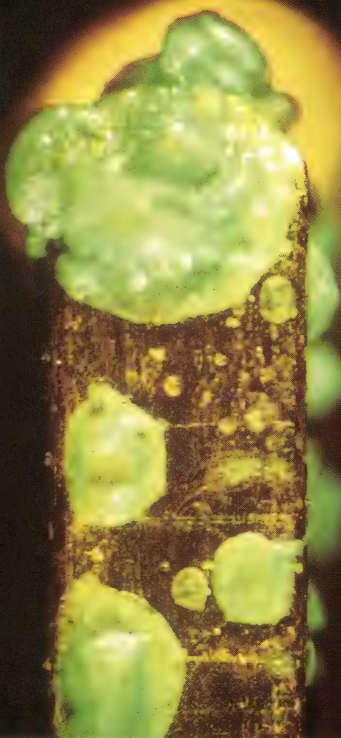


**ACTUAL MICROPHOTOS**  
of two plated header pins after  
1-hour nitric acid porosity test.

▶ **ROBEX™ plated contact (30 μ in.)**  
*Contact resistance remains constant.*  
Header pin remains bright, shiny,  
free from corrosion of base metal.

◀ **GOLD plated contact (30 μ in.)**  
*Contact resistance goes up because*  
porosity of gold plating allows  
corrosion product from base metal  
to migrate to surface.

**RN  
ROBEX™  
WINS!**

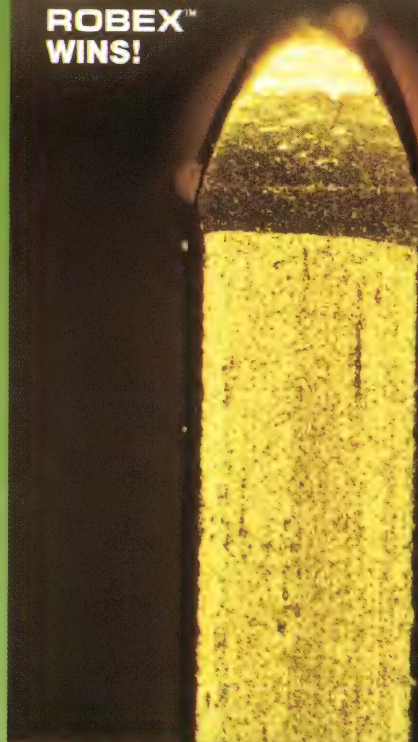

## New ROBEX™ plating puts gold to shame in punishing IDC connector reliability tests

Get ready to change your mind about the best way to achieve solid connector reliability. Gold is no longer the ultimate answer. These microphotos reveal surprising facts about the damaging porosity of gold plating. They also show how the non-porous nature of the revolutionary new Robinson Nugent **ROBEX™** palladium-nickel plating system offers a higher degree of connector reliability than gold will ever provide. Levels of reliability and stable contact resistance heretofore obtainable only through the use of high cost, thick gold plating can now be achieved with this new **ROBEX™** plating system.


This new **ROBEX™** plating system minimizes porosity, increases environ-

mental corrosion resistance, increases wear resistance and improves solderability.

**MAKE THE CHOICE!** Decide now to realize the advantage of the plating technology of the future. Call Robinson Nugent and ask us about **ROBEX™**. We'll send you a detailed technical brochure on this new revolutionary RN **ROBEX™** plating system. You may never specify costly gold plating again! Contact: Robinson Nugent, Inc. 800 E. Eighth St., New Albany, IN 47150. Phone: (812) 945-0211.



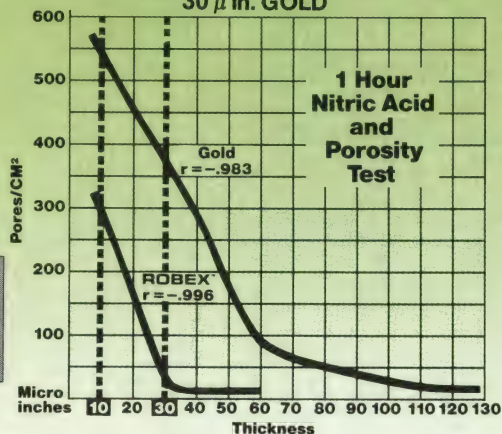**10 μ in. ROBEX™ OUTPERFORMS  
30 μ in. GOLD**



# Robinson Nugent

800 East Eighth Street, New Albany, Indiana 47150 • Phone: (812) 945-0211  
In Europe: Rue St. Georges 6, CH 2800 Delemont, Switzerland • Phone: (066) 22 98 22

CIRCLE NO 296



# MARKET FORECASTS

---

**Telecommunications Integrated Circuits (#659).** 157 pgs; \$1650; International Resource Development Inc, 6 Prowitt St, Norwalk, CT 06855.

This report covers more than 50 major competitors in the communications-IC market, including Japanese and European chip manufacturers. The report, which predicts a 30% growth rate for this market during the rest of the decade, analyzes technologies such as gallium arsenide and silicon compilation and also takes in to account Integrated Services Digital Networks (ISDN). The satellite- and military-equipment markets are already using chips designed in GaAs, but this report speculates that applications of this technology are just beginning to surface.

**Strategic Issues in Automated Production: The Challenge of Robotics and Computer Integrated Manufacturing,** by Tony Owen. 95 pgs; \$50; Manufacturing Technology Press Inc, Box 206, Lake Geneva, WI 53147.

With an assessment of the state of the art in computer-integrated manufacturing, this report discusses the economic future of robotics and computer-integrated manufacturing based on their strengths and weaknesses. The report analyzes worldwide industrial trends and their impact on current and future computer-integrated manufacturing. It includes information on automation, robot technology, vision systems, CAD/CAM, and the economics of the market.

**Digital Signal Processor (DSP) Market Report.** \$500; Business Development Group Inc, Box 3044, Stanford, CA 94305.

This report offers a review of the DSP market, products, competi-

tion, and technology, giving market forecasts and estimated competitive market share for the period between 1985 to 1990. It discusses advances in chip technology that, combined with the rising density and speed of VLSI circuits, is creating a new generation of digital signal processors. The success of the DSP market is based on the significant benefits and cost performance that these products provide in a wide range of real-time applications. The report places the products in seven categories: single-chip processors, specialized circuits, building-block circuits, data-flow and systolic-array devices, chip-sets, boards, and development systems.

**Multiusers  $\mu$ C Systems Market Through 1990.** \$2450; Venture Development Corp, Box 9000, Natick, MA 01760.

This report examines the US market for multiuser  $\mu$ Cs and LAN-based systems through 1990. It discusses strategic guidelines and recommendations for qualifying OEMs and VARs, how to select vertical markets, and how to develop an effective promotional marketing program. Results are based on a nationwide survey of OEMs/VARs and corporate users of multiuser systems, in which questions about  $\mu$ C-feature preferences, marketing and service requirements, vertical market applications, and future purchasing plans were asked. Profiles and competitive positions of 50 major industry participants are included.

**Connector Industry Forecast II.** 1600 pgs; \$15,000; Gnostic Concepts Inc, 951 Mariner's Island Blvd, Suite 300, San Mateo, CA 94404.

This report focuses on US consumption of 85 distinct types of con-

nectors, along with future market and technological directions for each connector type. Connector consumption is divided into 51 categories of electrical/industrial and electronic equipment producers with company profiles of 67 US and foreign connector and IC-socket manufacturers. The report describes the technological outlook for high-density designs, the impact of surface-mount technology, connector applications for EMI/RFI, and new materials used in manufacturing connectors. A fiber-optics update is also included, along with a 2-volume database, which presents value, quantity, price, and input/output coefficients by connector type for the 1984 to 1990 forecast period.

**Optical Memory's Impact on Magnetic Storage and Computer Systems Architecture.** \$1250; Electronic Trend Publications, 10080 N Wolfe Rd, Suite 372, Cupertino, CA 95014.

This report focuses on the development of optical data-storage technology and examines trends in CD ROM, write-once, read-many optical disk players and systems, and various types of erasable optical-disk products. The report reviews the problems that each optical technology must face and solve in order to become established; it also discusses the issues that have impeded the technology's growth in general. The study investigates current optical applications that represent attractive alternatives to paper-based and magnetic storage-based systems already in use. In addition, the key manufacturers who are shaping the market are discussed.





# SWITCH MODE MADE SIMPLE

## With Coilcraft pre-engineered magnetic components and experimenter's kits

Coilcraft makes building your own off-line switching power supplies and DC-DC converters easier than ever.

We're the single source for *all* your switching magnetics. And we're ready to help you at every step, from prototype right through to production.

Start with our handy experimenter's kits that put a wide range of component values at your fingertips. We not only provide detailed application notes, but Coilcraft engineers are as close as your phone, ready to help you solve any design problem.

As you move into production, you'll enjoy big cost savings thanks to our standardized configurations and our domestic and off-shore production capabilities.

For our latest switch mode magnetics catalog, circle the reader service number below or call Coilcraft at 312/639-6400.

## EXPERIMENTER'S KITS

To order call 312/639-6400.

### Common Mode Line Chokes

Current: 1/4-9 amps RMS  
Inductance: 508  $\mu$ H-10.5 mH  
8 styles, 2 each  
Kit P202 \$100

### Current Sensors

Sensing range: 0.5-35 amps  
Freq. resp.: 1-100 kHz, 50-400 Hz  
Transformer and sensor-only versions  
8 styles, 15 total pieces  
Kit P203 \$50

### Base/Gate Driver Trans.

Inductance: 1.5 mH Min.  
Frequency: 10-250 kHz  
2 single, 2 double section, 2 each  
Kit P204 \$50

### Power Filter Chokes

Current: 3, 5, 10 amps  
Inductance: 5-300  $\mu$ H  
18 styles, 48 total pieces  
Kit P205 \$75

### Mag Amp Toroids

Current: 1, 5 amps  
Volt-time product: 42-372 V- $\mu$ sec  
6 styles, 2 each  
Kit P206 \$100

### Power Switching Trans.

Coilcraft offers a variety of configurations with single and multiple outputs, and power ratings up to 800 W. For samples, please call 312/639-2361.




*Coilcraft*

Dept. D, 1102 Silver Lake Rd., Cary, IL 60013 312/639-6400

CIRCLE NO 297



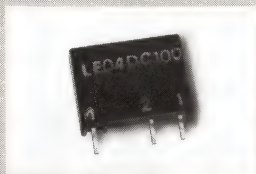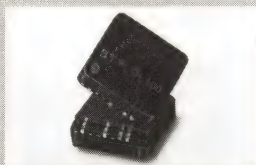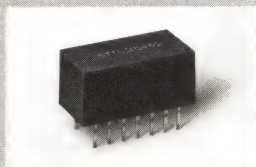**- Superstable  
- Superaccurate  
- Superrepeatable  
delay-line  
performance.**



Only Technitrol makes a selection of TTL active delay lines with 5 ns to 2000 ns delay intervals that are  $\pm 1$  ns or  $\pm 1\%$  repeatable over  $-55^\circ$  to  $+125^\circ\text{C}$ , at rated voltage input  $\pm 10\%$ .

So if you need a delay line with such good temperature and voltage stability, you'd save time by giving us a call first.

This is just a sample of what we can do with delay lines—not custom products, but standard production models. For high-rel military applications, commercial applications, flat-pack, slim-pack, surface-mount, and chip-carrier modules, contact Technitrol. We offer the best selection of high-performance lumped-constant active and passive delay lines.

## Technitrol, Inc.

1952 E. Allegheny Avenue  
Philadelphia, PA 19134 USA  
(215) 426-9105 • Telex 834245

active and passive delay lines  
• pulse transformers • Manchester  
encoder/decoders • data bus couplers  
• pulse-width regulators • high-  
voltage, Scott T, and ferroresonant  
transformers

8153

# NEW BOOKS

**The Professional Microcomputer Handbook**, by Ivan Flores. 881 pgs; \$49.95; Van Nostrand Reinhold Co Inc, New York, NY, 1985.

After an overview of microcomputers, this book presents a tutorial on four aspects of the subject: hardware, operating systems, programming, and application packages. Each section defines technical terms, explains how various mechanisms and programs work, and compares competitors' features. All types of personal computers are catalogued according to the size of their memory, their software, and their control systems. The computers' printed-circuit boards are also detailed. Further, design and coding with detailed instruction about MBasic and Basica, Pascal and PL/I are included. A general discussion on operating systems is supplemented by specific information on CP/M, PC-DOS, and MS-DOS.

**Inside the Technical Consulting Business: Launching and Building Your Independent Practice**, by Harvey Kaye. \$19.95; John Wiley & Sons Inc, New York, NY, 1986.

This book defines consulting and describes what you must do to become a good technical consultant. The author explains how you can use your abilities and skills to be a successful consultant, and he gives marketing tips to assist you to that end. A self-appraisal quiz is included to help you decide if consulting is the right career for you.

**Patenting and Marketing Your Invention**, by Bernard Rivkin. \$34.95; Van Nostrand Reinhold Co Inc, New York, NY, 1986.

This guide provides the legal and business information that inventors need to know in order to protect their products. It contains facts on

the legislation governing the protection of ideas, including the Presidential order of November 1984; fee schedules for patents and trademarks are listed. Other topics include patent searches, selecting patent attorneys and agents, the licensing and sale of patents, and guidelines on how to get a patent for your computer software. It discusses financing and developing an invention, including information on venture capital, research and development tax, and R&D limited partnerships. An appendix lists useful sources and services, completed patents, and trademarks.


**The C Primer**, by Les Hancock and Morris Krieger. 2nd ed; 303 pgs; \$17.95; Byte Books/McGraw-Hill, New York, NY, 1986.

This book examines the various features of the C language, demonstrates how to read and write programs written in this computer language, and shows how C can be used as an alternative to other high-level languages. This second edition contains information on bit fields and masks, functions that operate on single bits, and the development of a line-by-line sorting program. The book also contains extended treatment of subjects such as pointers, the C preprocessor, structures and unions, and the file I/O. Included are 129 complete program examples in C.

**Contemporary Electronics Circuits Deskbook**, edited by Harry L Helms. 253 pgs; \$29.95; McGraw-Hill Book Co, New York, NY, 1986.

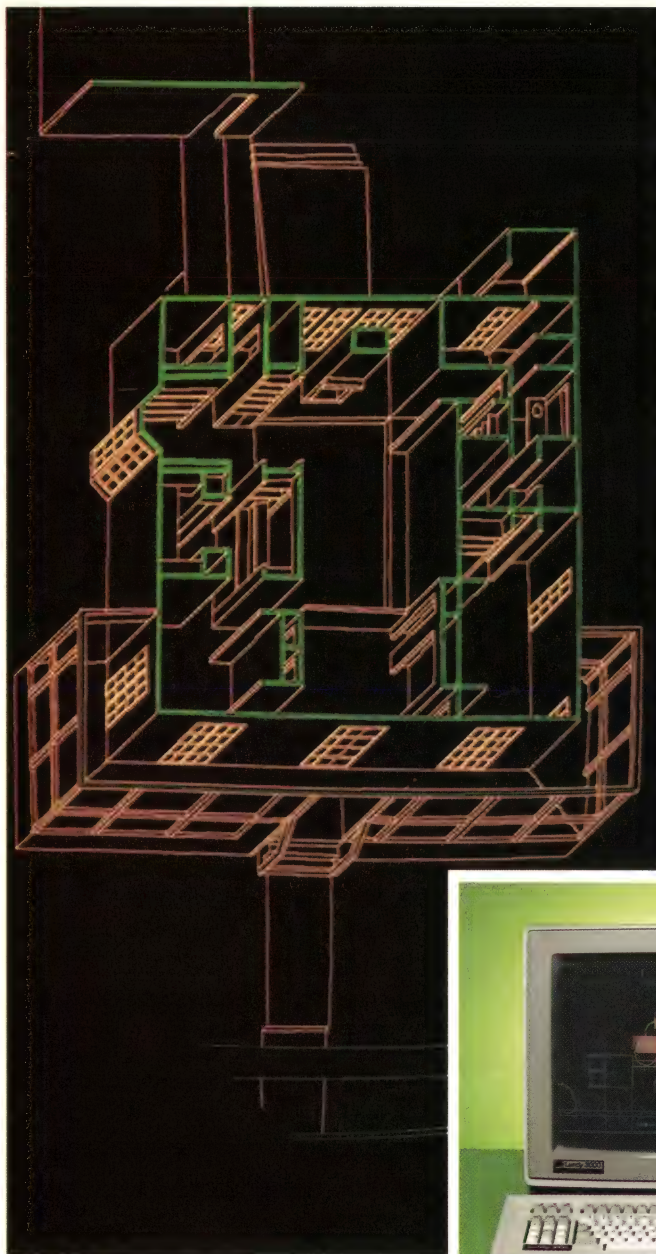This reference guide is a compilation of circuit designs and applications from recent electronics magazines, application notes, and data books. Each circuit diagram was reproduced directly from the original source. Topics examined include





## Look at What Lundy & Design Graphix™ Are Doing to PC-Based CADD.

Generate a design on the Lundy 3000 workstation and then compare it to a PC-based system. The differences may well amaze you. Lundy 3000 displays your work with a resolution that's simply unattainable with PC-based systems.

### Less Strain on Engineers

The sharpness and clarity of the Lundy 3000 permit very detailed, high quality design with less strain on your engineers. This results in overall productivity increases for you and your design staff. Lundy 3000 is

ideal for those who can benefit from a graphics system but are reluctant to invest the large sums of money required for advanced systems.

### Makes PC's Look Like Toys

When packaged with ESC's Design Graphix™ software, Lundy 3000 becomes an advanced, low cost CADD system with a level of responsiveness that can make PC-based systems look like toys. The flexible, high performance capabilities of Lundy 3000 make it very hard to grow out of. And that's a serious

consideration when purchasing a graphics system.

So if you're looking for a graphics system that's low in cost yet high on performance, look to the Lundy 3000 and see how inexpensive quality graphics design can be. Contact: Graphics Marketing Lundy Electronics & Systems, Inc. One Robert Lane, Glen Head, N.Y. 11545. (516) 671-9000.



**LUNDY**

DESIGN GRAPHIX™ is a trademark of Engineering Systems Corporation, Baton Rouge, Louisiana.

EDN April 17, 1986

CIRCLE NO 298

363



# TAILORED TUBES

There's only one place to go for seamless magnetic shield tubing: M<sub>μ</sub>Shield. We customize jobs to your specifications and back them with our 35 years of experience.

We design and build shields for electron microscopes, CAT and PET scan machines, computer terminals, and a host of other applications. We also make standard shields for photomultiplier cathode ray and storage tubes. Seamless shielding materials are available from stock. Our own heat-treating facility gives fabrications superior permeability and low shock sensitivity.



Find out what M<sub>μ</sub>Shield can do for you. Write or call us for more information.

**M<sub>μ</sub>SHIELD  
COMPANY**

DIVISION OF BOMCO, INC.  
121 Madison St.,  
Malden, MA 02148-6890  
Phone 617/321-4410

## NEW BOOKS

transmitters and receivers, audio circuits, test and measurement, video and television, digital circuits, automotive circuits, and telephone circuits. It provides circuit designs for such applications as frequency-synthesis circuits, single-sideband circuits, timer circuits, modem circuits, voltage-regulation circuits, and optoelectronic circuits. Descriptive paragraphs for each circuit give component values, construction tips, and restrictions on use.

**International CAD/CAM Software Directory**, edited by Philip C Flora. 180 pgs; \$35; Technical DataBase Corp, Conroe, TX, 1986.

This directory provides a detailed technical description of manufacturing and engineering graphics packages. Some of the applications covered include data acquisition, engineering calculation, inventory, computer-aided design, manufacturing management, operating efficiency, and computer-aided manufacturing. Each listing includes information such as the required hardware and software environment, minimum memory requirement, list price, documentation provided, availability of updates and source code, warranty policy, technical support provided, and delivery time. A glossary of terms and two indexes, one by application and one by vendor, are also included.

**Patent It Yourself**, by David Pressman. 421 pgs; \$24.95; Nolo Press, Berkeley, CA 94710, 1985.

This step-by-step guide shows you how to obtain an effective US patent. It includes an overview and comparison of patent, copyright, trademark, and trade secret laws. The book also contains information on how to assess the commercial potential of an invention, the specific criteria used by the US Patent Office for granting a patent, and

how to draft and file a complete patent application. This book will also tell you how to enforce and maintain your patent.

**Software Engineering Handbook**, by the staff of General Electric Co. 224 pgs; \$59.50; McGraw-Hill, 1985.

How to develop software systematically, document it during development, and improve its quality are some the topics of this book. It contains advice on how to plan, estimate, budget, and schedule software engineering, and how to apply up-to-date techniques to each phase of the process. Topics covered include defining the scope of a project, analyzing the functions and performance requirements, developing both an architectural representation and a procedural representation of the software, and using a programming language to transform the design representation into a functionally equivalent program. The book also outlines how to test software for latent defects and how to validate the software against the requirements. A section on small projects explains how to abbreviate some steps in the engineering process and shorten the necessary documentation for smaller projects.



# There's a name for adding value to your good name.



## It means the end of battery-related product complaints.

And the dryfit® name means you'll never again have a good design blamed when a questionable battery was at fault. dryfit delivers the longest, most reliable service life of any sealed lead-acid battery in the world. From four to eight, or even more absolutely maintenance-free years, depending on the model needed for your cycling or float application. For example, **Sola Electric** recently chose our 12 volt 28Ah battery for their SPS and UPS equipment.

To add even more value, consider that you won't face position-related design problems. dryfit batteries are made to operate and recharge in any position—even upside down! They are also deep discharge protected for up to 30 days and have a low self-discharge rate of approximately 0.1% per day at 20°C.

If that's still not enough to convince you,

consider these advantages. Leakproof construction, resealable safety vents, low space requirement, operation over a wide temperature range, simple "no fill or charge needed" installation. And the shock and vibration characteristics to survive the abuse of an armored tank.


### Why trust us?

Just check our credentials! dryfit batteries are made by Sonnenschein, inventor of the original gelled electrolyte battery system. With more different battery types, dryfit outnumbers all the competition. No wonder it has been Europe's most popular battery for decades!

And now, adding value to your good name is as easy as calling ours:
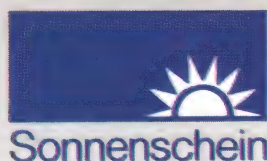
## 1-800-4dryfit

Exclusive Canadian Agent:  
Duracell, Inc., Mississauga



P.O. Box 339  
300 East Johnson Avenue  
Cheshire, CT 06410  
(203) 271-0091



**O.K.,** you're a design engineer with more than your share of dragons to slay day in and day out.

You want design flexibility. You want power range. You want a standard of reliability second to none. And you want a power supply company that's been around the block.

Quite simply, you want us.

We're Astec. And we've been in the rigors of the switching power business for over ten years. We've sold over 9 million switching power supplies to heavyweights in the computer, telecommunications and office automation industries.



And yes, while 9 million is a nice round number, we at Astec see our role as more than simply shipping a lot of product.

We're here to work right along with your specific requirements by providing over 30 standard models ranging from 25 to 400 watts and custom power supplies from 25 to 1500 watts.

And reliability? Well, to be honest, this is where we really shine.

Our incredible low product failure rate is the result of outstanding quality assurance. You'll find there's an average of 80,000 hours of mean-time-between-failures (MTBF) and less

than .3% field failure rate with zero defects as the final goal.

So when you're ready for a company that's setting the standard in power supplies, a company that acknowledges the importance of power range and design flexibility, a company that's here to stay, simply call Astec at (408) 748-1200 or the distributor nearest you.


We'll show how to slay your design dragon.



**ASTEC USA**  
2880 San Tomas Expwy., Suite 200  
Santa Clara, CA 95051  
(408) 748-1200

**Power Is Only Part Of It.**

# POWER HUNGRY.

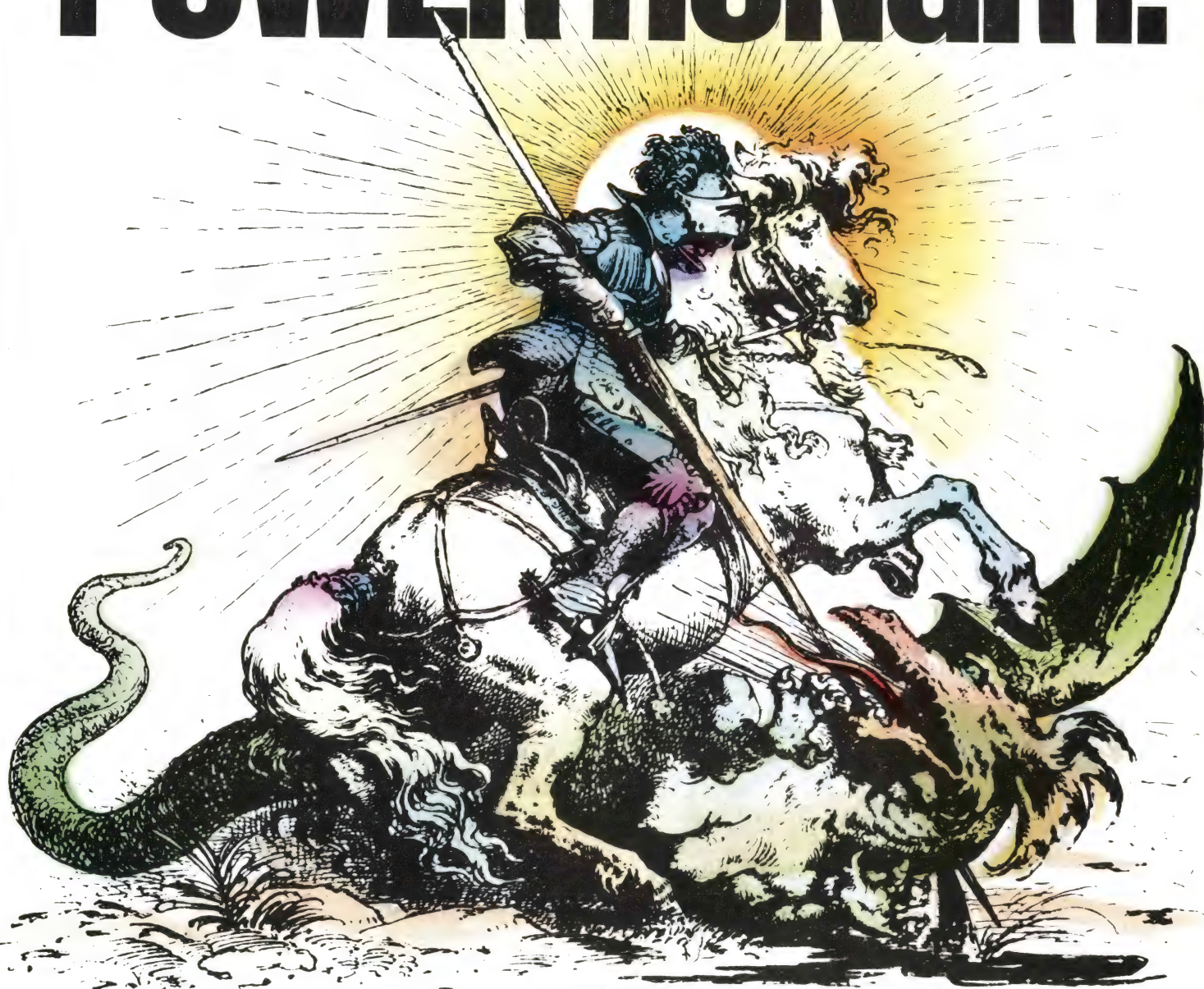

CIRCLE NO 300



## Employees find their pension benefits often add up to unkept promises


Deborah Asbrand, *Staff Editor*

At first glance, private businesses' pension funds appear to be overflowing with money. The assets of private pension funds in 1984 totalled nearly \$1 trillion, according to the Employee Benefit Research Institute, a Washington, DC, research organization. And new money continues to stream into the funds at a staggering rate: The Department of Commerce's Bureau of Economic Analysis estimates that, in 1984 alone, companies contributed \$68 billion to their employees' pension funds.

With billions of dollars flowing into pension coffers each year, it would seem that all employees who qualify for a pension would be well provided for. Yet nothing could be further from the truth. Tearing at the fabric of conventional retirement plans are social, economic, and political changes that have strained the pension system to the point where it no longer meets the needs of many workers.

The traditional retirement plans still in effect at many companies have become dusty relics, reflecting the work habits of a work force that has long since changed. Structured to reward long-time employment with one company, the plans have proven inadequate in providing a comfortable retirement income for employees who work for several employers throughout their careers.

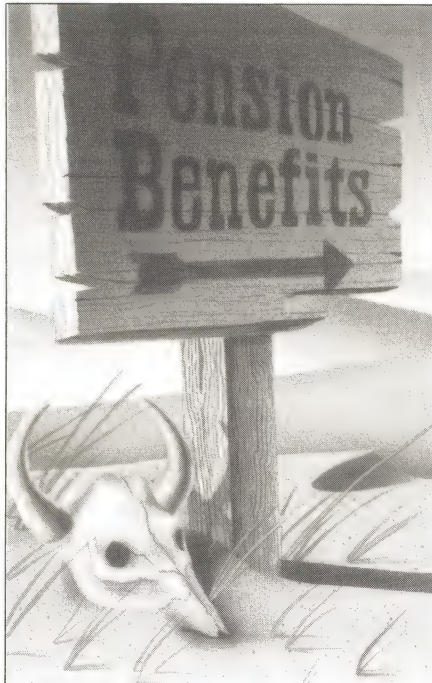Conventional retirement plans credit employees with a percentage of their salary for each year they work for the company. To take a simple example, employees in a pension plan might be credited with 1½% of their salaries for each year they worked for their company. An



employee who worked for an employer for 40 years consequently receives a pension that equals 60% of one year's average salary. Typical pension plans are actually more complex, factoring in what are referred to as "career averages" or "final averages" to determine the benefit.

When workers spent their entire careers with one company, they were able to fulfill their employers' vesting requirements to qualify for a pension. But employees today rarely spend their careers working for one employer. And even if they are fortunate enough to work for one employer long enough to qualify for a pension or become vested, many workers find that inflation has eaten away at the money that was set aside for them, leaving them with a benefit much smaller than they had anticipated. In addition, improved health care has extended average life spans so that more peo-

ple now live to retirement age and beyond. A longer life span means a pension that's effectively smaller by being distributed over more years.

Although private businesses are not required to provide pension plans for their employees, most do offer some kind of retirement benefits. To take the electronics industry as an example, more than 87% of respondents to the IEEE 1985 US Member Salary and Fringe Benefit Survey said they worked for employers who provide pension coverage. Companies keep a watchful eye on the balance sheets, however, and are usually reluctant to bear the costs incurred by expanding their retirement plans to meet changing conditions. As a result, legislative reforms that would aid workers are strongly opposed by industry lobbying groups.

Business groups view their voluntary participation in a pension plan as laudable, says Ann Moss, deputy director of the Pension Rights Center in Washington, DC. Consequently, they take a dim view of any federal attempts to regulate private pension funds. "If the government forces them to make too many changes that they consider expensive," says Moss, they threaten to eliminate their plans.

### Widespread corporate abuses

Inflation, improved health care, and frequent changes in employment are not the only factors that conspire to erode workers' pension benefits. Long a target for corruption, wealthy pension funds have become the subject of widespread corporate abuses in recent years, to the detriment of many workers. A current practice that has caused alarm among workers and govern-



# PROFESSIONAL ISSUES

ment officials is for companies to close down their employees' pension plans to gain access to interest earned on the funds.

When the stock market and interest rates began to soar in the early 1980s, many pension funds swelled far beyond their projected sums. Plan sponsors saw the overfunded pension plans as a source of extra income for the company. But the law prevents an employer from gaining access to a pension fund's so-called surplus assets unless the plan is terminated. So to fulfill their legal obligations, companies cancel the plan, buy annuities for the plan's participants, and then pocket the remaining interest sums.

The retirement plans that replace the cancelled plans often are based on individual contributions. In some cases, workers who were vested under the cancelled plans carry none of their vesting status into the replacement plans and have to begin accruing retirement benefits all over again.

Such maneuvers are neither sanctioned nor prohibited by the Internal Revenue Code, and companies have found a legal loophole. They can terminate plans when "erroneous actuarial assumptions" have been made, and the burden is not on them to prove that actuarial assumptions are in error. The practice of terminating healthy plans, known as asset reversion, has become so widespread and attracted so much attention that the Department of Labor has appointed a task force to study the problem. The task force is expected to announce its recommendations this spring.

## Job mobility hinders EEs

The problems engineers face in building retirement income are representative of those faced by employees in many industry sectors. Ben Leon, former chairman of the IEEE Pensions Committee, sees engineers' job mobility as their greatest obstacle in accumulating retirement income. Because many

engineers work for several employers throughout their careers, they frequently do not work for one company long enough to qualify for the traditional pension plan and begin earning retirement credits.

---

*Because many engineers work for several employers throughout their careers, they frequently do not work for one company long enough to qualify for the traditional pension plan.*

---

The 1974 Employee Retirement Income Security Act (ERISA) made some progress in reducing vesting requirements. Before ERISA was passed, vesting requirements at some companies stretched to 15 or 20 years. ERISA mandates that employees become vested in pension plans after no longer than 10 years with a company.

ERISA was a boon to millions of workers. The Bureau of Labor Statistics reports that in 1972, 32% of workers whose employers offered pension plans were vested in the plans; by 1983, that figure had risen to 48%.

Still, despite ERISA's improvements, Leon argues that 10-year vesting is too long for engineers. He points to an IEEE survey of its members that showed the average length of time an IEEE member works for an employer is seven years. During Leon's tenure as chairman, the IEEE testified in support of 1-year vesting before a Senate committee on aging in June 1985.


In testimony he gave at the same hearing, engineer Ron Sprague related to committee members the consequences of the direction his career has taken. "I have pursued a mobile career in engineering, having an average time per employer of

approximately five years..." Sprague testified. "In each instance of employment change, I felt that the changes I made were necessary and desirable from a career perspective. Unfortunately, the price my wife and I have paid for this mobility is the forfeiture of opportunities to accrue substantive retirement benefits..."
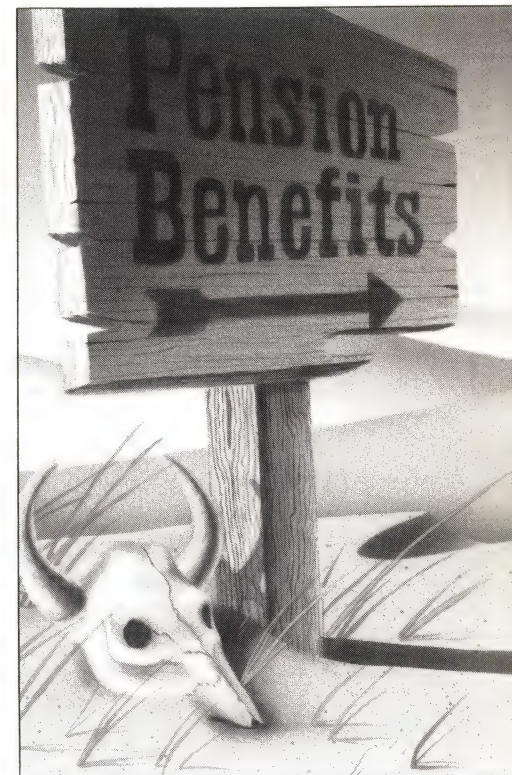
## Defined-contribution plans

Shortened vesting periods would qualify more engineers for the traditional pension plans, known as defined-benefit plans, that credit employees for each year they work for the company. But a better plan for engineers, says Leon, is the defined-contribution plan.

Under the terms of a defined-contribution plan, an employee contributes a certain amount of money to the fund. But the plans' rules vary: Some companies match a percentage of the employees' contributions, some allow employees to choose among several investment options, and some permit employees to take all of the funds that accrued to their account when they leave,





# PROFESSIONAL ISSUES

while others require that the funds remain in the company's account until the employee reaches retirement age.

"The best thing for engineers and professionals would be a system whereby all pensions would be fully vested, defined-contribution plans," Leon says. Vesting periods for defined-contribution plans are shorter than for typical pension plans—generally two to six years, he says. In some cases, individuals have the option of choosing to invest the money in stocks, low-risk mutual funds, or some combination of the two.

## Risks and uncertainties

But there are disadvantages to defined-contribution plans. The funds are not insured, as defined-benefit plan funds are, by the Pension Benefit Guaranty Corp. In addition, the defined-contribution plans incur added uncertainty for employees because there is no formula with which to calculate the final sum. Upon retirement, there is no fixed monthly benefit, only a lump sum from which to draw on.

Another disadvantage to defined-

contribution pension plans is that, at some companies, they are no more than the savings plans allowed by section 401(k) of the Internal Revenue Code. The 401(k) plans, as they're known, allow employees to contribute a percentage of their pretax income to an account in their name. No taxes are paid on the money in the account until it is withdrawn. Although 401(k) plans provide an incentive for saving money, they can't be considered true retirement plans because individuals are allowed to borrow from the account after a specified amount of time.

It is a misnomer for companies to institute 401(k) savings plans and refer to them as retirement plans, says Moss. The trend toward such "do-it-yourself" pension plans, she says, is one of the major problems facing pension participants. "The 401(k)s are not pension plans; they're tax shelters and savings plans," says Moss. Jack Andresen, current chairman of the IEEE Pensions Committee, calls the use of 401(k) plans as retirement plans "a perversion of the government's pur-

pose" in permitting the tax-free accounts. "If it's going to be a true retirement plan, you can't allow people to withdraw money, thereby making it simply a savings plan."

## Pension-reform legislation

Congress has two pension-reform bills before it, one of which addresses the problem of 401(k) plans that masquerade as retirement plans. A bill sponsored by Senator John Heinz (R-PA) and Congressman William Clay (D-MO) would eliminate the option of withdrawing money from a 401(k) account that is intended to be a retirement plan. The bill would also shorten the vesting period from the current 10-year limit to five years.

The Heinz-Clay bill also targets the problem of pension integration. Integration is the practice of calculating an employee's estimated Social Security benefits and then deducting that amount from the private pension benefit. In some instances, individuals have had their entire pensions eliminated by integration. The Heinz-Clay bill would limit Social Security integration to



Thomas Szumowski

•SZUMOWSKI•



# PROFESSIONAL ISSUES

50% of an employee's pension.

The second piece of pension-reform legislation, sponsored by Congresswoman Barbara Kennelly (D-CT), also calls for 5-year vesting and limits integration practices. In addition, the bill breaks some ground in allowing employees to take their accrued pension benefits with them when they leave their employers. Kennelly's bill would allow an employee to take pension benefits of at least \$7000 and place them in a tax-free Individual Retirement Account. The concept of making pension funds "portable" begins to address the needs of mobile employees and thus has gained support from many professional quarters, including engineering.

Calling the bills "a step in the right direction," Andresen says they still fall short of a solution. He discounts the impact portable pensions will have on the futures of engineers. "Engineers are mobile, it's true. But even if you haven't been mobile, if you've merely changed jobs once in your career, then you get a fraction of what you would have received had you stayed with one company." Inflation is the real culprit, Andresen believes. He would like to see Congress pass legislation that would require pension-plan sponsors to incorporate a mechanism into their calculations that would adjust participants' pay-

ments upward to account for the effects of inflation.

"A pension is deferred compensation, not a discretionary benefit conferred by the company," he says. "There is no place for plans that discriminate against" employees

---

*"Belatedly, many engineers are finding that when it comes to retirement, they may be without benefits unless they've been investing on their own."*

---

who become vested and then leave the company. As current salaries and wages are adjusted for inflation, so too should the past earnings of vested beneficiaries, he reasons.

Even if Congress passes legislation that requires companies to restructure their pension plans, engineering representatives agree that engineers' best defense against finding themselves with little or no retirement income is their own knowledge of how pension plans work. Yet there are no two ways about it: Understanding how pensions work takes a great deal of effort. The subject of pensions is a boring one to many people. It involves complex mathematical calculations and dry

discussion about vesting, benefits, interest rates, and annuities. Consequently, it's not hard to understand why many employees are unaware of how they will fare under the present system.

"Of those [engineers] under age 50, 75% don't understand the pension system," Leon estimates. "There's no question that self-education would ease the problem. It takes some work to understand your pension. It's a very complex issue; corporations, banks, and insurance companies have experts who work full time on pension issues." Leon confesses that he had been a vested participant of his own pension plan for 10 years before he took the time to assess it, and he did so only then because he was required to make some investment choices at the time.

"Belatedly, many engineers are finding that when it comes to retirement, they may be without benefits unless they've been investing on their own," says Bob Neuman, chairman of the Engineers and Scientists Joint Committee on Pensions, which represents engineers and scientists from more than 20 technical societies.

## Unkept promises

Andresen says that one of his goals this year is to prevent more engineers from discovering too late that their employers' retirement plans are "promises they cannot keep." He has actively sought to educate as many engineers as possible through articles he has written for the IEEE's monthly newspaper, *The Institute*, and its magazine for engineering students, *Potentials*. In addition, he has given seminars on the basics of pension plans to audiences at the Wescon and Southeastcon industry trade shows.

EDN

## Guides to evaluating your pension status

More information on pensions is available in the following publications:

- *How to evaluate your pension plan* (IEEE Catalog Number UH0161-0), IEEE Service Center, 445 Hoes Lane, Piscataway, NJ 08854. \$3 for IEEE members, \$4 for non-members.
- *Pension Facts*, American Council of Life Insurance, Information and Reference Services, 18 K St NW, Washington, DC 20006. (202) 862-4000.
- *A guide to understanding your pension plan*, Pension Rights Ctr, 1701 K St NW, Washington, DC 20006; (202) 296-3778. \$3.

Section Interest Quotient  
(Circle One)

High 518 Medium 519 Low 520



# CAREER OPPORTUNITIES

## 1986 Editorial Calendar and Planning Guide

Issue Date	Recruitment Deadline	EDN Editorial Emphasis	EDN CareerNews Closing: 5/8 Mailing: 5/20
May 15	Apr. 18	Programmable Logic Devices; CAE; Communications Components; Optoelectronics	
May 29	May 2	Analog Technology Special Issue; Data Converters; Analog ICs	
June 12	May 16	Digital Technology Special Issue; Personal Computer Boards; Development Systems (CAE-related*); Computer ICs; NCC Show Preview	Closing: 6/19 Mailing: 6/30
June 26	May 30	CAE Systems; Communications ICs; Military Microcomputers; Semicustom IC Design (CAE-related*)	
July 10	June 13	Product Showcase—Volume I; IDs & Semiconductors; Hardware & Interconnection Devices; Power Supplies/Sources; Software; Literature on Computers & Peripherals, Components, Test & Measurement Instruments, International Products	
July 24	June 27	Product Showcase—Volume II; Computers & Peripherals; Components; Test & Measurement Instruments; International Products; Literature on ICs & Semiconductors, Hardware & Interconnection Devices, Power Supplies/Sources, Software	

Call today for information.

East Coast Janet O. Penn (212) 576-8049

West Coast Dan Brink (714) 851-9422

National Roberta Renard (212) 576-8048

## CAREER OPPORTUNITIES WITH MICRON TECHNOLOGY

Micron Technology, Inc., one of America's foremost DRAM supplier, continues as a leader in new semiconductor designs, development and production. Our expansion in new product lines has created special career opportunities at our Boise, Idaho facility for professionals in the following areas:

- ELECTRICAL ENGINEERS
- MECHANICAL ENGINEERS
- TEST ENGINEERS
- Q A ENGINEERS
- CHARACTERIZATION/DEVICE ENGINEERS
- EQUIPMENT SUPPORT TECHNICIANS
- CHEMICAL ENGINEERS
- PRODUCT ENGINEERS
- PROCESS ENGINEERS
- APPLICATION ENGINEERS
- DESIGN & LAYOUT ENGINEERS
- ASSEMBLY ENGINEERS

For immediate consideration and confidential review, please forward your resume and salary history to:

**MICRON**  
TECHNOLOGY, INC.

D. Keith  
Professional Recruiting  
Micron Technology, Inc.  
2805 East Columbia Road  
Boise, Idaho 83706  
208/383-4038

**"We're building our reputation on innovation."**

An Equal Opportunity/Affirmative Action Employer



Sperry/Salt Lake City,  
Communication  
Systems Division

# The ultimate work environment

Living and working at Sperry/Salt Lake City enables you to pursue almost every conceivable professional, recreational and cultural activity. Indeed, living in the heart of the majestic Rocky Mountains, on the edge of the expansive western deserts, provides an unparalleled satisfying lifestyle.

If you are a U.S. citizen and have a BS, MS or PhD degree or experience in any of the following areas an immediate opportunity may be waiting for you.

## Communications

- Wideband air/land data link systems
- Spread Spectrum, low probability of intercept
- Digital signal processing, modulation and coding

## Telecommunications

- Mobile tactical satellite terminals
- LAN voice data
- Communication systems integration
- Data/voice switching systems

## Electronic Warfare

- Spread Spectrum ESM/ECCM/ECM
- Signal detection and estimation
- Optical processing
- Antijam systems

## Software Engineering

- Communication software
- Scientific, real time programming
- DEC 11/44, VAX 11/780, VMS, FORTRAN, ADA


## Advanced Technology

- Signal processing, artificial intelligence
- GaAs devices
- Heterojunction device physics
- Network analysis
- Signal detection theory
- Covert transmissions

For consideration, send your resumé to:
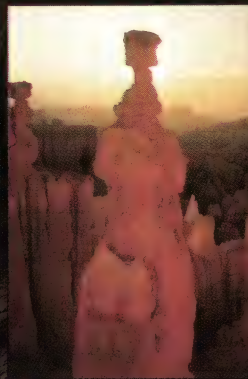
### Sperry


John E. Baird  
Employment Dept., Bldg. E  
640 North Sperry Way  
Salt Lake City, Utah 84116



Equal Opportunity Employer, m/f

© Sperry  
Corporation 1986



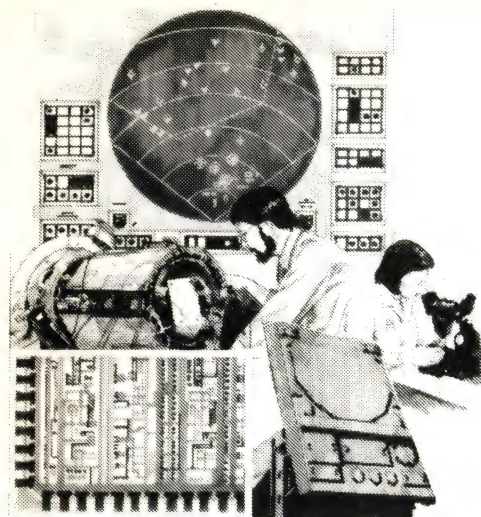

## Raytheon's Bedford Laboratories

# Every Project Reflects Today's State of the Art . . . And Defines Tomorrow's.

Reflection as a starting point. Followed by the definition of tomorrow's technological potential. Successful implementation of this process is the catalyst to the Bedford Laboratories of Fortune-100 Raytheon's Missile Systems Division's accelerating achievements in the research, design and development of highly sophisticated air defense systems.

Just a few of our new, on-going and expanding programs include PATRIOT, AMRAAM, next-generation HAWK, Sidewinder, a new vertical launch Sparrow, and Maverick. All reflect our uncompromised commitment to maintaining our preeminent position through technological synergy. We know what we've done. We know what we can do. And we have the confidence of our ability to meet the many challenges we continue to set for ourselves.

## Radar Systems Laboratory

### Advanced Radar Systems

- Perform conceptual design and analysis of advanced ground-based radars
- Generate performance requirements, implement trade-offs, and engage in proposal preparation

### Receiver/Signal Processing

- Design and test of analog/digital electrical circuits
- Task range from analog video circuits to microprocessor hardware/software
- Involvement with CAD/CAT

### Antenna Design and Development

- Design and development of wideband airborne antenna systems
- Antenna types include phased array and lens
- Familiarity with radar techniques for search, acquisition and track

## Missile Guidance Laboratory

### Microwave Circuit Design

- Responsible for active circuits design, focusing on amplifiers and oscillators for L-Band and Ka-Band frequency range
- Familiarity with microstrip, stripline, waveguide and microwave test equipment

### Missile Guidance Circuits

- Development of integrated circuit computer models as used in analog low frequency devices
- Familiarity with analog/digital circuits as used by servo control and low frequency electronics

## Digital Systems Laboratory

### Advanced Digital Computer Architectures

- Design bite capability and define diagnostic hardware procedures
- Use of CAE tools to design and test
- Complex circuit design and prototype testing

### Digital Pipeline Processors

- Lead implementation for design of MSI, LSI, VHSIC, gate array devices
- Interface with Mechanical and Software Laboratories for breadboard testing to production

### ATE Digital Test Development

- Subsystems functional test with Teradyne L200 automatic test station
- Familiar with LASAR and test software
- Support digital modules

## Systems Design Laboratory

### Radar/Surveillance Analysis

- Develop logic and algorithms for search, detection and track processing for surveillance operations against targets in clear, clutter and ECM environments

### Guidance and Control Analysis

- Perform analysis and simulation of missile flight control systems, seeker inertial stabilization systems, and guidance algorithms

### Systems Software Requirements

- Define software logic and algorithms and system architecture
- Development of test plans
- Support of system integration, test, and evaluation

## Mechanical Engineering Laboratory—CAD

### Electrical Checking

- Responsible for checking documents generated by the CADDs 4X system
- Qualifications include 5+ years experience in PC checking and/or design and an understanding of ANSI Y14.5M 1982, DoD-D-1000, DoD-STD-100 and MIL-STD-275E
- Experience should also include: Continuity using Schematics, Sizing Components, Automatic Insertion, Electrical Assemblies, Interconnecting Diagrams, Single and Two-Sided PWB's, Multi-Layer Boards, Net Lists, Stripline, Hybrids, Substrates, Ceramic Cards, Cables and Harnesses, and Flex Circuits

### PC Design

- These positions require 5+ years experience designing PWB's and working knowledge of MIL-STD-275E
- Experience in/or familiarity with several of the following areas is highly desirable: CADDs 4X System, Multi-Layer Boards, Digitizing Formats, Stripline and Microstrip Design, Analog and Digital Logic, High Density Designs, ECL, Board Fabrication, Automatic Component Insertion, Hybrid and Flex Circuits, and IPC Standards

### CAD Design/Checking

- Electro-mechanical packaging design in model mode for Manufacturing CAM interface on 2nd and 3rd shifts
- 2-5 plus years related experience, including 2 years on Computervision CADDs 4X System; knowledge of hybrid and printed and flex wiring desired

Raytheon's Bedford Laboratories, a million-square-foot facility, is located in one of suburban Boston's most desirable areas—convenient to the city's incomparable educational, cultural and entertainment resources and the innumerable four season, recreational activities of nearby New Hampshire, Maine, Vermont and Cape Cod.

A BS degree in an engineering discipline is necessary. Both experienced engineers and recent college graduates will be considered. Raytheon offers excellent salaries and many company-paid benefits as well as Stock Ownership and Savings and Investment Plans and liberal relocation assistance. Please send resume with salary requirements to:

**Stephen E. King, Raytheon Company, Missile Systems Division, Hartwell Road, Bedford, MA 01730. An Equal Opportunity Employer. U.S. Citizenship required.**

## Quality Starts with Fundamentals

# Raytheon



# METROLOGY SUPERINTENDENT

**Primary Standards Laboratory-  
PMEL Manager**

## INTERNATIONAL OPPORTUNITY


A major internationally based aerospace contractor is establishing a Primary Standards PMEL facility in the Middle East. The ideal candidate will be someone with recent experience in a management role in a TYPE I laboratory and with the capability to technically supervise metrologists and Type I and II technicians. The lab will service Precision Measurement Equipment for a major peaceful Middle Eastern country's civilian and military aircraft. Prior USAF experience is desirable.

### TYPE I TECHNICIAN POSITIONS ALSO AVAILABLE.

In addition to an excellent salary, you will receive tax free income, free housing, insurance and R&R travel to the U.S. A one year contract is offered, with an extendable option.

CALL OR SEND RESUME IMMEDIATELY TO:

**STEVE BOMBOLA**  
714/752-6228

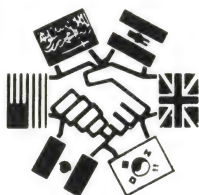

**INTERNATIONAL STAFFING  
CONSULTANTS, INC.**

19762 MacArthur Blvd.  
Irvine, CA 92715

### NATIONAL OPENINGS TECHNICAL WRITERS

MGR TECH PUBS .....	to 50K
PUBS SUPERVISOR .....	to 48K
SUPV PARTS LISTING .....	to 40K
ENGING WRITER .....	to 44K

TEST PROCEDURES/PROPOSALS/IPB MANUALS (theory of operation, instal) SYSTEM SOFTWARE/LOGISTIC SUPPORT

SYSTEMS TO BE DOCUMENTED INCLUDE:  
radar/combat/avionics/elec warfare/telecommunications/  
signal processing/sonar/simulation/infra red

Please call Michael Dunn (collect) at 609-424-8600  
or send resume to:



**Judge Inc.**  
Suite G37  
1930 E. Route 70  
Cherry Hill, NJ 08003

All positions are direct career opportunities-all fees  
and interviewing expenses paid by client companies.

**If You're Looking  
For a Job,  
You've Come to  
The Right Place.**


**EDN CAREER  
OPPORTUNITIES**

**EDN**



# Intel...

## Changing Technological Horizons Again

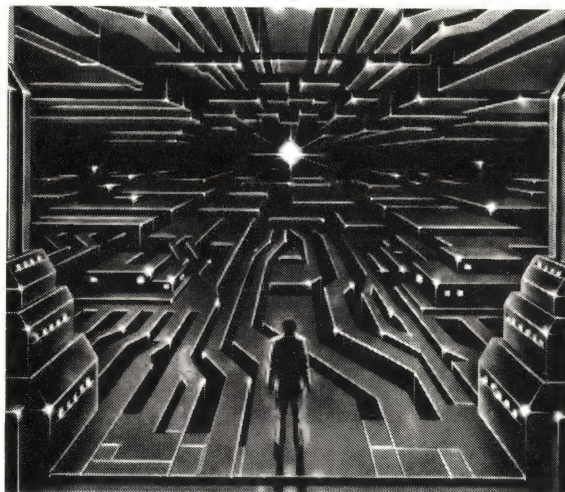

### Design & CAD Engineering Opportunities In Arizona & California!

The ability to adapt quickly to rapid changes in both market and technology is the mark of an Intel professional. As a result, we have contributed to a number of "firsts" in the microelectronic industry. Now, we're setting industry standards in our Telecom, Automotive and Military Groups, and the increased activity has generated immediate openings for the following professionals:

#### Design Engineers

Qualified candidates must have 2+ years experience in one or more of the following areas: VLSI logic/circuit design, CMOS, controller design, computer architectures or analog components. Heavy interaction with customers to define chip function in addition to intracompany interfaces with Fabs, Product Engineering and Marketing. BSEE required, MSEE preferred.

#### CAD Software Engineers

Positions require 2<sup>+</sup> years experience using "C", PASCAL or MAINSAIL languages in the areas of: graphics CAD tool development, IC design, compilers, silicon performance verification, silicon compilation and layout generation. MSCS/EE required, PhD preferred.

For immediate consideration, please call collect or send your resume to the location of your choice. Arizona: Mike Gore, Intel Corporation, 5000 W. Chandler Blvd., Chandler, AZ 85226, (602) 961-5794. California: Becky Canary, Intel Corporation, P.O. Box 2546, Santa Clara, CA 95051, (408) 496-8186. An Equal Opportunity Employer M/F/H.

# intel<sup>®</sup>



# IEEE-488



## GPIB ↔ PC

### Hardware Flexibility

- Low cost for instrument control
  - 300K bytes per second
  - \$395 complete with software
- High performance data links
  - Maximum speed of GPIB
  - On-board buffering

### Software


- Software specially tested for the IBM PC and compatibles
- Over \$1,000,000 in software development
- Easy to use, yet handles any GPIB application
- Works with Lotus 1-2-3
- UNIX, DOS and over 12 languages

### Applications Support

- Applications Library with sample programs & TIPS for all major instruments
- Full staff of Applications Engineers dedicated to support your specific needs
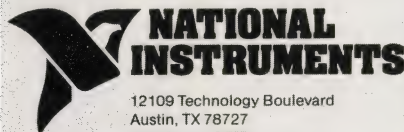
### Other IEEE-488 Products

- Interfaces & Software for
  - Multibus VMEbus
  - DEC Q-bus & UNIBUS
  - STD & S-100 bus
- General GPIB Products
  - GPIB Bus Testers
  - GPIB Bus Extenders
  - Stand-Alone Controllers



12109 Technology Boulevard  
Austin, TX 78727  
1 (800) 531-GPIB  
In Texas (800) IEEE-488  
Telex: 756737 NAT INST AUS

CIRCLE NO 93

## BUSINESS/CORPORATE STAFF

**F Warren Dickson**  
Vice President/Publisher  
Newton, MA 02158  
(617) 964-3030  
Telex 940573  
Diann Siegel, Assistant

**Peter D Coley**  
National Sales Manager  
Newton, MA 02158  
(617) 964-3030  
Stacey Vorias, Assistant

**NEW ENGLAND**  
Bob Sommer, Regional Manager  
275 Washington St  
Newton, MA 02158  
(617) 964-3030

**STAMFORD 06904**  
George Isbell, Regional Manager  
8 Stamford Forum, Box 10277  
(203) 328-2580

**NEW YORK CITY 10016**  
Daniel J Rowland, Regional Manager  
Chris Platt, Regional Manager  
475 Park Avenue South  
(212) 576-8014  
(212) 576-8017

**PHILADELPHIA AREA**  
Steve Farkas, Regional Manager  
999 Old Eagle School Rd  
Wayne, PA 19087  
(215) 293-1212

**CHICAGO AREA**  
Clayton Ryder, Regional Manager  
Randolph D King, Regional Manager  
Cahners Plaza  
1350 E Touhy Ave, Box 5080  
Des Plaines, IL 60018  
(312) 635-8800

**DENVER 80206**  
John Huff, Regional Manager  
Joseph A Vitiello, Regional Manager  
270 St Paul St  
(303) 388-4511

**DALLAS 75234**  
Don Ward, Regional Manager  
13740 Midway, Suite 515  
(214) 980-0318

**SAN JOSE 95128**  
Walt Patstone, Regional Manager  
Bill Klanke, Regional Manager  
Philip J Branon, Regional Manager  
Mark Holdreith, Regional Manager  
3031 Tisch Way, Suite 100  
(408) 243-8838

**LOS ANGELES 90064**  
Charles J Stillman, Jr  
Regional Manager  
12233 W Olympic Blvd  
(213) 826-5818

**ORANGE COUNTY/  
SAN DIEGO 92715**  
Ed Schrader, Regional Manager  
Jim McErlean, Regional Manager  
18818 Teller Ave, Suite 170  
Irvine, CA  
(714) 851-9422

**PORTLAND, OREGON 97221**  
Pat Dakin, Regional Manager  
Walt Patstone, Regional Manager  
1750 SW Skyline Blvd, Box 6  
(503) 297-3382

**UNITED KINGDOM, THE NETHERLANDS,  
SCANDINAVIA**  
Jan Dawson, Regional Manager  
39A Bowling Green Lane  
London EC1R/0BJ UK  
1-278-2152  
Telex: 28339

**BELGIUM/FRANCE**  
Robert Broekman  
American Publishers Representatives  
4 Rue Robert de Flers  
75015 Paris, France  
33-1-46099595  
Telex: 270560

**GERMANY/SWITZERLAND**  
Wolfgang Richter  
Sudring 53  
7240 Horb/Neckar  
West Germany  
49-7451-7828

**AUSTRIA**  
Igal Elan  
Elan Marketing Group  
Neutor g 2, Box 84  
1013 Vienna, Austria  
43222-663012, 638461

**SOUTHERN EUROPE**  
Igal Elan  
Elan Marketing Group  
13 Haifa St, Box 33439  
Tel-Aviv, Israel  
Tel: 25 29 67

**FAR EAST**  
Ed Schrader, Director of Sales  
18818 Teller Ave, Suite 170  
Irvine, CA 92715  
(714) 851-9422; Telex: 940573

**TOKYO 107**  
Kaoru Hara  
Dynaco International Inc  
7-2-8 Minamiaoyama  
Minato-Ku,  
Tokyo 107, Japan  
Tel: 011-81-3-409-4569  
Fax: 011-81-3-499-4554

**TAIWAN**  
Owen Wang, Gen Mgr  
Ace Marketing Inc  
Box 26-578  
Taipei, Taiwan  
Republic of China  
86-2-703-4272  
Telex: (785) 14142

**KOREA**  
Korea Media Inc  
101-10, 2-KA, Pil-Dong, Chung-Gu  
Seoul, Korea  
Tel: 011-82-2-273-7011  
Telex: K26249

**PRODUCT MART**  
Joanne Dorian, Manager  
475 Park Avenue South  
New York, NY 10016  
(212) 576-8015

**CAREER OPPORTUNITIES/  
CAREER NEWS**  
Roberta Renard  
National Sales Manager  
475 Park Avenue South  
New York, NY 10016  
(212) 576-8048

Janet O Penn  
Eastern Sales Manager  
475 Park Avenue South  
New York, NY 10016  
(212) 576-8049

Dan Brink  
Western Sales Manager  
2041 Business Center Dr, Suite 109  
Irvine, CA 92715  
(714) 851-9422

Maria Cubas  
Production Assistant  
(212) 576-8045

**Cahners Magazine Division**  
William Platt, President  
Terry McDermott, Executive Vice President  
Tom Dellamaria, VP/Production & Manufacturing

**Circulation**  
Denver, CO: (303) 388-4511  
Sherri Gronli, Group Manager  
Eric Schmierer, Manager

Reprints of EDN articles are available on a custom printing basis at reasonable prices in quantities of 500 or more. For an exact quote, contact Ernie Kummer, Cahners Reprint Service, Cahners Plaza, 1350 E Touhy Ave, Box 5080, Des Plaines, IL 60018. Phone (312) 635-8800.




# ADVERTISERS INDEX

ACDC Electronics	150	Dialight Corp	227	Interface Products Inc	42
Adaptec Inc	189	Digelec Inc	345	International Microtronic Corp	345
Advance Power Supplies Inc*	129	Digitec Corp	302	International Nickel*	254
Advanced Micro Devices	52-53	Disc Instruments Inc	280, 308	International Rectifier	56
Advanced Micro Systems Inc	345	Displex Inc	322	Interplex Electronics/ Global Specialties	261
Advanced Power Corp	311	Douglas Corp	318	Interplex Technologies	356
AIE Magnetics	343	DY-4 Systems Inc	346	Introl Corp	348
Airpax Corp	339	E G & G Wakefield Engineering Components Div	313	ITT Schadow Inc	348
American Automation	96	Eldre Components Inc	348	ITT Zuerich	318
American Research and Engineering	86	Electrochemical Industries	340	Iwatsu Instruments Inc	260
AMF Inc-Potter & Brumfield	281	Electronic Designs Inc	274-275	Japan Aviation Electronics Industry Ltd	320
AMP Inc	232-233	Electronic Measurements Inc	288	John Fluke Manufacturing Co Inc	6, 101, 169
Amperex Electronic Corp	346	Electronic Solutions	106	KEC Electronics Inc	126
Amphenol Products, An Allied Co	196-197	Electroswitch Corp	295	Kepeco Inc	255-258
Amtelco	350	Elfab Corp	310	KIK	324-325
Analog and Digital Peripherals Inc	349	Elographics Inc	265	Kineticon Systems	346
Anritsu Corp	355	Endicott Research Group Inc	252	Language Resources Inc	277
Apex Microtechnology Corp	31	Epoxy Technology Inc	88	Laser Video Inc	350
Applied Microsystems Inc	90-91	ETA Power Systems	341	Lemo USA Inc	333
Arnold Magnetics Corp	307	E-TA Circuit Breakers	273	Logical Devices Inc	354
Astec USA	366	Fairchild Digital	94-95	Logical Systems Corp	348
AT&T Technologies	119-121	Feller AG	236	Lundy Electronics and Systems Inc	363
Autodesk	67	Force Computers Inc	28-29	3M Commercial Chemicals Div	122-123
Avocet Systems Inc	319	Forth Inc	334	Mactac Industrial Products	225
AVX Corp	113	Fujitsu American Inc/ Storage Products	298-299	Matra Harris Semiconductor	290
BBC Brown Boveri	142	GE/Intersil Systems	C2	McGill Mfg Co Inc, Electrical Div	316
Behlman Engineering Corp	335	GE Plastics	58	Medinova Corp	346
Bertan Associates Inc	296	General Instrument Corp/ Lamp Div	247	Memory Protection Devices Inc	335
Brooktree Corp	14-15	Generic Software	346	Methode Electronics Inc	345
Burr-Brown Corp	231	Gentron Corp	269	Micom	332
Cahners Exposition Group	194-195	Germanium Power Supplies Devices Corp	172	Micro-Craft	347
Calay Systems	104-105	Glassman High Voltage Inc	329	MicroSim Corp	89
California Instruments	323	Grayhill Inc	151	Mikul	345
Calmos Systems Inc	34	Gresham Powerdyne**	55	Minelco, A Tally Industries Co	270
Canadian Thermostats and Control Devices Ltd	347	Hamilton Avnet Electronics	300	Mini-Circuits Laboratories	24-25, 243, 380
Canon USA Inc	264	Hamilton Standard	191	Monolithic Memories Inc	16-17
Carroll Touch Inc	30	Harris Semiconductor	229	Motion Control Devices Inc	314
Case Technology	174	Hitachi America Ltd*	75-78	MuShield/Bomco	364
Casio Inc	357	Hoffman Engineering Co	251	National Instruments	376
Cermetek Microelectronics Inc	349	Honeywell Digital Products Center	321	NCR Power Systems*	152
Cherry Semiconductor	279	Hughes Connecting Devices	111	New Micro	80
Chomerics Inc	239	Hunting Highvolt Ltd	301	Nicolet Computer Graphics	352
Coilcraft	361	Huntron Instruments Inc	347	Nicolet Oscilloscope Div	23
Compcontrol	289	Hurricane Electronics Lab	349	Nohan Corp	350
Compumotor Corp	345	Hybrid Systems Corp	117	North Hills Electronics Inc	322
Computer Parts Mart	350	Hypertronics Corp	266	Octagon Systems Corp	348
Computer Products Inc, Compower Div	326	I-Bus Systems Inc	378	Oki Semiconductor	50
Computer Products Inc, Power Products Div	141	IC Master*	234A	Oliver Advanced Engineering Inc	305
Converter Concepts Inc	330	IC Sensors	346	Olation Inc	349
Cooper Group*	234C	IEE	284	Omron Electronics Inc*	108, 109
Covercraft Co Inc	349	Ikegami Electronics	312	Onan Power Electronics	327, 329, 331
Crystek Microelectronics	350	Industrial Devices Inc	336	One/D	38
CTS Corp	303	Industrial Programming	285	Optimal Technology Inc	349
Cybernetic Microsystems	118, 350	Inlab Inc	338	OrCAD Systems Corp	347
DATA Inc	286	Inland Motor Power Technology Group	144	Orion Instrument	297
Dallas Semiconductor	238	Inmos Corp	10-11, 294	Otto Controls	321
Data Delay Devices Inc	327	Integrated Device Technology	61	P & C Shiten Enterprise Co Ltd	349
Data I/O Corp	C4	Integrated Systems Products	348	Panasonic Industrial Co	282-283
Dense Pac Microsystems Inc	234	Intel Corp	198-199	Parlex Corp	87



# The PC Bus:

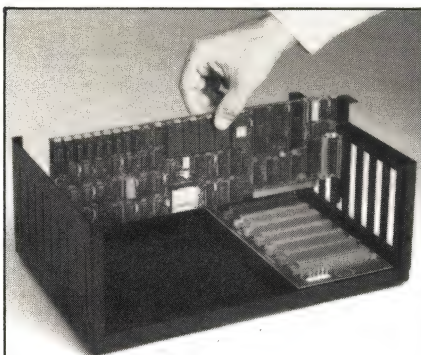
## Cost-Effective, Board-Level Solution To System Integration



Get your dedicated system to market *months* sooner with the PC Bus. Full board-level implementation by I-Bus lets you plug together system components from hundreds of PC Bus board manufacturers, and directly execute software developed on and for the IBM® PC.

I-Bus has board-level CPU's with 8088 or 80188 processors, full disk or diskless operation and up to 160K of EPROM, 256K of RAM on board. We have the most complete line of system packaging for the PC Bus, too.

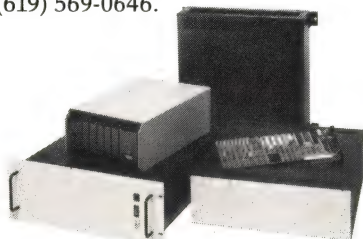Start cutting your schedule today—give us a call today at (800) 382-4229. In California, call (619) 569-0646.



# I-BUS

## SYSTEMS

9235 Chesapeake Drive  
San Diego, CA 92123

CIRCLE NO 303

## ADVERTISERS INDEX

Pärmag Corp	40	Teledyne Semiconductor	85, 127
Philips Elcoma Div**	36-37, 76-77	Teledyne Solid State Products	348
Philips Test & Measuring Instruments Inc**	125	Telesis	351
Pico Electronics Inc	346	Texas Instruments Inc	211-218
Pioneer Magnetics	145	Thaler Corp	66
Plessey Microsystems	293	Thomson Semiconductors	78
Polytronix Inc	171	TL Industries Inc	345
Powerex Inc	12-13	Todd Products	39
Power General	309	Tokin Corp	253
Power-One Inc	41	Toko America Inc	358
Power-Sonic Corp	358	Torwico Electronics	347
Powertec Inc*	66A-D	Toshiba America Inc/ Semiconductor Div	249
Precision Monolithics Inc	173	Toshiba Corp	344
Prem Magnetics Inc	34	Triplett Corp	139
Preston Scientific	347	TRW/LSI Products Div	21
Pro-Log Corp	4	Uddeholm Corp	42
Qualidyne Systems Inc	116	Unimax Switch Corp	304
Quartic Systems Inc	314	Uppermost Electronic Industries Co Ltd	171
Quelo	350	Ven-Tel	26-27
Rantec Power Systems	128	Versatec, A Xerox Co	73
RCA Solid State Div	43, 44-45, 46-47	Vicor Corp*	115
Reliability Inc	317	Video Monitors Inc	26
Rifa Inc/Capacitors	262-263	Wavetek San Diego Inc	3
Rifa Inc/Power Products	250	Wells Electronics Inc	271
RO Associates Inc	149	Whitesmiths Ltd	328
Robinson-Halpern	347	Winchester Electronics	353
Robinson-Nugent Inc	357	Wintek Corp	337, 346
Rockwell International	276	Zax Corp	210
Roederstein Electronics Inc	348	Zitel Corp	63
Rogers Corp	349		
Rohde and Schwarz**	75		
Saft America Inc*	234D		
Howard W Sams & Co	287		
Samtec Inc	315		
SBE Inc	68		
SGS Semiconductor Corp*	167		
Shogyo International	38		
Siemens Corp*	36-37, 125		
Siggraph	237		
Signetics	92-93		
Silicon Systems Inc	64, 65		
Siliconix Inc	48-49		
Software Publishing Co	268		
Sohio Engineered Materials Co	170		
Sola Electric	148		
Solartron Instruments	8		
Solitron Devices Inc	272		
Sonnenschein Batteries Inc	365		
Southern Computer Corp	349		
Spectrol Electronics Corp	306		
Spectrum Software	245		
Sprague Electric Co	35, 83		
Stag Microsystems Inc	18		
Stockwell Rubber Co Inc	350		
Summation Inc*	54-55		
Summit Electronics	143		
Sunrise Electronics	342		
Switching Power Inc	278		
Symbolics Inc	165		
Sysoft	270		
Tadiran Electronic Industries Inc	C3		
TDK Corp of America	171, 235		
Technipower Div/Penril Corp	331		
Technitrol Inc	362		
Tektronix Inc	32-33, 102-103, 163, 192-193, 240		

### Recruitment Advertising

Intel	375
ISC	374
Judge Inc	374
Micron	371
Raytheon	373
Sperry	372

\* Advertiser in US edition

\*\* Advertiser in International edition

This index is provided as an additional service. The publisher does not assume any liability for errors or omissions.



# LOOKING AHEAD

EDITED BY GEORGE STUBBS

## Monolithic units swell data-converter market

The average annual growth of the data-converter market through the remainder of the decade will be 17.7%, reports the market-research company Venture Development Corp (Natick, MA). The dollar value of the total converter market will be \$1.13 billion in 1990, more than double 1985's \$501.6 million. The force behind this growth, says VDC, will be the increasing popularity of monolithic A/D and D/A converters, whose combined sales will grow at an annual rate of 20%.

Ten years ago, the monolithic data converter was virtually nonexistent, and as recently as four years ago, the highest resolution of these devices was 12 bits. Today, the devices furnish resolutions of 16 bits and higher. Furthermore, compared with hybrid and modular converters, the monolithic parts offer a smaller size with more functions in the same board space, lower costs due to higher production volumes, lower power dissipation and heat generation, and high reliability.

Though the demand for hybrid and modular converters will not vanish, these parts will increasingly serve more specialized applications.

Advances in process technology are giving the monolithic devices a big boost. CMOS converters achieve greater chip densities, and, with the aid of VLSI technology, bipolar converters can now handle higher conversion speeds. In addition, BiMOS promises to combine the virtues of bipolar and CMOS technology and have a significant effect upon the market within two or three years.

Power dissipation is important in most data-converter applications, says VDC, and CMOS will consequently be the most popular process technology for A/D and D/A converters through 1990. CMOS parts will be limited only by their slower conversion speed and higher cost. Although high-speed applications may use significant numbers of CMOS flash converters within a few years, CMOS devices will most likely have their greatest impact in such slow- and medium-speed applications as industrial-control sys-

tems, medical analyzers, data-acquisition systems, and automatic test equipment.


## Portable data recorders: programmability the key

For remote data recording, pen and paper have given way to the portable data recorder (PDR), and now the basic PDR is yielding to the programmable PDR. Vendors shipped 145,000 programmable PDRs in 1984 vs 25,000 nonprogrammable units; shipment totals in 1989 will be 453,000 (programmable) vs 65,000 (nonprogrammable), according to the market-research company Frost & Sullivan Inc (New York, NY). The dollar value of these market segments in 1989 will be \$465.9 million for programmable PDRs and \$43.8 million for the nonprogrammable recorders.

The ubiquitous bar code, so popular in retailing and other industries, has rendered the PDR a necessity in many types of data-collection centers. Further, wireless communications networks have facilitated the transmission of collected data from the PDR to a central site. Programmable PDRs can provide a number of services, including 2-way communication, faster error checking, multiple functions, compatibility with a variety of peripherals and hosts, and the ability to discriminate automatically among a variety of codes.


Frost & Sullivan predicts that competition in the market will be stiff. Approximately 25 manufacturers now vie for market share, and the number is growing. Currently, Telxon and MSI account for 53.7% of the market's dollar value. Norand is ranked third (13.2%) and Motorola fourth (11.7%). Vendors must decide whether they are going to emphasize programmable or nonprogrammable units, and they face some competition from manufacturers of portable computers as well.
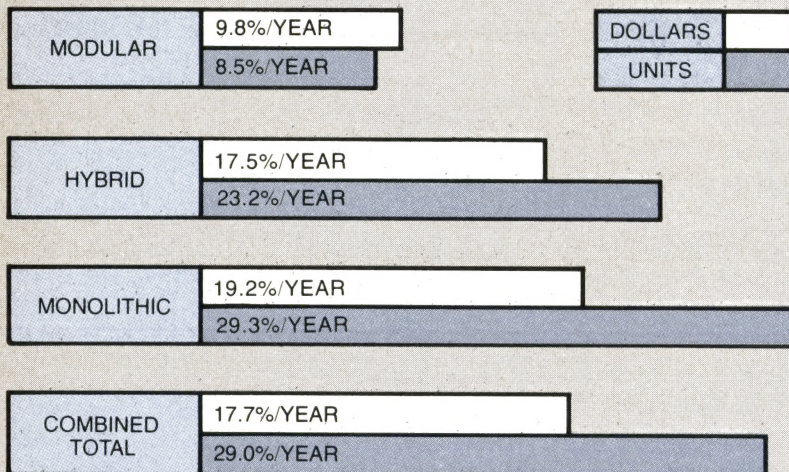
### AVERAGE ANNUAL GROWTH OF A/D-, D/A-CONVERTER SHIPMENTS (1985-1990)



(SOURCE: VENTURE DEVELOPMENT CORP)



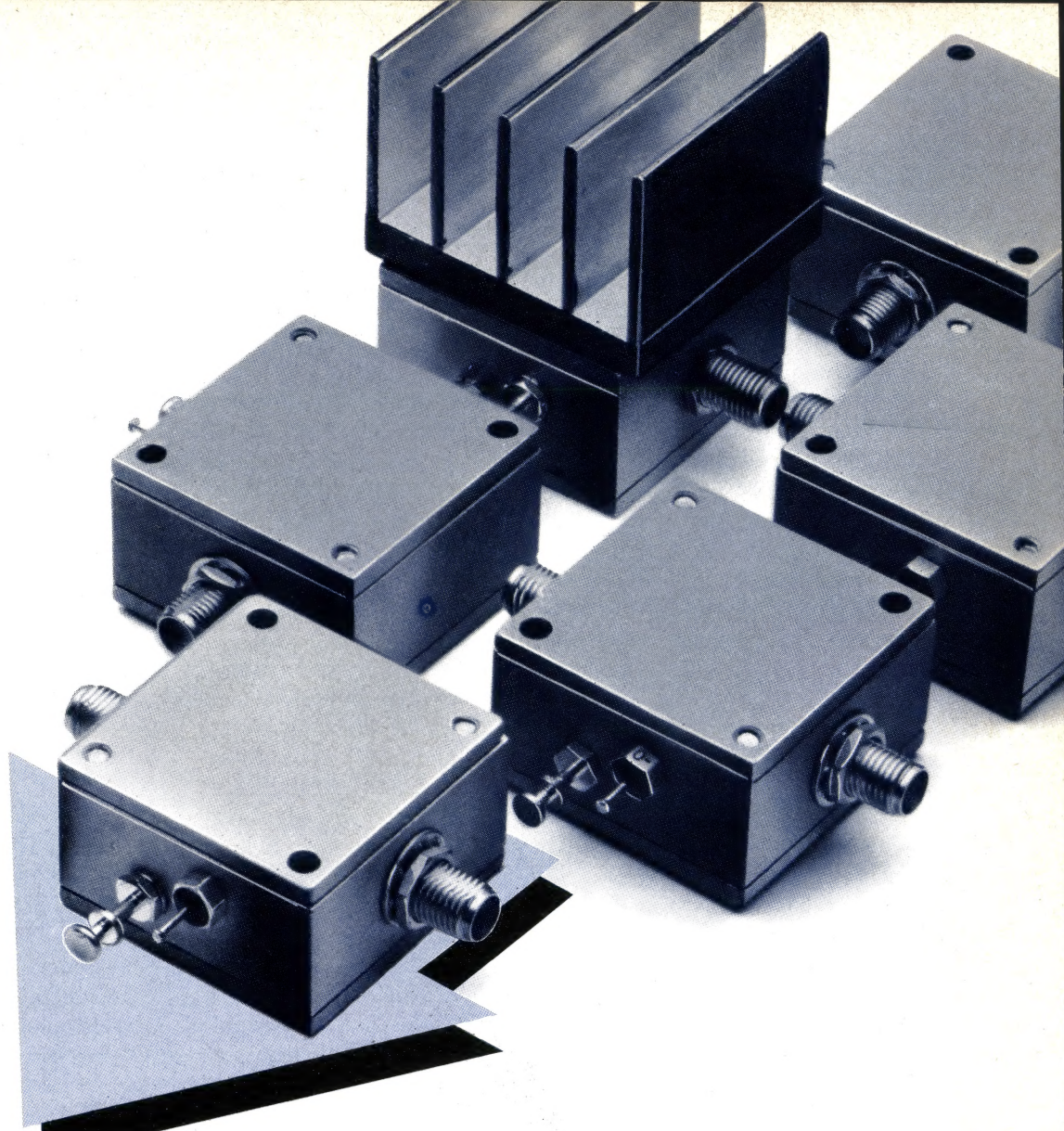

# Amplifier Arsenal

50KHz to 2000MHz, 100mW output Gain Controlled From **\$69.95**

Our ZFL-2000 miniature wideband amplifier hit a bulls-eye when we introduced it last year. Now we've added more models to offer you a competitive edge in the continuing battle for systems improvement.

The ZFL-2000, flat from 10 to 2000MHz, delivers +17 dBm output and is still priced at only \$179.

Need more output? Our ZFL-1000H, flat from 10 to 1000MHz, delivers +20 dBm output.

Variable gain important? Our ZFL-1000G, flat from 10 to 1000MHz, delivers +3 dBm output with 30 dB gain control while maintaining constant input/output impedance.

Searching for a high-quality, low-cost amplifier? Our ZFL-500 flat from 50KHz to 500MHz, delivers 10 dBm output for the unbelievably low price of only \$69.

One week delivery... one year guarantee.

Gain the competitive edge... specify Mini-Circuits RF/IF signal-processing components.

## SPECIFICATIONS

Model No.	ZFL-500	ZFL-1000G	ZFL-2000	ZFL-1000H
Freq (MHz)	0.05-500	10-1000	10-2000	10-1000
Gain (dB), Min.	20	17	20	28
Gain Flatness (dB) Max.	±1.0	±1.5	±1.5	±1.0
Max. Power (dBm)				
(1dB compression)	+10	+3	+17*	+20
NF (dB) typ.	5.3	12.0	7.0	5.0
3rd order				
Intercept pt (dBm)	+18	+13	+25	+33
Current at 15V dc	80mA	90mA	100mA	150mA
Price \$	69.95	199	179	219
qty.	1-24	1-9	1-9	1-9

For complete specs on these and our 1- and 2-W models refer to 1985-86 Gold Book or Microwaves directory.  
\*+15 dBm below 1000MHz

finding new ways...  
setting higher standards

**Mini-Circuits**




A Division of Scientific Components Corporation  
World's largest manufacturer of Double Balanced Mixers  
P.O. Box 166, Brooklyn, New York 11235 (718) 934-4500  
Domestic and International Telex 125460 International Telex 620156

CIRCLE NO 302

C101 REV. A



# Here's to the memory

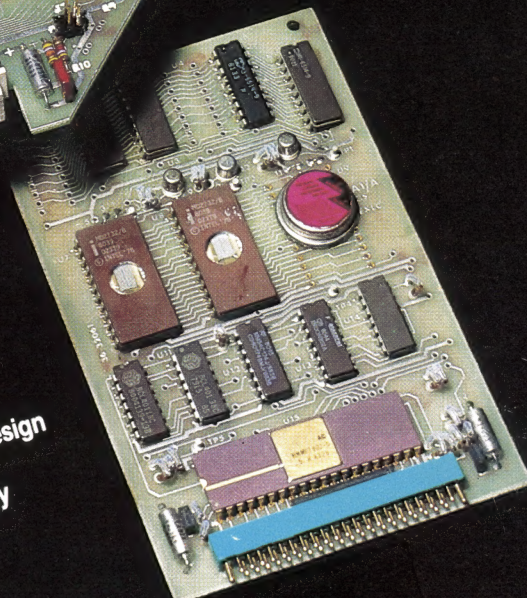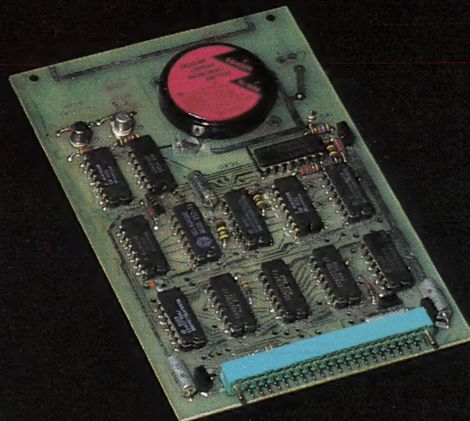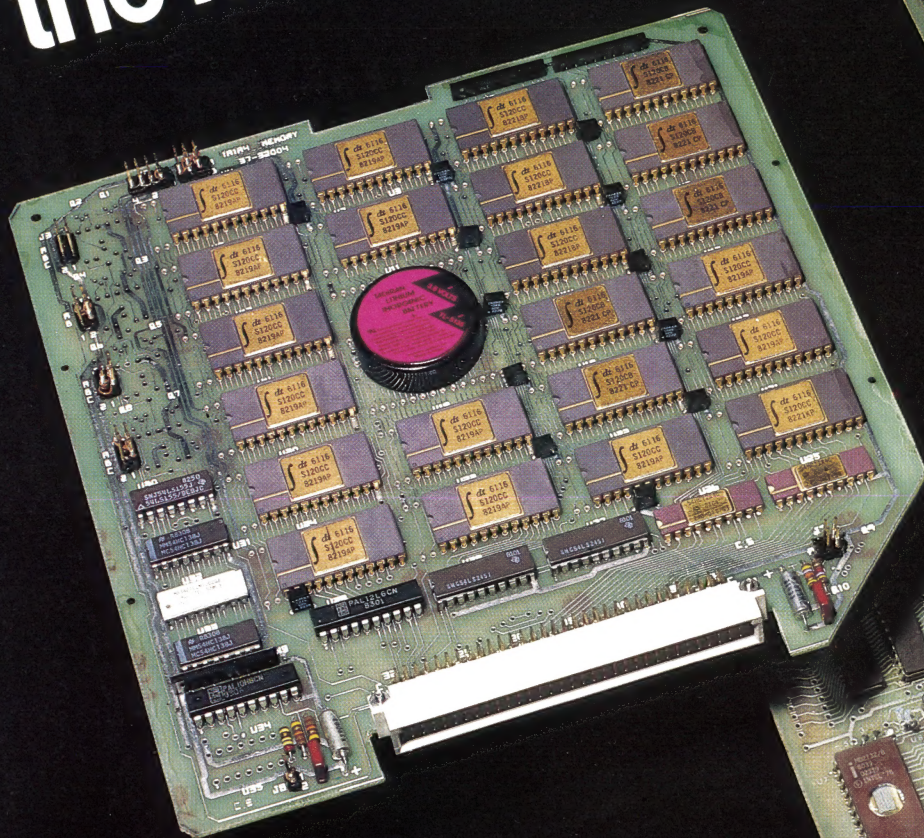

## Tadiran™ Lithium Wafer Cells

- Ideal in memory back-up applications
- Compact assembly for streamlined PCB design


All the benefits of Tadiran lithium technology

**TADIRAN**  
Electronic Industries, Inc.

40 Seaview Blvd., Port Washington, NY 11050, U.S.A. Tel. 516-621-4980  
800-367-6859  
Lakeland Plaza Professional Bldg., Suite 263 Woodland Hills, CA 91367, U.S.A.  
Telephone: 214-221-7523  
6312 Variel Ave., Suite 203, Woodland Hills, CA 91367, U.S.A.  
Telephone: 818-884-3884, 800-882-3882 TLX W.U. 705384  
3000 Dundee Rd. Suite 308, Northbrook, IL 60062, U.S.A.  
Telephone: 312-564-4960

CIRCLE NO 217



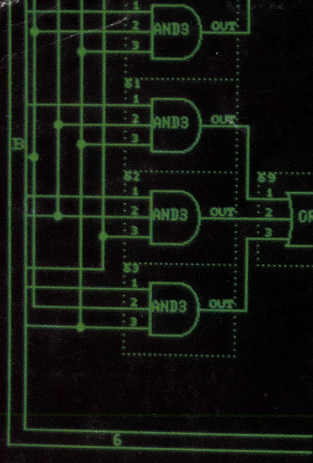

ABEL(tm) Version 1.13 - Doc  
12 to 4 multiplexer  
Equations for Module PLD01

Device IC1

Reduced Equations:

$$Y3 = (A3 \& !S1 \& !S2 \& S3)$$

$$Y2 = (A2 \& !S1 \& !S2 \& S3)$$

$$Y1 = (A1 \& !S1 \& !S2 \& S3)$$

$$Y0 = (A0 \& !S1 \& !S2 \& S3)$$


C>\_

8:05

9:37

10:58

11:05

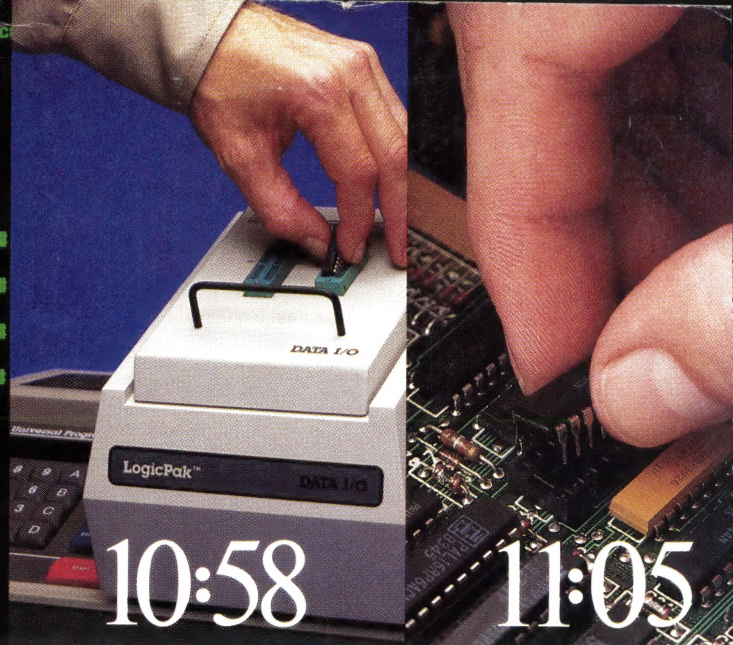

# CONCEPT TO SILICON IN 3 HOURS FLAT.

## ALL THE BENEFITS OF CUSTOM DESIGN WITHOUT THE WAIT.

Sometimes, the only way to optimize a design is by using custom parts. But some application-specific integrated circuits (ASICs), like gate arrays, can take weeks to develop.

Programmable Logic Devices (PLDs) may be the right solution for your application. They offer low risk and high design flexibility to reduce your development costs.

## LOGIC CONCEPT TO FINAL DEVICE RIGHT AT YOUR DESK.

Data I/O's Personal Silicon Foundry gives you all the tools you need to take logic from concept to programmed device in just hours. The Personal Silicon Foundry, based on an IBM® Personal Computer, automates time-consuming tasks such as design, logic reduction, test vector generation and verification. You can easily experiment to optimize your design and quickly test each iteration in an actual circuit.

## FOUR WAYS TO EXPRESS YOUR DESIGN.

With our FutureNet DASH™ schematic design package and ABEL™, the industry-standard logic



The Personal Silicon Foundry™

language, you can express your concept in any combination of schematics, truth tables, state diagrams or Boolean equations — whichever you prefer.

## CREATE A FULLY TESTABLE DEVICE IN MINUTES.

Because simulation is an integral part of the Personal Silicon Foundry, you can segment your logic circuit, develop test vectors and debug the design in one process. You can also automatically analyze design testability and generate device test vectors. The result: You easily produce a fully testable PLD.

**SUPPORTS PLDS OF YOUR CHOICE.** You have the flexibility to choose any PLD from virtually any manufacturer.

Select one of two Data I/O logic programmers to match your device requirements. Both give you full-functional testing and easy operation from the PC keyboard.

## AUTOMATICALLY DOCUMENTS THE ENTIRE PROCESS.

Throughout design, simulation, programming and testing, the Personal Silicon Foundry generates all necessary documentation. Your PLD is ready for the production line just hours after your concept is developed.

## CONFIGURE YOUR OWN PERSONAL SILICON FOUNDRY. ASK US HOW.

As the world leaders in PC-based CAE and PLD support tools, Data I/O and FutureNet\* can help you tailor your own Personal Silicon Foundry. Call us today, toll free **1-800-426-1045** and ask for your free guide to PLDs and the Personal Silicon Foundry.

Capturing the power of PLDs is that simple. And fast.

\*FutureNet is a Data I/O company.

YOUR GUIDE  
TO THE  
PERSONAL  
SILICON FOUNDRY

# DATA I/O

The Personal Silicon Foundry is distributed by Hamilton Avnet.  
IBM is a registered trademark of International Business Machines Corporation.

**DATA I/O Corporation** 10525 Willows Road N.E., P.O. Box 97046, Redmond, WA 98073-9746, U.S.A. (206) 881-6444/Telex 15-2167  
**FutureNet Corporation** 9310 Topanga Canyon Boulevard, Chatsworth, CA 91311-5728 (818) 700-0691/Telex 910-494-2681

**DATA I/O Europe** World Trade Center, Strawinskylaan 633, 1077 XX Amsterdam, The Netherlands (20) 622866/Telex 16616 DATIO NL

**DATA I/O Germany** Bahnhofstrasse 3, D-6453 Seligenstadt, Federal Republic of Germany (6182) 3088/Telex 4184962 DATA D

**DATA I/O Japan** Ginza Orient Building, 6F, 8-19-13, Ginza Chuo-ku, Tokyo 104, Japan (03) 574-0211/Telex 2522685 DATAIO J